


CHAPTER 1- INTRODUCTION OF ELECTRONIC DEVICES

-MRS RASIKA B. NAIK

POINTS TO BE COVERED IN TODAY'S CLASS


- DC Load Line analysis
- Common Base Configuration
- Input Output Characteristics of CB configuration
- Common Collector Configuration
- Input Output Characteristics of CC configuration
- Comparison of CE, CB and CC

COMMON BASE CONFIGURATION

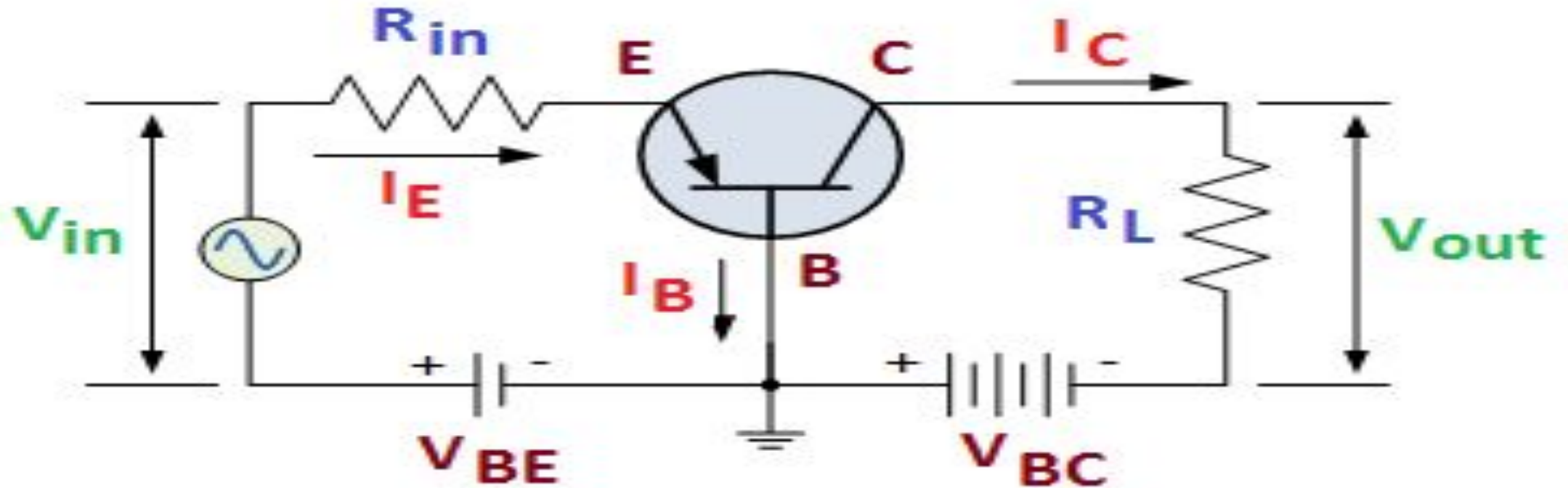


Common Base Configuration

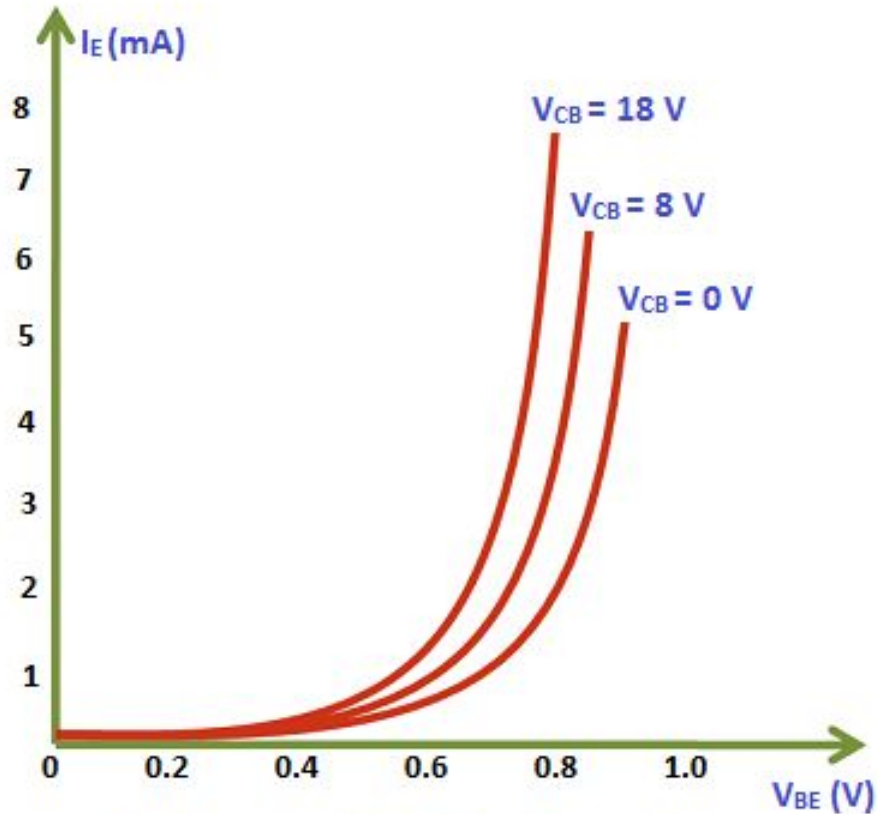
INPUT OUTPUT CHARACTERISTICS OF CB AMPLIFIER




I/p characteristics CB configuration

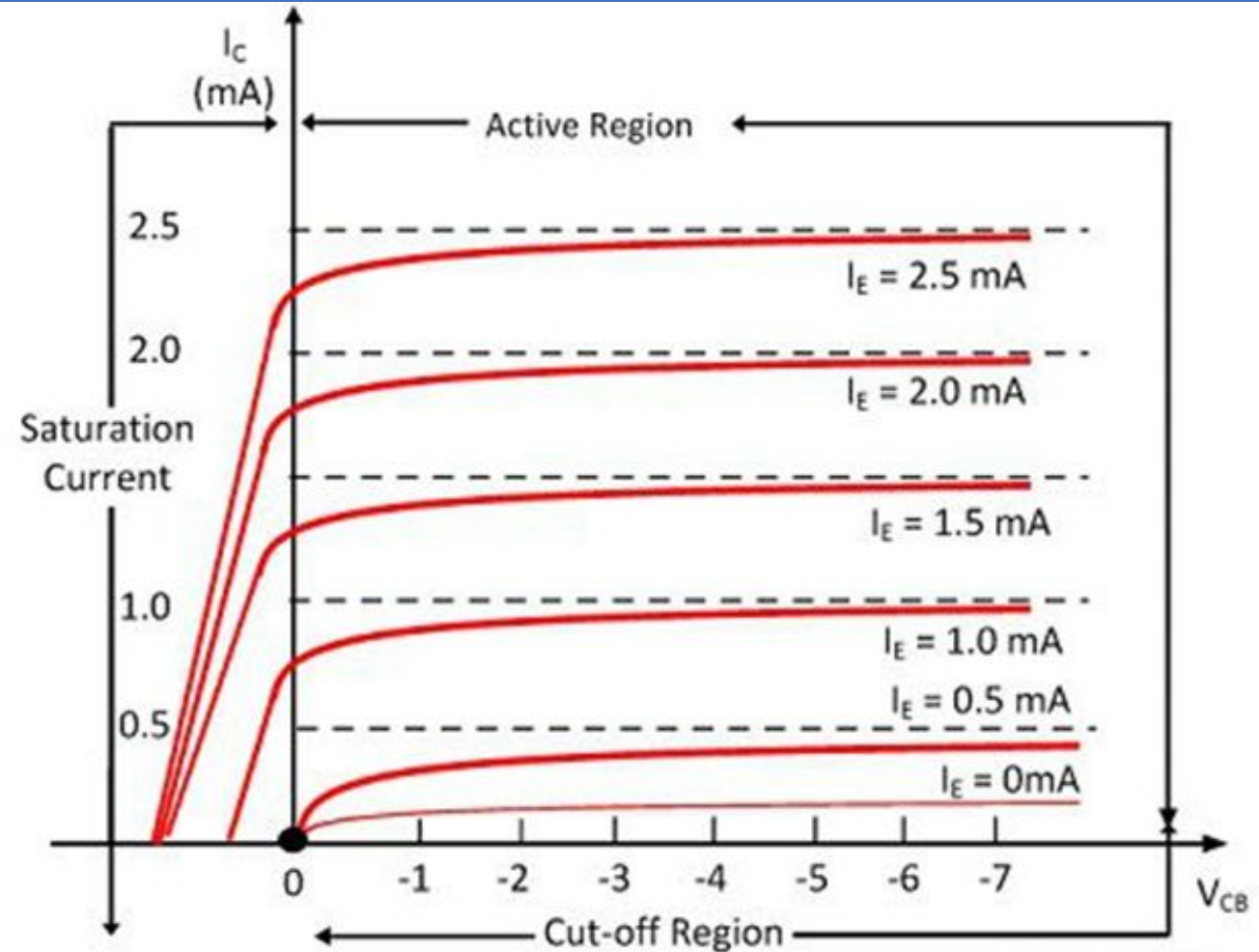

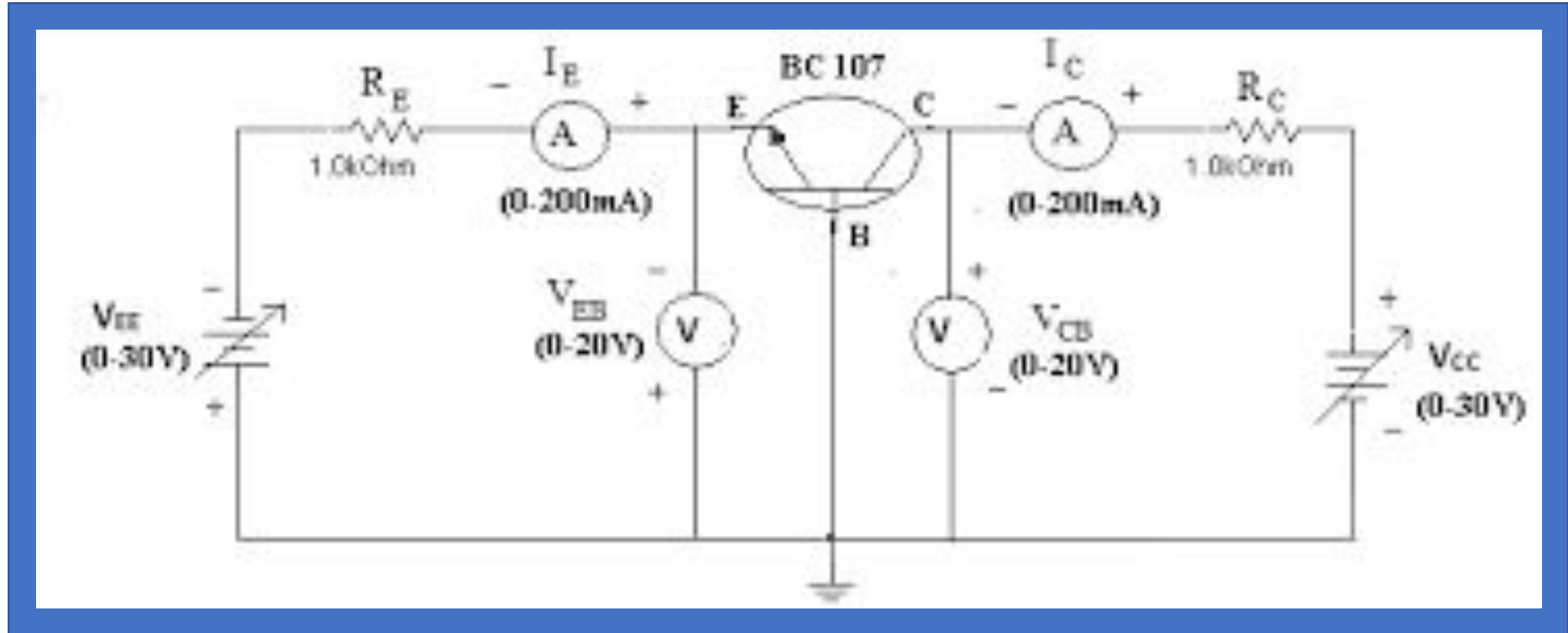CIRCUIT ARRANGEMENT TO FIND INPUT AND OUTPUT CHARACTERISTICS




COMMON EMITTER CONFIGURATION

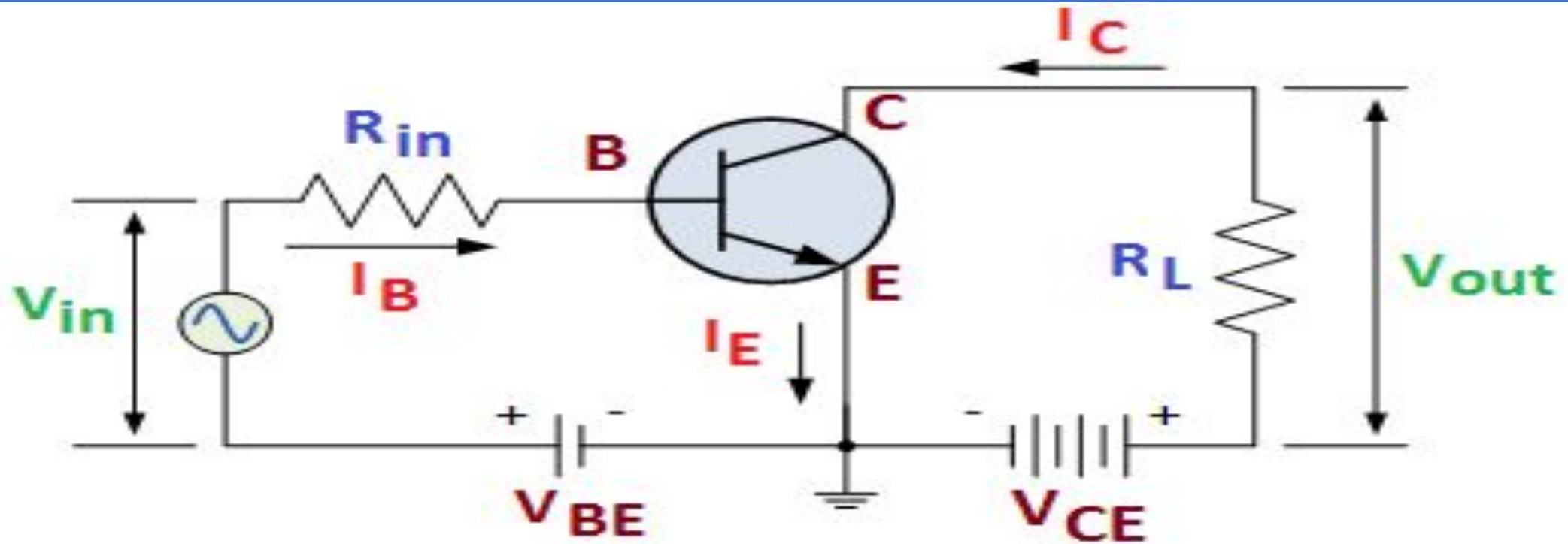


Common Emitter Configuration

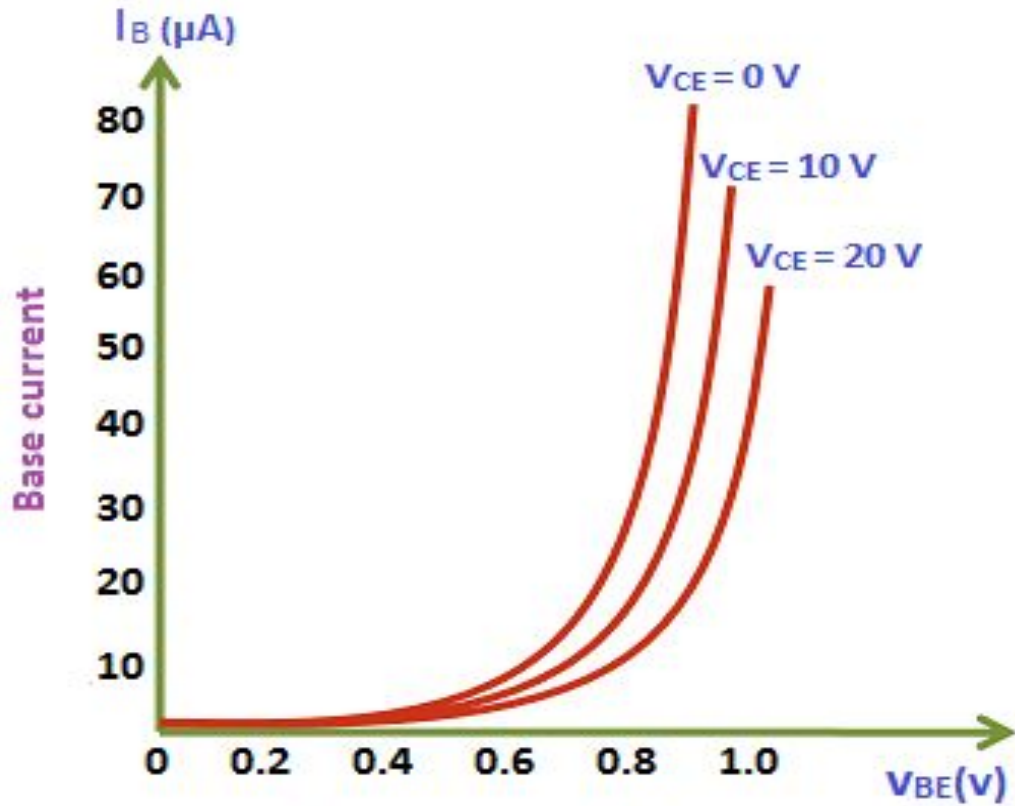INPUT OUTPUT CHARACTERISTICS OF CE AMPLIFIER




Base-emitter voltage

I/P characteristics CE configuration

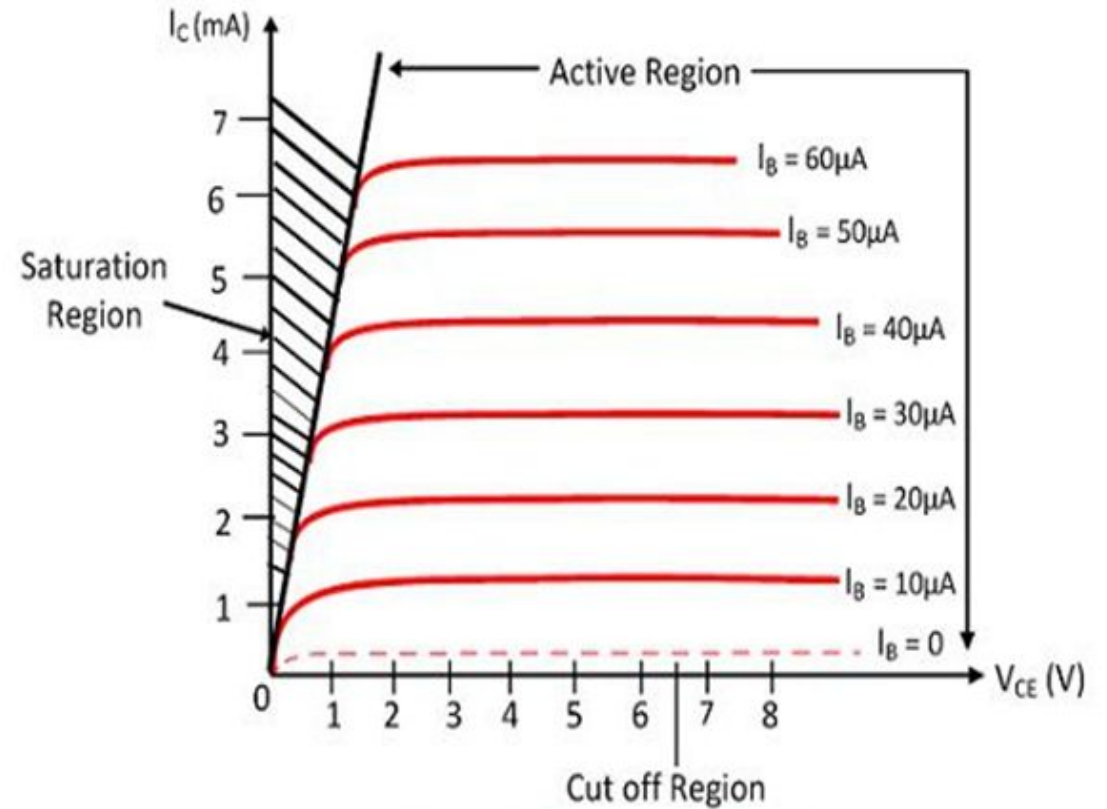


Output Characteristic Curve

COMMON COLLECTOR CONFIGURATION

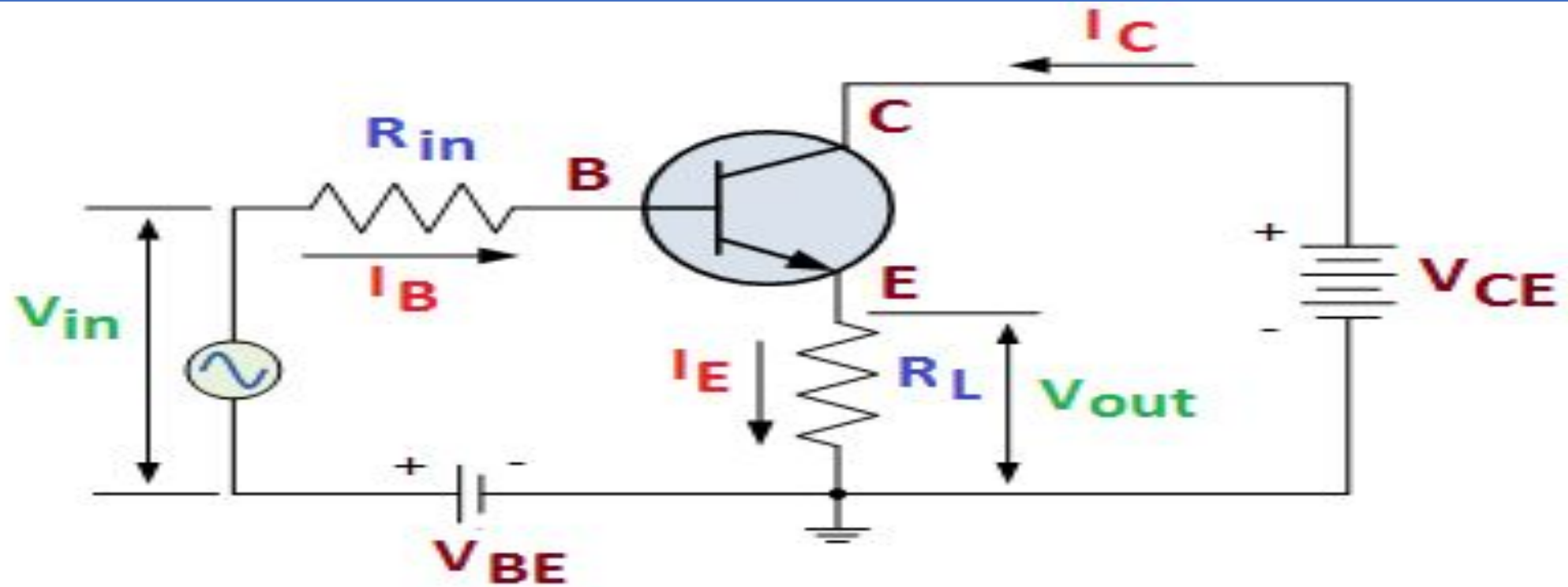


Common Collector Configuration

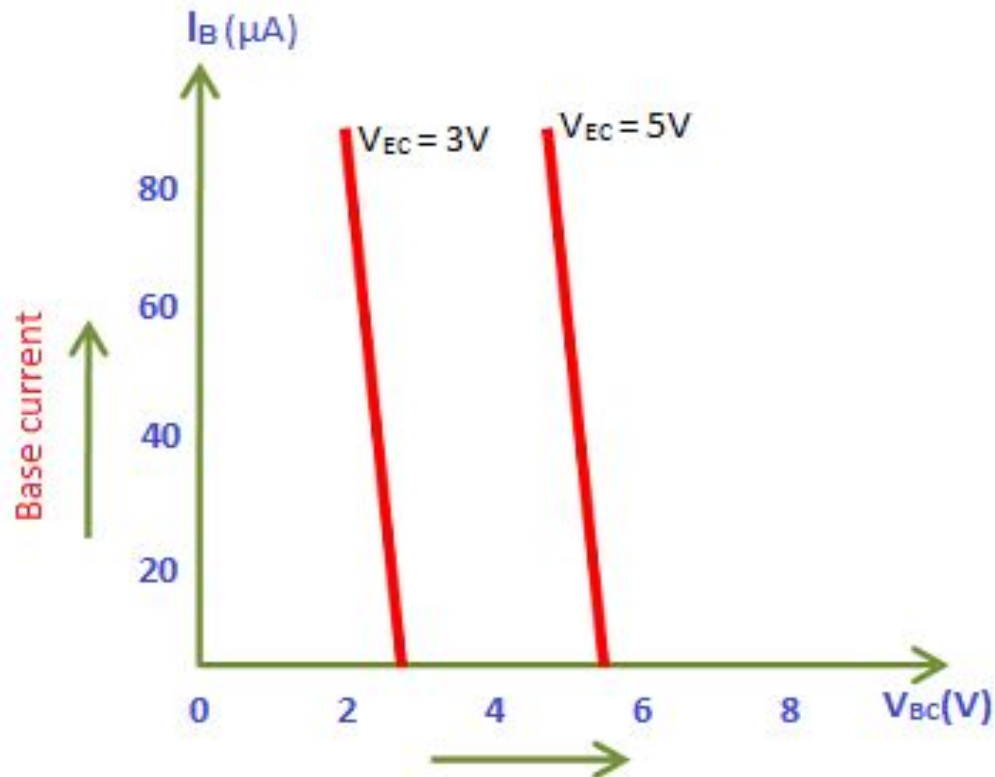INPUT OUTPUT CHARACTERISTICS OF CC AMPLIFIER



Input characteristics

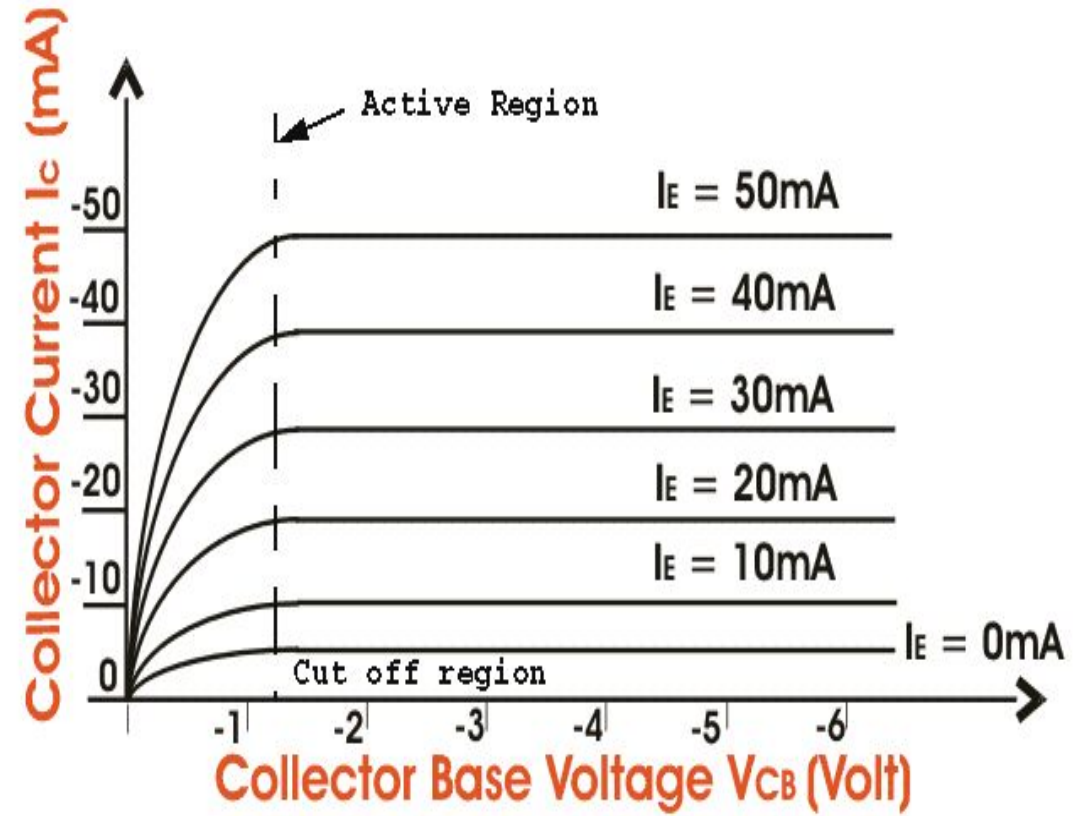

CURRENT AMPLIFICATION FACTOR

In CC- Current Amplification Factor (γ_{dc})

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

$$I_E = I_C + I_B$$

$$\Delta I_E = \Delta I_C + \Delta I_B$$

$$\Delta I_B = \Delta I_E - \Delta I_C$$


$$\gamma = \frac{\Delta I_E}{\Delta I_E - \Delta I_C}$$

$$\gamma = \frac{\Delta I_E / \Delta I_E}{\Delta I_E / \Delta I_E - \Delta I_C / \Delta I_E}$$

$$\gamma = \frac{1}{1 - \Delta I_C / \Delta I_E}$$

$$\gamma = \frac{1}{1 - \alpha}$$

CURRENT AMPLIFICATION FACTOR

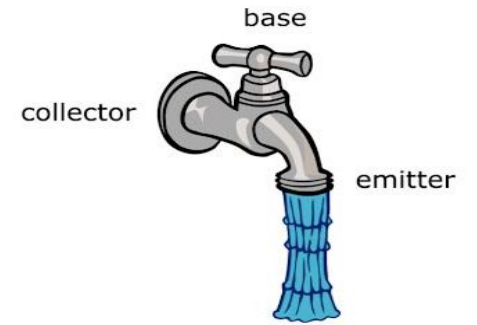

In CB- Current Amplification Factor (α_{dc}):

For a transistor with common base configuration it is defined as the ratio of static (d.c.) collector current I_C to the static emitter current I_E at a constant collector voltage with respect to base.

$$\alpha_{dc} = \left(\frac{I_C}{I_E} \right)_{[V_{CB}=\text{constant}]} \quad \beta_{dc} = \left(\frac{I_C}{I_E} \right)_{[V_{CE}=\text{constant}]}$$

In CE- For a transistor with common emitter configuration it is defined as the ratio of static collector current I_C to the static base current I_B at a constant collector voltage with respect to emitter.

RELATION BETWEEN α_{DC} AND β_{DC} :

We know that

$$I_E = I_B + I_C$$

Dividing both sides by I_C , we get

$$\frac{I_E}{I_C} = \frac{I_B}{I_C} + 1$$

$$\text{or, } \frac{1}{\alpha_{dc}} = \frac{1}{\beta_{dc}} + 1$$

$$\alpha_{dc} = \frac{\beta_{dc}}{1 + \beta_{dc}}$$

$$\text{or, } \beta_{dc} = \frac{\alpha_{dc}}{1 - \alpha_{dc}}$$

COLLECTOR CURRENT IN TERMS OF LEAKAGE CURRENT

$$I_C = \alpha I_\beta + I_{CBO}$$

$$I_E = I_C + I_B = (\alpha I_\beta + I_{CBO}) + I_B$$

$$I_E(1 - \alpha) = I_\beta + I_{CBO}$$


$$I_E = I_B \left(\frac{1}{1 - \alpha} \right) + I_{CBO} \left(\frac{1}{1 - \alpha} \right)$$

$$= (\beta + 1)I_B + (\beta + 1)I_{CBO}$$

Comparison of configurations




Sr. No.	Parameter	CB	CE	CC
1.	Common terminal between input and output	Base	Emitter	Collector
2.	Input current	I_E	I_B	I_B
3.	Output current	I_C	I_C	I_E
4.	Current gain	$\alpha_{dc} = I_C / I_E$	$\beta_{dc} = I_C / I_B$	$\gamma_{dc} = I_E / I_B$
5.	Input voltage	V_{EB}	V_{BE}	V_{BC}
6.	Output voltage	V_{CB}	V_{CE}	V_{BC}
7.	Voltage gain	Medium	Medium	Less than 1
8.	Input resistance	Very low (20 Ω)	Low (1k Ω)	High (500 k Ω)
9.	Output resistance	Very high (1M Ω)	High (40 K Ω)	Low (50 Ω)
10.	Applications	As preamplifier	Audio amplifier	For impedance matching

DC LOAD LINE

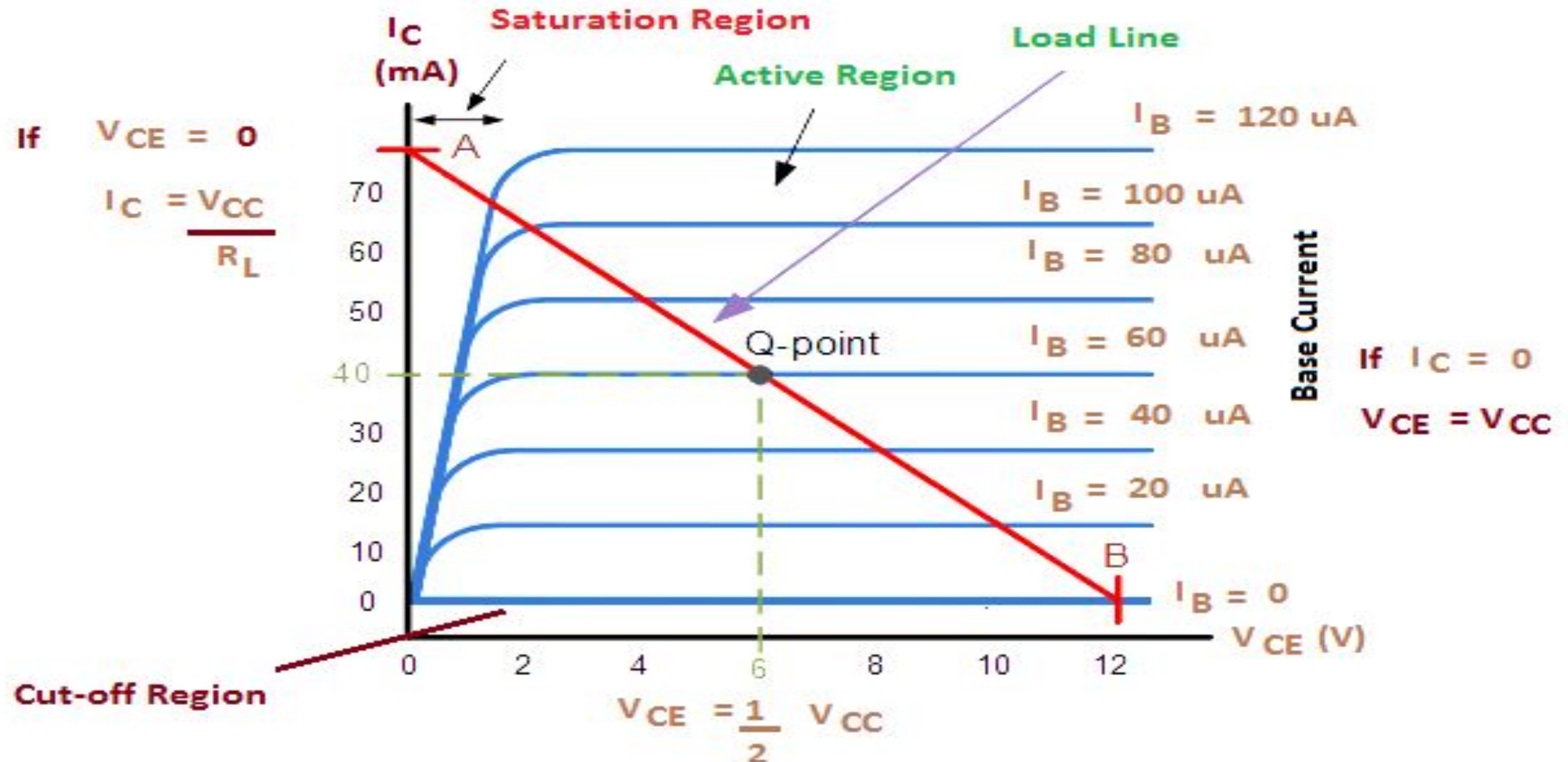

Transistor Testing

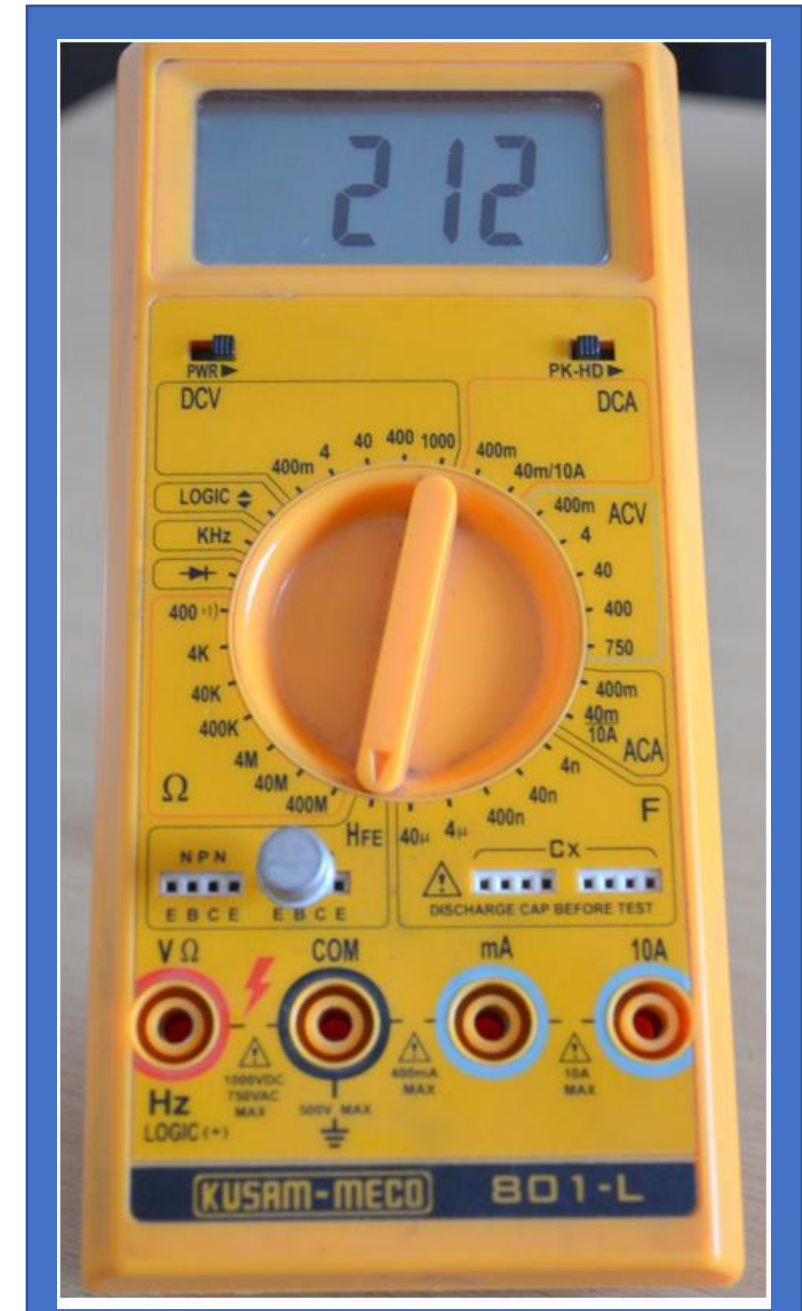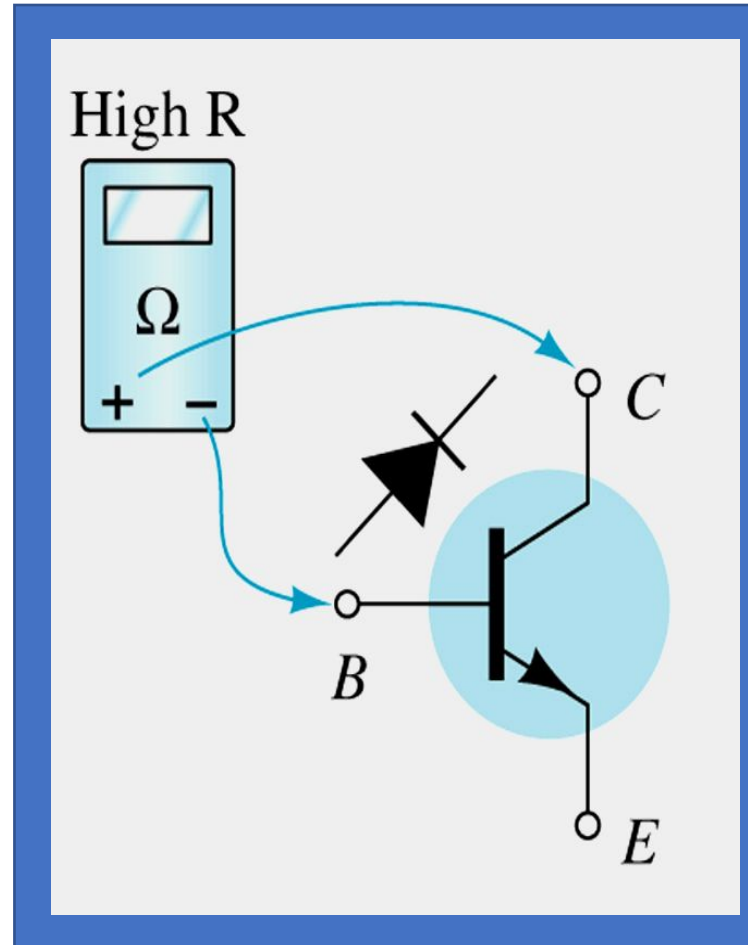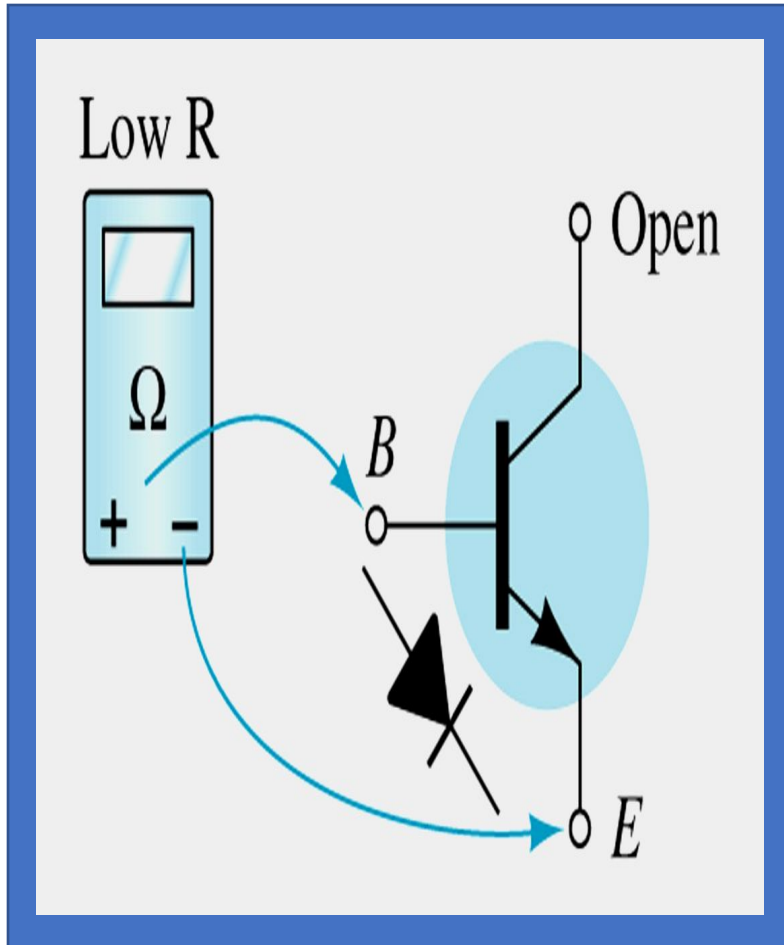Using DMM: some DMM's will measure β_{DC} or h_{fe} .



REFLECTION SPOT



testmoz.com/4766730

<https://www.youtube.com/watch?v=7ukDKVHnac4>

SUMMARY

- DC Load Line analysis
- Common Base Configuration
- Input Output Characteristics of CB configuration
- Common Collector Configuration
- Input Output Characteristics of CC configuration
- Comparison of CE, CB and CC