

1. Which of the following is the correct relationship between base and emitter current of a BJT?

- a) $I_B = \beta I_E$
- b) $I_B = I_E$
- c) $I_B = (\beta + 1) I_E$
- d) $I_E = (\beta + 1) I_B$

View Answer

Answer: d

Explanation: For a BJT, the collector current $I_C = \beta I_B$ and $I_E = I_C + I_B$

Hence, $I_E = (\beta + 1) I_B$.

2. For best operation of a BJT, which region must the operating point be set at?


- a) Active region
- b) Cutoff region
- c) Saturation region
- d) Reverse active region

View Answer

Answer: a

Explanation: Operating point for a BJT must always be set in the active region to ensure proper functioning. Setting up of Q-point in any other region may lead to reduced functionality.

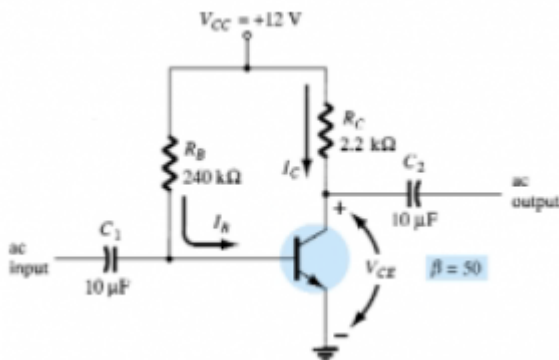3. From the given circuit, using a silicon transistor, what is the value of I_{BQ} ?



- a) 47.08 mA
- b) 47.08 μ A
- c) 50 μ A
- d) 0 mA

View Answer

Answer: b

Explanation: Consider the BJT to be in saturation. Then $I_C = 12 - 0.2 / 2.2k = 5.36$ mA

And $I_B = 12 - 0.8 / 240k = 0.047$ mA

$I_{BMIN} = I_{CSAT} / \beta = 5.09 / 50 = 0.1072$ mA which is greater than above I_B .


Hence transistor is in the active region.

Thus $I_C = \beta I_B$.

$V_{BE} = 0.7$ V

$I_B = 12 - 0.7 / 240 = 47.08 \mu$ A

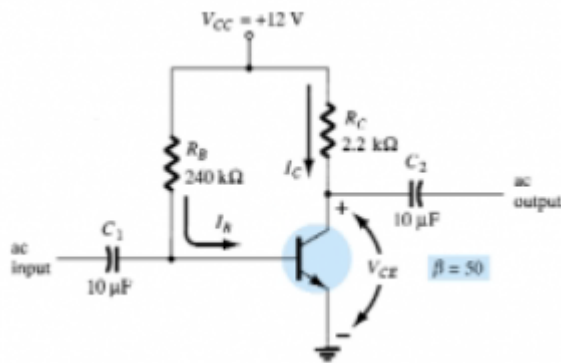4. From the given circuit, using a silicon BJT, what is the value of V_{CEQ} ?



- a) 7 V
- b) 0.7 V
- c) 6.83 V
- d) 7.17 V

[View Answer](#)

Answer: c

Explanation: Consider the BJT to be in saturation. Then $I_C = 12 - 0.2 / 2.2k = 5.36$ mA

And $I_B = 12 - 0.8 / 240k = 0.047$ mA

$I_{BMIN} = I_{CSAT} / \beta = 5.09 / 50 = 0.1072$ mA which is greater than above I_B .

Hence transistor is in the active region.

Thus $I_C = \beta I_B$.


$V_{BE} = 0.7$ V

$I_B = 12 - 0.7 / 240 = 47.08 \mu A$

$I_C = 50 \times 47.08 = 2.354$ mA

$V_{CE} = V_{CC} - I_C R_C = 12 - 2.354 \times 2.2 = 12 - 5.178 = 6.83$ V.

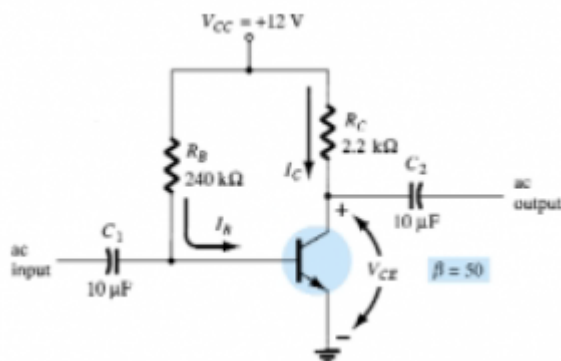5. From the given circuit, using a silicon BJT, what is the value of V_{BC} ?



- a) 6.13 V
- b) -6.13 V
- c) 7 V
- d) -7 V

[View Answer](#)

Answer: b

Explanation: Consider the BJT to be in saturation. Then $I_C = 12 - 0.2 / 2.2k = 5.36$ mA

And $I_B = 12 - 0.8 / 240k = 0.047$ mA

$I_{BMIN} = I_{CSAT} / \beta = 5.09 / 50 = 0.1072$ mA which is greater than above I_B .

Hence transistor is in the active region.

Thus $I_C = \beta I_B$.

$V_{BE} = 0.7$ V


$$I_B = 12 - 0.7 / 240 = 47.08 \mu A$$

$$I_C = 50 \times 47.08 = 2.354 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C = 12 - 2.354 \times 2.2 = 12 - 5.178 = 6.83 \text{ V}$$

$$\text{Hence } V_{BC} = 0.7 - 6.83 = -6.13 \text{ V.}$$

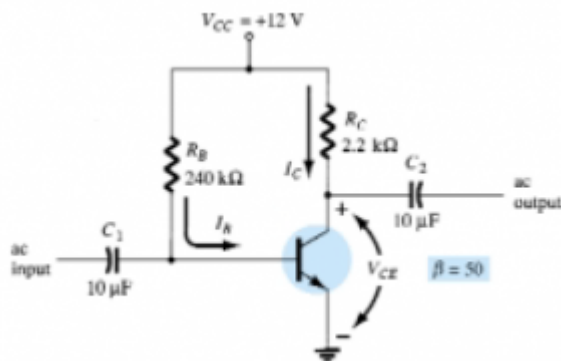6. From the given circuit, using silicon BJT, what is the value of the saturation collector current?




- a) 5 mA
- b) 5.36 mA
- c) 5.45 mA
- d) 10.9 mA

[View Answer](#)

Answer: b

Explanation: To obtain an approximate answer, under saturation the BJT is ON and hence acts like a short circuit. However, ideally a drop exists for the transistor which is a fixed value. For an exact answer, if the BJT is a Silicon transistor, then drop $V_{CE} = 0.2 \text{ V}$ and current is $12 - 0.2 / 2.2 = 5.36 \text{ mA}$.

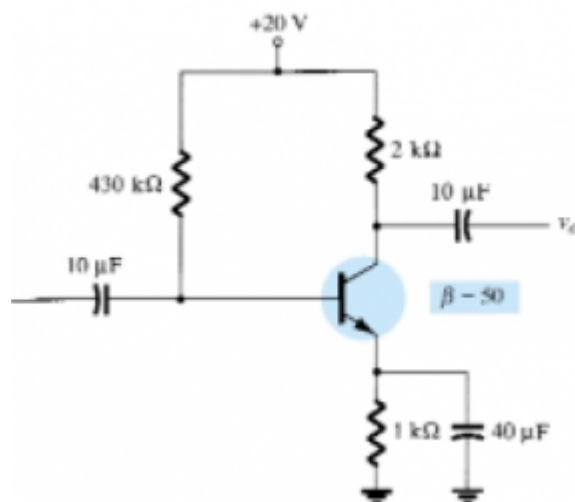7. In the given circuit, what is the value of I_C if the BJT is made of Silicon?



- a) 2.01 mA
- b) 2.01 uA
- c) 10.05 mA
- d) 10.05 uA

[View Answer](#)

Answer: a

Explanation: Consider the BJT to be in saturation. Then $I_C = 20 - 0.2 / 2k = 9.9 \text{ mA}$
And $I_B = 20 - 0.8 / 430k = 0.044 \text{ mA}$

$I_{BMIN} = I_{CSAT} / \beta = 5.09 / 50 = 0.198 \text{ mA}$ which is greater than above I_B .

Hence transistor is in the active region.


Thus $I_C = \beta I_B$.

$V_{BE} = 0.7 \text{ V}$

$I_B = (20 - 0.7) / 430 = 44.88 \mu\text{A}$

$I_C = 50 \times 44.88 = 2.24 \text{ mA}$.

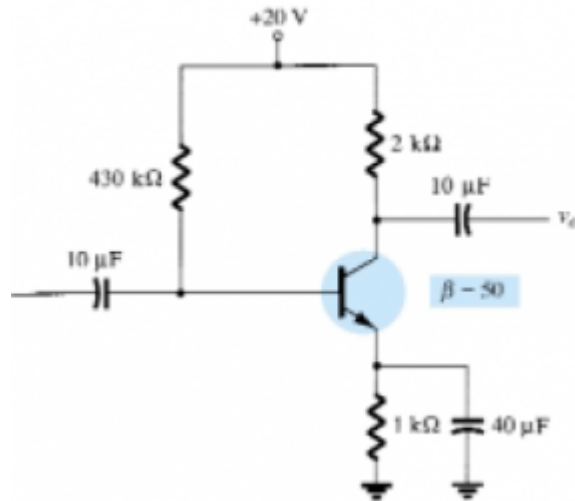8. In the given circuit, using a silicon BJT, what is the value of V_{CE} ?



a) 20 V

b) 15.52 V

c) 14.98 V

d) 13.97 V

[View Answer](#)

Answer: b

Explanation: Consider the BJT to be in saturation. Then $I_C = (20 - 0.2) / 2\text{k} = 9.9 \text{ mA}$

And $I_B = (20 - 0.8) / 430\text{k} = 0.044 \text{ mA}$

$I_{BMIN} = I_{CSAT} / \beta = 5.09 / 50 = 0.198 \text{ mA}$ which is greater than above I_B .

Hence transistor is in the active region.

Thus $I_C = \beta I_B$.


$V_{BE} = 0.7 \text{ V}$

$I_B = (20 - 0.7) / 430 = 44.88 \mu\text{A}$

$I_C = 50 \times 44.88 = 2.24 \text{ mA}$

$V_{CE} = 20 - 2.24 \times 2 = 15.52 \text{ V}$.

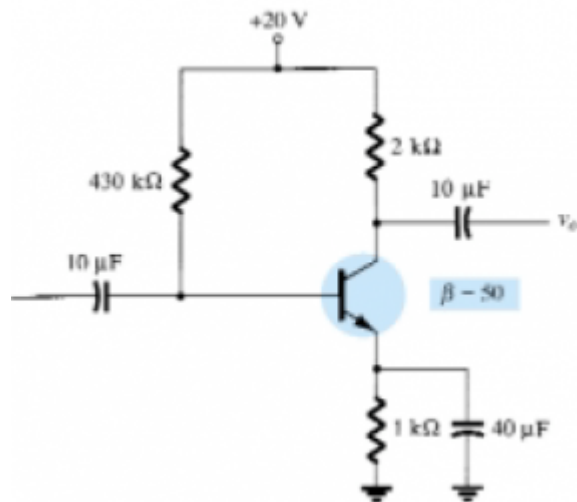9. In the given circuit, what is the value of V_E when using a silicon BJT?



- a) 2.01 V
- b) 0.28 V
- c) 0 V
- d) 2.28 V

[View Answer](#)

Answer: d

Explanation: Consider the BJT to be in saturation. Then $I_C = 20 - 0.2/2k = 9.9 \text{ mA}$

And $I_B = 20 - 0.8/430k = 0.044 \text{ mA}$

$I_{BMIN} = I_{CSAT}/\beta = 5.09/50 = 0.198 \text{ mA}$ which is greater than above I_B .

Hence transistor is in the active region.

Thus $I_C = \beta I_B$.

$V_{BE} = 0.7 \text{ V}$


$I_B = 20 - 0.7/430 = 44.88 \mu\text{A}$

$I_C = 50 \times 44.88 = 2.24 \text{ mA}$

$V_{CE} = 20 - 2.24 \times 2 = 15.52 \text{ V}$

$V_E = I_E R_E = (1 + \beta) I_B R_E = 51 \times 44.88 \times 1 = 2.28 \text{ V}$.

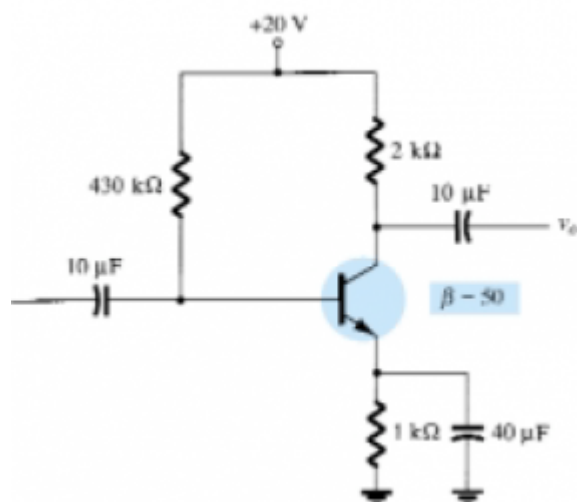10. In the given circuit using a silicon BJT, what is the value of saturation collector current?



- a) 10 mA
- b) 8.77 mA

c) 6.67 mA

d) 5 mA

[View Answer](#)

Answer: c

Explanation: To obtain an approximate answer, under saturation the BJT is ON and hence acts like a short circuit. However, ideally a drop exists for the transistor which is a fixed value. For an exact answer, if the BJT is a Silicon transistor, then drop $V_{CE} = 0.2V$ and current is $20 - 0.2 / 2.2 = 9.9$ mA.