

Name :- Ishan Sonam

Class :- D9 A

Rollno:- 52

Subject :- PCE

Assignment 03

(Q.1)

Ans (i) Modulation index: It is defined as the ratio of frequency deviation (Δf) to the modulating frequency (f_m).

$$M.I = \frac{\text{frequency deviation}}{\text{modulating frequency.}} = \frac{\Delta f}{f_m}$$

(ii) Frequency deviation: The amount of change in carrier frequency produced by the modulating signal is known as frequency deviation.

(iii) Deviation ratio: It is the worst case modulation index and is equal to the maximum peak frequency deviation divided by the maximum modulating signal frequency producing the widest frequency spectrum.


$$[DR = \frac{\Delta f_{\text{max}}}{f_{m\text{max}}}]$$

(Q.2)

Ans

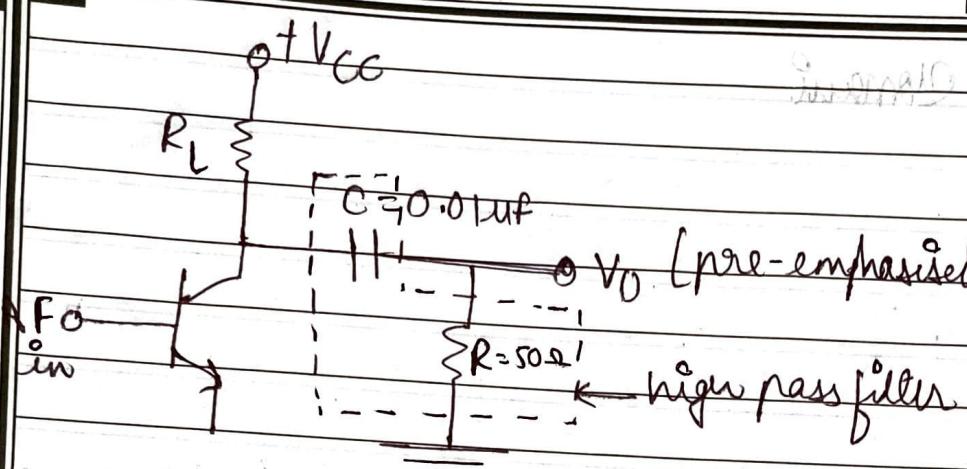
(i) Pre-emphasis:

The artificial boosting of higher audio modulating frequencies in accordance with prearranged response curve is called pre-emphasis.



- AF is passed through a high-pass filter, before applying to FM modulator.
- As modulating frequency (f_m) increases, capacitive reactance decreases and modulating voltage goes on increasing.
- $f_m \propto$ voltage of modulating signal applied to FM modulator.

(ii) De-emphasis:

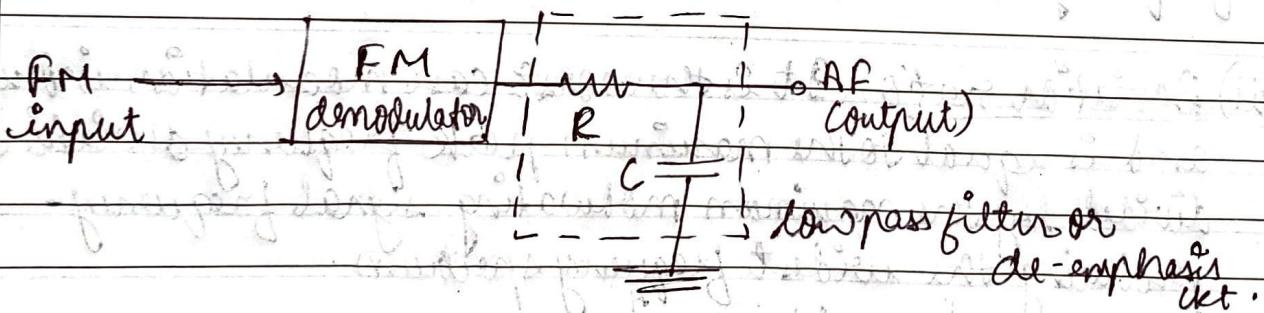

- De-modulated FM is applied to the de-emphasis circuit where with increase in f_m , capacitive reactance X_C decreases so that output of de-emphasis circuit also reduces.

(2.3)

AM

AM:


FM

parameters :

- (1) definition . Amplitude of carrier is varied in accordance with amplitude of modulating signal keeping frequency & phase constant . Frequency of carrier is varied in accordance with the amplitude of modulating signal keeping amplitude and phase constant .

- (2) constant parameters . Frequency and phase . Amplitude and phase .

- (3) Modulating signal .

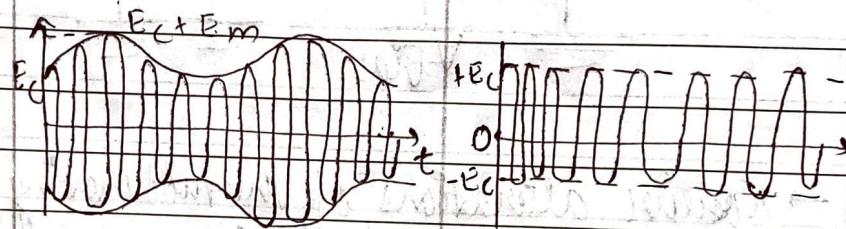

- (4) modulation index $m = E_m / E_C$

$$m = E_m / E_C$$

$$m = \sqrt{1 + f_m^2}$$

- (5) No. of sidebands Only two

Infinite if dispersion
is present


- (6) Bandwidth. $BW = 2f_m$

$$BW = 2(f_m + f_{mod})$$

- (7) Application MW, SW band broadcasting, Increasing FM, video transmission in TV, radio (audio) transmission in TV .


(P.4)

(i) Varactor diode modulator:

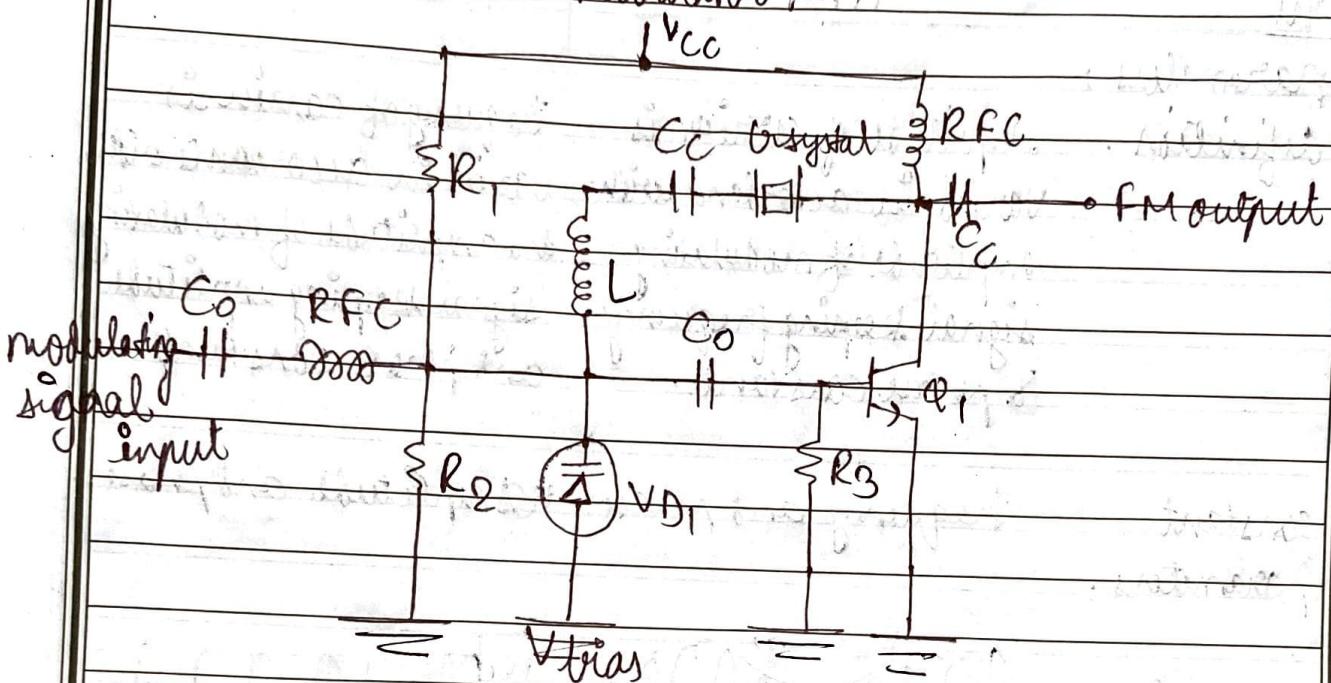

- positive alterations of the modulating signal increase the reverse bias of VD_1 , which decreases its capacitance and increases the frequency of the oscillation.
- negative alterations of the modulating signal decrease the reverse bias of VD_1 , which increases its capacitance and decreases the frequency of the oscillation.
- simple to use, stable and reliable but limited peak frequency deviation thus limited use to low power applications.

(ii) FET Resistance method:-

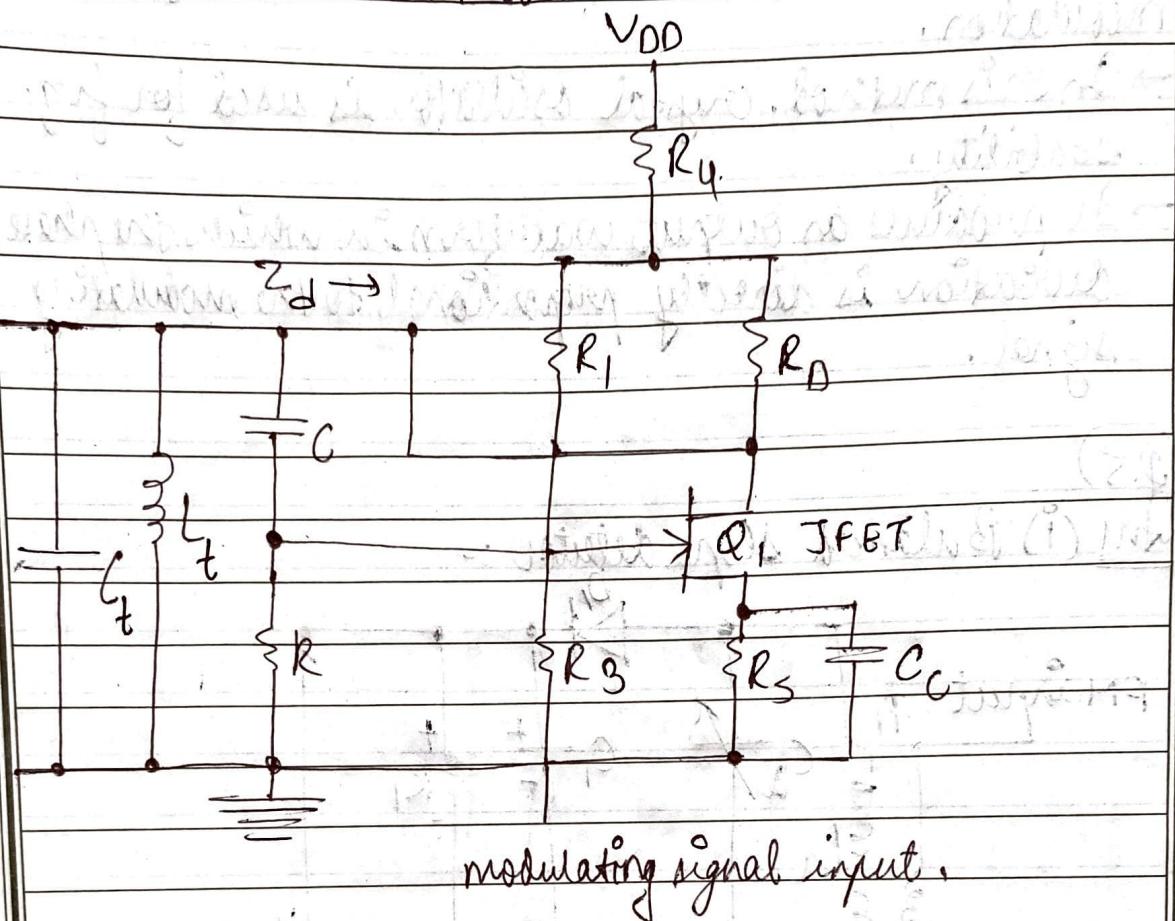

- The circuit shown in figure is the basic circuit of a FET resistance modulator which behaves as a three terminal resistance that may be connected across the tank circuit of the oscillator to be frequency modulated.
- It can be made inductive or capacitive by a simple component changes.
- FET is used in the circuit here for simplicity only.


(iii) Demodulation method:-

- Indirect method of FM generation is also known as demodulation method of FM generation.

- In this method, the FM is obtained through phase modulation.
- In this method, crystal oscillator is used for freq. stability.
- It produces an output waveform in which the phase duration is directly proportional to the modulating signal.

(Q.5)


Ans (i) Balanced slope detector :-

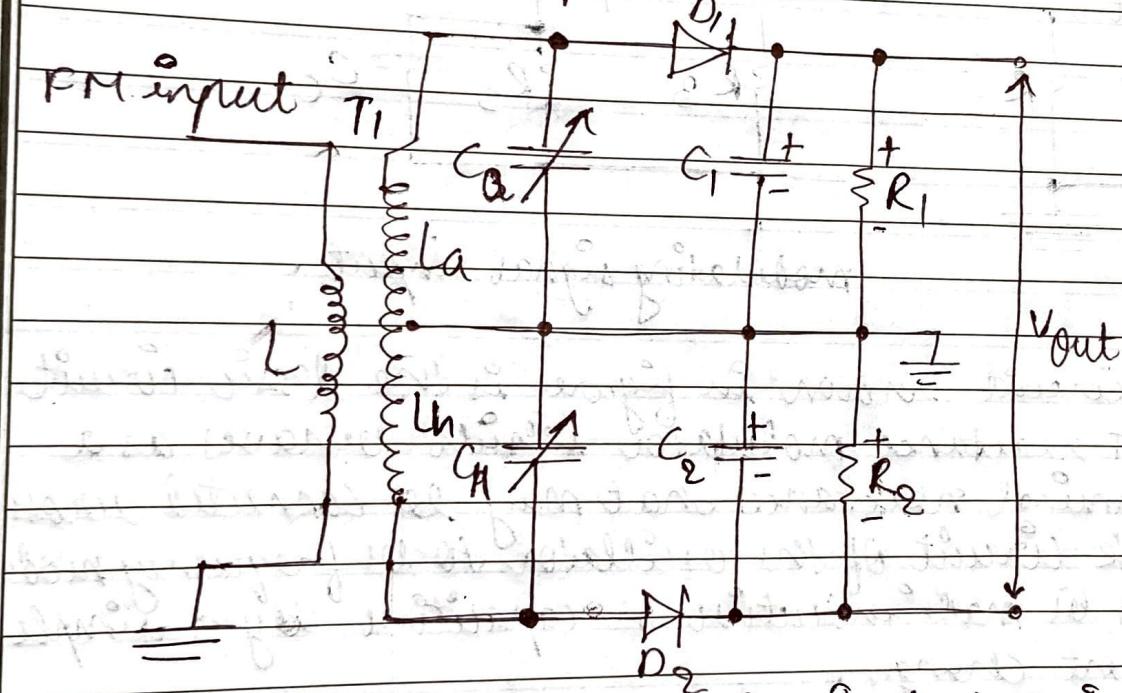

- balanced slope detector is simply two single-ended slope detector connected in parallel and fed 180° out of phase.
- phase inversion accomplished by centre tapping secondary windings of T_1 .
- tuned circuits (C_1, C_2, L_1, L_2) perform an FM-to-AM conversion.

- Balanced peak detectors (D_1, C_1, R_1 , & D_2, R_2, C_2) remove the information from the AM envelope.
- L_a & C_a is tuned to frequency f_a that is about IF centre frequency (f_c).
- L_b & C_b is tuned to frequency f_b that is below IF centre frequency (f_c).

(ii) Foster-Seeley Discriminator:-

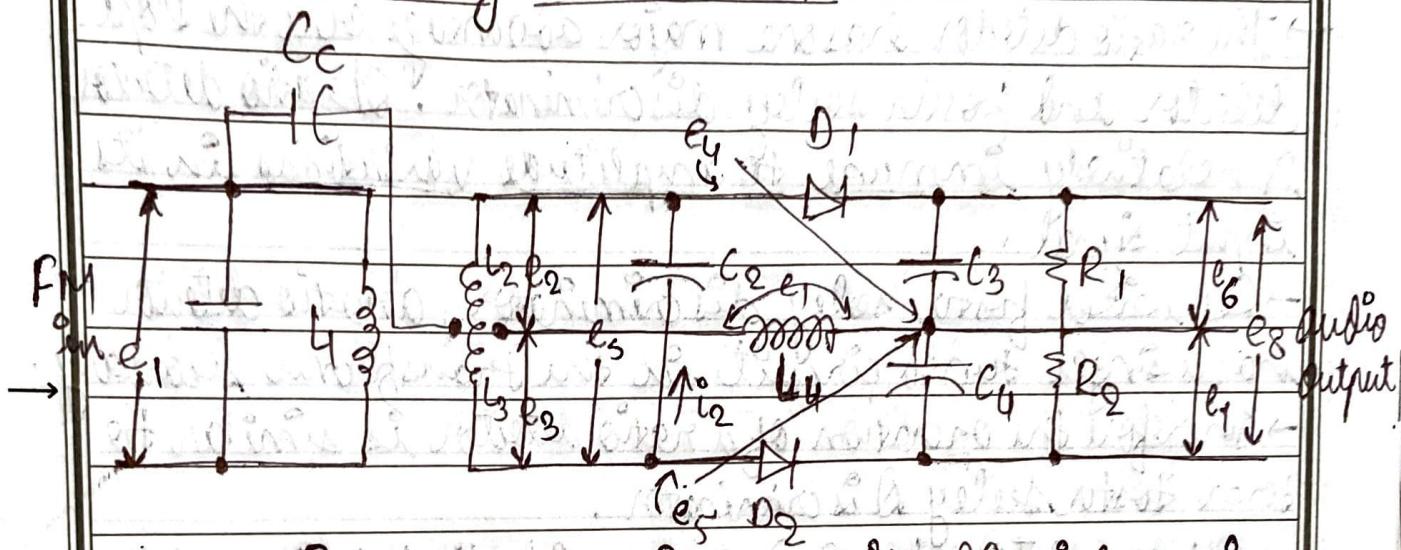


→ sometimes called as Phase shift Discriminator is a tuned circuit frequency discriminator whose operation is very similar to that of the balanced signle detector.

→ The capacitance values for C_c , C_1 , & C_2 are chosen such that they are short circuits for IF center frequency.

→ therefore the right side of L_2 is at ground potential and the IF signal (V_{in}) is fed directly across L_2 .

→ the inverting IF is inverted 180 degrees by transformer T_1 and divided equally between L_a & L_b .

(iii) Ratio detector:

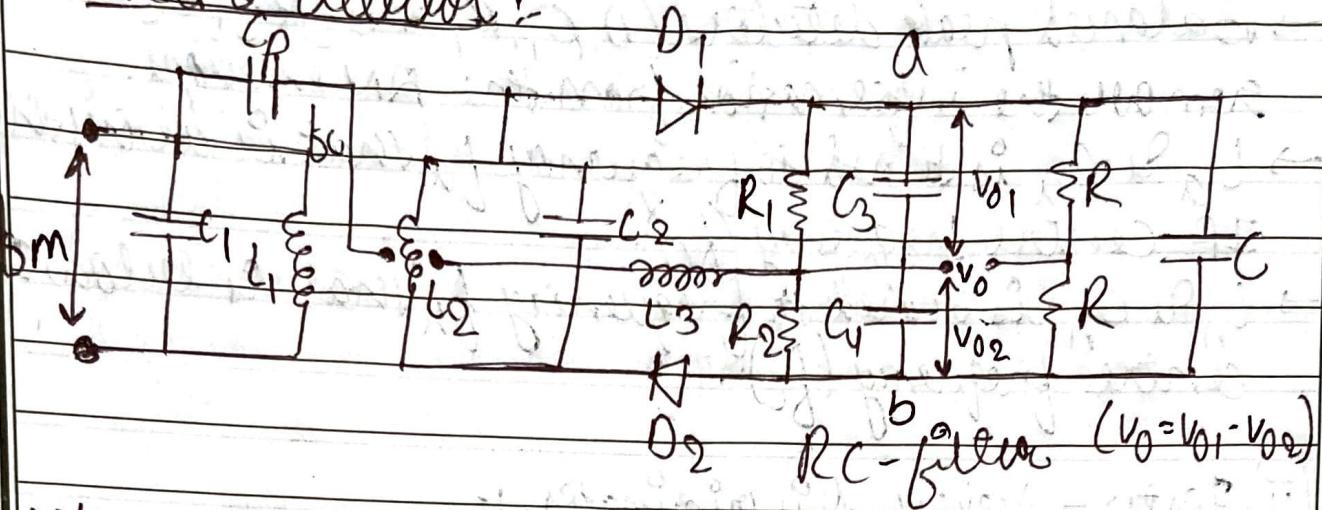

→ The ratio detector has one major advantage over the slope detector and Foster Seeley discriminator. A ratio detector is relatively immune to amplitude variations in its input signal.

→ As with Foster Seeley discriminator, a ratio detector has a single tuned circuit in the transformer secondary.

→ Therefore the operation of a ratio detector is similar to that Foster Seeley Discriminator.

→ Voltage vectors for D_1 & D_2 are identical to those of the F.S. discriminator.

→ However the ratio detector, one diode (D_2) is reversed and current (I_d) can flow around the outermost loop of the circuit.

→ Therefore after several cycles of the input signal, sixty capacitor C_3 charges to approximately the peak voltage across the secondary winding of T_1 .

Q. 6
(a)

Ans $[y \text{ fm} = 10 \sin(6\pi \cdot 10^6 t) + 20 \sin 2\pi \cdot 10^3 t]$.