

# **Chapter 5 Synchronous Sequential Logic**

# CHAPTER OBJECTIVES


1. Know how to distinguish a sequential circuit from a combinational circuit.
2. Understand the functionality of a *SR* latch, transparent latch, *D* flip-flop, *JK* flip-flop, and *T* flip-flop.
3. Know how to use the characteristic table and characteristic equation of a flip-flop.
4. Know how to derive the state equation, state table, and state diagram of a clocked sequential circuit.
5. Know the difference between Mealy and Moore finite state machines.
6. Given the state diagram of a finite state machine, be able to write a HDL model of the machine.
7. Understand the HDL models of latches and flip-flops.
8. Know how to write synthesizable HDL models of clocked sequential circuits.
9. Know how to design a state machine using manual methods.
10. Know how to eliminate equivalent states in a state table.
11. Know how to define a one-hot state assignment code.
12. Be able to design a sequential circuit with (a) *D* flip-flops, (b) *JK* flip-flops, and (c) *T* flip-flops.

## 5.1 INTRODUCTION

Hand-held devices, cell phones, navigation receivers, personal computers, digital cameras, personal media players, and virtually all electronic consumer products have the ability to send, receive, store, retrieve, and process information represented in a binary format. The technology enabling and supporting these devices is critically dependent on electronic components that can store information, that is, have memory. This chapter examines the operation and control of these devices and their use in circuits and enables you to better understand what is happening in these devices when you interact with them. The digital circuits considered thus far have been combinational—their output depends only and immediately on their inputs—they have no memory, that is, they do not depend on past values of their inputs. Sequential circuits, however, act as storage elements and have memory. They can store, retain, and then retrieve information when needed at a later time. It is important that you understand the distinction between sequential and combinational circuits.

## 5.2 SEQUENTIAL CIRCUITS

[Figure 5.1](#) shows a block diagram of a sequential circuit. It consists of a combinational circuit to which memory elements are connected to form a feedback path. The storage elements are devices capable of storing binary information. The binary information stored in these elements at any given time defines the *state* of the sequential circuit at that time. The sequential circuit receives binary information from external inputs that, together with the present state of the storage elements, determine the binary value of the outputs. These external inputs also determine the condition for changing the state in the storage elements. The block diagram demonstrates that the outputs in a sequential circuit are a function not only of the inputs but also of the present state of the storage elements. The next state of the storage elements is also a function of external inputs and the present state. Thus, **a sequential circuit is specified by a time sequence of inputs, outputs, and internal states**. In contrast, the outputs of combinational logic depend on only the present values of the inputs.

 

**FIGURE 5.1**

Block diagram of sequential circuit


There are two main types of sequential circuits, and their classification is a function of the timing of their signals. A *synchronous* sequential circuit is a system whose behavior can be defined from the knowledge of its signals at discrete instants of time. The behavior of an *asynchronous* sequential circuit depends upon the input signals at any instant of time *and* the order in which the inputs change. The storage elements commonly used in asynchronous sequential circuits are time-delay devices. The storage

capability of a time-delay device varies with the time it takes for the signal to propagate through the device. In practice, the internal propagation delay of logic gates is of sufficient duration to produce the needed delay, so that actual delay units may not be necessary. In gate-type asynchronous systems, the storage elements consist of logic gates whose propagation delay provides the required storage. Thus, an asynchronous sequential circuit may be regarded as a combinational circuit with feedback. Because of the feedback among logic gates, an asynchronous sequential circuit may become unstable at times. The instability problem imposes many difficulties on the designer, and limits their use. These circuits will not be covered in this text.

A *synchronous* sequential circuit employs signals that affect the storage elements at only discrete instants of time. Synchronization is achieved by a timing device called a *clock generator*, which provides a clock signal having the form of a periodic sequence of *clock pulses*. The clock signal is commonly denoted by the identifiers *clock* and *clk*. The clock pulses are distributed throughout the system in such a way that storage elements are affected only with the arrival of each pulse. In practice, the clock pulses determine *when* computational activity will occur within the circuit, and other signals (external inputs and otherwise) determine *what* changes will take place affecting the storage elements and the outputs. For example, a circuit that is to add and store two binary numbers would compute their sum from the values of the numbers and store the sum at the occurrence of a clock pulse. Synchronous sequential circuits that use clock pulses to control storage elements are called *clocked sequential circuits* and are the most frequently encountered type in practice. They are called *synchronous circuits* because the activity within the circuit and the resulting updating of stored values is synchronized to the occurrence of clock pulses. The design of synchronous circuits is feasible because they seldom manifest instability problems, and their timing is easily broken down into independent discrete steps, each of which can be considered separately.

The storage elements (memory) used in clocked sequential circuits are called *flip-flops*. A flip-flop is a binary storage device capable of storing one bit of information. In a stable state, the output of a flip-flop is either 0 or 1. A sequential circuit may use many flip-flops to store as many bits as necessary. For example, a word of data may be stored as a 64-bit value. The block diagram of a synchronous clocked sequential circuit is shown in [Fig. 5.2](#). The *outputs* are formed by a combinational logic function of the

inputs to the circuit or the values stored in the flip-flops (or both). The value that is stored in a flip-flop when the clock pulse occurs is also determined by the inputs to the circuit or the values presently stored in the flip-flop (or both). The new value is stored (i.e., the flip-flop is updated) when a pulse of the clock signal occurs. Prior to the occurrence of the clock pulse, the combinational logic forming the next value of the flip-flop must have reached a stable value. Consequently, the speed at which the combinational logic circuits operate is critical. If the clock (synchronizing) pulses arrive at a regular interval, as shown in the timing diagram in [Fig. 5.2](#), the combinational logic must respond to a change in the state of the flip-flop in time to be updated before the next pulse arrives. Propagation delays play an important role in determining the minimum interval between clock pulses that will allow the circuit to operate correctly. A change in state of the flip-flops is initiated only by a clock pulse transition—for example, when the value of the clock signals changes from 0 to 1. When a clock pulse is not active, the feedback loop between the value stored in the flip-flop and the value formed at the input to the flip-flop is effectively broken because the flip-flop outputs cannot change even if the outputs of the combinational circuit driving their inputs change. Thus, the transition from one state to the next occurs only at predetermined intervals dictated by the clock pulses.

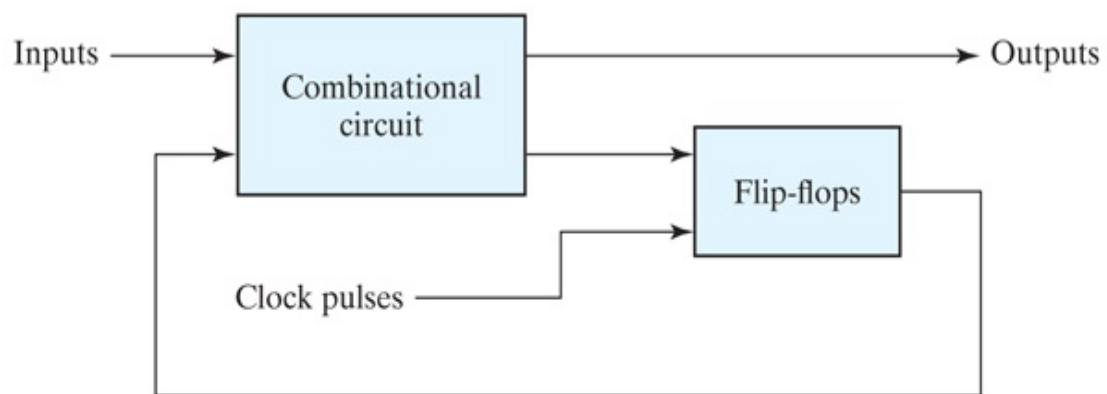

(a) Block diagram



(b) Timing diagram of clock pulses

**FIGURE 5.2**

[Description](#)

## Practice Exercise 5.1

1. Describe the fundamental difference between the output of a combinational circuit and the output of a sequential circuit.

**Answer:** The output of a combinational circuit depends on only the inputs to the circuit; the output of a sequential circuit depends on the inputs to the circuit and the present state of the storage elements.


## 5.3 STORAGE ELEMENTS: LATCHES

A storage element in a digital circuit can maintain a binary state indefinitely (as long as power is delivered to the circuit), until directed by an input signal to switch states. The major differences among various types of storage elements are in the number of inputs they possess and in the manner in which the inputs affect the binary state. *Storage elements that operate with signal levels (rather than signal transitions) are referred to as latches; those controlled by a clock transition are flip-flops.* Latches are said to be *level-sensitive* devices; flip-flops are *edge-sensitive* devices. The two types of storage elements are related because latches are the basic circuits from which all flip-flops are constructed. Although latches are useful for storing binary information and for the design of asynchronous sequential circuits, they are not practical for use as storage elements in synchronous sequential circuits. Because they are the building blocks of flip-flops, however, we will now consider the fundamental storage mechanism used in latches before considering flip-flops in the next section.
 
### SR Latch

The SR latch is a circuit with two cross-coupled NOR gates or two cross-coupled NAND gates, and two inputs labeled *S* for set, and *R* for reset. The SR latch constructed with two cross-coupled NOR gates is shown in [Fig. 5.3](#). The latch has two useful states. When output  $Q=1$  and  $Q'=0$ , the latch is said to be in the *set state*. When  $Q=0$  and  $Q'=1$ , it is in the *reset state*. Outputs  $Q$  and  $Q'$  are normally the complement of each other. However, when both inputs are equal to 1 at the same time, a condition in which both outputs are equal to 0 (rather than be mutually complementary) occurs. If both inputs are then switched to 0 simultaneously, the device will enter an unpredictable or undefined state or a metastable state. Consequently, in practical applications, **setting both inputs to 1 is forbidden.**





## FIGURE 5.3


SR latch with NOR gates

### Description

Under normal conditions, both inputs of the latch remain at 0 unless the state has to be changed. The application of a momentary 1 to (only) the  $S$  input causes the latch to go to the set state. The  $S$  input must go back to 0 before any other changes take place, in order to avoid the occurrence of an undefined next state that results from the forbidden input condition. As shown in the function table of [Fig. 5.3\(b\)](#), two input conditions cause the circuit to be in the set state. The first condition ( $S=1, R=0$ ) is the action that must be taken by input  $S$  to bring the circuit to the set state. Removing the active input from  $S$  leaves the circuit in the same state. After both inputs return to 0, it is then possible to shift to the reset state by momentarily applying a 1 to the  $R$  input. The 1 can then be removed from  $R$ , whereupon the circuit remains in the reset state. Thus, when both inputs  $S$  and  $R$  are equal to 0, the latch can be in either the set or the reset state, depending on which input was most recently a 1. When inputs are applied, the resulting (next) state of the latch depends on the inputs and on the present state of the latch.

If a 1 is applied to both the  $S$  and  $R$  inputs of the latch, both outputs go to 0. This action produces an undefined next state, because the state that results from the input transitions depends on the order in which they return to 0. It also violates the requirement that outputs be the complement of each other. In normal operation, this condition is avoided by making sure that 1's are not applied to both inputs simultaneously.

The SR latch with two cross-coupled NAND gates is shown in [Fig. 5.4](#). It operates with both inputs normally at 1, unless the state of the latch has to be changed. The application of 0 to the S input causes output Q to go to 1, putting the latch in the set state. When the S input goes back to 1, the circuit remains in the set state. After both inputs go back to 1, we are allowed to change the state of the latch by placing a 0 in the R input. This action causes the circuit to go to the reset state and stay there even after both inputs return to 1. The condition that is forbidden for the NAND latch is both inputs being equal to 0 at the same time, an input combination that should be avoided.

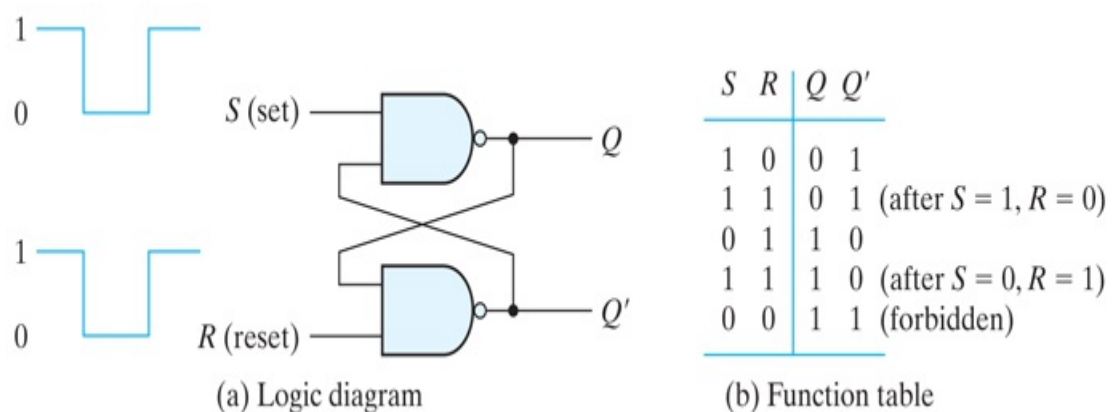

## FIGURE 5.4


SR latch with NAND gates

### [Description](#)

In comparing the NAND with the NOR latch, note that the input signals for the NAND require the complement of those values used for the NOR latch. Because the NAND latch requires a 0 signal to change its state, it is sometimes referred to as an S'R' latch. The primes (or, sometimes, bars over the letters) designate the fact that the inputs must be in their complement form to activate the circuit.

The operation of the basic SR latch can be modified by providing an additional input signal that determines (controls) *when* the state of the latch can be changed by determining whether S and R (or S' and R') can affect the circuit. An SR latch with a control input is shown in [Fig. 5.5](#). It consists of the basic SR latch and two additional NAND gates. The control

input  $En$  acts as an *enable* signal for the other two inputs. The outputs of the two additional NAND gates stay at the logic-1 level as long as the enable signal remains at 0. This is the quiescent condition for the  $SR$  latch. When the enable input goes to 1, information from the  $S$  or  $R$  input is allowed to affect the latch. The set state is reached with  $S=1$ ,  $R=0$ , and  $En=1$  (active-high enabled). To change to the reset state, the inputs must be  $S=0$ ,  $R=1$ , and  $En=1$ . In either case, when  $En$  returns to 0, the circuit remains in its current state. The control input disables the circuit by applying 0 to  $En$ , so that the state of the output does not change regardless of the values of  $S$  and  $R$ . Moreover, when  $En=1$  and both the  $S$  and  $R$  inputs are equal to 0, the state of the circuit does not change. These conditions are listed in the function table accompanying the diagram.

 

## FIGURE 5.5

$SR$  latch with control input

### [Description](#)

An indeterminate condition occurs when all three inputs are equal to 1. This condition places 0's on both inputs of the basic  $SR$  latch, which puts it in the undefined state. When the enable input goes back to 0, one cannot conclusively determine the next state, because it depends on whether the  $S$  or  $R$  input goes to 0 first. This indeterminate condition makes this circuit difficult to manage, and it is seldom used in practice. Nevertheless, the  $SR$  latch is an important circuit because other useful latches and flip-flops are constructed from it.

## Practice Exercise 5.2

1. (a) What input condition puts an *SR NOR* latch into an indeterminate state?


**Answer:** Both inputs are 1.

2. (b) What input condition puts an *SR NAND* latch into an indeterminate state?

**Answer:** Both inputs are 0.
 
## D Latch (Transparent Latch)

One way to eliminate the undesirable condition of the indeterminate state in the *SR* latch is to ensure that inputs *S* and *R* are never equal to 1 at the same time. This is done in the *D* latch, shown in [Fig. 5.6](#). This latch has only two inputs: *D* (data) and *En* (enable). The *D* input goes directly to the *S* input, and its complement is applied to the *R* input. As long as the enable input is at 0, the cross-coupled *SR* latch has both inputs at the 1 level and the circuit cannot change state regardless of the value of *D*. The *D* input is sampled when *En*=1. If *D*=1, the *Q* output goes to 1, placing the circuit in the set state. If *D*=0, output *Q* goes to 0, placing the circuit in the reset state.



(a) Logic diagram

<i>En</i>	<i>D</i>	Next state of <i>Q</i>
0	X	No change
1	0	<i>Q</i> = 0; reset state
1	1	<i>Q</i> = 1; set state

(b) Function table


# FIGURE 5.6

## D latch
 
### [Description](#)

The *D* latch receives that designation from its ability to hold *data* in its internal storage. It is suited for use as a temporary storage for binary information between a unit and its environment. *The binary information present at the data input of the D latch is transferred to the Q output when the enable input is asserted.* The output follows changes in the data input as long as the enable input is asserted. This situation provides a path from input *D* to the output, and for this reason, the circuit is often called a *transparent* latch. When the enable input signal is de-asserted, the binary information that was present at the data input at the time the transition of *enable* occurred is retained (i.e., stored) at the *Q* output until the enable input is asserted again. Note that an inverter could be placed at the enable input. Then, depending on the physical circuit, the external enabling signal will be a value of 0 (active low) or 1 (active high).

The graphic symbols for the various latches are shown in [Fig. 5.7](#). A latch is designated by a rectangular block with inputs on the left and outputs on the right. One output designates the normal output, and the other (with the bubble designation) designates the complement output. The graphic symbol for the *SR* latch has inputs *S* and *R* indicated inside the block. In the case of a NAND gate latch, bubbles are added to the inputs to indicate that setting and resetting occur with a logic-0 signal. The graphic symbol for the *D* latch has inputs *D* and *En* indicated inside the block.



# FIGURE 5.7

Graphic symbols for latches

[Description](#)

## Practice Exercise 5.3

1. Describe the functionality of a transparent latch.

**Answer:** A transparent latch has a data input, an enable input, and output. When the enable input is asserted, the output of the latch follows the input to the latch. When the enable input is de-asserted, the output of the latch is held at the value that was present at the moment the enable input was de-asserted.


## 5.4 STORAGE ELEMENTS: FLIP-FLOPS

A change in the control input of a latch or flip-flop switches its state. This momentary change is called a *trigger*, and the transition it causes is said to trigger the flip-flop. The *D* latch with pulses in its control input is essentially a flip-flop that is triggered every time the pulse goes to the logic-1 level. As long as the pulse input remains at this level, any changes in the data input will change the output and the state of the latch.

As seen from the block diagram of [Fig. 5.2](#), a sequential circuit has a feedback path from the outputs of the flip-flops to the input of the combinational circuit. Consequently, the inputs of the flip-flops are derived in part from the outputs of the same and other flip-flops. When latches are used for the storage elements, a serious difficulty arises. The state transitions of the latches start as soon as the clock pulse changes to the logic-1 level. The new state of a latch appears at the output while the pulse is still active. This output is connected to the inputs of the latches through the combinational circuit. If the inputs applied to the latches change while the clock pulse is still at the logic-1 level, the latches will respond to new values and a new output state may occur. The result is an unpredictable situation, since the state of the latches may keep changing for as long as the clock pulse stays at the active level. Because of this unreliable operation, the output of a latch cannot be applied directly or through combinational logic to the input of the same or another latch when all the latches are triggered by a common clock source.

Flip-flop circuits are constructed in such a way as to make them operate properly when they are part of a sequential circuit that employs a common clock. The problem with the latch is that it responds to a change in the *level* of a clock pulse. As shown in [Fig. 5.8\(a\)](#), a positive level response in the enable input allows changes in the output when the *D* input changes while the clock pulse stays at logic 1. The key to the proper operation of a flip-flop is to trigger it only during a signal *transition*. This can be accomplished by eliminating the feedback path that is inherent in the operation of the sequential circuit using latches. A clock pulse goes through two transitions: from 0 to 1 and the return from 1 to 0. As shown

in [Fig. 5.8](#), the positive transition is defined as the positive edge and the negative transition as the negative edge. There are two ways that a latch can be modified to form a flip-flop. One way is to employ two latches in a special configuration that isolates the output of the flip-flop and prevents it from being affected while the input to the flip-flop is changing. Another way is to produce a flip-flop that triggers only during a signal transition (from 0 to 1 or from 1 to 0) of the synchronizing signal (clock) and is disabled during the rest of the clock pulse. We will now proceed to show the implementation of both types of flip-flops.

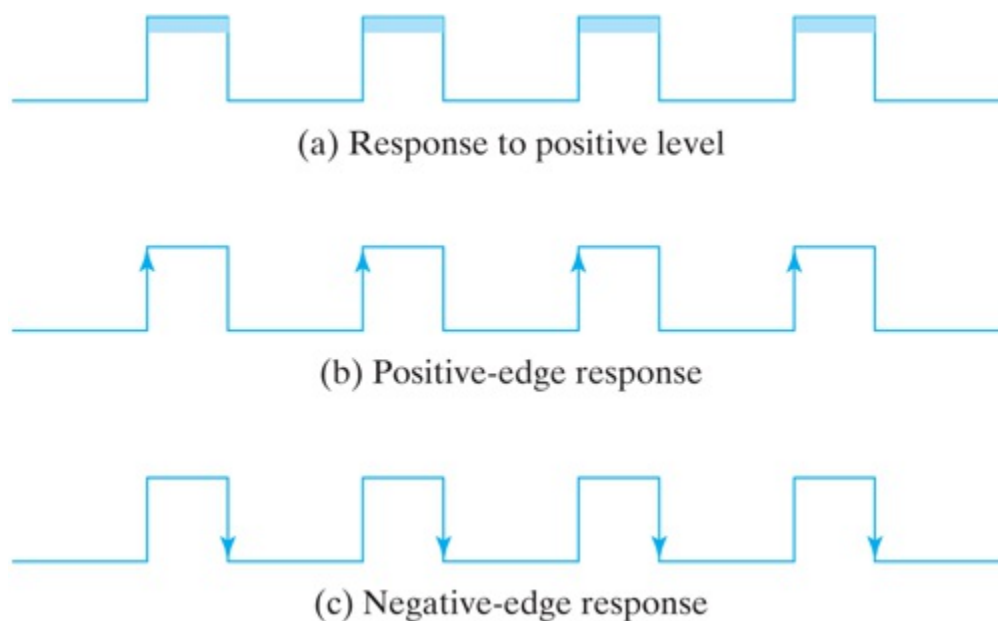

## FIGURE 5.8

Clock response in latch and flip-flop


[Description](#)
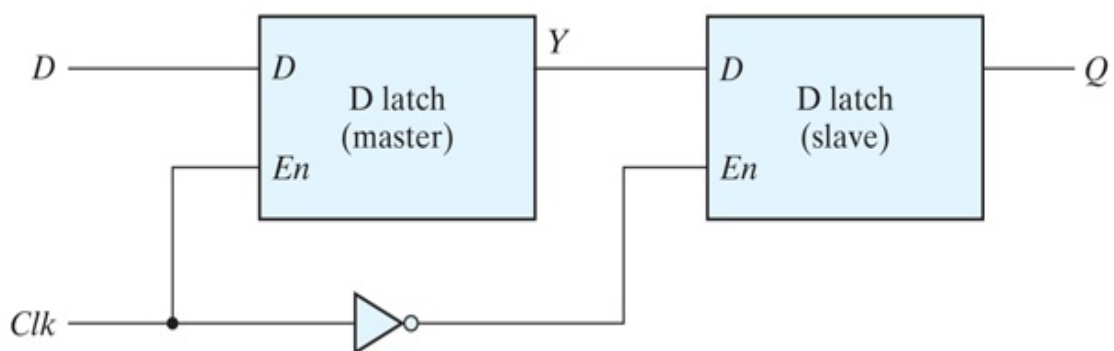
## Edge-Triggered *D* Flip-Flop

The construction of a *D* flip-flop with two *D* latches and an inverter is shown in [Fig. 5.9](#). It is often referred to as a master–slave flip-flop. The first latch is called the *master* and the second the *slave*. The circuit samples the *D* input and changes its output *Q* only at the negative edge of the synchronizing or controlling clock (designated as *Clk*). When *Clk* is 0, the



output of the inverter is 1. The slave latch is enabled, and its output  $Q$  is equal to the master output  $Y$ . The master latch is disabled because  $Clk=0$ . When the input ( $Clk$ ) pulse changes to the logic-1 level, the data from the external  $D$  input are transferred to the master. The slave, however, is disabled as long as the clock remains at the 1 level, because its *enable* input is equal to 0. Any change in the input changes the master output at  $Y$ , but cannot affect the slave output. When the clock pulse returns to 0, the master is disabled and is isolated from the  $D$  input. At the same time, the slave is enabled and the value of  $Y$  is transferred to the output of the flip-flop at  $Q$ . Thus, *a change in the output of the flip-flop can be triggered only by and during the transition of the clock from 1 to 0.*




## FIGURE 5.9

Master–slave  $D$  flip-flop

The behavior of the master–slave flip-flop just described dictates that (1) the output may change only once, (2) a change in the output is triggered by the negative edge of the clock, and (3) the change may occur only during the clock's negative level. The value that is produced at the output of the flip-flop is the value that was *stored in the master stage immediately before the negative edge occurred*. It is also possible to design the circuit so that the flip-flop output changes on the positive edge of the clock. This happens in a flip-flop that has an additional inverter between the  $Clk$  terminal and the junction between the other inverter and input  $En$  of the master latch. Such a flip-flop is triggered with a negative pulse, so that the negative edge of the clock affects the master and the positive edge affects the slave and the output terminal.

Another construction of an edge-triggered  $D$  flip-flop uses three  $SR$  latches

as shown in [Fig. 5.10](#). Two latches respond to the external  $D$  (data) and  $Clk$  (clock) inputs. The third latch provides the outputs for the flip-flop. The  $S$  and  $R$  inputs of the output latch are maintained at the logic-1 level when  $Clk=0$ . This causes the output to remain in its present state. Input  $D$  may be equal to 0 or 1. If  $D=0$  when  $Clk$  becomes 1,  $R$  changes to 0. This causes the flip-flop to go to the reset state, making  $Q=0$ . If there is a change in the  $D$  input while  $Clk=1$ , terminal  $R$  remains at 0 because  $Q$  is 0. Thus, the flip-flop is locked out and is unresponsive to further changes in the input. When the clock returns to 0,  $R$  goes to 1, placing the output latch in the quiescent condition without changing the output. Similarly, if  $D=1$  when  $Clk$  goes from 0 to 1,  $S$  changes to 0. This causes the circuit to go to the set state, making  $Q=1$ . Any change in  $D$  while  $Clk=1$  does not affect the output.

 

**FIGURE 5.10**


*D*-type positive-edge-triggered flip-flop

## Description

In sum, when the input clock in the positive-edge-triggered flip-flop makes a positive transition, the value of  $D$  is transferred to  $Q$ . A negative transition of the clock (i.e., from 1 to 0) does not affect the output, nor is the output affected by changes in  $D$  when  $Clk$  is in the steady logic-1 level or the logic-0 level. Hence, this type of flip-flop responds to the transition from 0 to 1 and nothing else.

The timing of the response of a flip-flop to input data and to the clock must be taken into consideration when one is using edge-triggered flip-flops. There is a minimum time called the *setup time* during which the  $D$  input must be maintained at a constant value prior to the occurrence of the clock transition. Similarly, there is a minimum time called the *hold time* during which the  $D$  input must not change after the application of the positive transition of the clock. The propagation delay time of the flip-flop is defined as the interval between the trigger edge and the stabilization of the output to a new state. These and other parameters are specified in manufacturers' data books for specific logic families.

The graphic symbol for the edge-triggered  $D$  flip-flop is shown in [Fig. 5.11](#). It is similar to the symbol used for the  $D$  latch, except for the arrowhead-like symbol in front of the letter  $Clk$ , designating a *dynamic* input. The *dynamic indicator* ( $>$ ) denotes the fact that the flip-flop responds to the edge transition of the clock. A bubble outside the block adjacent to the dynamic indicator designates a negative edge for triggering the circuit. The absence of a bubble designates a positive-edge response.

 

# FIGURE 5.11

Graphic symbol for edge-triggered  $D$  flip-flop

[Description](#)

## Practice Exercise 5.4


1. What is meant by “a positive-edge flip-flop?”

**Answer:** A positive-edge flip-flop is one that is activated by the rising (positive) edge of the clock (synchronizing signal).
 
## Other Flip-Flops

Very large-scale integrated circuits contain several thousands of gates within one package. Circuits are constructed by interconnecting the various gates to provide a digital system. Each flip-flop is constructed from an interconnection of gates. The most economical and efficient flip-flop constructed in this manner is the edge-triggered  $D$  flip-flop, because it requires the smallest number of gates. Other types of flip-flops can be constructed by using the  $D$  flip-flop and external logic. Two flip-flops less widely used in the design of digital systems are the  $JK$  and  $T$  flip-flops.

There are three operations that can be performed with a flip-flop: Set it to 1, reset it to 0, or complement its output. With only a single input, the  $D$  flip-flop can set or reset the output, depending on the value of the  $D$  input immediately before the clock transition. Synchronized by a clock signal, the  $JK$  flip-flop has two inputs and performs all three operations. The circuit diagram of a  $JK$  flip-flop constructed with a  $D$  flip-flop and gates is shown in [Fig. 5.12\(a\)](#). The  $J$  input sets the flip-flop to 1, the  $K$  input resets it to 0, and when both inputs are enabled, the output is complemented. This can be verified by investigating the circuit applied to the  $D$  input:



## FIGURE 5.12


*JK* flip-flop

### Description

$$D = JQ' + K'Q$$

When  $J=1$  and  $K=0$ ,  $D=Q'+Q=1$ , so the next clock edge sets the output to 1. When  $J=0$  and  $K=1$ ,  $D=0$ , so the next clock edge resets the output to 0. When both  $J=K=1$  and  $D=Q'$  the next clock edge complements the output. When both  $J=K=0$  and  $D=Q$ , the clock edge leaves the output unchanged. The graphic symbol for the *JK* flip-flop is shown in [Fig. 5.12\(b\)](#). It is similar to the graphic symbol of the *D* flip-flop, except that now the inputs are marked *J* and *K*.

 The *T* (toggle) flip-flop is a complementing flip-flop and can be obtained from a *JK* flip-flop when inputs *J* and *K* are tied together. This is shown in [Fig. 5.13\(a\)](#). When  $T=0$  ( $J=K=0$ ), a clock edge does not change the output. When  $T=1$  ( $J=K=1$ ), a clock edge complements the output. The complementing flip-flop is useful for designing binary counters.



## FIGURE 5.13

*T* flip-flop

### Description

The *T* flip-flop can be constructed with a *D* flip-flop and an exclusive-OR gate as shown in [Fig. 5.13\(b\)](#). The expression for the *D* input is

$$D = T \oplus Q = TQ' + T'Q$$

When  $T=0$ ,  $D=Q$  and there is no change in the output. When  $T=1$ ,  $D=Q'$  and the output complements. The graphic symbol for this flip-flop has a *T* symbol in the input.

## Characteristic Tables

A characteristic table defines the logical properties of a flip-flop by describing its operation in tabular form. The characteristic tables of three types of flip-flops are presented in [Table 5.1](#). They define the next state (i.e., the state that results from a clock transition) as a function of the inputs and the present state.  $Q(t)$  refers to the present state (i.e., the state present prior to the application of a clock edge).  $Q(t+1)$  is the next state one clock period later. Note that the clock edge input is not included in the characteristic table, but is implied to occur between times  $t$  and  $t+1$ . Thus,  $Q(t)$  denotes the state of the flip-flop immediately before the clock edge, and  $Q(t+1)$  denotes the state that results from the clock transition.

# Table 5.1 *Flip-Flop Characteristic Tables*

## *JK Flip-Flop*

*J K Q(t+1)*

0 0  $Q(t)$     No change

0 1 0        Reset

1 0 1        Set

1 1  $Q'(t)$     Complement

<i>D Flip-Flop</i>			<i>T Flip-Flop</i>		
<i>D</i>	$Q(t+1)$		<i>T</i>	$Q(t+1)$	
0	0	Reset	0	$Q(t)$	No change
1	1	Set	1	$Q'(t)$	Complement

The characteristic table for the *JK* flip-flop shows that the next state is equal to the present state when inputs *J* and *K* are both equal to 0. This condition can be expressed as  $Q(t+1)=Q(t)$ , indicating that the clock produces no change of state. When  $K=1$  and  $J=0$ , the clock resets the flip-

flop and  $Q(t+1)=0$ . With  $J=1$  and  $K=0$ , the flip-flop sets and  $Q(t+1)=1$ . When both  $J$  and  $K$  are equal to 1, the next state changes to the complement of the present state, a transition that can be expressed as  $Q(t+1)=Q'(t)$ .

The next state of a  $D$  flip-flop is dependent on only the  $D$  input and is independent of the present state. This can be expressed as  $Q(t+1)=D$ . It means that the next-state value is equal to the value of  $D$ . Note that the  $D$  flip-flop does not have a “no-change” condition. Such a condition can be accomplished either by disabling the clock or by operating the clock by having the output of the flip-flop connected into the  $D$  input. Either method effectively circulates the output of the flip-flop when the state of the flip-flop must remain unchanged.

The characteristic table of the  $T$  flip-flop has only two conditions: When  $T=0$ , the clock edge does not change the state; when  $T=1$ , the clock edge complements the state of the flip-flop.

## Characteristic Equations

The logical properties of a flip-flop, as described in the characteristic table, can be expressed algebraically with a characteristic equation. For the  $D$  flip-flop, we have the characteristic equation

$$Q(t+1)=D$$

which states that the next state of the output will be equal to the value of input  $D$  in the present state. The characteristic equation for the  $JK$  flip-flop can be derived from the characteristic table or from the circuit of [Fig. 5.12](#). We obtain

$$Q(t+1)=JQ'+K'Q$$

where  $Q$  is the value of the flip-flop output prior to the application of a clock edge. The characteristic equation for the  $T$  flip-flop is obtained from the circuit of [Fig. 5.13](#):



$$Q(t+1)=T\oplus Q=TQ'+T'Q$$


 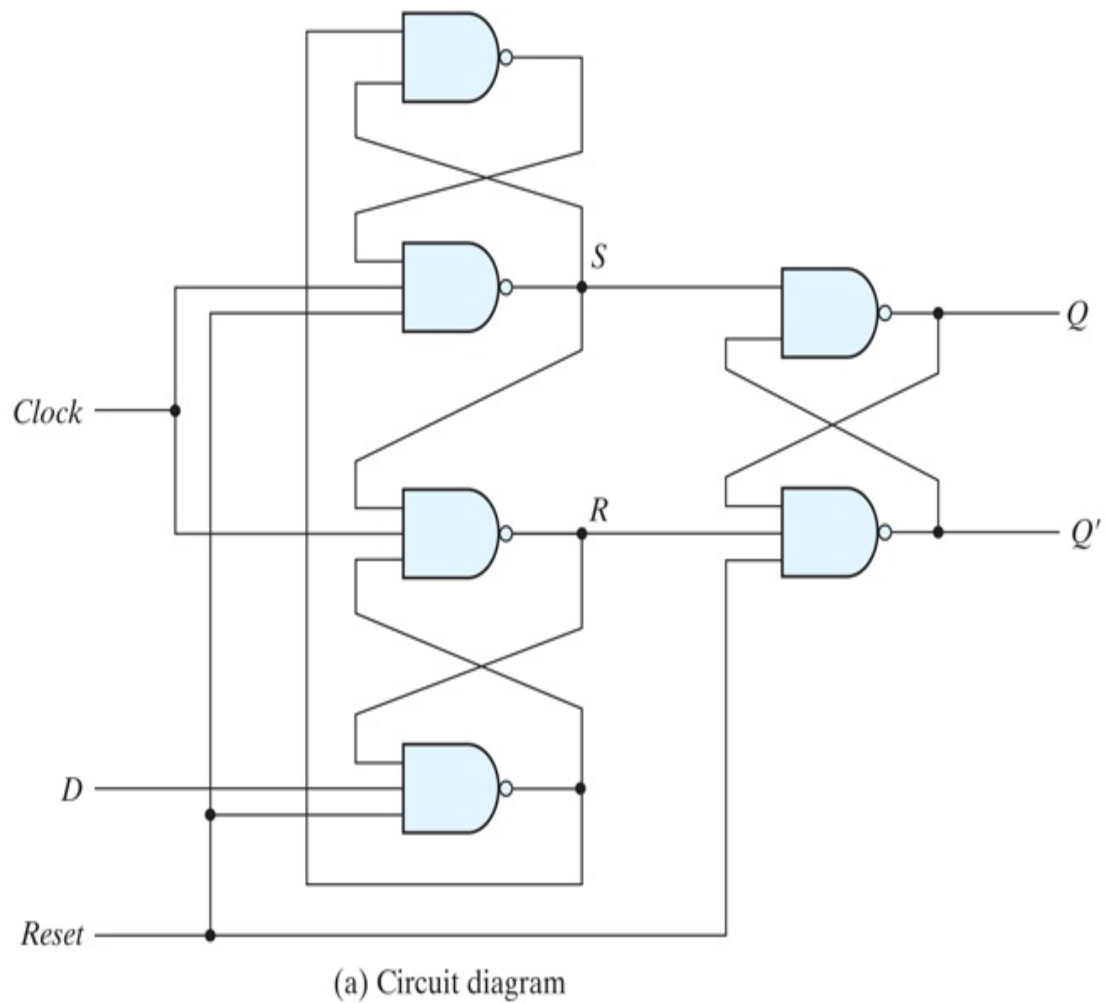
# Direct Inputs

Some flip-flops have asynchronous inputs that are used to force the flip-flop to a particular state independently of the clock. The input that sets the flip-flop to 1 is called *preset* or *direct set*. The input that clears the flip-flop to 0 is called *clear* or *direct reset*. When power is turned on in a digital system, the state of the flip-flops is unknown. The direct inputs are useful for bringing all flip-flops in the system to a known starting state prior to the clocked operation.

A positive-edge-triggered *D* flip-flop with active-low asynchronous reset is shown in [Fig. 5.14](#). The circuit diagram is the same as the one in [Fig. 5.10](#), except for the additional reset input connections to three NAND gates. When the reset input is 0, it forces output  $Q'$  to stay at 1, which, in turn, clears output  $Q$  to 0, thus resetting the flip-flop. Two other connections from the reset input ensure that the  $S$  input of the third *SR* latch stays at logic 1 while the reset input is at 0, regardless of the values of  $D$  and  $Clk$ .



R	Clk	D	Q	Q'
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

(c) Function table

# FIGURE 5.14

D flip-flop with asynchronous reset

## Description

The graphic symbol for the *D* flip-flop with a direct reset has an additional input marked with *R*. The bubble along the input indicates that the reset is active at the logic-0 level. Flip-flops with a direct set use the symbol *S* for the asynchronous set input.

The function table specifies the operation of the circuit. When  $R=0$ , the output is reset to 0. This state is independent of the values of *D* or *Clk*. Normal clock operation can proceed only after the reset input goes to logic 1. The clock at *Clk* is shown with an upward arrow to indicate that the flip-flop triggers on the positive edge of the clock. The value in *D* is transferred to *Q* with every positive-edge clock signal, provided that  $R=1$ .

## Practice Exercise 5.5

1. Describe the functionality of a *D*-type flip-flop.

**Answer:** A *D*-type flip-flop has a *D* (data) input, a clock input, and possibly asynchronous or synchronous clear (reset) or set signal. If *set* or *clear* are not asserted, the clock signal synchronizes the transfer of *D* to *Q*, the output. If *set* or *reset* are asynchronous, their action controls the flip-flop independently of the clock. *set* causes the output to be 1; *reset* causes the output to be 0. If *set* or *reset* are synchronous, their action has effect at the synchronizing edge of the clock.

## 5.5 ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS


Analysis describes what a given circuit will do under certain operating conditions. The behavior of a clocked sequential circuit is determined from the inputs, the outputs, and the state of its flip-flops. The outputs and the next state are both a function of the inputs and the present state. The analysis of a sequential circuit consists of obtaining a table or a diagram for the time sequence of inputs, outputs, and internal states. It is also possible to write Boolean expressions that describe the behavior of the sequential circuit. These expressions must include the necessary time sequence, either directly or indirectly.

A logic diagram is recognized as a clocked sequential circuit if it includes flip-flops with clock inputs. The flip-flops may be of any type, and the logic diagram may or may not include combinational logic gates. In this section, we introduce an algebraic representation for specifying the next-state condition in terms of the present state and inputs. A state table and state diagram are then presented to describe the behavior of the sequential circuit. Another algebraic representation is introduced for specifying the logic diagram of sequential circuits. Examples are used to illustrate the various procedures.

### State Equations

The behavior of a clocked sequential circuit can be described algebraically by means of state equations. A *state equation* (also called a *transition equation*) specifies the next state as a function of the present state and inputs. Consider the sequential circuit shown in [Fig. 5.15](#). We will later show that it acts as a 0-detector by asserting its output when a 0 is detected in a stream of 1's. It consists of two *D* flip-flops *A* and *B*, an input *x* and an output *y*. Since the *D* input of a flip-flop determines the value of the next state (i.e., the state reached after the clock transition), it is possible to write a set of state equations directly from the logic diagram in [Fig. 5.151](#):

<sup>1</sup> Here the + symbol denotes the logical OR operator; the logical AND operator is not shown explicitly (e.g.,  $Bx$  is the result of ANDing  $B$  with  $x$ ).

 

**FIGURE 5.15**

Example of sequential circuit

Description

$$A(t+1) = A(t)x(t) + B(t)x(t) \quad B(t+1) = A'(t)x(t)$$

A state equation is an algebraic expression that specifies the condition for

a flip-flop state transition. The left side of the equation, with  $(t+1)$ , denotes the next state of the flip-flop one clock edge later. The right side of the equation is a Boolean expression that specifies the present state and input conditions that make the next state equal to 1. Since all the variables in the Boolean expressions are a function of the present state, we can omit the designation  $(t)$  after each variable for convenience and can express the state equations in the more compact form

$$A(t+1)=Ax+Bx \quad B(t+1)=A'x$$

The Boolean expressions for the state equations can be derived directly from the gates that form the combinational circuit part of the sequential circuit, since the  $D$  values of the combinational circuit determine the next state. Similarly, the present-state value of the output can be expressed algebraically as

$$y(t)=[A(t)+B(t)]x'(t)$$

By removing the symbol  $(t)$  for the present state, we obtain the output Boolean equation:

$$y=(A+B)x'$$

## State Table

The time sequence of inputs, outputs, and flip-flop states can be enumerated in a *state table* (sometimes called a *transition table*). The state table for the circuit of [Fig. 5.15](#) is shown in [Table 5.2](#). The table consists of four sections labeled *present state*, *input*, *next state*, and *output*. The present-state section shows the states of flip-flops  $A$  and  $B$  at any given time  $t$ . The input section gives a value of  $x$  for each possible present state. The next-state section shows the states of the flip-flops one clock cycle later, at time  $t+1$ . The output section gives the value of  $y$  at time  $t$  for each present state and input condition.

### **Table 5.2 *State Table for the Circuit of [Fig. 5.15](#)***

### Present State Input Next State Output

<i>A</i>	<i>B</i>	<i>x</i>	<i>A</i>	<i>B</i>	<i>y</i>
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

The derivation of a state table requires listing all possible binary combinations of present states and inputs. In this case, we have eight binary combinations from 000 to 111. The next-state values are then determined from the logic diagram or from the state equations. The next state of flip-flop *A* must satisfy the state equation

$$A(t+1) = Ax + Bx$$

In words: the next state of *A* is formed by ORing (1) the result of ANDing the present state of *A* with the input (*Ax*), with (2) the result of ANDing the

present state of  $B$  with the input ( $Bx$ ).

The next-state section in the state table under column  $A$  has three 1's where the present state of  $A$  and input  $x$  are both equal to 1 or the present state of  $B$  and input  $x$  are both equal to 1. Similarly, the next state of flip-flop  $B$  is derived from the state equation

$$B(t+1) = A'x$$

and is equal to 1 when the present state of  $A$  is 0 and input  $x$  is equal to 1. The output column is derived from the output equation

$$y = Ax' + Bx'$$

The state table of a sequential circuit with  $D$ -type flip-flops is obtained by the same procedure outlined in the previous example. In general, a sequential circuit with  $m$  flip-flops and  $n$  inputs needs  $2^{m+n}$  rows in the state table. The binary numbers from 0 through  $2^{m+n}-1$  are listed under the present state and input columns. The next-state section has  $m$  columns, one for each flip-flop. The binary values for the next state are derived directly from the state equations. The output section has as many columns as there are output variables. Its binary value is derived from the circuit or from the Boolean function in the same manner as in a truth table.

It is sometimes convenient to express the state table in a slightly different form having only three sections: present state, next state, and output. The input conditions are enumerated under the next-state and output sections. The state table of [Table 5.2](#) is repeated in [Table 5.3](#) in this second form. For each present state, there are two possible next states and outputs, depending on the value of the input. One form may be preferable to the other, depending on the application.

## Table 5.3 *Second Form of the State Table*

	Next State	Output
Present State		




	x=0 x=1		x=0 x=1	
A	B	A B A B	y	y
0	0	0 0 0 1	0	0
0	1	0 0 1 1	1	0
1	0	0 0 1 0	1	0
1	1	0 0 1 0	1	0
 
## State Diagram

The information available in a state table can be represented graphically in the form of a state diagram. In this type of diagram, a state is represented by a circle, and the (clock-triggered) transitions between states are indicated by directed lines connecting the circles. Each line originates at a present state and terminates at a next state, depending on the input applied when the circuit is in the present state. The state diagram of the sequential circuit of [Fig. 5.15](#) is shown in [Fig. 5.16](#). The state diagram provides the same information as the state table and is obtained directly from [Table 5.2](#) or [Table 5.3](#). The binary number inside each circle identifies the state of the flip-flops. The directed lines are labeled with two binary numbers separated by a slash. The input value during the present state is labeled first, and the number after the slash gives the output during the *present* state with the given input. (It is important to remember that the bit value listed for the output along the directed line occurs during the present state and with the indicated input, and has nothing to do with the transition to the next state.) For example, the directed line from state 00 to 01 is labeled 1/0, meaning that when the sequential circuit is in the present state 00 and the input is 1, the output is 0. After the next clock cycle, the circuit goes to the next state, 01, as determined by the directed edge from 00 to 01. If the

input changes to 0, then the output becomes 1, but if the input remains at 1, the output stays at 0. This information is obtained from the state diagram along the two directed lines emanating from the circle with state 01. A directed line connecting a circle with itself indicates that no change of state occurs.



# FIGURE 5.16

State diagram of the circuit of [Fig. 5.15](#)

## Description

The steps presented in this example are summarized below:

Circuit diagram → Equations → State table → State diagram

This sequence of steps begins with a structural representation of the circuit and proceeds to an abstract representation of its behavior. An HDL model can be in the form of a gate-level description or in the form of a behavioral description.

It is important to note that a gate-level approach requires that the designer understands how to select and connect gates and flip-flops to form a circuit having a particular behavior. That understanding comes with experience. On the other hand, an approach based on behavioral modeling does not require the designer to know how to invent a schematic—the designer needs only to know how to describe behavior using the constructs of the

HDL, because the circuit can be produced automatically by a synthesis tool. Therefore, one does not have to accumulate years of experience in order to become a productive designer of digital circuits; nor does one have to first acquire an extensive background in electrical engineering.

There is no difference between a state table and a state diagram, except in the manner of representation. The state table is easier to derive from a given logic diagram and the state equation. The state diagram follows directly from the state table. *The state diagram gives a pictorial view of state transitions and is the form more suitable for human interpretation of the circuit's operation.* For example, the state diagram of [Fig. 5.16](#) clearly shows that, starting from state 00, the output is 0 as long as the input stays at 1. The first 0 input after a string of 1's gives an output of 1 and transfers the circuit back to the initial state, 00. The machine represented by this state diagram acts to detect a zero in the bit stream of data. It corresponds to the behavior of the circuit in [Fig. 5.15](#). Other circuits that detect a zero in a stream of data may have a simpler circuit diagram and state diagram.

## Flip-Flop Input Equations

The logic diagram of a sequential circuit consists of flip-flops and gates. The interconnections among the gates form a combinational circuit and may be specified algebraically with Boolean expressions. The knowledge of the type of flip-flops and a list of the Boolean expressions of the combinational circuit provide the information needed to draw the logic diagram of the sequential circuit. The part of the combinational circuit that generates external outputs is described algebraically by a set of Boolean functions called *output equations*. The part of the circuit that generates the inputs to flip-flops is described algebraically by a set of Boolean functions called *flip-flop input equations* (or, sometimes, *excitation equations*). We will adopt the convention of using the flip-flop input symbol to denote the input equation variable and a subscript to designate the name of the flip-flop output. For example, the following input equation specifies an OR gate with inputs  $x$  and  $y$  connected to the  $D$  input of a flip-flop whose output is labeled with the symbol  $Q$ :

$$DQ = x + y$$

The sequential circuit of [Fig. 5.15](#) consists of two  $D$  flip-flops  $A$  and  $B$ , an

input  $x$ , and an output  $y$ . The logic diagram of the circuit can be expressed algebraically with two flip-flop input equations and an output equation:

$$DA = Ax + Bx \quad DB = A'x \quad y = (A + B)x'$$

The three equations provide the necessary information for drawing the logic diagram of the sequential circuit. The symbol  $DA$  specifies the data input of a  $D$  flip-flop labeled  $A$ .  $DB$  specifies the data input of a second  $D$  flip-flop labeled  $B$ . The Boolean expressions associated with these two variables and the expression for output  $y$  specify the combinational circuit part of the sequential circuit.


The flip-flop input equations constitute a convenient algebraic form for specifying the logic diagram of a sequential circuit. They imply the type of flip-flop from the letter symbol, and they fully specify the combinational circuit that drives the flip-flops. Note that the expression for the input equation for a  $D$  flip-flop is identical to the expression for the corresponding state equation. This is because of the characteristic equation that equates the next state to the value of the  $D$  input:  $Q(t+1) = DQ$ .

## Analysis with $D$ Flip-Flops

We will summarize the procedure for analyzing a clocked sequential circuit with  $D$  flip-flops by means of a simple example. The circuit we want to analyze is described by the input equation

$$DA = A \oplus x \oplus y$$

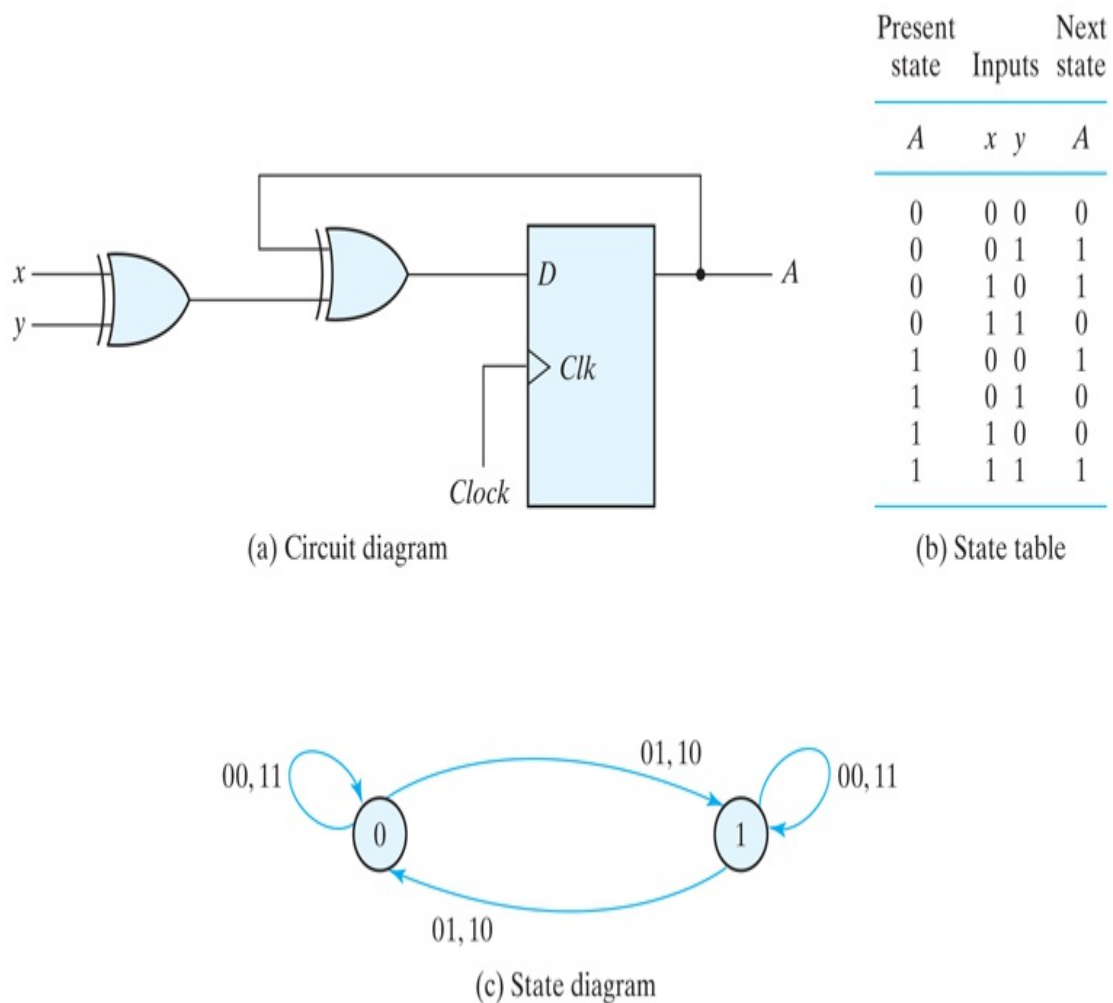The  $DA$  symbol implies a  $D$  flip-flop with output  $A$ . The  $x$  and  $y$  variables are the inputs to the circuit. No output equations are given, which implies that the output comes from the output of the flip-flop. The logic diagram is obtained from the input equation and is drawn in [Fig. 5.17\(a\)](#).



# FIGURE 5.17

Sequential circuit with *D* flip-flop

## Description

The state table has one column for the present state of flip-flop *A*, two columns for the two inputs, and one column for the next state of *A*. The binary numbers under *Axy* are listed from 000 through 111 as shown in [Fig. 5.17\(b\)](#). The next-state values are obtained from the state equation

$$A(t+1) = A \oplus x \oplus y$$

The expression specifies an odd function and is equal to 1 when only one variable is 1 or when all three variables are 1. This is indicated in the column for the next state of *A*.

The circuit has one flip-flop and two states. The state diagram consists of two circles, one for each state as shown in [Fig. 5.17\(c\)](#). The present state and the output can be either 0 or 1, as indicated by the number inside the circles. A slash on the directed lines is not needed, because there is no output from a combinational circuit. The two inputs can have four possible combinations for each state. Two input combinations during each state transition are separated by a comma to simplify the notation.

## Practice Exercise 5.6

1. What determines the next state of a  $D$ -type flip-flop?

**Answer:** The next state of a  $D$ -type flip-flop is the value of  $D$  at the synchronizing edge of the clock.


## Analysis with $JK$ Flip-Flops

A state table consists of four sections: present state, inputs, next state, and outputs. The first two are obtained by listing all binary combinations. The output section is determined from the output equations. The next-state values are evaluated from the state equations. For a  $D$ -type flip-flop, the state equation is the same as the input equation. When a flip-flop other than the  $D$  type is used, such as  $JK$  or  $T$ , it is necessary to refer to the corresponding characteristic table or characteristic equation to obtain the next-state values. We will illustrate the procedure first by using the characteristic table and again by using the characteristic equation.

The next-state values of a sequential circuit that uses  $JK$ - or  $T$ -type flip-flops can be derived as follows:

1. Determine the flip-flop input equations in terms of the present state and input variables.
2. List the binary values of each input equation.
3. Use the corresponding flip-flop characteristic table to determine the next-state values in the state table.

As an example, consider the sequential circuit with two *JK* flip-flops *A* and *B* and one input *x*, as shown in [Fig. 5.18](#). The circuit has no outputs; therefore, the state table does not need an output column. (The outputs of the flip-flops may be considered as the outputs in this case.) The circuit can be specified by the flip-flop input equations

 

**FIGURE 5.18**

Sequential circuit with *JK* flip-flop

Description

$$JA=B \quad KA=Bx' \quad JB=x' \quad KB=A'x+Ax'=A\oplus x$$

The state table of the sequential circuit is shown in [Table 5.4](#). The present state and input columns list the eight binary combinations. The binary values listed under the columns labeled *flip-flop inputs* are not part of the state table, but they are needed for the purpose of evaluating the next state as specified in step 2 of the procedure. These binary values are obtained directly from the four input equations in a manner similar to that for

obtaining a truth table from a Boolean expression. The next state of each flip-flop is evaluated from the corresponding  $J$  and  $K$  inputs and the characteristic table of the  $JK$  flip-flop listed in [Table 5.1](#). There are four cases to consider. When  $J=1$  and  $K=0$ , the next state is 1. When  $J=0$  and  $K=1$ , the next state is 0. When  $J=K=0$ , there is no change of state and the next-state value is the same as that of the present state. When  $J=K=1$ , the next-state bit is the complement of the present-state bit. Examples of the last two cases occur in the table when the present state  $AB$  is 10 and input  $x$  is 0.  $JA$  and  $KA$  are both equal to 0 and the present state of  $A$  is 1. Therefore, the next state of  $A$  remains the same and is equal to 1. In the same row of the table,  $JB$  and  $KB$  are both equal to 1. Since the present state of  $B$  is 0, the next state of  $B$  is complemented and changes to 1.

**Table 5.4 *State Table for Sequential Circuit with JK Flip-Flops***

**Present State Input Next State Flip-Flop Inputs**

$A$	$B$	$x$	$A$	$B$	$JA$	$KA$	$JB$	$KB$
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1



1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

The next-state values can also be obtained by evaluating the state equations from the characteristic equation. This is done by using the following procedure:

1. Determine the flip-flop input equations in terms of the present state and input variables.
2. Substitute the input equations into the flip-flop characteristic equation to obtain the state equations.
3. Use the corresponding state equations to determine the next-state values in the state table.

The input equations for the two *JK* flip-flops of [Fig. 5.18](#) were listed a couple of paragraphs ago. The characteristic equations for the flip-flops are obtained by substituting *A* or *B* for the name of the flip-flop, instead of *Q*:

$$A(t+1) = JA' + K'AB \quad B(t+1) = JB' + K'B$$

Substituting the values of *JA* and *KA* from the input equations, we obtain the state equation for *A*:


$$A(t+1) = BA' + (Bx')'A = A'B + AB' + Ax$$

The state equation provides the bit values for the column headed “Next State” for *A* in the state table. Similarly, the state equation for flip-flop *B* can be derived from the characteristic equation by substituting the values of *JB* and *KB* :

$$B(t+1) = x'B' + (A \oplus x)'B = B'x' + ABx + A'Bx'$$

The state equation provides the bit values for the column headed “Next State” for  $B$  in the state table. Note that the columns in [Table 5.4](#) headed “Flip-Flop Inputs” are not needed when state equations are used.

The state diagram of the sequential circuit is shown in [Fig. 5.19](#). Note that since the circuit has no outputs, the directed lines out of the circles are marked with one binary number only, to designate the value of input  $x$ .

 

**FIGURE 5.19**

State diagram of the circuit of [Fig. 5.18](#)

[Description](#)

## Practice Exercise 5.7

1. What determines the next state of a  $JK$ -type flip-flop?


**Answer:** The next state of a  $JK$ -type flip-flop is determined by the value of inputs  $J$  and  $K$  at the synchronizing edge of the clock.

## Analysis with $T$ Flip-Flops

The analysis of a sequential circuit with  $T$  flip-flops follows the same procedure outlined for  $JK$  flip-flops. The next-state values in the state table can be obtained by using either the characteristic table listed in [Table 5.1](#) or the characteristic equation

$$Q(t+1) = T \oplus Q = T'Q + TQ'$$

Now consider the sequential circuit shown in [Fig. 5.20](#). It has two flip-flops  $A$  and  $B$ , one input  $x$ , and one output  $y$  and can be described algebraically by two input equations and an output equation:

 

**FIGURE 5.20**

Sequential circuit with  $T$  flip-flops (Binary Counter)

### Description

$$TA = Bx \quad TB = x \quad y = AB$$

The state table for the circuit is listed in [Table 5.5](#). The values for  $y$  are obtained from the output equation. The values for the next state can be derived from the state equations by substituting  $TA$  and  $TB$  in the characteristic equations, yielding

**Table 5.5 *State Table for Sequential Circuit with T Flip-Flops***

**Present State Input Next State Output**

<i>A</i>	<i>B</i>	<i>x</i>	<i>A</i>	<i>B</i>	<i>y</i>
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0

1	1	0	1	1	1
1	1	1	0	0	1


$$A(t+1) = (Bx)'A + (Bx)A' = AB' + Ax' + A'Bx \quad B(t+1) = x \oplus B$$

The next-state values for  $A$  and  $B$  in the state table are obtained from the expressions of the two state equations.

The state diagram of the circuit is shown in [Fig. 5.20\(b\)](#). As long as input  $x$  is equal to 1, the circuit behaves as a binary counter with a sequence of states 00, 01, 10, 11, and back to 00. When  $x=0$ , the circuit remains in the same state. Output  $y$  is equal to 1 when the present state is 11. Here, the output depends on the present state only and is independent of the input. The two values inside each circle and separated by a slash are for the present state and output.

## Mealy and Moore Models of Finite State Machines

The most general model of a sequential circuit has inputs, outputs, and internal states. It is customary to distinguish between two models of sequential circuits: the Mealy model and the Moore model. Both are shown in [Fig. 5.21](#). They differ only in the way the output is generated. In the Mealy model, the output is a function of both the present state and the input. In the Moore model, the output is a function of only the present state. A circuit may have both types of outputs. The two models of a sequential circuit are commonly referred to as a *finite state machine*, abbreviated FSM. The Mealy model of a sequential circuit is referred to as a Mealy FSM or Mealy machine. The Moore model is referred to as a Moore FSM or Moore machine.

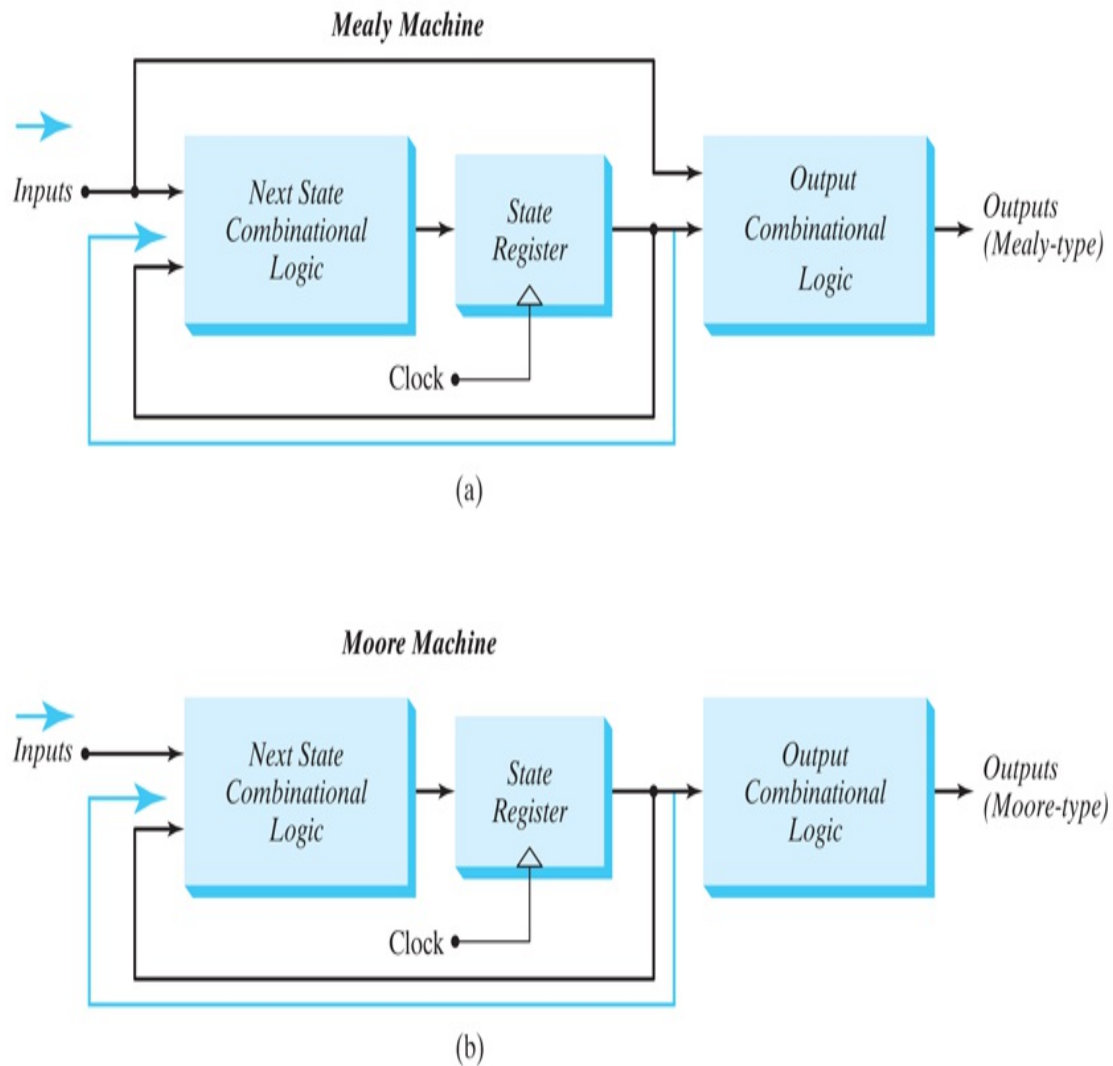

**FIGURE 5.21**

Block diagrams of Mealy and Moore state machines

[Description](#)

## Practice Exercise 5.8

1. What determines the next state of a *T*-type flip-flop?

**Answer:** If the *T* input is asserted, the next state is the complement of the present state (output) at the synchronizing edge of the clock. If *T* is not asserted, the state remains fixed.

The circuit presented previously in [Fig. 5.15](#) is an example of a Mealy machine. Output  $y$  is a function of both input  $x$  and the present state of  $A$  and  $B$ . The corresponding state diagram in [Fig. 5.16](#) shows both the input and output values, separated by a slash along the directed lines between the states.

An example of a Moore model is given in [Fig. 5.18](#). Here, the output is a function of the present state only. The corresponding state diagram in [Fig. 5.19](#) has only inputs marked along the directed lines. The outputs are the flip-flop states marked inside the circles. Another example of a Moore model is the sequential circuit of [Fig. 5.20](#). The output depends only on flip-flop values, and that makes it a function of the present state only. The input value in the state diagram is labeled along the directed line, whereas the output value is indicated inside the circle together with the present state.

**In a Moore model, the outputs of the sequential circuit are synchronized with the clock, because they depend only on flip-flop outputs, which are synchronized with the clock.** In a Mealy model, the outputs may change if the inputs change during the clock cycle. Moreover, the outputs may have momentary false values because of the delay encountered from the time that the inputs change and the time that the flip-flop outputs change to their final values. In order to synchronize a Mealy-type circuit, the inputs of the sequential circuit must be synchronized with the clock and the outputs must be sampled immediately before the clock edge. The inputs are changed at the inactive edge of the clock to ensure that the inputs to the flip-flops stabilize before the active edge of the clock occurs. Thus, **the output of the Mealy machine is the value that is present immediately before the active edge of the clock.**

## Practice Exercise 5.9

1. What is the difference between a Mealy and Moore state machine?

**Answer:** The output of a Moore state machine depends on only the state of the machine; the output of a Mealy machine depends on the present state and the inputs to the machine.

## Practice Exercise 5.10

1. What does an edge of a state machine chart represent?

**Answer:** The edge of a state machine chart represents a transition of the machine between two states.

## Practice Exercise 5.11

1. In a synchronous finite state machine, when does a transition between states occur?

**Answer:** A transition between the states of a finite state machine occurs at the active edge of the synchronizing signal (clock).

## Practice Exercise 5.12

1. What kinds of reset may a finite state machine have?

**Answer:** A finite state machine may have synchronous or asynchronous reset.

## Practice Exercise 5.13

1. Cite a reason why it is an important practice to implement a reset signal in a finite state machine?

**Answer:** Without a reset signal a finite state machine cannot be driven into a known initial state.

## Practice Exercise 5.14

1. What type of finite state machine may have an output that depends on one or more inputs?



**Answer:** The outputs of a Mealy state machine may depend on the inputs to the machine.

## 5.6 SYNTHESIZABLE HDL MODELS OF SEQUENTIAL CIRCUITS

Behavioral models are abstract representations of the functionality of digital hardware. That is, they describe how a circuit behaves, but don't specify the internal details of the circuit. Historically, the abstraction of a circuit has been described by truth tables, state tables, and state diagrams. An HDL describes the functionality differently, by language constructs that describe the operations of registers in a machine. It is important for you to know how to write and use synthesizable behavioral models, because they can be simulated to produce waveforms demonstrating the behavior of the machine, and because synthesis tools can create physical circuits from properly-written behavioral models.

### Behavioral Modeling with Verilog

There are two kinds of abstract behaviors in the Verilog HDL. Behavior declared by the keyword **initial** is called *single-pass behavior* and specifies a single statement or a block statement (i.e., a list of statements enclosed by either a **begin . . . end** or a **fork . . . join** keyword pair). A single-pass behavior expires after the associated statement executes. In practice, designers use single-pass behavior primarily to prescribe stimulus signals in a testbench—never to model the behavior of a circuit—because synthesis tools do not synthesize hardware from descriptions that use the **initial** statement. The **always** keyword declares a *cyclic behavior*. Both types of behaviors begin executing when the simulator launches at time  $t=0$ . The **initial** behavior expires after its statement executes; the **always** behavior executes and re-executes indefinitely, until the simulation is stopped. A module may contain an arbitrary number of **initial** or **always** behavioral statements. They execute concurrently with respect to each other, starting at time 0, and may interact through common variables.

Here's a word description of how an **always** statement works for a simple

behavioral model of a *D* flip-flop with synchronous reset: Whenever the rising edge of the clock occurs, if the reset input is asserted, the output *Q* gets 0; otherwise the output *Q* gets the value of the input *D*. The execution of statements triggered by the clock is repeated until the simulation ends. We'll see shortly how to write this description in Verilog.

An **initial** behavioral statement executes only once. It begins its execution at the start of simulation and expires after all of its statements have completed execution. As mentioned at the end of [Section 4.12](#), the **initial** statement is useful for generating input signals to stimulate a design. In simulating a sequential circuit, it is necessary to generate a clock source for triggering the flip-flops and other synchronous devices. The following are two possible ways to provide a free-running clock that operates for a specified number of cycles:

<b>initial</b>	<b>initial</b>
 <b>begin</b>	 <b>begin</b>
 clock = 1'b0;	 clock = 1'b0;
 <b>repeat</b> (30)	 <b>end</b>
 #10 clock = ~clock;	
 <b>end</b>	 <b>initial</b> #300 \$finish;
	 <b>always</b> #10 clock = ~clock;

In the first version, the **initial** block contains two statements enclosed within the **begin** and **end** keywords. The first statement sets *clock* to 0 at time=0. The second statement specifies a loop that re-executes 30 times to wait 10 time units and then complement the value of *clock*. This produces 15 clock cycles, each with a cycle time of 20 time units. In the second

version, the first **initial** behavior has a single statement that sets *clock* to 0 at time=0, and it then expires (causes no further simulation activity). The second single-pass behavior declares a stopwatch to terminate the simulation. The system task **\$finish** causes the simulation to terminate unconditionally after 300 time units have elapsed. Because this behavior has only one statement associated with it, there is no need to write the **begin . . . end** keyword pair. After 10 time units, the **always** statement repeatedly pauses for 10 time units, then it complements *clock*, providing a clock generator having a cycle time of 20 time units. The three behavioral statements in the second example can be written in any order.

## Practice Exercise 5.15—Verilog

1. When does an **initial** block statement expire?

**Answer:** An **initial** block statement expires when the last statement executes.

## Practice Exercise 5.16—Verilog

1. What is the primary use of an **initial** statement?

**Answer:** The primary use of an **initial** statement is in describing behavioral statements in a testbench.

## Practice Exercise 5.17—Verilog

1. Under what conditions is an initial statement synthesizable?

**Answer:** There are no conditions under which an initial statement is synthesizable.

Here is another way to describe a free-running clock:

```
initial begin clock = 0; forever #10 clock = ~clock; end
```

This version, with two statements in one block statement, initializes the

clock and then executes an indefinite loop (**forever**) in which the clock is complemented after a delay of 10 time steps. Note that in this example the single-pass behavior never finishes executing and so does not expire. Another behavior would have to terminate the simulation.

The activity associated with either type of behavioral statement can be controlled by a delay operator that waits for a certain time or by an event control operator that waits for certain conditions to become true or for specified events (changes in signals) to occur. Time delays specified with the *# delay control operator* are commonly used in single-pass behaviors. The delay control operator suspends execution of statements until a specified time has elapsed. We've already seen examples of its use to specify signals in a testbench. Another operator, *@*, is called the *event control operator* and is used to *suspend* activity until an event occurs. An event can be an unconditional change in a signal value, for example, *@ (A)* or a specified transition of a signal value (*@ (posedge clock)*). The general form of this type of statement is

```
always @ (event control expression) begin  
    // Procedural assignment statements that execute when the co  
end
```

The event control expression specifies the condition that must occur to launch execution of the procedural assignment statements. The variables to which value is assigned, that is, the left-hand side of the procedural statements, must be declared as having **reg** data type. The right-hand side can be any expression that produces a value using Verilog-defined operators.

The event control expression (also called the sensitivity list) specifies the events that must occur to launch execution of the procedural statements associated with the **always** block. Statements within the block execute sequentially from top to bottom. After the last statement executes, the behavior waits for the event control expression to be satisfied. Then the statements are executed again. The sensitivity list can specify level-sensitive events, edge-sensitive events, or a combination of the two. In practice, designers do not make use of the third option, because this third form is not one that synthesis tools are able to translate into physical hardware. Level-sensitive events occur in combinational circuits and in latches. For example, the statement

```
always @ (A or B or C)
```

will initiate execution of the procedural statements in the associated **always** block if a change occurs in *A*, *B*, or *C*. In synchronous sequential circuits, changes in flip-flops occur only in response to a transition of a clock pulse. The transition may be either a positive edge or a negative edge of the clock, but not both. Verilog HDL takes care of these conditions by providing two keywords: **posedge** and **negedge**. For example, the expression

```
always @(posedge clock or negedge reset)           // Verilog 1995
```

will initiate execution of the associated procedural statements only if the clock goes through a positive transition or if *reset* goes through a negative transition. The 2001 and 2005 revisions to the Verilog language allow a comma-separated list for the event control expression (or sensitivity list):

```
always @(posedge clock, negedge reset) // Verilog 2001, 2005
```

A procedural assignment is an assignment of a logic value to a variable within an **initial** or **always** statement. This is in contrast to a continuous assignment discussed in [Section 4.12](#) with dataflow modeling. A continuous assignment has an *implicit* level-sensitive sensitivity list consisting of all of the variables on the right-hand side of its assignment statement. The updating of a continuous assignment is triggered whenever an event occurs in a variable included on the right-hand side of its expression. In contrast, a procedural assignment is made only when an assignment statement is executed and assigns value to it within a behavioral statement. For example, the clock signal in the preceding example was complemented only when the statement `clock=~clock` executed; the statement did not execute until 10 time units after the simulation began. It is important to remember that a variable having type **reg** remains unchanged until a procedural assignment is made to give it a new value.

There are two kinds of procedural assignments: *blocking* and *nonblocking*. The two are distinguished by the symbols that they use. Blocking assignments use the symbol (=) as the assignment operator, and nonblocking assignments use (<=) as the operator. Blocking assignment statements are executed sequentially in the order they are listed in a block of statements. Nonblocking assignments are executed concurrently by evaluating the set of expressions on the right-hand side of the list of

statements; they do not make assignments to their left-hand sides until all of the expressions are evaluated. The two types of assignments may be better understood by means of an illustration. Consider these two procedural blocking assignments:

```
B = A;  
C = B + 1;
```

The first statement transfers the value of *A* into *B*. The second statement increments the value of *B* and transfers the new value to *C*. At the completion of the assignments, *C* contains the value of *A*+1.

Now consider the two statements as nonblocking assignments:

```
B <= A;  
C <= B + 1;
```

When the statements are executed, the expressions on the right-hand side are evaluated and stored in a temporary location. The value of *A* is kept in one storage location and the value of *B*+1 in another. After all the expressions in the block are evaluated and stored, the assignment to the targets on the left-hand side is made using the stored values. In this case, *C* will contain the original value of *B*, plus 1. A general rule is to **use blocking assignments when sequential ordering is imperative and in a cyclic behavior that is level sensitive** (i.e., in combinational logic). **Use nonblocking assignments when modeling concurrent execution** (e.g., edge-sensitive behavior such as synchronous, concurrent register transfers) **and when modeling latched behavior**. Nonblocking assignments are imperative in dealing with register transfer level design, as shown in [Chapter 8](#). They model the concurrent operations of physical hardware synchronized by a common clock. Today's designers are expected to know what features of an HDL are useful in a practical way and how to avoid features that are not. Following these rules for using the assignment operators will prevent conditions that lead synthesis tools astray and create mismatches between the behavior of a model and the behavior of physical hardware that is produced from the model by a synthesis tool.

## Practice Exercise 5.18—Verilog

1. What is the role of the @ operator and a sensitivity list in an **always**

statement?

**Answer:** The @ operator suspends execution of the **always** statement until an event defined by the sensitivity list occurs.

## Practice Exercise 5.19—Verilog

1. When does an **always** procedural statement terminate?

**Answer:** An **always** procedural statement executes repeatedly, without termination.

## Behavioral Modeling with VHDL

A **process** is the basic VHDL construct for describing behavioral models of hardware. In [Section 4.13](#) we saw that the keywords **process . . . end process** establish the scope of a process. The keywords enclose signal and variable assignment statements, and other constructs controlling the flow of execution. Within a process, procedural assignments are used to evaluate expressions and assign value to signals and variables. The statements are like those used to control the flow of execution in other languages. Loops, conditionals, and other constructs provide the flexibility needed to describe arithmetic and logic operations and algorithms. A key feature of a process is that it automatically associates memory with the variables and signals that are assigned value by the process. When simulation begins, a process executes once immediately, then pauses at the process statement, where the sensitivity list is monitored. Thus, a process is either suspended or active (running) subject to conditions imposed by the sensitivity list. The sensitivity list controls when and whether the statements in the process execute again, for the life of the simulation. Signal assignments made within a process execute concurrently, and all processes that are sensitive to the same clock execute concurrently.

## Practice Exercise 5.20—VHDL

1. What are the three VHDL constructs that execute concurrently?



**Answer:** Components, concurrent signal assignment statements, and processes.

# HDL Models of Latches and Flip-Flops

The examples in this section present HDL descriptions of various flip-flops and a *D* latch. The *D* latch (see [Section 5.3](#)) is said to be *transparent* because it responds to a change in data input with a change in the output as long as the enable input is asserted—viewing the output is the same as viewing the input. The behavior of a flip-flop is synchronized to a clock signal.

## HDL Example 5.1 (*D* Latch)

### Verilog

The *D* latch has two inputs, *D* and *enable*, and one output, *Q*. Since *Q* is assigned value by a procedural statement, its type must be declared to be **reg**. Hardware latches respond to input signal *levels*, so the two inputs are listed without edge qualifiers in the sensitivity list following the @ symbol in the **always** statement. In this model, there is only one nonblocking procedural assignment statement, and it specifies the transfer of input *D* to output *Q* if *enable* is true (logic 1).<sup>2</sup> Note that this statement is executed every time there is a change in *D* if *enable* is 1. The nonblocking assignment operator is used in modeling flip-flops and other synchronous devices so that all such devices are operating concurrently, and with no dependence on the order in which the flip-flops appear in the code.

<sup>2</sup> The statement (single or block) associated with **if** (Boolean expression) executes if the Boolean expression is true.

```
// Description of D latch (see Fig. 5.6)
module D_latch (Q, D, enable);
    output Q;
    input D, enable;
```

```

reg    Q;
always @ (enable, D)
    if (enable) Q <= D;    // Same as: if (enable == 1)
endmodule

// Alternative syntax (Verilog 2001, 2005)
module D_latch (output reg Q, input enable, D);
    always @ (enable, D)
        if (enable) Q <= D;    // No action if enable not asserted
endmodule

```

## VHDL

The functionality of a *D* latch is described by a level-sensitive VHDL **process**. Whenever *enable* or *D* have an event, the process executes and checks whether *enable* is asserted. If so, the output of the latch is assigned the value of the input to the latch. Thus, the output tracks the input. If *enable* is not asserted, no assignment is made (i.e., *Q* is left unchanged), and the process returns to the sensitivity list, where it waits for the next event of *enable* or *D*. If the process is launched by a de-assertion of *enable*, *Q* will retain its current value until *enable* is asserted again. Remember, the variables and signals in a process have memory, and change only when explicitly assigned a value by a procedural statement.

```

-- Description of D latch (see Fig. 5.6)
entity D_latch_vhdl is
    port (Q: out Std_Logic; D, enable: in Std_Logic);
end D_latch_vhdl;

architecture Behavioral of D_latch_vhdl is
    process (enable, D) begin
        if enable = '1' then Q <= D; end if;
    end process;
end Behavioral;

```

## Practice Exercise 5.21—VHDL

1. Explain what happens if the process in the architecture of `D_latch_vhdl` is activated by a de-assertion of *enable*.

**Answer:** If the process is activated by a de-assertion of *enable*, the value of *Q* is left unchanged. The output is effectively “latched.”

# HDL Example 5.2 (*D*-Type Flip-Flop)

A *D*-type flip-flop is the simplest example of a sequential machine. This HDL example describes two positive-edge *D* flip-flops. The first responds only to the clock; the second includes an asynchronous reset input.

## Verilog

Output *Q* in *D\_FF* is assigned value by a procedural statement, so it must be declared as a **reg** data type in addition to being listed as an output. The keyword **posedge** ensures that the transfer of input *D* into *Q* is synchronized by the positive-edge transition of *Clk*. A change in *D* at any other time does not change *Q*.

```
// D flip-flop without reset
module D_FF (Q, D, Clk);
    output Q;
    input  D, Clk;
    reg    Q;
    always @ (posedge Clk)
        Q <= D;
endmodule
```

```
// D flip-flop with active-low, asynchronous reset (V2001, V2002)
module DFF (output reg Q, input D, Clk, rst);
    always @ (posedge Clk, negedge rst)
        if (!rst) Q <= 1'b0;    // Same as: if (rst == 0)
        else Q <= D;
endmodule
```

The sensitivity list of the second flip-flop model includes an asynchronous reset input in addition to the synchronous clock. A specific form of an **if** statement is used to describe such a flip-flop so that the model can be synthesized by a software tool. In general, the sensitivity list after the **@** symbol following the **always** statement may include edge events of any number of signals, either **posedge** or **negedge**, but for modeling hardware, one of the events must be a clock event, that is, the event of a synchronizing signal. The remaining events specify conditions under which asynchronous logic is to be executed. The designer knows which

signal is the clock, but *clock* is not an identifier that software tools automatically recognize as the synchronizing signal of a circuit. The tool must be able to infer which signal is the clock, so *the description must be written in a way that enables the tool to infer the clock correctly*. The rules are simple to follow: (1) Each **if** or **else if** statement in the procedural assignment statements is to correspond to an asynchronous event, (2) the **else** clause of the last such statement corresponds to the clock event, and (3) the asynchronous events are decoded and tested first. There are two edge events in the second module of [HDL Example 5.2](#). The **negedge** *rst* (reset) event is asynchronous, since it matches the **if** (*!rst*) statement. Moreover, the decoding of the **if** statement implies that *rst* has priority—enabling it to override the action of the clock. As long as *rst* is 0, *Q* is cleared to 0. If *Clk* has a positive transition, its effect is blocked. Only if *rst*=1 can the **posedge** clock event synchronously transfer *D* into *Q*.

## Practice Exercise 5.22—Verilog

1. In the procedural statement below, when does the reset action occur?

```
always @(negedge clock) begin
if (!reset) D <= 0; else Q <= D;
end
```

**Answer:** The reset action occurs if *reset* is 0 at the negative edge of *clock*.

## VHDL

Two VHDL models of flip-flops are presented below. The sensitivity list of the process in the first model is sensitive to only *Clk*. If *Clk* changes, the process launches and immediately checks whether the triggering event of *Clk* was a positive edge. The term *Clk'*event denotes a VHDL predefined attribute associated with *Clk*. It is Boolean True if *Clk* has an event in the current simulation cycle. Given an event of *Clk*, it is necessary to determine whether the event corresponds to a rising edge transition. If so, *Q* is assigned the value of *D*. If not, *Q* is not changed. This corresponds to the behavior of a *D* flip-flop without reset. It merely passes data to the output on every active edge of the clock. In the second model, the

sensitivity list monitors *Clk* and *rst*. When an event is detected, the process checks first whether an assertion of *rst* triggered the launch. If so, *Q* is reset to 0; if not, *Clk* is checked to determine whether the clock has had a positive edge. If so, *Q* is assigned the value of *D*. No action is taken on the inactive edges of the clock, leaving *Q* at whatever value it had immediately before the edge of the clock.

```
-- D flip-flop without reset
entity D_FF_vhdl is
  port (Q: out Std_Logic; D, Clk: in Std_Logic);
end

architecture Behavioral of D_FF_vhdl is
  process (Clk) begin
    if Clk_b and Clk = '1' then Q <= D;
  end Behavioral;

-- D flip-flop with active-low, asynchronous reset
entity DFF_vhdl is
  port (Q: out Std_Logic; D, Clk, rst_b: in Std_Logic);
end

architecture Behavioral of DFF_vhdl is
  process (Clk, rst_b) begin
    if rst_b'event and rst_b = '0' then Q <= '0';
    else if Clk'event and Clk = '1' then Q <= D; end if;
    end if;
  end process;
end Behavioral;
```

A process may contain any number of signals in its sensitivity list. For modeling hardware, one of them must be a synchronizing signal. The remaining events specify conditions under which asynchronous logic is to be executed. The designer knows which signal is the clock, but *clock* is not an identifier that software synthesis tools automatically recognize as the synchronizing signal of a circuit. The tool must be able to infer which signal is the clock, so the *description must be written in a way that enables the tool to infer the synchronizing signal correctly*.

The process in *Behavioral* of *DFF\_vhdl* gives priority to *rst\_b* by first checking whether it was launched by a falling edge of *rst\_b*. If so, the output is reset to 0 and remains at 0 as long as *rst\_b* is zero. Otherwise, the process checks whether a rising edge of *Clk* has occurred. If so, the output *Q* gets the value of *D*. For a synchronous behavior, one of the signals in the sensitivity list must be the synchronizing signal, independently of its

name.<sup>3</sup> The reset action is asynchronous because a transition of *rst\_b* can launch the process independently of *Clk*. It is important to note that the reset event is decoded by the first **if** statement following the sensitivity list, thereby giving priority to *rst*. This enables a synthesis tool to infer that the remaining signal, *Clk* is the synchronizing signal of the flip-flop. The rules are straightforward: (1) The asynchronous events are tested first. (2) Each **if** or **else if** statement in the signal assignment statements is to correspond to an asynchronous event. (3) The **else** clause of the last such statement corresponds to the clock (synchronizing) event. In the second model for *D\_FF\_vhdl* in [HDL Example 5.3](#) there are two signals in the process sensitivity list. The *rst\_event* is asynchronous because it matches the *if rst = '0'* statement, and is not conditioned on *Clk*. If *Clk* has a positive transition, its effect is blocked if *rst* is 0. Only if *rst* is 1 can a positive edge of *Clk* transfer *D* to *Q*.

<sup>3</sup> *Clk*, clock and other similarly named signals are not automatically inferred to be a synchronizing signal. Also, the order in which signals appear in a sensitivity list does not determine which signal is the synchronizing signal.

## Practice Exercise 5.23—VHDL

1. In the process below, when does the reset action occur?

```
process (Clk, rst) begin
  if rst'event and rst = '1' then Q <= '0';
    else if Clk'event and Clk = '0' then Q <= D; end if;
  end if;
end process;
```

**Answer:** The reset action occurs at the rising edge of *rst*.

## Reset Signals

Digital hardware always has a reset signal. It is strongly recommended that all models of sequential circuits include a reset (or preset) signal; otherwise, the initial state of the flip-flops of the sequential circuit cannot be determined. A sequential circuit cannot be tested with HDL simulation unless an initial state can be assigned with by an external input signal.

There is no market for untested circuits.

## Alternative Models of Flip-Flops

D-type flip-flops can be used to construct a T or JK flip-flop. Their circuits are described with the characteristic equations of their flip-flops:

$Q(t+1) = Q \text{ xor } T$  for a JK flip-flop  
 $Q(t+1) = JQ' + K'Q$  for a T flip-flop

The HDL model of either type of flip-flop must form the data input of the D-type flip-flop according to the right-hand side of the above equations.

## HDL Example 5.3 (Alternative T, JK flip-flops)

### Verilog

```
// T flip-flop from D flip-flop and gates
module TFF (output Q, input T, Clk, rst);
  wire      DT;
  assign DT = Q ^ T;
  // Instantiate the D flip-flop
  DFF TF1 (Q, DT, Clk, rst);    // Active-low, asynchronous res
endmodule

// JK flip-flop from D flip-flop and gates
module JKFF (output reg Q, input J, K, Clk, rst);
  wire JK;
  assign JK = (J & ~Q) | (~K & Q);
  // Instantiate D flip-flop
  DFF (output reg Q, input D, Clk, rst);
endmodule
```

### VHDL

```
entity TFF_vhdl is
  port ( Q: out Std_Logic; T, Clk, rst: in Std_Logic);
```

```

end TFF_vhdl;

architecture Behavioral of TFF_vhdl is
  component DFF_vhdl port (Q: out Std_logic; D, clk, rst: in Std_
    signal DT: Std_Logic; ;
  begin
    DT <= Q xor T;
    M0: DFF_vhdl port map (Q => Q, D => DT, Clk => Clk, rst=> rst)
  end Behavioral;
  -- JK flip-flop D flip-flop and gates
entity JKFF is
  port (Q: out Std_Logic; J, K, Clk, rst: in Std_Logic);
end JKFF;

architecture Behavioral of JKFF is
  signal JK <= (J and not(Q)) or (not(k) and Q);
  component DFF port (q: out Std_Logic, D: in Std_Logic, Clk, rs
  end component;
  begin
    // Instantiate D flip-flop
    M0: DFF port map (Q => Q, D => JK, Clk => Clk, rst => rst);
  end Behavioral;

```

Another way to describe a *JK* flip-flop uses the characteristic *table* rather than the characteristic *equation*. A **case** statement checks the two-bit number obtained by concatenating the bits of *J* and *K*. The **case** expression is evaluated and compared with the list of statements that follows. The statement at the first value that matches the true condition is executed. Since the concatenation of *J* and *K* produces a two-bit number, it can be equal to 00, 01, 10, or 11. The first bit gives the value of *J* and the second the value of *K*. The four possible conditions specify the value of the next state of *Q* after the application of a positive-edge clock.

## HDL Example 5.4 (*JK* Flip-Flop)

### Verilog

```

// Functional description of JK flip-flop using a case statemen
module JK_FF (input J, K, Clk, output reg Q, output Q_b);
  assign Q_b = ~Q;
  always @ (posedge Clk)
    case ({J,K})
      2'b00: Q <= Q;
      2'b01: Q <= 1'b0;

```



```

    2'b10: Q <= 1'b1;
    2'b11: Q <= !Q;
  encase;
endmodule;

```

## VHDL

```

entity JK_FF_vhdl is
  port (Q, Q_b: out Std_Logic; J, K, Clk, rst: in Std_Logic);
end JK_FF_vhdl;

  architecture Behavioral_Case_vhdl of JK_FF_vhdl is
    Q_b <= not Q;
  process (Clk) begin
    if (Clk'event and Clk = '1') then
      case (J & K) is
        when '00' => Q <= Q;
        when '01' => Q <= '0';
        when '10' => Q <= '1';
        when '11' => Q <= not Q;
      end case;
    end if;
  end process;
end Behavioral_Case;

```

## State Diagram-Based HDL Models

An HDL model of the functionality of a sequential circuit can be based on the format of the circuit's state diagram. A Mealy HDL model is presented in [HDL Example 5.5](#) for the zero-detector machine described by the sequential circuit in [Fig. 5.15](#) and its state diagram shown in [Fig. 5.16](#). The input, output, clock, and reset are declared in the usual manner. The state of the flip-flops is declared with identifiers *state* and *next\_state*. These signals hold the values of the present state and the next value of the state of the sequential circuit. The state's binary assignment is done with a **parameter** statement. (Verilog allows constants to be defined in a module by the keyword **parameter** followed by an identifier and an assignment of value.) The four states S0 through S3 are assigned binary 00 through 11. The notation S2=2'b10 is preferable to the alternative S2=2. The former uses only two bits to store the value, whereas the latter results in a binary number with 32 (or 64) bits because an unsized number is interpreted and sized as an integer.

# HDL Example 5.5 (Mealy Machine: Zero Detector)

## Verilog

```
// Mealy FSM zero detector (see Fig. 5.15 and Fig. 5.16) Veril
// Asynchronous reset
module Mealy_Zero_Detector (output reg y_out, input x_in, cloc
  reg [1: 0] state, next_state;
  parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
  always @ (posedge clock, negedge reset) Verilog 2001, 2005 sy
    if (!reset) state <= S0;
    else state <= next_state;
  always @ (state, x_in) // Form the next state
  case (state)
    S0: if (x_in)      next_state = S1;          else next_state
    S1: if (x_in)      next_state = S3;          else next_state
    S2:      if (!x_in) next_state = S0;          else ne
    S3: if (x_in)      next_state = S2;          else next_state
  endcase
  always @ (state, x_in) // Form the Mealy output
  case (state)
    S0: y_out = 0;
    S1, S2, S3: y_out = !x_in;
  endcase
endmodule

module t_Mealy_Zero_Detector;
  wire t_y_out;
  reg t_x_in, t_clock, t_reset;
  Mealy_Zero_Detector M0 (t_y_out, t_x_in, t_clock, t_reset);
  initial #200 $finish;
  initial begin t_clock = 0; forever #5 t_clock = ~t_clock; end
  initial fork
    t_reset = 0;
    #2 t_reset = 1;
    #87 t_reset = 0;
    #89 t_reset = 1;
    #10 t_x_in = 1;
    #30 t_x_in = 0;
    #40 t_x_in = 1;
    #50 t_x_in = 0;
    #52 t_x_in = 1;
    #54 t_x_in = 0;
    #80 t_x_in = 1;
```

```

#100 t_x_in = 0;
#120 t_x_in = 1;
join
endmodule


```

The Mealy\_FSM\_zero\_detector machine detects a 0 following a sequence of 1's in a serial bit stream. Its Verilog model uses three **always** blocks that execute concurrently and interact through common signals. The first **always** statement resets the circuit to the initial state  $S_0=00$  and specifies the synchronous clocked operation. The statement `state <= next_state` is synchronized to a positive-edge transition of the clock. This means that any change in the value of *next\_state* in the second **always** block can affect the value of *state* only as a result of a **posedge** event of *clock*.

The second **always** block determines the value of the next state transition as a function of the present state and input. The value assigned to *state* by the nonblocking assignment is the value of *next\_state* immediately before the rising edge of *clock*. Notice how the multiway branch condition implements the state transitions specified by the annotated edges in the state diagram of [Fig. 5.16](#). The third **always** block specifies the output as a function of the present state and the input. Although this block is listed as a separate behavior for clarity, it could be combined with the second block. Note that the value of output *y\_out* may change if the value of input *x\_in* changes while the circuit is in any given state.

So let's summarize how the model describes the behavior of the machine: At every rising edge of *clock*, if *reset* is not asserted, the state of the machine is updated by the first **always** block; when *state* is updated by the first **always** block, the change in *state* is detected by the sensitivity list mechanism of the second **always** block; then the second **always** block updates the value of *next\_state* (it will be used by the first **always** block at the *next* tick of the clock); the third **always** block also detects the change in *state* and updates the value of the output. In addition, the second and third **always** blocks detect changes in *x\_in* and update *next\_state* and *y\_out* accordingly. The testbench provided with *Mealy\_Zero\_Detector* provides some waveforms to stimulate the model, producing the results shown in [Fig. 5.22](#). Notice how *t\_y\_out* responds to changes in both the state and the input, and has a glitch (a transient logic value). We display both *state*[1:0] and *next\_state*[1:0] to illustrate how changes in *t\_x\_in* influence the value of *next\_state* and *t\_y\_out*. The Mealy glitch in *t\_y\_out* is due to the (intentional) dynamic behavior of *t\_x\_in*. The input, *t\_x\_in*, settles to a

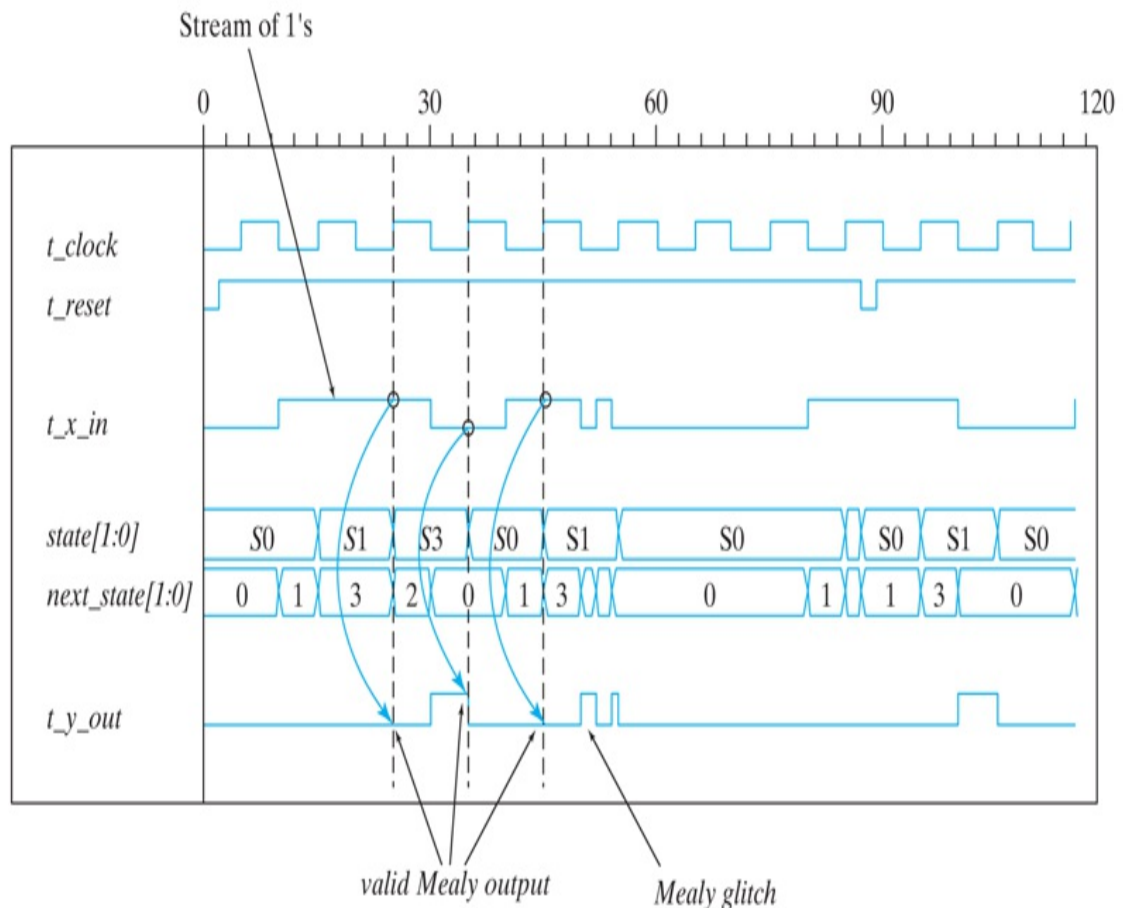value of 0 at  $t=54$ , immediately before the rising edge at  $t=55$ , and, at the clock, the state makes a transition from S0 to S1, which is consistent with [Fig. 5.16](#). The output is 1 in state S1 immediately before the clock, and changes to 0 as the state enters S0.



## FIGURE 5.22

Simulation output of *Mealy\_Zero\_Detector*

### [Description](#)

The description of waveforms in the testbench uses the **fork . . . join** construct. Statements within the **fork . . . join** block *execute in parallel*, so the time delays are relative to a common reference of  $t=0$ , the time at which the block begins execution.<sup>4</sup> It is usually more convenient to use the **fork . . . join** block instead of the **begin . . . end** block in describing waveforms. Notice that the waveform of *reset* is triggered “on the fly” to demonstrate that the machine recovers from an unexpected (asynchronous)

reset condition during any state.

<sup>4</sup> A **fork . . . join** block completes execution when the last executing statement within it completes its execution. The **fork . . . join** construct is used in testbenches, but it is not synthesizable.

How does our Verilog model *Mealy\_Zero\_Detector* correspond to hardware? The first **always** block corresponds to a *D* flip-flop implementation of the state register in [Fig. 5.21](#); the second **always** block is the combinational logic describing the next state; the third **always** block describes the output combinational logic of the zero-detecting Mealy machine. The register operation of the state transition uses the nonblocking assignment operator (`<=`) because the (edge-sensitive) flip-flops of a sequential machine are updated concurrently by a common clock. The second and third **always** blocks describe combinational logic, which is level sensitive, so they use the blocking (`=`) assignment operator. Their sensitivity lists include both the state and the input because their logic must respond to a change in either or both of them.

Note: The modeling style illustrated by *Mealy\_Zero\_Detector* is commonly used by designers because it has a close relationship to the state diagram of the machine that is being described. Notice that the reset signal is associated with the **always** block that synchronizes the state transitions—not with the combinational logic describing the next-state logic. In this example, it is modeled as an active-low reset. Because the reset condition is included in the description of the state transitions, there is no need to include it in the combinational logic that specifies the next state and the output, and the resulting description is less verbose, simpler, and more readable.

## VHDL

The architecture in the VHDL model of a Mealy zero detector FSM has three processes. The first process controls the synchronous updating of the state of the machine, as *state* gets *next\_state*, subject to asynchronous reset. The process resets the machine to state *S0* and synchronizes state transitions to the positive edge of the clock. This means that any change in the value of *next\_state* in the second process can affect the value of *state* only at the rising edge of *clock*. The second process is level sensitive to

changes in *state* and *x\_in* (the inputs). When either changes, *next\_state* is specified, depending on the present state and the inputs. The value assigned to *state* by the signal assignment statement is the value of *next\_state* immediately before the rising edge of *clock*. The second process implements the *next\_state* logic according to the edges of the state diagram of the machine. The multiway branch condition implements the state transitions specified by the annotated edges of the state diagram in [Fig. 5.16](#). The third process is also sensitive, in general, to the state and the inputs, and specifies the (Mealy or Moore) outputs of the machine. Although this process is written as a separate process for clarity, it could be combined with the second process. Note that the state diagram in [Fig. 5.15](#) does not show the reset action explicitly. To include it would require an edge from every state to the reset state, cluttering up the diagram. Likewise, the process specifying the next state action of the machine does not include the reset signal. Instead, it is considered in the first process, which governs the synchronous behavior of the state transitions subject to asynchronous reset.

A testbench is also provided. The signal assignments within it create the waveforms for the inputs and the reset signal. They act concurrently, so the statements have no interaction. The processes of the state machine are interactive. A change in the state activates the process that specifies the output, and activates the process that specifies the next state. The first process synchronizes state changes to occur with the rising edge of the clock, subject to the reset signal. A thorough test program would demonstrate that the model implements the state diagram by reaching every state and by exercising every transition from every state. The machine should not get trapped in a state, and it should recover gracefully from an unexpected asynchronous reset condition while operating.

It is strongly recommended that you follow this style of describing a finite state machine, that is, writing three processes as shown above. By decomposing the architecture into three separate, but interacting, processes we create a clear, readable representation of the dynamics of the machine, and reduce the difficulty of troubleshooting a model when it fails to conform to specifications for its behavior. The discipline of following this style of designing a state machine reduces the risk and cost of the design effort.

```
library ieee;
use ieee.std_logic_1164.all;
```

```

entity Mealy_Zero_Detector_vhdl is
  port (y_out: out std_logic; x_in, clock, reset: in std_logic);
end Mealy_Zero_Detector_vhdl;

architecture Behavioral of Mealy_Zero_Detector_vhdl is
  type state_type (S0, S1, S2, S3); -- machine states
  signal state, next_state : state_type;

  process (clock, reset) begin -- Synchronous state transitions
    if (reset'event and reset = '0' then state <= S0;
      else if clock'event and clock = '1' then state <= next_state
      end if;
  end process;

  process (state, x_in) begin -- Next state
    case (state) is
      when S0 => if x_in = '1' then next_state = S1; else next_s
      else end if;
      when S1 => if x_in = '1' then next_state = S3; else next_s
      else end if;
      when S2 => if x_in = '0' then next_state = S0; els
      else end if;
      when S3 => if x_in = '1' then next_state = S2; else next_s
      else end if;
      when others => next_state <= S0;
    end case;
  end process;

  process (state, x_in) begin -- Output
    case (state) is
      when S0 => y_out = '0';
      when S1 => y_out = not x_in;
      when S2 => y_out = not x_in;
      when S3 => y_out = not x_in;
    end case;
  end process;
end Behavioral;

entity t_Meally_Zero_Detector_vhdl is
end Mealy_Zero_Detector_vhdl;

architecture Behavioral of t_Mealy_Zero_Detector_vhdl is
  signal t_y_out: std_logic;
  signal t_x_in: std_logic;
begin
  -- Instantiate the UUT
  UUT: Mealy_Zero_Detector_vhdl port map (y_out => t_y_out, x_i

  -- Create free-running clock signal;
  process (clock) begin

```

```

    clock <= not clock after 5 ns;
end process;

-- Specify stimulus signal signals
process begin
    t_reset   <= '0';
    t_reset   <= '1' after 2 ns;
    t_reset   <= '0' after 87 ns;
    t_reset   <= '1' after 89 ns;
    t_x_in <= '1' after 10 ns;
    t_x_in <= '0' after 30 ns;
    t_x_in <= '1' after 40 ns;
    t_x_in <= '0' after 50 ns;
    t_x_in <= '1' after 52 ns;
    t_x_in <= '0' after 54 ns;
    t_x_in <= '1' after 70 ns;
    t_x_in <= '0' after 80 ns;
    t_x_in <= '1' after 90 ns;
    t_x_in <= '0' after 100 ns;
    t_x_in <= '1' after 120 ns;
    t_x_in <= '0' after 160 ns;
    t_x_in <= '1' after 170 ns;
end process ;
end Behavioral;

```

## HDL Example 5.6 (Moore Machine)


### Verilog

The Verilog behavioral model of the Moore FSM shown in [Fig. 5.18](#) has the state diagram given in [Fig. 5.19](#). The model illustrates an alternative style in which the state transitions of the machine are described by a single clocked (i.e., edge-sensitive) cyclic behavior, that is, by one **always** block. The present state of the circuit is identified by the variable *state*, and its transitions are triggered by the rising edge of *clock* according to the conditions listed in the **case** statement. The combinational logic that determines the next state is included in the nonblocking assignment to *state*. In this example, the output of the circuits is independent of the input and is taken directly from the outputs of the flip-flops. The two-bit output *y\_out* is specified with a continuous assignment statement and is equal to



the value of the present state vector.

 [Figure 5.23](#) shows some simulation results for *Moore\_Model\_Fig\_5\_19*. Here are some important observations: (1) the output depends on only the state, (2) reset “on-the-fly” forces the state of the machine back to S0 (00), and (3) the state transitions are consistent with [Fig. 5.19](#).



## FIGURE 5.23

Simulation output of [HDL Example 5.6](#)

### Description

```
// Moore model FSM (see Fig. 5.19)      Verilog 2001, 2005 synt
module Moore_Model_Fig_5_19 (output [1: 0] y_out, input x_in, c
  reg [1: 0] state;
  parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
  always @ (posedge clock, negedge reset)
    if (reset == 0) state <= S0; // Initialize to state S0
    else case (state)
      S0: if (!x_in) state <= S1; else state <= S0;
      S1: if ( x_in) state <= S2; else state <= S3;
      S2: if (!x_in) state <= S3; else state <= S2;
      S3: if (!x_in) state <= S0; else state <= S3;
    endcase
  assign y_out = state; // Output of flip-flops
endmodule
```

## Practice Exercise 5.24—Verilog

1. Does the following code fragment describe the output of a Mealy or a Moore machine? Why?

```
assign y_out = (x_in == 2'b10) && (state == s_3);
```

**Answer:** *y\_out* describes the output of a Mealy machine, because *y\_out* depends on the input and the state. The output of a Moore machine depends on only the state.

## VHDL

The VHDL behavioral model of the circuit in [Fig. 5.18](#) has the state diagram in [Fig. 5.19](#). An alternative description of the machine consists of a single process and an output signal assignment. Notice that the combinational logic forming the next state of the machine is not shown explicitly.

```
-- Moore model FSM (see Fig. 5.19)
entity Moore_Model_Fig_5_19_vhdl is
  port ( y_out: out, bit_vector 1 downto 0; x_in, clock, reset:
end Moore_Model_vhdl;

architecture Behavioral of Moore_Model_Fig_5_19 is
  type State_type is (S0, S1, S2, S3);    -- names of states
  signal state: State_type;

  process (Clk, reset)    -- State transition
  begin
    if rst = '0' state <= S0;    -- Synchronous reset
    else case (state)
      when S0    => if not x_in then state <= S1; else state <=
      when S1    => if x_in      then state <= S2; else state <=
        when S2  => if not x_in then state <= S3; else state <=
        when S3  => if not x_in then state <= S0; else state <=
    end process;
    y_out <= state;          // Output signal assignment
end Behavioral;
```

## Structural Description of Clocked


# Sequential Circuits Verilog

Combinational logic circuits can be described in Verilog by a connection of gates (primitives and UDPs), by dataflow statements (continuous assignments), or by level-sensitive cyclic behaviors (**always** blocks). Sequential circuits are composed of combinational logic and flip-flops, and their HDL models use sequential UDPs and behavioral statements (edge-sensitive cyclic behaviors) to describe the operation of flip-flops. One way to describe a sequential circuit uses a combination of dataflow and behavioral statements. The flip-flops are described with an **always** statement. The combinational part can be described with **assign** statements and Boolean equations. The separate modules can be combined to form a structural model by instantiation within a **module**.

The structural description of a Moore-type binary counter sequential circuit is shown in [HDL Example 5.7](#). We encourage the reader to consider alternative ways to model a circuit, so as a point of comparison, we first present *Moore\_Model\_Fig\_5\_20*, a Verilog behavioral description of a binary counter having the state diagram examined earlier shown in [Fig. 5.20\(b\)](#). This style of modeling follows directly from the state diagram. An alternative style, used in *Moore\_Model\_STR\_Fig\_5\_20*, represents the structure shown in [Fig. 5.20\(a\)](#). This style uses two modules. The first describes the circuit of [Fig. 5.20\(a\)](#). The second describes the *T* flip-flop that will be used by the circuit. We also show two ways to model the *T* flip-flop. The first asserts that, at every clock tick, the value of the output of the flip-flop toggles if the toggle input is asserted. The second model describes the behavior of the toggle flip-flop in terms of its characteristic equation. The first style is attractive because it does not require the reader to remember the characteristic equation. Nonetheless, the models are interchangeable and will synthesize to the same hardware circuit. A testbench module provides stimulus for verifying the functionality of the circuit. The sequential circuit is a two-bit binary counter controlled by input *x\_in*. The output, *y\_out*, is enabled when the count reaches binary 11. Flip-flops *A* and *B* are included as outputs in order to check their operation. The flip-flop input equations and the output equation are evaluated with continuous assignment (**assign**) statements having the corresponding Boolean expressions. The instantiated *T* flip-flops use *TA* and *TB* as defined by the input equations.

The second module describes the *T* flip-flop. The *reset* input resets the flip-flop to 0 with an active-low signal. The operation of the flip-flop is specified by its characteristic equation,  $Q(t+1)=Q\oplus T$ .

The testbench includes both models of the machine. The stimulus module provides common inputs to the circuits to simultaneously display their output responses. The first **initial** block provides eight clock cycles with a period of 10 ns. The second **initial** block specifies a toggling of input *x\_in* that occurs at the negative edge transition of the clock. The result of the simulation is shown in [Fig. 5.24](#). The pair (*A*, *B*) goes through the binary sequence 00, 01, 10, 11, and back to 00. The change in the count is triggered by a positive edge of the clock, provided that *x\_in* = 1. If *x\_in* = 0, the count does not change. *y\_out* is equal to 1 when both *A* and *B* are equal to 1. This verifies the main functionality of the circuit, but not a recovery from an unexpected reset event. It should also be tested.

 

## FIGURE 5.24

Simulation output of [HDL Example 5.7](#)

[Description](#)

# HDL Example 5.7 (Moore Machine—Binary Counter)

## Verilog

```
// State-diagram-based behavioral model (V2001, 2005)
module Moore_Model_Fig_5_20 (output y_out, input x_in, clock, r
    reg [1: 0] state;
    parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
    always @ (posedge clock, negedge reset)
        if (!reset) state <= S0; // Initialize to state S0
        else case (state)
            S0: if (x_in) state <= S1; else state <= S0;
            S1: if (x_in) state <= S2; else state <= S1;
            S2: if (x_in) state <= S3; else state <= S2;
            S3: if (x_in) state <= S0; else state <= S3;
        endcase
    assign y_out = (state == S3); // Output of flip-flops
endmodule
```

```
// Structural model with T flip-flops
module Moore_Model_STR_Fig_5_20 (output y_out, A, B, input x_in
    wire TA, TB;
    // Flip-flop input equations
    assign TA = x_in && B;
    assign TB = x_in;
    // Output equation
    assign y_out = A & B;
    // Instantiate Toggle flip-flops
    Toggle_flip_flop M_A (A, TA, clock, reset);
    Toggle_flip_flop M_B (B, TB, clock, reset);
endmodule
```

```
module Toggle_flip_flop (Q, T, CLK, RST_b);
    output Q;
    input T, CLK, RST_b;
    reg Q;
    always @ (posedge CLK, negedge RST_b)
        if (!RST_b) Q <= 1'b0;
        else if (T) Q <= ~Q;
endmodule
```

```
// Alternative model using characteristic equation
// module Toggle_flip_flop (Q, T, CLK, RST_b);
// output Q;
```

```

// input      T, CLK, RST_b;
// reg  Q;
// always @ (posedge CLK, negedge RST_b)
//   if (!RST_b) Q <= 1'b0;
//   else Q <= Q ^ T;
// endmodule

module t_Moore_Fig_5_20;
  wire  t_y_out_2, t_y_out_1;
  reg    t_x_in, t_clock, t_reset;
  Moore_Model_Fig_5_20      M1 (t_y_out_1, t_x_in, t_clock,
  Moore_Model_STR_Fig_5_20  M2 (t_y_out_2, A, B, t_x_in, t_
  initial #200 $finish;
  initial begin
    t_reset = 0;
    t_clock = 0;
    #5 t_reset = 1;
    repeat (16)
      #5 t_clock = !t_clock;
  end

  initial begin
    t_x_in = 0;
    #15 t_x_in = 1;
    repeat (8)
      #10 t_x_in = !t_x_in;
    end
  endmodule

```

## VHDL

```

library IEEE;
use IEEE.std_logic_1164.all;

-- Moore model FSM (see Fig. 5.19)

entity Moore_Model_Fig_5_20_vhdl is
  port ( y_out: out STD_LOGIC; x_in, clock, rst_b: in STD_logic)
end Moore_Model_Fig_5_20_vhdl;

architecture Behavioral of Moore_Model_Fig_5_20_vhdl is
  type State_type is (S0, S1, S2, S3);      -- names of states
  signal state, next_state: State_type;

  process (Clk)                                -- State transition
  begin
    if rst_b = '0' state <= S0; end if;      -- Synchronous
    else if Clk'event and Clk = '1'; then
      case (state)

```

```

        when S0 => if not x_in then state <= S1; else state <=
        when S1 => if x_in then state <= S2; else state <=
        when S2 => if not x_in then state <= S3; else state <=
        when S3 => if not x_in then state <= S0; else state <=
    end case
end if;
end process;
y_out <= state = S3;      -- Output logic
end Behavioral;

-- Components
-- D flip-flop with active-low, asynchronous reset
entity DFF_vhdl is
    port (Q: out Std_Logic; D, Clk, rst: in Std_Logic);
end DFF_vhdl;

architecture Behavioral of DFF_vhdl is
    process (Clk, rst_b) begin
        if rst'event and rst_b = '0' then Q <= '0';
        else if Clk'event and Clk = '1' then Q <= D; end if;
        end if;
    end process;
end Behavioral;

-- T flip-flop from D flip-flop and components
entity TFF_vhdl is
    port ( Q: out, bit; T, clk, rst: in bit);
end TFF_vhdl;
    architecture Behavioral of T_FF_vhdl is
        signal DT;
        component DFF_vhdl
            port ( Q: out Std_Logic; D, clk, rst: in Std_Logic);
        end component DFF_vhdl;
    begin
        DT <= Q xor T;      -- Signal assignment
        TF1: DFF_vhdl port map (Q => Q, D => DT, clk => clk, rst => r
    end Behavioral;

entity Moore_Model_STR_Fig_5_20_vhdl is
    port ( y_out, A, B: out STD_LOGIC; x_in, clock, reset: in STD_
end Moore_Model_vhdl;

architecture T_STR of Moore_Model_Fig_5_20 is
    signal TA, TB;
    component TFF_vhdl port (Q: out bit; clk, rst: in bit); end co
begin -- Instantiate toggle flip-flops

M_A: TFF_vhdl port map (Q => A, T => TA, clk => clock, rst =>
M_B: TFF_vhdl port map (Q => B, T => TB, clk => clock, rst =>
TA <= x_in and B;      -- Flip-flop input equations
TB <= x_in;

```

```

    y_out <= A and B;                -- Output logic
end T_STR;

-- Alternative model using characteristic equation

entity Toggle_flip_flop is
    port (Q: out Std_Logic; T, CLK, RST_b: in Std_Logic);
end Toggle_flip_flop;

architecture Char_Eq of Toggle_flip_flop is
    process (CLK, RST_b) begin
        if (RST'event and RST_b = '0' then Q <= '0';
        else if CLK'event and clk = '1' then Q <= Q xor T; end if;
        end if;
    end process
end Char_Eq;

-- Testbench

entity t_Moore_Fig_5_20 is
    port ();
end t_Moore_Fig_5_20;

architecture Behavioral of t_Moore_Fig_5_20 is
    component Moore_Model_STR_Fig_5_20_vhdl port(y_out: out bit; A
    signal t_y_out_1, t_y_out_2, t_A, t_B: Std_Logic;
    signal t_x_in, clock, reset: Std_Logic;
    variable i: Positive := '1';
    -- Instantiate UUTs
M1: Moore_Model_STR_Fig_5_20_vhdl
    port map ( y_out => t_y_out_1, A => t_A, B => t_B, x_in =>
M2: Moore_Model_STR_Fig_5_20_vhdl
    port map ( y_out => t_y_out_2, A => t_A, B => t_B, x_in =>

-- Generate stimulus signals
process begin
    t_reset <= 0;                -- Active-low reset
    t_clock <= 0;
    t_reset <= 1; after 5ns; -- Enable synchronous action
    for i in 1 to 16 loop
        t_clock <= not t_clock after 5ns;
    end loop;
end process;
end Behavioral;

```

## Practice Exercise 5.25—VHDL

1. Describe the steps that are taken to create a structural model of a



sequential circuit.

**Answer:** (1) Define components, (2) Instantiate and interconnect components.


## 5.7 STATE REDUCTION AND ASSIGNMENT

*Analysis* of sequential circuits starts from a circuit diagram and culminates in a state table or diagram. *Design* (synthesis) of a sequential circuit starts from a set of specifications and culminates in a logic diagram. Design procedures are presented in [Section 5.8](#). Two sequential circuits may exhibit the same input–output behavior, but have a different number of internal states in their state diagram. The current section discusses certain properties of sequential circuits that may simplify a design by reducing the number of gates and flip-flops it uses. In general, reducing the number of flip-flops reduces the cost of a circuit.

### State Reduction

The reduction in the number of flip-flops in a sequential circuit is referred to as the *state-reduction* problem. State-reduction algorithms are concerned with procedures for reducing the number of states in a state table, while keeping the external input–output requirements unchanged. Since  $m$  flip-flops produce  $2^m$  states, a reduction in the number of states may (or may not) result in a reduction in the number of flip-flops. An unpredictable effect in reducing the number of flip-flops is that sometimes the equivalent circuit (with fewer flip-flops) may require more combinational gates to realize its next state and output logic.

We will illustrate the state-reduction procedure with an example. We start with a sequential circuit whose specification is given in the state diagram of [Fig. 5.25](#). In our example, only the input–output sequences are important; the internal states are used merely to provide the required sequences. For that reason, the states marked inside the circles are denoted by letter symbols instead of their binary values. This is in contrast to a binary counter, wherein the binary value sequence of the states themselves is taken as the outputs.

 

**FIGURE 5.25**

State diagram

### Description

There are an infinite number of input sequences that may be applied to the circuit; each results in a unique output sequence. As an example, consider the input sequence 01010110100 starting from the initial state *a*. Each input of 0 or 1 produces an output of 0 or 1 and causes the circuit to go to the next state. From the state diagram, we obtain the output and state sequence for the given input sequence as follows: With the circuit in initial state *a*, an input of 0 produces an output of 0 and the circuit remains in state *a*. With present state *a* and an input of 1, the output is 0 and the next state is *b*. With present state *b* and an input of 0, the output is 0 and the next state is *c*. Continuing this process, we find the complete sequence to be as follows:

**state *a a b c d e f f g f g a***

input 0 1 0 1 0 1 1 0 1 0 0

output 0 0 0 0 0 1 1 0 1 0 0

In each column, we have the present state, input value, and output value. The next state is written on top of the next column. It is important to realize that in this circuit the states themselves are of secondary importance, because we are interested only in output sequences caused by input sequences.

Now let us assume that we have found a sequential circuit whose state diagram has fewer than seven states, and suppose we wish to compare this circuit with the circuit whose state diagram is given by [Fig. 5.25](#). If identical input sequences are applied to the two circuits and identical outputs occur for all input sequences, then the two circuits are said to be *equivalent*; they cannot be distinguished from each other on the basis of their input–output behavior, and one may be replaced by the other. The problem of state reduction is to find ways of reducing the number of states in a sequential circuit, thereby reducing hardware, without altering the input–output relationships.

We now proceed to reduce the number of states for this example. First, we need the state table; it is more convenient to apply procedures for state reduction with the use of a table rather than a diagram. The state table of the circuit is listed in [Table 5.6](#) and is obtained directly from the state diagram.

## Table 5.6 State Table

Present State	Next State Output			
	x=0		x=1	
	a	a	b	0
				0

<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

The following algorithm for the state reduction of a completely specified state table is given here without proof: “Two states are said to be equivalent if, for each member of the set of inputs, they give exactly the same output and send the circuit either to the same state or to an equivalent state.” When two states are equivalent, one of them can be removed without altering the input–output relationships.

Now apply this algorithm to [Table 5.6](#). Going through the state table, we look for two present states that go to the same next state and have the same output for both input combinations. States *e* and *g* are two such states: They both go to states *a* and *f* and have outputs of 0 and 1 for  $x=0$  and  $x=1$ , respectively. Therefore, states *g* and *e* are equivalent, and one of these states can be removed. The procedure of removing a state and replacing it by its equivalent is demonstrated in [Table 5.7](#). The row with present state *g* is removed, and state *g* is replaced by state *e* each time it occurs in the columns headed “Next State.”

## Table 5.7 Reducing the State Table

Present State	Next State Output			
	x=0	x=1	x=0	x=1

<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>e</i>	<i>f</i>	0	1

Present state *f* now has next states *e* and *f* and outputs 0 and 1 for  $x=0$  and  $x=1$ , respectively. The same next states and outputs appear in the row with present state *d*. Therefore, states *f* and *d* are equivalent, and state *f* can be removed and replaced by *d*. The final reduced table is shown in [Table 5.8](#). The state diagram for the reduced table consists of only five states and is shown in [Fig. 5.26](#). This state diagram satisfies the original input–output specifications and will produce the required output sequence for any given input sequence. The following list derived from the state diagram of [Fig. 5.26](#) is for the input sequence used previously (note that the same output sequence results, although the state sequence is different):

## Table 5.8 Reduced State Table

**Next State Output**  
**Present State**

**x=0 x=1 x=0 x=1**


*a*      *a*   *b*   0   0

*b*      *c*   *d*   0   0

*c*      *a*   *d*   0   0

*d*      *e*   *d*   0   1

*e*      *a*   *d*   0   1

 

**FIGURE 5.26**

Reduced state diagram

[Description](#)

state *a a b c d e d d e d e a*

input 0 1 0 1 0 1 1 0 1 0 0

output 0 0 0 0 0 1 1 0 1 0 0

In fact, this sequence is exactly the same as that obtained for [Fig. 5.25](#) if we replace *g* by *e* and *f* by *d*.

Checking each pair of states for equivalency can be done systematically by means of a procedure that employs an implication table, which consists of squares, one for every suspected pair of possible equivalent states. By judicious use of the table, it is possible to determine all pairs of equivalent states in a state table.

The sequential circuit of this example was reduced from seven to five states. In general, reducing the number of states in a state table may result in a circuit with less physical hardware. However, the fact that a state table has been reduced to fewer states does not guarantee a saving in the number of flip-flops or the number of gates. In actual practice designers may skip this step because target devices are rich in resources.

## State Assignment

In order to design a sequential circuit with physical components, it is necessary to assign unique coded binary values to the states. For a circuit with  $m$  states, the codes must contain  $n$  bits, where  $2^n \geq m$ . For example, with three bits, it is possible to assign codes to eight states, denoted by binary numbers 000 through 111. If the state table of [Table 5.6](#) is used, we must assign binary values to seven states; the remaining state is unused. If the state table of [Table 5.8](#) is used, only five states need binary assignment, and we are left with three unused states. Unused states are treated as don't-care conditions during the design. Since don't-care conditions usually help in obtaining a simpler circuit, it is more likely but not certain that the circuit with five states will require fewer combinational gates than the one with seven states.



The simplest way to code five states is to use the first five integers in binary counting order, as shown in the first assignment of [Table 5.9](#). Another similar assignment is the Gray code shown in assignment 2. Here, only one bit in the code group changes when going from one number to the next. This code makes it easier for the Boolean functions to be placed in a Karnaugh map for simplification. Another possible assignment often used in the design of state machines to control datapath units is the *one-hot* assignment. This configuration uses as many bits as there are states in the circuit. At any given time, only one bit is equal to 1 while all others are kept at 0. This type of assignment uses one flip-flop per state, which is not an issue for register-rich field-programmable gate arrays. (See [Chapter 7](#).) *One-hot encoding usually leads to simpler decoding logic for the next state and output.* One-hot machines can be faster than machines with sequential binary encoding, and the silicon area required by the extra flip-flops can be offset by the area saved by using simpler decoding logic. This trade-off is not guaranteed, so it must be evaluated for a given design.

## Table 5.9 Three Possible Binary State Assignments

State	Assignment 1, Binary	Assignment 2, Gray Code	Assignment 3, One-Hot
<i>a</i>	000	000	00001
<i>b</i>	001	001	00010
<i>c</i>	010	011	00100
<i>d</i>	011	010	01000
<i>e</i>	100	110	10000

[Table 5.10](#) is the reduced state table with binary assignment 1 substituted for the letter symbols of the states. A different assignment will result in a state table with different binary values for the states. The binary form of the state table is used to derive the next-state and output-forming combinational logic part of the sequential circuit. The complexity of the combinational circuit depends on the binary state assignment chosen.

## Table 5.10 Reduced State Table with Binary Assignment 1

Present State	Next State Output			
	x=0	x=1	x=0	x=1
000	000	001	0	0
001	010	011	0	0
010	000	011	0	0
011	100	011	0	1
100	000	011	0	1

Sometimes, the name *transition table* is used for a state table with a binary assignment. This convention distinguishes it from a state table with

symbolic names for the states. In this book, we use the same name for both types of state tables.

## 5.8 DESIGN PROCEDURE

Design procedures or methodologies specify hardware that will implement a desired behavior. The design effort for small circuits may be manual, but industry relies on automated synthesis tools for designing massive integrated circuits. The sequential building block used by synthesis tools is the *D* flip-flop. Together with additional logic, it can implement the behavior of *JK* and *T* flip-flops when needed. In fact, designers generally do not concern themselves with the type of flip-flop; rather, their focus is on correctly describing the sequential functionality that is to be implemented by the synthesis tool. Here we will illustrate manual methods using *D*, *JK*, and *T* flip-flops.

The design of a clocked sequential circuit starts from a set of specifications and culminates in a logic diagram or a list of Boolean functions from which the logic diagram can be obtained. In contrast to a combinational circuit, which is fully specified by a truth table, a sequential circuit requires a state table for its specification. The first step in the design of sequential circuits is to obtain a state table or an equivalent representation, such as a state diagram.<sup>5</sup>

<sup>5</sup> Chapter 8 will examine another important representation of a machine's behavior—the algorithmic state machine (ASM) chart.

A synchronous sequential circuit is made up of flip-flops and combinational gates. The design of the circuit consists of choosing the flip-flops and then finding a combinational gate structure that, together with the flip-flops, produces a circuit which fulfills the stated specifications. The number of flip-flops is determined from the number of states needed in the circuit and the choice of state assignment codes. The combinational circuit is derived from the state table by evaluating the flip-flop input equations and output equations. In fact, once the type and number of flip-flops are determined, the design process involves a transformation from a sequential circuit problem into a combinational circuit problem. In this way, the techniques of combinational circuit design can be applied.

The procedure for designing synchronous sequential circuits can be summarized by a list of recommended steps:


1. From the word description and specifications of the desired operation, derive a state diagram for the circuit.
2. Reduce the number of states if necessary.
3. Assign binary values to the states.
4. Obtain the binary-coded state table.
5. Choose the type of flip-flops to be used.
6. Derive the simplified flip-flop input equations and output equations.
7. Draw the logic diagram.

The word specification of the circuit behavior usually assumes that the reader is familiar with digital logic terminology. It is necessary that the designer use intuition and experience to arrive at the correct interpretation of the circuit specifications, because word descriptions may be incomplete and inexact. Once such a specification has been set down and the state diagram obtained, it is possible to use known synthesis procedures to complete the design. Although there are formal procedures for state reduction and assignment (steps 2 and 3), they are seldom used by experienced designers. Steps 4 through 7 in the design can be implemented by exact algorithms and therefore can be automated. The part of the design that follows a well-defined procedure is referred to as *synthesis*. Designers using logic synthesis tools (software) can follow a simplified process that develops an HDL description directly from a state diagram, letting the synthesis tool minimize combinational logic and determine the circuit elements and structure that implement the description.

The first step is a critical part of the process, because succeeding steps depend on it. We will give one simple example to demonstrate how a state diagram is obtained from a word specification.

Suppose we wish to design a circuit that detects a sequence of three or more consecutive 1's in a string of bits coming through an input line (i.e., the input is a *serial bit stream*). The state diagram for this type of circuit is shown in [Fig. 5.27](#). It is derived by starting with state S0, the reset state. While the input is 0, the circuit stays in S0, but if the input is 1, it goes to state S1 to indicate that a 1 was detected. If the next input is 1, the change

is to state S2 to indicate the arrival of two consecutive 1's, but if the input is 0, the state goes back to S0. The third consecutive 1 sends the circuit to state S3. If more 1's are detected, the circuit stays in S3. Any 0 input sends the circuit back to S0. In this way, the circuit stays in S3 as long as there are three or more consecutive 1's received. This is a Moore model sequential circuit, since the output is 1 when the circuit is in state S3 and is 0 otherwise.

 

**FIGURE 5.27**

State diagram for sequence detector

[Description](#)

## Synthesis Using *D* Flip-Flops

Once the state diagram has been derived, the rest of the design follows a straightforward synthesis procedure. In fact, we can design the circuit by using an HDL description of the state diagram and the proper HDL synthesis tools to obtain a synthesized netlist. (The HDL description of the state diagram will be similar to HDL [Example 5.6](#) in [Section 5.6](#).) To design the circuit by hand, we need to assign binary codes to the states and list the state table. This is done in [Table 5.11](#). The table is derived from the state diagram of [Fig. 5.27](#) with a sequential binary assignment. We choose two *D* flip-flops to represent the four states, and we label their outputs *A*

and  $B$ . There is one input ( $x$ ) and one output ( $y$ ). The characteristic equation of the  $D$  flip-flop is  $Q(t+1)=DQ$ , which means that the next-state values in the state table specify the  $D$  input condition for the flip-flop. The flip-flop input equations can be obtained directly from the next-state columns of  $A$  and  $B$  and expressed in sum-of-minterms form as

## Table 5.11 State Table for Sequence Detector


**Present State Input Next State Output**

$A$	$B$	$x$	$A$	$B$	$y$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

$$A(t+1)=DA(A, B, x)=\Sigma(3, 5, 7) \quad B(t+1)=DB(A, B, x)=\Sigma(1, 5, 7) \\ y(A, B, x)=\Sigma(6, 7)$$

where  $A$  and  $B$  are the present-state values of flip-flops  $A$  and  $B$ ,  $x$  is the input, and  $DA$  and  $DB$  are the input equations. The minterms for output  $y$  are obtained from the output column in the state table.

 The Boolean equations are simplified by means of the maps plotted in [Fig. 5.28](#). The simplified equations are



# FIGURE 5.28


K-Maps for sequence detector

## Description

$$DA = Ax + Bx \quad DB = Ax + B'x \quad y = AB$$

The advantage of designing with  $D$  flip-flops is that the Boolean equations describing the inputs to the flip-flops can be obtained directly from the state table. Software tools automatically infer and select the  $D$ -type flip-flop from a properly written HDL model. The schematic of the sequential circuit is drawn in [Fig. 5.29](#).



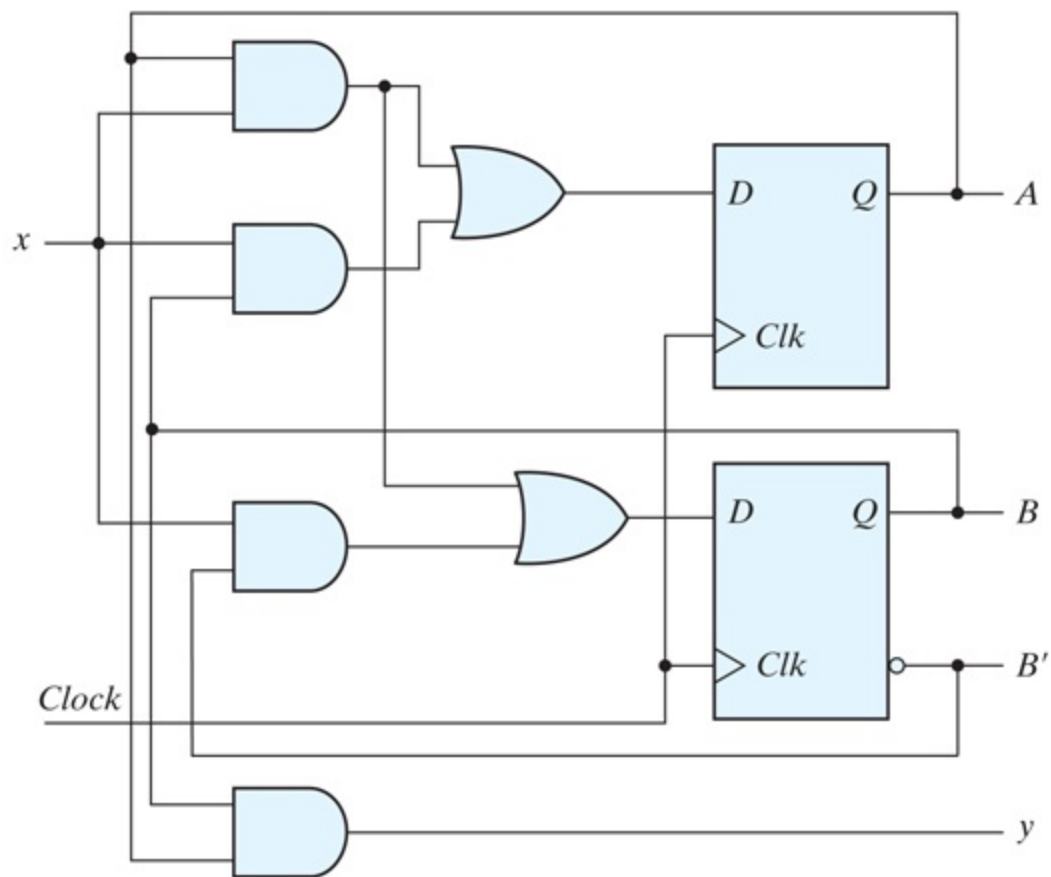

**FIGURE 5.29**

Logic diagram of a Moore-type sequence detector

[Description](#)

## Excitation Tables

The design of a sequential circuit with flip-flops other than the  $D$  type is complicated by the fact that the input equations for the circuit must be derived indirectly from the state table. When  $D$ -type flip-flops are employed, the input equations are obtained directly from the next state. This is not the case for the  $JK$  and  $T$  types of flip-flops. In order to determine the input equations for these flip-flops, it is necessary to derive a functional relationship between the state table and the input equations.

The flip-flop characteristic tables presented in [Table 5.1](#) provide the value

of the next state when the inputs and the present state are known. These tables are useful for analyzing sequential circuits and for defining the operation of the flip-flops. During the design process, we usually know the transition from the present state to the next state and wish to find the flip-flop input conditions that will cause the required transition. For this reason, we need a table that lists the required inputs for a given change of state. Such a table is called an *excitation table*.

[Table 5.12](#) shows the excitation tables for the two flip-flops ( $JK$  and  $T$ ). Each table has a column for the present state  $Q(t)$ , a column for the next state  $Q(t+1)$ , and a column for each input to show how the required transition is achieved. There are four possible transitions from the present state to the next state. The required input conditions for each of the four transitions are derived from the information available in the characteristic table. The symbol  $X$  in the tables represents a don't-care condition, which means that it does not matter whether the input is 1 or 0.

## Table 5.12 Flip-Flop Excitation Tables

$Q(t)$   $Q(t+1)$   $J$   $K$   $Q(t)$   $Q(t+1)$   $T$

0      0      0  $X$    0      0      0

0      1      1  $X$    0      1      1

1      0       $X$  1   1      0      1

1      1       $X$  0   1      1      0

(a)  $JK$  Flip-Flop (b)  $T$  Flip-Flop

The excitation table for the  $JK$  flip-flop is shown in part (a). When both present state and next state are 0, the  $J$  input must remain at 0 and the  $K$  input can be either 0 or 1. Similarly, when both present state and next state are 1, the  $K$  input must remain at 0, while the  $J$  input can be 0 or 1. If the flip-flop is to have a transition from the 0-state to the 1-state,  $J$  must be equal to 1, since the  $J$  input sets the flip-flop. However, input  $K$  may be either 0 or 1. If  $K=0$ , the  $J=1$  condition sets the flip-flop as required; if  $K=1$  and  $J=1$ , the flip-flop is complemented and goes from the 0-state to the 1-state as required. Therefore, the  $K$  input is marked with a don't-care condition for the 0-to-1 transition. For a transition from the 1-state to the 0-state, we must have  $K=1$ , since the  $K$  input clears the flip-flop. However, the  $J$  input may be either 0 or 1, since  $J=0$  has no effect and  $J=1$  together with  $K=1$  complements the flip-flop with a resultant transition from the 1-state to the 0-state.

The excitation table for the  $T$  flip-flop is shown in part (b). From the characteristic table, we find that when input  $T=1$ , the state of the flip-flop is complemented, and when  $T=0$ , the state of the flip-flop remains unchanged. Therefore, when the state of the flip-flop must remain the same, the requirement is that  $T=0$ . When the state of the flip-flop has to be complemented,  $T$  must equal 1.

## Synthesis Using $JK$ Flip-Flops

The manual synthesis procedure for sequential circuits with  $JK$  flip-flops is the same as with  $D$  flip-flops, except that the input equations must be evaluated from the present-state to the next-state transition derived from the excitation table. To illustrate the procedure, we will synthesize the sequential circuit specified by [Table 5.13](#). In addition to having columns for the present state, input, and next state, as in a conventional state table, the table shows the flip-flop input conditions from which the input equations are derived. The flip-flop inputs are derived from the state table in conjunction with the excitation table for the  $JK$  flip-flop. For example, in the first row of [Table 5.13](#), we have a transition for flip-flop  $A$  from 0 in the present state to 0 in the next state. In [Table 5.12](#), for the  $JK$  flip-flop, we find that a transition of states from present state 0 to next state 0 requires that input  $J$  be 0 and input  $K$  be a don't care. So 0 and X are entered in the first row under  $J_A$  and  $K_A$ , respectively. Since the first row also shows a transition for flip-flop  $B$  from 0 in the present state to 0 in the

next state, 0 and X are inserted into the first row under JB and KB, respectively. The second row of the table shows a transition for flip-flop *B* from 0 in the present state to 1 in the next state. From the excitation table, we find that a transition from 0 to 1 requires that *J* be 1 and *K* be a don't care, so 1 and X are copied into the second row under JB and KB, respectively. The process is continued for each row in the table and for each flip-flop, with the input conditions from the excitation table copied into the proper row of the particular flip-flop being considered.


## Table 5.13 State Table and JK Flip-Flop Inputs

**Present State Input Next State Flip-Flop Inputs**

<i>A</i>	<i>B</i>	<i>x</i>	<i>A</i>	<i>B</i>	<i>JA</i>	<i>KA</i>	<i>JB</i>	<i>KB</i>
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0

1      1      1      0      0      X      1      X      1

The flip-flop inputs in [Table 5.13](#) specify the truth table for the input equations as a function of present state  $A$ , present state  $B$ , and input  $x$ . The input equations are simplified in the maps of [Fig. 5.30](#). The next-state values are not used during the simplification, since the input equations are a function of the present state and the input only. Note the advantage of using  $JK$ -type flip-flops when sequential circuits are designed *manually*. The fact that there are so many don't-care entries indicates that the combinational circuit for the input equations is likely to be simpler, because don't-care minterms usually help in obtaining simpler expressions. If there are unused states in the state table, there will be additional don't-care conditions in the map. Nonetheless,  $D$ -type flip-flops are more amenable to an automated design flow.

 


## FIGURE 5.30

Maps for  $J$  and  $K$  input equations
 
### [Description](#)

The four input equations for the pair of  $JK$  flip-flops are listed under the maps of [Fig. 5.30](#). The logic diagram (schematic) of the sequential circuit is drawn in [Fig. 5.31](#).




## FIGURE 5.31

Logic diagram for sequential circuit with  $JK$  flip-flops

### [Description](#)

## Synthesis Using $T$ Flip-Flops

The procedure for synthesizing circuits using  $T$  flip-flops will be demonstrated by designing a binary counter. An  $n$ -bit binary counter consists of  $n$  flip-flops that can count in binary from 0 to  $2^n - 1$ . The state diagram of a three-bit counter is shown in [Fig. 5.32](#). As seen from the binary states indicated inside the circles, the flip-flop outputs repeat the binary count sequence with a return to 000 after 111. The directed lines between circles are not marked with input and output values as in other state diagrams. Remember that state transitions in clocked sequential circuits are initiated by a clock edge; the flip-flops remain in their present states if no clock is applied. For that reason, the clock does not appear explicitly as an input variable in a state diagram or state table. From this point of view, the state diagram of a counter does not have to show input and output values along the directed lines. The only input to the circuit is the clock, and the outputs are specified by the present state of the flip-flops. The next state of a counter depends entirely on its present state, and the state transition occurs every time the clock goes through a transition.

 

**FIGURE 5.32**

State diagram of three-bit binary counter

[Table 5.14](#) is the state table for the three-bit binary counter. The three flip-flops are symbolized by  $A_2$ ,  $A_1$ , and  $A_0$ . Binary counters are constructed most efficiently with  $T$  flip-flops because of their complement property. The flip-flop excitation for the  $T$  inputs is derived from the excitation table of the  $T$  flip-flop and by inspection of the state transition of the present state to the next state. As an illustration, consider the flip-flop input entries for row 001. The present state here is 001 and the next state is 010, which

is the next count in the sequence. Comparing these two counts, we note that A2 goes from 0 to 0, so TA2 is marked with 0 because flip-flop A2 must not change when a clock occurs. Also, A1 goes from 0 to 1, so TA1 is marked with a 1 because this flip-flop must be complemented in the next clock edge. Similarly, A0 goes from 1 to 0, indicating that it must be complemented, so TA0 is marked with a 1. The last row, with present state 111, is compared with the first count 000, which is its next state. Going from all 1's to all 0's requires that all three flip-flops be complemented.

## Table 5.14 State Table for Three-Bit Counter


**Present State Next State Flip-Flop Inputs**

A2	A1	A0	A2	A1	A0	TA2	TA1	TA0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1



1   1   1   0   0   0   1   1   1


The flip-flop input equations are simplified in the maps of [Fig. 5.33](#). Note that  $TA_0$  has 1's in all eight minterms because the least significant bit of the counter is complemented with each count. A Boolean function that includes all minterms defines a constant value of 1. The input equations listed under each map specify the combinational part of the counter. Including these functions with the three flip-flops, we obtain the logic diagram of the counter, as shown in [Fig. 5.34](#). For simplicity, the reset signal is not shown, but be aware that every design should include a reset signal.

 

**FIGURE 5.33**

Maps for three-bit binary counter

[Description](#)

 

**FIGURE 5.34**

Logic diagram of three-bit binary counter

[Description](#)

# PROBLEMS

(Answers to problems marked with \* appear at the end of the book. Where appropriate, a logic design and its related HDL modeling problem are cross-referenced.) Unless SystemVerilog is explicitly named, the HDL compiler for solving a problem may be Verilog, SystemVerilog, or VHDL. Note: For each problem that requires writing and verifying an HDL model, a basic test plan should be written to identify which functional features are to be tested during the simulation and how they will be tested. For example, a reset on-the-fly could be tested by asserting the reset signal while the simulated machine is in a state other than the reset state. The test plan is to guide development of a testbench that will implement the plan. Simulate the model, using the testbench, and verify that the behavior is correct. If synthesis tools are available, the HDL descriptions developed for Problems 5.34–5.42 can be assigned as synthesis exercises. The circuit produced by the synthesis tools should be simulated and compared to the simulation results for the pre-synthesis model.


1. 5.1 The *D* latch of [Fig. 5.6](#) is constructed with four NAND gates and an inverter. Consider the following three other ways for obtaining a *D* latch. In each case, draw the logic diagram and verify the circuit operation.
  1. (a) Use NOR gates for the *SR* latch part and AND gates for the other two. An inverter may be needed.
  2. (b) Use NOR gates for all four gates. Inverters may be needed.
  3. (c) Use four NAND gates only (without an inverter). This can be done by connecting the output of the upper gate in [Fig. 5.6](#) (the gate that goes to the *SR* latch) to the input of the lower gate (instead of the inverter output).
2. 5.2 Construct a *JK* flip-flop using a *D* flip-flop, a two-to-one-line multiplexer, and an inverter. (HDL—see [Problem 5.34](#).)
3. 5.3 Show that the characteristic equation for the complement output of a *JK* flip-flop is

$$Q'(t+1)=J'Q'+KQ$$

4. 5.4 A *PN* flip-flop has four operations: clear to 0, no change, complement, and set to 1, when inputs *P* and *N* are 00, 01, 10, and 11, respectively.
  1. (a) Tabulate the characteristic table.
  2. (b)\* Derive the characteristic equation.
  3. (c) Tabulate the excitation table.
  4. (d) Show how the *PN* flip-flop can be converted to a *D* flip-flop.
5. 5.5 Explain the differences among a truth table, a state table, a characteristic table, and an excitation table. Also, explain the difference among a Boolean equation, a state equation, a characteristic equation, and a flip-flop input equation.
6. 5.6 A sequential circuit with two *D* flip-flops *A* and *B*, two inputs, *x* and *y*; and one output *z* is specified by the following next-state and output equations (HDL—see [Problem 5.35](#)):


$$A(t+1)=xy'+xB \quad B(t+1)=xA+xB' \quad z=A$$

1. (a) Draw the logic diagram of the circuit.
  2. (b) List the state table for the sequential circuit.
  3. (c) Draw the corresponding state diagram.
7. 5.7\* A sequential circuit has one flip-flop *Q*, two inputs *x* and *y*, and one output *S*. It consists of a full-adder circuit connected to a *D* flip-flop, as shown in [Fig. P5.7](#). Derive the state table and state diagram of the sequential circuit.

 

**FIGURE P5.7**

8. 5.8\* Derive the state table and the state diagram of the sequential circuit shown in [Fig. P5.8](#). Explain the function that the circuit performs. (HDL—see [Problem 5.36](#).)

 

**FIGURE P5.8**

[Description](#)

9. 5.9 A sequential circuit has two *JK* flip-flops *A* and *B* and one input *x*. The circuit is described by the following flip-flop input equations:

$$JA=x \quad KA=B \quad JB=x \quad KB=A'$$

1. (a)\* Derive the state equations  $A(t+1)$  and  $B(t+1)$  by substituting the input equations for the *J* and *K* variables.
  2. (b) Draw the state diagram of the circuit.
10. 5.10 A sequential circuit has two *JK* flip-flops *A* and *B*, two inputs *x* and *y*, and one output *z*. The flip-flop input equations and circuit output equation are

$$JA=Bx+B'y' \quad KA=B'xy' \quad JB=A'x \quad KB=A+xy' \quad z=Ax'y'+Bx'y'$$

1. (a) Draw the logic diagram of the circuit.
  2. (b) Tabulate the state table.
  3. (c)\* Derive the state equations for *A* and *B*.
11. 5.11 For the circuit described by the state diagram of [Fig. 5.16](#),
1. (a)\* Determine the state transitions and output sequence that will be generated when an input sequence of 010110111011110 is applied to the circuit and it is initially in the state 00.
  2. (b) Find all of the equivalent states in [Fig. 5.16](#) and draw a simpler, but equivalent, state diagram.
  3. (c) Using *D* flip-flops, design the equivalent machine (including its logic diagram) described by the state diagram in (b).
12. 5.12 For the following state table

	Next State Output			
Present State				
	x=0	x=1	x=0	x=1


<i>a</i>	<i>f</i>	<i>b</i>	0	0
<i>b</i>	<i>d</i>	<i>c</i>	0	0
<i>c</i>	<i>f</i>	<i>e</i>	0	0
<i>d</i>	<i>g</i>	<i>a</i>	1	0
<i>e</i>	<i>d</i>	<i>c</i>	0	0
<i>f</i>	<i>f</i>	<i>b</i>	1	1
<i>g</i>	<i>g</i>	<i>h</i>	0	1
<i>h</i>	<i>g</i>	<i>a</i>	1	0

1. (a) Draw the corresponding state diagram.
  2. (b)\* Tabulate the reduced state table.
  3. (c) Draw the state diagram corresponding to the reduced state table.
13. 5.13\* Starting from state *a*, and the input sequence 01110010011, determine the output sequence for
1. (a) The state table of the previous problem.
  2. (b) The reduced state table from the previous problem. Show that the same output sequence is obtained for both.
14. 5.14 Substitute the one-hot assignment 3 from [Table 5.9](#) to the states

in [Table 5.8](#) and obtain the binary state table.

 15. 5.15 List a state table for the *JK* flip-flop using *Q* as the present and next state and *J* and *K* as inputs. Design the sequential circuit specified by the state table and show that it is equivalent to [Fig. 5.12\(a\)](#).
16. 5.16 Design a sequential circuit with two *D* flip-flops *A* and *B*, and one input *x<sub>in</sub>*.
  1. (a)\* When *x<sub>in</sub>*=0, the state of the circuit remains the same. When *x<sub>in</sub>*=1, the circuit goes through the state transitions from 00 to 01, to 11, to 10, back to 00, and repeats.
  2. (b) When *x<sub>in</sub>*=0, the state of the circuit remains the same. When *x<sub>in</sub>*=1, the circuit goes through the state transitions from 00 to 11, to 01, to 10, back to 00, and repeats. (HDL—see [Problem 5.38](#).)
17. 5.17 Design a one-input, one-output serial 2's complementer. The circuit accepts a string of bits from the input and generates the 2's complement at the output. The circuit can be reset asynchronously to start and end the operation. (HDL—see [Problem 5.39](#).)
18. 5.18\* Design a sequential circuit with two *JK* flip-flops *A* and *B* and two inputs *E* and *F*. If *E*=0, the circuit remains in the same state regardless of the value of *F*. When *E*=1 and *F*=1, the circuit goes through the state transitions from 00 to 01, to 10, to 11, back to 00, and repeats. When *E*=1 and *F*=0, the circuit goes through the state transitions from 00 to 11, to 10, to 01, back to 00, and repeats. (HDL—see [Problem 5.40](#).)
19. 5.19 A sequential circuit has three flip-flops *A*, *B*, and *C*; one input *x<sub>in</sub>*; and one output *y<sub>out</sub>*. The state diagram is shown in [Fig. P5.19](#). The circuit is to be designed by treating the unused states as don't-care conditions. Analyze the circuit obtained from the design to determine the effect of the unused states. (HDL—see [Problem 5.41](#).)





## FIGURE P5.19

### Description

1. (a)\* Use *D* flip-flops in the design.
  2. (b) Use *JK* flip-flops in the design.
20. 5.20 Design the sequential circuit specified by the state diagram of [Fig. 5.19](#), using *T* flip-flops.
21. 5.21 What is the main difference
1. (a) between an **initial** statement and an **always** statement in a Verilog procedural block?
  2. (b) between a variable assignment and a signal assignment in a VHDL process?
22. 5.22 Draw the waveform generated by the statements below:
1. (a)
 

```

initial begin

```

```

        w = 0; #10 w = 1; # 40 w = 0; # 20 w = 1; #15 w = 0
    end

```

2. (b)

```

    initial fork
        w = 0; #10 w = 1; # 40 w = 0; # 20 w = 1; #15 w = 0
    join

```

23. 5.23\* What are the values of RegA and RegB after the following statements, assuming that *RegA* contains the value of 50 initially.

Verilog

1. (a) RegA=125; RegB=RegA;
2. (b) RegA <= 125; RegB <= RegA;

VHDL

1. (a) RegA := 125; RegB := RegA;
2. (b) RegA <= 125; RegB <= RegA;

24. 5.24 Write and verify an HDL behavioral description of a positive-edge-sensitive *D* flip-flop with asynchronous preset and clear.
25. 5.25 A special positive-edge-triggered flip-flop circuit component has four inputs *D1*, *D2*, *D3*, and *D4*, and a two-bit control input that chooses between them. Write and verify an HDL behavioral description of this component.
26. 5.26 Write and verify an HDL behavioral description of the *JK* flip-flop using an **if-else** statement based on the value of the present state.
1. (a)\* Obtain the characteristic equation when *Q*=0 or *Q*=1.
  2. (b) Specify how the *J* and *K* inputs affect the output of the flip-flop at each clock tick.
27. 5.27 Rewrite and verify the description of HDL [Example 5.5](#) by combining the state transitions and output into (a) one Verilog **always** block or (b) one VHDL **process**.

28. 5.28 Simulate the sequential circuit shown in [Fig. 5.17](#).

1. (a) Write the HDL description of the state diagram (i.e., behavioral model).
2. (b) Write the HDL description of the logic (circuit) diagram (i.e., a structural model).
3. (c) Write an HDL stimulus with a sequence of inputs: 00, 01, 11, 10. Verify that the response is the same for both descriptions.

29. 5.29 Write a behavioral description of the state machine described by the state diagram shown in [Fig. p5.19](#). Write a testbench and verify the functionality of the description.

30. 5.30 Draw the logic diagram for the sequential circuit described by the following HDL code:

1. (a) **Verilog**

```
always @ (posedge CLK)
begin
    E <= A | B;
    Q <= E & C;
end
```


2. (b) **VHDL**

```
process (CLK) begin
    if CLK'event and CLK = '1' then
        begin
            E <= A or B;
            Q <= E and C;
        end process;
```

31. 5.31\*

1. (a) How should the description in [Problem 5.30](#) (a) be written to have the same behavior when the assignments are made with=instead of with <= ?
2. (b) How should the description in [Problem 5.30](#) (b) be written to have the same behavior if A, B, C, D, and E are variables and the assignments are made with=instead of <= ?

 32. 5.32 Using (a) an **initial** statement with a **begin . . . end** block write a Verilog description of the waveforms shown in [Fig. p5.32](#). Repeat using a **fork . . . join** block. (b) Write a VHDL process to describe the waveforms in [Fig. P5.32](#).



## FIGURE P5.32


Waveforms for [Problem 5.32](#)

### [Description](#)

33. 5.33 Explain why it is important that the stimulus signals in a testbench be synchronized to the *inactive* edge of the clock of the sequential circuit that is to be tested.
34. 5.34 Write and verify an HDL structural description of the machine having the circuit diagram (schematic) obtained in [Problem 5.2](#).
35. 5.35 Write and verify an HDL model of the sequential circuit described in [Problem 5.6](#).
36. 5.36 Write and verify an HDL structural description of the machine having the circuit diagram (schematic) shown in [Fig. p5.8](#).


37. 5.37 Write and verify HDL behavioral descriptions of the state machines shown in [Figs. 5.25](#) and [Fig. 5.26](#). Write a testbench to compare the state sequences and input–output behaviors of the two machines.
38. 5.38 Write and verify an HDL behavioral description of the machine described in [Problem 5.16](#).
39. 5.39 Write and verify a behavioral description of the machine specified in [Problem 5.17](#).
40. 5.40 Write and verify a behavioral description of the machine specified in [Problem 5.18](#).
41. 5.41 Write and verify a behavioral description of the machine specified in [Problem 5.19](#). (*Hint*: See the discussion of the **default** case item (Verilog) or the **others** case item (VHDL) preceding [HDL Example 4.8](#) in [Chapter 4](#).)
42. 5.42 Write and verify an HDL structural description of the circuit shown in [Fig. 5.29](#).
43. 5.43 Write and verify an HDL behavioral description of the three-bit binary counter in [Fig. 5.34](#).
44. 5.44 Write and verify an HDL behavioral model of a *D* flip-flop having asynchronous reset.
45. 5.45 Write and verify an HDL behavioral description of the sequence detector described in [Fig. 5.27](#).
46. 5.46 A synchronous finite state machine has an input *x\_in* and an output *y\_out*. When *x\_in* changes from 0 to 1, the output *y\_out* is to assert for three cycles, regardless of the value of *x\_in*, and then de-assert for two cycles before the machine will respond to another assertion of *x\_in*. The machine is to have active-low synchronous reset.
  1. (a) Draw the state diagram of the machine.
  2. (b) Write and verify a HDL model of the machine.

47. 5.47 Write a HDL model of a synchronous finite state machine whose output is the sequence 0, 2, 4, 6, 8 10, 12, 14, 0 . . . . The machine is controlled by a single input, *Run*, so that counting occurs while *Run* is asserted, suspends while *Run* is de-asserted, and resumes the count when *Run* is re-asserted. Clearly state any assumptions that you make.
48. 5.48 Write an HDL model of the Mealy FSM described by the state diagram in [Fig. P5.48](#). Develop a testbench and demonstrate that the machine state transitions and output correspond to its state diagram.

 

**FIGURE P5.48**

49. 5.49 Write an HDL model of the Moore FSM described by the state diagram in [Fig. P5.49](#). Develop a testbench and demonstrate that the machine's state transitions and output correspond to its state diagram.

 

**FIGURE P5.49**

50. 5.50 A synchronous Moore FSM has a single input,  $x_{in}$ , and a single output  $y_{out}$ . The machine is to monitor the input and remain in its reset state until a second sample of  $x_{in}$  is detected to be 1. Upon detecting the second assertion of  $x_{in}$   $y_{out}$  is to assert and remain asserted until a fourth assertion of  $x_{in}$  is detected. When the fourth assertion of  $x_{in}$  is detected the machine is to return to its reset state and resume monitoring of  $x_{in}$ .

1. (a) Draw the state diagram of the machine.
2. (b) Write and verify an HDL model of the machine.

51. 5.51 Draw the state diagram of the machine described by the HDL model given below.

1. (a) **Verilog**

```

module Prob_5_51 (output reg y_out, input x_in, clk, reset_b)
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10, s3 = 2'b11;
reg [1:0] state, next_state;
always @ (posedge clk, negedge reset_b) begin
    if (reset_b == 1'b0) state <= s0;
    else state <= next_state;
always @(state, x_in) begin
    y_out = 0;
    next_state = s0;
    case (state)
        s0: begin y_out = 0; if (x_in) next_state = s1; else
        s1: begin y_out = 0; if (x_in) next_state = s2; else
        s2: begin y_out = 1; if (x_in) next_state = s3; else
        s3: begin y_out = 1; if (x_in) next_state = s0; else
        default: next_state = s0;
    endcase
end
endmodule

```

## 2. (b) VHDL

```

entity Prob_5_51_vhdl is
    port (y_out: out std_Logic; clk, reset_b: in Std_Logic)
end Prob_5_51;

architecture Behavioral of Prob_5_51 is
    constant s0 = '00', s1 = '01', s2 = '10', s3 = '11';
    signal state, next_state: Std_Logic_Vector (1 downto 0);
    process (clk, reset_b) begin
        if reset_b'event and reset_b = '0' then state <= s0;
        else state <= next_state;
    end process;

    process (state, x_in) begin
        y_out <= 0;
        next_state <= s0;
        case state is
            when s0 => begin y_out <= 0; if x_in = '1' then next_state := s1; end if;
            when s1 => begin y_out <= 0; if x_in = '1' then next_state := s2; end if;
            when s2 => begin y_out <= 1; if x_in = '1' then next_state := s3; end if;
            when s3 => begin y_out <= 1; if x_in = '1' then next_state := s0; end if;
            when others => next_state = s0;
        end case;
    end process;
end Behavioral;

```



52. 5.52 Draw the state diagram of the machine described by the HDL model given below.

1. (a) **Verilog**

```

module Prob_5_52 (output reg y_out, input x_in, clk, reset_b)
  parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10, s3 = 2'b11;
  reg [1:0] state, next_state;
  always @ (posedge clk, negedge reset_b) begin
    if (reset_b == 1'b0) state <= s0;
    else state <= next_state;
  always @(state, x_in) begin
    y_out = 0;
    next_state = s0;
    case (state)
      s0: if x_in = 1 begin y_out = 0; if (x_in) next_state = s1; end;
      s1: if x_in = 1 begin y_out = 0; if (x_in) next_state = s2; end;
      s2: if x_in = 1 if (x_in) begin next_state = s3; y_out = 1; end;
      s3: if x_in = 1 begin y_out = 1; if (x_in) next_state = s0; end;
      default: next_state = s0;
    endcase
  end
endmodule

```

2. (b) **VHDL**

```

entity Prob_5_52_vhdl is
  port (y_out: out std_Logic; clk, reset_b: in Std_Logic)
end Prob_5_52;

architecture Behavioral of Prob_5_52 is
  constant s0 = '00', s1 = '01', s2 = '10', s3 = '11';
  signal state, next_state: Std_Logic_Vector (1 downto 0);
  process (clk, reset_b) begin
    if reset_b'event and reset_b = '0' then state <= s0;
    else state <= next_state;
  end process;

  process (state, x_in) begin
    y_out <= 0;
    next_state <= s0;
    case state is
      when s0 => begin y_out <= 0; if x_in = '1' then next_state <= s1; end;
      when s1 => begin y_out <= 0; if x_in = '1' then next_state <= s2; end;
      when s2 => if x_in = '1' then begin y_out <= 0; next_state <= s3; end;
      when s3 => begin y_out <= 1; if x_in = '1' then next_state <= s0; end;
      when others => next_state = s0;
    end case;
  end process;

```

**end Behavioral;**

53. 5.53 Draw a state diagram and write an HDL model of a Mealy synchronous state machine having a single input  $x_{in}$  and a single output  $y_{out}$ , such that  $y_{out}$  is asserted if the total number of 1's received is a multiple of 3.
54. 5.54 A synchronous Moore machine has two inputs  $x_1$  and  $x_2$ , and an output  $y_{out}$ . If both inputs have the same value, the output is asserted for one cycle; otherwise, the output is 0. Develop a state diagram and a write an HDL behavioral model of the machine. Demonstrate that the machine operates correctly.
55. 5.55 Develop the state diagram for a Mealy state machine that detects a sequence of three or more consecutive 1's in a string of bits coming through an input line.
56. 5.56 Using manual methods, obtain the logic diagram of a three-bit counter that counts in the sequence 0, 2, 4, 6, 0, . . . .
57. 5.57 Write and verify an HDL behavioral model of a three-bit counter described in [Problem 5.6](#) that counts in the sequence 0, 2, 4, 6, 0, . . . .
58. 5.58 Write and verify an HDL behavioral model of the ones counter designed in [Problem 5.55](#).
59. 5.59 Write and verify an HDL structural model of the three-bit counter described in [Problem 5.56](#).
60. 5.60 Write and verify an HDL behavioral model of a four-bit counter that counts in the sequence 0, 1, . . . , 9, 0, 1, 2, . . . .

# REFERENCES

- 1. Bhasker, J. 1998. *Verilog HDL Synthesis*. Allentown, PA: Star Galaxy Press.
- 2. Ciletti, M. D. 1999. *Modeling, Synthesis, and Rapid Prototyping with Verilog HDL*. Upper Saddle River, NJ: Prentice Hall.
- 3. Dietmeyer, D. L. 1988. *Logic Design of Digital Systems*, 3rd ed., Boston: Allyn Bacon.
- 4. Hayes, J. P. 1993. *Introduction to Digital Logic Design*. Reading, MA: Addison-Wesley.
- 5. Katz, R. H. 2005. *Contemporary Logic Design*. Upper Saddle River, NJ: Prentice Hall.
- 6. Mano, M. M. and C. R. Kime. 2015. *Logic and Computer Design Fundamentals & Xilinx 6.3 Student Edition*, 5th ed., Upper Saddle River, NJ: Full Arc Press.
- 7. Nelson, V. P., H. T. Nagle, J. D. Irwin, and B. D. Carroll. 1995. *Digital Logic Circuit Analysis and Design*. Englewood Cliffs, NJ: Prentice Hall.
- 8. Readler, B. 2014. *VHDL by Example*. Upper Saddle River, NJ: Pearson.
- 9. Roth, C. H. 2009. *Fundamentals of Logic Design*, 6th ed., St. Paul, MN: Brooks/Cole.
- 10. Short, K.L. 2008. *VHDL for Engineers*. Upper Saddle River, NJ: Pearson.
- 11. Thomas, D. E. and P. R. Moorby. 2002. *The Verilog Hardware Description Language*, 6th ed., Boston: Kluwer Academic Publishers.
- 12. Wakerly, J. F. 2006. *Digital Design: Principles and Practices*, 4th ed., Upper Saddle River, NJ: Prentice Hall.

# WEB SEARCH TOPICS

- Asynchronous state machine
- Binary counter
- *D*-type flip-flop
- Finite state machine
- *JK*-type flip-flop
- Logic design
- Mealy state machine
- Moore state machine
- One-hot/cold codes
- State diagram
- Synchronous state machine
- SystemVerilog
- Toggle flip-flop
- Verilog
- VHDL