

* Types.


- (1) Tuned radio freq. (TRF) receiver.
- (2) Superheterodyne radio receiver.

①

Block diagram

Block diagram TRF with comparison superheterodyne

Receiving Antenna

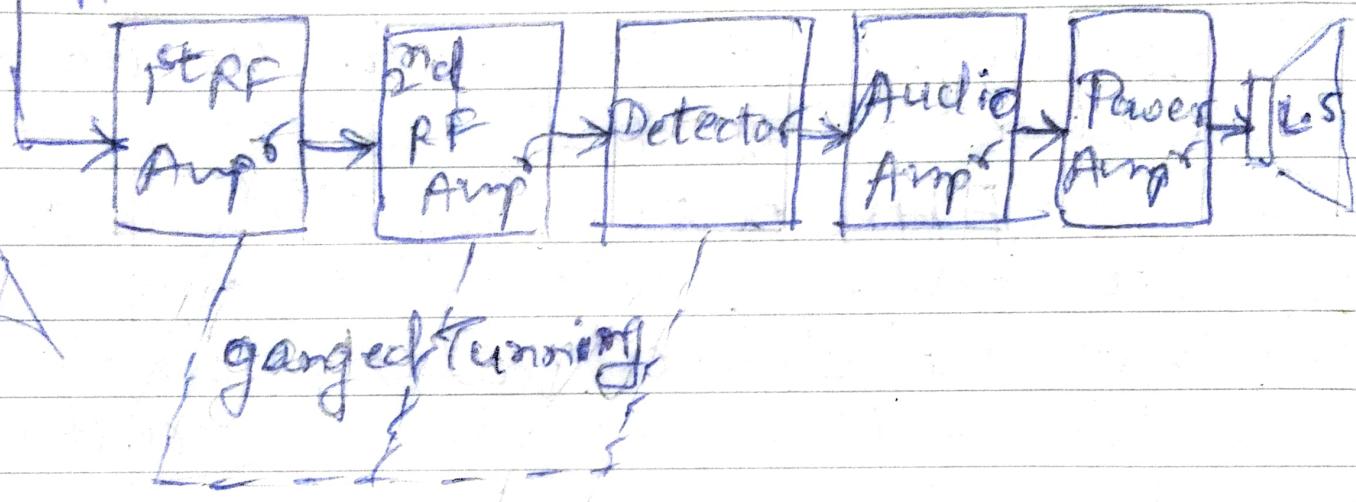

(1) RFamp → TRF radio receiver uses two or three stages of RF amp all tuned simultaneously to the desired signal freq. so that these stages provide selection as well as amplification to the incoming signal.

(2) Detector → Detector is nothing but the demodulator. It recovers the original information i.e. audio.

Extracting signal from the amplified amplitude modulated signal.


(3) Audion Power amp \rightarrow The demodulator.

Demodulated signal (audio) is amplified by the AF amp & power amp stages and fed to the loudspeaker & it converts electrical signal into sound signal.

* Draw back of TRF radio receiver.

- (1) Instability in gain.
- (2) Insufficient adjacent freq. rejection.
- (3) Bandwidth variation.

* Superhetrodyne radio receiver.

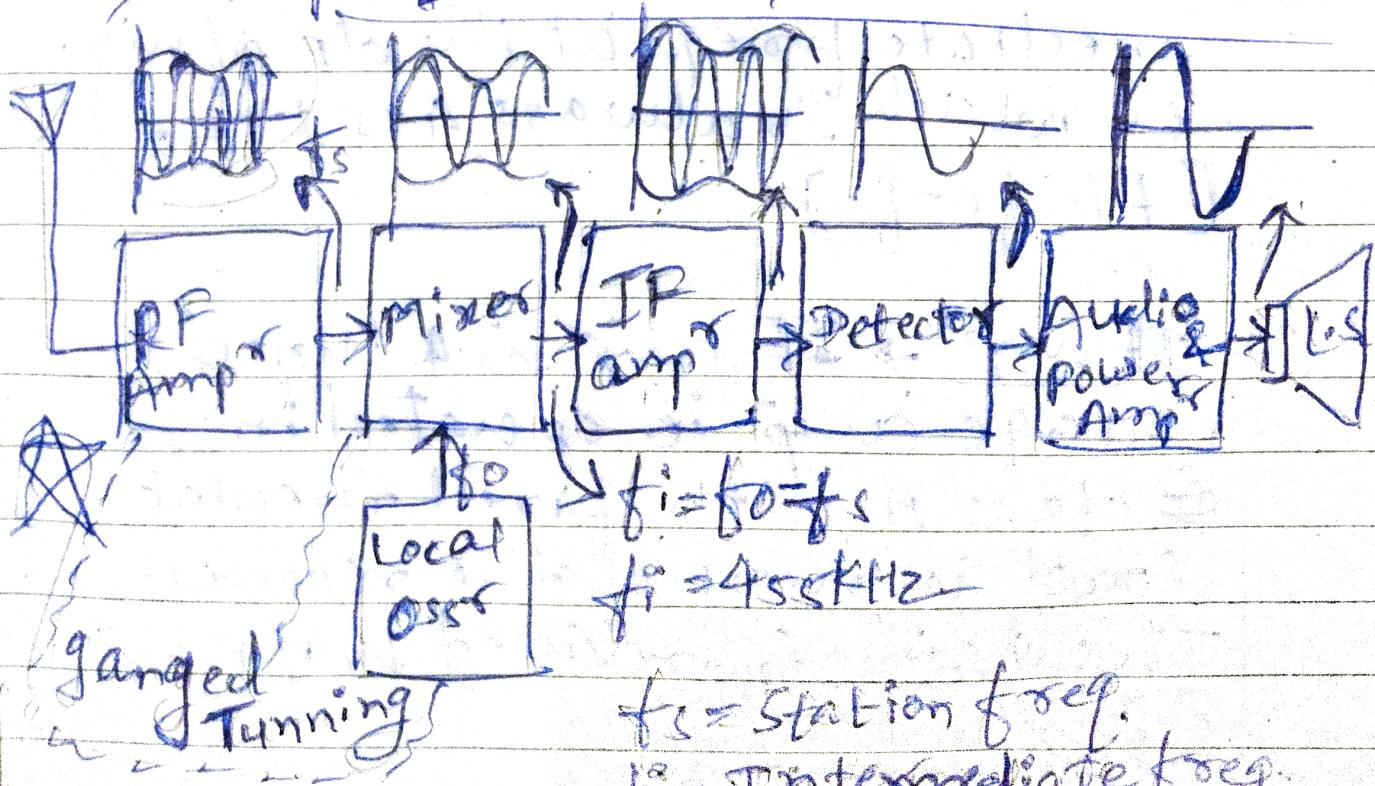

$$f_S = \text{Station freq.}$$

$$f_I = \text{Intermediate freq.}$$

Improving Selectivity Reducing the adjacent channel interference.

(1) RF amp → This tuned voltage amp coupled through the antenna to the mixer. It selects the desired signal from the antenna & amplifies them. This stage improves the sensitivity & selectivity of the radio receiver. It also isolates local oscillator circuit from the antenna thereby preventing the local oscillator energy.

(2) Mixer & local oscillator (conversion stage)
It is a conversion stage in super heterodyne receiver. The RF amp, mixer, & the local oscillator are gang-tuned together to produce intermediate freq. at the diff of mixer which is always 455 kHz ($f_i = f_o - f_s$).

(3) IF amp → IF amp is a tuned voltage amp ie. operated in class A with fixed rheostat load in most of the receiver. The gain is provided by IF amp.

(4) Detector → The amplified signal is fed to the ~~demodulator~~ detector or demodulator. It recovers the original information from the amplitude modulated wave.


(5) Audio & Power amp.

Audio amp amplifies the incoming signal & power amp generates the required power to drive the loud speaker.

(6) Coupling speakers → It converts electrical energy into sound energy.

Parameters of AM radio receiver.

* Sensitivity

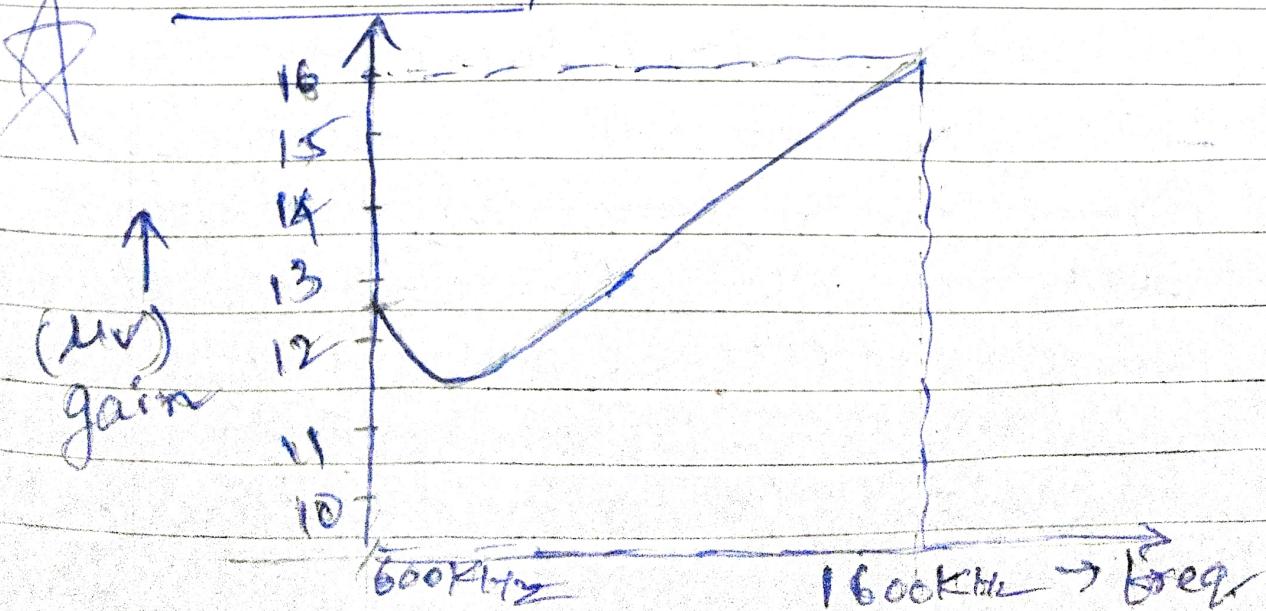

Sensitivity of the radio receiver is to amplify the weak signal. Mathematically the sensitivity of radio receiver is defined as a carrier voltage which must be applied to the receiver input terminal.

Sensitivity of a radio receiver is expressed in microvolts & millivolts or in decibels below one volt.


The sensitivity may be measured at various carrier frequencies in a given band. From the graph it is seen that sensitivity varies over the tuning band. At 1600 Hz this particular receiver has a sensitivity of 12.7 Microvolts or -98 decibel volts (below 1volt). Sometimes sensitivity definition is extended & the manufacturer of this receiver may quote to be 12.7 Microvolts for signal to noise ratio of 20 dB in

the op of the receiver.

~~Frequency response~~

The most important factor determining the sensitivity of superhetodyne receiver are the gain of the ~~IF~~ ^{I_F} amp & that of the RF amp.

* Selectivity

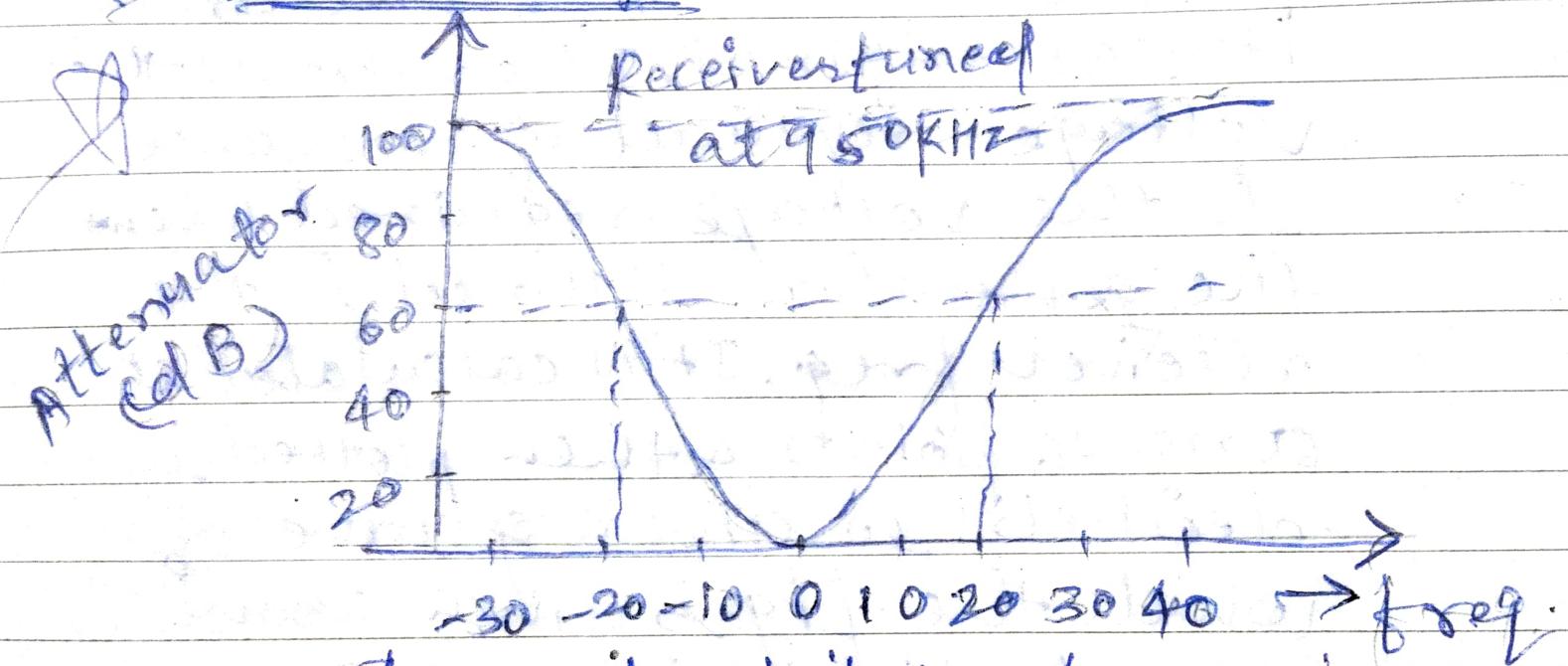

The selectivity of receiver is its ability to reject the unwanted signals. It is expressed as a curve such as the fig. shows.

The attenuation that the receiver offers to the signal at frequencies near to the one to which it is tuned. Selectivity is measured at the end of the sensitivity test.

with conditions the same as for sensitivity except that now the freq. of the generator is varied to either side of freq. to which the receiver is tuned. The d.p. of the receiver naturally falls, since the ilp freq. is now incorrect. The ilp voltage must be used until the d.p. is same as it was original. The ratio of the voltage required of resonance to the voltage required when the generator is tuned to the receiver freq. It is calculated at a no. of points & then plotted in decibels to give a curve of which the fig is given above.

Looking at the curve we see that, at 20 kHz below the receiver tuned freq & the interfering signal would have to be 60dB greater than the wanted signal to come out with the same amplitude.

Selectivity varies with the receiver freq; if ordinary tuned

$$f_i = f_0 - f_s$$

$$f_{si} = f_0 + f_i$$

$$f_{si} = f_s + 2f_i$$

hence

TOTAL

Circuits are used in the IF section & becomes somewhat worse when the receiving freq is raised. In general it is determined by the response of the RF section, with the mixer & RF amp / IP ckts place a small but significant part. It should be noted that its selectivity determines adjacent channels rejection of a receiver.

Q) Image freq. and its rejection.

In a translocal broadcast receiver the local oscillator freq. is made higher than the incoming signal freq. For reasons that will become apparent, it is made equal at all times to the signal freq. plus the intermediate freq.

$$f_0 = f_s + f_i$$

If the freq. f_{si} manages to reach the mixer such that,

$$f_{si} = f_0 + f_i \rightarrow ①$$

$$\text{i.e. } f_{si} = f_s + f_i + f_i : f_0 = f_s + f_i$$

$$\therefore f_{si} = f_s + 2f_i$$

where, f_{si} = image freq.

Then this freq. will also produce 'f_i' when mixed with 'f_o'. This IF signal can also be amplified by the IF stage, & will so provide interference.

The term 'f_{si}' is called as image freq. & is defined as the signal freq. plus twice the intermediate freq. i.e. $f_{si} = f_s + 2f_i$.

A) Image freq. rejection.

To avoid interference due to image freq. signal it is necessary that these signals do not reach the mixer. This can be achieved firstly by using the no. of tuned ckt's. betw the antenna & mixer & secondly by giving there selectivity against image freq. signals.

* choice of Intermediate freq.

The following are the major factors affecting the choice of Intermediate freq. in a particular system.

- 1) If the IF is too high, poor selectivity & poor adjacent channel rejection.
- 2) A high value of Intermediate freq. poses tracking difficulties.
- 3) As the intermediate freq. is lowered image freq. rejection becomes poor.
- (4) If the IF is very low the freq. stability of local oscillator must be made correspondingly higher because any freq. drift is now larger proportion of the lower IF than the higher IF.
- 5) IF must not fall within the tuning range of the receiver, or else the instability will occur & hydrodyne whistle will be heard, making it possible to tune the freq. band.