

# Graph Theory

## 5.1 || INTRODUCTION

The purpose of network analysis is to find voltage across and current through all the elements. When the network is complicated and has a large number of nodes and closed paths, network analysis can be done conveniently by using 'Network Topology'. This theory does not make any distinction between different types of physical elements of the network but makes the study based on a geometric pattern of the network. The basic elements of this theory are nodes, branches, loops and meshes.

**Node** It is defined as a point at which two or more elements have a common connection.

**Branch** It is a line connecting a pair of nodes, the line representing a single element or series connected elements.

**Loop** Whenever there is more than one path between two nodes, there is a circuit or loop.

**Mesh** It is a loop which does not contain any other loops within it.

## 5.2 || GRAPH OF A NETWORK


A linear graph is a collection of nodes and branches. The nodes are joined together by branches.

The graph of a network is drawn by first marking the nodes and then joining these nodes by lines which correspond to the network elements of each branch. All the voltage and current sources are replaced by their internal impedances. The voltage sources are replaced by short circuits as their internal impedances are zero whereas current sources are replaced by open circuits as their internal impedances are infinite. Nodes and branches are numbered. Figure 5.1 shows a network and its associated graphs.

Each branch of a graph may be given an orientation or a direction with the help of an arrow head which represents the assigned reference direction for current. Such a graph is then referred to as a directed or oriented graph.

Branches whose ends fall on a node are said to be incident at that node. Degree of a node is defined as the number of branches incident to it. Branches 2, 3 and 4 are incident at Node 2 in Fig. 5.1(c). Hence, the degree of Node 2 is 3.


## 5.2 Circuit Theory and Networks—Analysis and Synthesis

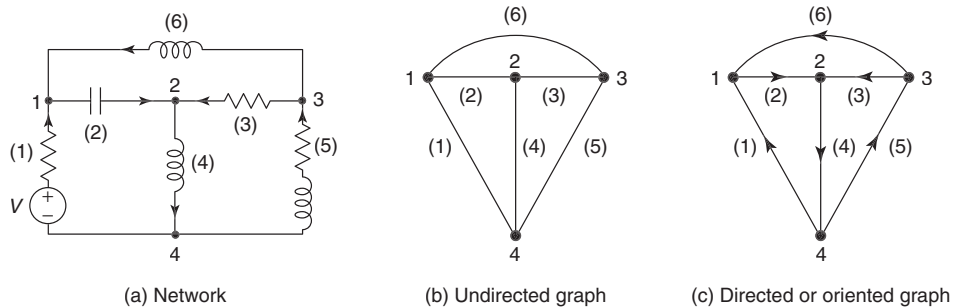

**Fig. 5.1** Network and its graphs


## 5.3 GRAPH TERMINOLOGIES

**1. Planar Graph** A graph drawn on a two-dimensional plane is said to be planar if two branches do not intersect or cross at a point which is other than a node. Figure 5.2 shows such graphs.

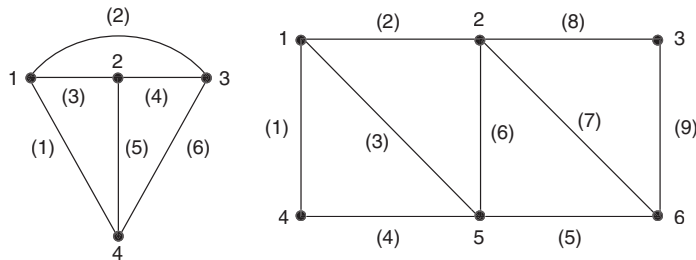


**Fig. 5.2** Planar graphs

**2. Non-planar Graph** A graph drawn on a two-dimensional plane is said to be non-planar if there is intersection of two or more branches at another point which is not a node. Figure 5.3 shows non-planar graphs.

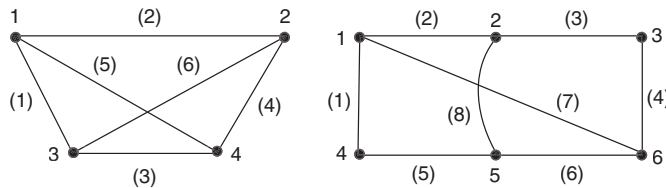

**Fig. 5.3** Non-planar graphs

**3. Sub-graph** It is a subset of branches and nodes of a graph. It is a proper sub-graph if it contains branches and nodes less than those on a graph. A sub-graph can be just a node or only one branch of the graph. Figure 5.4 shows a graph and its proper sub-graph.

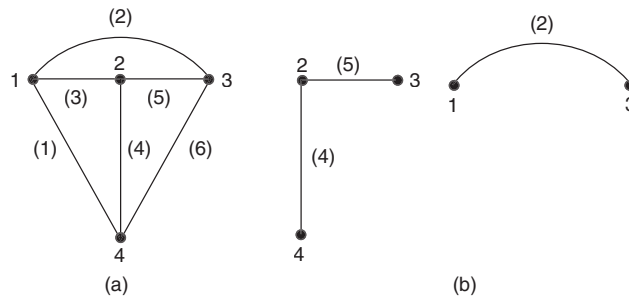


**Fig. 5.4** (a) Graph (b) Proper sub-graph

**4. Path** It is an improper sub-graph having the following properties:

1. At two of its nodes called terminal nodes, there is incident only one branch of sub-graph.
2. At all remaining nodes called internal nodes, there are incident two branches of a graph.

In Fig. 5.5, branches 2, 5 and 6 together with all the four nodes, constitute a path.

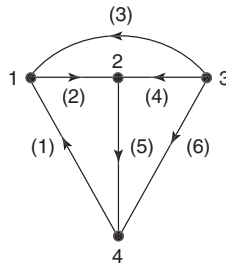


**Fig. 5.5** Path

**5. Connected Graph** A graph is said to be connected if there exists a path between any pair of nodes. Otherwise, the graph is disconnected.

**6. Rank of a Graph** If there are  $n$  nodes in a graph, the rank of the graph is  $(n - 1)$ .

**7. Loop or Circuit** A loop is a connected sub-graph of a connected graph at each node of which are incident exactly two branches. If two terminals of a path are made to coincide, it will result in a loop or circuit.

Figure 5.6 shows two loops.

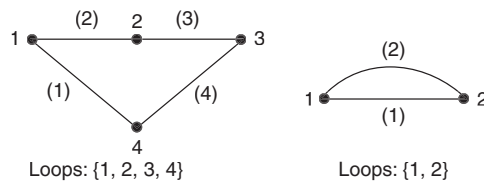

**Fig. 5.6** Loops

Loops of a graph have the following properties:


1. There are at least two branches in a loop.
2. There are exactly two paths between any pair of nodes in a circuit.
3. The maximum number of possible branches is equal to the number of nodes.

## 5.4 Circuit Theory and Networks—Analysis and Synthesis

**8. Tree** A tree is a set of branches with every node connected to every other node in such a way that removal of any branch destroys this property.

Alternately, a tree is defined as a connected sub-graph of a connected graph containing all the nodes of the graph but not containing any loops.

Branches of a tree are called twigs. A tree contains  $(n - 1)$  twigs where  $n$  is the number of nodes in the graph. Figure 5.7 shows a graph and its trees.

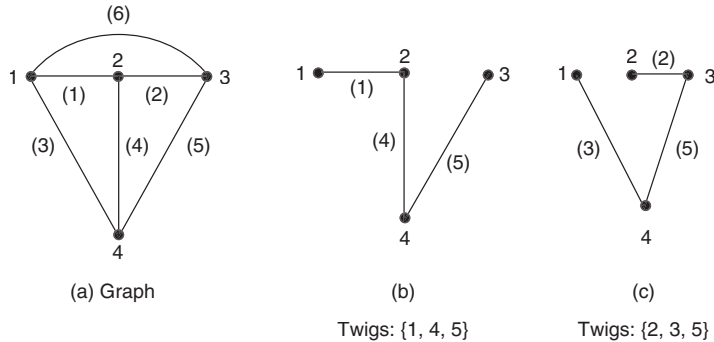

**Fig. 5.7** Graph and its trees

Trees have the following properties:


1. There exists only one path between any pair of nodes in a tree.
2. A tree contains all nodes of the graph.
3. If  $n$  is the number of nodes of the graph, there are  $(n - 1)$  branches in the tree.
4. Trees do not contain any loops.
5. Every connected graph has at least one tree.
6. The minimum terminal nodes in a tree are two.

**9. Co-tree** Branches which are not on a tree are called links or chords. All links of a tree together constitute the complement of the corresponding tree and is called the co-tree.

A co-tree contains  $b - (n - 1)$  links where  $b$  is the number of branches of the graph.

In Fig. 5.7 (b) and (c) the links are  $\{2, 3, 6\}$  and  $\{1, 4, 6\}$  respectively.

**Example 5.1** Draw directed graph of the networks shown in Fig. 5.8.

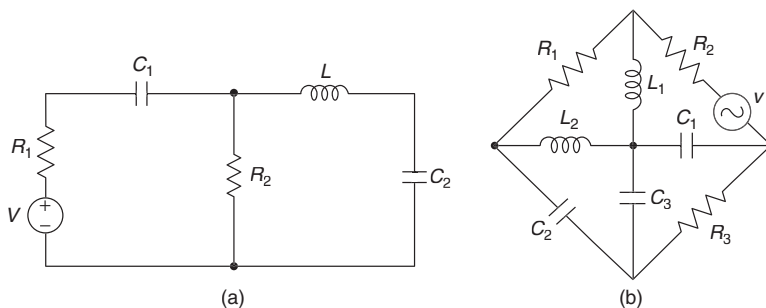

**Fig. 5.8**

**Solution** For drawing the directed graph,

1. replace all resistors, inductors and capacitors by line segments,
2. replace the voltage source by a short-circuit,
3. assume directions of branch currents, and
4. number all the nodes and branches.

The directed graph for the two networks are shown in Fig. 5.9.

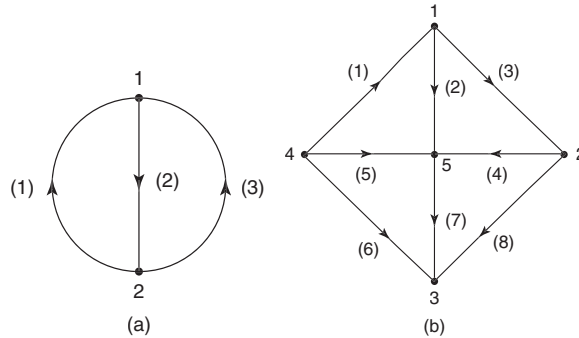


Fig. 5.9

### Example 5.2

Figure 5.10 shows a graph of the network. Show all the trees of this graph.

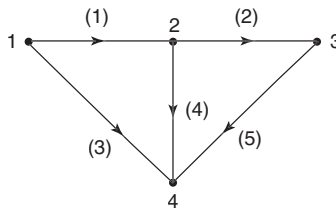


Fig. 5.10

**Solution** A graph has many trees. A tree is a connected sub-graph of a connected graph containing all the nodes of the graph but not containing any loops. Figure 5.11 shows various trees of the given graph.

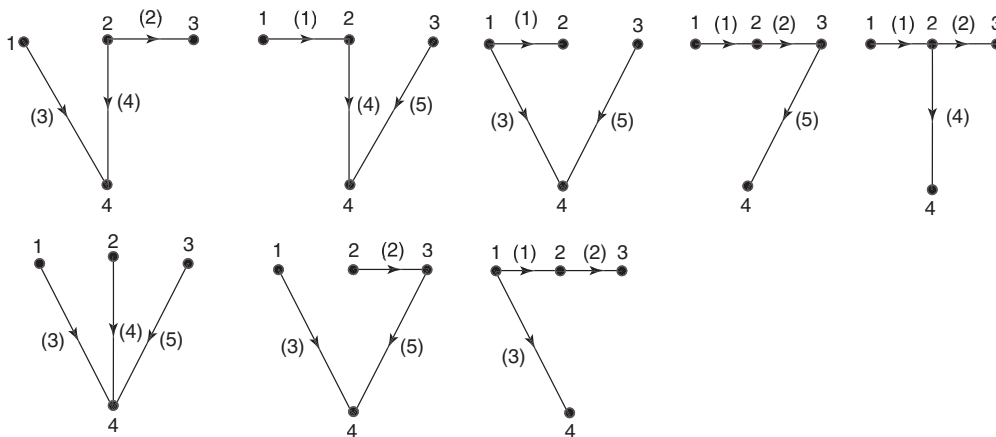


Fig. 5.11

## 5.4 INCIDENCE MATRIX

A linear graph is made up of nodes and branches. When a graph is given, it is possible to tell which branches are incident at which nodes and what are its orientations relative to the nodes.

### 5.4.1 Complete Incidence Matrix ( $A_a$ )

For a graph with  $n$  nodes and  $b$  branches, the complete incidence matrix is a rectangular matrix of order  $n \times b$ . Elements of this matrix have the following values:

$$\begin{aligned} a_{ij} &= 1, \text{ if branch } j \text{ is incident at node } i \text{ and is oriented away from node } i. \\ &= -1, \text{ if branch } j \text{ is incident at node } i \text{ and is oriented towards node } i. \\ &= 0, \text{ if branch } j \text{ is not incident at node } i. \end{aligned}$$

For the graph shown in Fig. 5.12, branch 1 is incident at nodes 1 and 4. It is oriented away from Node 1 and oriented towards Node 4. Hence,  $a_{11} = 1$  and  $a_{41} = -1$ . Since branch 1 is not incident at nodes 2 and 3,  $a_{21} = 0$  and  $a_{31} = 0$ . Similarly, other elements of the complete incidence matrix are written.

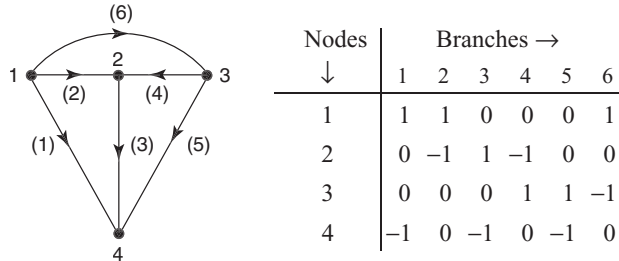


Fig. 5.12 Graph

The complete incidence matrix is

$$A_a = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 1 & -1 \\ -1 & 0 & -1 & 0 & -1 & 0 \end{bmatrix}$$

It is seen from the matrix  $A_a$  that the sum of the elements in any column is zero. Hence, any one row of the complete incidence matrix can be obtained by the algebraic manipulation of other rows.

### 5.4.2 Reduced Incidence Matrix ( $A$ )

The reduced incidence matrix  $A$  is obtained from the complete incidence matrix  $A_a$  by eliminating one of the rows. It is also called *incidence matrix*. It is of order  $(n - 1) \times b$ .

Eliminating the third row of matrix  $A_a$ ,

$$A = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ -1 & 0 & -1 & 0 & -1 & 0 \end{bmatrix}$$

When a tree is selected for the graph as shown in Fig. 5.13, the incidence matrix is obtained by arranging a column such that the first  $(n - 1)$  column corresponds to twigs of the tree and the last  $b - (n - 1)$  branches corresponds to the links of the selected tree.

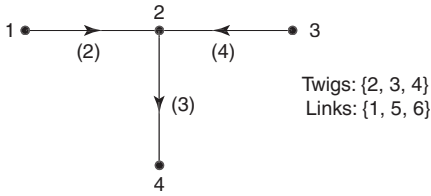


Fig. 5.13 Tree

$$A = \begin{array}{c} \begin{array}{ccc} \text{Twigs} & & \text{Links} \\ & 2 & 3 & 4 & 1 & 5 & 6 \end{array} \\ \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 1 \\ -1 & 1 & -1 & 0 & 0 & 0 \\ 0 & -1 & 0 & -1 & -1 & 0 \end{bmatrix} \end{array}$$

The matrix  $A$  can be subdivided into submatrices  $A_t$  and  $A_l$ .

$$A = [A_t : A_l]$$

Where  $A_t$  is the twig matrix and  $A_l$  is the link matrix.

### 5.4.3 Number of Possible Trees of a Graph

Let the transpose of the reduced incidence matrix  $A$  be  $A^T$ . It can be shown that the number of possible trees of a graph will be given by

$$\text{Number of possible trees} = |AA^T|$$

For the graphs shown in Fig. 5.12, the reduced incidence matrix is given by

$$A = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ -1 & 0 & -1 & 0 & -1 & 0 \end{bmatrix}$$

Then transpose of this matrix will be

$$A^T = \begin{bmatrix} 1 & 0 & -1 \\ 1 & -1 & 0 \\ 0 & 1 & -1 \\ 0 & -1 & 0 \\ 0 & 0 & -1 \\ 1 & 0 & 0 \end{bmatrix}$$

Hence, number of all possible trees of the graph

$$AA^T = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ -1 & 0 & -1 & 0 & -1 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & -1 \\ 1 & -1 & 0 \\ 0 & 1 & -1 \\ 0 & -1 & 0 \\ 0 & 0 & -1 \\ 1 & 0 & 0 \end{bmatrix} = \begin{bmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix}$$

$$|AA^T| = \begin{vmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{vmatrix} = 3(9-1) + (1)(-3-1) - 1(1+3) = 16$$

Thus, 16 different trees can be drawn.

## 5.5 LOOP MATRIX OR CIRCUIT MATRIX

When a graph is given, it is possible to tell which branches constitute which loop or circuit. Alternately, if a loop matrix or circuit matrix is given, we can reconstruct the graph.

For a graph having  $n$  nodes and  $b$  branches, the loop matrix  $B_a$  is a rectangular matrix of order  $b$  columns and as many rows as there are loops.

Its elements have the following values:

- $b_{ij} = 1$ , if branch  $j$  is in loop  $i$  and their orientations coincide.
- $= -1$ , if branch  $j$  is in loop  $i$  and their orientations do not coincide.
- $= 0$ , if branch  $j$  is not in loop  $i$ .

A graph and its loops are shown in Fig. 5.14.

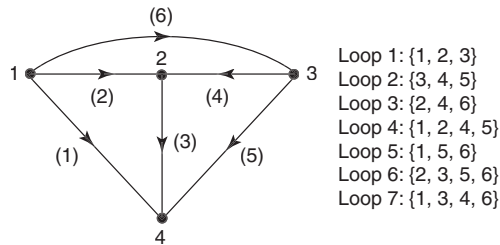


Fig. 5.14 Graph

All the loop currents are assumed to be flowing in a clockwise direction.

Loops ↓	Branches →					
	1	2	3	4	5	6
1	-1	1	1	0	0	0
2	0	0	-1	-1	1	0
3	0	-1	0	1	0	1
4	-1	1	0	-1	1	0
5	-1	0	0	0	1	1
6	0	-1	-1	0	1	1
7	-1	0	1	1	0	1


$$B_a = \begin{bmatrix} -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & -1 & -1 & 1 & 0 \\ 0 & -1 & 0 & 1 & 0 & 1 \\ -1 & 1 & 0 & -1 & 1 & 0 \\ -1 & 0 & 0 & 0 & 1 & 1 \\ 0 & -1 & -1 & 0 & 1 & 1 \\ -1 & 0 & 1 & 1 & 0 & 1 \end{bmatrix}$$

### 5.5.1 Fundamental Circuit (Tieset) and Fundamental Circuit Matrix

When a graph is given, first select a tree and remove all the links. When a link is replaced, a closed loop or circuit is formed. Circuits formed in this way are called fundamental circuits or  $f$ -circuits or tiesets.

Orientation of an  $f$ -circuit is given by the orientation of the connecting link. The number of  $f$ -circuits is same as the number of links for a graph. In a graph having  $b$  branches and  $n$  nodes, the number of  $f$ -circuits or tiesets will be  $(b - n + 1)$ . Figure 5.15 shows a tree and  $f$ -circuits (tiesets) for the graph shown in Fig. 5.14.

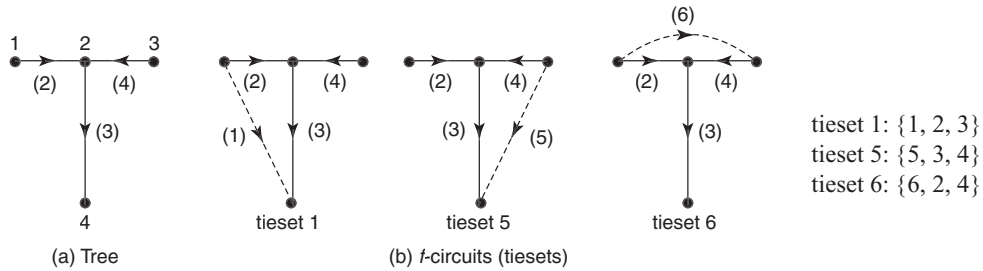

Fig. 5.15 Tree and  $f$ -circuits

Here,  $b = 6$  and  $n = 4$ .

$$\text{Number of tiesets} = b - n + 1 = 6 - 4 + 1 = 3$$

$f$ -circuits are shown in Fig. 5.15. The orientation of each  $f$ -circuit is given by the orientation of the corresponding connecting link.

The branches 1, 2 and 3 are in the tieset 1. Orientation of tieset 1 is given by orientation of branch 1. Since the orientation of branch 1 coincides with orientation of tieset 1,  $b_{11} = 1$ . The orientations of branches 2 and 3 do not coincide with the orientation of tieset 1, Hence,  $b_{12} = -1$  and  $b_{13} = -1$ . The branches 4, 5 and 6 are not in tieset 1. Hence,  $b_{14} = 0$ ,  $b_{15} = 0$  and  $b_{16} = 0$ . Similarly, other elements of the tieset matrix are written. Then, the tieset schedule will be written as

Tiesets ↓	Branches →					
	1	2	3	4	5	6
1	1	-1	-1	0	0	0
5	0	0	-1	-1	1	0
6	0	-1	0	1	0	1

Hence, an  $f$ -circuit matrix or tieset matrix will be given as

$$B = \begin{bmatrix} 1 & -1 & -1 & 0 & 0 & 0 \\ 0 & 0 & -1 & -1 & 1 & 0 \\ 0 & -1 & 0 & 1 & 0 & 1 \end{bmatrix}$$

Usually, the  $f$ -circuit matrix  $B$  is rearranged so that the first  $(n - 1)$  columns correspond to the twigs and  $b - (n - 1)$  columns to the links of the selected tree.

	Twigs			Links		
	2	3	4	1	5	6

$$B = \begin{bmatrix} -1 & -1 & 0 & 1 & 0 & 0 \\ 0 & -1 & -1 & 0 & 1 & 0 \\ -1 & 0 & 1 & 0 & 0 & 1 \end{bmatrix}$$

The matrix  $B$  can be partitioned into two matrices  $B_t$  and  $B_l$ .

$$B = [B_t : B_l] = [B_t : U]$$

where  $B_t$  is the twig matrix,  $B_l$  is the link matrix and  $U$  is the unit matrix.

### 5.5.2 Orthogonal Relationship between Matrix A and Matrix B

For a linear graph, if the columns of the two matrices  $A_a$  and  $B_a$  are arranged in the same order, it can be shown that

$$A_a B_a^T = 0$$

or

$$B_a A_a^T = 0$$

The above equations describe the orthogonal relationship between the matrices  $A_a$  and  $B_a$ .

If the reduced incidence matrix  $A$  and the  $f$ -circuit matrix  $B$  are written for the same tree, it can be shown that

$$A B^T = 0$$

or

$$B A^T = 0$$

These two equations show the orthogonal relationship between matrices  $A$  and  $B$ .

## 5.6 CUTSET MATRIX

Consider a linear graph. By removing a set of branches without affecting the nodes, two connected sub-graphs are obtained and the original graph becomes unconnected. The removal of this set of branches which results in cutting the graph into two parts are known as a *cutset*. The cutset separates the nodes of the graph into two groups, each being in one of the two groups.

Figure 5.16 shows a graph.

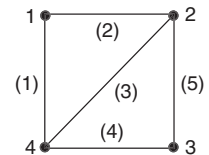


Fig. 5.16 Graph


Branches 1, 3 and 4 will form a cutset. This set of branches separates the graph into two parts. One having an isolated node 4 and other part having branches 2 and 5 and nodes 1, 2 and 3.

Similarly, branches 1 and 2 will form a cutset. Each branch of the cutset has one of its terminals incident at a node in one part and its other end incident at other nodes in the other parts. The orientation of a cutset is made to coincide with orientation of defining branch.

For a graph having  $n$  nodes and  $b$  branches, the cutset matrix  $Q_a$  is a rectangular matrix of order  $b$  columns and as many rows as there are cutsets. Its elements have the following values:

- $q_{ij} = 1$ , if the branch  $j$  is in the cutset  $i$  and the orientation coincide.
- $= -1$ , if the branch  $j$  is in the cutset  $i$  and the orientations do not coincide.
- $= 0$ , if the branch  $j$  is not in the cutset  $i$ .

Figure 5.17 shows a directed graph and its cutsets.

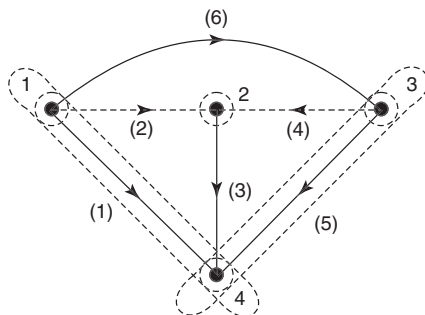

- Cutset 1: {1, 2, 6}
- Cutset 2: {2, 3, 4}
- Cutset 3: {3, 1, 5}
- Cutset 4: {4, 5, 6}
- Cutset 5: {5, 2, 3, 6}
- Cutset 6: {6, 1, 3, 4}

Cutsets ↓	Branches →					
	1	2	3	4	5	6
1	1	1	0	0	0	1
2	0	1	-1	1	0	0
3	1	0	1	0	1	0
4	0	0	0	1	1	-1
5	0	-1	1	0	1	-1
6	1	0	1	-1	0	1

Fig. 5.17 Directed graph

For the cutset 2, which cuts the branches 2, 3 and 4 and is shown by a dotted circle, the entry in the cutset schedule for the branch 2 is 1, since the orientation of this cutset is given by the orientation of the branch 2 and hence it coincides. The entry for branch 3 is  $-1$  as orientation of branch 3 is opposite to that of cutset 2,

i.e., branch 2 goes into cutset while branch 3 goes out of cutset. The entry for branch 4 is 1 as the branch 2 and the branch 4 go into the cutset. Thus their orientations coincide.

Hence, the cutset matrix  $Q_a$  is given as

$$Q_a = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & -1 & 1 & 0 & 0 \\ 1 & 0 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & 1 & -1 \\ 0 & -1 & 1 & 0 & 1 & -1 \\ 1 & 0 & 1 & -1 & 0 & 1 \end{bmatrix}$$

### 5.6.1 Fundamental Cutset and Fundamental Cutset Matrix

When a graph is given, first select a tree and note down its twigs. When a twig is removed from the tree, it separates a tree into two parts (one of the separated part may be an isolated node). Now, all the branches connecting one part of the disconnected tree to the other along with the twig removed, constitutes a cutset. This set of branches is called a fundamental cutset or  $f$ -cutset. A matrix formed by these  $f$ -cutsets is called an  $f$ -cutset matrix. The orientation of the  $f$ -cutset is made to coincide with the orientation of the defining branch, i.e., twig. The number of  $f$ -cutsets is the same as the number of twigs for a graph.

Figure 5.18 shows a graph, selected tree and  $f$ -cutsets corresponding to the selected tree.

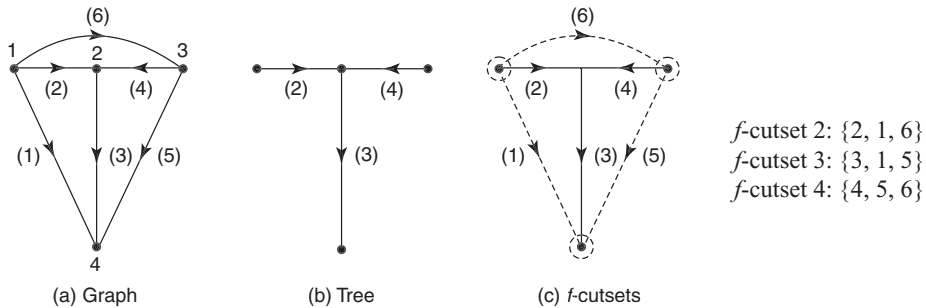


Fig. 5.18 Graph, selected tree and  $f$ -cutsets

The branches 2, 1, and 6 are in the  $f$ -cutset 2. Orientation of  $f$ -cutset 2 is given by orientation of the branch 2 which is moving away from the  $f$ -cutset 2. Since the orientations of branches 2, 1 and 6 coincide with the orientation of the  $f$ -cutset 2,  $q_{11} = 1$ ,  $q_{12} = 1$  and  $q_{16} = 0$ . The branches 3, 4 and 5 are not in the  $f$ -cutset 2. Hence,  $q_{13} = 0$ ,  $q_{14} = 0$  and  $q_{15} = 0$ .

Similarly, other elements of the  $f$ -cutset matrix are written.

The cutset schedule is

$f$ -cutsets	Branches $\rightarrow$					
$\downarrow$	1	2	3	4	5	6
2	1	1	0	0	0	1
3	1	0	1	0	1	0
4	0	0	0	1	1	-1

Hence, the  $f$ -cutset matrix  $Q$  is given by

$$Q = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 1 & 0 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & 1 & -1 \end{bmatrix}$$

The  $f$ -cutset matrix  $Q$  is rearranged so that the first  $(n - 1)$  columns correspond to twigs and  $b - (n - 1)$  columns to links of the selected tree.

## 5.12 Circuit Theory and Networks—Analysis and Synthesis

$$\begin{array}{c}
 \text{Twigs} \qquad \qquad \text{Links} \\
 \begin{array}{ccc} 2 & 3 & 4 \end{array} \quad \begin{array}{ccc} 1 & 5 & 6 \end{array} \\
 Q = \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & 1 & 1 & 0 \\ 0 & 0 & 1 & 0 & 1 & -1 \end{bmatrix}
 \end{array}$$

The matrix  $Q$  can be subdivided into matrices  $Q_t$  and  $Q_l$ .

$$Q = [Q_t : Q_l] = [U : Q_l]$$

where  $Q_t$  is the twig matrix,  $Q_l$  is the link matrix and  $U$  is the unit matrix.

### 5.6.2 Orthogonal Relationship between Matrix B and Matrix Q

For a linear graph, if the columns of two matrices  $B_a$  and  $Q_a$  are arranged in the same order, it can be shown that

$$Q_a B_a^T = 0$$

or

$$B_a Q_a^T = 0$$

If the  $f$ -circuit matrix  $B$  and the  $f$ -cutset matrix  $Q$  are written for the same selected tree, it can be shown that

$$B Q^T = 0$$

or

$$Q B^T = 0$$

These two equations show the orthogonal relationship between matrices  $A$  and  $B$ .

## 5.7 || RELATIONSHIP AMONG SUBMATRICES OF A, B AND Q

Arranging the columns of matrices  $A$ ,  $B$  and  $Q$  with twigs for a given tree first and then the links, we get the partitioned forms as

$$A = [A_t : A_l]$$

$$B = [B_t : B_l] = [B_t : U]$$

$$Q = [Q_t : Q_l] = [U : Q_l]$$

From the orthogonal relation,  $AB^T = 0$ ,

$$AB^T = [A_t : A_l] \begin{bmatrix} B_t^T \\ \dots \\ B_l^T \end{bmatrix}$$

$$A_t B_t^T + A_l B_l^T = 0$$

$$A_t B_t^T = -A_l B_l^T$$

Since  $A_t$  is non-singular, i.e.,  $|A| \neq 0$ ,  $A_t^{-1}$  exists.

Premultiplying with  $A_t^{-1}$ ,

$$B_t^T = -A_t^{-1} A_l B_l^T$$

$$B_l = -B_l (A_t^{-1} \cdot A_l)^T$$

Since  $B_l$  is a unit matrix

$$B_l = -(A_t^{-1} \cdot A_l)^T$$

Hence, matrix  $B$  is written as

$$B = [-(A_t^{-1} \cdot A_t)^T : U] \quad \dots(5.1)$$

We know that

$$AB^T = 0$$

$$A_t B_t^T = -A_t B_t^T$$

Postmultiplying with  $(B_t^T)^{-1}$ ,

$$A_t = -A_t B_t^T (B_t^T)^{-1} = -A_t B_t^T (B_t^{-1})^T = -A_t (B_t^{-1} \cdot B_t)^T$$

Hence matrix  $A$  can be written as

$$\begin{aligned} A &= [A_t : -A_t (B_t^{-1} \cdot B_t)^T] \\ &= A_t [U : -(B_t^{-1} \cdot B_t)^T] \end{aligned} \quad \dots(5.2)$$

Similarly we can prove that

$$Q = [U : -(B_t^{-1} \cdot B_t)^T] \quad \dots(5.3)$$

From Eqs (5.2) and (5.3), we can write

$$A = A_t Q$$

$$Q = A_t^{-1} A = A_t^{-1} [A_t : A_t] = [U : A_t^{-1} A_t]$$

We have shown that

$$B_t = -(A_t^{-1} \cdot A_t)^T$$

$$B_t^T = -(A_t^{-1} \cdot A_t)$$

Hence,  $Q$  can be written as

$$Q = [U : -B_t^T]$$

$$Q_1 = -B_t^T$$

**Example 5.3** For the circuit shown in Fig. 5.19, draw the oriented graph and write the (a) incidence matrix, (b) tieset matrix, and (c) f-cutset matrix.

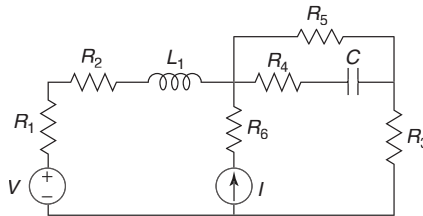


Fig. 5.19

**Solution** For drawing the oriented graph,

1. replace all resistors, inductors and capacitors by line segments,
2. replace the voltage source by short circuit and the current source by an open circuit,
3. assume the directions of branch currents arbitrarily, and
4. number all the nodes and branches.

The oriented graph is shown in Fig. 5.20.

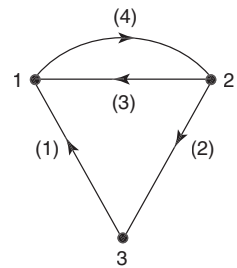


Fig. 5.20

### 5.14 Circuit Theory and Networks—Analysis and Synthesis

(a) Incidence Matrix ( $A$ )

Nodes ↓	Branches →			
	1	2	3	4
1	-1	0	-1	1
2	0	1	1	-1
3	1	-1	0	0

$$A_a = \begin{bmatrix} -1 & 0 & -1 & 1 \\ 0 & 1 & 1 & -1 \\ 1 & -1 & 0 & 0 \end{bmatrix}$$

Eliminating the third row from the matrix  $A_a$ , we get the incidence matrix  $A$ .

$$A = \begin{bmatrix} -1 & 0 & -1 & 1 \\ 0 & 1 & 1 & -1 \end{bmatrix}$$

(b) Tieset Matrix ( $B$ )

The oriented graph, selected tree and tiesets are shown in Fig. 5.21.

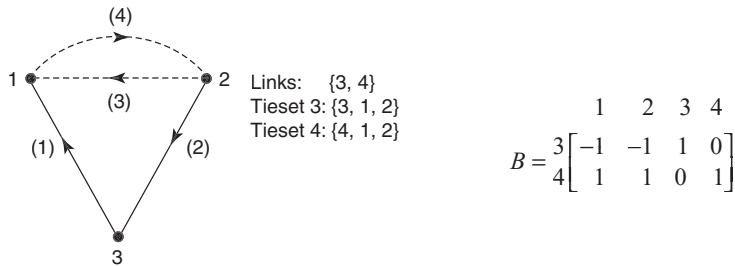


Fig. 5.21

(c)  $f$ -cutset Matrix ( $Q$ )

The oriented graph, selected tree and  $f$ -cutsets are shown in Fig. 5.22.

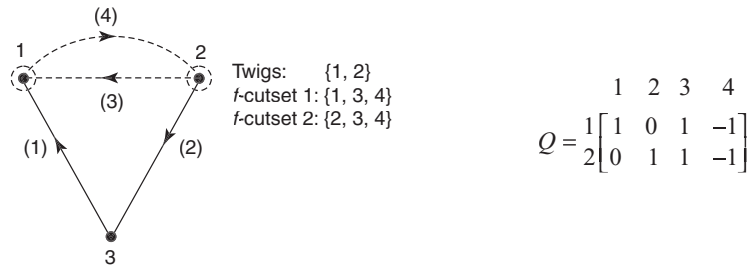


Fig. 5.22

**Example 5.4** For the network shown in Fig. 5.23, draw the oriented graph and write the (a) incidence matrix, (b) tieset matrix, and (c)  $f$ -cutset matrix.

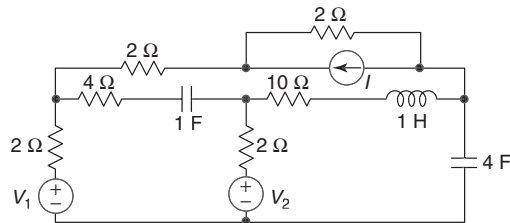


Fig. 5.23

**Solution** For drawing the oriented graph,

1. replace all resistors, inductors and capacitors by line segments,
2. replace all voltage sources by short circuits and current source by an open circuit,
3. assume directions of branch currents arbitrarily, and
4. number all the nodes and branches.

The oriented graph is shown in Fig. 5.24.

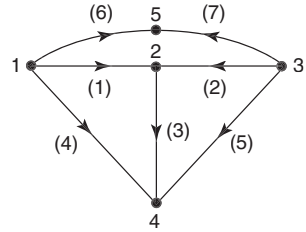


Fig. 5.24

(a) Incidence Matrix ( $A$ )

Nodes ↓	Branches →						
	1	2	3	4	5	6	7
1	1	0	0	1	0	1	0
2	-1	-1	1	0	0	0	0
3	0	1	0	0	1	0	1
4	0	0	-1	-1	-1	0	0
5	0	0	0	0	0	-1	-1

$$A_a = \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 1 & 0 \\ -1 & -1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 0 & -1 & -1 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & -1 \end{bmatrix}$$

Eliminating the last row from the matrix  $A_a$ , we get the incidence matrix  $A$ .

$$A = \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 1 & 0 \\ -1 & -1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 0 & -1 & -1 & -1 & 0 & 0 \end{bmatrix}$$

(b) Tieset Matrix ( $B$ )

The oriented graph, selected tree and tiesets are shown in Fig. 5.25.

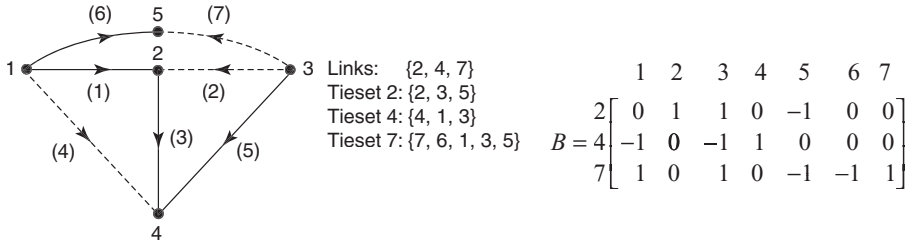


Fig. 5.25

(c)  $f$ -cutset Matrix ( $Q$ )

The oriented graph, selected tree and  $f$ -cutsets are shown in Fig. 5.26.

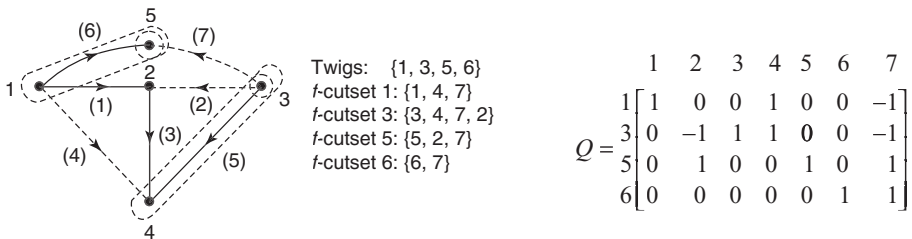


Fig. 5.26

**Example 5.5** For the circuit shown in Fig. 5.27, draw the oriented graph and write (a) incidence matrix, (b) tieset matrix, and (c) cutset matrix.

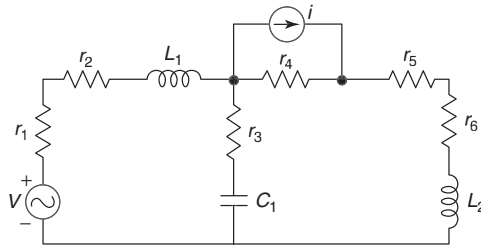


Fig. 5.27

**Solution** For drawing the oriented graph,

1. replace all resistors, inductors and capacitors by line segments,
2. replace voltage source by short circuit and current source by an open circuit,
3. assume directions of branch currents arbitrarily, and
4. number the nodes and branches.

The oriented graph is shown in Fig. 5.28.

(a) Incidence Matrix ( $A$ )

Nodes ↓	Branches →			
	1	2	3	4
1	-1	1	0	-1
2	0	0	1	1
3	1	-1	-1	0

$$A_a = \begin{bmatrix} -1 & 1 & 0 & -1 \\ 0 & 0 & 1 & 1 \\ 1 & -1 & -1 & 0 \end{bmatrix}$$

Eliminating the third row from the matrix  $A_a$ , we get the incidence matrix  $A$ .

$$A = \begin{bmatrix} -1 & 1 & 0 & -1 \\ 0 & 0 & 1 & 1 \end{bmatrix}$$

(b) Tieset Matrix ( $B$ )

The oriented graph, selected tree and tiesets are shown in Fig. 5.29.

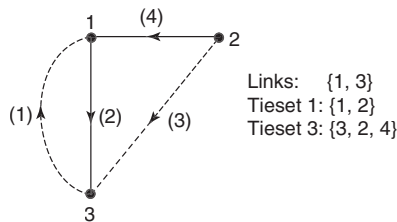



Fig. 5.29

$$B = \begin{bmatrix} 1 & 2 & 3 & 4 \\ 1 & 1 & 0 & 0 \\ 0 & -1 & 1 & -1 \end{bmatrix}$$

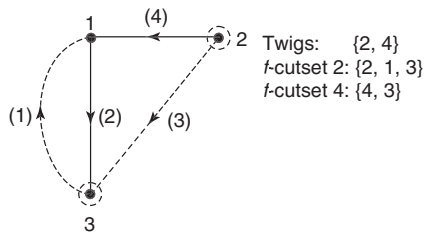(c)  $f$ -cutset Matrix ( $Q$ )

The oriented graph, selected tree and  $f$ -cutsets are shown in Fig. 5.30.





$$Q = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 \end{matrix} \\ \begin{matrix} 2 \\ 4 \end{matrix} & \begin{bmatrix} -1 & 1 & 1 & 0 \\ 0 & 0 & 1 & 1 \end{bmatrix} \end{matrix}$$

Fig. 5.30

**Example 5.6** For the circuit shown in Fig. 5.31, (a) draw its graph, (b) draw its tree, and (c) write the fundamental cutset matrix.

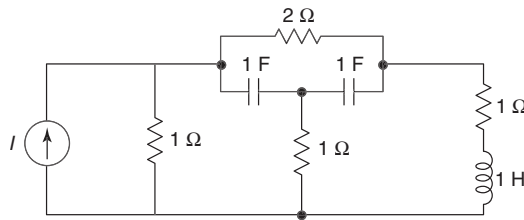


Fig. 5.31

### Solution

- (a) For drawing the oriented graph,
1. replace all resistors, inductors and capacitors by line segments,
  2. replace the current source by an open circuit,
  3. assume directions of branch currents, and
  4. number all the nodes and branches.

The oriented graph is shown in Fig. 5.32.

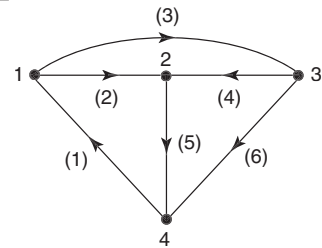


Fig. 5.32

- (b) Tree

The oriented graph and its selected tree are shown in Fig. 5.33.

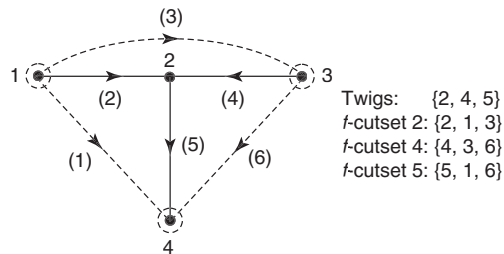


Fig. 5.33

- (c) Fundamental Cutset Matrix ( $Q$ )

$$Q = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 \end{matrix} \\ \begin{matrix} 2 \\ 4 \\ 5 \end{matrix} & \begin{bmatrix} 1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & 1 \\ 1 & 0 & 0 & 0 & 1 & 1 \end{bmatrix} \end{matrix}$$

**Example 5.7** The graph of a network is shown in Fig. 5.34. Write the (a) incidence matrix, (b) tieset matrix, and (c)  $f$ -cutset matrix.

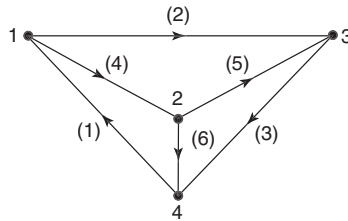


Fig. 5.34

### Solution

(a) Incidence Matrix ( $A$ )

$$A_a = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \end{matrix} & \begin{bmatrix} -1 & 1 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 1 \\ 0 & -1 & 1 & 0 & -1 & 0 \\ 1 & 0 & -1 & 0 & 0 & -1 \end{bmatrix} \end{matrix}$$

The incidence matrix  $A$  is obtained by eliminating any row from the matrix  $A_a$ .

$$A = \begin{bmatrix} -1 & 1 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 1 \\ 0 & -1 & 1 & 0 & -1 & 0 \end{bmatrix}$$

(b) Tieset, Matrix ( $B$ )

The oriented graph, selected tree and tiesets are shown in Fig. 5.35.

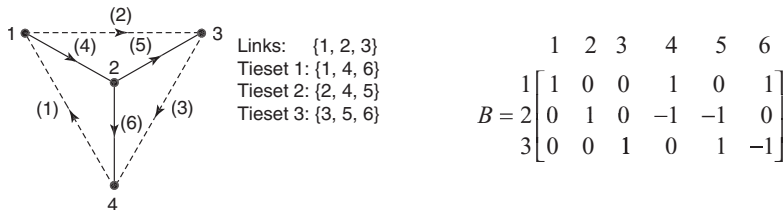


Fig. 5.35

(c)  $f$ -cutset Matrix ( $Q$ )

The oriented graph, selected tree and  $f$ -cutsets are shown in Fig. 5.36.

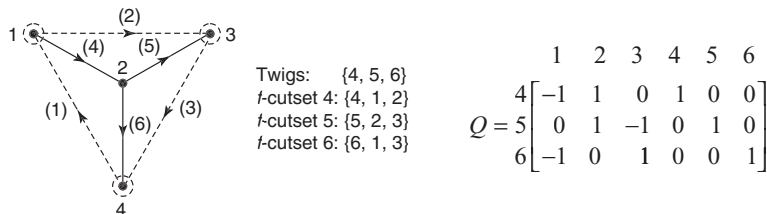


Fig. 5.36

**Example 5.8**

For the graph shown in Fig. 5.37, write the incidence matrix, tieset matrix and  $f$ -cutset matrix.

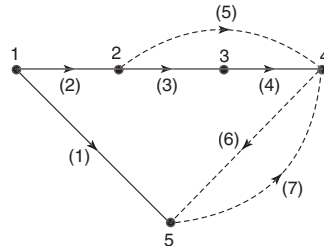


Fig. 5.37

**Solution**

(a) Incidence Matrix ( $A$ )

$$A_a = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \\ 5 \end{matrix} & \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & -1 & 1 & -1 \\ -1 & 0 & 0 & 0 & 0 & -1 & 1 \end{bmatrix} \end{matrix}$$

The incidence matrix  $A$  is obtained by eliminating any row from the matrix  $A_a$ .

$$A = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & -1 & 1 & -1 \end{bmatrix}$$

(b) Tieset Matrix ( $B$ )

Links: {5, 6, 7}

Tieset 5: {5, 3, 4}

Tieset 6: {6, 1, 2, 3, 4}

Tieset 7: {7, 1, 2, 3, 4}

$$B = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \end{matrix} \\ \begin{matrix} 5 \\ 6 \\ 7 \end{matrix} & \begin{bmatrix} 0 & 0 & -1 & -1 & 1 & 0 & 0 \\ -1 & 1 & 1 & 1 & 0 & 1 & 0 \\ 1 & -1 & -1 & -1 & 0 & 0 & 1 \end{bmatrix} \end{matrix}$$

(c)  $f$ -cutset Matrix ( $Q$ )

The oriented graph, selected tree and  $f$ -cutsets are shown in Fig. 5.38.

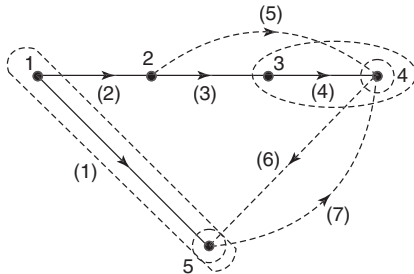


Fig. 5.38

Twigs: {1, 2, 3, 4}  
 $f$ -cutset 1: {1, 6, 7}  
 $f$ -cutset 2: {2, 6, 7}  
 $f$ -cutset 3: {3, 5, 6, 7}  
 $f$ -cutset 4: {4, 5, 6, 7}

$$Q = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \end{matrix} & \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 1 & -1 \\ 0 & 1 & 0 & 0 & 0 & -1 & 1 \\ 0 & 0 & 1 & 0 & 1 & -1 & 1 \\ 0 & 0 & 0 & 1 & 1 & -1 & 1 \end{bmatrix} \end{matrix}$$

**Example 5.9** For the graph shown in Fig. 5.39, write the incidence matrix, tieset matrix and  $f$ -cutset matrix.

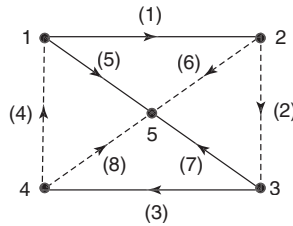


Fig. 5.39

### Solution

(a) Incidence Matrix ( $A$ )

$$A_a = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \\ 5 \end{matrix} & \begin{bmatrix} 1 & 0 & 0 & -1 & 1 & 0 & 0 & 0 \\ -1 & 1 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & -1 & -1 & -1 & -1 \end{bmatrix} \end{matrix}$$

The incidence matrix is obtained by eliminating any one row.

$$A = \begin{bmatrix} 1 & 0 & 0 & -1 & 1 & 0 & 0 & 0 \\ -1 & 1 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

(b) Tieset Matrix ( $B$ )

Links: {2, 4, 6, 8}

Tieset 2: {2, 7, 5, 1}

Tieset 4: {4, 5, 7, 3}

Tieset 6: {6, 5, 1}

Tieset 8: {8, 7, 3}

$$B = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \end{matrix} \\ \begin{matrix} 2 \\ 4 \\ 6 \\ 8 \end{matrix} & \begin{bmatrix} 1 & 1 & 0 & 0 & -1 & 0 & 1 & 0 \\ 0 & 0 & 1 & 1 & 1 & 0 & -1 & 0 \\ 1 & 0 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & -1 & 1 \end{bmatrix} \end{matrix}$$

(c)  $f$ -cutset Matrix ( $Q$ )

The oriented graph, selected tree and  $f$ -cutsets are shown in Fig. 5.40.

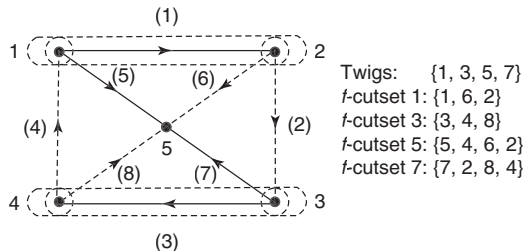


Fig. 5.40

$$Q = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \end{matrix} \\ \begin{matrix} 1 \\ 3 \\ 5 \\ 7 \end{matrix} & \begin{bmatrix} 1 & -1 & 0 & 0 & 0 & -1 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 & 0 & -1 \\ 0 & 1 & 0 & -1 & 1 & 1 & 0 & 0 \\ 0 & -1 & 0 & 1 & 0 & 0 & 1 & 1 \end{bmatrix} \end{matrix}$$

**Example 5.10**

How many trees are possible for the graph of the network of Fig. 5.41.

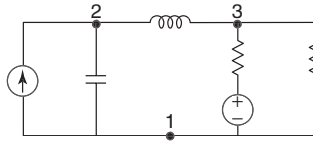


Fig. 5.41

**Solution** To draw the graph,

1. replace all resistors, inductors and capacitors by line segments,
2. replace voltage source by short circuit and current source by an open circuit,
3. assume directions of branch currents arbitrarily, and
4. number all the nodes and branches.

The oriented graph is shown in Fig. 5.42.

 The complete Incidence Matrix ( $A_a$ ) is written as

$$A_a = \begin{bmatrix} 1 & 2 & 3 & 4 \\ \begin{matrix} 1 \\ 2 \\ 3 \end{matrix} \begin{bmatrix} 1 & 0 & -1 & 1 \\ -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & -1 \end{bmatrix} \end{bmatrix}$$

 The reduced incidence matrix  $A$  is obtained by eliminating the last row from matrix  $A_a$ .

$$A = \begin{bmatrix} 1 & 0 & -1 & 1 \\ -1 & 1 & 0 & 0 \end{bmatrix}$$

$$AA^T = \begin{bmatrix} 1 & 0 & -1 & 1 \\ -1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} 1 & -1 \\ 0 & 1 \\ -1 & 0 \\ 1 & 0 \end{bmatrix} = \begin{bmatrix} 3 & -1 \\ -1 & 2 \end{bmatrix}$$

 The number of possible trees =  $|AA^T| = \begin{vmatrix} 3 & -1 \\ -1 & 2 \end{vmatrix} = 6 - 1 = 5$ .

**Example 5.11**

Draw the oriented graph from the complete incidence matrix given below;

Nodes ↓	Branches →							
	1	2	3	4	5	6	7	8
1	1	0	0	0	1	0	0	1
2	0	1	0	0	-1	1	0	0
3	0	0	1	0	0	-1	1	-1
4	0	0	0	1	0	0	-1	0
5	-1	-1	-1	-1	0	0	0	0

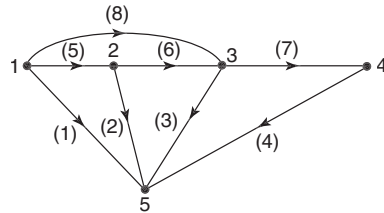


Fig. 5.43

**Solution** First, note down the nodes 1, 2, 3, 4, 5 as shown in Fig. 5.43. From the complete incidence matrix, it is clear that the branch number 1 is between nodes 1 and 5 and it is going away from node 1 and towards node 5 as the entry against node 1 is 1 and that against 5 is -1. Hence, connect the nodes 1 and 5 by a line, point the arrow towards 5 and call it branch 1 as shown in Fig. 5.43. Similarly, draw the other oriented branches.

## 5.22 Circuit Theory and Networks—Analysis and Synthesis

**Example 5.12** The reduced incidence matrix of an oriented graph is given below. Draw the graph.

$$A = \begin{bmatrix} 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

**Solution** First, writing the complete incidence matrix from the matrix  $A$  such that the sum of all entries in each column of  $A_a$  will be zero, we have

$$A_a = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \end{matrix} & \begin{bmatrix} 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \\ 1 & 1 & 0 & 0 & 0 \end{bmatrix} \end{matrix}$$

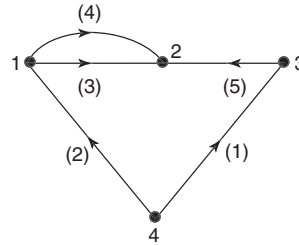


Fig. 5.44

Now, the oriented graph can be drawn with matrix  $A_a$  as shown in Fig. 5.44.

**Example 5.13** The reduced incidence matrix of an oriented graph is

$$A = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

(a) Draw the graph. (b) How many trees are possible for this graph? (c) Write the tieset and cutset matrices.

**Solution**

(a) First, writing the complete incidence matrix  $A_a$  such that the sum of all the entries in each column of  $A_a$  is zero, we have

$$A_a = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \end{matrix} & \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \\ 1 & 1 & 0 & 1 & 0 \end{bmatrix} \end{matrix}$$

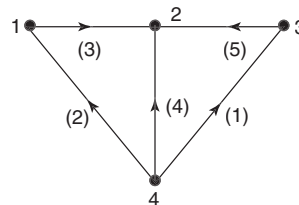


Fig. 5.45

Now, the oriented graph can be drawn with the matrix  $A_a$ , as shown in Fig. 5.45.

(b) The number of possible trees =  $|AA^T|$

$$AA^T = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0 & 0 & -1 \\ -1 & 0 & 0 \\ 1 & -1 & 0 \\ 0 & -1 & 0 \\ 0 & -1 & 1 \end{bmatrix} = \begin{bmatrix} 2 & -1 & 0 \\ -1 & 3 & -1 \\ 0 & -1 & 2 \end{bmatrix}$$

$$|AA^T| = \begin{vmatrix} 2 & -1 & 0 \\ -1 & 3 & -1 \\ 0 & -1 & 2 \end{vmatrix} = 2(6-1) + 1(-2) = 8$$

The number of possible trees = 8.

(c) Tieset Matrix ( $B$ )

The oriented graph, selected tree and tiesets are shown in Fig. 5.46.

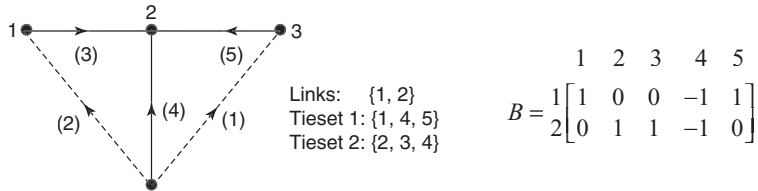


Fig. 5.46

$f$ -cutset Matrix ( $Q$ )

The oriented graph, selected tree and  $f$ -cutsets are shown in Fig. 5.47

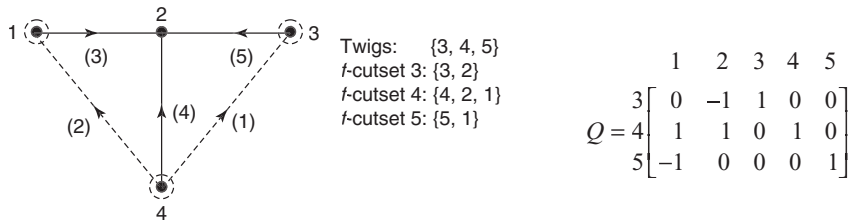


Fig. 5.47

### Example 5.14

The fundamental cutset matrix of a network is given as follows;

Twigs			Links		
$a$	$c$	$e$	$b$	$d$	$f$
1	0	0	1	0	1
0	1	0	0	1	1
0	0	1	1	1	1

Draw the oriented graph.

**Solution**

No. of links  $l = b - n + 1$

No. of nodes  $n = b - l + 1 = 6 - 3 + 1 = 4$

$f$ -cutsets are written as,

$f$ -cutsets  $a$ : { $a$ ,  $b$ ,  $f$ }

$f$ -cutsets  $c$ : { $c$ ,  $d$ ,  $f$ }

$f$ -cutsets  $e$ : { $e$ ,  $b$ ,  $d$ ,  $f$ }

The oriented graph is drawn as shown in Fig. 5.48.

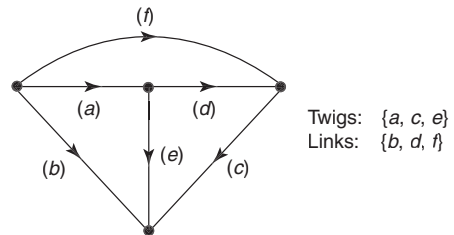


Fig. 5.48

**Example 5.15**

Draw the oriented graph of a network with the  $f$ -cutset matrix as shown below:

Twigs				Links		
1	2	3	4	5	6	7
1	0	0	0	-1	0	0
0	1	0	0	1	0	1
0	0	1	0	0	1	1
0	0	0	1	0	1	0

**Solution** No. of links  $l = b - n + 1$

No. of nodes  $n = b - l + 1 = 7 - 3 + 1 = 5$

$f$ -cutsets are written as


$f$ -cutset 1: {1, 5}

$f$ -cutset 2: {2, 5, 7}

$f$ -cutset 3: {3, 6, 7}

$f$ -cutset 4: {4, 6}

Then oriented graph can be drawn as shown in Fig. 5.49.

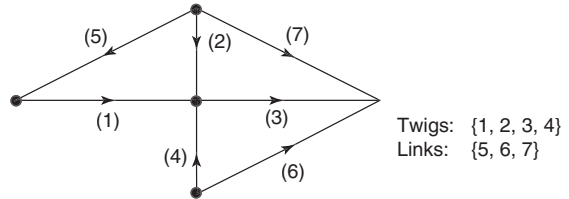

**Fig. 5.49**

**5.8****KIRCHHOFF'S VOLTAGE LAW**

KVL states that if  $v_k$  is the voltage drop across the  $k^{\text{th}}$  branch, then

$$\sum v_k = 0$$

the sum being taken over all the branches in a given loop. If  $l$  is the number of loops or  $f$ -circuits, then there will be  $l$  number of KVL equations, one for each loop. The KVL equation for the  $f$ -circuit or loop ' $l$ ' can be written as

$$\sum_{k=1}^b b_{ik} v_k = 0 \quad (k = 1, 2, \dots, l)$$

where  $b_{ik}$  is the elements of the tieset matrix  $B$ ,  $b$  being the number of branches. The set of  $l$  KVL equations can be written in matrix form.

$$BV_b = 0$$

where

$$V_b = \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_b \end{bmatrix} \text{ is a column vector of branch voltages.}$$

and  $B$  is the fundamental circuit matrix.

**5.9****KIRCHHOFF'S CURRENT LAW**

KCL states that if  $i_k$  is the current in the  $k^{\text{th}}$  branch then at a given node

$$\sum i_k = 0$$

the sum being taken over all the branches incident at a given node. If there are ' $n$ ' nodes, there will ' $n$ ' such equations, one for each node



$$\sum_{k=1}^b a_{ik} i_k = 0 \quad (k = 1, 2, \dots, n)$$

so that set of  $n$  equations can be written in matrix form.

$$A_a I_b = 0 \quad \dots(5.4)$$

where

$$I_b = \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_b \end{bmatrix} \text{ is a column vector of branch currents.}$$

and  $A_a$  is the complete incidence matrix.

If one node is taken as reference node or datum node, we can write the Eq. (5.4) as,

$$A I_b = 0 \quad \dots(5.5)$$

where  $A$  is the incidence matrix of order  $(n-1) \times b$ .

We know that

$$A = A_t Q$$

Equation (5.5) can be written as

$$A_t Q I_b = 0$$

Premultiplying with  $A_t^{-1}$ ,

$$A_t^{-1} A_t Q I_b = A_t^{-1} \cdot 0$$

$$I Q I_b = 0$$

$$Q I_b = 0$$

where  $Q$  is the  $f$ -cutset matrix.

## 5.10

### RELATION BETWEEN BRANCH VOLTAGE MATRIX $V_b$ , TWIG VOLTAGE MATRIX $V_t$ AND NODE VOLTAGE MATRIX $V_n$

We know that

$$B V_b = 0$$

$$[B_t : B_l] \begin{bmatrix} V_t \\ \dots \\ V_l \end{bmatrix} = 0$$

$$B_t V_t + B_l V_l = 0$$

$$B_l V_l = -B_t V_t$$

Premultiplying with  $B_l^{-1}$ .

$$V_l = -B_l^{-1} B_t V_t = -(B_l^{-1} B_t) V_t$$

Now

$$V_b = \begin{bmatrix} V_t \\ \dots \\ V_l \end{bmatrix}$$

$$= \begin{bmatrix} V_t \\ \dots \\ -(B_l^{-1} B_t) V_t \end{bmatrix} = \begin{bmatrix} U \\ \dots \\ -(B_l^{-1} B_t) \end{bmatrix} \cdot V_t \quad \dots(5.6)$$

## 5.26 Circuit Theory and Networks—Analysis and Synthesis

Also,

$$V_b = Q^T V_t$$

$$Q = A_t^{-1} A$$

$$Q^T = A^T (A_t^{-1})^T = A^T (A_t^T)^{-1}$$

Hence Eq. (5.6) can be written as

$$V_b = A^T (A_t^T)^{-1} V_t = A^T \{ (A_t^T)^{-1} V_t \} = A^T V_n$$

where

$$V_n = (A_t^T)^{-1} V_t \text{ is node voltage matrix.}$$

### 5.11

## RELATION BETWEEN BRANCH CURRENT MATRIX $I_b$ AND LOOP CURRENT MATRIX $I_l$

We know that,  $A I_b = 0$

$$[A_t : A_l] \begin{bmatrix} I_t \\ \dots \\ I_l \end{bmatrix} = 0$$

$$A_t I_t + A_l I_l = 0$$

$$A_t I_t = -A_l I_l$$

Premultiplying with  $A_t^{-1}$ ,

$$I_t = -A_t^{-1} A_l I_l = -(A_t^{-1} A_l) I_l$$

$$I_b = \begin{bmatrix} I_t \\ \dots \\ I_l \end{bmatrix} = \begin{bmatrix} -(A_t^{-1} A_l) I_l \\ \dots \\ I_l \end{bmatrix} = \begin{bmatrix} -(A_t^{-1} A_l) \\ \dots \\ U \end{bmatrix} \cdot I_l$$

Now

$$I_b = B^T I_l$$

### 5.12

## NETWORK EQUILIBRIUM EQUATION

### 5.12.1 KVL Equation

1. If there is a voltage source  $v_{sk}$  in the branch  $k$  having impedance  $z_k$  and carrying current  $i_k$ , as shown in Fig. 5.50,

$$v_k = z_k i_k - v_{sk} \quad (k = 1, 2, \dots, b)$$

In matrix form,

$$V_b = Z_b I_b - V_s$$

where  $Z_b$  is the branch impedance matrix,  $I_b$  is the column vector of branch currents and  $V_s$  is the column vector of source voltages. Hence, KVL equation can be written as

$$B V_b = 0$$

$$B (Z_b I_b - V_s) = 0$$

$$B Z_b I_b = B V_s$$

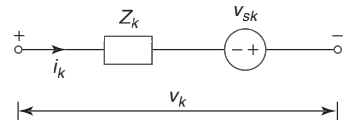


Fig. 5.50 Circuit diagram

Also,

$$\begin{aligned} I_b &= B^T I_l \\ B Z_b B^T I_l &= B V_s \\ Z I_l &= E \end{aligned}$$

where

$$E = B V_s$$

and

$$Z = B Z_b B^T$$

The matrix  $Z$  is called *loop impedance matrix*.

2. If there is a voltage source in series with an impedance and a current source in parallel with the combination as shown in Fig. 5.51,

$$i_k = \frac{(v_k + v_{sk})}{z_k} - i_{sk}$$

$$v_k = z_k i_k + z_k i_{sk} - v_{sk}$$

In matrix form,

$$V_b = Z_b I_b + Z_b I_s - V_s$$

KVL equation is  $B V_b = 0$ .

$$B V_b = B(Z_b I_b + Z_b I_s - V_s) = 0$$

$$B Z_b I_b = B V_s - B Z_b I_s$$

Now

$$I_b = B^T I_l$$

$$B Z_b B^T I_l = B V_s - B Z_b I_s$$

$$Z I_l = B V_s - B Z_b I_s$$

where  $Z = B Z_b B^T$  is the loop impedance matrix. This is the generalised KVL equation.

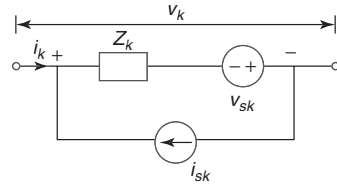


Fig. 5.51 Circuit diagram

### 5.12.2 KCL Equation

1. If the branch  $k$  contains an input current source  $i_{sk}$  and an admittance  $y_k$  as shown in Fig. 5.52,

$$i_k = y_k v_k - i_{sk} \quad (k = 1, 2, \dots, b)$$

In the matrix form,

$$I_b = Y_b V_b - I_s$$

where  $Y_b$  is the branch admittance matrix.

Hence KCL equation is given by,

$$A I_b = 0$$

$$A(Y_b V_b - I_s) = 0$$

$$A Y_b V_b = A I_s$$

Also

$$V_b = A^T V_n$$

$$A Y_b A^T V_n = A I_s$$

$$Y V_n = I$$

where

$$Y = A Y_b A^T$$

and

$$I = A I_s$$

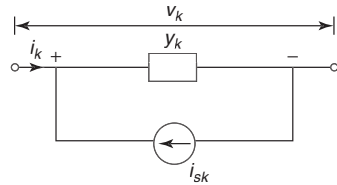


Fig. 5.52 Circuit diagram

## 5.28 Circuit Theory and Networks—Analysis and Synthesis

The matrix  $Y$  is called admittance matrix. This is the KCL equation in matrix form. In terms of  $f$ -cutset matrix, the KCL equation can be written as

$$\begin{aligned} Q I_b &= 0 \\ Q(Y_b V_b - V_s) &= 0 \\ Q Y_b V_b &= Q I_s \end{aligned}$$

Also

$$\begin{aligned} V_b &= Q^T V_t \\ Q Y_b Q^T V_t &= Q I_s \\ Y V_t &= I \end{aligned}$$

where

$$Y = Q Y_b Q^T$$

and

$$I = Q I_s$$

This is the KCL equation in matrix form.

- If there is a voltage source in series with an impedance and a current source in parallel with the combination as shown in Fig. 5.53,

$$\begin{aligned} y_k &= \frac{1}{z_k} \\ i_k &= y_k v_k + y_k v_{sk} - i_{sk} \end{aligned}$$

In matrix form,

$$I_b = Y_b V_b + Y_b V_s - I_s$$

KCL equation will be given by,

$$\begin{aligned} A I_b &= 0 \\ A(Y_b V_b + Y_b V_s - I_s) &= 0 \\ A Y_b V_b &= A I_s - A Y_b V_s \end{aligned}$$

Also

$$\begin{aligned} V_b &= A^T V_n \\ A Y_b A^T V_n &= A I_s - A Y_b V_s \\ Y V_n &= A I_s - A Y_b V_s \end{aligned}$$

where  $Y = A Y_b A^T$  is the node admittance matrix. This is a generalised KCL equation.


In terms of  $f$ -cutset matrix, the KCL equation can be written as

$$\begin{aligned} Q I_b &= 0 \\ Q(Y_b V_b + Y_b V_s - I_s) &= 0 \\ Q Y_b V_b &= Q I_s - Q Y_b V_s \end{aligned}$$

Also

$$\begin{aligned} V_b &= Q^T V_t \\ Q Y_b Q^T V_t &= Q I_s - Q Y_b V_s \\ Y V_t &= Q I_s - Q Y_b V_s \end{aligned}$$

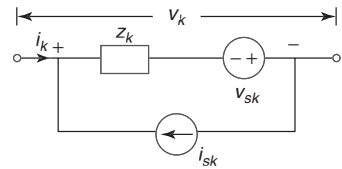This is a generalised KCL equation.

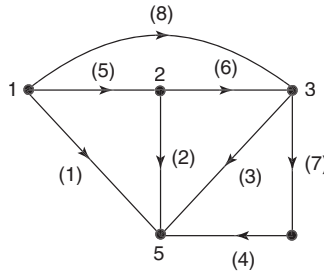


**Fig. 5.53** Circuit diagram

**Note**

- (i) For a graph having  $b$  branches, the branch impedance matrix  $Z_b$  is a square matrix of order  $b$ , having branch impedances as diagonal elements and the mutual impedances between the branches as non-diagonal elements. For a network having no mutual impedances, only diagonal elements will be present in the branch impedance matrix.
- (ii) For a graph having  $b$  branches, the branch admittance matrix  $Y_b$  is a square matrix of order  $b$ , having branch admittances as diagonal elements and the mutual admittances between the branches as non-diagonal elements. For a network having no mutual admittances, only diagonal elements will be present in the branch admittance matrix.
- (iii) For a graph having  $b$  branches, the voltage source matrix or vector  $V_s$  is a rectangular matrix of order  $b \times 1$ , having the value of the voltage source in the particular branch. The value will be positive if there is a voltage rise in the direction of current and will be negative if there is a voltage fall in the direction of current.
- (iv) For a graph having  $b$  branches, the current source matrix or vector  $I_s$  is a rectangular matrix of order  $b \times 1$ , having the value of the current source in the particular parallel branch. The value will be positive if the direction of the current source and the corresponding parallel branch current are not same. The value will be negative if the directions of the current source and corresponding parallel branch current are same.

**Example 5.16** Write the incidence matrix of the graph of Fig. 5.54 and express branch voltages in terms of node voltages. Write the tieset matrix and express branch currents in terms of loop currents.

**Fig. 5.54****Solution**

(a) Incidence Matrix

$$A_a = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \\ 5 \end{matrix} & \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & -1 & 1 & -1 \\ 0 & 0 & 0 & 1 & 0 & 0 & -1 & 0 \\ -1 & -1 & -1 & -1 & 0 & 0 & 0 & 0 \end{bmatrix} \end{matrix}$$

The incidence matrix is obtained by eliminating any one row.

$$A = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & -1 & 1 & -1 \\ 0 & 0 & 0 & 1 & 0 & 0 & -1 & 0 \end{bmatrix}$$

### 5.30 Circuit Theory and Networks—Analysis and Synthesis


(b) Branch voltages in terms of node voltages

$$V_b = A^T V_n$$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \\ V_7 \\ V_8 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & -1 & 0 & 0 \\ 0 & 1 & -1 & 0 \\ 0 & 0 & 1 & -1 \\ 1 & 0 & -1 & 0 \end{bmatrix} \begin{bmatrix} V_{n_1} \\ V_{n_2} \\ V_{n_3} \\ V_{n_4} \end{bmatrix}$$

(c) Tieset Matrix

Selected tree and tiesets are shown in Fig. 5.55.

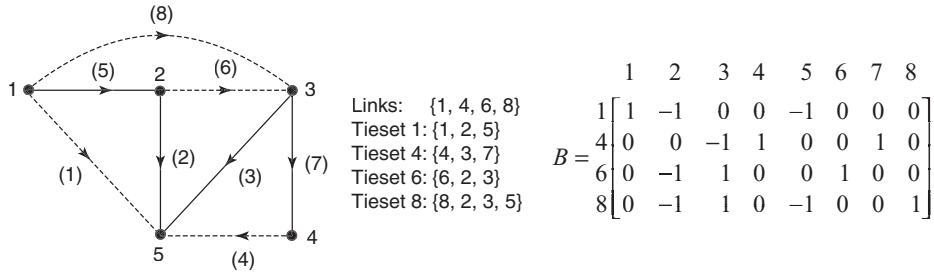

**Fig. 5.55**

(d) Branch currents in terms of loop currents

$$I_b = B^T I_l$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \\ I_6 \\ I_7 \\ I_8 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 \\ -1 & 0 & -1 & -1 \\ 0 & -1 & 1 & 1 \\ 0 & 1 & 0 & 0 \\ -1 & 0 & 0 & -1 \\ 0 & 0 & 1 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} I_{l_1} \\ I_{l_2} \\ I_{l_3} \\ I_{l_4} \end{bmatrix}$$

#### Example 5.17

Branch current and loop-current relationships are expressed in matrix form as

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \\ I_6 \\ I_7 \\ I_8 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & -1 \\ 0 & 1 & 0 & -1 \\ 0 & 1 & 1 & 0 \\ 0 & 1 & 1 & 0 \\ 1 & -1 & 0 & 0 \\ 0 & 0 & -1 & 0 \\ -1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} I_{l_1} \\ I_{l_2} \\ I_{l_3} \\ I_{l_4} \end{bmatrix}$$

Draw the oriented graph.

**Solution** Writing the equation in matrix form,

$$I_b = B^T I_l$$

$$B^T = \begin{bmatrix} 1 & 0 & 0 & -1 \\ 0 & 1 & 0 & -1 \\ 0 & 1 & 1 & 0 \\ 0 & 1 & 1 & 0 \\ 1 & -1 & 0 & 0 \\ 0 & 0 & -1 & 0 \\ -1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} \quad \therefore B = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \end{matrix} \\ \begin{matrix} 1 \\ 0 \\ 0 \\ 0 \\ 1 \\ -1 \\ -1 \end{matrix} & \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & 0 & -1 & 0 \\ 0 & 1 & 1 & 1 & -1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 & 0 & -1 & 0 & 0 \\ -1 & -1 & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \end{matrix}$$


From tieset matrix,

No. of links  $l = 4$

No of branches  $b = 8$


No of nodes  $n = b - l + 1 = 8 - 4 + 1 = 1$

The oriented graph is shown in Fig. 5.56.

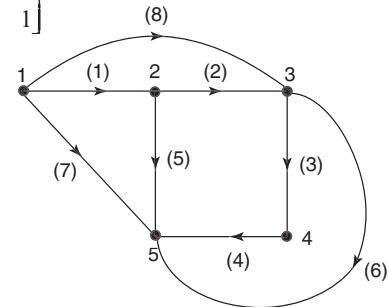


**Fig. 5.56**

**Example 5.18** For the given graph shown in Fig. 5.57, write down the basic tieset matrix and taking a tree of branches 2, 4, 5, write down KVL equations from the matrix.

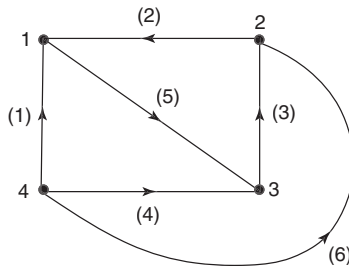

**Fig. 5.57**

**Solution** Selecting branches 2, 4, and 5 as the tree as shown in Fig. 5.58,

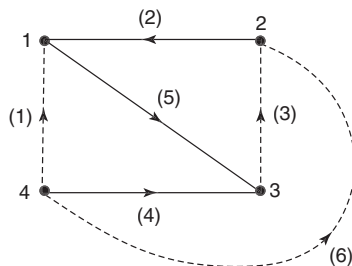

**Fig. 5.58**

Links:  $\{1, 3, 6\}$   
 Tieset 1:  $\{1, 5, 4\}$   
 Tieset 3:  $\{3, 2, 5\}$   
 Tieset 6:  $\{6, 2, 5, 4\}$

$$B = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 \end{matrix} \\ \begin{matrix} 1 \\ 3 \\ 6 \end{matrix} & \begin{bmatrix} 1 & 0 & 0 & -1 & 1 & 0 \\ 0 & 1 & 1 & 0 & 1 & 0 \\ 0 & 1 & 0 & -1 & 1 & 1 \end{bmatrix} \end{matrix}$$

### 5.32 Circuit Theory and Networks—Analysis and Synthesis

The KVL equation in matrix form is given by

$$BV_b = 0$$

$$\begin{bmatrix} 1 & 0 & 0 & -1 & 1 & 0 \\ 0 & 1 & 1 & 0 & 1 & 0 \\ 0 & 1 & 0 & -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \end{bmatrix} = 0$$

$$V_1 - V_4 + V_5 = 0$$

$$V_2 + V_3 + V_5 = 0$$

$$V_2 - V_4 + V_5 + V_6 = 0$$

**Example 5.19** Obtain the  $f$ -cutset matrix for the graph shown in Fig. 5.59 taking 1, 2, 3, 4 as tree branches. Write down the network equations from the  $f$ -cutset matrix.

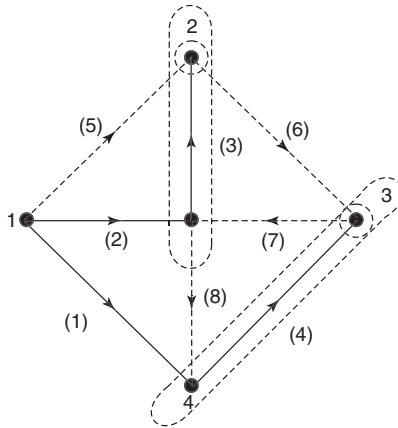


Fig. 5.59

**Solution** Twigs: {1, 2, 3, 4}  
 $f$ -cutset 1 : {1, 6, 7, 8}  
 $f$ -cutset 2 : {2, 5, 6, 7, 8}  
 $f$ -cutset 3 : {3, 5, 6}  
 $f$ -cutset 4 : {4, 6, 7}

$$Q = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \end{matrix} & \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 1 & -1 & 1 \\ 0 & 1 & 0 & 0 & 1 & -1 & 1 & -1 \\ 0 & 0 & 1 & 0 & 1 & -1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 1 & -1 & 0 \end{bmatrix} \end{matrix}$$

The KCL equation in matrix form is given by

$$QI_b = 0$$

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 1 & -1 & 1 \\ 0 & 1 & 0 & 0 & 1 & -1 & 1 & -1 \\ 0 & 0 & 1 & 0 & 1 & -1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \\ I_6 \\ I_7 \\ I_8 \end{bmatrix} = 0$$



$$\begin{aligned}
 I_1 + I_6 - I_7 + I_8 &= 0 \\
 I_2 + I_5 - I_6 + I_7 - I_8 &= 0 \\
 I_3 + I_5 - I_6 &= 0 \\
 I_4 + I_6 - I_7 &= 0
 \end{aligned}$$

**Example 5.20** The reduced incidence matrix of a graph is given as

$$A = \begin{bmatrix} 1 & 0 & 0 & 0 & -1 \\ -1 & -1 & -1 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 \end{bmatrix}$$

Express branch voltages in terms of node voltages.

**Solution** For the given graph,  
 No of branches  $b = 5$   
 No of nodes  $n = 3$

Branch voltages can be expressed in terms of node voltages by

$$\begin{aligned}
 V_b &= A^T V_n \\
 \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix} &= \begin{bmatrix} 1 & -1 & 0 \\ 0 & -1 & 0 \\ 0 & -1 & 1 \\ 0 & 0 & -1 \\ -1 & 0 & 0 \end{bmatrix} \begin{bmatrix} V_{n_1} \\ V_{n_2} \\ V_{n_3} \end{bmatrix} \\
 V_1 &= V_{n_1} - V_{n_2} \\
 V_2 &= -V_{n_2} \\
 V_3 &= -V_{n_2} + V_{n_3} \\
 V_4 &= -V_{n_3} \\
 V_5 &= -V_{n_1}
 \end{aligned}$$

**Example 5.21** The fundamental cutset matrix of a graph is given as

$$Q = \begin{bmatrix} -1 & 1 & 0 & 0 & -1 \\ 0 & 0 & 1 & 0 & -1 \\ 1 & 0 & 0 & 1 & 0 \end{bmatrix}$$

Express branch voltages in terms of twig voltages.

**Solution** For the given graph,  
 No. of branches  $b = 5$   
 No. of twigs = 3

Branch voltages are expressed in terms of twig voltages by

$$\begin{aligned}
 V_b &= Q^T V_t \\
 \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix} &= \begin{bmatrix} -1 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & -1 & 0 \end{bmatrix} \begin{bmatrix} V_{t_1} \\ V_{t_2} \\ V_{t_3} \end{bmatrix}
 \end{aligned}$$

### 5.34 Circuit Theory and Networks—Analysis and Synthesis

$$V_1 = -V_{t_1} + V_{t_3}$$

$$V_2 = V_{t_1}$$

$$V_3 = V_{t_2}$$

$$V_4 = V_{t_3}$$

$$V_5 = -V_{t_1} - V_{t_2}$$

**Example 5.22** For this network shown in Fig. 5.60, write down the tieset matrix and obtain the network equilibrium equation in matrix form using KVL. Calculate the loop currents and branch currents.

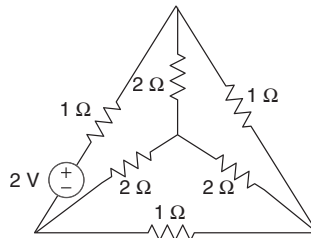


Fig. 5.60

**Solution** The oriented graph and one of its trees are shown in Fig. 5.61.

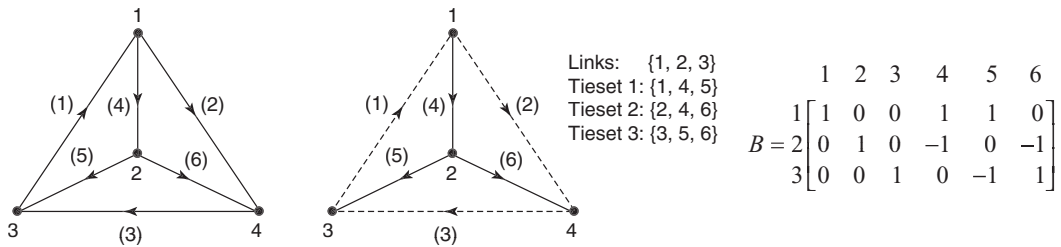


Fig. 5.61

The KVL equation in matrix form is given by

$$B Z_b B^T I_l = B V_s - B Z_b I_s$$

Here,

$$I_s = 0,$$

$$B Z_b B^T I_l = B V_s$$

$$Z_b = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 2 & 0 & 0 \\ 0 & 0 & 0 & 0 & 2 & 0 \\ 0 & 0 & 0 & 0 & 0 & 2 \end{bmatrix}; B^T = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & -1 & 1 \end{bmatrix}; V_s = \begin{bmatrix} 2 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{aligned}
 BZ_b &= \begin{bmatrix} 1 & 0 & 0 & 1 & 1 & 0 \\ 0 & 1 & 0 & -1 & 0 & -1 \\ 0 & 0 & 1 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 2 & 0 & 0 \\ 0 & 0 & 0 & 0 & 2 & 0 \\ 0 & 0 & 0 & 0 & 0 & 2 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 2 & 2 & 0 \\ 0 & 1 & 0 & -2 & 0 & -2 \\ 0 & 0 & 1 & 0 & -2 & 2 \end{bmatrix} \\
 BZ_b B^T &= \begin{bmatrix} 1 & 0 & 0 & 2 & 2 & 0 \\ 0 & 1 & 0 & -2 & 0 & -2 \\ 0 & 0 & 1 & 0 & -2 & 2 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & -1 & 1 \end{bmatrix} = \begin{bmatrix} 5 & -2 & -2 \\ -2 & 5 & -2 \\ -2 & -2 & 5 \end{bmatrix} \\
 BV_s &= \begin{bmatrix} 1 & 0 & 0 & 1 & 1 & 0 \\ 0 & 1 & 0 & -1 & 0 & -1 \\ 0 & 0 & 1 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} 2 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \\ 0 \end{bmatrix}
 \end{aligned}$$

The KVL equation in matrix form is given by

$$\begin{bmatrix} 5 & -2 & -2 \\ -2 & 5 & -2 \\ -2 & -2 & 5 \end{bmatrix} \begin{bmatrix} I_{l_1} \\ I_{l_2} \\ I_{l_3} \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \\ 0 \end{bmatrix}$$

Solving this matrix equation,

$$I_{l_1} = \frac{6}{7} \text{ A}$$

$$I_{l_2} = \frac{4}{7} \text{ A}$$

$$I_{l_3} = \frac{4}{7} \text{ A}$$

The branch currents are given by

$$I_b = B^T I_l$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \\ I_6 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} \frac{6}{7} \\ \frac{4}{7} \\ \frac{4}{7} \end{bmatrix} = \begin{bmatrix} \frac{6}{7} \\ \frac{4}{7} \\ \frac{4}{7} \\ \frac{2}{7} \\ \frac{2}{7} \\ \frac{2}{7} \end{bmatrix}$$

**Example 5.23** For the network shown in Fig. 5.62, write down the tieset matrix and obtain the network equilibrium equation in matrix form using KVL. Calculate loop currents.

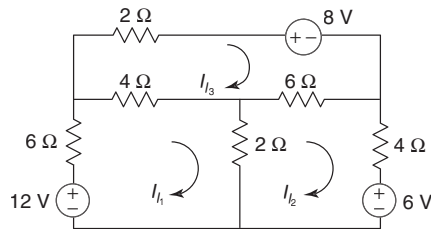


Fig. 5.62

**Solution** The oriented graph and its selected tree are shown in Fig. 5.63.

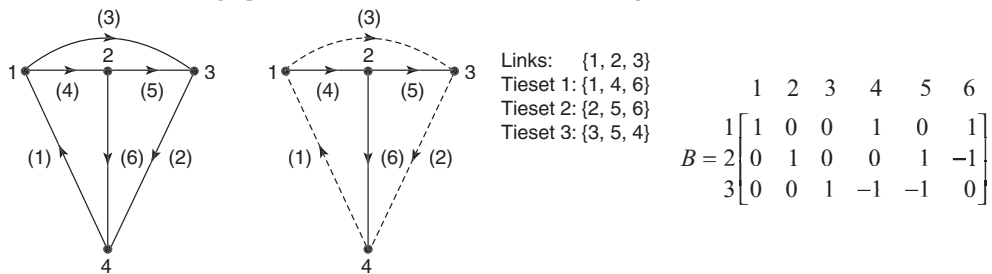


Fig. 5.63

The KVL equation in matrix form is given by

$$B Z_b B^T I_l = B V_s - B Z_b I_s$$

Here,

$$I_s = 0,$$

$$B Z_b B^T I_l = B V_s$$

$$Z_b = \begin{bmatrix} 6 & 0 & 0 & 0 & 0 & 0 \\ 0 & 4 & 0 & 0 & 0 & 0 \\ 0 & 0 & 2 & 0 & 0 & 0 \\ 0 & 0 & 0 & 4 & 0 & 0 \\ 0 & 0 & 0 & 0 & 6 & 0 \\ 0 & 0 & 0 & 0 & 0 & 2 \end{bmatrix}; B^T = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & -1 \\ 0 & 1 & -1 \\ 1 & -1 & 0 \end{bmatrix}; V_s = \begin{bmatrix} 12 \\ -6 \\ -8 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$B Z_b = \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 & -1 \\ 0 & 0 & 1 & -1 & -1 & 0 \end{bmatrix} \begin{bmatrix} 6 & 0 & 0 & 0 & 0 & 0 \\ 0 & 4 & 0 & 0 & 0 & 0 \\ 0 & 0 & 2 & 0 & 0 & 0 \\ 0 & 0 & 0 & 4 & 0 & 0 \\ 0 & 0 & 0 & 0 & 6 & 0 \\ 0 & 0 & 0 & 0 & 0 & 2 \end{bmatrix} = \begin{bmatrix} 6 & 0 & 0 & 4 & 0 & 2 \\ 0 & 4 & 0 & 0 & 6 & -2 \\ 0 & 0 & 2 & -4 & -6 & 0 \end{bmatrix}$$

$$B Z_b B^T = \begin{bmatrix} 6 & 0 & 0 & 4 & 0 & 2 \\ 0 & 4 & 0 & 0 & 6 & -2 \\ 0 & 0 & 2 & -4 & -6 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & -1 \\ 0 & 1 & -1 \\ 1 & -1 & 0 \end{bmatrix} = \begin{bmatrix} 12 & -2 & -4 \\ -1 & 12 & -6 \\ -4 & -6 & 12 \end{bmatrix}$$

$$BV_s = \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 & -1 \\ 0 & 0 & 1 & -1 & -1 & 0 \end{bmatrix} \begin{bmatrix} 12 \\ -6 \\ -8 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 12 \\ -6 \\ -8 \end{bmatrix}$$

Hence, the KVL equation in matrix form is given by

$$\begin{bmatrix} 12 & -2 & -4 \\ -2 & 12 & -6 \\ -4 & -6 & 12 \end{bmatrix} \begin{bmatrix} I_{l_1} \\ I_{l_2} \\ I_{l_3} \end{bmatrix} = \begin{bmatrix} 12 \\ -6 \\ -8 \end{bmatrix}$$

Solving this matrix equation,

$$I_{l_1} = 0.55 \text{ A}$$

$$I_{l_2} = -0.866 \text{ A}$$

$$I_{l_3} = -0.916 \text{ A}$$

**Example 5.24** For the network shown in Fig. 5.64, draw the oriented graph. Write the tieset schedule and hence obtain the equilibrium equation on loop basis. Calculate the values of branch currents and branch voltages.

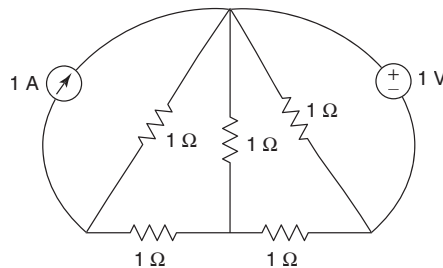


Fig. 5.64

**Solution** The oriented graph and one of its trees are shown in Fig. 5.65.

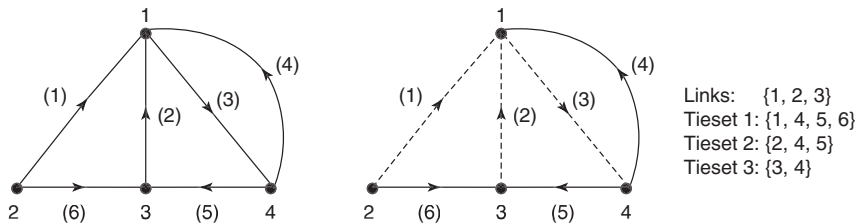


Fig. 5.65

$$B = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 1 & 1 & 0 & 0 & -1 & 1 & -1 \\ 2 & 0 & 1 & 0 & -1 & 1 & 0 \\ 3 & 0 & 0 & 1 & 1 & 0 & 0 \end{bmatrix}$$

### 5.38 Circuit Theory and Networks—Analysis and Synthesis

The KVL equation in matrix form is given by

$$BZ_b B^T I_l = BV_s - BZ_b I_s$$

$$Z_b = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}; B^T = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & -1 & 1 \\ 1 & 1 & 0 \\ -1 & 0 & 0 \end{bmatrix}; V_s = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \\ 0 \\ 0 \end{bmatrix}; I_s = \begin{bmatrix} -1 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$BZ_b = \begin{bmatrix} 1 & 0 & 0 & -1 & 1 & -1 \\ 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & -1 \\ 0 & 1 & 0 & 0 & 1 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \end{bmatrix}$$

$$BZ_b B^T = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & -1 \\ 0 & 1 & 0 & 0 & 1 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & -1 & 1 \\ 1 & 1 & 0 \\ -1 & 0 & 0 \end{bmatrix} = \begin{bmatrix} 3 & 1 & 0 \\ 1 & 2 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$BV_s = \begin{bmatrix} 1 & 0 & 0 & -1 & 1 & -1 \\ 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -1 \\ -1 \\ 1 \end{bmatrix}$$

$$BZ_b I_s = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & -1 \\ 0 & 1 & 0 & 0 & 1 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} -1 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -1 \\ 0 \\ 0 \end{bmatrix}$$

Hence, the KVL equation in matrix form is given by

$$\begin{bmatrix} 3 & 1 & 0 \\ 1 & 2 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} I_{l_1} \\ I_{l_2} \\ I_{l_3} \end{bmatrix} = \begin{bmatrix} -1 \\ -1 \\ 1 \end{bmatrix} - \begin{bmatrix} -1 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ -1 \\ 1 \end{bmatrix}$$

Solving this matrix equation,

$$I_{l_1} = \frac{1}{5} \text{ A}$$

$$I_{l_2} = -\frac{3}{5} \text{ A}$$

$$I_{l_3} = 1 \text{ A}$$

The branch currents are given by

$$I_b = B^T I_l + I_s$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \\ I_6 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & -1 & 1 \\ 1 & 1 & 0 \\ -1 & 0 & 0 \end{bmatrix} \begin{bmatrix} \frac{1}{5} \\ \frac{3}{5} \\ -\frac{1}{5} \end{bmatrix} + \begin{bmatrix} -1 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -\frac{4}{5} \\ -\frac{3}{5} \\ -\frac{1}{5} \\ 1 \\ \frac{7}{5} \\ -\frac{2}{5} \end{bmatrix}$$

The branch voltages are given by

$$V_b = Z_b I_b - V_s$$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} -\frac{4}{5} \\ -\frac{3}{5} \\ -\frac{1}{5} \\ 1 \\ \frac{7}{5} \\ -\frac{2}{5} \end{bmatrix} - \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -\frac{4}{5} \\ -\frac{3}{5} \\ -\frac{1}{5} \\ 1 \\ -\frac{2}{5} \\ -\frac{1}{5} \end{bmatrix}$$

### Example 5.25

For the network shown in Fig. 5.66, obtain the loop equation in matrix form.

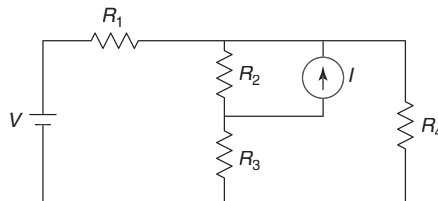


Fig. 5.66

**Solution** The oriented graph and one of its trees are shown in Fig. 5.67.

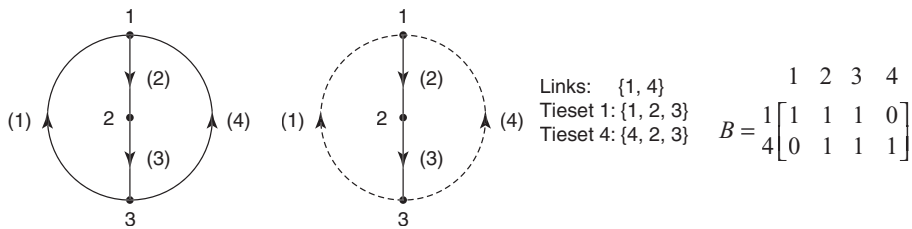


Fig. 5.67

### 5.40 Circuit Theory and Networks—Analysis and Synthesis

The KVL equation in matrix form is given by

$$\begin{aligned}
 B Z_b B^T I_l &= B V_s - B Z_b I_s \\
 Z_b &= \begin{bmatrix} R_1 & 0 & 0 & 0 \\ 0 & R_2 & 0 & 0 \\ 0 & 0 & R_3 & 0 \\ 0 & 0 & 0 & R_4 \end{bmatrix}; B^T = \begin{bmatrix} 1 & 0 \\ 1 & 1 \\ 1 & 1 \\ 0 & 1 \end{bmatrix}; V_s = \begin{bmatrix} V \\ 0 \\ 0 \\ 0 \end{bmatrix}; I_s = \begin{bmatrix} 0 \\ I \\ 0 \\ 0 \end{bmatrix} \\
 B Z_b &= \begin{bmatrix} 1 & 1 & 1 & 0 \\ 0 & 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} R_1 & 0 & 0 & 0 \\ 0 & R_2 & 0 & 0 \\ 0 & 0 & R_3 & 0 \\ 0 & 0 & 0 & R_4 \end{bmatrix} = \begin{bmatrix} R_1 & R_2 & R_3 & 0 \\ 0 & R_2 & R_3 & R_4 \end{bmatrix} \\
 B Z_b B^T &= \begin{bmatrix} R_1 & R_2 & R_3 & 0 \\ 0 & R_2 & R_3 & R_4 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \\ 1 & 1 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} R_1 + R_2 + R_3 & R_2 + R_3 \\ R_2 + R_3 & R_2 + R_3 + R_4 \end{bmatrix} \\
 B V_s &= \begin{bmatrix} 1 & 1 & 1 & 0 \\ 0 & 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} V \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} V \\ 0 \end{bmatrix} \\
 B Z_b I_s &= \begin{bmatrix} R_1 & R_2 & R_3 & 0 \\ 0 & R_2 & R_3 & R_4 \end{bmatrix} \begin{bmatrix} 0 \\ I \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} R_2 I \\ R_2 I \end{bmatrix}
 \end{aligned}$$

Hence, the KVL equation in matrix form is given by

$$\begin{bmatrix} R_1 + R_2 + R_3 & R_2 + R_3 \\ R_2 + R_3 & R_2 + R_3 + R_4 \end{bmatrix} \begin{bmatrix} I_{l_1} \\ I_{l_4} \end{bmatrix} = \begin{bmatrix} V \\ 0 \end{bmatrix} - \begin{bmatrix} R_2 & I \\ R_2 & I \end{bmatrix} = \begin{bmatrix} V - R_2 I \\ -R_2 I \end{bmatrix}$$

**Example 5.26** For the network shown in Fig. 5.68, write down the tieset matrix and obtain the network equilibrium equation in matrix form using KVL.


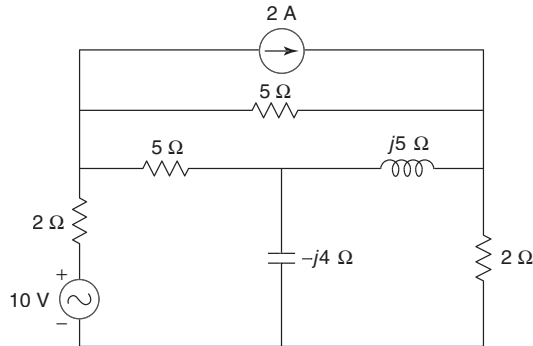


Fig. 5.68

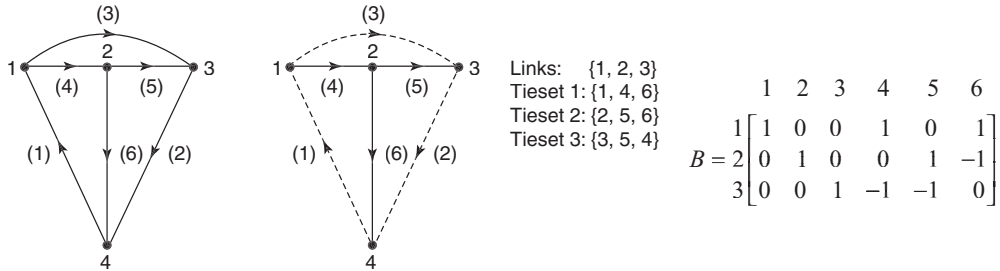

**Solution** The oriented graph and its selected tree are shown in Fig. 5.69.



**Fig. 5.69**

The KVL equation in matrix form is given by

$$B Z_b B^T I_l = B V_s - B Z_b I_s$$

$$Z_b = \begin{bmatrix} 2 & 0 & 0 & 0 & 0 & 0 \\ 0 & 2 & 0 & 0 & 0 & 0 \\ 0 & 0 & 5 & 0 & 0 & 0 \\ 0 & 0 & 0 & 5 & 0 & 0 \\ 0 & 0 & 0 & 0 & j5 & 0 \\ 0 & 0 & 0 & 0 & 0 & -j4 \end{bmatrix}; B^T = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & -1 \\ 0 & 1 & -1 \\ 1 & -1 & 0 \end{bmatrix}; V_s = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}; I_s = \begin{bmatrix} 0 \\ 0 \\ -2 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$B Z_b = \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 & -1 \\ 0 & 0 & 1 & -1 & -1 & 0 \end{bmatrix} \begin{bmatrix} 2 & 0 & 0 & 0 & 0 & 0 \\ 0 & 2 & 0 & 0 & 0 & 0 \\ 0 & 0 & 5 & 0 & 0 & 0 \\ 0 & 0 & 0 & 5 & 0 & 0 \\ 0 & 0 & 0 & 0 & j5 & 0 \\ 0 & 0 & 0 & 0 & 0 & -j4 \end{bmatrix} = \begin{bmatrix} 2 & 0 & 0 & 5 & 0 & -j4 \\ 0 & 2 & 0 & 0 & j5 & j4 \\ 0 & 0 & 5 & -5 & -j5 & 0 \end{bmatrix}$$

$$B Z_b B^T = \begin{bmatrix} 2 & 0 & 0 & 5 & 0 & -j4 \\ 0 & 2 & 0 & 0 & j5 & j4 \\ 0 & 0 & 5 & -5 & -j5 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & -1 \\ 0 & 1 & -1 \\ 1 & -1 & 0 \end{bmatrix} = \begin{bmatrix} 7-j4 & j4 & -5 \\ j4 & 2+j1 & -j5 \\ -5 & -j5 & 10+j5 \end{bmatrix}$$

$$B V_s = \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 & -1 \\ 0 & 0 & 1 & -1 & -1 & 0 \end{bmatrix} \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$

$$B Z_b I_s = \begin{bmatrix} 2 & 0 & 0 & 5 & 0 & -j4 \\ 0 & 2 & 0 & 0 & j5 & j4 \\ 0 & 0 & 5 & -5 & -j5 & 0 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ -2 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ -10 \end{bmatrix}$$

### 5.42 Circuit Theory and Networks—Analysis and Synthesis

Hence, the KCL equation in matrix form is given by

$$\begin{bmatrix} 7-j4 & j4 & -5 \\ j4 & 2+j1 & -j5 \\ -5 & -j5 & 10+j5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix} - \begin{bmatrix} 0 \\ 0 \\ -10 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 10 \end{bmatrix}$$

**Example 5.27** For the network shown in Fig. 5.70, write down the tieset matrix and obtain the network equilibrium equation in matrix form using KVL.

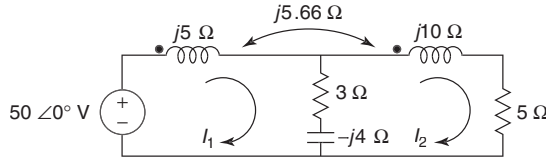


Fig. 5.70

**Solution** The branch currents are so chosen that they assume the direction out of the dotted terminals. Because of this choice of current direction, the mutual inductance is positive. The oriented graph and its selected tree are shown in Fig. 5.71.

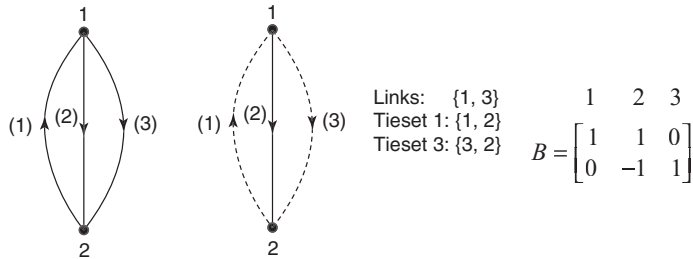


Fig. 5.71

The KVL equation in matrix form is given by

$$B Z_b B^T I_l = B V_s - B Z_b I_s$$

Here,  $I_s = 0$ ,

$$B Z_b B^T I_l = B V_s$$

$$Z_b = \begin{bmatrix} j5 & 0 & j5.66 \\ 0 & 3-j4 & 0 \\ j5.66 & 0 & 5+j10 \end{bmatrix}; B^T = \begin{bmatrix} 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix}; V_s = \begin{bmatrix} 50 \angle 0^\circ \\ 0 \\ 0 \end{bmatrix}$$

$$B Z_b = \begin{bmatrix} 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} j5 & 0 & j5.66 \\ 0 & 3-j4 & 0 \\ j5.66 & 0 & 5+j10 \end{bmatrix} = \begin{bmatrix} j5 & 3-j4 & j5.66 \\ j5.66 & -3+j4 & 5+j10 \end{bmatrix}$$

$$B Z_b B^T = \begin{bmatrix} j5 & 3-j4 & j5.66 \\ j5.66 & -3+j4 & 5+j10 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 3+j1 & -3+j9.66 \\ -3+j9.66 & 8+j6 \end{bmatrix}$$

$$B V_s = \begin{bmatrix} 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} 50 \angle 0^\circ \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 50 \angle 0^\circ \\ 0 \end{bmatrix}$$

Hence, the KVL equation in matrix form is given by

$$\begin{bmatrix} 3 + j1 & -3 + j9.66 \\ -3 + j9.66 & 8. j6 \end{bmatrix} \begin{bmatrix} I_{l_1} \\ I_{l_2} \end{bmatrix} = \begin{bmatrix} 50 \angle 0^\circ \\ 0 \end{bmatrix}$$

**Example 5.28** For the network shown in Fig. 5.72, write down the tieset matrix and obtain the network equilibrium equation in matrix form using KVL.

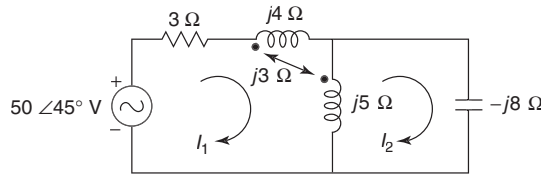


Fig. 5.72

**Solution** The branch currents are so chosen that they assume the direction out of the dotted terminals. Because of this choice of current direction, the mutual inductance is positive. The oriented graph and its selected tree are shown in Fig. 5.73.

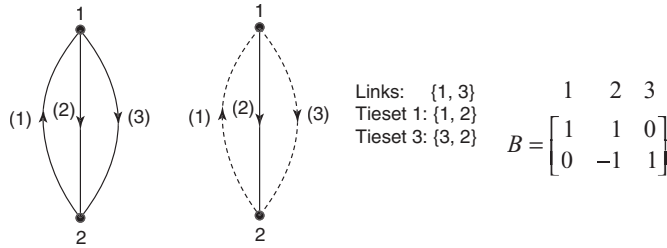


Fig. 5.73

The KVL equation in matrix form is given by

$$B Z_b B^T I_l = B V_s - B Z_b I_s$$

Here,

$$I_s = 0,$$

$$B Z_b B^T I_l = B V_s$$

$$Z_b = \begin{bmatrix} 3 + j4 & j3 & 0 \\ j3 & j5 & 0 \\ 0 & 0 & -j8 \end{bmatrix}; B^T = \begin{bmatrix} 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix}; V_s = \begin{bmatrix} 50 \angle 45^\circ \\ 0 \\ 0 \end{bmatrix}$$

$$B Z_b = \begin{bmatrix} 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} 3 + j4 & j3 & 0 \\ j3 & j5 & 0 \\ 0 & 0 & -j8 \end{bmatrix} = \begin{bmatrix} 3 + j7 & j8 & 0 \\ -j3 & -j5 & -j8 \end{bmatrix}$$

$$B Z_b B^T = \begin{bmatrix} 3 + j7 & j8 & 0 \\ -j3 & -j5 & -j8 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 3 + j15 & -j8 \\ -j8 & -j3 \end{bmatrix}$$

$$B V_s = \begin{bmatrix} 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} 50 \angle 45^\circ \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 50 \angle 45^\circ \\ 0 \end{bmatrix}$$

#### 5.44 Circuit Theory and Networks—Analysis and Synthesis

Hence, the KVL equation in matrix form is given by,

$$\begin{bmatrix} 3 + j15 & -j8 \\ -j8 & -j3 \end{bmatrix} \begin{bmatrix} I_{l_1} \\ I_{l_3} \end{bmatrix} = \begin{bmatrix} 50 \angle 45^\circ \\ 0 \end{bmatrix}$$

**Example 5.29** For the network shown in Fig. 5.74, obtain branch voltages using KCL equation on node basis.

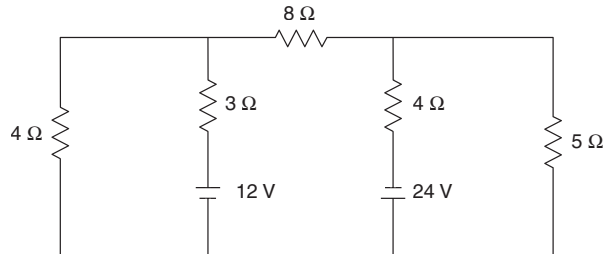


Fig. 5.74

**Solution** The oriented graph is shown in Fig. 5.75.

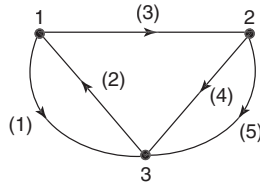


Fig. 5.75

The complete incidence matrix for the graph is

$$A_a = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \end{matrix} & \begin{bmatrix} 1 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 \\ -1 & 1 & 0 & -1 & -1 \end{bmatrix} \end{matrix}$$

Eliminating the last row from the matrix  $A_a$ , we get the incidence matrix  $A$ .

$$A = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 \end{matrix} \\ \begin{matrix} 1 \\ 2 \end{matrix} & \begin{bmatrix} 1 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 \end{bmatrix} \end{matrix}$$

The KCL equation in matrix form is given by

$$AY_b A^T V_n = AI_s - AY_b V_s$$

$$I_s = 0,$$

Here,

$$AY_b A^T V_n = -AY_b V_s$$

$$Y_b = \begin{bmatrix} \frac{1}{4} & 0 & 0 & 0 & 0 \\ 0 & \frac{1}{3} & 0 & 0 & 0 \\ 0 & 0 & \frac{1}{8} & 0 & 0 \\ 0 & 0 & 0 & \frac{1}{4} & 0 \\ 0 & 0 & 0 & 0 & \frac{1}{5} \end{bmatrix}; A^T = \begin{bmatrix} 1 & 0 \\ -1 & 0 \\ 1 & -1 \\ 0 & 1 \\ 0 & 1 \end{bmatrix}; V_s = \begin{bmatrix} 0 \\ 12 \\ 0 \\ 24 \\ 0 \end{bmatrix}$$

$$AY_b = \begin{bmatrix} 1 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} \frac{1}{4} & 0 & 0 & 0 & 0 \\ 0 & \frac{1}{3} & 0 & 0 & 0 \\ 0 & 0 & \frac{1}{8} & 0 & 0 \\ 0 & 0 & 0 & \frac{1}{4} & 0 \\ 0 & 0 & 0 & 0 & \frac{1}{5} \end{bmatrix} = \begin{bmatrix} \frac{1}{4} & -\frac{1}{3} & \frac{1}{8} & 0 & 0 \\ 0 & 0 & -\frac{1}{8} & \frac{1}{4} & \frac{1}{5} \end{bmatrix}$$

$$AY_b A^T = \begin{bmatrix} \frac{1}{4} & -\frac{1}{3} & \frac{1}{8} & 0 & 0 \\ 0 & 0 & -\frac{1}{8} & \frac{1}{4} & \frac{1}{5} \end{bmatrix} \begin{bmatrix} 1 & 0 \\ -1 & 0 \\ 1 & -1 \\ 0 & 1 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} \frac{17}{24} & -\frac{1}{8} \\ -\frac{1}{8} & \frac{23}{40} \end{bmatrix}$$

$$AY_b V_s = \begin{bmatrix} \frac{1}{4} & -\frac{1}{3} & \frac{1}{8} & 0 & 0 \\ 0 & 0 & -\frac{1}{8} & \frac{1}{4} & \frac{1}{5} \end{bmatrix} \begin{bmatrix} 0 \\ 12 \\ 0 \\ 24 \\ 0 \end{bmatrix} = \begin{bmatrix} -4 \\ 6 \end{bmatrix}$$

Hence, the KCL equation in matrix form is given by

$$\begin{bmatrix} \frac{17}{24} & -\frac{1}{8} \\ -\frac{1}{8} & \frac{23}{40} \end{bmatrix} \begin{bmatrix} V_{n_1} \\ V_{n_2} \end{bmatrix} = -\begin{bmatrix} -4 \\ 6 \end{bmatrix} = \begin{bmatrix} 4 \\ -6 \end{bmatrix}$$

Solving this matrix equation,

$$V_{n_1} = 3.96 \text{ V}$$

$$V_{n_2} = -9.57 \text{ V}$$

### 5.46 Circuit Theory and Networks—Analysis and Synthesis

Branch voltages are given by,

$$V_b = A^T V_n$$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ -1 & 0 \\ 1 & -1 \\ 0 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 3.96 \\ -9.57 \end{bmatrix} = \begin{bmatrix} 3.96 \\ -3.96 \\ 13.53 \\ -9.57 \\ -9.57 \end{bmatrix}$$

**Example 5.30** For the network shown in Fig. 5.76, write down the  $f$ -cutset matrix and obtain the network equilibrium equation in matrix form using KCL.

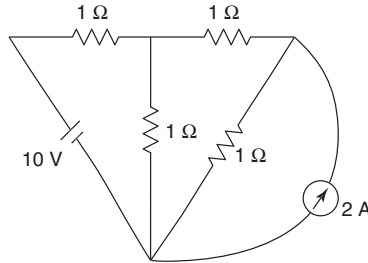


Fig. 5.76

**Solution** The oriented graph and its selected tree are shown in Fig. 5.77.

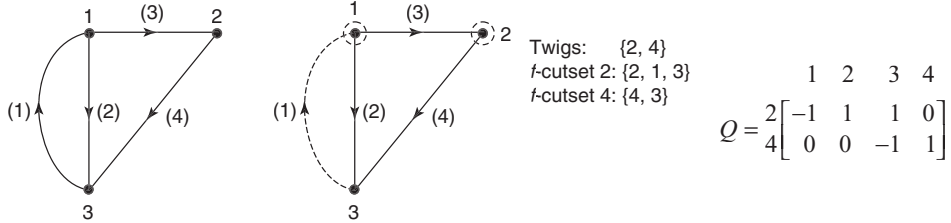


Fig. 5.77

The KCL equation in matrix form is given by

$$Q Y_b Q^T V_t = Q I_s - Q Y_b V_s$$

$$Y_b = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}; I_s = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 2 \end{bmatrix}; V_s = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}; Q^T = \begin{bmatrix} -1 & 0 \\ 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix}$$

$$Q Y_b = \begin{bmatrix} -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} = \begin{bmatrix} -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & 1 \end{bmatrix}$$

$$Q Y_b Q^T = \begin{bmatrix} -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} -1 & 0 \\ 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 3 & -1 \\ -1 & 2 \end{bmatrix}$$

$$QI_s = \begin{bmatrix} -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 0 \\ 2 \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \end{bmatrix}$$

$$QY_b V_s = \begin{bmatrix} -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -10 \\ 0 \end{bmatrix}$$

Hence, the KCL equation is given by

$$\begin{bmatrix} 3 & -1 \\ -1 & 2 \end{bmatrix} \begin{bmatrix} V_{t_2} \\ V_{t_4} \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \end{bmatrix} - \begin{bmatrix} -10 \\ 0 \end{bmatrix} = \begin{bmatrix} 10 \\ 2 \end{bmatrix}$$

Solving this matrix equation,

$$V_{t_2} = 4.4 \text{ V}$$

$$V_{t_4} = 3.2 \text{ V}$$

### Example 5.31

Calculate the twig voltages using KCL equation for the network shown in Fig. 5.78.

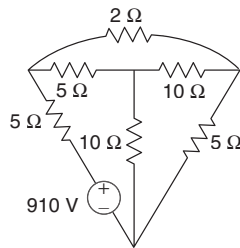


Fig. 5.78

**Solution** The oriented graph and one of the trees are shown in Fig. 5.79.

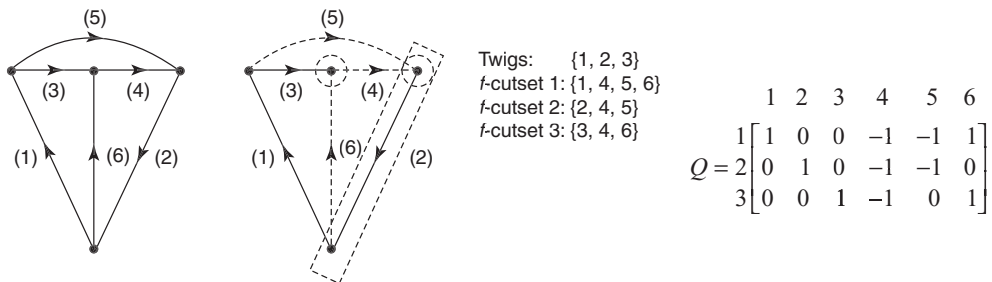


Fig. 5.79

The network equilibrium equation on node basis can be written as

$$QY_b Q^T V_t = QI_s - QY_b V_s$$

Here,

$$I_s = 0,$$

$$QY_b Q^T V_t = -QY_b V_s$$

### 5.48 Circuit Theory and Networks—Analysis and Synthesis

$$Y_b = \begin{bmatrix} 0.2 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0.2 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0.2 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0.1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0.5 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0.1 \end{bmatrix}; Q^T = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & -1 & -1 \\ -1 & -1 & 0 \\ 1 & 0 & 1 \end{bmatrix}; V_s = \begin{bmatrix} 910 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$QY_b = \begin{bmatrix} 1 & 0 & 0 & -1 & -1 & 1 \\ 0 & 1 & 0 & -1 & -1 & 0 \\ 0 & 0 & 1 & -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0.2 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0.2 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0.2 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0.1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0.5 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0.1 \end{bmatrix} = \begin{bmatrix} 0.2 & 0 & 0 & -0.1 & -0.5 & 0.1 \\ 0 & 0.2 & 0 & -0.1 & -0.5 & 0 \\ 0 & 0 & 0.2 & -0.1 & 0 & 0.1 \end{bmatrix}$$

$$QY_b Q^T = \begin{bmatrix} 0.2 & 0 & 0 & -0.1 & -0.5 & 0.1 \\ 0 & 0.2 & 0 & -0.1 & -0.5 & 0 \\ 0 & 0 & 0.2 & -0.1 & 0 & 0.1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & -1 & -1 \\ -1 & -1 & 0 \\ 1 & 0 & 1 \end{bmatrix} = \begin{bmatrix} 0.9 & 0.6 & 0.2 \\ 0.6 & 0.8 & 0.1 \\ 0.2 & 0.1 & 0.3 \end{bmatrix}$$

$$QY_b V_s = \begin{bmatrix} 0.2 & 0 & 0 & -0.1 & -0.5 & 0.1 \\ 0 & 0.2 & 0 & -0.1 & -0.5 & 0 \\ 0 & 0 & 0.2 & -0.1 & 0 & 0.1 \end{bmatrix} \begin{bmatrix} 910 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 182 \\ 0 \\ 0 \end{bmatrix}$$

Hence, KCL equation can be written as,

$$\begin{bmatrix} 0.9 & 0.6 & 0.2 \\ 0.6 & 0.8 & 0.1 \\ 0.2 & 0.1 & 0.3 \end{bmatrix} \begin{bmatrix} v_{t_1} \\ v_{t_2} \\ v_{t_3} \end{bmatrix} = \begin{bmatrix} -182 \\ 0 \\ 0 \end{bmatrix}$$

Solving this matrix equation,

$$v_{t_1} = -460 \text{ V}$$

$$v_{t_2} = 320 \text{ V}$$

$$v_{t_3} = 200 \text{ V}$$

### Example 5.32

For the network shown in Fig. 5.80, obtain equilibrium equation on node basis.


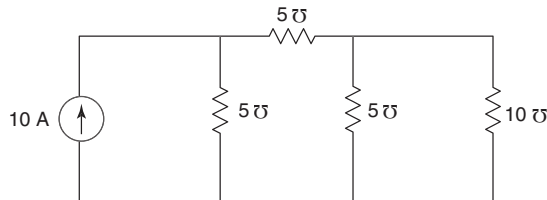


Fig. 5.80

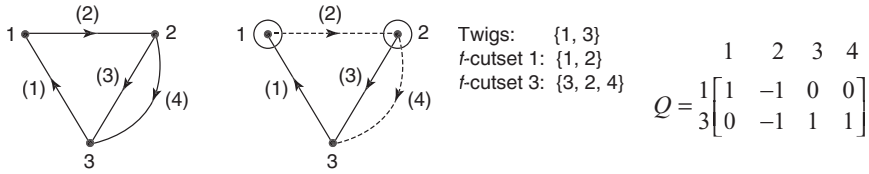

**Solution** The oriented graph and its selected tree are shown in Fig. 5.81.



**Fig. 5.81**

The KCL equation in matrix form is given by

$$QY_b Q^T V_t = QI_s - QY_b V_s$$

Here,

$$V_s = 0,$$

$$QY_b Q^T V_t = QI_s$$

$$Y_b = \begin{bmatrix} 5 & 0 & 0 & 0 \\ 0 & 5 & 0 & 0 \\ 0 & 0 & 5 & 0 \\ 0 & 0 & 0 & 10 \end{bmatrix}; Q^T = \begin{bmatrix} 1 & 0 \\ -1 & -1 \\ 0 & 1 \\ 0 & 1 \end{bmatrix}; I_s = \begin{bmatrix} -10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$QY_b = \begin{bmatrix} 1 & -1 & 0 & 0 \\ 0 & -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} 5 & 0 & 0 & 0 \\ 0 & 5 & 0 & 0 \\ 0 & 0 & 5 & 0 \\ 0 & 0 & 0 & 10 \end{bmatrix} = \begin{bmatrix} 5 & -5 & 0 & 0 \\ 0 & -5 & 5 & 10 \end{bmatrix}$$

$$QY_b Q^T = \begin{bmatrix} 5 & -5 & 0 & 0 \\ 0 & -5 & 5 & 10 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ -1 & -1 \\ 0 & 1 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 10 & 5 \\ 5 & 20 \end{bmatrix}$$

$$QI_s = \begin{bmatrix} 1 & -1 & 0 & 0 \\ 0 & -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} -10 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -10 \\ 0 \end{bmatrix}$$

Hence, KCL equation will be written as

$$\begin{bmatrix} 10 & 5 \\ 5 & 20 \end{bmatrix} \begin{bmatrix} v_{t_1} \\ v_{t_3} \end{bmatrix} = \begin{bmatrix} -10 \\ 0 \end{bmatrix}$$

Solving this matrix equation,

$$v_{t_1} = -\frac{8}{7}V$$

$$v_{t_3} = \frac{2}{7}V$$

**Example 5.33** For the network shown in Fig. 5.82, write down the  $f$ -cutset matrix and obtain the network equilibrium equation in matrix form using KCL and calculate  $v$ .

### 5.50 Circuit Theory and Networks—Analysis and Synthesis

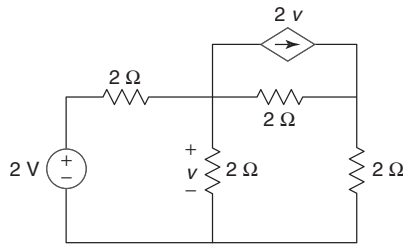


Fig. 5.82

**Solution** The oriented graph and its selected tree are shown in Fig. 5.83. Since voltage  $v$  is to be determined, Branch 2 is chosen as twig,

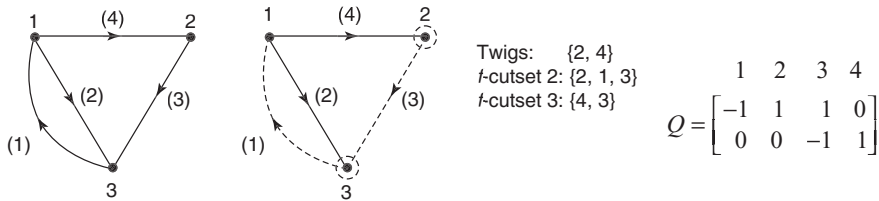


Fig. 5.83

The KCL equation in matrix form is given by

$$QY_b Q^T V_t = QI_s - QY_b V_s$$

$$Y_b = \begin{bmatrix} 0.5 & 0 & 0 & 0 \\ 0 & 0.5 & 0 & 0 \\ 0 & 0 & 0.5 & 0 \\ 0 & 0 & 0 & 0.5 \end{bmatrix}; Q^T = \begin{bmatrix} -1 & 0 \\ 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix}; I_s = \begin{bmatrix} 0 \\ 0 \\ 0 \\ -2v \end{bmatrix}; V_s = \begin{bmatrix} 2 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$QY_b = \begin{bmatrix} -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} 0.5 & 0 & 0 & 0 \\ 0 & 0.5 & 0 & 0 \\ 0 & 0 & 0.5 & 0 \\ 0 & 0 & 0 & 0.5 \end{bmatrix} = \begin{bmatrix} -0.5 & 0.5 & 0.5 & 0 \\ 0 & 0 & -0.5 & 0.5 \end{bmatrix}$$

$$QY_b Q^T = \begin{bmatrix} -0.5 & 0.5 & 0.5 & 0 \\ 0 & 0 & -0.5 & 0.5 \end{bmatrix} \begin{bmatrix} -1 & 0 \\ 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 1.5 & -0.5 \\ -0.5 & 1 \end{bmatrix}$$

$$QI_s = \begin{bmatrix} -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 0 \\ -2v \end{bmatrix} = \begin{bmatrix} 0 \\ -2v \end{bmatrix}$$

$$QY_b V_s = \begin{bmatrix} -0.5 & 0.5 & 0.5 & 0 \\ 0 & 0 & -0.5 & 0.5 \end{bmatrix} \begin{bmatrix} 2 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -1 \\ 0 \end{bmatrix}$$

$$QI_s - QY_b V_s = \begin{bmatrix} 1 \\ -2v \end{bmatrix}$$

Hence, the KCL equation can be written as

$$\begin{bmatrix} 1.5 & -0.5 \\ -0.5 & 1 \end{bmatrix} \begin{bmatrix} v_{t_2} \\ v_{t_4} \end{bmatrix} = \begin{bmatrix} 1 \\ -2v \end{bmatrix}$$

From Fig. 5.82,  $v_{t_2} = v$

Solving this matrix equation,

$$v_{t_2} = 0.44 \text{ V}$$

$$v_{t_4} = 0.66 \text{ V}$$

$$v = v_{t_2} = 0.44 \text{ V}$$

**Example 5.34** For the network shown in Fig. 5.84, write down the  $f$ -cutset matrix and obtain the network equilibrium equation in matrix form using KCL and calculate  $v$ .

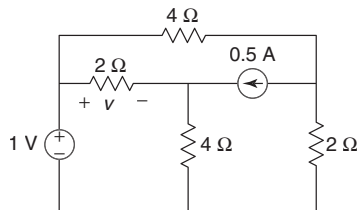


Fig. 5.84

**Solution** The voltage and current sources are converted into accompanied sources by source-shifting method as shown in Fig. 5.85.

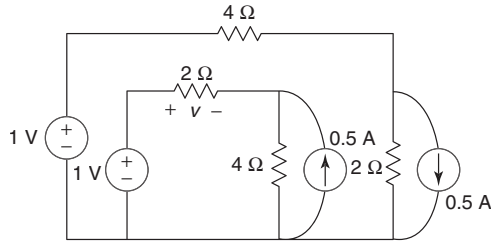


Fig. 5.85

The oriented graph and its selected tree are shown in Fig. 5.86.

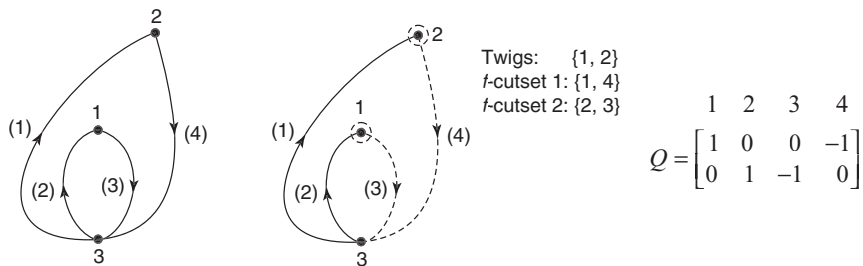


Fig. 5.86

### 5.52 Circuit Theory and Networks—Analysis and Synthesis

The KCL equation in the matrix form is given by

$$\begin{aligned}
 QY_b Q^T V_t &= QI_s - QY_b V_s \\
 Y_b &= \begin{bmatrix} 0.25 & 0 & 0 & 0 \\ 0 & 0.5 & 0 & 0 \\ 0 & 0 & 0.25 & 0 \\ 0 & 0 & 0 & 0.5 \end{bmatrix}; Q^T = \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 0 & -1 \\ -1 & 0 \end{bmatrix}; I_s = \begin{bmatrix} 0 \\ 0 \\ 0.5 \\ -0.5 \end{bmatrix}; V_s = \begin{bmatrix} 1 \\ 1 \\ 0 \\ 0 \end{bmatrix} \\
 QY_b &= \begin{bmatrix} 1 & 0 & 0 & -1 \\ 0 & 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} 0.25 & 0 & 0 & 0 \\ 0 & 0.5 & 0 & 0 \\ 0 & 0 & 0.25 & 0 \\ 0 & 0 & 0 & 0.5 \end{bmatrix} = \begin{bmatrix} 0.25 & 0 & 0 & -0.5 \\ 0 & 0.5 & -0.25 & 0 \end{bmatrix} \\
 QY_b Q^T &= \begin{bmatrix} 0.25 & 0 & 0 & -0.5 \\ 0 & 0.5 & -0.25 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 0 & -1 \\ -1 & 0 \end{bmatrix} = \begin{bmatrix} 0.75 & 0 \\ 0 & 0.75 \end{bmatrix} \\
 QI_s &= \begin{bmatrix} 1 & 0 & 0 & -1 \\ 0 & 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 0.5 \\ -0.5 \end{bmatrix} = \begin{bmatrix} 0.5 \\ -0.5 \end{bmatrix} \\
 QY_b V_s &= \begin{bmatrix} 0.25 & 0 & 0 & -0.5 \\ 0 & 0.5 & -0.25 & 0 \end{bmatrix} \begin{bmatrix} 1 \\ 1 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0.25 \\ 0.5 \end{bmatrix} \\
 QI_s - QY_b V_s &= \begin{bmatrix} 0.25 \\ -1 \end{bmatrix}
 \end{aligned}$$

Hence, the KCL equation can be written as

$$\begin{bmatrix} 0.75 & 0 \\ 0 & 0.75 \end{bmatrix} \begin{bmatrix} v_{t_1} \\ v_{t_2} \end{bmatrix} = \begin{bmatrix} 0.25 \\ -1 \end{bmatrix}$$

Solving this matrix equation,

$$v_{t_1} = 0.33 \text{ V}$$

$$v_{t_2} = -1.33 \text{ V}$$

From Fig. 5.85,

$$v = 1 + v_{t_2} = -0.33 \text{ V}$$

# Exercises

5.1 For the networks shown in Fig. 5.87–5.90, write the incidence matrix, tieset matrix and  $f$ -cutset matrix.

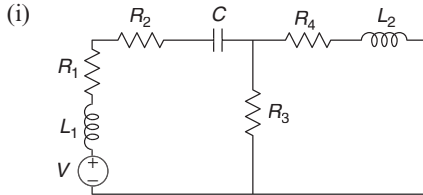


Fig. 5.87

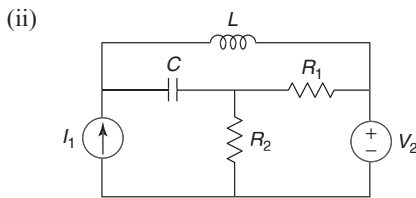


Fig. 5.88

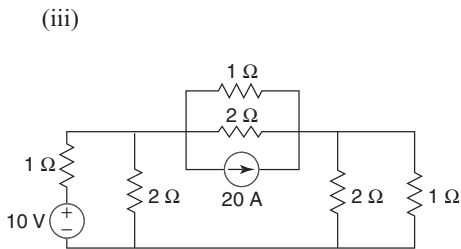


Fig. 5.89

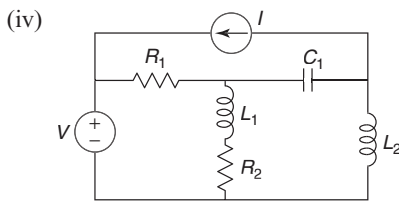


Fig. 5.90

5.2 For the graph shown in Fig. 5.91, write the incidence matrix, tieset matrix and  $f$ -cutset matrix.

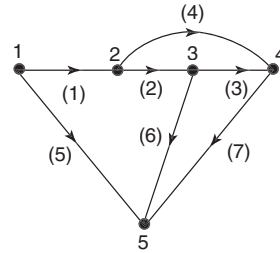


Fig. 5.91

5.3 The incidence matrix is given as follows:

Branches →							
1	2	3	4	5	6	7	8
-1	-1	0	0	0	0	1	0
0	1	1	0	1	0	0	0
0	0	-1	-1	0	1	0	0
1	0	0	1	0	0	0	1

Draw oriented graph and write tieset matrix.

5.4 The incidence matrix is given below:

Branches →									
1	2	3	4	5	6	7	8	9	10
0	0	1	1	1	1	0	1	0	0
0	-1	-1	0	0	0	-1	0	0	-1
-1	1	0	0	0	0	0	-1	-1	1
1	0	0	0	-1	-1	1	0	0	0

Draw the oriented graph.

5.5 For the network shown in Fig. 5.92, draw the oriented graph and obtain the tieset matrix. Use this matrix to calculate the current  $i$ .


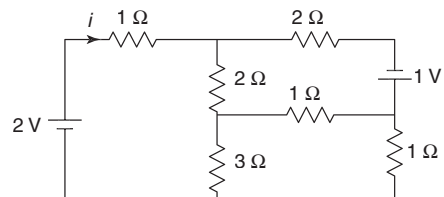


Fig. 5.92

[0.91 A]

**5.54** *Circuit Theory and Networks—Analysis and Synthesis*

- 5.6** Using the principles of network topology, write the loop/node equation in matrix form for the network shown in Fig. 5.93.

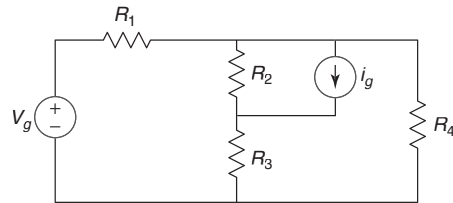

**Fig. 5.93**


## Objective-Type Questions

- 5.1** The number of independent loops for a network with  $n$  nodes and  $b$  branches is  
 (a)  $n - 1$   
 (b)  $b - n$   
 (c)  $b - n + 1$   
 (d) independent of the number of nodes

- 5.2** A network has 7 nodes and 5 independent loops. The number of branched in the network is

- (a) 13 (b) 12  
 (c) 11 (d) 10


- 5.3** Identify which of the following is NOT a tree of the graph shown in Fig. 5.94.

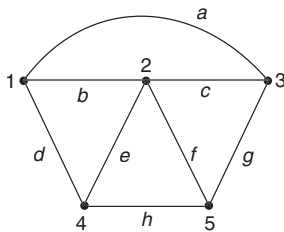

**Fig. 5.94**

- (a)  $begh$  (b)  $defg$   
 (c)  $adfg$  (d)  $aegh$


- 5.4** The minimum number of equations required to analyze the circuit shown in Fig. 5.95 is

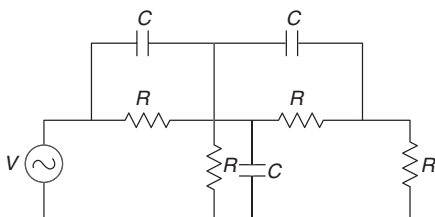

**Fig. 5.95**


- (a) 3 (b) 4  
 (c) 6 (d) 7

- 5.5** Consider the network graph shown in Fig. 5.96.

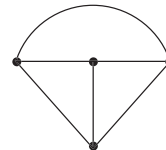


**Fig. 5.96**

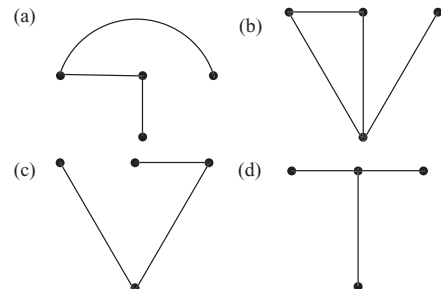- Which one of the following is NOT a tree of this graph?



- 5.6** Figure 5.97 below shows a network and its graph is drawn aside. A proper tree chosen for analyzing the network will contain the edges.

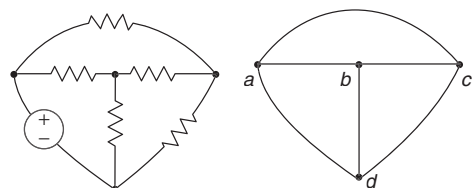

**Fig. 5.97**

- (a)  $ab, bc, ad$  (b)  $ab, bc, ca$   
 (c)  $ab, bd, ca$  (d)  $ac, bd, ad$

5.7 The graph of an electrical network has  $n$  nodes and  $b$  branches. The number of links with respect to the choice of a tree is given by

- (a)  $b - n + 1$  (b)  $b + n$   
(c)  $n - b + 1$  (d)  $n - 2b - 1$ .

5.8 In the graph shown in Fig. 5.98, one possible tree is formed by the branches 4, 5, 6, 7. Then one possible fundamental cutset is

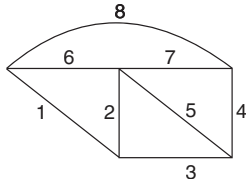


Fig. 5.98

- (a) 1, 2, 3, 8 (b) 1, 2, 5, 6  
(c) 1, 5, 6, 8 (d) 1, 2, 3, 7, 8

5.9 Which one of the following represents the total number of trees in the graph given in Fig. 5.99?

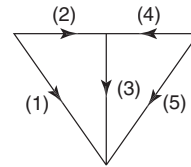


Fig. 5.99

- (a) 4 (b)  $C$   
(c) 5 (d) 8

5.10 Which one of the following is a cutset of the graph shown in Fig. 5.100?

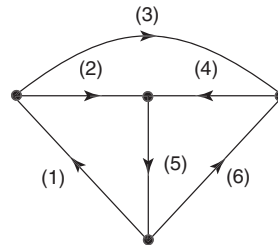


Fig. 5.100

- (a) 1, 2, 3 and 4 (b) 2, 3, 4 and 6  
(c) 1, 4, 5 and 6 (d) 1, 2, 4 and 5

## Answers to Objective-Type Questions

- 5.1. (c) 5.2. (c) 5.3. (c) 5.4. (b) 5.5. (b)  
5.6. (d) 5.7. (a) 5.8. (d) 5.9. (d) 5.10. (d)