


Module 2

Page No. _____

Date _____


Applications of op-amp-

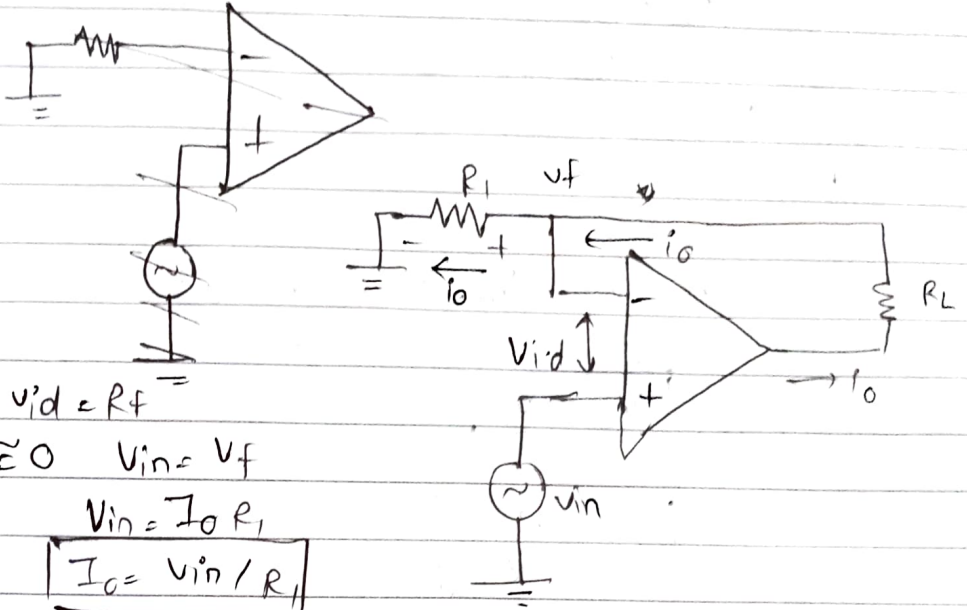- ① Voltage to current converter with floating load



Used in many applications like diode match finders, LED Tester, Zener diode tester low voltage AC and DC

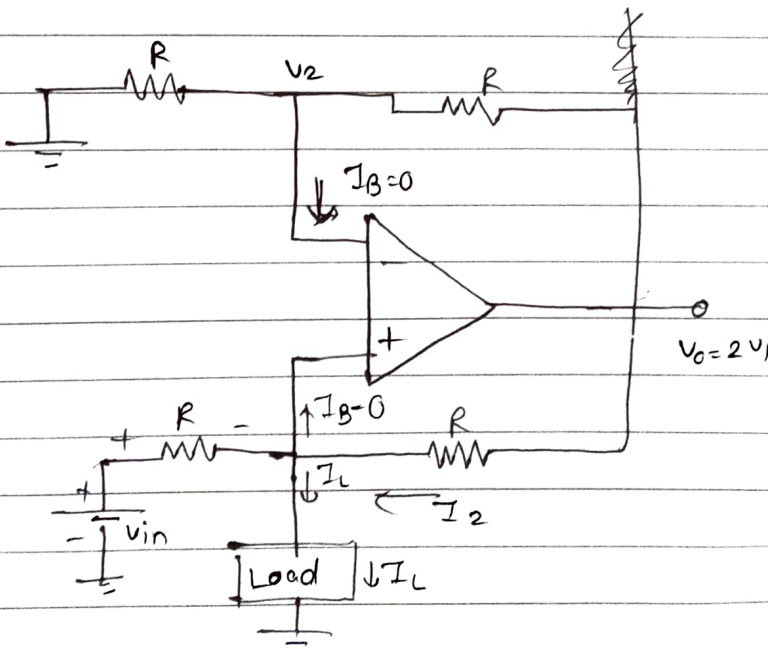* Voltage to current with grounded load: voltage meter



$$I_1 + I_2 = I_B + I_L$$

$$I_1 + I_2 = I_L$$

$$\frac{V_{in} - V_1}{R} + \frac{V_1 - V_0}{R} = I_L$$

$$V_1 =$$

$$V_{in} - V_1 + V_0 - V_1 = I_L R$$

$$V_{in} + V_0 - 2V_1 = I_L R$$

$$I_L R - V_{in} + V_0 = 2V_1$$

$$I_L R$$


$$\frac{V_{in} + V_0}{2} = \frac{V_{in} + V_0 - I_L R}{2}$$

$$V_0 = 2V_1$$

$$I_L = \frac{V_{in}}{R}$$

i/p sin square三角
o/p cos三角 sin

* Op-amp as Integrator:

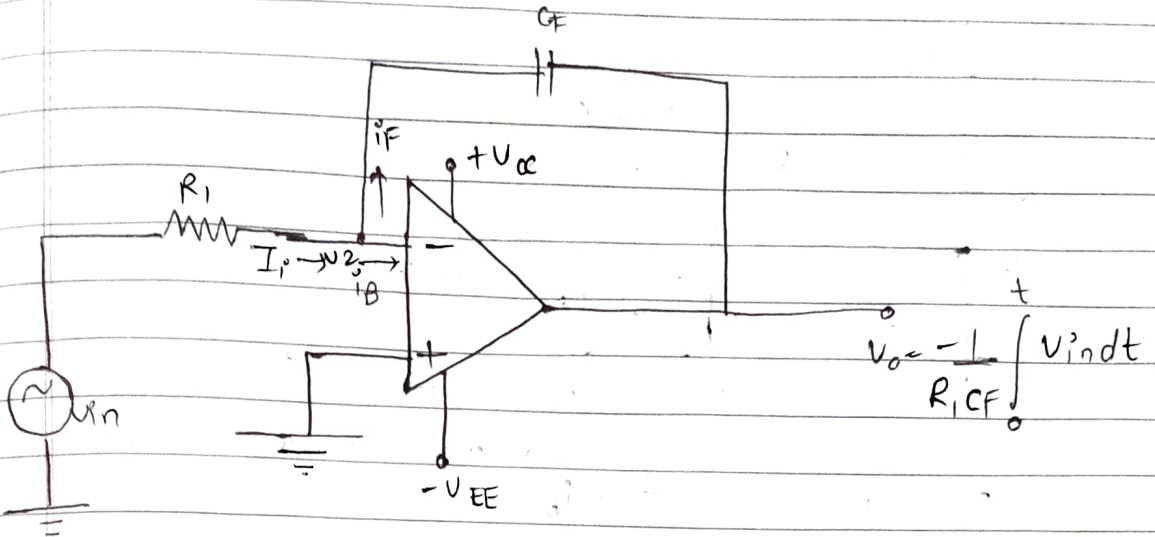

instead of $R_F = C_F$

KVL at V_2 ,

$$I_i \approx I_F$$

$$\frac{V_{in} - V_2}{R_1} = C_F \frac{d(V_2 - V_o)}{dt}$$

$$V_2 \approx 0$$

$$\frac{V_{in}}{R_1} = -C_F \frac{dV_o}{dt}$$

$$V_{in} = -R_1 C_F \frac{dV_o}{dt}$$


$$V_o = -\frac{1}{R_1 C_F} \int V_{in} dt + C$$

$$A_v = -\frac{X_C}{R_1}$$

$$A_v = -\frac{1}{2\pi f_c R_1}$$

produces error voltage

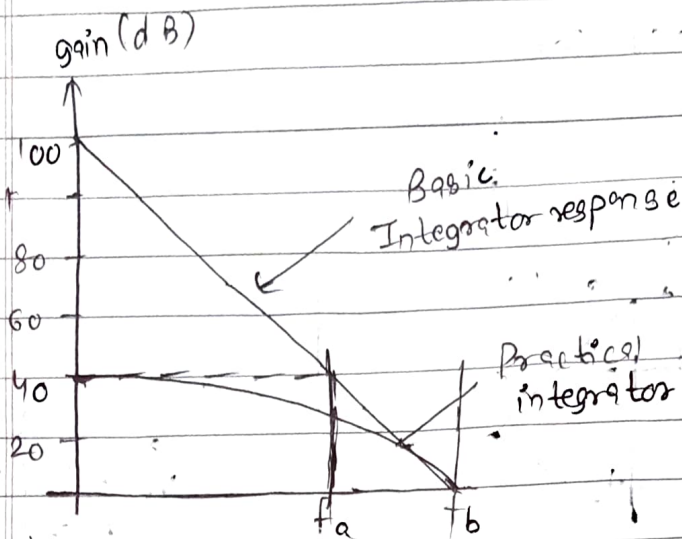At low frequency, C_F will act as open circuit. If we connect R_F in parallel to Open circuit, it will limit the gain, hence ^{called} practical integrator



~~for~~ Criteria to design integrator

$$F_a = \frac{1}{2\pi R_1 C_F}$$

$$F_a < F_b$$

$$F_b = \frac{1}{2\pi R_F C_F}$$

$$F_a = \frac{f_b}{10}$$

$$2\pi R_F C_F$$


$$T \geq R_F C_F$$

- ① In ideal integrator at low frequency, capacitor will behave as an open circuit, due to this whole circuit will act as a open loop configuration, so even small amount of input offset voltage produces a error voltage at output, so to avoid this practical integrator is used and R_F is connected across capacitor C_F so that gain will be limited, i.e. $-\frac{R_F}{R_1}$


$$V_o = -\frac{1}{R_1 C_F} \int_0^t V_{in} dt$$

$$= \left[-\int_0^1 2 dt + \int_1^2 2 dt + \int_2^3 2 dt + \int_3^4 2 dt \right]$$

$$V_o = -8$$

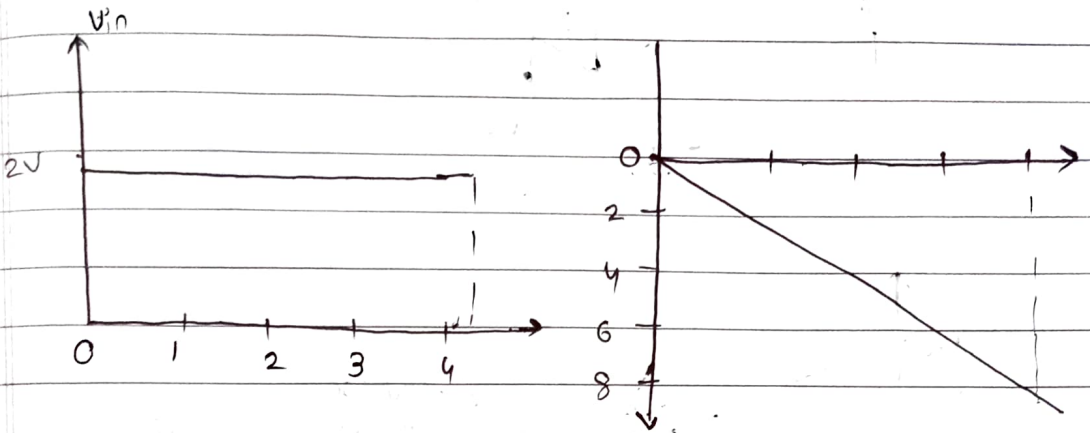

* Differentiator

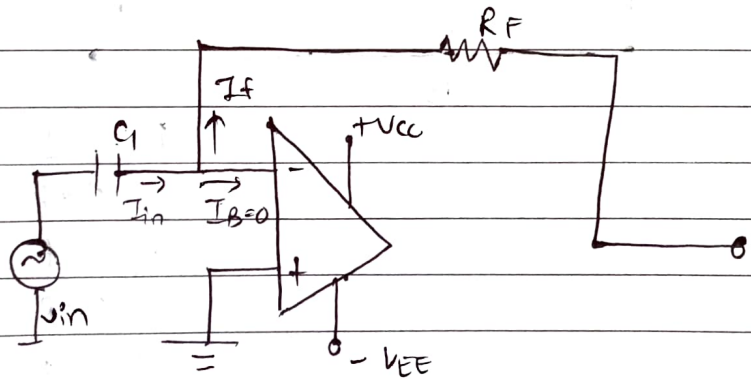

$$V_o = -R_F C_1 \frac{dV_{in}}{dt}$$



$$C_1 \frac{dV_{in}}{dt} = -\frac{V_o}{R_F}$$

$$A_v = -\frac{R_F}{X_c}$$

$$= -R_F 2\pi f_c$$

i/p
sin
square
triang
square

For practical differentiator,

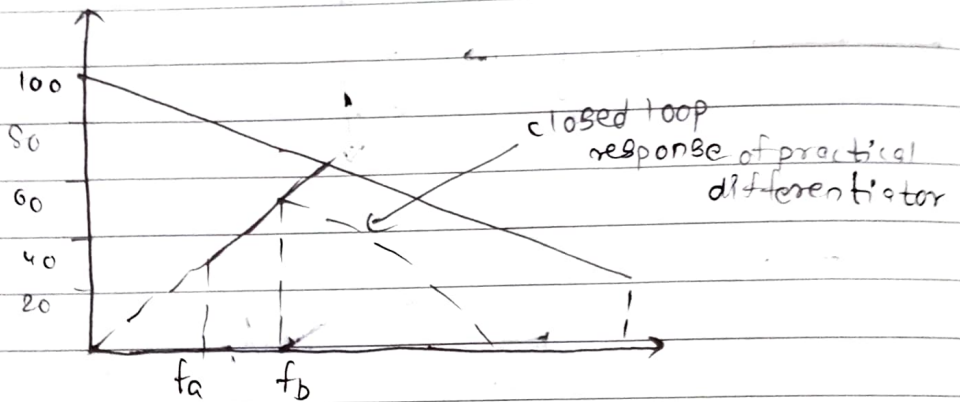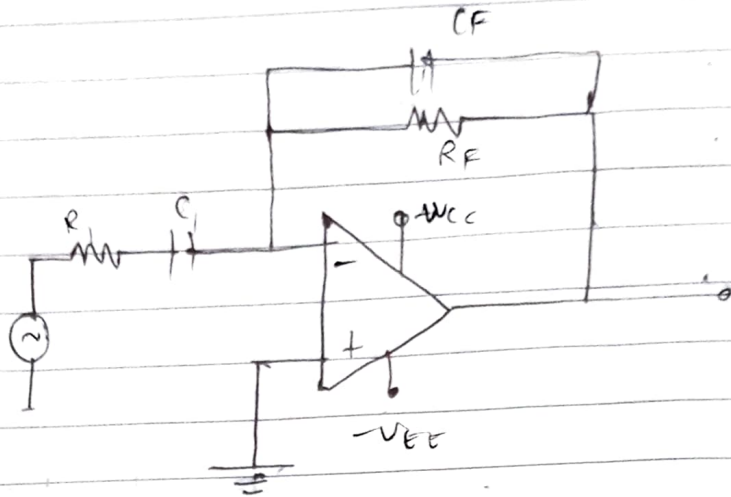

$$F_a = \frac{1}{2\pi R_F C_F}$$

$$F_b = \frac{1}{2\pi R_i C_i}$$

$$F_a < F_b < F_c$$

$$T > R_F C_F$$

4. Design a differentiator to differentiate an input signal that varies from 10 Hz to 1 kHz.

If a sin wave of 1 volt peak at 1 kHz is applied to differentiator, then derive output.

$$V_o = -R_F C_1 \frac{dV_{in}}{dt}$$

$$f_c < f_b < f_c$$

$$f_a = 1 \text{ kHz}$$

(min/p
freq)

$$\textcircled{1} F_a = \frac{1}{2\pi R_F C_1}$$

$$C = \text{less than } 1 \mu\text{F}$$

$$C_1 = 0.1 \mu\text{F}$$

$$R_F = 1.59 \text{ k}\Omega$$

$$\textcircled{2} f_b = 20 \text{ kHz}$$

$$f_b = \frac{1}{2\pi R_1 C_1}$$

$$R_1 = 79.5 \Omega$$

$$\textcircled{3} R_1 C_1 = R_F C_F$$

$$C_F = \frac{79.5 \times 0.1 \times 10^{-6}}{1.59 \times 10^3}$$

$$C_F = 5 \text{ nF}$$

$$V_o = -R_F C_1 \frac{dV_{in}}{dt}$$

$$= -1.59 \times 10^3 \times 0.1 \times 10^{-6} \frac{d}{dt} (V_p \sin \omega t)$$

$$= -0.159 \times 10^{-3} \frac{d}{dt} \sin 2\pi \times 10^3 t \quad (V_p = 1)$$





$$2\pi \times 10^3 \times 0.159 \times 10^{-3} \cos 2\pi \times 10^3 t$$


$$= -0.99 \cos(2\pi \times 10^3 t)$$

Module

Filters

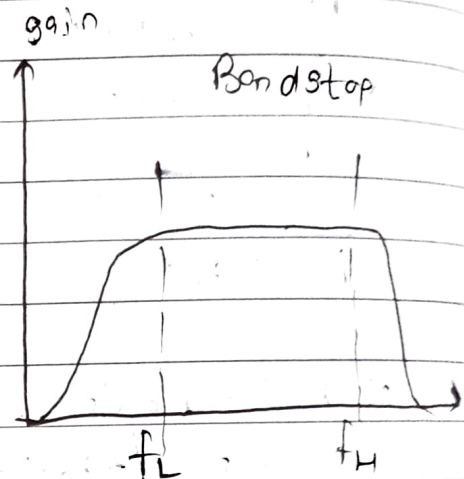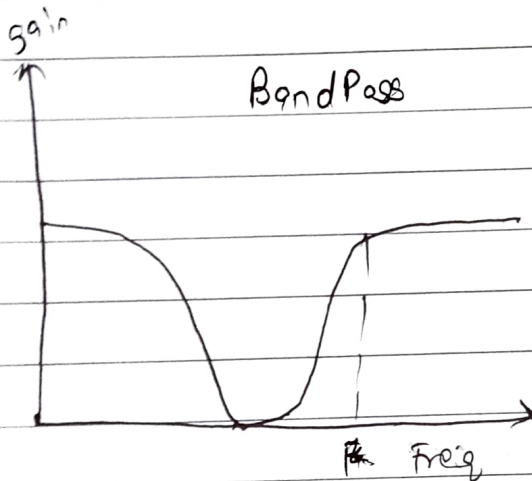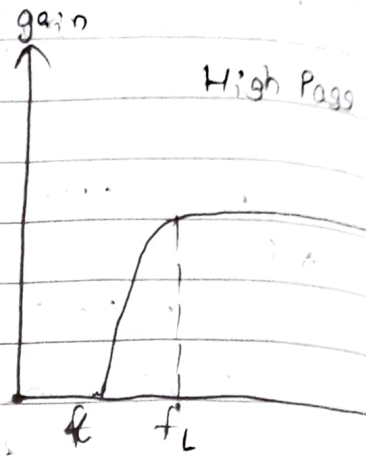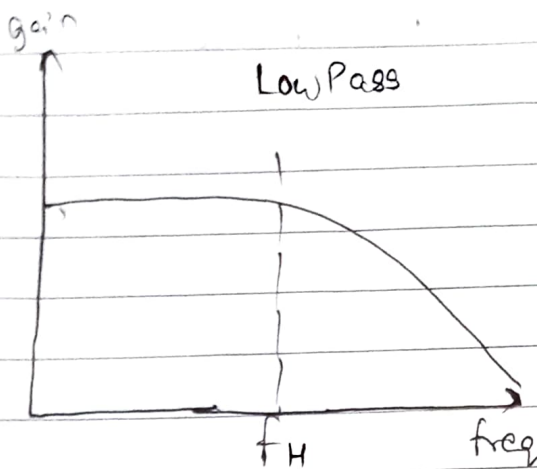- 1) Active or Passive
- 2) RF or AF _(LF) _(HF)
- 3) RC or LC Analog or Digital



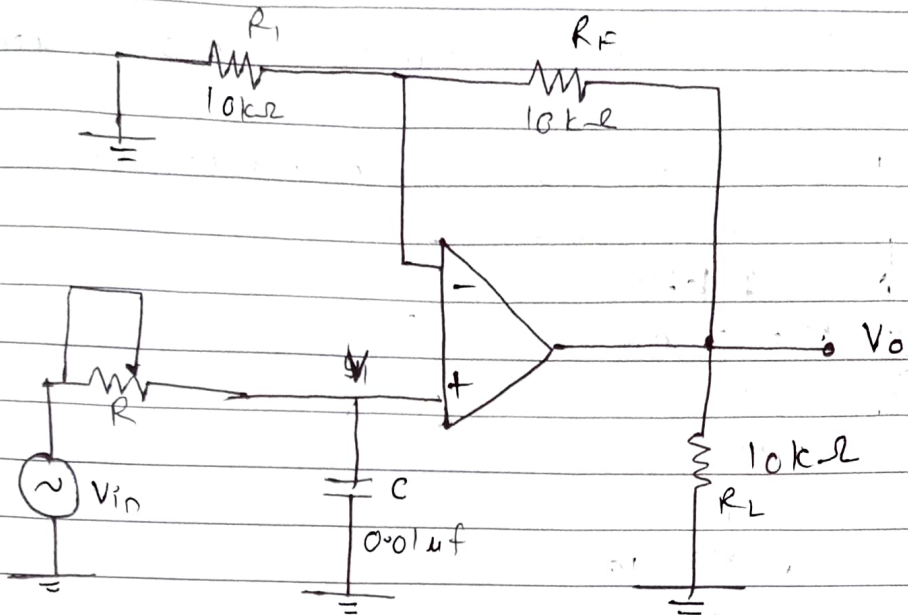1) 1st order Low Pass Filter

$$V_1 = \frac{-jX_C \cdot V_{in}}{R + jX_C}$$

$$V_o = (1 + R_F/R_1) V_1$$

$$V_1 = \frac{V_{in}}{1 + j2\pi f R_C}$$

$$V_o = (1 + R_F/R_1) V_1$$

$$V_1 = \frac{V_{in}}{1 + j2\pi f R_C}$$

$$V_o = \frac{(1 + R_F/R_1) V_{in}}{1 + j2\pi f R_C}$$

$$\frac{V_o}{V_{in}} = \frac{A_f}{1 + j(f/f_H)}$$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_f}{\sqrt{1 + (f/f_H)^2}}$$

(5M)

Design steps

- ① Choose a high cutoff frequency f_H .
- ② Select the value of capacitor less than or equal to $1\mu F$.
- ③ Calculate the value of R .
- ④ Select the value of R_1 and R_F for desired gain.

eg:- Design a low pass filter with cutoff frequency $1kHz$ pass band gain of 2.

→ ① $f_H = 1 kHz$

② $C = 0.1 \mu F$

③ $f = \frac{1}{2\pi RC}$

$$R = \frac{1}{2\pi \times 10^3 \times 10^{-7}}$$

$$= \frac{10^4}{2\pi}$$

$$= 1591.5$$


$$= 1.59 k\Omega$$

$$A_F = 1 + \frac{R_F}{R_1} = 2$$

$$\frac{R_F}{R_1} = 1$$

$$R_F = 1k\Omega, R_1 = 1k\Omega$$

* Second Order Low Pass Filter

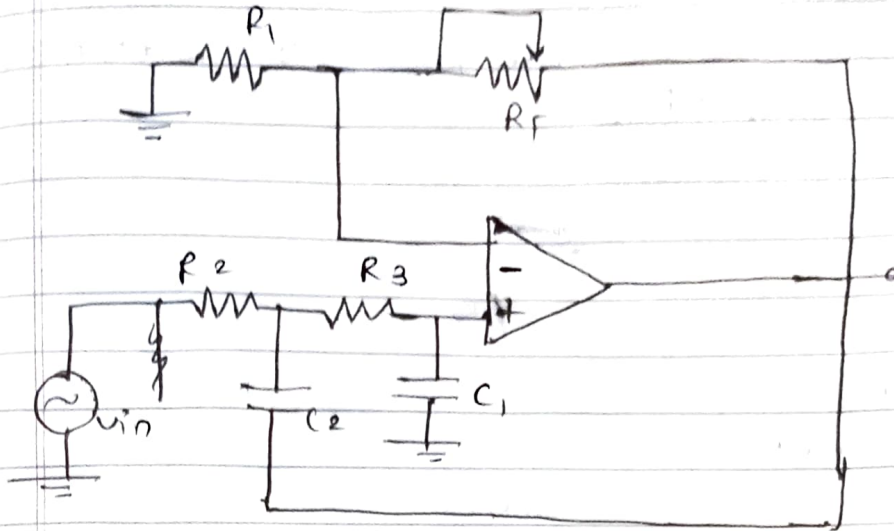


$$f_H = \frac{1}{2\pi\sqrt{R_2 R_3 C_1 C_2}}$$

$$\left| \frac{V_O}{V_{in}} \right| = \frac{A_f}{\sqrt{1 + \left(\frac{f}{f_H} \right)^4}}$$

$$A_f = 1 + \frac{R_F}{R_1}$$
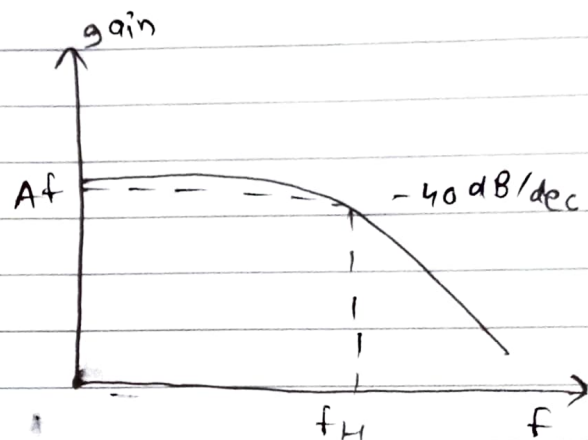
$$f_H = \frac{1}{2\pi\sqrt{R_2 R_3 C_1 C_2}}$$



Design a second order filter

① Choose a value of higher cutoff frequency f_H .

② Assume $R_2, R_3 = R$

$$C_1 = C_2 = C$$

$$C < 1\mu F$$

$$\textcircled{3} f_H = \frac{1}{2\pi RC}$$

Calculate value of R based on formula,

④ Determine the value of R_F and R_1 should be less than equal to $100\text{ k}\Omega$ ($R_1 \leq 100\text{ k}\Omega$)

eg: 1) Design a second order low pass filter with high cutoff frequency 1 kHz .

① $f_H = 1\text{ kHz}$

② $C = 0.0047$

③ $f_H = \frac{1}{2\pi RC}$

$R = 33.86\text{ k}\Omega$

④ $1 + \frac{R_F}{R_1}$

$R_1 = 30\text{ k}\Omega$

$R_F = 17.58\text{ k}\Omega$