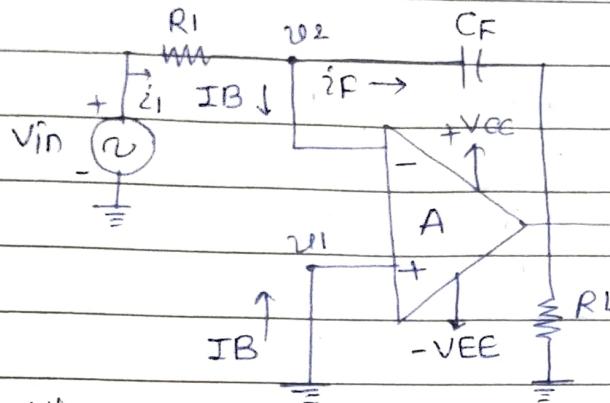


⇒ Integrator (Integrating amp) ⇒



- In this ckt the O/P waveform is the integral of the I/P vfg. wlf.
- This ckt is obtained by using a basic inverting amp config. if the f/b resi RF is replaced by a capacitor CF.



- If  $V_{in} = 0$ , CF will act as short ckt. Hence CF will charge due to  $i_F$  of error vfg. is produced.

$$V_{out} = -\frac{1}{R_1 \cdot C_F} \int V_{in} dt + C$$

- To remove this use RF.

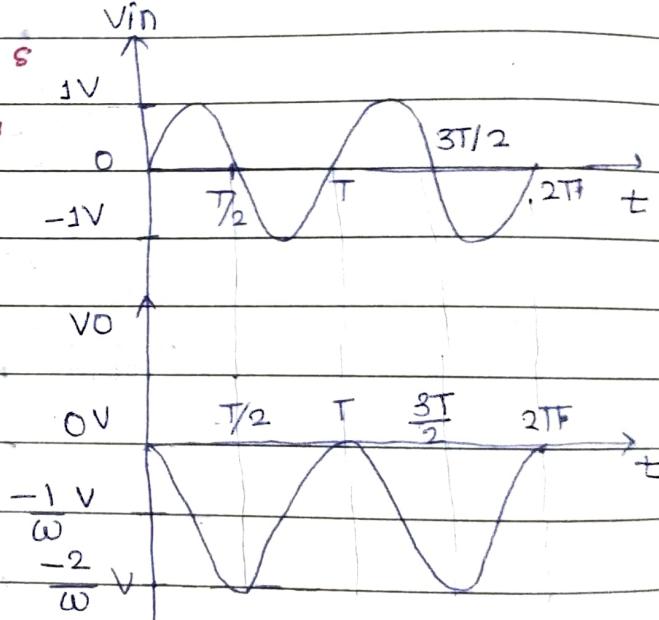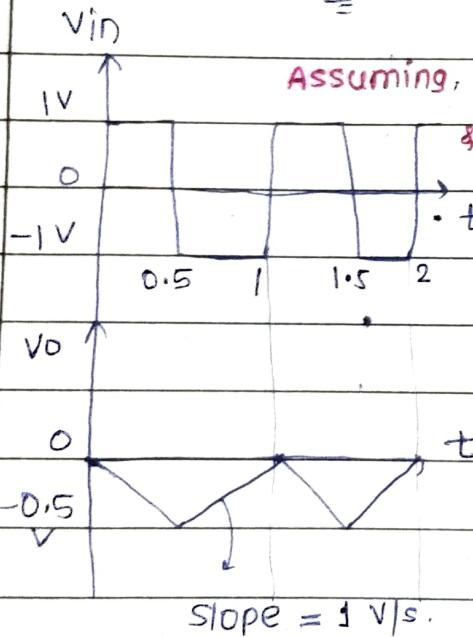

- Using KCL at node  $v_2$ ,

$$i_i = i_B + i_F$$

∴  $i_B$  is negligibly small (due to  $R_i \gg$ )

$$i_i \approx i_F$$

we know the relation bet<sup>1</sup> current flowing the C & vfg. acc C

$$i_C = C \cdot \frac{dV_C}{dt}$$

$$\therefore \frac{v_{in} - v_2}{R_1} = CF \cdot \left( \frac{d}{dt} \right) (v_2 - v_0)$$

However,  $v_1 = v_2 \approx 0$  because A is very large.

$$\therefore \frac{v_{in}}{R_1} = CF \cdot \frac{d}{dt} (-v_0)$$

The O/P vrg. can be obtained by integrating both sides w.r.t time

$$\int_0^t \frac{v_{in} \cdot dt}{R_1} = \int_0^t CF \cdot \frac{d}{dt} (-v_0) \cdot dt$$


$$= CF (-v_0) + \cancel{C} \mid t=0$$

$$\therefore v_0 = -\frac{1}{R_1 \cdot CF} \int_0^t v_{in} dt + C \rightarrow @$$

where C is the integration constant & is proportional to the value of the output voltage  $v_0$  at time  $t=0$  sec

eqn @ indicates that O/P vrg is directly  $\propto$  to the -ve integral of the IIP vrg. & inversely  $\propto$  to the time constant  $R_1 C F$ .

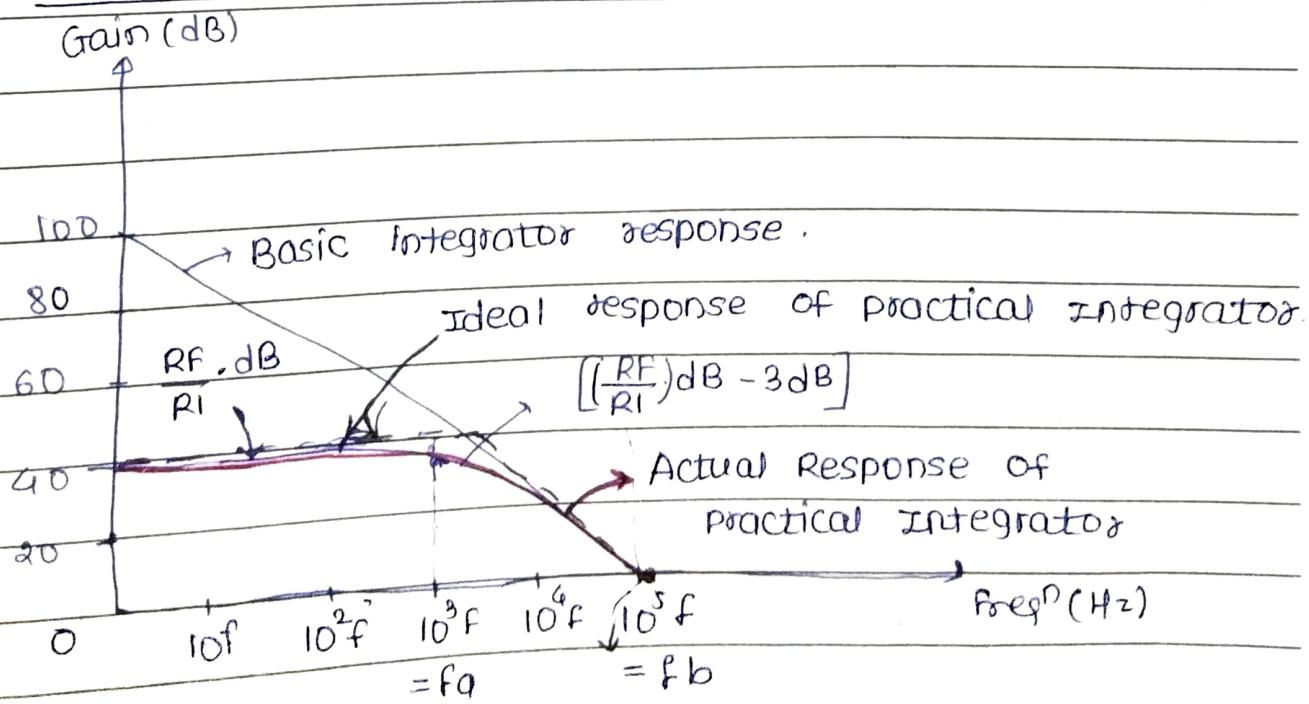→ freq<sup>n</sup> Response of Integrator ckt:




Here,  $f_a = 3 \text{ dB}$  below max gain gives this freq<sup>n</sup> i.e called as break freq<sup>n</sup>  $= \frac{1}{2\pi R_F C_F} = f_a$

&  $f_b = \text{freq}^n$  at which gain is 0.

$$f_b = \frac{1}{2\pi R_I C_F}$$

### Practical Integrator :-

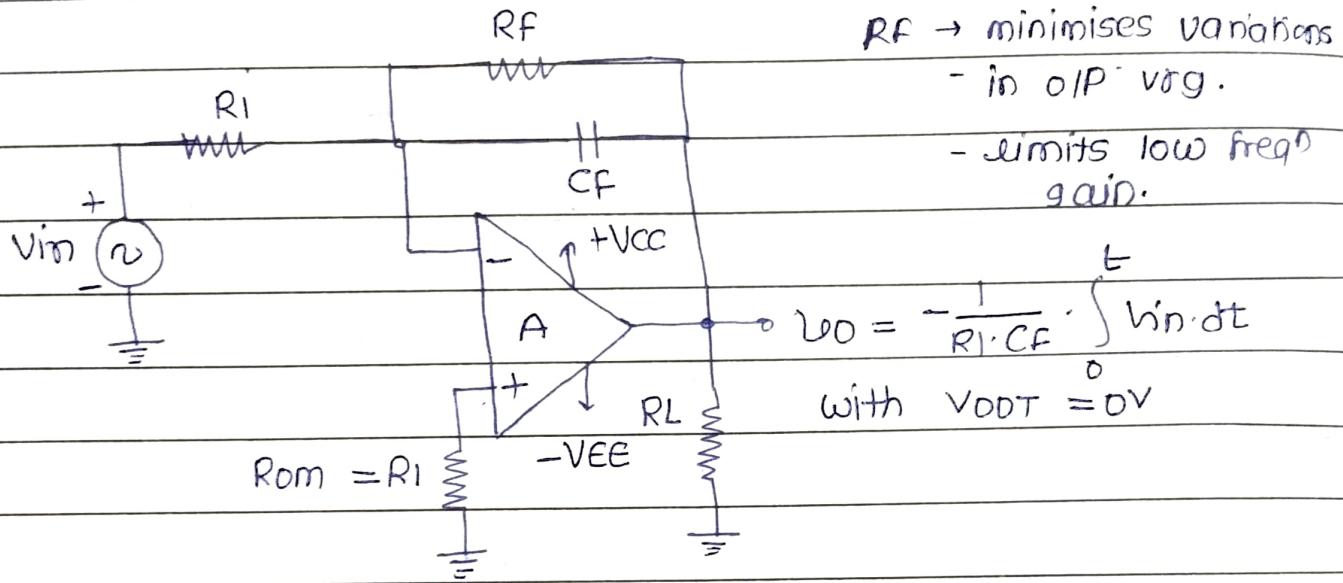

- for proper operation of the ckt,

- value of  $f_a$  & in turn  $R_I C_F$  &  $R_F C_F$  should be selected such that  $f_a < f_b$ .

e.g. if  $f_a = f_b / 10$  then  $R_F = 10 R_I$

- i.e.  $T \geq R_F C_F$ . ( $R_I C_F \geq R_F C_F$ ).

where,  $R_F C_F = \frac{1}{2\pi f_a}$

### Application:



- Analog computers

- ADC

- signal wave shaping ckt's.

⇒ Differentiator  $\Rightarrow$  (differentiation amp)

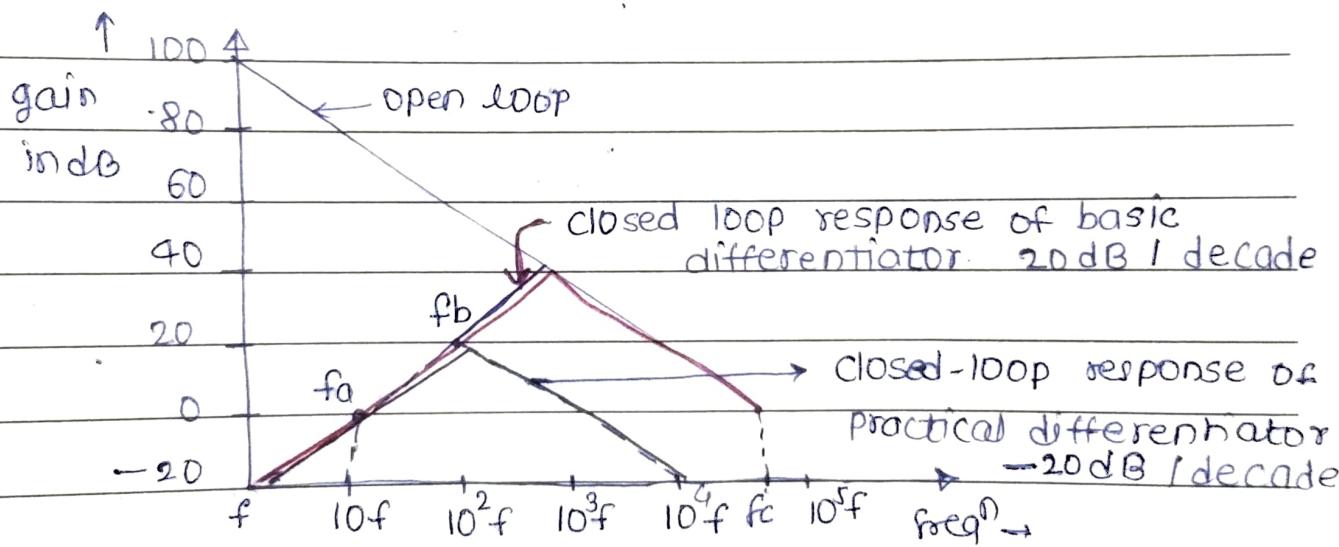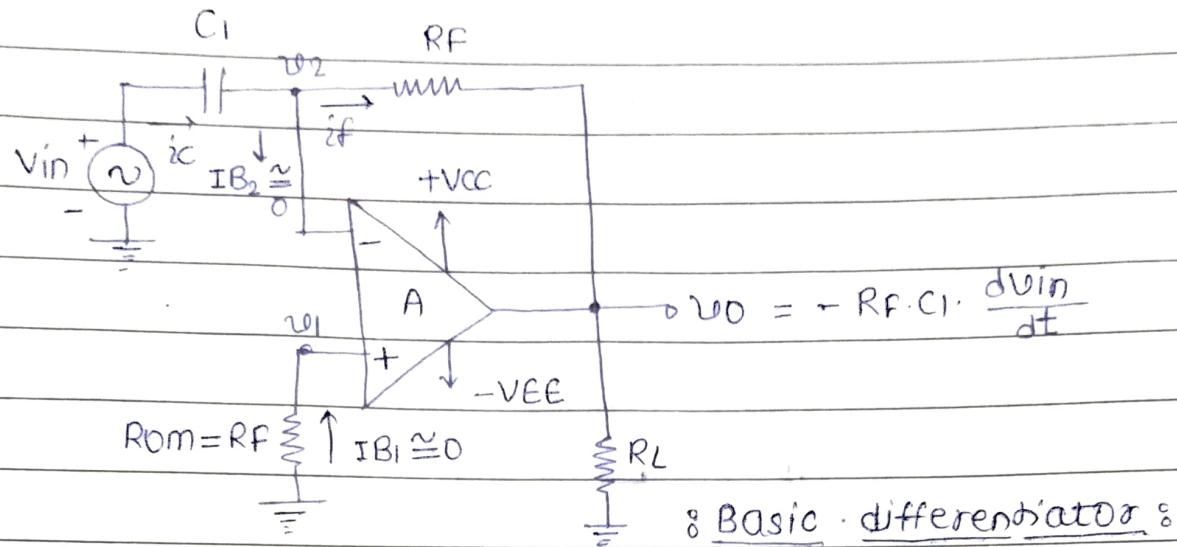- The O/P wlf is the derivative of the IIP wlf.
- It can be constructed from a basic inv. amp if an IIP resistor  $R_1$  is replaced by a capacitor  $C_1$ .



: frequency Response:

Apply KCL at node  $V_2$ ,

$$i_C = i_B + i_f$$

$$\therefore i_B \approx 0$$

$$i_C = i_f$$

$$C_1 \cdot \frac{d(V_{in} - V_2)}{dt} = \frac{V_2 - V_{20}}{R_F}$$

But  $V_{21} = V_2 \approx 0 \text{ V}$ , because  $A$  is very large.

$$\therefore C_1 \cdot \frac{dV_{in}}{dt} = -\frac{V_{20}}{R_F}$$

$$\text{or } V_o = -R_{FCF} \cdot \frac{dV_{in}}{dt}$$

- In freq<sup>n</sup> response,


$f_a$  = freq<sup>n</sup> at which gain is 0.

$$= \frac{1}{2\pi R_{FCF}}$$

~~$f_b$~~  = unity gain B/w.

$f$  = relative operating freq<sup>n</sup>.

⇒ Practical differentiator :-

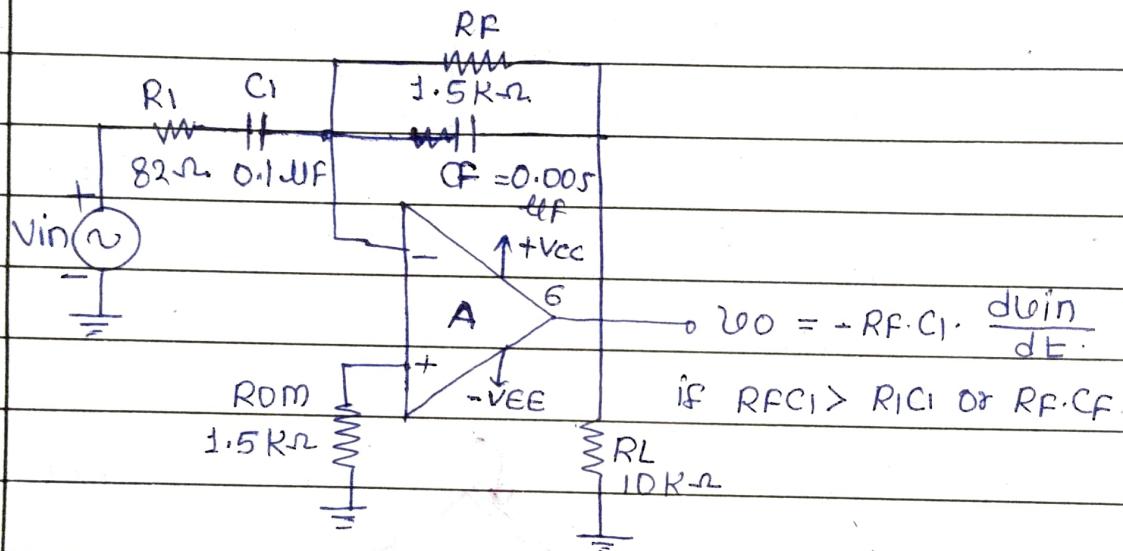

$R_1 \& C_F$  :- To eliminate high freq<sup>n</sup> noise problem.

- To increase stability.

$$f_b = \text{gain limiting freq} = \frac{1}{2\pi R_{IC1} C_1}$$

- Generally value of  $f_b$  i.e  $R_{IC1} \& R_{FCF}$  should be selected such that,

$$f_a < f_b < f_c$$

$$\text{where, } f_a = \frac{1}{2\pi R_{IC1}}$$

$$f_b = \frac{1}{2\pi R_{IC1}} = \frac{1}{2\pi R_{FCF}}$$

$f_c$  = unity gain freq<sup>n</sup> in open loop

→ for proper differentiation,

$$T \geq R_F \cdot C_1$$

→ for workable differentiator, Design steps are:

- select  $f_0 = \text{highest IIP freq}^n$  to be differentiated

- assume  $C_1 < 1\text{UF}$  & calculate value of  $R_F$ .


- choose  $f_b = 20f_0$  & calculate value of  $R_1$  &  $C_F$ .

so that  $R_1 C_1 = R_F C_F$ .

→ Applications :-

- waveshaping CKTS to detect high freq<sup>n</sup> components in IIP signals
- AS a rate of change detector in FM modulators.

→ waveforms:

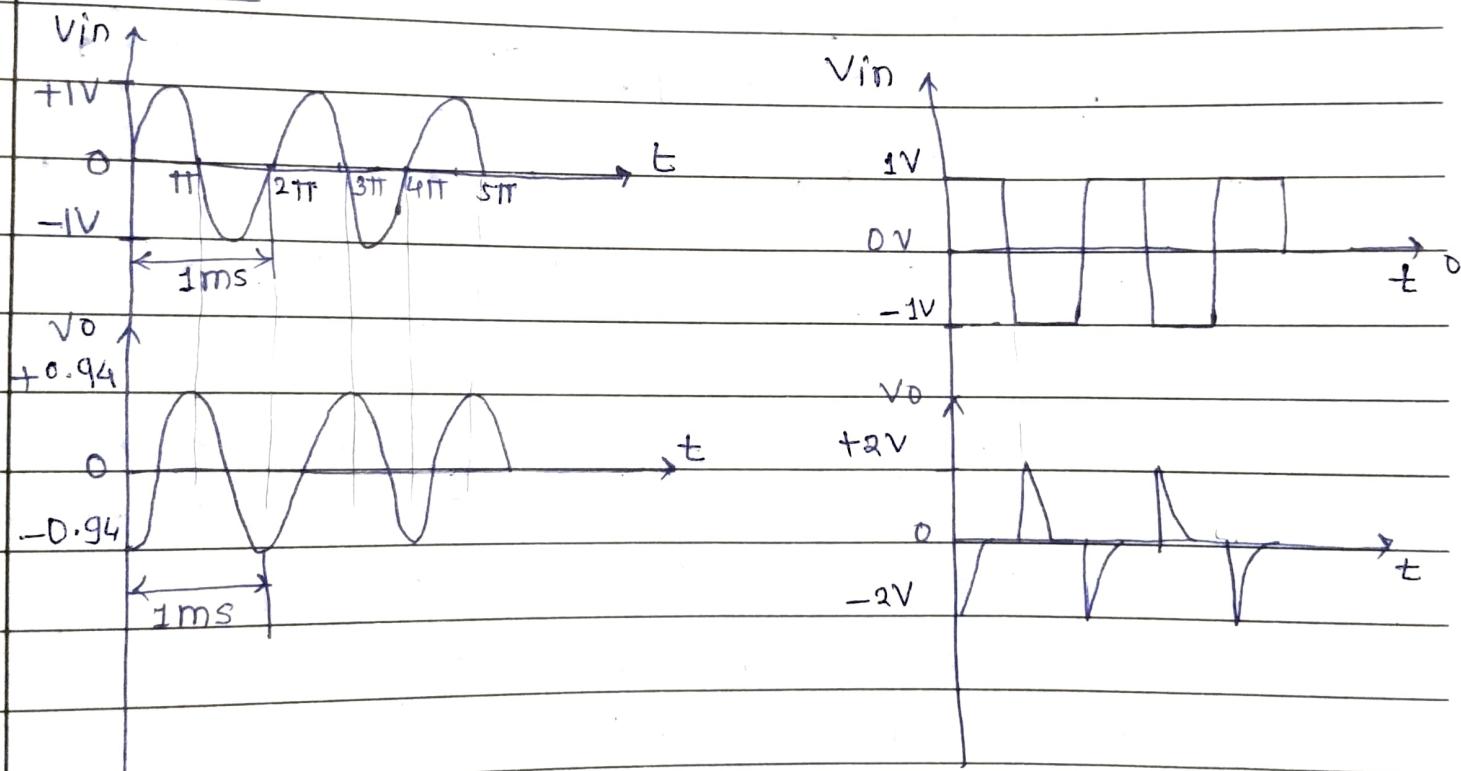

- gain of ckt ↑ with ↑ in IIP freq<sup>n</sup>. at rate 20dB/decade.


↳  $X_{C1}$  (IIP impedance) ↓ when IIP freq<sup>n</sup> ↑.

- ckt becomes very susceptible to noise.

when amplified this noise overrides the differentiated o/p.

Examples based on Integrator & differentiator:

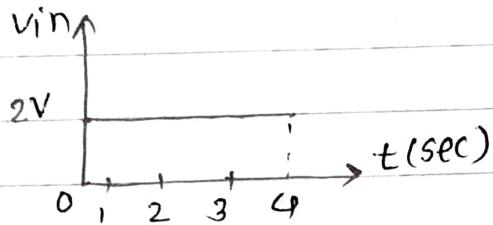
- 1). In the basic integrator ckt. if  $R_1 C_F = 1 \text{ sec}$ . &  $\tau_{IP}$   $v_{in}$  is a step IIP (DC vrg) as shown below. Determine the o/p vrg.  $v_o$  & sketch it. Assume that op-amp is initially nulled. ( $v_{out} = 0$ ) .



$$t = 4$$

$$v_o = - \int_0^4 2 dt$$
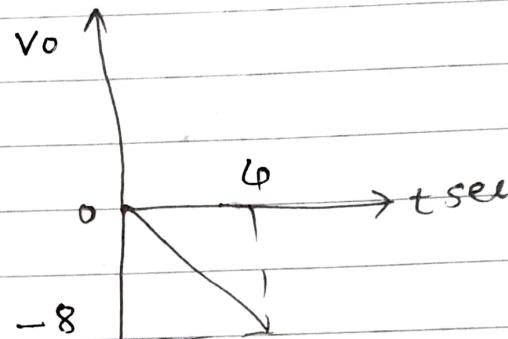
$$= - \left[ \int_0^0 2 dt + \int_0^1 2 dt + \int_0^2 2 dt + \int_0^3 2 dt + \int_0^4 2 dt \right] = -8 \text{ V}$$



- 2) Design a differentiator to differentiate an IIP signal that varies in freqn from 10Hz to about 1KHz.

$\rightarrow$   $f_a = 1 \text{ KHz}$  — max IIP freqn.

$$= \frac{1}{2\pi R_F C_1}$$

Let  $C_1 = 0.1 \mu\text{F}$  then

$$R_F = 1.59 \text{ k}\Omega \cong 1.5 \text{ k}\Omega \text{ -- std. value.}$$

$$\Rightarrow f_b = 20 \text{ KHz} \quad (\because f_b = 20f_a) \quad R_1 = 79.5 \Omega$$

$$(R_1 C_1 = R_1 C_F) \quad \text{Let } R_1 = 82 \Omega \quad \because C_F = 0.0055 \mu\text{F}$$

$$R_{out} = R_F$$

## Introduction

An electronic filter ~~is~~ in general, is frequency selective circuit that allows a specified range of frequencies to pass through & blocks or attenuates signals of frequencies outside this band.

A filter circuit has at least one pass band so that the signals can easily pass to the output. Similarly, it must have at least one attenuation band so that the signals can be blocked or attenuated to the output.

### → Necessity of filter circuits

Many times in electronic systems, the desired signal contains some unwanted signals called noise which must be kept away in order to get correct information. Also, sometimes it is necessary that the signals of certain frequencies should pass at the output & remaining signals should be attenuated. So there is necessity to filter circuits to pass certain range of frequencies & to attenuate other unwanted frequencies.

### → Classification of filters

#### → Analog or Digital filter

The analog filters are designed to process the analog i/p signals whereas the o/p of filtered is analog signal.

[freq i.e. → frequencies]

The digital filters work entirely in digital domain. They use the digital data as the input signal.

## → Passive & active filter


Passive filter are using only passive components such as resistors, capacitors & inductors. They do not use active device such as FET or transistors or OPAMP. Also this filter have low efficiency & their frequency response characteristics are not sharp.

Active filters use active devices such as an OPAMP or transistors along with the passive components. This filter have more sharp frequency response characteristics & have many advantages.

## → Audio frequency or Radiofrequency filters.

R-C filters can operate only in audio freq. range whereas L-C filters or crystal filters are used in radio frequency range.

### Filters

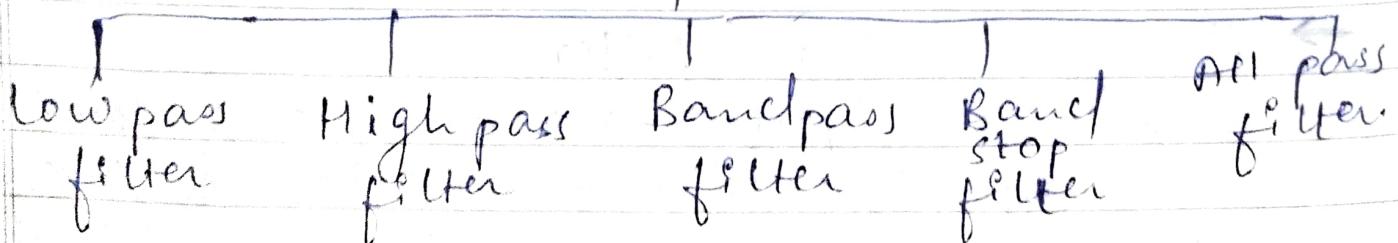

## Merits & Demerits of active filters over passive filters

### Merits

i) Flexibility in gain & frequency adjustment.

In passive filter  $\text{IIP}_3$  signal is attenuated while passing passing through filter but in active filter as an OPAMP can provide a gain, the  $\text{IIP}_3$  signal is not attenuated. In addition, the active filter is easy to tune,  $\therefore$  easy freq. adjustment is possible.

ii) No loading Problem

The OPAMP has high  $\text{IIP}_3$  resistance & low output resistance  $\therefore$  active filter using OPAMP don't load the  $\text{IIP}_3$  source or load.

iii) low cost

Due to easy availability of variety of cheaper OP-AMPS & due to absence of inductors in the active filters, the active filters are more economical than the passive filters.

iv) No Insertion loss

Active filters do not exhibit any insertion loss.

v) Passband gain

Active filter can be designed to provide some passband gain. In passive filter not possible.

vi) Interstage isolation & control of inductor

Active filter allows for interstage isolation ~~and~~ for control of  $\text{IIP}_3$  &  $\text{OIP}_3$  resistance.

### vii) Small component size.

Component required for active filters are of smaller size as compared to those used for passive filter.

### viii) Use of inductors can be avoided


It is possible to avoid the use of inductor in the complex active filters, this reduces the size of filters to great extent.

## → Demerits

- i) Active filters require dc power supply for their operation.
- ii) Active filters are limited in their frequency range because an OPAMP has a finite gain bandwidth product.
- iii) Active filter can not handle large amounts of power, while passive filter can handle hundreds of watts.

## Concept of Passive & Active filter.

### → Passive RC low pass filter.

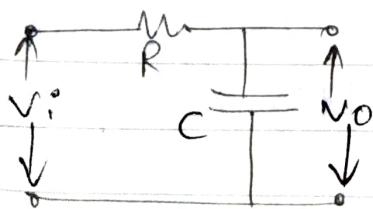


It is basically an RC integrator circuit. Here we have used only passive components.

OP is taken across capacitor.


$$V_o = \frac{X_C}{\sqrt{R^2 + X_C^2}} V_i$$

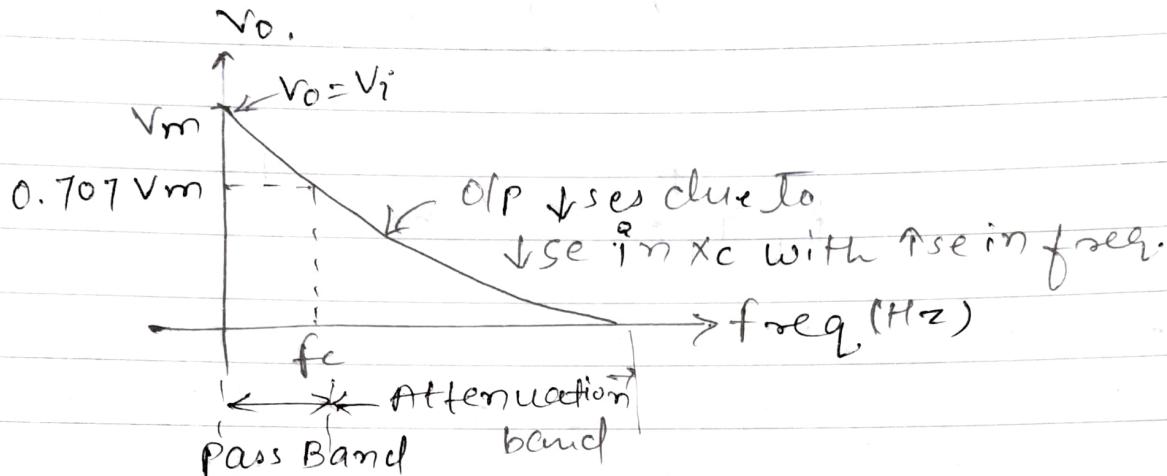- At  $f=0$ , the reactance  $X_C = \frac{1}{2\pi f C} = \infty$ .  $\therefore V_o = V_i$
- But if freq. rises, the  $X_C$  i.e. capacitor reactance  $X_C$  will decrease. Hence the o/p voltage will  $\downarrow$ se because as o/p is,  $\frac{V_o}{\sqrt{R^2 + X_C^2}} \propto V_i$



- This circuit is called as low pass filter since it passes the low freq. signal.
- The cutoff freq.  $f_c$  corresponds to an o/p v/g of ~~0.707~~  $0.707 V_m$  or  $3\text{dB}$  below maximum. This freq. will separates the pass band & stop band of the filter.

### → RC passive high pass filter

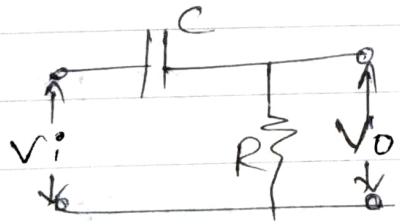


This circuit diagram shows that this is an RC passive high pass filter.

Here o/p is now being taken across the  $R$  rather than capacitor.

$$\text{o/p voltage is given by } V_o = \frac{R}{R - jX_C} V_i$$

$$\therefore V_o = \frac{R}{\sqrt{R^2 + X_C^2}} V_i$$

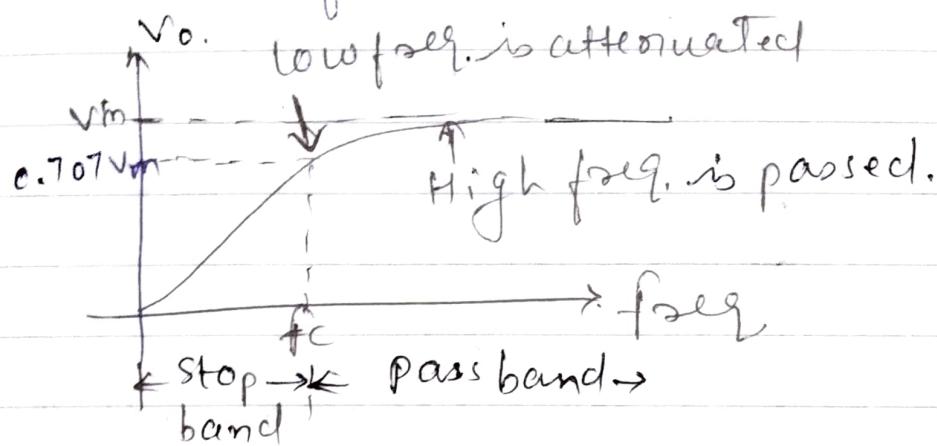→ At  $f=0$ ,  $X_C = \infty$ , hence  $V_o = 0$ . But freq. of ilp. signal rises,  $X_C$  will decrease & o/p voltage will rise as shown in fig.



- This circuit attenuates low freq. & passes High freq. signal.  $\therefore$  called as high pass filter.
- But at  $\text{high freqies}$  the reactance of  $C$  is almost  $0$  & o/p voltage is equal to ilp vlg.

### But Disadvantages of Passive filter.

- These circuit cannot provide gain.
- There is no isolation between ilp & o/p.
- If inductors are used then circuit becomes bulky.

### 2. Advantages of Passive filter

- They do not need additional dc power supplies for operation
- No limitation on the freq. range.
- They can handle large voltages, currents & powers.



## Concept of Active filter

It uses passive as well as active device such as OPAMP.

If we are using OPAMP then the value of  $R_{eff}$  decides value of passband gain.

→ Advantages of Active filter.

→ Gain is provided.

→ Frequency response is more sharp.

→ Comparison between active & passive filter.


Parameter	Passive filter	Active filter
Component used	$R \& C$ or $L \& C$	$R_C$ or $L_C$ & OPAMP
Active component	Not used	OPAMP
Gain	Less than 1	Greater than 1 - present.
Isolation bet' i/p & o/p	Absent	
Freq. Response.	Not sharp	sharp.

→ Cut off frequency → It is the frequency which separates passband & stopband.

→ Passband → It is the band or range of frequency which are allowed to pass through to the o/p by filter without any attenuation.

→ Stopband → It is the band or range of freq. which are not allowed to pass through to the o/p by the filter.


## → Roll off Rate

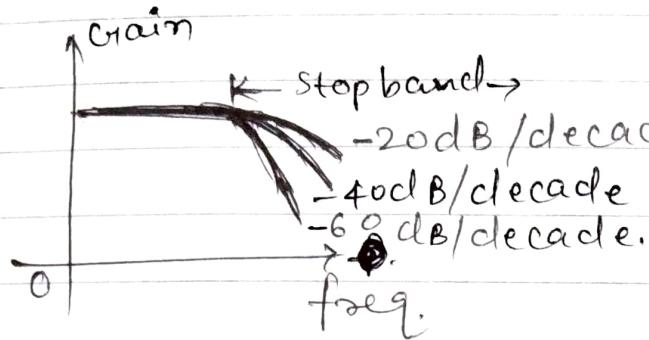

The rate at which it falls off is called as the roll off rate.

- The roll off rate is decided by the order of the filter. If we ↑se the filter order by 1, then roll off rate is ↑sed by 20dB/decade.
- If we ↑se the order of the filter then circuit become too much complex but response becomes more & more sharp.
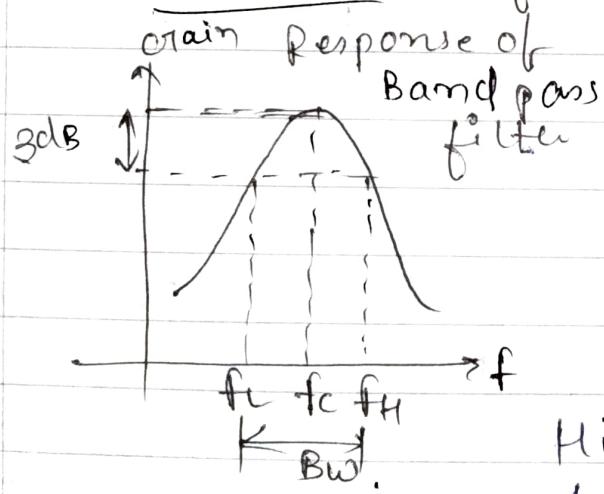
## → $\alpha$ (quality factor) & Bandwidth of filter




Relation between center freq.,  $\alpha$  & bandwidth is as follows.  $\alpha = \frac{f_C}{BW}$

Higher the value of ' $\alpha$ ' sharper the freq. response.


- Bandwidth is defined as the difference between two cut off freq. i.e.  $f_H$  &  $f_L$   
 $\therefore BW = f_H - f_L$

# Ideal & Actual characteristics of filter.

## → Low pass filter

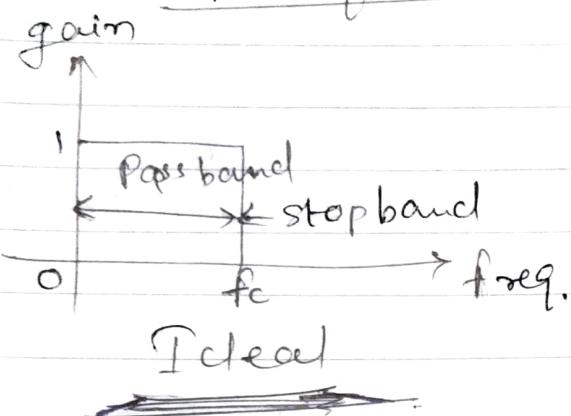

Ideal

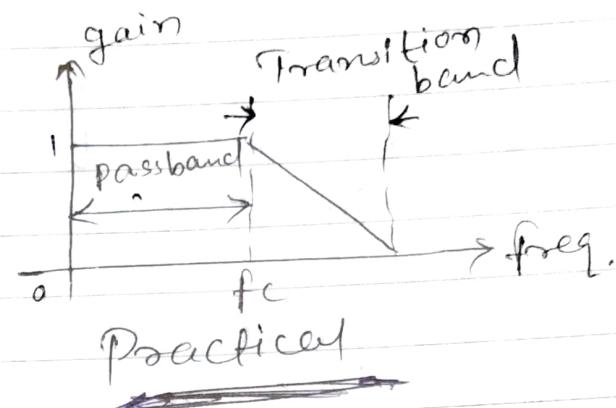


Practical


→ In ideal chara. gain is const. from 0 Hz to High cut off freq. & these frequencies are known as passband frequencies & beyond this freq. are known as stopband freq. At  $f=f_c$  gain makes sudden transition to zero.  $\therefore$  freq. beyond  $f_c$  are completely attenuated.

→ In practical chara. filter gain does not change suddenly at  $f=f_c$ . Instead as  $f$  rises, gain reduces gradually. But by using special design techniques, precision component values & high speed OPAMPS it is possible to design practical filter having chara. very close to ideal chara.

## → High Pass filter

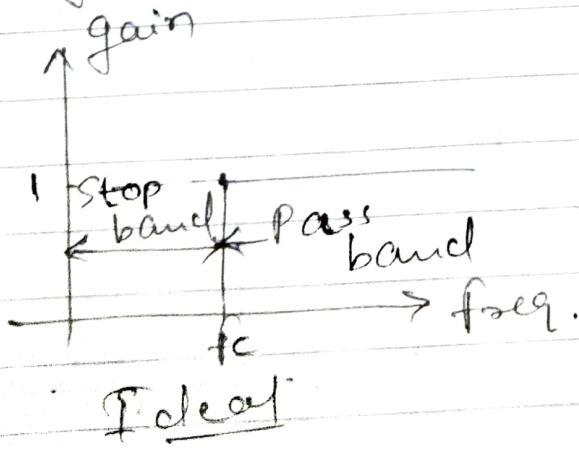

Ideal


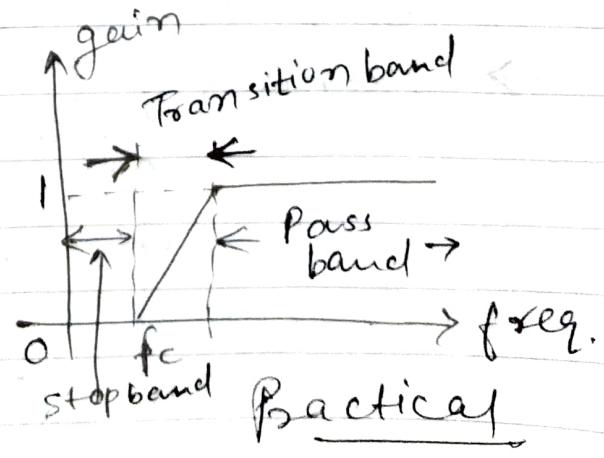


Practical

→ In ideal chara, stop band extends from  $f=0$  to  $f=f_c$ , where  $f_c$  is the cutoff freq., The 'passband' will be for all freqs above ' $f_c$ '. The gain makes sudden transition from 0 to 1 at  $f=f_c$ .

→ In practical high pass filter gain changes gradually, ∵ it has finite transition band.

→ Band pass filter

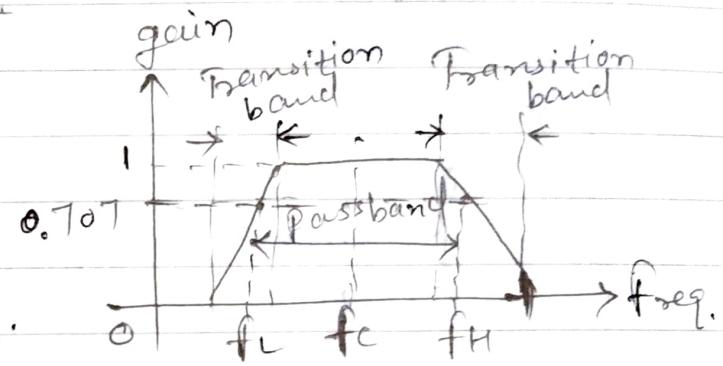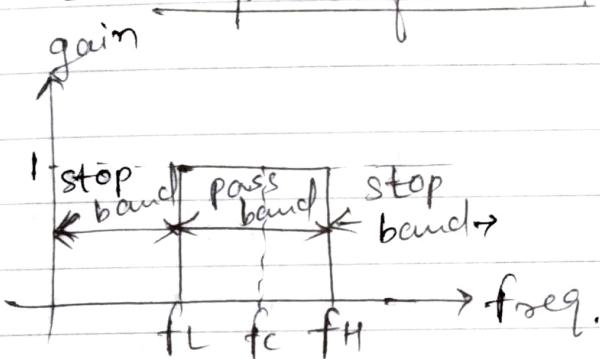



Ideal

Practical

→ In ideal, passband extends between the two cut off frequencies  $f_L$  &  $f_H$  with  $f_H > f_L$ . The freqs. outside this passband lie in the stopband or attenuation band. The gain of an ideal filter will make sudden transition from 0 to 1 at  $f=f_L$  & from 1 to 0 at  $f=f_H$ .


→ In practical, gain does not change suddenly at  $f=f_L$  &  $f=f_H$  instead it changes gradually.

→ Bandstop filter

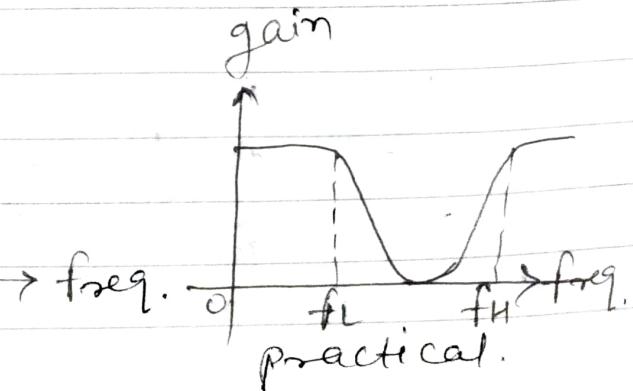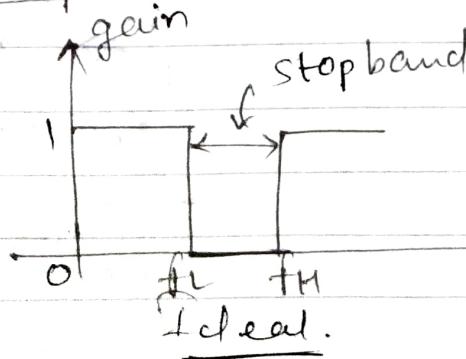



- It is opposite to Bandpass filter i.e. complementary to the bandpass filter.
- It blocks out the freq. within stop band.
- In ideal case it will suddenly take transition but practically it will not.

→ All pass filter

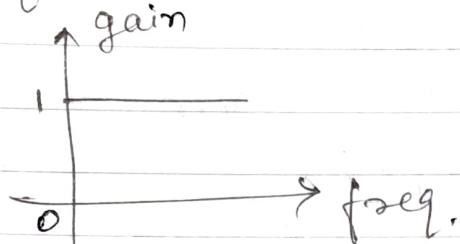

This filter passes all the freq. ∴ it is known as all pass filter.

First order Low pass filter

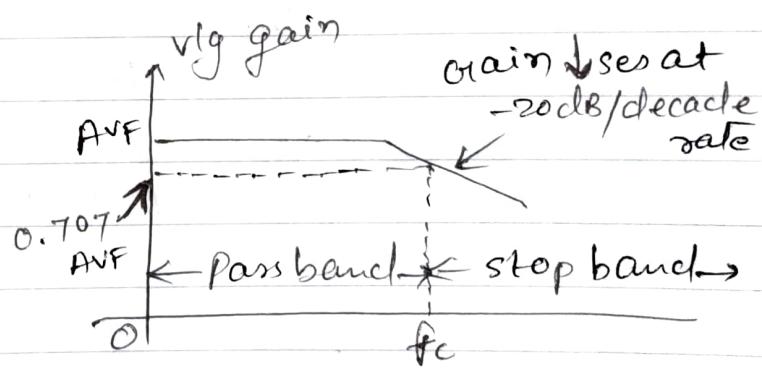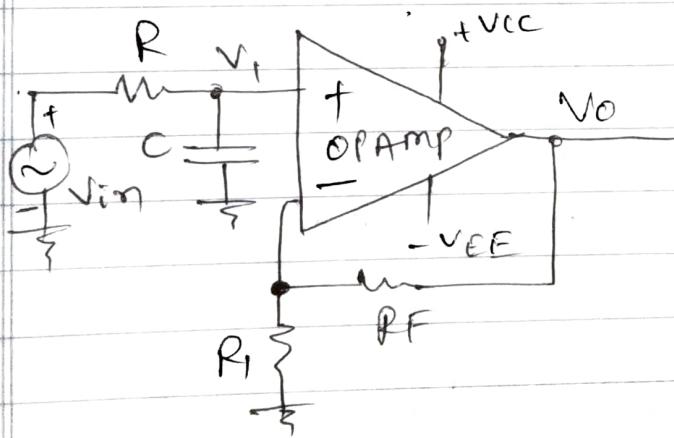

- First order low-pass filter which is also known as one pole lowpass filter.
- This circuit uses R-C network for filtering & the OPAMP is used in non-inverting configuration.
- $R$  &  $C$  values decides the cut off frequency of filter whereas  $R_F$  &  $R_1$  will decide its gain.

As the opamp is used in non-inverting config.

$$AVF = 1 + RF/R_1$$

→ We want to obtain the expression for  $V_i$ . It is nothing but voltage across 'C'. The R & 'C' forms a voltage divider across i/p vlg.  $V_{in}$ .

$$\therefore V_i = \frac{-jX_C}{R-jX_C} \cdot V_{in}$$

$$\text{But } X_C = 1/2\pi f_C$$

$$\therefore V_i = \frac{-j(1/2\pi f_C)}{R-j(1/2\pi f_C)} V_{in} = \frac{-jV_{in}}{2\pi fRC - j}$$

Dividing numerator & denominator by  $-j$ ,

$$\therefore V_i = \frac{V_{in}}{\frac{1-2\pi fRC}{j}}$$

$$\text{But } Y_j = -j$$

$$V_i = \frac{V_{in}}{1+j2\pi fRC}$$

$$\text{Now, } V_o = AVF \cdot V_i$$

$$\therefore V_o = \left(1 + \frac{RF}{R_1}\right) \frac{V_{in}}{1+j2\pi fRC}$$

$$\therefore \frac{V_o}{V_{in}} = \frac{AVF}{1+j2\pi fRC}$$

$$\text{Now put } 2\pi RC = Y_{fc}$$

$$\& f_C = \text{cut off freq.} = 1/2\pi RC$$

$$\therefore \frac{V_o}{V_{in}} = \frac{AVF}{1+j(f/f_C)}$$

Now taking mod on both sides,

$$\left| \frac{V_o}{V_{in}} \right| \cancel{AVF} = \frac{AVF}{\sqrt{1+(f/f_C)^2}}$$

Now there are three cases,

I) At very low frequencies  $f < f_c$ ,

$$\left| \frac{V_o}{V_{in}} \right| \approx AVF \text{ ie. maximum gain.}$$

II) At  $f = f_c$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{AVF}{\sqrt{1+1^2}} = \frac{AVF}{\sqrt{2}} = 0.707 AVF$$

At  $f = f_c$  the gain of the filter reduces to 3dB since dB value of 0.707 is -3dB.

III) At very High frequency i.e.  $f > f_c$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{AVF}{\sqrt{(f/f_c)^2}} = \frac{AVF}{f/f_c}$$

& As the value of  $f/f_c$  is greater than 1

$$\therefore \left| \frac{V_o}{V_{in}} \right| < AVF$$

i.e. the filter gain will keep decreasing with rise in frequency. This rise takes place at the rate of -20dB/decade.

It means if frequency is increased 10 times then gain is decreased 20dB which is shown by 've' sign.

## → Designing Steps

→ Choose the ~~at~~ cut off freq.  $f_c$ ,

→ Select a value of 'C' usually between 0.001 to 0.1μF.

→ Calculate R using  $R = 1/2\pi f_c C$

→ Select the value of  $R_1$  &  $R_F$  depending on desired value of AVF i.e.  $AVF = 1 + R_F/R_1$

Eg Design first order low pass filter for  
pass band gain = 2  
cut off freq  $f_c = 10\text{kHz}$

$$\rightarrow \text{gain is, } \text{AVF} = 1 + \frac{R_F}{R_1}$$

$$\text{But } \text{AVF} = 2$$

$$\therefore \frac{R_F}{R_1} = 1$$

$$\text{let us choose } R_F = 10\text{k}\Omega$$

$$\therefore R_F = R_1 = 10\text{k}\Omega$$

$$\text{Now choose } C = 0.001\mu\text{F}$$

$$\text{But } f_c = \frac{1}{2\pi R C}$$

$$\therefore R = \frac{1}{2\pi f_c C}$$



$$\therefore R = \frac{1}{2\pi \times 10 \times 10^3 \times 0.001 \times 10^{-6}}$$

$$\therefore R = 15.9\text{k}\Omega$$

(\*)
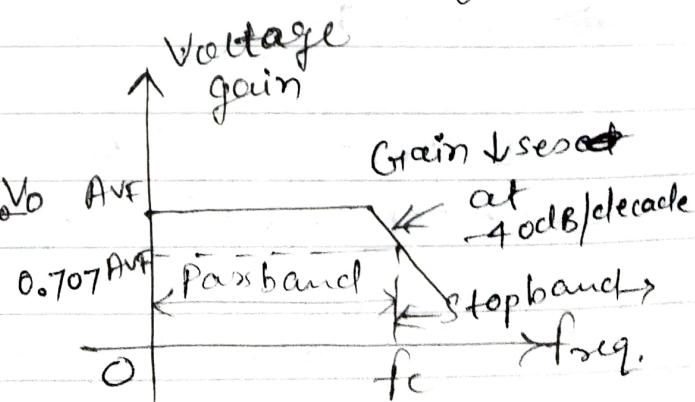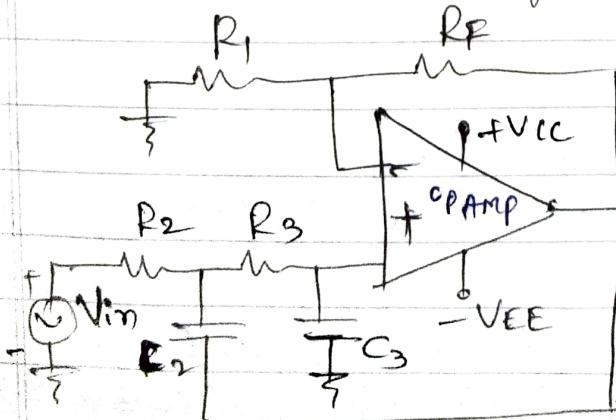
### Second order Low pass filter

The second order low pass filter can be obtained simply by inserting an additional RC n/w into first order low pass filter.



The response shows that in stopband  $20\text{dB/ octave}$  is  $-40\text{dB/decade}$ .

→ The resistors  $R_F$  &  $R_1$  will decide the gain of the filter.

→ Cut off freq.  $f_c$  is determined by  $R_2, C_2, R_3, C_3$ . as follows,

$$f_c = \frac{1}{2\pi \sqrt{R_2 R_3 C_2 C_3}}$$

The voltage gain magnitude is given by,

$$\left| \frac{V_o}{V_{in}} \right| = \frac{AVF}{\sqrt{1 + (f/f_c)^4}}$$

where  $AVF = 1 + \frac{R_F}{R_1}$

$f$  = Freq. of input signal.

$f_c$  = Cut off frequency.

### → Design Procedure

→ Choose the cutoff freq.  $f_c$ .

→ Assume  $R_2 = R_3 = R$  &  $C_2 = C_3 = C$  & then choose 'C' in the range of  $0.001\text{ mF}$  to  $0.1\text{ mF}$ .

→ Calculate the value of  $R$  as,

$$R = \frac{1}{2\pi f_c C}$$

→ Now depending upon gain choose the value of  $R_1$  &  $R_F$ . Select gain  $\geq 1.586 \therefore R_F = 0.586 R_1$

→ Case I At  $f < f_c$ ,  $\left| \frac{V_o}{V_{in}} \right| \approx AVF$  ie max gain

Case II At  $f = f_c$ ,  $\left| \frac{V_o}{V_{in}} \right| = \frac{AVF}{\sqrt{2}} = 0.707 AVF$

Case III At  $f > f_c$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{AVF}{\sqrt{(f/f_c)^4 - 1}} \therefore \left| \frac{V_o}{V_{in}} \right| < AVF$$

filter:

Derive expression for second-order LPF (Butterworth filter).

$$f_H = \frac{1}{2\pi\sqrt{R_2 R_3 C_2 C_3}}$$

f: For analysis, we will use Laplace transform.  
All components & ckt parameters are expressed in s domain  
where  $s = j\omega$ .

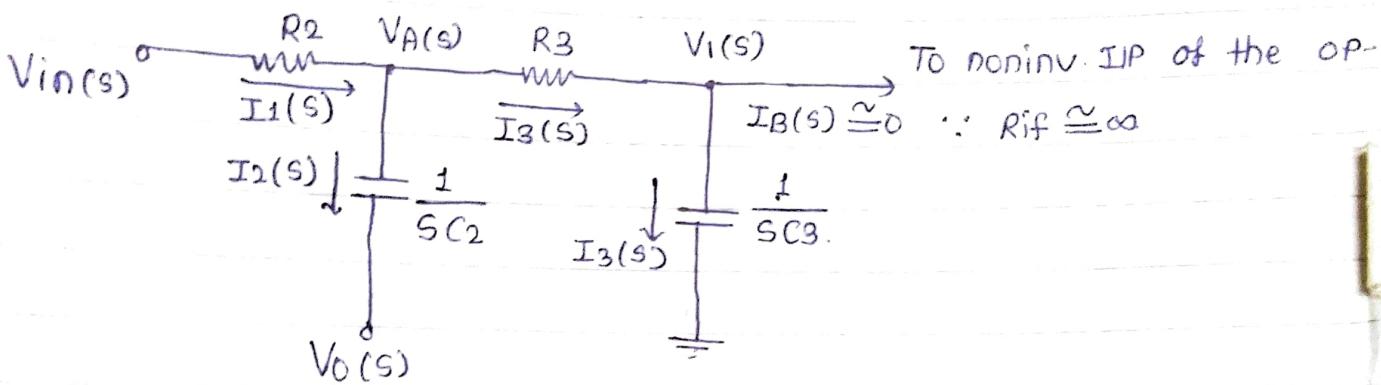


Fig: transformed into S domain:

By Kirchhoff's current law at node VA(s),

$$I_1 = I_2 + I_3.$$

or  $\frac{V_{in} - V_A}{R_2} = \frac{V_A - V_O}{1/SC_2} + \frac{V_A - V_I}{R_3}$  -- ①

But  $V_3 = \frac{1/SC_3}{R_3 + (1/SC_3)} V_A$   $\because R_{if} \approx \infty, I_B \approx 0A.$   
 $= \frac{V_A}{R_3 C_3 S + 1}.$

or  $V_A = (R_3 C_3 S + 1) \cdot V_I.$

Substitute value of VA in eqn ①.

$$\therefore \frac{V_{in}}{R_2} - \left[ \frac{1/SC_3}{R_3 + (1/SC_3)} \frac{V_A}{R_2} \right] =$$

$$\frac{V_{in}}{R_2} - (R_3 C_3 S + 1) \cdot V_I = \frac{(R_3 C_3 S + 1) \cdot V_I - V_O}{1/SC_2} + \frac{(R_3 C_3 S + 1) \cdot V_I - V_I}{R_3}$$

$$\therefore V_I = \frac{R_3 \cdot V_{in} + (R_3 R_2 C_2 S) \cdot V_O}{(R_3 C_3 S + 1)(R_2 + R_3 + R_3 R_2 C_2 S) - R_2}$$

But  $V_o = AF \cdot V_i$

where  $AF = 1 + \frac{RF}{R_1}$  --- Non-INV config.

$$\therefore V_o = \frac{(AF) \cdot [ (R_3)(V_{in}) + (R_3 R_2 C_2 s)(V_o) ]}{(R_3 C_3 s + 1) (R_2 + R_3 + R_3 R_2 C_2 s) - R_2}$$

Re-arrange to get  $\frac{V_o}{V_{in}}$

$$\frac{V_o}{V_{in}} = \frac{AF}{s^2 + \frac{(R_3 C_3 + R_2 C_2 + R_2 C_2 - AFR_2 C_2)s + \frac{R_2}{R_2 R_3 C_2 C_3} 1}{R_2 R_3 C_2 C_3}}$$

For freq<sup>n</sup>s above  $f_H$ , gain of 2<sup>nd</sup> order LPF rolls off at the rate of  $-40\text{dB/dec}$ .

i.e. The denominator quadratic in the gain ( $V_o/V_{in}$ ) eq<sup>n</sup> must have two real & equal roots.

This means that,


$$\omega^2 H = \frac{1}{R_2 R_3 C_2 C_3}$$

$$\text{Or } \omega H = \frac{1}{\sqrt{R_2 R_3 C_2 C_3}}$$

$$\therefore f_H = \frac{1}{2\pi \sqrt{R_2 R_3 C_2 C_3}}$$

★

# First Order High pass filter

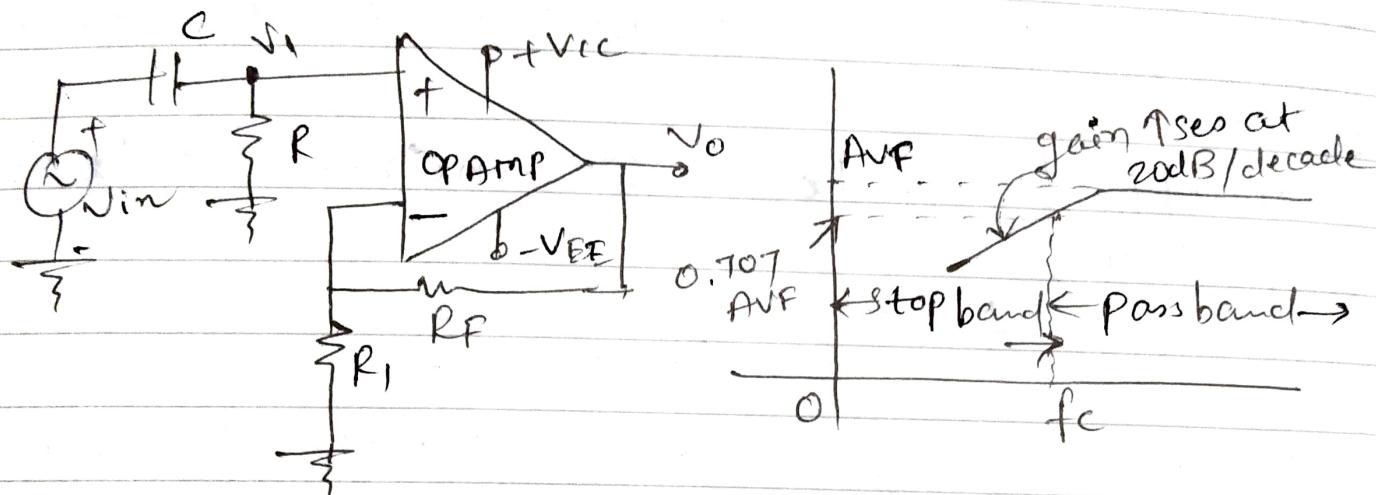

The RC component decide the cut-off freq. of high pass filter & \$R\_F\$ and \$R\_1\$ decides the gain.

$$AVF = \left[ 1 + \frac{R_F}{R_1} \right]$$

→ Determining the \$V\_i\$ using the concept of voltage divider. \$V\_i\$ is nothing but voltage across \$R\$.

$$\therefore V_i = \frac{R}{R - jX_C} V_{in}$$

$$\text{But } X_C = 1/2\pi f C$$

$$\therefore V_i = \frac{R}{R - j/2\pi f C} V_{in} = \frac{V_{in}}{1 - j/2\pi f C R}$$

Substitute  $2\pi R C = 1/f_c$   
 where  $f_c = \text{cutoff freq.}$   
 $\therefore f_c = \frac{1}{2\pi R C}$

$$\therefore V_1 = \frac{V_{in}}{1 - j(f_c/f)}$$

$$\text{Now, } V_o = \text{AVF} \cdot V_1$$

$$\therefore \frac{V_o}{V_{in}} = \left( \frac{\text{AVF}}{1 - j(f_c/f)} \right) \cdot V_{in}$$

$$\therefore \frac{V_o}{V_{in}} = \frac{\text{AVF}}{1 - j(f_c/f)}$$

$$\therefore \left| \frac{V_o}{V_{in}} \right| = \frac{\text{AVF}}{\sqrt{1 + (f_c/f)^2}}$$

Case I At low freq. ie.  $f < f_c$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{\text{AVF}}{\sqrt{(f_c/f)^2}} = \frac{\text{AVF}}{f_c/f}$$

Since  $f_c/f > 1$

$$\left| \frac{V_o}{V_{in}} \right| < \text{AVF}$$

Case II At  $f = f_c$  ie. cutoff freq = i/p freq.

$$\left| \frac{V_o}{V_{in}} \right| = \frac{\text{AVF}}{\sqrt{2}} = 0.707 \text{ AVF}$$

This filter gain is down by 3dB as 0.707 corresponds to -3dB.

case III At  $f > f_c$

$$\left| \frac{V_o}{V_{in}} \right| \approx \text{AVF} \text{ ie. constant}$$

Thus the gain will remain constant in the pass band.

### → Design Procedure


- choose the value of cut off freq  $f_c$ .
- select the value of 'C' bet  $0.001\mu F$  &  $0.1\mu F$
- calculate  $R$  using,

$$R = \frac{1}{2\pi f_c C}$$

- Select the values of  $R_1$  &  $R_F$ , depending on the desired value of pass band gain.

$$\text{AVF} = 1 + \frac{R_F}{R_1}$$

### Second order High Pass filter

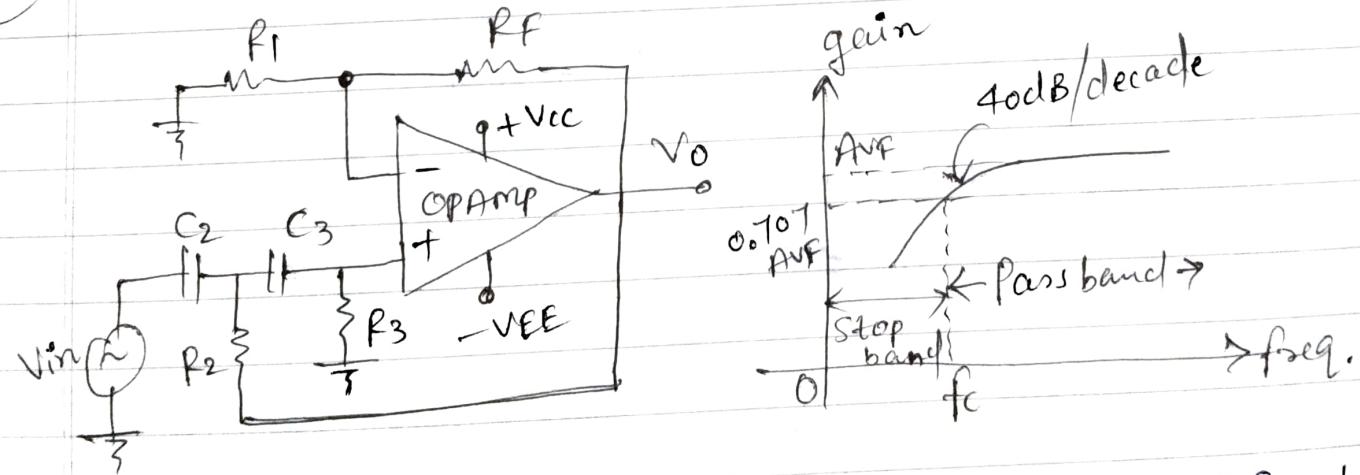

It is obtained by simply inserting  $CR$  in  $\omega$  into first order high pass filter.

The  $R_1$  &  $R_F$  will decide the gain of the high pass filter.

Cut off freq.  $f_c$  is determined by  $R_2, R_3, C_2 \& C_3$ .

$$f_c = \frac{1}{2\pi \sqrt{R_2 R_3 C_2 C_3}}$$

gain,

$$\left| \frac{V_o}{V_{in}} \right| = \frac{AVF}{\sqrt{1 + (f_c/f)^4}}$$

where  $AVF = 1 + \frac{R_f}{R_1}$  = gain of filter.

$f$  = i/p signal frequency

$f_c$  = low cut off freq.

From the response it is clear that gain rises at a rate of 40dB/decade. which is twice the rate of first order & because of this the frequency response becomes sharper.

Case I when  $f < f_c$

$$\therefore \left| \frac{V_o}{V_{in}} \right| = \frac{AVF}{\sqrt{(f_c/f)^4}}$$

$$\therefore \left| \frac{V_o}{V_{in}} \right| = \frac{AVF}{(f_c/f)^2}$$

Since ~~but~~  $f_c > 1$

$$\therefore \left| \frac{V_o}{V_{in}} \right| < AVF$$

Case II when  $f = f_c$ ,

$$\left| \frac{V_o}{V_{in}} \right| = \frac{\cancel{AVF}}{\cancel{1 + f_c^4}} \frac{AVF}{\sqrt{1 + (f_c/f)^4}}$$

$$\therefore \left| \frac{V_o}{V_{in}} \right| = \frac{AVF}{\sqrt{2}} = 0.707 AVF$$

Case III At  $f > f_c$

$$\left| \frac{V_o}{V_{in}} \right| \approx AVF$$

## → Designing Steps

→ choose cutoff freq.  $f_c$ .

→ Assume  $R_2 = R_3 = R$  &  $C_2 = C_3 = C$ .

Then choose value of  $C$  between 0.001uf & 0.1uf.

$$R = \frac{1}{2\pi f_c C}$$

→ Calculate the value of  $R$ .

→ Calculate the value of  $R_i$  &  $R_F$  depending upon the value of gain.

i.e.  $A_{VF} = \frac{1 + R_F}{R_i}$ , Select gain = 1.586.

$$\therefore R_F = 0.586 R_i$$

(A)

## Band Pass filter

Bandpass filter has passband between two cutoff freqsies  $f_H$  &  $f_L$ , such that  $f_H > f_L$ . Any ip freq. outside this passband will be attenuated.


→ There are two types of bandpass filter.

i) wide band pass filter.  $Q < 10$

ii) narrow band pass filter.  $Q > 10$




## Wide bandpass filter

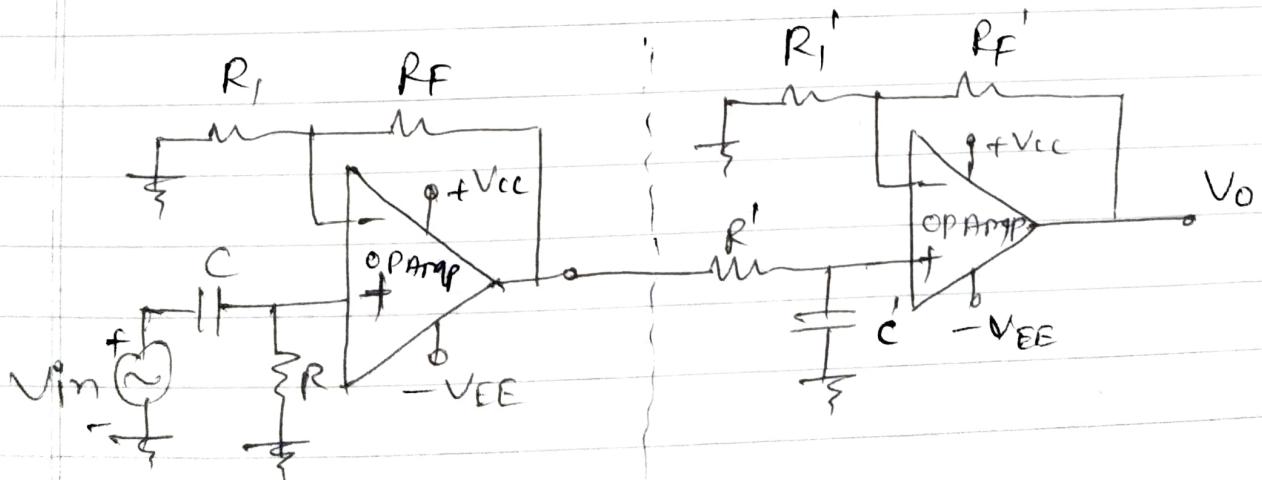

First order High-pass → First order low-pass section.

~~filter~~ section

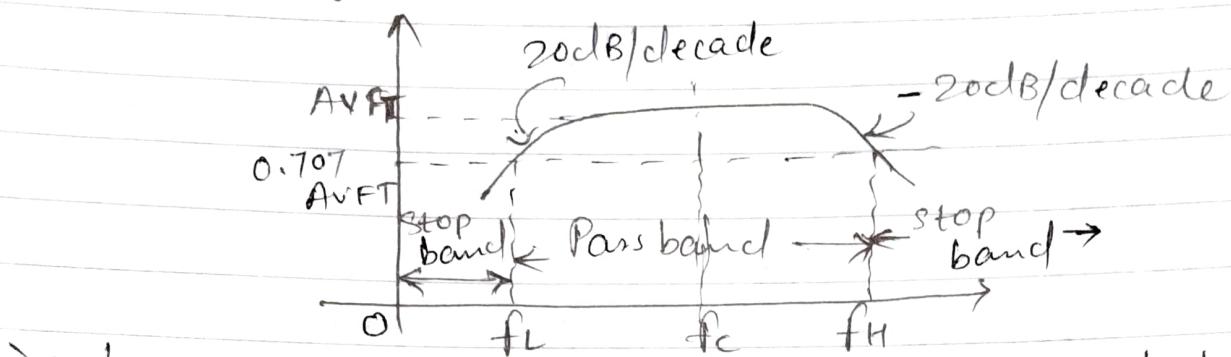It is formed by cascading a 1<sup>st</sup> order high-pass filter & first order low pass filter.



' $f_H$ ' is cut off freq. of low pass filter while ' $f_L$ ' is cut off freq. for high pass filter.

Total pass band gain  $AVFT = AVF_1 \times AVF_2$

$AVF_1$  = Gain of high pass filter

$AVF_2$  = Gain of low pass filter.

If we want sharper frequency response then we can cascade second order high pass & low pass filter instead of first order.

$$f_L = \frac{1}{2\pi R C} = \frac{1}{2\pi R C}$$

$$\& f_H = \frac{1}{2\pi R' C} = \frac{1}{2\pi R' C}$$

Center frequency of bandpass filter is,

$$f_c = \sqrt{f_H f_L}$$

$$\omega = \frac{f_c}{f_H - f_L}$$

$$\& \text{the } f_H - f_L = BW.$$

$$\therefore Q = \frac{f_c}{BW}$$

## Designing steps

- From cut off freq of low pass filter ( $f_{L1}$ ), calculate values of  $R'$  &  $C'$ .
- From cut off freq. of high pass filter ( $f_{H1}$ ) calculate values of  $R$  &  $C$ .
- $\text{AVFT} = \text{AVF}_1 \times \text{AVF}_2$   
Assume value of  $\text{AVF}_1$  &  $\text{AVF}_2$ . Then calculate values of  $R_F$ ,  $R_i$ ,  $R'_F$  &  $R_i'$ .

Eg Design wide bandpass filter for  $f_L = 100\text{Hz}$ ,  $f_{H1} = 1\text{KHz}$  & passband gain = 4. Also calculate value of  $\alpha$ .

⇒ Assuming  $C' = 0.01\mu\text{F}$

$$\therefore R' = \frac{1}{2\pi f_{L1} C'} = \frac{1}{2\pi \times 10^3 \times 0.01 \times 10^{-6}} = 15.9 \text{ k}\Omega$$

Gain of low pass filter  $\text{AVF}_2 = 2$

$$\therefore 2 = 1 + \frac{R'_F}{R'_i}$$

$$\therefore R'_F = R'_i$$

choose  $R'_i = 10\text{k}\Omega \therefore R'_F = 10\text{k}\Omega$

Components for low pass filter are,

$$R'_i = 10\text{k}\Omega, R' = 15.9 \text{ k}\Omega$$

$$R'_F = 10\text{k}\Omega, C = 0.01\mu\text{F}$$

Now assume  $C = 0.05\mu\text{F}$ .

$$\therefore R = \frac{1}{2\pi f_{L1} C} = \frac{1}{2\pi \times 100 \times 0.05 \times 10^{-6}}$$

$$\therefore R = 3.1483 \text{ k}\Omega$$

The gain of high pass filter  $\text{AVF}_1 = 2$

$$\therefore 2 = 1 + \frac{R_F}{R_i} \quad \therefore R_F = R_i$$

choose  $R_1 = 10\text{k}\Omega \therefore R_F = 10\text{k}\Omega$

Thus components for high pass filter are,

$$R_1 = 10\text{k}\Omega, R = 31.83\text{k}\Omega$$

$$R_F = 10\text{k}\Omega, C = 0.05\mu\text{F}$$

$$\Omega = \frac{f_c}{f_H - f_L} \quad \text{But } f_c = \sqrt{f_H \cdot f_L}$$

$$\therefore \Omega = \frac{\sqrt{f_H \cdot f_L}}{f_H - f_L} = \frac{\sqrt{1000 \times 100}}{(1000 - 100)} = 0.351$$



## Narrow Bandpass filter

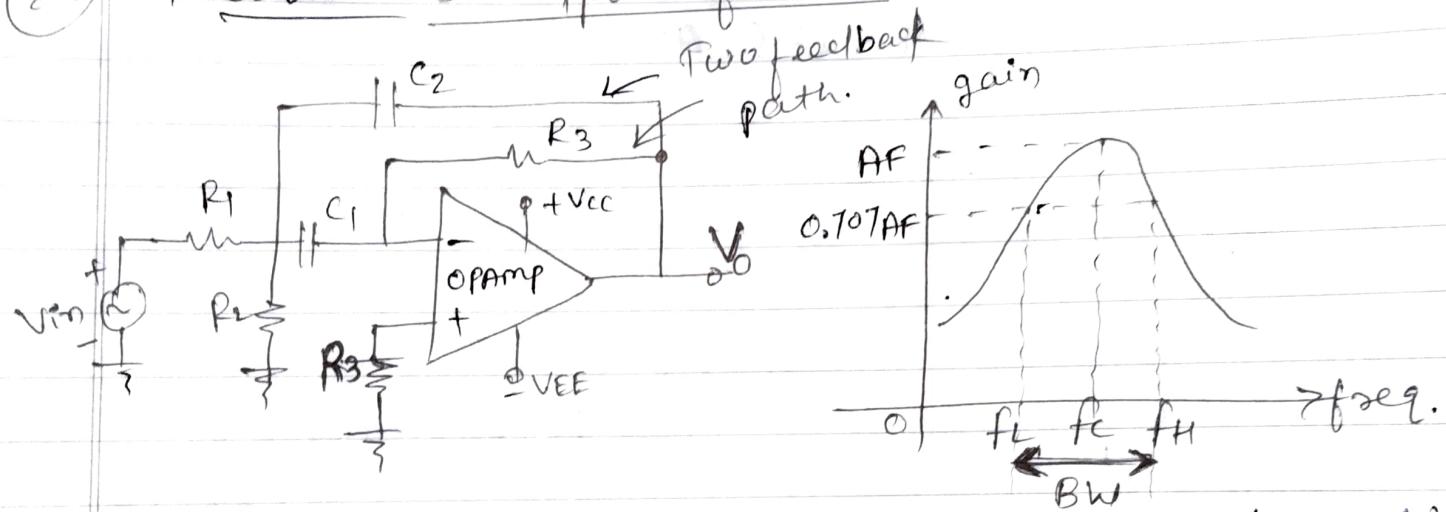


Fig. shows the circuit of narrow bandpass filter.

The main advantage is it uses only one OPAMP.

### → Features

→ It uses one OPAMP.

→ It has multipath feedback

→ OPAMP is used as inverting amp.

### → Meaning of narrow bandpass.

→ It is the bandpass filter with small bandwidth.

&  $BW = f_H - f_L$ .

→ Freq. response of filter is sharper than wide BPF.

→  $\Omega$  is higher than wide BPF.

## → Advantages of Narrow BPF

- i) It uses only one OPAMP.
- ii) We can change center freq.  $f_c$  to a new value without changing gain or bandwidth.

## → Designing steps

$$\rightarrow \text{select } C_1 = C_2 = C$$

$$\rightarrow R_1 = \frac{\alpha}{2\pi f_c C A_F}$$

$$\rightarrow R_2 = \frac{\alpha}{2\pi f_c C (2\alpha^2 - A_F)}$$

$$\rightarrow R_3 = \frac{\alpha}{\pi f_c C}$$

$\rightarrow$  AF is gain at  $f = f_c$  &  $A_F = \frac{R_3}{2R_1}$

& gain AF is  $A_F < 2\alpha^2$

$\rightarrow$  To change center freq 'f<sub>c</sub>' to new value of f<sub>c'</sub> by changing the resistance R<sub>2</sub> to R<sub>2'</sub>

$$R_2' = R_2 \left( \frac{f_c}{f_c'} \right)^2$$



## Band Reject filter (Band Stop filter)

This filter will attenuate (stop) the frequencies in the stopband & pass all the frequencies outside the stopband.

### → Types of Band reject filter


- i) Wide Band reject filters.
- ii) Narrow Band reject filters.



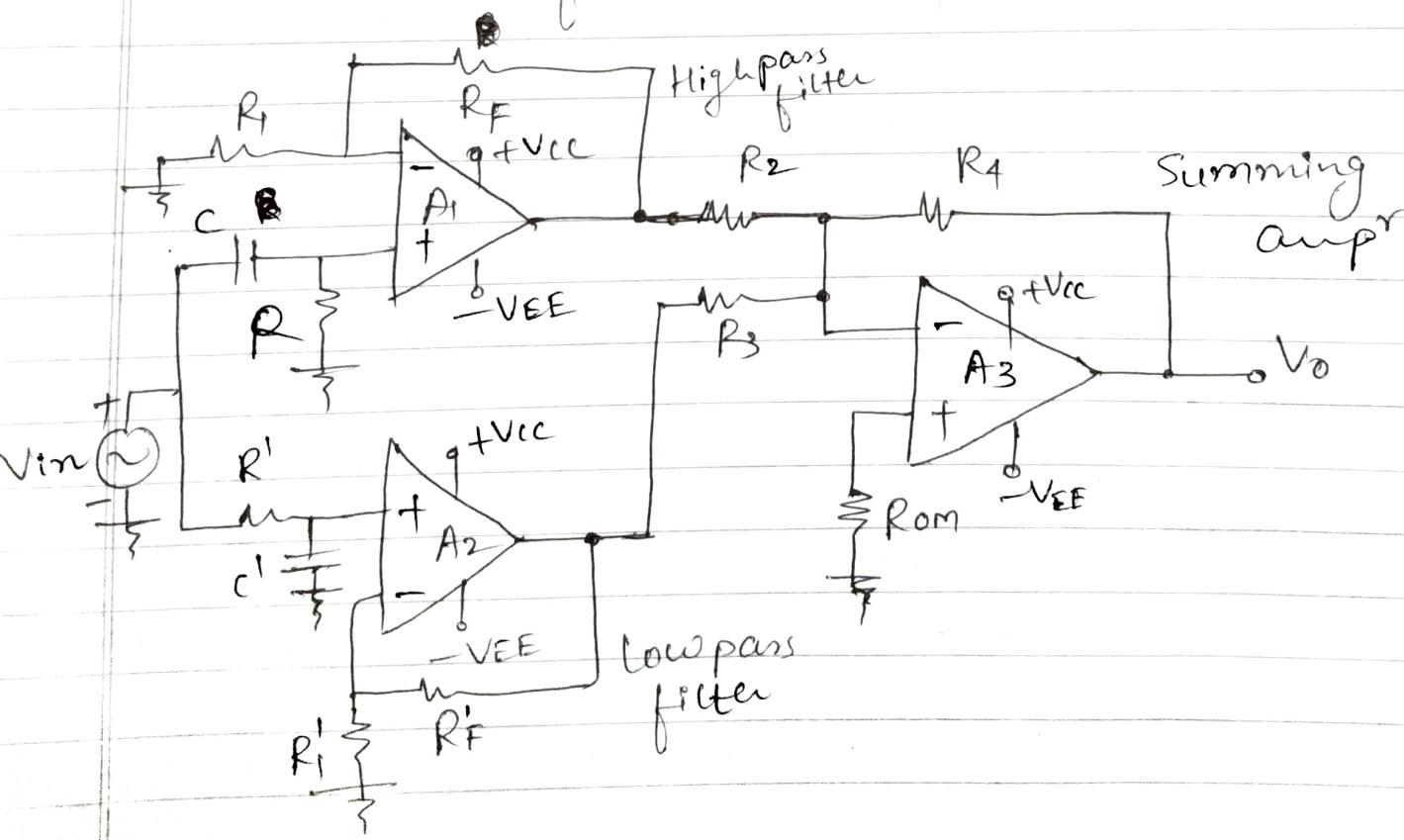
### Wide band reject filter

It consist of low pass filter, high pass filter & summing amp.

To practically obtain the freq. of wide band ~~reject~~ filter, we have to adjust the cut off freq.  $f_L$  of high pass filter to be higher than cut off freq.  $f_H$  of low pass filter.  
ie.  $f_L > f_H$ .



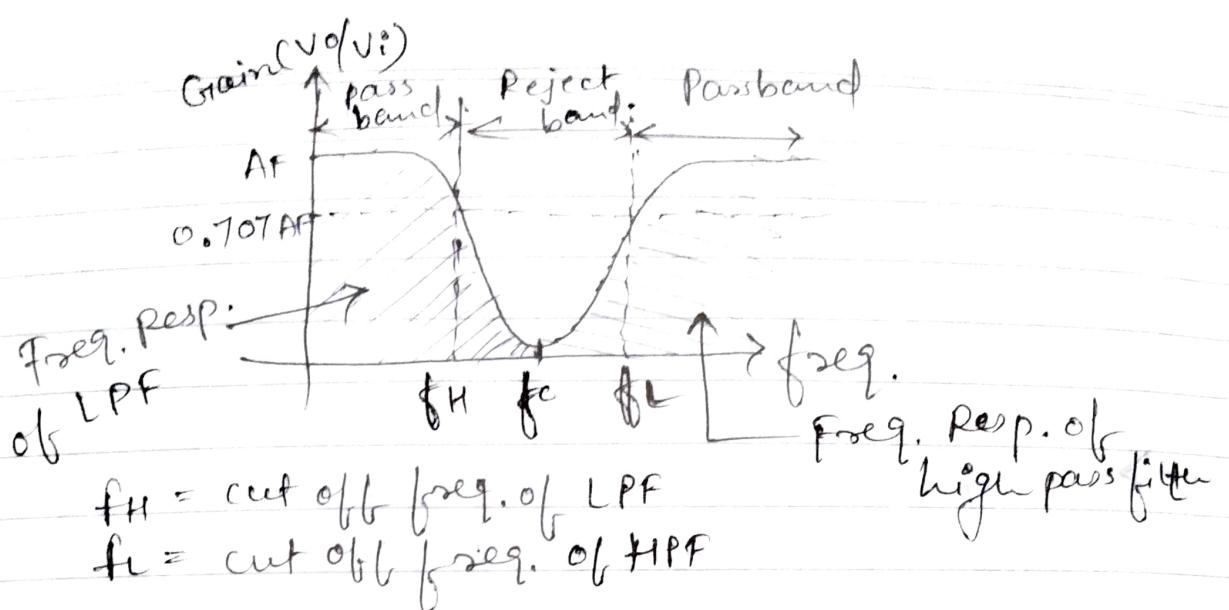

$$\text{Center freq.} \rightarrow f_C = \sqrt{f_H \cdot f_L}$$

→ Design wide band reject filter having  
 $f_H = 100\text{Hz}$  &  $f_L = 2\text{kHz}$ .

Sol<sup>n</sup>

Design for High pass section

$$\text{let } C = 0.01\mu\text{F}$$

$$\therefore R = \frac{1}{2\pi f_L C} = \frac{1}{2\pi \times 2 \times 10^3 \times 0.01 \times 10^{-6}} = 7.96\text{k}\Omega$$

$$\text{let gain} = 2.$$

$$\therefore AVF = 1 + \frac{R_F}{R_1} \quad \therefore 1 + \frac{R_F}{R_1} = 2$$

$$\therefore R_F = R_1 \quad \text{let us assume } R_F = R_1 = 10\text{k}\Omega$$

Design for Low pass section

$$\text{let } C' = 0.1\mu\text{F}$$


$$\therefore R' = \frac{1}{2\pi f_H C'} = \frac{1}{2\pi \times 100 \times 0.1 \times 10^{-6}} = 15.9\text{k}\Omega$$

Assuming same gain  $\therefore AVF = 2 \quad \downarrow R_F' = R_1' = 10\text{k}\Omega$


Assuming selecting  
 For summing amp,  $R_2 = R_3 = R_4 = 10\text{k}\Omega$
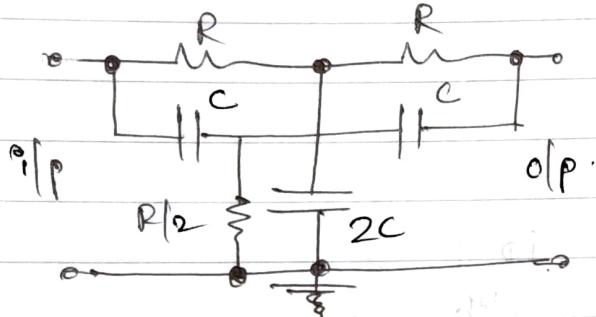
## (\*) Narrow Band Reject filter (Notch filter)

- It is also called as notch filter. The 'Q' of this filter is higher than that of wide band reject filter (i.e.  $Q > 10$ )
- Therefore it has very sharp frequency response. Notch filter commonly uses 'Twin-T' n/w as a frequency rejecting n/w.



Twin-T n/w

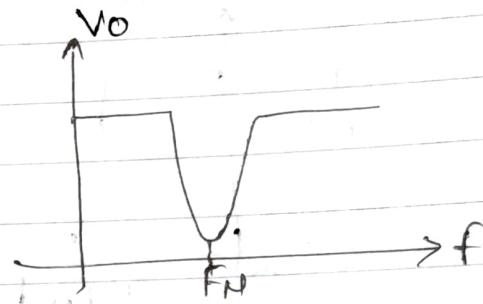

Freq. Response.

→ The first 'T' contains two resistors & one capacitor while as second one contains two capacitor & one resistor.

→ Maximum attenuation is obtained at a freq. called notch-cut frequency 'f\_N',

$$f_N = \frac{1}{2\pi RC}$$

→ The main drawback of 'T'n/w is that its 'Q' is low. Hence freq. response is not sharp.

→ This problem of low Q can be solved by using voltage follower after Twin-T n/w.



$$f_N = \frac{1}{2\pi RC}$$

App

→ In Communication circuits

→ In biomedical in order to eliminate undesired freq.

## → Active notch filter

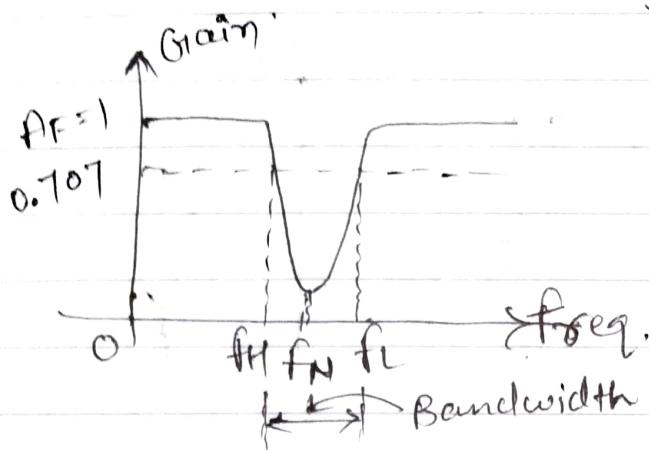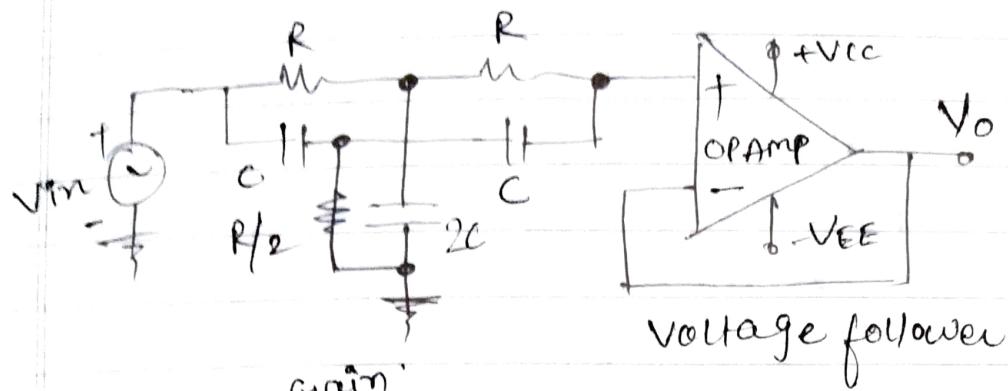

## → Design Procedure


- Select capacitor  $C$  of value less than 1  $\mu F$ .
- Calculate  $R = \frac{1}{2\pi f_N C}$

→ Design active notch filter for rejecting mains frequency 50Hz.

Sol?  $f_N = 50\text{Hz}$



Let us,  $C = 0.47\text{ }\mu F$ .
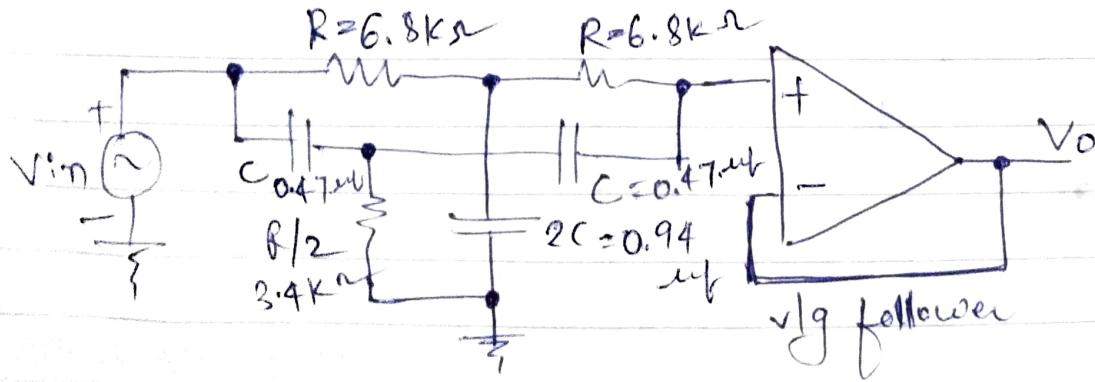
$$\therefore R = \frac{1}{2\pi f_N C} = \frac{1}{2\pi \times 50 \times 0.47 \times 10^{-6}} = 6.77\text{ k}\Omega$$


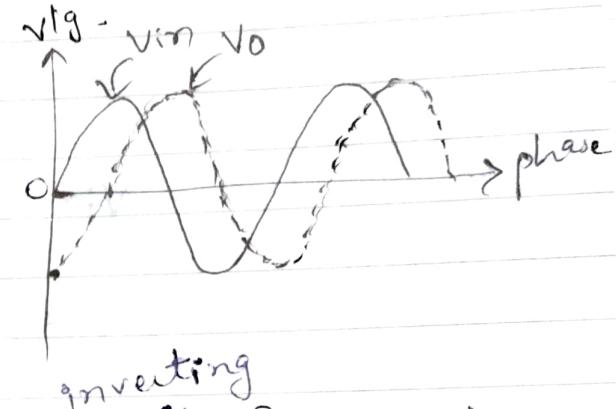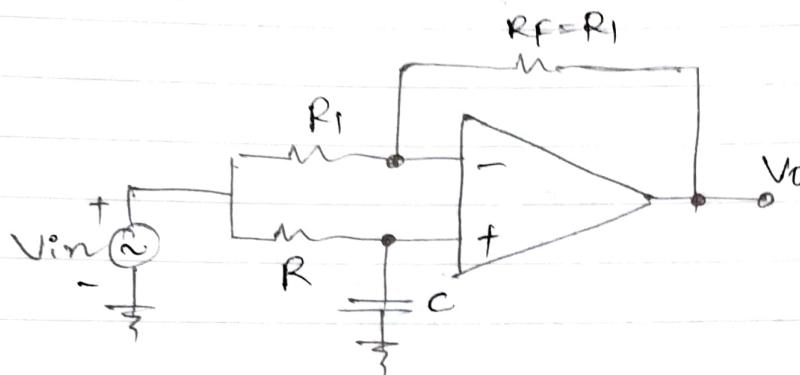
## ★ All Pass filter (Phase corrector)

- It is a special type of filter which passes all freq. component of ilp sig to off without any attenuation.
- But it introduces phase shift for different frequency components of ilp sig.
- They also called as phase corrector.



Case I Considering Vin is applied at ilp & non-inv terminal connected to ground:

$$V_o' = -\frac{R_F}{R_I} V_{in}$$

$$\text{But } R_F = R_I$$

$$\therefore V_o' = -V_{in}$$

Case II considering ilp is applied to non inv. terminal through RC & inv. terminal is grounded.

$$V_o'' = \text{Gain} \times \text{vlq across 'C'}$$

$$\therefore V_o'' = \left[ 1 + \frac{R_F}{R_I} \right] \times \left( \frac{-jX_C}{R - jX_C} \right) V_{in}$$

$$V_o'' = 2 \frac{-jX_C}{R - jX_C} V_{in} \quad \because R_F = R_I$$

$$\text{Now } V_o = V_o' + V_o''.$$

$$\therefore V_o = -V_{in} - \frac{2jX_C V_{in}}{R-jX_C}$$

$$\text{But } j = 1/j \quad \& \quad X_C = \frac{1}{2\pi f C}$$

$$\therefore V_o = V_{in} \left[ -1 + \frac{2 \left( \frac{1}{2\pi f C} \right)}{j \left( R + \frac{1}{j 2\pi f C} \right)} \right]$$

$$= V_{in} \left[ -1 + \frac{\left( \frac{1}{2\pi f C} \right) \times j 2\pi f C}{j \left( j 2\pi f R C + 1 \right)} \right]$$

$$= V_{in} \left[ -1 + \frac{2}{1+j 2\pi f R C} \right]$$

$$= V_{in} \left[ \frac{-1 - j 2\pi f R C + 2}{1+j 2\pi f R C} \right]$$

$$= \cancel{V_{in}} \left[ \cancel{\frac{-1 - j 2\pi f R C + 2}{1+j 2\pi f R C}} \right]$$

$$V_o = V_{in} \left[ \frac{1 - j 2\pi f R C}{1+j 2\pi f R C} \right]$$

$$\therefore \frac{V_o}{V_{in}} = \frac{1 - j 2\pi f R C}{1+j 2\pi f R C}$$

By taking mod on both side will get,

$$\frac{|V_o|}{|V_{in}|} = 1 \quad \text{ie. } |V_o| = |V_{in}|$$

That means amplitude of  $\frac{V_o}{V_{in}}$  will be 1.

App^n

→ In telephone n/w for compensation of phase change.

→ In T.V. to compensate phase change because phase contains the information.

Design a band pass filter for  $\alpha = 3$ , gain = 5  
 $\& f_c = 1 \text{ KHz}$

Soln  $\alpha < 10 \therefore$  given circuit is wide bandpass filter.

$$\alpha = 3 \quad \& f_c = 1 \text{ KHz}$$

$$\alpha = \frac{f_c}{BW} = \frac{\sqrt{f_H \cdot f_L}}{f_H - f_L}$$

$$3 = \frac{1 \text{ KHz}}{\frac{f_H - f_L}{\sqrt{f_H \cdot f_L}}} \therefore f_H - f_L = \frac{1 \times 10^3}{3} = 333.33 \text{ Hz}$$

$$\therefore f_H - f_L + 333.33$$

$$\text{Now, } f_c = \sqrt{f_H \cdot f_L}$$

$$\therefore f_c^2 = (1 \times 10^3)^2 = f_H \cdot f_L$$

$$\therefore f_H \cdot f_L = 10^6$$

$$\therefore (f_L + 333.33)f_L = 10^6$$

$$\therefore f_L^2 + 333.33f_L - 10^6 = 0.$$

This is quadratic equation.

$$\therefore f_L = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$= \frac{-333.33 \pm \sqrt{(333.33)^2 - 4 \times 1 \times 10^6}}{2 \times 1}$$

$$= -333.33 \pm \frac{\sqrt{4111108.889}}{2}$$

$$f_L = -333.33 \pm 2027.29$$

$$\therefore f_L = \frac{-333.33 + 2027.29}{2} \quad \text{or} \quad \frac{-333.33 - 2027.29}{2}$$

$$\therefore f_L = 847.13 \text{ Hz} \quad \because \text{freq} \neq -ve.$$

$$\therefore f_H = 847.13 + 333.33 = 1180.46 \text{ Hz}$$

For HPF,  $f_L = 847.13 \text{ Hz}$

choosing  $C = 0.1 \mu\text{F}$ ,

$$\therefore f_L = \frac{1}{2\pi RC} \quad \therefore R = \frac{1}{2\pi f_L C} = 1.87 \text{ k}\Omega$$

For LPF,

$$f_H = 1180.5 \text{ Hz}$$

choosing  $C' = 0.01 \mu\text{F}$ ,

$$f_H = \frac{1}{2\pi R' C'}$$

$$\therefore R' = \frac{1}{2\pi f_H C'} = 13.48 \text{ k}\Omega$$

Chain of filter = 5

$$\therefore A_{FT} = A_{F1} \cdot A_{F2} = 5$$

$$A_{FT} = \left(1 + \frac{R_f}{R_1}\right) \left(1 + \frac{R_f'}{R_1'}\right) = 5$$

Assuming  $R_f = R_f'$  &  $R_1 = R_1'$

$$\left(\frac{1 + R_f}{R_1}\right)^2 = (\sqrt{5})^2$$

$$\therefore \frac{1 + R_f}{R_1} = 2.236$$

$$\therefore \frac{R_f}{R_1} = 1.236$$


$$\therefore R_f = 1.236 R_1$$

$$\text{let } R_1 = 1 \text{ k}\Omega \quad \therefore R_f = 1.236 \text{ k}\Omega$$

multiple f/b filters:-

more than one f/b path.

- exploit full open-loop gain & also referred to as  $\infty$  gain filters.
- with RRC filters, they are most popular single op-amp realization of the 2nd order responses.

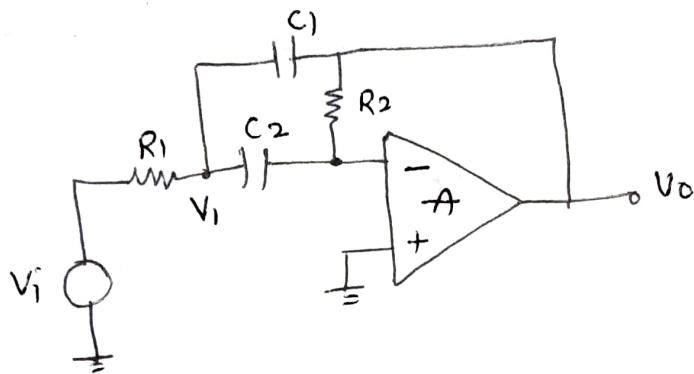Band Pass filters:-

The op-amp acts as differentiator w.r.t.  $V_1$ .

$$\therefore V_o = -s R_2 C_2 V_1 \quad \dots \textcircled{1}$$

summing currents at node  $V_1$ ,

$$\frac{V_i - V_1}{R_1} + \frac{V_o - V_1}{1/sC_1} + \frac{0 - V_1}{1/sC_2} = 0.$$

eliminating  $V_1$ , Let  $s \rightarrow j\omega$  & rearrange terms

$$\therefore H(j\omega) = \frac{V_o}{V_i} = \frac{-j\omega R_2 C_2}{1 - \omega^2 R_1 R_2 C_1 C_2 + j\omega R_1 (C_1 + C_2)} \quad \dots \textcircled{2}$$

To put eq<sup>n</sup> ② in std. form,

$$H(j\omega) = H_{OBP} H_{BP}(j\omega), \text{ we impose}$$

$$\omega^2 R_1 R_2 C_1 C_2 = (\omega/\omega_0)^2 \text{ to get}$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \quad \dots \textcircled{3}$$

$$\& j\omega R_1 (C_1 + C_2) = (j\omega/\omega_0)/Q \text{ to get,}$$


$$Q = \frac{\sqrt{R_2/R_1}}{\sqrt{C_1/C_2} + \sqrt{C_2/C_1}} \quad \dots \textcircled{4}$$

Finally we impose,  $-j\omega R_2 C_2 = H_{OBP} \times (j\omega/\omega_0)/\varrho$  to get

$$H_{OBP} = \frac{-R_2/R_1}{1 + C_1/C_2} \quad \dots \textcircled{5}$$

filter is of integrating type. Let  $C_1 = C_2 = C$
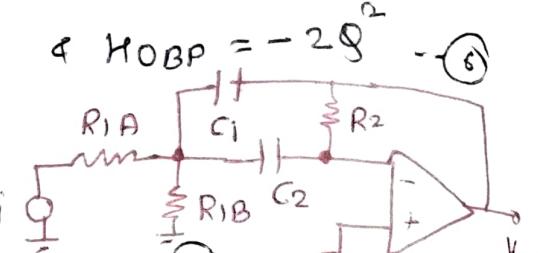
$$\therefore \omega_0 = \frac{1}{\sqrt{R_1 \cdot R_2 \cdot C}} \quad \varrho = 0.5\sqrt{R_1/R_2} \quad \& \quad H_{OBP} = -2\varrho^2 \quad \textcircled{6}$$



The corresponding design eqns are.

$$R_1 = 1/2\omega_0 \varrho C, \quad R_2 = 2\varrho/\omega_0 C. \quad \dots \textcircled{7}$$

Let resonance gain magnitude as  $H_0 = |H_{OBP}|$

If  $H_0 < 2\varrho^2$ , replace  $R_1$  with a voltage divider and,

$$\therefore R_{1A} = \varrho / H_0 \omega_0 C, \quad R_{1B} = R_{1A} / (2\varrho^2 / H_0 - 1).$$

Example: Design a multiple f/b BPF with  $f_0 = 1\text{kHz}$ ,  $\varrho = 10$  &  $H_0 = 20\text{dB}$ .

Soln :- Let  $C_1 = C_2 = 10\text{nF}$ .

$$\begin{aligned} \therefore R_2 &= 2 \times 10 / (2\pi \times 10^3 \times 10^{-8}) = 318.3\text{k}\Omega \\ &= 316\text{k}\Omega \quad \dots \text{std.} \end{aligned}$$

$H_0 = 20\text{dB} \Rightarrow 10\text{V/V}$ , which is less than  $2\varrho^2 = 200$ ,  
i.e  $H_0 < 2\varrho^2$ .

$\therefore$  we need IIP attenuator.


Thus  $R_{1A} = \varrho / H_0 \omega_0 C$

$$\begin{aligned} &= 10 / (10 \times 2\pi \times 10^3 \times 10^{-8}) = 15.92\text{k}\Omega \\ &= 15.8\text{k}\Omega \quad \dots \text{std.} \end{aligned}$$

$$\begin{aligned} \varrho R_{1B} &= R_{1A} / ([2\varrho^2 / H_0] - 1), \\ &= 15.92 / ((200/10) - 1). \end{aligned}$$

$$= 845\text{\Omega} \quad \dots \text{std.}$$

## Low Pass filter :- (∞ gain)

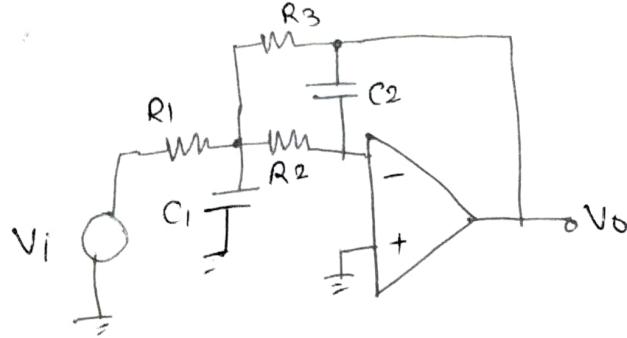

- $R_1 - C_1$  (low pass stage) followed by integrator stage ( $R_2, C_2$ ).
- presence of +ve f/b via  $R_3$  should allow for  $\Omega$  control.
- AC analysis gives,

$$\frac{V_o}{V_i} = H_{OLP} \cdot H_{LP} \text{ where}$$

$$H_{OLP} = -\frac{R_3}{R_1}, \quad \omega_0 = \frac{1}{\sqrt{R_2 R_3 C_1 C_2}} \quad \dots \textcircled{1}$$

$$\Omega = \frac{\sqrt{C_1/C_2}}{\sqrt{R_2 R_3 / R_1^2} + \sqrt{R_3 / R_2} + \sqrt{R_2 / R_3}} \quad \dots \textcircled{2}$$

ie  $\uparrow R_3$  to adjust  $\omega_0$ , &  $\downarrow R_1$  to adjust  $\Omega$ .

Example: Design multiple f/b LPF with  $H_0 = 2V/V$ ,  $f_0 = 10\text{KHz}$  &  $\Omega = 4$ .

Sol:- Design procedure:

1. choose  $C_2$  & calculate  $C_1$

$$C_1 = n C_2, \text{ where } n \rightarrow \text{capacitance spread.}$$

$$n > 4\Omega^2 (1+H_0).$$

2.  $H_0 \rightarrow$  desired dc gain magnitude.

$$\therefore R_3 = \frac{1 + \sqrt{1 + 4\Omega^2 (1+H_0) / n}}{2\omega_0 \Omega C_2}$$

$$R_1 = \frac{R_3}{H_0}$$

$$R_2 = \frac{1}{\omega_0^2 R_3 C_1 C_2}$$

$$dV \rightarrow Q \uparrow, THD \Rightarrow n\%$$

SOL :-  $n > 192$ .

Let  $n = 200$ .

Let  $C_2 = 1\text{nF}$

$\therefore C_1 = 0.2\text{uF}$

$R_3 = 2.387\text{ k}\Omega$

$= 2.37\text{ k}\Omega \text{ --- std.}$


$R_1 = 1.194\text{ k}\Omega$

$= 1.18\text{ k}\Omega \text{ --- std.}$

$R_3 = 530.5\Omega$

$= 536\Omega \text{ --- std.}$

### Notch Filter :-

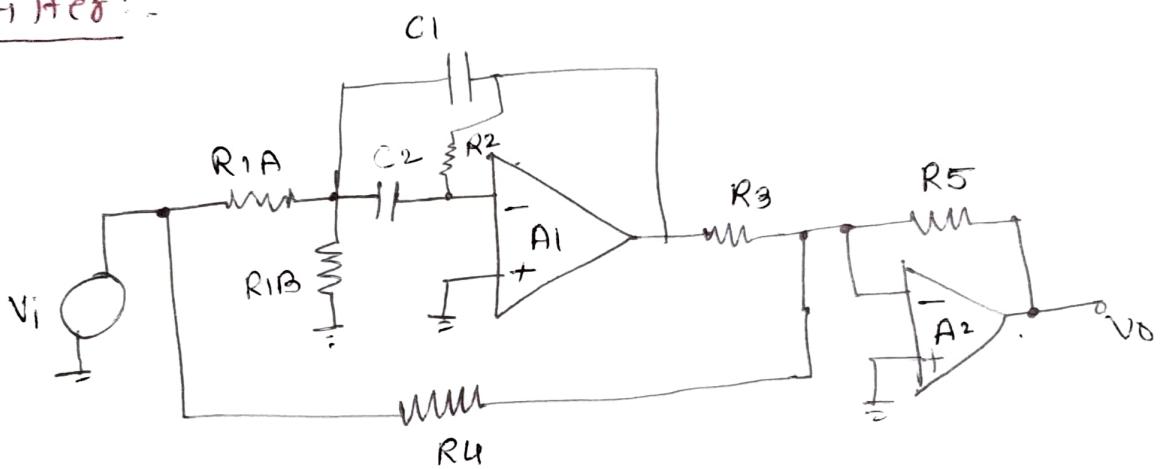

$$V_o = -\frac{R_5}{R_3} \left[ -H_0 H_{BP} \right] V_i - \left( \frac{R_5}{R_4} \right) \cdot V_i$$

$$= -\frac{R_5}{R_4} \left[ 1 - \left( H_0 R_4 / R_3 \right) H_{BP} \right] \cdot V_i$$

If  $H_0 R_4 / R_3 = 1$ ,

$$\therefore V_o / V_i = H_{ON} H_N, H_{ON} = -R_5 / R_4.$$

Ex:- Design a Notch filter with  $f_0 = 1\text{kHz}$ ,  $Q = 10$  &  $H_{ON} = 0\text{dB}$ .

SOL :-  $f_0 = 1\text{kHz}$ ,  $Q = 10$  &  $H_0 = 1\text{V/V}$ ,

$C_1 = C_2 = 10\text{nF}$ .

$R_2 = 318.3\text{k}\Omega$

$R_{1A} = 159.2\text{k}\Omega$

$R_{1B} = 799.8\Omega$

Select  $R_3 = R_4 = R_5 = 10\text{k}\Omega$ .