


Exp-2

Aim → VI characteristics of PN junction diode.

App → DIN4002, 100Ω resistor, power supply, breadboard, connecting wires, current meter

Circuit diagram →

Forward bias.

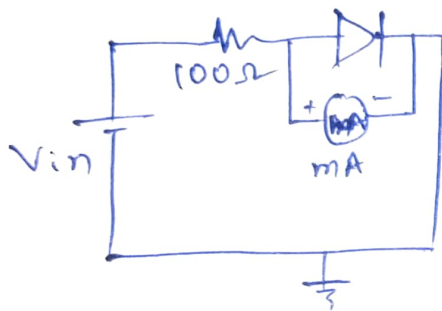

Observation

$V_{in}(V)$	$I_D(mA)$
0.1	
0.2	
⋮	
1V.	


Graph






PSPICE

PRINT OUT

Forward bias

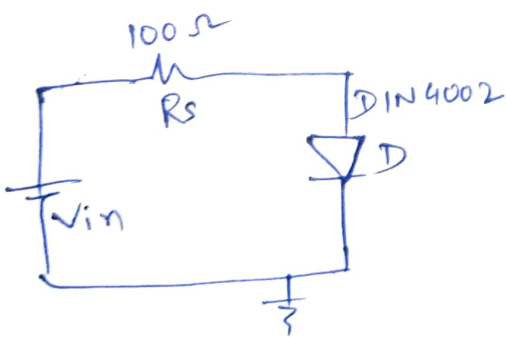

Reverse bias

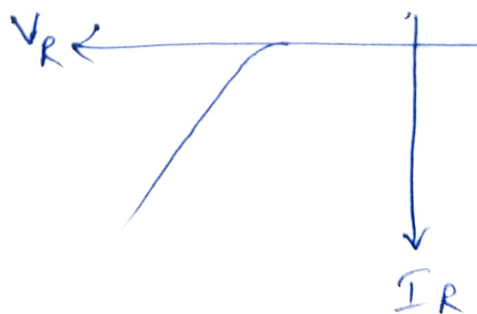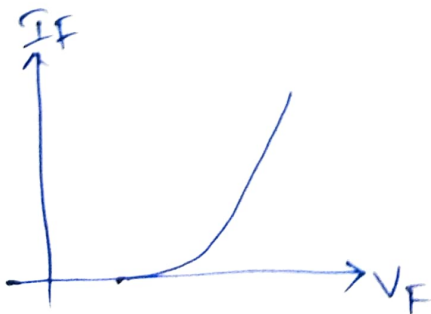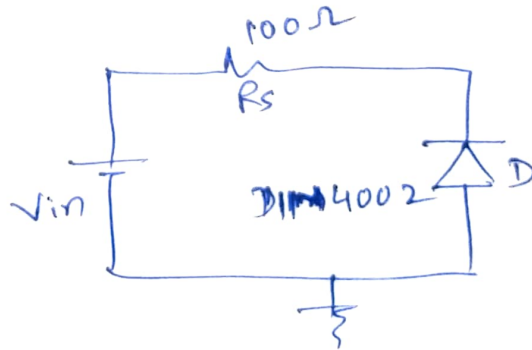


Conclusion →

Exp - 3

AIM → Zener diode as a regulator

App → power supply, 100Ω resistor, $10k\Omega$ potentiometer, Zener diode, current meter, breadboard, ~~power~~ connecting wires, Digital Multimeter.

Circuit diagram →

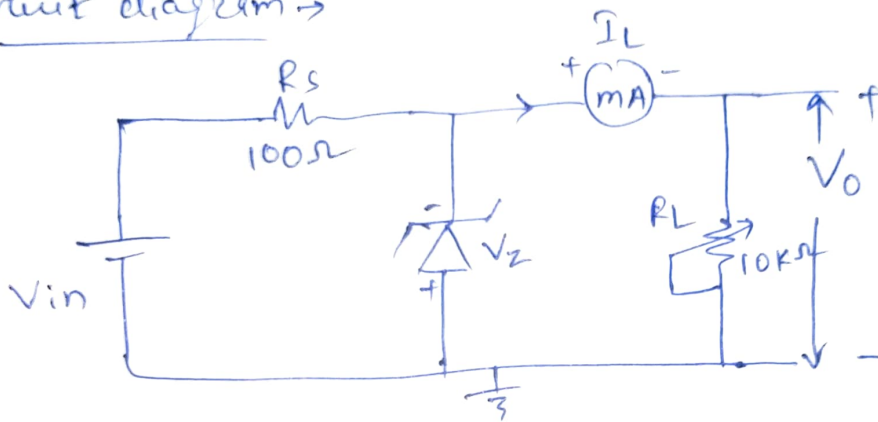


Observation

Load Regulation

$V_{in} = 5V$

$I_L (mA)$	$V_o (V)$
1 mA	
2 mA	
3 mA	
⋮	
7 mA	


Graph

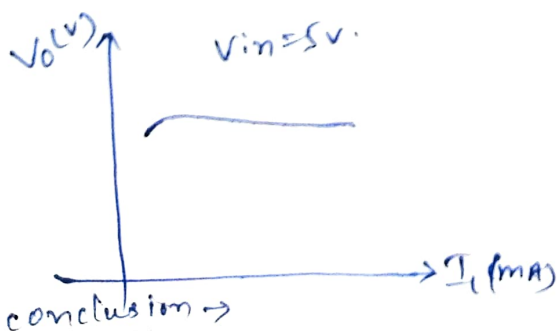

Line Regulation

$I_L = 4mA$

$V_{in} (V)$	$V_o (V)$
1V	
2V	
3V	
⋮	
7V	


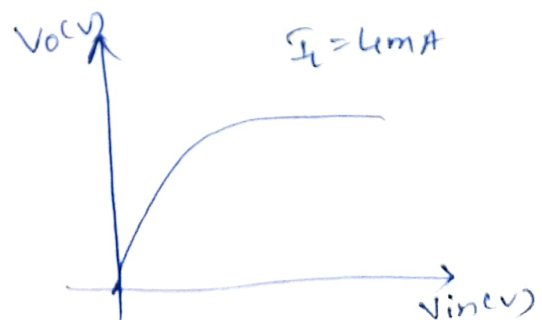


Exp-4

AIM → Stability factor of BJT fixed bias with & without feedback (ie. RE)

App → Power supply, breadboard, connecting wires, Resistors 1M Ω , 4.7K Ω , 820 Ω , Current meter (μ A & mA), Digital multimeter, Q2N2222

Circuit diagram

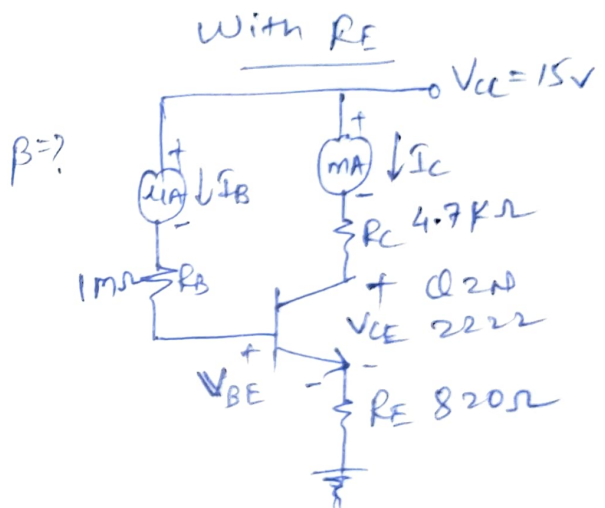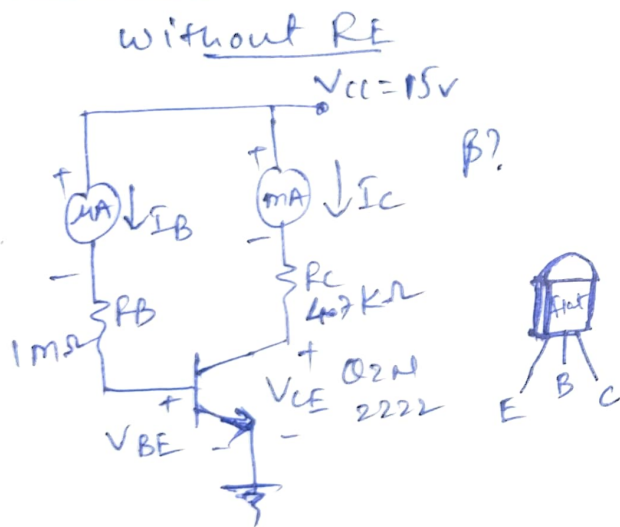

Observation

	I_B (mA)	I_C (mA)	V_{CE} (V)
Obs.			
Calculated.			

	I_B (mA)	I_C (mA)	V_{CE} (V)
Obs.			
Calculated			

Calculation

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B (1 + \beta) R_E}$$

$$I_C = \beta I_B$$


$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Exp-5

Aim - Q point of JFET using self bias.

App → power supply, breadboard, connecting wires,
Resistors $3.3K\Omega$, $1M\Omega$, $1K\Omega$, current meter,
Digital multimeter, BFW10/11.

Circuit Diagram

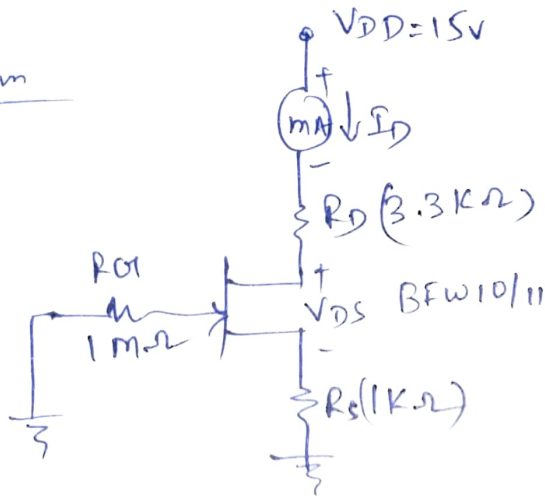

Substrate folded
then clockwise
GDS

Observation

	I_D (mA)	V_{GS} (V)	V_{DS} (V)
Observed			
Calculated			

Calculation. $I_{DSS} = 8mA$ & $V_P = -2.5V$

$$V_{GS} = -I_D R_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$0 = A I_D^2 + B I_D + C$$

select lower value of I_D .


$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

Exp - 6

Aim → Input & output characteristics of CE configuration, & find 'h' parameter.

App → Q2N2222, resistors $10k\Omega$, $1k\Omega$, breadboard, power supply, Ammeter, voltmeter, DMM, connecting wires.

Circuit diagram →

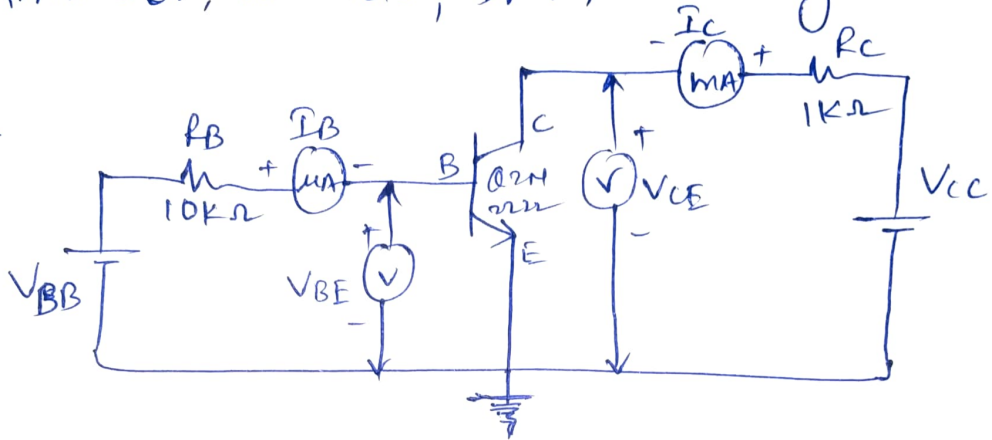

Observation

inp characteristics.

$V_{CE} = 2V$ $V_{CE} = 5V$


$V_{BE}(V)$	$I_B(\mu A)$
0.1V	
0.2V	
...	
1V	

$$V_{BE} = h_{ie} I_B + h_{re} V_{CE} \quad (1)$$

$$I_C = h_{fe} I_B + h_{oe} V_{CE} \quad (2)$$

Graph

inp chara.

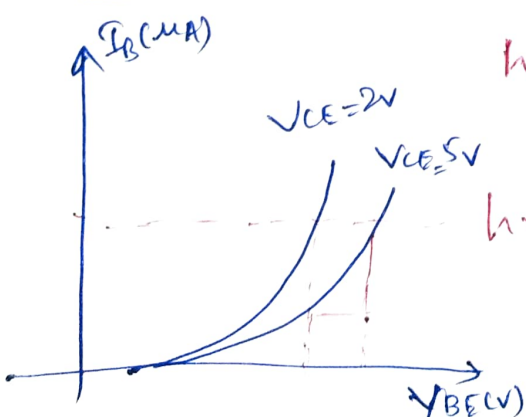

$$h_{ie} = \left. \frac{\Delta V_{BE}}{\Delta I_B} \right|_{V_{CE}}$$

$$h_{re} = \left. \frac{\Delta V_{BE}}{\Delta V_{CE}} \right|_{I_B}$$


o/p characteristics

$I_B = 50\mu A$

$I_B = 100\mu A$

$V_{CE}(V)$	$I_C(mA)$
1V	
2V	
...	
10V	

o/p chara

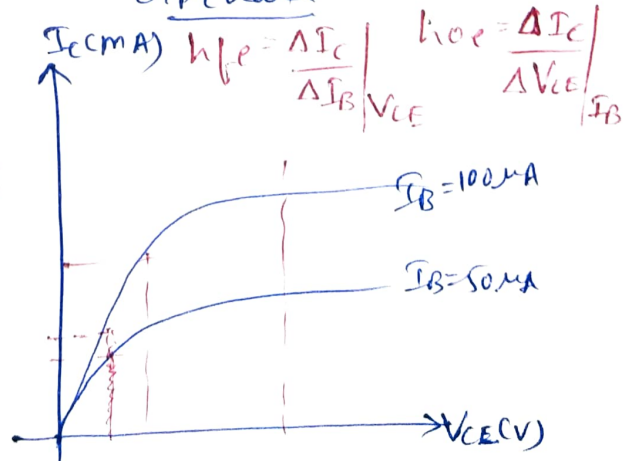


$$h_{fe} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE}} \quad h_{oe} = \left. \frac{\Delta I_C}{\Delta V_{CE}} \right|_{I_B}$$

Exp - 7

Aim → Frequency Response of CE amplifier.

App → Resistors, $82k\Omega$, $22k\Omega$, $5.6k\Omega$, $1.2k\Omega$, Capacitors $10\mu F$, $100\mu F$, BC547, function generator, power supply, CRO, Breadboard, connecting wires.


Circuit diagram →

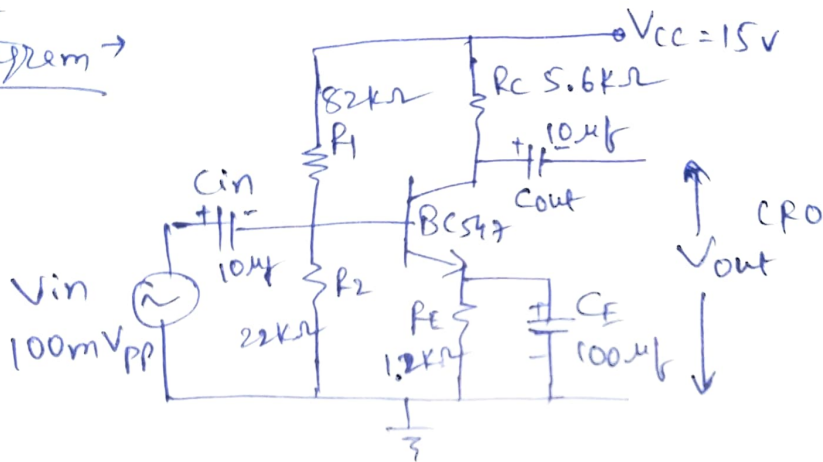

Observation $V_{in} = 100mV_{pp}$

Freq (Hz)	$V_o (V)$	gain (V_o/V_i)	gain dB $20\log(V_o/V_i)$
10			
20			
...			
100			
200			
...			
1K			
2K			
...			
10K			
...			
1MHz			

Graph

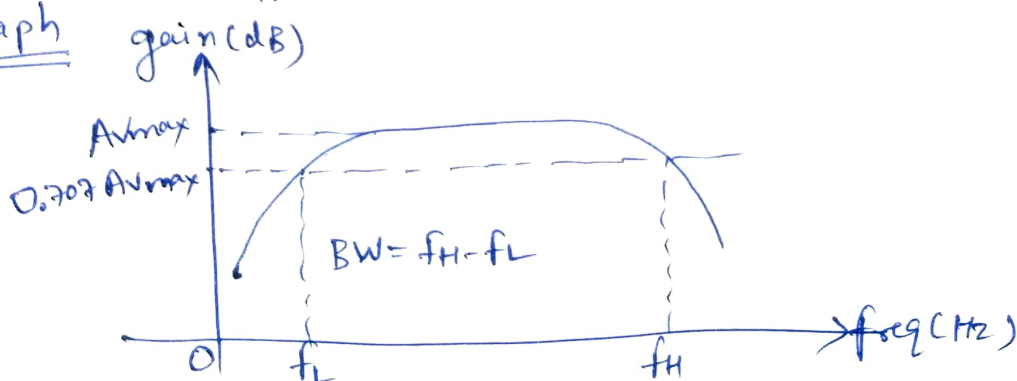


Exp- 8

Aim → Frequency response of CS-CS amplifier.
[Multistage amplifier].

App → PSpice Software. For resistor meg

Circuit
diag. →

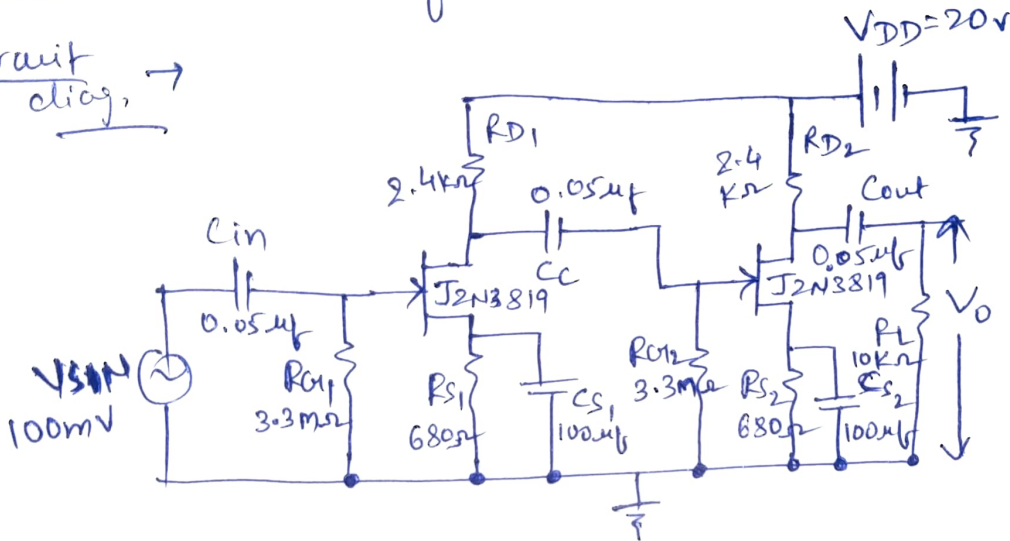


Print out i/p & o/p wave form.

Transient

Print step = 0ms
final step = 5ms.

Vsin

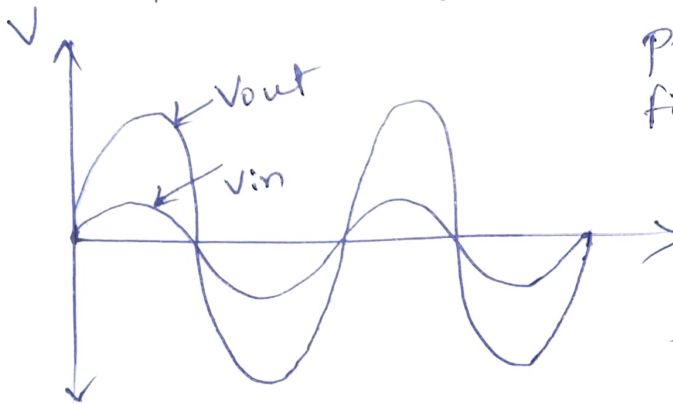
DC = 0V
AC = 100mV
VOFF = 0
Vamp = 50mV
freq = 1KHz



AC sweep

AC sweep type:
• Decade
sweep parameters:
pts = 101
start = 10Hz
Final = 100Meg
or end

Freq. response

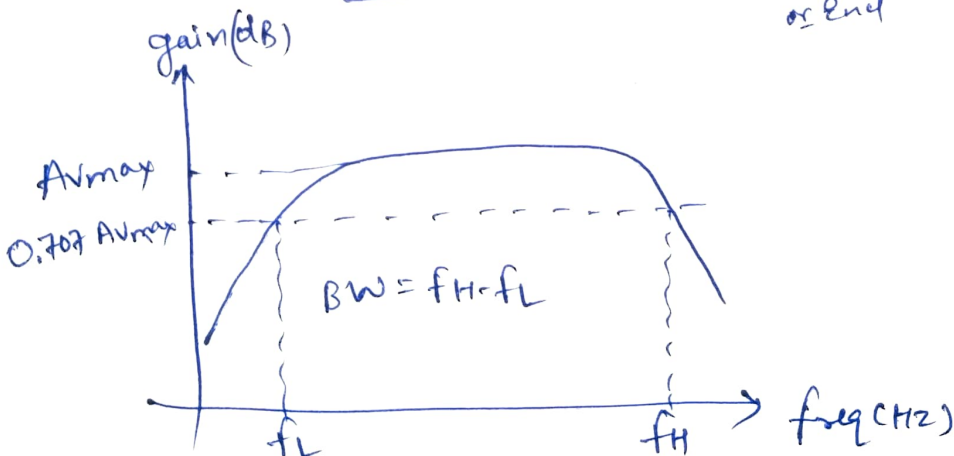

Exp-9

AIM →

Class B & class AB power amplifier.


Observe cross over distortion & remove it.
Calculate efficiency.

App →

PSPICE software

Circuit diagram →


Class B power amp

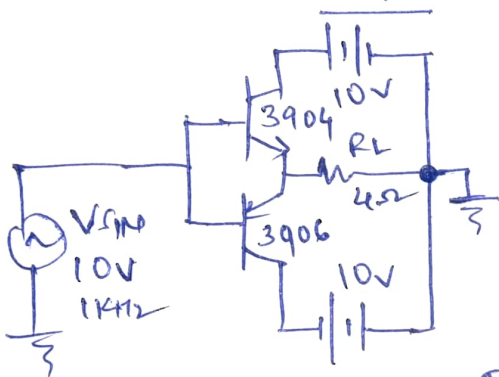



ilp o/p waveform

Printout

Class AB power amplifier

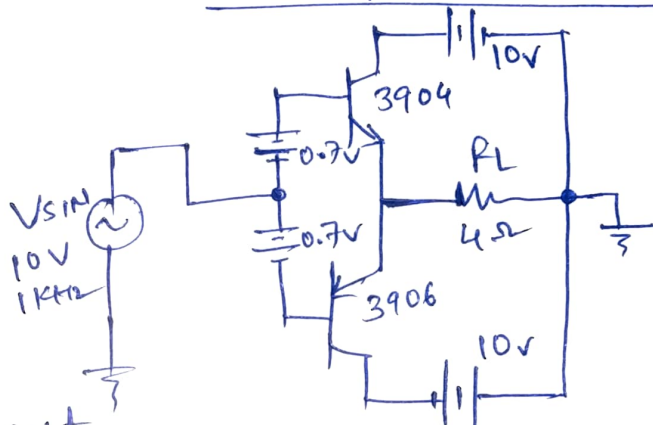

ilp o/p waveform

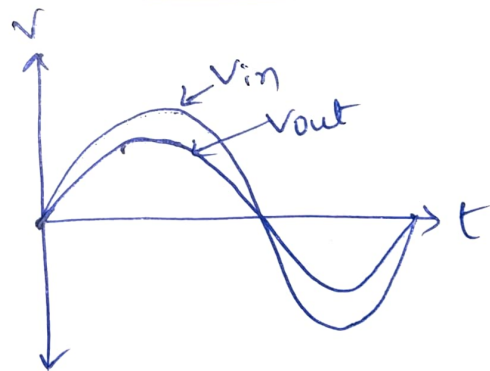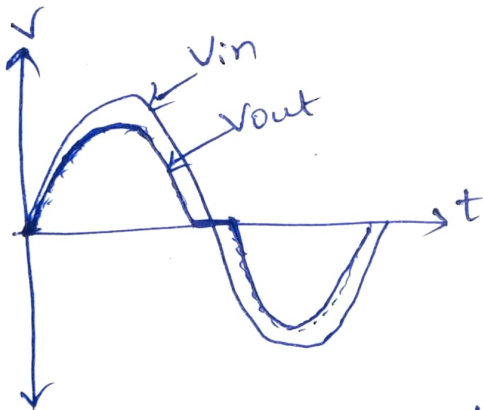

Calculation

$$P_{o(ac)} = \frac{V_{o(peak)}^2}{2R_L} =$$

$$P_{i(dc)} = \frac{2 V_{o(peak)} \times V_{cc}}{\pi R_L} =$$

$$\% \text{ Efficiency } \% \eta = \frac{P_{o(ac)}}{P_{i(dc)}} \times 100 =$$

Calculate for Both