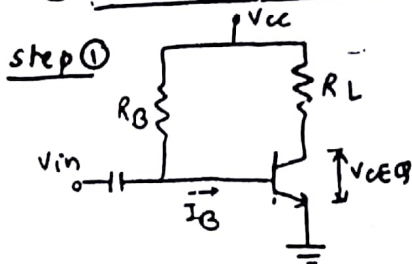


* Class A Amplifiers :-

① Direct coupled class A Amplifier :-

- load is directly coupled to collector.



② DC Analysis :-

Applying KVL in base loop

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$\therefore I_B R_B = V_{CC} - V_{BE}$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B} \Rightarrow I_B = \frac{V_{CC}}{R_B}$$

$$I_{CQ} = \beta I_B \quad \text{--- (1)}$$

Applying KVL in collector ck, b,

$$V_{CC} - I_{CQ} R_L - V_{CEQ} = 0$$

$$\therefore V_{CEQ} = V_{CC} - I_{CQ} R_L \quad \text{--- (2)}$$

Operating Point $Q = (V_{CEQ}, I_{CQ})$

step ③ DC load line :-

from Eqn (2), $I_{CQ} R_L = V_{CC} - V_{CEQ}$

$$I_{CQ} = \frac{V_{CC}}{R_L} - \frac{V_{CEQ}}{R_L}$$

$$I_{CQ} = \left(-\frac{1}{R_L}\right) V_{CEQ} + \frac{V_{CC}}{R_L} \quad \text{--- (3)}$$

$y = mx + c$ \therefore slope $= -\frac{1}{R_L}$
(of DC load line)

To find 2 pt's

(i) Transistor in saturation
 $V_{CE} \approx 0$ put in (3),

$$\therefore I_{CQ} = \frac{V_{CC}}{R_L}$$

(ii) Trans in cutoff


$I_{CQ} = 0$ put in (3)

$$V_{CE} = V_{CC}$$

from graph,

$$V_{CEQ} = \frac{V_{CC}}{2} \text{ \& } I_{CQ} = \frac{V_{CC}}{2R_L}$$

--- (4)

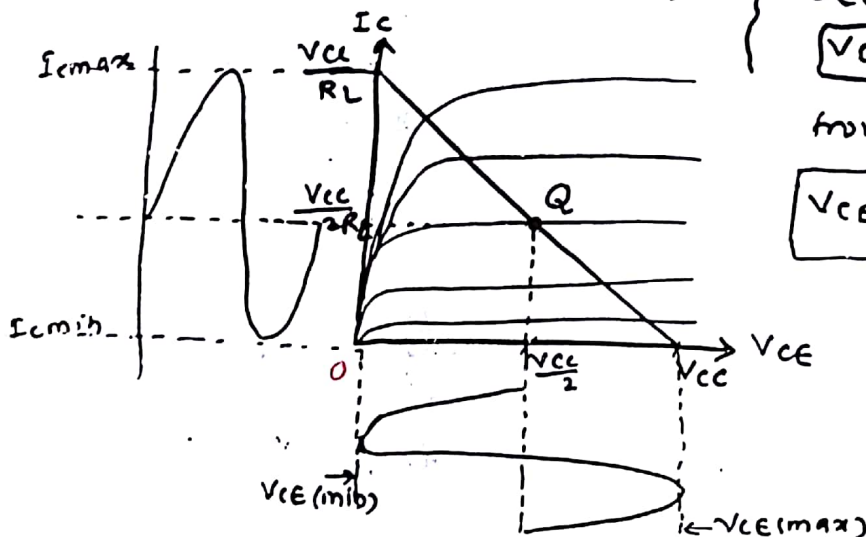

step ④ AC load line: same (\because ac & dc load are same).

step ⑤ DC signal power :- Assume $I_B = 0$

$$P_{DC} = I_{CQ} \cdot V_{CC} \text{ using (4), } P_{DC} = \frac{V_{CC}}{2R_L} \cdot V_{CC} \Rightarrow P_{DC} = \frac{V_{CC}^2}{2R_L} \quad \text{--- (5)}$$

step ⑥ AC power given to load :-

$$P_{ac} = V_{rms} \cdot I_{rms} = I_{rms}^2 R_L = \frac{V_{rms}^2}{R_L}$$

In terms of Peak values,

$$P_{ac} = \left(\frac{V_o(p)}{\sqrt{2}} \right) \cdot \left(\frac{I_o(p)}{\sqrt{2}} \right) = \frac{V_o(p) \cdot I_o(p)}{2} \quad \text{--- ②}$$

In terms of Peak to Peak values,

$$P_{ac} = \left(\frac{V_o(pp)}{2\sqrt{2}} \right) \cdot \left(\frac{I_o(pp)}{2\sqrt{2}} \right) = \frac{V_o(pp) \cdot I_o(pp)}{8} \quad \text{--- ③}$$

In terms of Max & Min values,

$$P_{ac} = \left[\frac{(V_{ce\max} - V_{ce\min})}{2\sqrt{2}} \right] \cdot \left[\frac{(I_{c\max} - I_{c\min})}{2\sqrt{2}} \right]$$

$$P_{ac} = \frac{(V_{ce\max} - V_{ce\min})(I_{c\max} - I_{c\min})}{8} \quad \text{--- ④}$$

By Referring graph,

$$P_{ac} = \frac{(V_{cc} - 0)(V_{cc}/R_L - 0)}{8} \quad \therefore \boxed{P_{ac(\max)} = \frac{V_{cc}^2}{8R_L}} \quad \text{--- ⑤}$$

step ⑦ Efficiency of amp^r (Theoretically)

$$\% \eta = \frac{P_{ac}}{P_{dc}} \times 100 \quad \therefore \text{from eqn ⑤ \& ⑥,}$$

$$\eta_{\max} = \frac{\frac{V_{cc}^2}{8R_L}}{\frac{V_{cc}^2}{4R_L}} \times 100 = \frac{100}{4} = 25\% \quad \boxed{\eta = 25\%}$$

step ⑧ Power Dissipation in transistor :

$$P_D = V_{ceQ} \times I_{cQ} \quad \text{using eqn ⑥,}$$

$$P_{D\max} = \frac{V_{cc}}{2} \cdot \frac{V_{cc}}{2R_L} = \frac{V_{cc}^2}{4R_L}$$

step ⑨ Figure of Merit :-

$$FM = \frac{P_{D\max}}{P_{ac\max}} = \frac{\frac{V_{cc}^2}{4R_L}}{\frac{V_{cc}^2}{8R_L}} = 2 \quad \boxed{FM = 2}$$

* Angle of conduction = 360°

η = very poor (25%)


FM = 2

Transistor Power Dissipation = Very large

Drawback = less η , higher P_D , Generates Hum

* Transformer coupled class A Amplifier:-


① ckt diagram:-

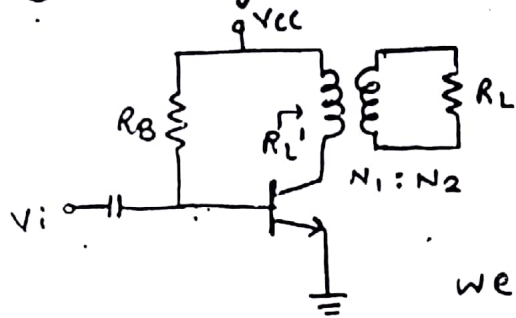

- AF transformer is used with turns ratio as $N_1:N_2$

- By adjusting no. of turns, o/p resist. of X'mer can be matched with load resist R_L for Max. Power Transfer.

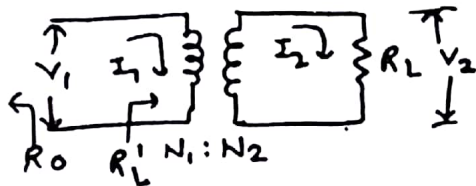We know, $\frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1} = K$



or $K = \frac{V_2/R_L}{V_1/R_L'} = \frac{I_2}{I_1}$

R_L' = load Resi. seen from primary

$\therefore K = \frac{V_2}{V_1} \cdot \frac{R_L'}{R_L} = \frac{1}{K} \frac{R_L'}{R_L} \therefore \frac{R_L'}{R_L} = K^2$ or $\frac{R_L'}{R_L} = \left(\frac{N_1}{N_2}\right)^2$

OR $\frac{N_1}{N_2} = \sqrt{\frac{R_L'}{R_L}} \Rightarrow$ By adjusting N_1, N_2 , we can (adjust) make o/p resist. of amplr = Reflected load Resistance R_L' .

② DC Analysis or DC load line:-


Apply KVL in Base loop, $I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B}$; $I_{BQ} \approx \frac{V_{CC}}{R_B}$

$\therefore I_{CQ} = \beta I_{BQ}$

Apply KVL in collector loop, for DC, $f=0$, X_L of Primary = 0

$\therefore V_{CEQ} = V_{CC}$ \therefore Q point is (V_{CEQ}, I_{CQ})


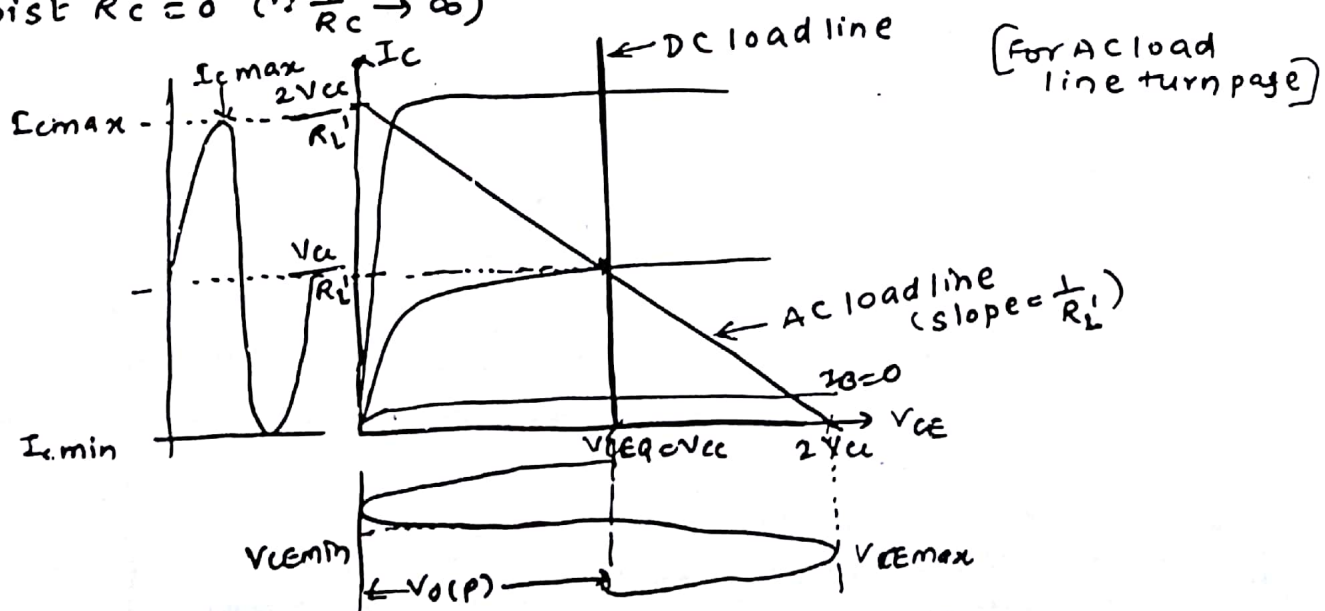
To draw DC load line, $V_{CEQ} = V_{CC} \therefore$ slope = $\infty \therefore$ collector DC resist $R_C = 0$ ($\because \frac{1}{R_C} \rightarrow \infty$)



To draw AC load line, primary winding inductance is always selected in such a manner that for ac ilp signal, it works as open. (10)

ie value of L_p is very large & current flowing through it will always remains constant.

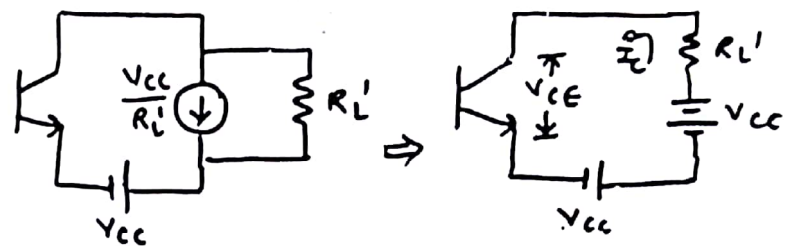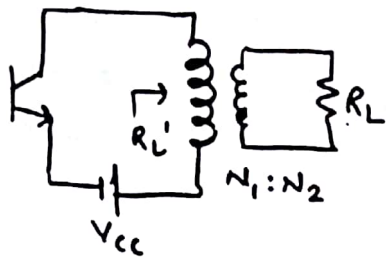∴ Primary of x'mer can be replaced by const current source



Replacing const current source with vtg source

Now considering worst condⁿ of transistors,

① In cutoff, $I_c = 0$ ($I_c R_L' = 0$) ∴ $V_{CE} = 2V_{CC}$

② In saturation, $V_{CE} = 0$ ∴ $I_c = \frac{2V_{CC}}{R_L'}$ ∴ pts $\Rightarrow (2V_{CC}, 0)$ & $(0, \frac{2V_{CC}}{R_L'})$

from the graph, $V_{CEQ} = \frac{V_{CEmax}}{2} = V_{CC}$

$$I_{CQ} = \frac{I_{Cmax}}{2} = \frac{2V_{CC}}{R_L'} \cdot \frac{1}{2} = \frac{V_{CC}}{R_L'}$$

③ DC ilp Power (P_{dc}) :-

$$P_{dc} = I_{CQ} \cdot V_{CC}$$

$$P_{dcmax} = \frac{V_{CC}}{R_L'} \cdot V_{CC} = \boxed{\frac{V_{CC}^2}{R_L'}}$$

④ AC power given to load (P_{ac})

(any formula from a, b, c in previous case)

$$P_{ac(max)} = \frac{(V_{CEmax} - V_{CEmin})(I_{Cmax} - I_{Cmin})}{8} = \frac{(2V_{CC} - 0)(\frac{2V_{CC}}{R_L'} - 0)}{8} = \frac{4V_{CC}^2}{8R_L'}$$

$$\therefore \boxed{P_{acmax} = \frac{V_{CC}^2}{2R_L'}}$$

⑤ Max η of Amplr :-

$$\eta_{max} = \frac{P_{acmax}}{P_{dcmax}} \times 100$$

$$= \frac{\frac{V_{CC}^2}{2R_L'}}{\frac{V_{CC}^2}{R_L'}} \times 100$$

$$\boxed{\eta_{max} = 50\%} \text{ — Better than Direct coupled}$$

⑦ Figure of Merit (FM) :-

$$FM = \frac{P_{dmax}}{P_{acmax}} = \frac{\frac{V_{CC}^2}{R_L'}}{\frac{V_{CC}^2}{2R_L'}} = 2 \Rightarrow \boxed{P_{dmax} = 2P_{acmax}}$$


$$\therefore \boxed{FM = 2}$$

⑥ Power dissipation in Trans. (max)

$$P_{dmax} = I_{CQmax} \times V_{CEmax} = \frac{V_{CC}}{R_L'} \times V_{CC} = \frac{V_{CC}^2}{R_L'}$$

* Drawbacks of single ended Transformer coupled A (Class A)

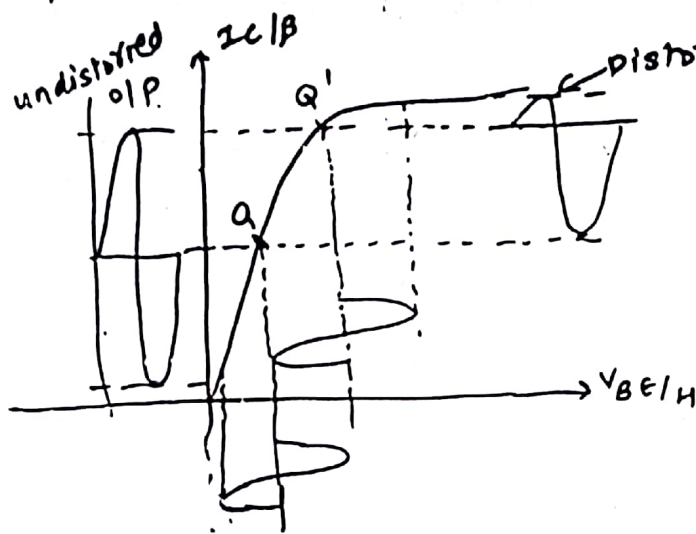- ① \therefore Q pt is in center of transfer characteristics, $I_c = I_{cq}$
Even when i/p is not applied, Hence continuous power dissipation of power occurs. \Rightarrow reduces η of Amplifier.




Q = Q pt before core saturation

Q' = Q pt (shifted) after saturation of core

- ② \therefore large dc current flows through x'mer primary windings, even $V_{ic} = 0$, core becomes saturated.

Due to core saturation, variation in o/p collector current will not be according to i/p variation. This generates distortion in o/p.

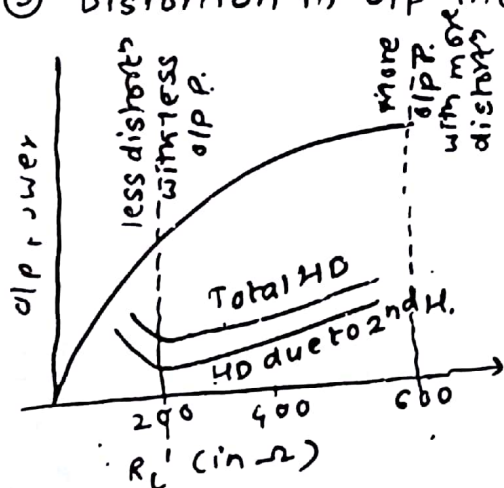- ③ Distortion in o/p increases with increase in load resistance



- ④ Distortion due to 2nd Harmonic is Max


- ⑤ operating pt at which distortion is less, o/p is also less.
Hence max power & min distortion points are different.

For designing this amplifier, it will be a compromise betⁿ Max Power & min distortion.

* Distortion in Power Amplifiers:-

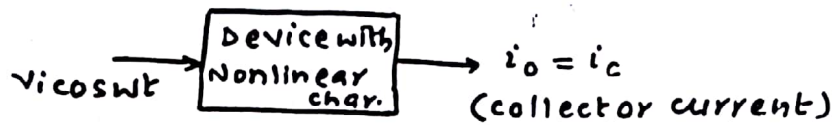(12)

- In VA, Q pt is selected at the center of load line.
 \therefore amplitude of i/p vtg is small, operation of transistor remains in linear region.
- In PA, i/p vtg swing is large. \therefore operation of transistor also enters in nonlinear region.
- If a signal $v_i = V_i \cos \omega t$ is applied to an active device (eg transistor) with nonlinear charct, the o/p current is given by Taylor's series.



$$\begin{aligned}
 i_c &= I_c + a_1 v_i \cos \omega t + a_2 (v_i \cos \omega t)^2 + a_3 (v_i \cos \omega t)^3 + \dots \\
 &= I_c + a_1 v_i \cos \omega t + a_2 v_i^2 \frac{1}{2} (\cos 2\omega t + 1) + \dots \\
 &= I_c + \frac{a_2 v_i^2}{2} + a_1 v_i \cos \omega t + \frac{a_2 v_i^2}{2} \cos 2\omega t + \dots \quad [\because \cos^2 \theta = \frac{1 + \cos 2\theta}{2}] \\
 &= I_c + \frac{a_2 v_i^2}{2} + a_1 v_i \cos (2\pi f t) + \frac{a_2 v_i^2}{2} \cos (2\pi f t) + \dots \quad \text{--- ①}
 \end{aligned}$$

where $\frac{a_2 v_i^2}{2}$ is new dc vtg at o/p

f = fundamental freq of i/p signal

$2f, 3f, 4f = 2^{nd}, 3^{rd} \text{ \& } 4^{th}$ harmonics of i/p signal.

\therefore Eqⁿ ① can be written as,

$$i_c = I_c + A_0 + A_1 \cos \omega t + A_2 \cos 2\omega t + A_3 \cos 3\omega t + \dots \quad \text{--- ②}$$

from eqⁿ ②,


- ① If signal with f freq is applied at i/p of nonlinear device, we get fundamental freq with harmonics of i/p freq.

This type of distortion is known as Harmonic Distortion (HD)

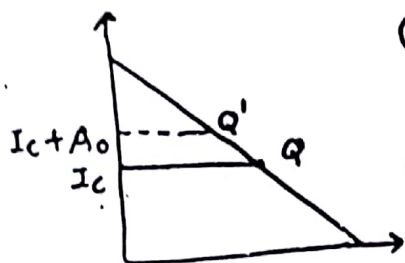(i) Amplitude of 2nd harmonic is max.

- ② At o/p we also get a new dc current. A_0 added to designed dc current I_c . Hence Q point will get shifted towards saturation.

This changes shape of o/p signal in +ve peak. This type of distortion is called as Amplitude distortion (AD)



- ③ \therefore charact of transistor is not linear the o/p current i_c is not directly proportional v_i . Hence we get distortion in o/p. This type of distortion is known as Non linear Distortion

Total Distortion / THD in PA:-

from eqn ②, % HD produced by 2nd harmonic is given by,

$$D_2 = \frac{A_2}{A_1} \times 100$$


while due to 3rd harmonics

$$D_3 = \frac{A_3}{A_1} \times 100$$

$$\therefore \boxed{\text{THD} = \sqrt{D_2^2 + D_3^2 + D_4^2 + \dots}}$$


* class A pushpull amplifier:-

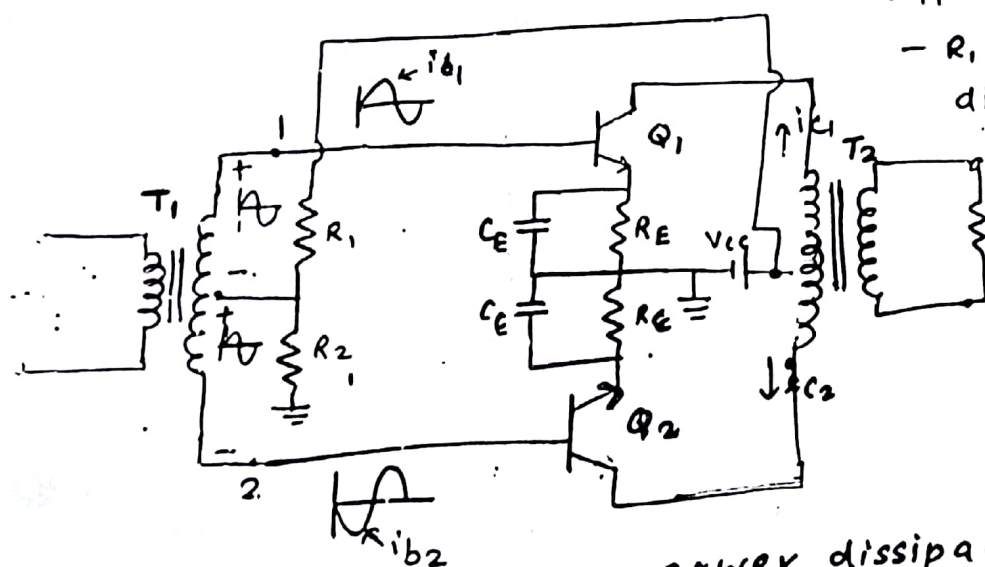- Q_1 & Q_2 are matched
- R_1 & R_2 is potential divider for biasing.
- R_1, R_2 selected such that Q pt of Q_1, Q_2 remains in the center of load line. (class A operate)



- R_E very small to reduce power dissipation. R_E used to provide stability of Q pt.
- T_1 : center-tapped i/p x'mer
- T_2 : combines o/p of Q_1 & Q_2 provides power amplified i/p signal.

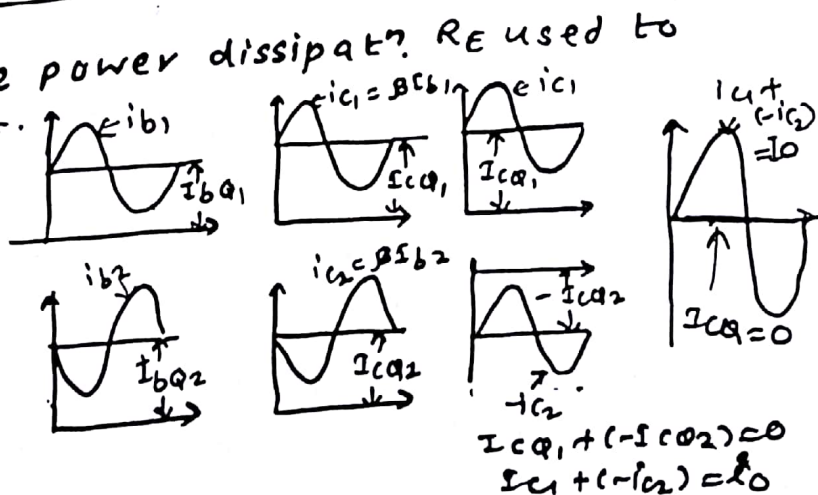$i_{c1} \rightarrow$ pulled down } so push pull
 $i_{c2} \rightarrow$ pushed up } Amplifier



* Advantages of Pushpull amplifiers :-

13

① How distortion is reduced in pushpull amplr?

→ If we assume Q_1, Q_2 both matched transistors

$v_i = V_i \cos \omega t$ then i_{b1} & i_{b2} are 180° out of phase

$$e_{b1} = V_i \cos \omega t$$

$$e_{b2} = V_i \cos(\omega t + \pi)$$

Then $i_{c1} = I_c + A_0 + A_1 \cos \omega t + A_2 \cos 2\omega t + A_3 \cos 3\omega t + \dots$ — (a)

$$i_{c2} = I_c + A_0 + A_1 \cos(\omega t + \pi) + A_2 \cos 2(\omega t + \pi) + A_3 \cos 3(\omega t + \pi) + \dots$$

But $\cos(\theta + n\pi) = \cos \theta$ — n is even

$\cos(\theta + n\pi) = -\cos \theta$ — if n is odd

$$\therefore i_{c2} = I_c + A_0 - A_1 \cos \omega t + A_2 \cos 2\omega t - A_3 \cos 3\omega t + \dots$$
 — (b)

\therefore o/p current is $i = i_{c1} - i_{c2}$

$$\therefore \boxed{I = 2A_1 \cos \omega t + 2A_3 \cos 3\omega t} \quad \text{--- (c)}$$

— Here component with $2\omega t$ is cancelled.

\therefore main source of HD is 2nd harmonic which is cancelled.
so (HD) Harmonic distortion reduces.

— from eq (c), all dc components are cancelled, problem of core saturatⁿ is eliminated.

\therefore Amplitude Distortⁿ due to core saturatⁿ is eliminated.

— from eq (c), amplitude of fundamental components get doubled.

— other than pushpull amplr, even if power supply is rectified, filtered, we get some ripple at o/p in the form of 'humming' Noise

In this pushpull amplr, ripples get cancelled.

(rippled current flow in opposite directⁿ in 2 halves of o/p transformer. Hence ripple v_{tg} doesn't affect o/p).

— It is less constly, power supply can be used.