

Multistage Amplifiers

In many applications, a single amplifier cannot provide all the gains that is required to drive a particular kind of load.

- e.g. a loud speaker represents a 'heavy' load (low R_L) in an audio amplifier system & several amplifier stages may be required to boost a signal originating at a microphone or magnetic tape head to a level sufficient to provide a large amount of power to the speaker.

- When the output of one amplifier stage is connected to the input of another amplifier, the amplifier stages are said to be in cascade.


- overall frequency

Z_i - overall input impedance of a multistage amplifier = input impedance of the first stage.

Note: g/p stage is normally an FET amplifier or Darlington connected BJT amplifier for high i/p impedance applications.

Z_o - overall output impedance of a multistage amplifier = output impedance of the last stage.

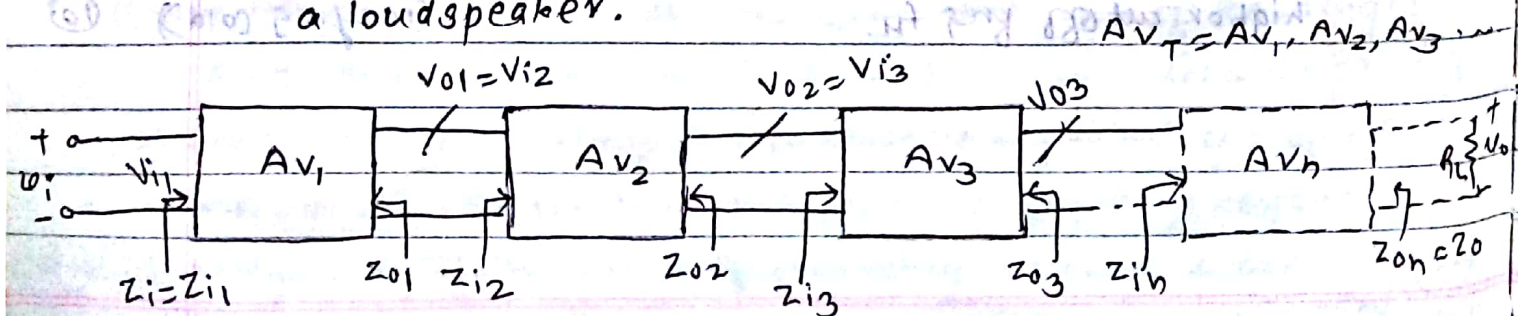Note: The last stage is normally a common collector power stage or a CE transformer coupled power stage for driving a low resistance load such as a loudspeaker.



Voltage Gain of a multistage Amplifier :-

If there are three stages cascaded,

$$\begin{aligned} A_v &= \frac{v_o}{v_i} = \frac{v_{o3}}{v_{i1}} = \frac{A_{v3} \cdot v_{i3}}{v_{i1}} \\ &= \frac{A_{v3} \cdot v_{o2}}{v_{i1}} = \frac{A_{v3} \cdot A_{v2} \cdot v_{i2}}{v_{i1}} \\ &= \frac{A_{v3} \cdot A_{v2} \cdot v_{o1}}{v_{i1}} = \frac{A_{v3} \cdot A_{v2} \cdot A_{v1} \cdot v_{i1}}{v_{i1}} \end{aligned}$$

$$A_v = A_{v1} \cdot A_{v2} \cdot A_{v3}$$

$$\therefore \frac{v_o}{v_s} = A_{vs} = A_{v1} \cdot A_{v2} \cdot A_{v3} \cdot \left(\frac{Z_i}{Z_i + R_s} \right)$$

$$\text{Where } A_{v1} = g_{m1} (Z_{o1} \parallel Z_{i2})$$

$$A_{v2} = g_{m2} (Z_{o2} \parallel Z_{i3})$$

$$A_{v3} = g_{m3} (Z_{o3} \parallel R_L)$$

* Advantages of cascaded Multistage Amplifiers :-

① Control over the input impedance :-

The i/p stage is usually required to provide a high i/p resistance in order to avoid loss of signal level when the amplifier is fed from a high resistance voltage source.

In a differential amplifier, the i/p stage must also provide large common-mode rejection.

② Control over the output impedance :-

The main function of the last (i.e. o/p) stage of an amplifier is to provide a low o/p resistance (if o/p is a v/bg signal) in order to avoid loss of gain when a low valued load resistance is connected to the amplifier.

Also, the o/p stage should be able to supply the current required by the load in an efficient manner. i.e. without dissipating an unduly large amount of power in the o/p transistors.

③ Controlling the voltage gain, $A_v = A_{v1} \cdot A_{v2} \cdot A_{v3} \dots$

The function of the middle (intermediate) stages of an amplifier cascade is to provide the bulk of the voltage gain.

In addition, the middle stages provide such other functions as the conversion of the signal from differential mode to single ended mode & the shifting of the dc level of the signal.

④ Controlling the bandwidth :-

eg CE-CB or CB-CG configuration for wideband frequency applications.

* Types of coupling :-


There are three types of coupling

① RC coupling

② Direct coupling

③ Transformer coupling

① RC coupling :-

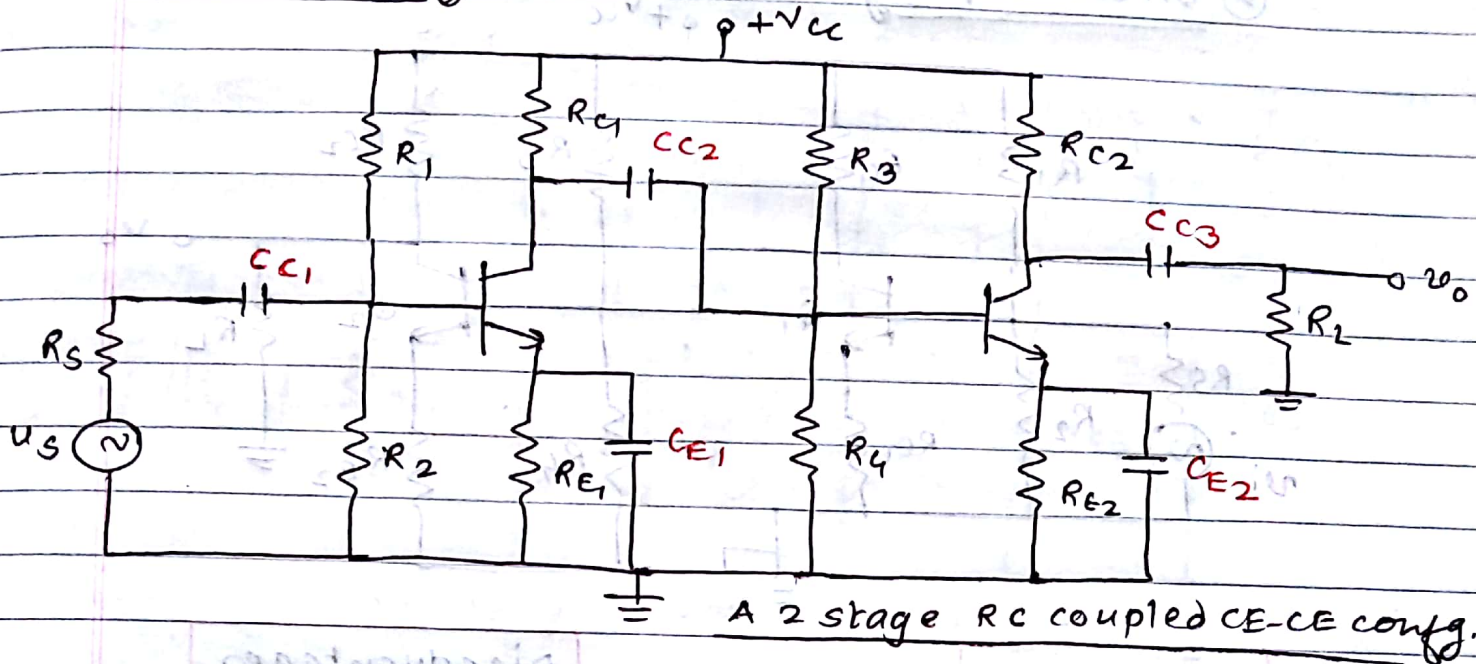


Advantages

- i) Q point of 1st stage will not affect Q pt of 2nd stage
- ii) Bandwidth is more

Disadvantages

- i) Q point of 1st stage affects Q pt of 2nd stage
- ii) It has poor impedance matching
- iii) It is not used in integrated ckt (\because it is difficult and uneconomical to fabricate large value capacitors)
- iv) It affects LF resp. ~~is less~~
- v) Cost is more.


Frequency Response :-

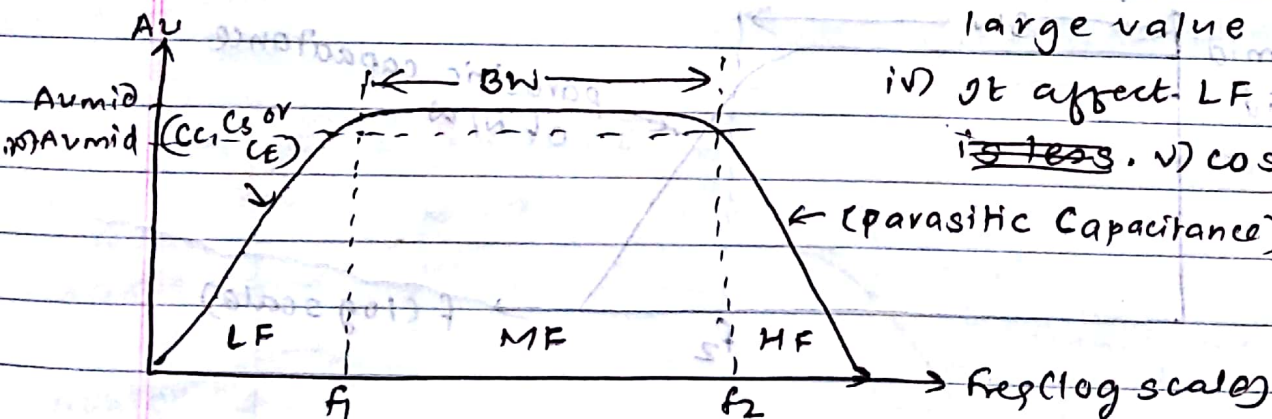

Applications :-

- used in Audio amplifiers.

② Direct coupling :-

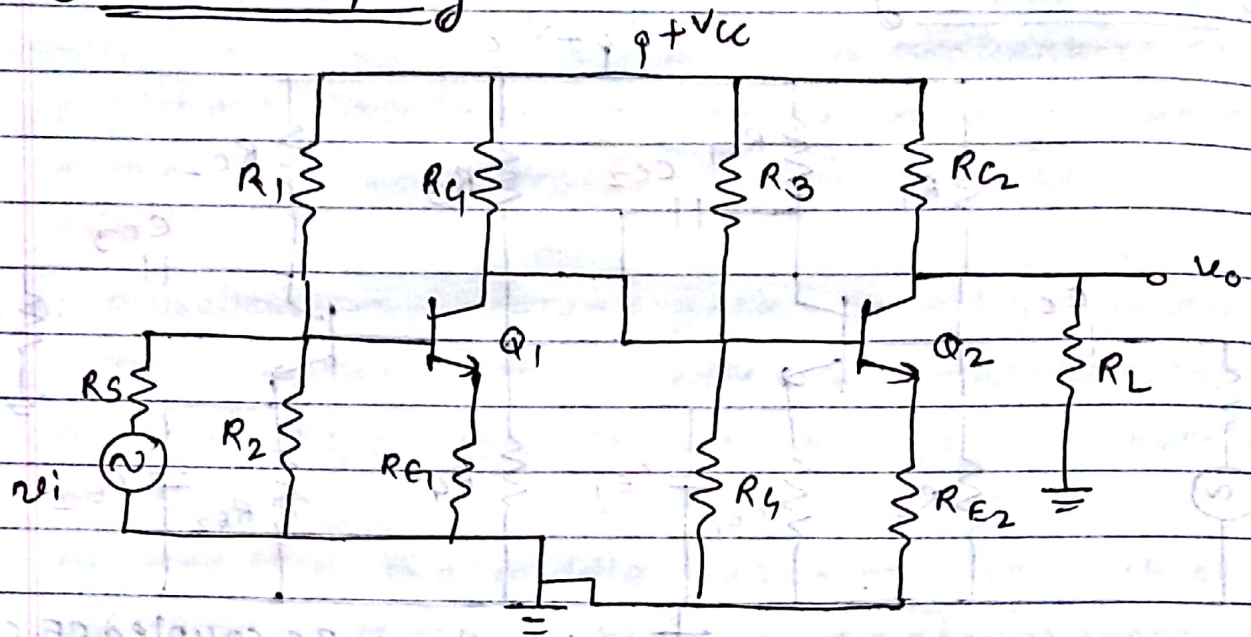


Advantages

- i) ckt is simple
- ii) No. of component required is less
- iii) space required is less
- iv) cost is less

Disadvantages

- i) Q point of 1st stage will affect Q pt of next stage (Unstable)
- ii) BW is less


Frequency Response.

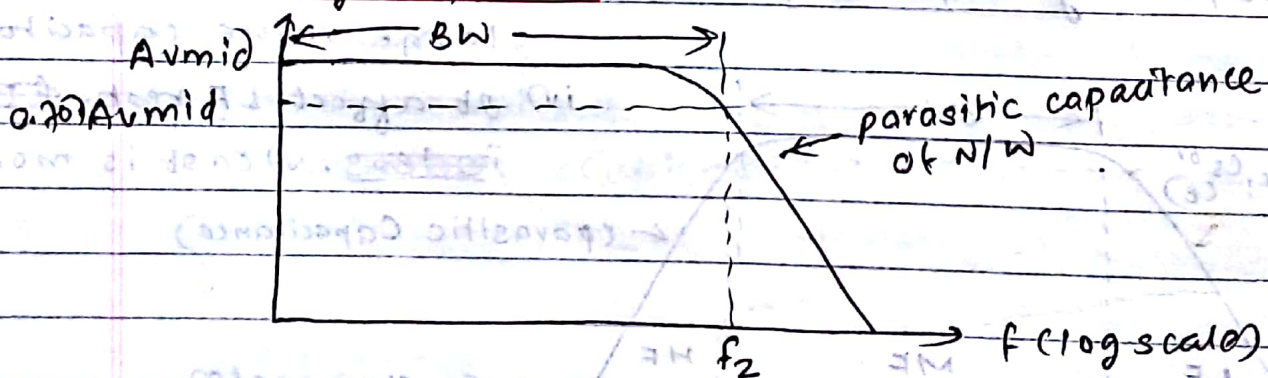

Applications :-

- It is used in integrated ckt (eg op-amp ckt)

③ Transformer coupling :-

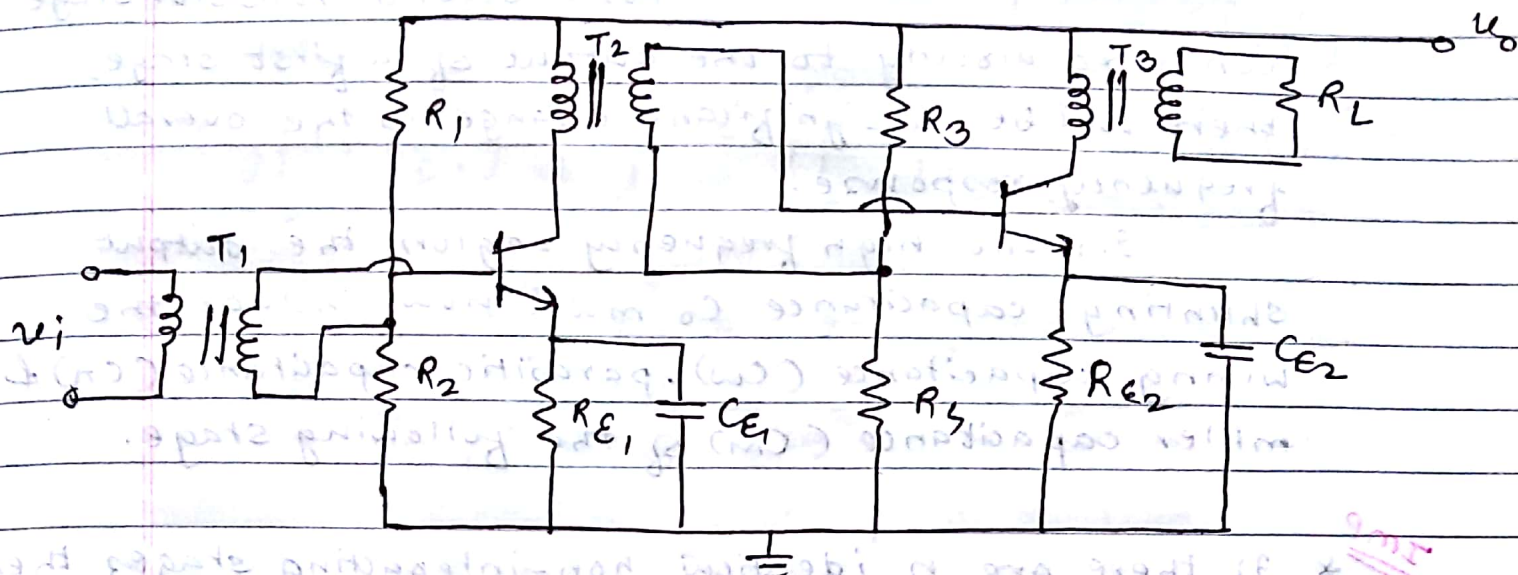

Advantages

i) Electrical isolation is achieved between the two stages.

ii) A part of first stage will not affect the next stage.

iii) Impedance matching is achieved with the help of

transformer.

Disadvantages

i) Transformer size is large.


ii) Cost is high.

iii) Space required is more.

iv) Losses in transformer are more.

v) Cannot be used in integrated circuit because of large size (of x'men).

Frequency Response

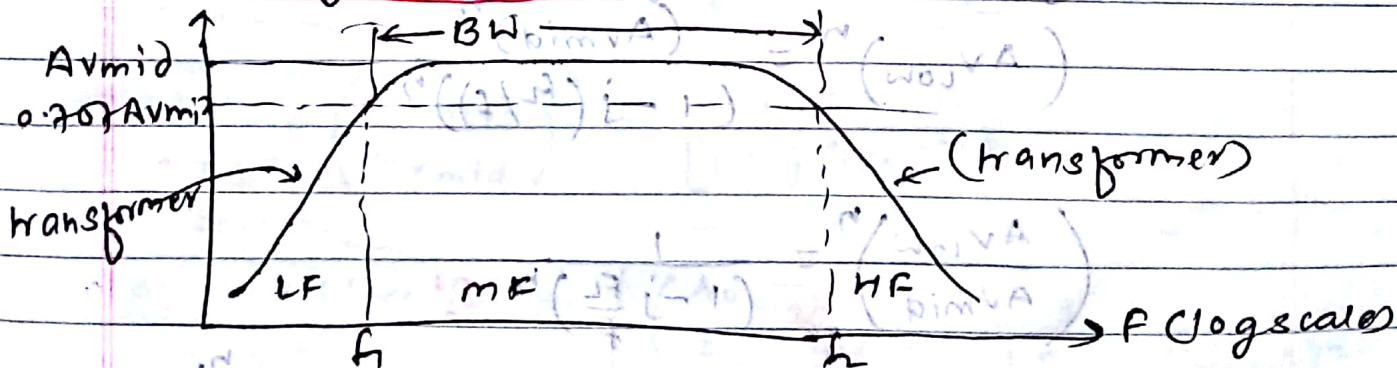

Applications :-

- It is used in power amplifiers.

* Multistage frequency effects :-

For a second transistor stage connected directly to the output of a first stage, there will be a significant change in the overall frequency response.

In the high frequency region, the output shunting capacitance C_o must now include the wiring capacitance (C_w), parasitic capacitance (C_n) & miller capacitance (C_m) of the following stage.

Imp * If there are n identical non-interacting stages, then it can be shown that, the overall lower & upper cut off frequencies are :-

$$f_L' = \frac{f_L}{\sqrt{2^{1/n} - 1}} \quad \& \quad f_H' = f_H \sqrt{2^{1/n} - 1}$$

Proof

for LF region, $A_{V_{Low}} = \frac{A_{V_{mid}}}{1 - j(f_L/f)}$

\therefore For n -stage amp^r, $A_{V_{(overall)(Low)}} = A_{V_1(Low)} \times A_{V_2(Low)} \times \dots$

\because each stage is identical, $A_{V_1(Low)} = A_{V_2(Low)} = \dots = A_{V_n(Low)}$

\therefore overall gain in the LF region,

$$(A_{V_{Low}})^n = \frac{(A_{V_{mid}})^n}{(1 - j(f_L/f))^n}$$

$$\left(\frac{A_{V_{Low}}}{A_{V_{mid}}} \right)^n = \frac{1}{(1 - j \frac{f_L}{f})^n}$$

At cutoff freq, $f = f_L'$ $|A_{V_{Low}}|^n = \frac{1(A_{V_{mid}})^n}{\sqrt{2}}$

$$\therefore \left| \left(\frac{A_{v_{low}}}{A_{v_{mid}}} \right)^n \right| = \frac{1}{\sqrt{2}} = \frac{1}{\left[\sqrt{1 + \left(\frac{f_L}{f_{L'}} \right)^2} \right]^n}$$

$$\text{ie. } \left\{ \left[1 + \left(\frac{f_L}{f_{L'}} \right)^2 \right]^{1/2} \right\}^n = \left\{ \left[1 + \left(\frac{f_L}{f_{L'}} \right)^2 \right]^n \right\}^{1/2} = (2)^{1/2}$$

$$\left[1 + \left(\frac{f_L}{f_{L'}} \right)^2 \right]^n = 2$$

$$1 + \left(\frac{f_L}{f_{L'}} \right)^2 = 2^{1/n}$$

$$\therefore \left(\frac{f_L}{f_{L'}} \right)^2 = 2^{1/n} - 1$$

$$\left(\frac{f_L}{f_{L'}} \right) = \sqrt{2^{1/n} - 1}$$

$$\therefore \boxed{f_{L'} = \frac{f_L}{\sqrt{2^{1/n} - 1}}}$$

Similarly for **HF region**

$$A_{v_{high}} = \frac{A_{v_{mid}}}{1 + j(f/f_H)}$$

overall gain in the high frequency region for n -identical stages,

$$(A_{v_{high}})^n = \frac{(A_{v_{mid}})^n}{[1 + j(f/f_H)]^n}$$

$$\therefore \left(\frac{A_{v_{high}}}{A_{v_{mid}}} \right)^n = \frac{1}{[1 + j(f/f_H)]^n}$$

$$\text{At cut off freq } f = f_H' \quad \left| \left(\frac{A_{v_{high}}}{A_{v_{mid}}} \right)^n \right| = \frac{1}{\left| [1 + j(f_H'/f_H)]^n \right|} = \frac{1}{\sqrt{2}}$$

$$\therefore \left\{ \left[1 + \left(\frac{f_H'}{f_H} \right)^2 \right]^{1/2} \right\}^n = (2)^{1/2}$$

$$\left[1 + \left(\frac{f_H'}{f_H} \right)^2 \right]^n = 2 \quad \therefore 1 + \left(\frac{f_H'}{f_H} \right)^2 = 2^{1/n}$$

$$\left(\frac{f_H'}{f_H}\right)^2 = 2^{n-1}$$


$$\left(\frac{f_H'}{f_H}\right) = \sqrt{2^{n-1}}$$

$$f_H' = f_H \sqrt{2^{n-1}}$$

| n | $\sqrt{2^{n-1}}$ | f_H' | f_L' |
|---|------------------|------------|------------|
| 1 | 1 | f_H | f_L |
| 2 | 0.64 | $0.64 f_H$ | $1.56 f_L$ |
| 3 | 0.51 | $0.51 f_H$ | $1.96 f_L$ |

For an identical two stage non-interacting amplifier the upper cutoff freq becomes 64% for a single stage while the lower cutoff freq becomes 1.56 f_L .
for $n=3$, upper cutoff freq is approx. 50% of a single stage while f_L' becomes almost twice the single stage value.

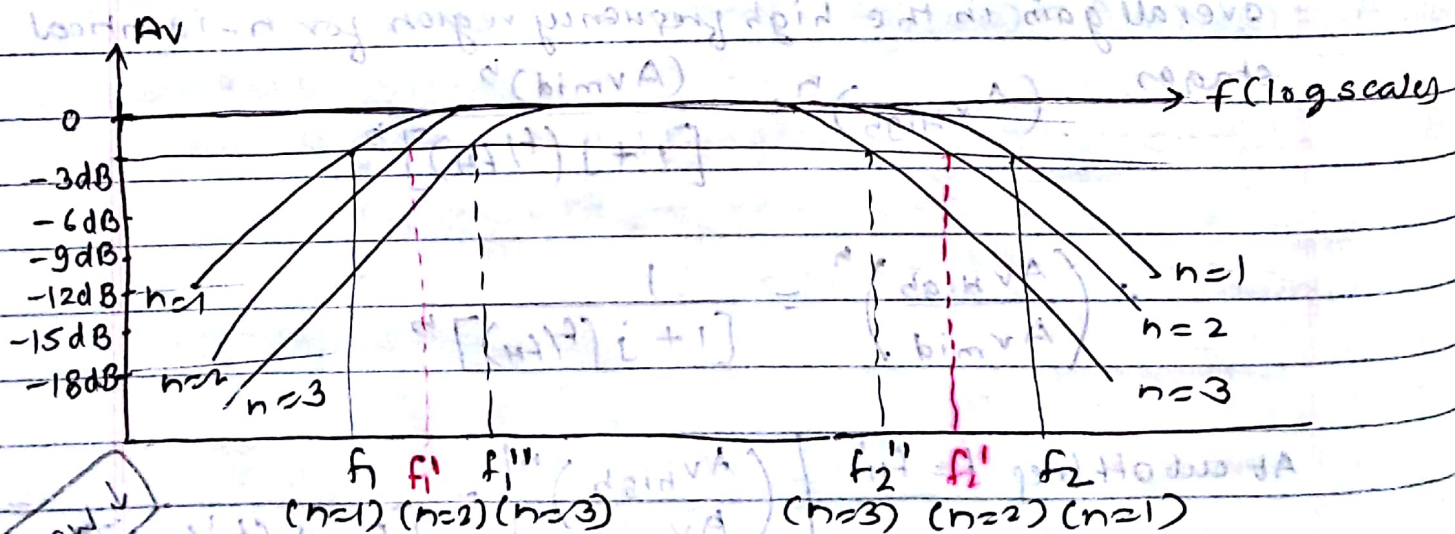* Frequency Response of cascaded/multistage amplifiers:-



effect of increased number of stages on the cut off frequencies