

## → Inverter (Sign changer)


It is same as the inverting amp<sup>\*</sup> in closed loop configuration.

But value of both resistors are same.

## → OPAMP as a Summing Amp<sup>\*</sup> or Adder.

It is possible to apply more than one i/p sig to an inverting amp<sup>\*</sup>. This ckt will then add all these i/p sigs to produce their addition at the o/p.

## → Inverting adder

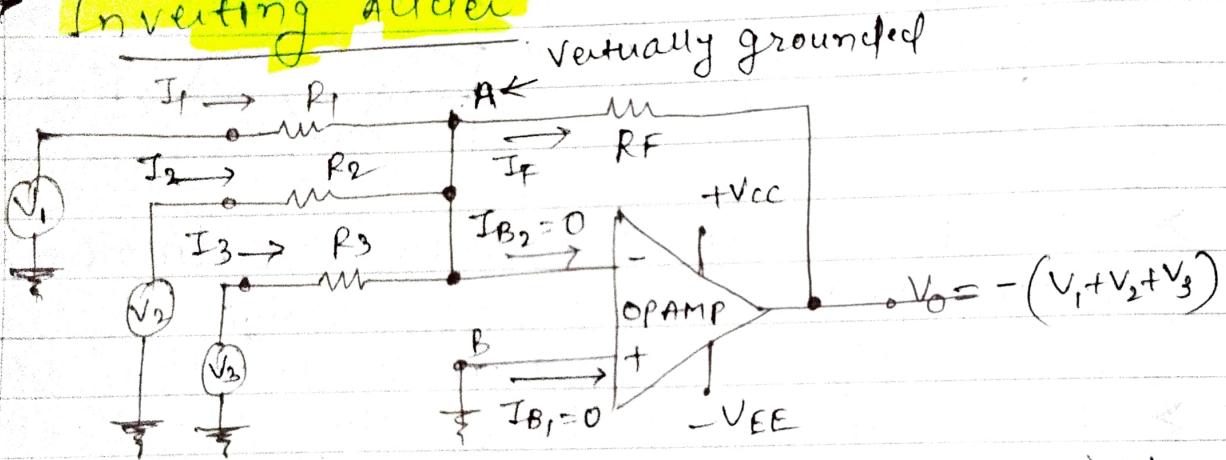

- Fig. shows Inverting summing amp<sup>\*</sup> with 3' i/p's  $V_1, V_2$  &  $V_3$ . Also depending upon the value of i/p resistance  $R_1, R_2$  &  $R_3$  this same ckt can be used as scaling amp<sup>\*</sup> or averaging amp<sup>\*</sup>. If  $R_f$  is the fb resistor.

- Applying KCL at node A,

$$I_1 + I_2 + I_3 = I_{B2} + I_F$$

but  $I_{B2} = 0$   $\Rightarrow R_i = \infty$  Ideally

&  $V_A = V_B = 0$  due to Virtual ground.

[ckt → Circuit, amp<sup>\*</sup> → amplifier]

Hence  $I_1 + I_2 + I_3 = IF$  (from KCL)  
 $I_F = V_i - V_A$ ,  $I_2 = \frac{V_2 - V_A}{R_2}$ ,  $I_3 = \frac{V_3 - V_A}{R_3}$  but  $V_A = 0$ .

$$\therefore IF = \frac{V_A \cdot N_o}{R_F} = \frac{-V_o}{R_F} \therefore V_A = 0.$$

$$\therefore \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = \frac{-V_o}{R_F}$$

OR

$$V_o = - \left[ \frac{R_F V_1}{R_1} + \frac{R_F V_2}{R_2} + \frac{R_F V_3}{R_3} \right] \rightarrow (A)$$

If we substitute  $R_F = R_1 = R_2 = R_3 = R$  then,

$$[V_o = -(V_1 + V_2 + V_3)]$$

As we see o/p is negative sum of i/p vls.  $\therefore$  It is called as Inverting adder. Also we can add any no. of ips.

→ As an Scaling or Weighted amp

Inverting adder ckt can also be used as an scaling or weighted amp.

- This can be done if each ip vlg is amplified by a different factor & this can be happened if resistors  $R_1, R_2$  &  $R_3$  are different in value.  
ie. From equation (A) shown above,

$$[V_o = - \left[ \frac{R_F V_1}{R_1} + \frac{R_F V_2}{R_2} + \frac{R_F V_3}{R_3} \right]]$$

where  $R_1 \neq R_2 \neq R_3$

So we can 'scale' each ip as per our requirement.

[no. of  $\rightarrow$  number of, ckt  $\rightarrow$  Circuit]

## → Averaging amp

- Also inverting adder ckt can be used as an averaging amp if  $R_1 = R_2 = R_3 = R$  &  $R_F = \frac{R}{3}$ . Substituting these values in equation (A),

$$V_o = -\frac{R_F}{R} (V_1 + V_2 + V_3) = -\frac{R/3}{R} (V_1 + V_2 + V_3)$$

$$\therefore V_o = -\frac{(V_1 + V_2 + V_3)}{3}$$


- So the magnitude of o/p vlg is equal to average of three i/p v/gs.

We can increase the no. of i/p's by setting

$$R_F = R/n \text{ & } R_1 = R_2 = \dots = R_n = R \text{ Then o/p vlg is,}$$



$$V_o = -\frac{(V_1 + V_2 + V_3 + \dots + V_n)}{n}$$

## → Non-Inverting Adder

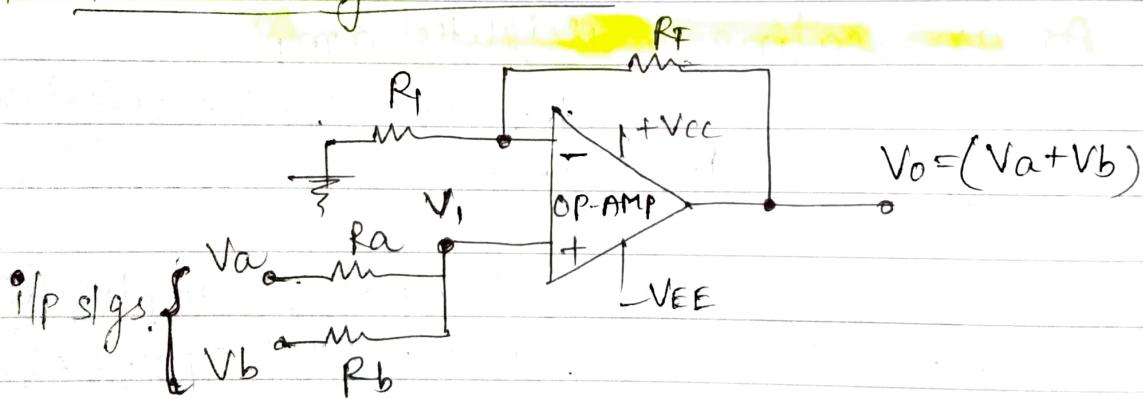

- In this adder circuit, we can produce addition of its i/p slgs without inversion. There are two i/p's  $V_a$  &  $V_b$  are applied to the non-inverting terminal through their resistors.

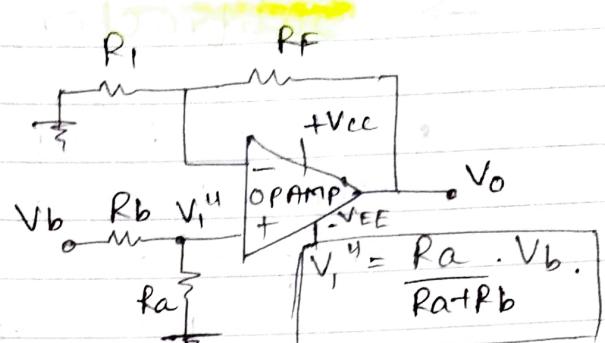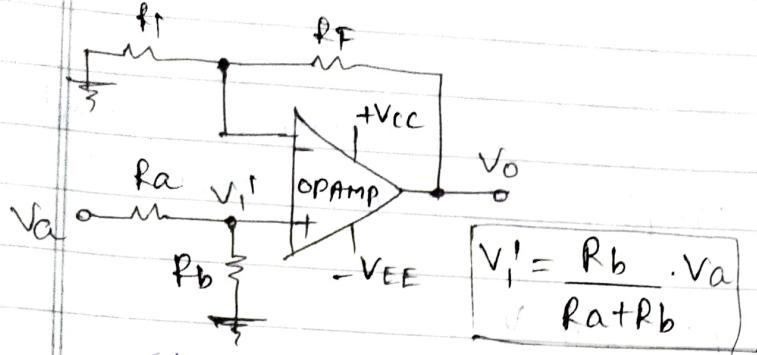[no. of → number of, amp = amplifier, ckt = circuit]



If  $V_b = 0$ ,

If  $V_a = 0$ ,

Case 1 :- Let  $V_b = 0$  i.e. connected to ground.

v/g at non-inverting side to  $V_a$  is given by,

$$V_1' = \frac{R_b}{R_a + R_b} \cdot V_a$$

Assuming  $R_a = R_b = R \therefore V_1' = V_a/2 \rightarrow ①$

Case 2 : Now  $V_a = 0$  i.e. connected to ground.

$$V_1'' = \frac{R_a}{R_a + R_b} \cdot V_b$$

Assuming  $R_a = R_b = R \therefore V_1'' = V_b/2 \rightarrow ②$

$V_1 = V_1' + V_1''$  ie. addition of equation ① & ②

$$V_1 = \frac{V_a + V_b}{2} \rightarrow ③$$

- The amplifier is non-inverting, so the gain is,

$$AVF = \frac{1 + R_f}{R_1}$$

&  $R_f = R_1 = R$

$$\text{then } AVF = 1 + 1 = 2 \rightarrow ④$$

Op v/g  $V_o = AVF \times V_1$

$$V_o = 2 \left( \frac{V_a + V_b}{2} \right) \quad \text{--- from equation ③ & ④}$$

$$\therefore V_o = V_a + V_b$$

- Thus op v/g is addition of two o/p & it is +ve  $\therefore$  it is known as nonInv. adder.

[i.e.  $\rightarrow$  that is]



## Subtractor

- The circuit of subtractor is same as closed loop differential amp as shown & derived in page No. 12.

Its o/p vlg  $V_o = \frac{R_F}{R_i} (V_1 - V_2)$

- If we substitute  $R_i = R_F = R$  then o/p vlg is,

$$V_o = (V_1 - V_2)$$

So differential amp gets transformed into a subtractor.

→ Differential Amplifiers :-

- Closed looped differential amplifiers:

1) Diff<sup>n</sup> amp<sup>r</sup> with one - op-amp


2) Diff<sup>n</sup> amp<sup>r</sup> with two op-amps:

- Applications :-

- In instrumentation & industrial applications. to amplify diff<sup>n</sup> bet<sup>n</sup> two IIP signals.

- These are preferred because they are better able to reject common mode (noise) voltages than single ZIP ckt.

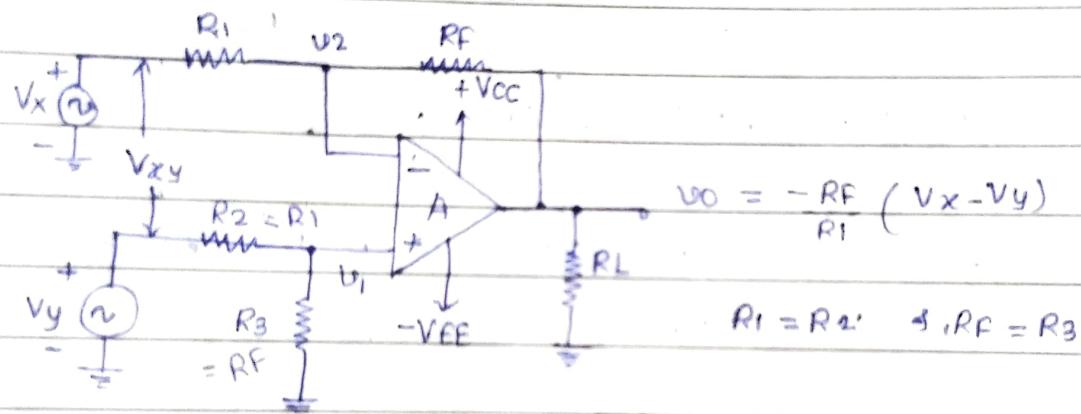1) Differential amp<sup>r</sup> with one op-amp:



- It is a comb<sup>n</sup> of inverting & non-inv amp<sup>r</sup>. ie when  $V_x = 0$  the ckt will be a non-inv amp<sup>r</sup> & when  $V_y = 0$ , the ckt will be a inv. amp<sup>r</sup>.

→ vrg. gain of diff<sup>n</sup> amp<sup>r</sup>:

- It has 2 ZIPs, therefore, use the superposition theorem in order to establish the relationship bet<sup>n</sup> IIPs & OIPs.

when  $V_y = 0V$ , the config. becomes Inv. amp<sup>r</sup>. hence the OIP is due to  $V_x$  only & given by,

$$V_{Ox} = -\frac{RF}{R_1} (V_x)$$

- similarly when  $V_x = 0V$ , non-inv. amp<sup>r</sup>. with a vrg. divider now composed of  $R_2$  &  $R_3$  at the non-inverting zip.

$$\therefore V_1 = \frac{R_3 (V_y)}{R_2 + R_3}$$

& the o/p due to  $V_y$  then is

$$V_{OY} = \left( 1 + \frac{RF}{R_1} \right) \cdot V_I$$

i.e  $V_{OY} = R_3 \left( \frac{R_1 + RF}{R_1} \right) \cdot V_y$

$\therefore R_1 = R_2$  &  $RF = R_3$ ,

$$V_{OY} = \frac{RF(V_y)}{R_1}$$

i.e  $V_O = V_{OX} + V_{OY}$ .

$$= -\frac{RF}{R_1} (V_x - V_y) = -\frac{RF(V_{xy})}{R_1}$$

or the vtg. gain , 
$$\boxed{AD = \frac{V_O}{V_{xy}} = -\frac{RF}{R_1}} \quad \text{--- (1)}$$

- The gain of the diff<sup>n</sup> amp<sup>r</sup> is the same as that of the inverting amp<sup>r</sup>.

→ IIP resistance of the diff<sup>n</sup> amp<sup>r</sup>: :- ( $R_{IF}$ )

- Is the resi. determined looking into either one of the two IIP terminals with the other grounded.

- ∵ with  $V_y = 0V$ , inv. amp<sup>r</sup>.

$$R_{IFX} \approx R_1$$

- similarly,  $V_x = 0V$ , non-inv. amp<sup>r</sup>.

$$R_{IFY} \approx (R_2 + R_3)$$


- we can see that both the resistances are not same.

- To make these resi. same, we have to modify the ckt.

- To perform properly this ckt both  $R_1$  &  $(R_2 + R_3)$  can be made much larger than the source resi. so that the loading at the signal sources does not occur.

⇒ Differential amp. with two op-amps:-

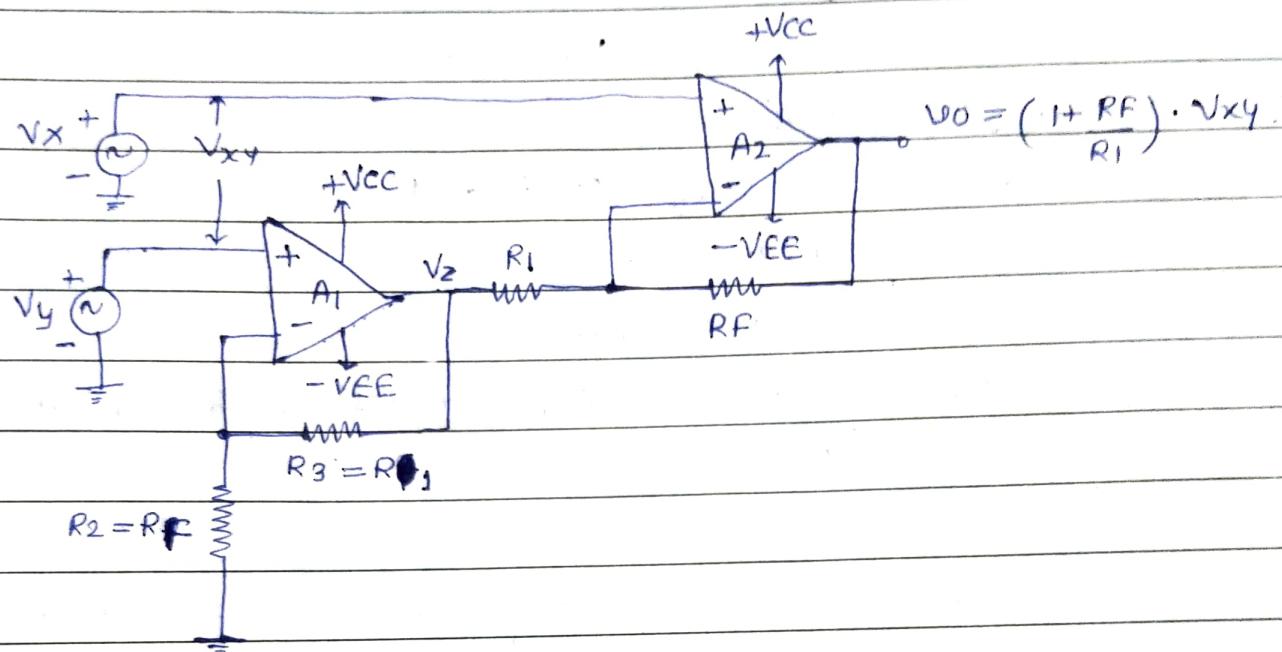- To ↑ gain & OIP resi. we can use 2 op-amps in diff<sup>n</sup> amp.
- This char. of this amp<sup>r</sup> are same → those of non-inv. amp<sup>r</sup>.



→ Voltage gain →

- This ckt is composed of two stages:

1) The non-inverting amp<sup>r</sup> &

2) The diff<sup>n</sup> amp<sup>r</sup> with unequal gains,

- By finding the gain of two stages, we can obtain overall gain of the ckt as follows:

The OIP V<sub>2</sub> of the 1st stage is,

$$V_2 = \left(1 + \frac{R_3}{R_2}\right) \cdot V_y$$

By applying the superposition theorem to the 2nd stage, we can obtain the output voltage.

$$V_O = -\frac{R_F(V_2)}{R_1} + \left(1 + \frac{R_F}{R_1}\right) \cdot V_x$$

Substituting the value of V<sub>2</sub> from above eq<sup>n</sup> we get,

$$V_O = -\left(\frac{R_F}{R_1}\right) \cdot \left(1 + \frac{R_3}{R_2}\right) \cdot V_y + \left(1 + \frac{R_F}{R_1}\right) \cdot V_x$$

Since R<sub>1</sub> = R<sub>3</sub> & R<sub>F</sub> = R<sub>2</sub>,

$$V_o = \frac{(1+RF)}{R_1} \cdot (V_x - V_y)$$

$$\therefore A_D = \frac{V_o}{V_{xy}} = \frac{1+RF}{R_1}$$

where  $V_{xy} = V_x - V_y$ .

### INPUT Resistance:

- At the 1st stage  $A_1$  is a non-inv. amp.

∴ its IIP resi is,

$$R_{ify} = R_i(1+AB)$$

where  $R_i = \text{open-loop ZIP resi of the op-amp}$ .

$$B = R_2$$

$$R_2 + R_3$$

Similarly, with  $V_y = 0V$ ,  $A_2$  is also non-inv amp.

$$\therefore R_{ifx} = R_i(1+AB)$$

where  $R_i = \text{open-loop ZIP resi of the op-amp}$ .

$$B = R_1$$

$$R_1 + RF$$

- Here we use  $R_1 = R_3$  &  $RF = R_2$ , then also  $R_{ify} \neq R_{ifx}$

& hence the loading of ZIP source occur. i.e the o/p signal may be smaller in amplitude than expected.


- This reduction in o/p is the drawback of diff<sup>n</sup> compr.

- To overcome this, with proper selection of components, both  $R_{ify}$  &  $R_{ifx}$  can be made much larger than the source resistances so that the loading of the ZIP does not occur.

## ⇒ Instrumentation amp<sup>r</sup>:

- In many industrial & consumer applications the measurement & control of physical conditions are very important.
- Generally a transducer is used at the measuring site to obtain the required information easily & safely.
- Transducer converts one form of energy into another.
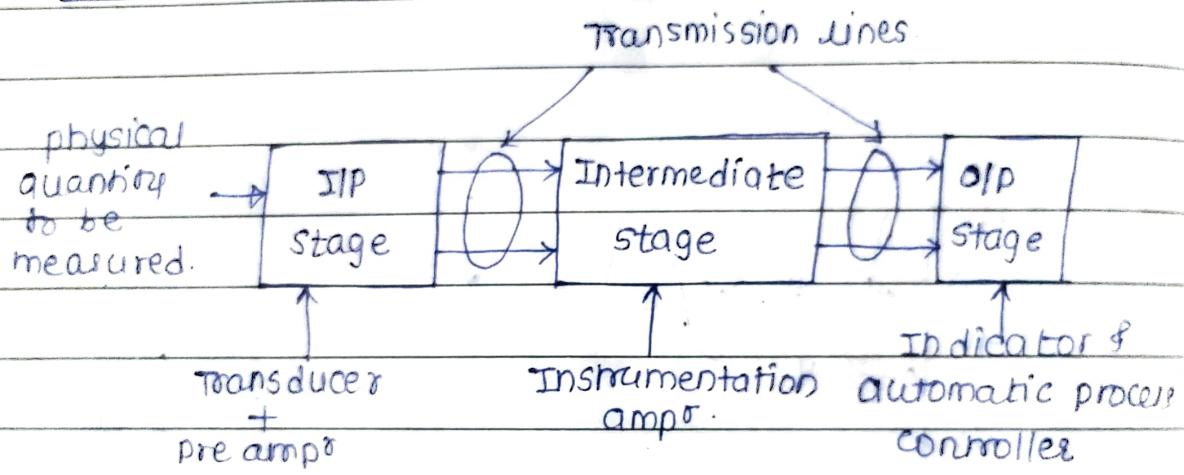
## ⇒ Block dia. of an instrumentation system:-




- To amplify the low level OIP signal at the transducer so that it can drive the indicator or display is the major func of the instrumentation amp<sup>r</sup>.
- ie IA is intended for precise, low level signal amplification where low noise, low thermal & time drift, high IIP resistance & accurate closed-loop gain are required.
- Besides that, low power consumption, high CMRR & high slew rate are desirable for superior performance.

## ⇒ IA circuits:-

- Using one op-amp
- Using two op-amps


(on a new page)

IA using one op-amp :-

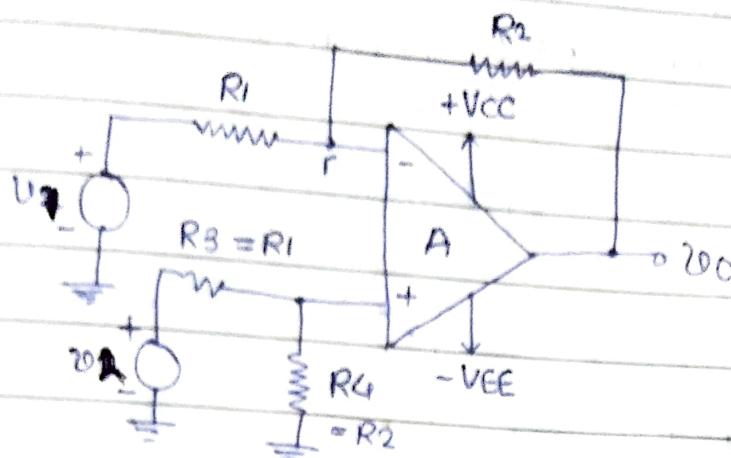

- It is same as a diff<sup>n</sup> amp<sup>r</sup>. (sub)
- when gain = 1 ,  $V_O = V_1 - V_2$

IA with 2 op-amps :-

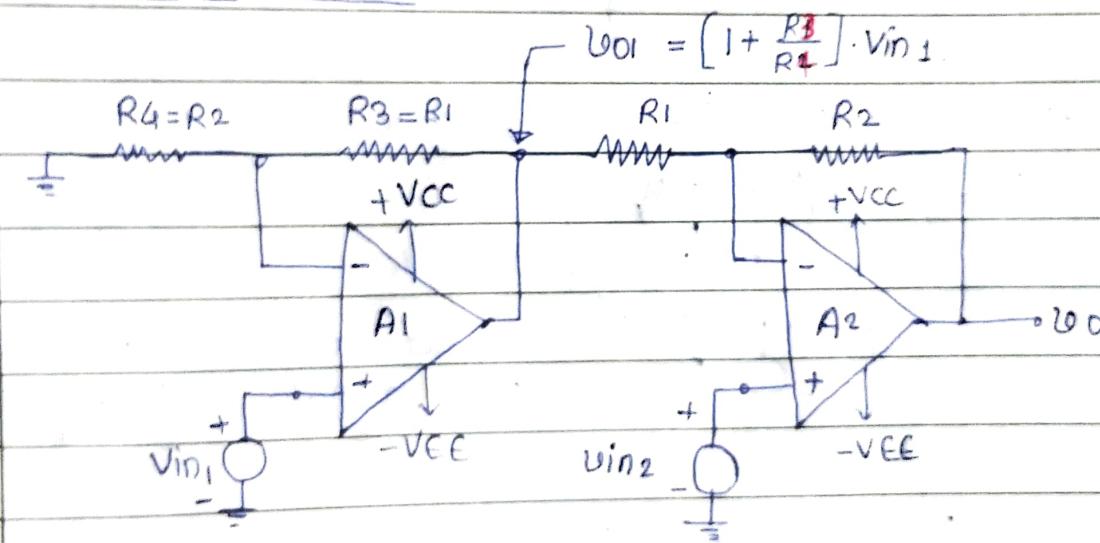

- This config. is used when the cost of ckt is to be reduced.

- A<sub>1</sub> is a non-inv amp<sup>r</sup>,

hence its OIP utg. is given by,

$$V_{O1} = \left[ 1 + \frac{R3}{R4} \right] \cdot V_{in1} \rightarrow ①$$

-  $V_{O1}$  is applied at inv terminal of A<sub>2</sub>.

Hence A<sub>2</sub> will act as a difference amp<sup>r</sup>.

The OIP can be obtained by using superposition theorem.


Consider  $v_{o1}$  &  $v_{o2}$  separately.

- OIP due to  $v_{in1}$  if  $v_{o1}'$  can be calculated as,

$$v_{o1}' = -\frac{R_F}{R_1} \left[ 1 + \frac{R_3}{R_4} \right] \cdot v_{in1}.$$

$$\therefore v_{o1} = \left[ 1 + \frac{R_3}{R_4} \right] \cdot v_{in1}.$$

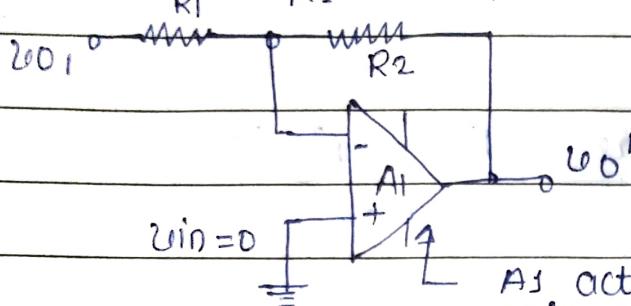
$$\therefore v_{o1}' = -\frac{R_2}{R_1} \cdot \left[ 1 + \frac{R_3}{R_4} \right] \cdot v_{in1} \rightarrow (2)$$



As acts as an inv. amp<sup>r</sup> with gain of  $R_2/R_1$ .

: OIP due to  $v_{in1}$  only :-

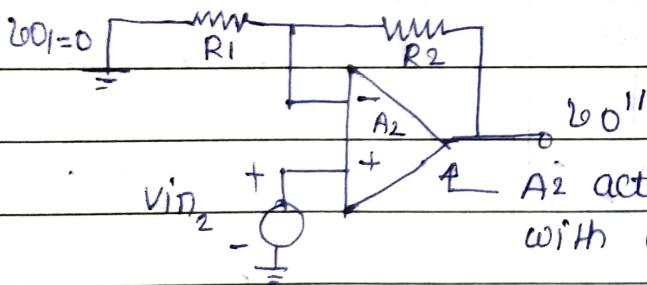→ OIP due to  $v_{in1}$  is  $v_{o1}''$  & is given as,



A<sub>2</sub> acts as a non-inverting amp<sup>r</sup> with a gain of  $(1 + \frac{R_3}{R_4})$ .

$$v_{o1}'' = \left[ 1 + \frac{R_3}{R_4} \right] \cdot v_{in2}. \rightarrow (3)$$

Hence the OIP vrg.

$$v_o = v_{o1}' + v_{o1}''$$

From eq<sup>n</sup> (2) & (3) we get,

$$v_o = -\frac{R_2}{R_1} \left[ 1 + \frac{R_3}{R_4} \right] \cdot v_{in1} + \left[ 1 + \frac{R_3}{R_4} \right] \cdot v_{in2}$$

$$= \left[ 1 + \frac{R_3}{R_4} \right] \cdot v_{in2} - \left[ \frac{R_2}{R_1} \left( 1 + \frac{R_3}{R_4} \right) \right] \cdot v_{in1}$$

Take out  $1 + (R_2/R_1)$  common from R.H.S.

$$V_O = \frac{1+R_2}{R_1} \left[ V_{in2} - \frac{1 + (R_3/R_4) \cdot V_{in1}}{1 + (R_1/R_2)} \right].$$

The C.R.C will work as a true difference amp if

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \quad \text{or} \quad \frac{1+R_1}{R_2} = \frac{1+R_3}{R_4}.$$


when this condition is true,

$$V_O = \left[ 1 + \frac{R_2}{R_1} \right] \cdot (V_{in2} - V_{in1}) \rightarrow (4).$$

→ Advantages of dual op-amp IA:-

- High IIP resi
- low OIP resi
- CMRR can be maximized & unbalance can be minimized if we replace one of the resistors (say  $R_6$ ) by a trimmer i.e variable resistor.

→ IA using 2 op-amps with variable gain:

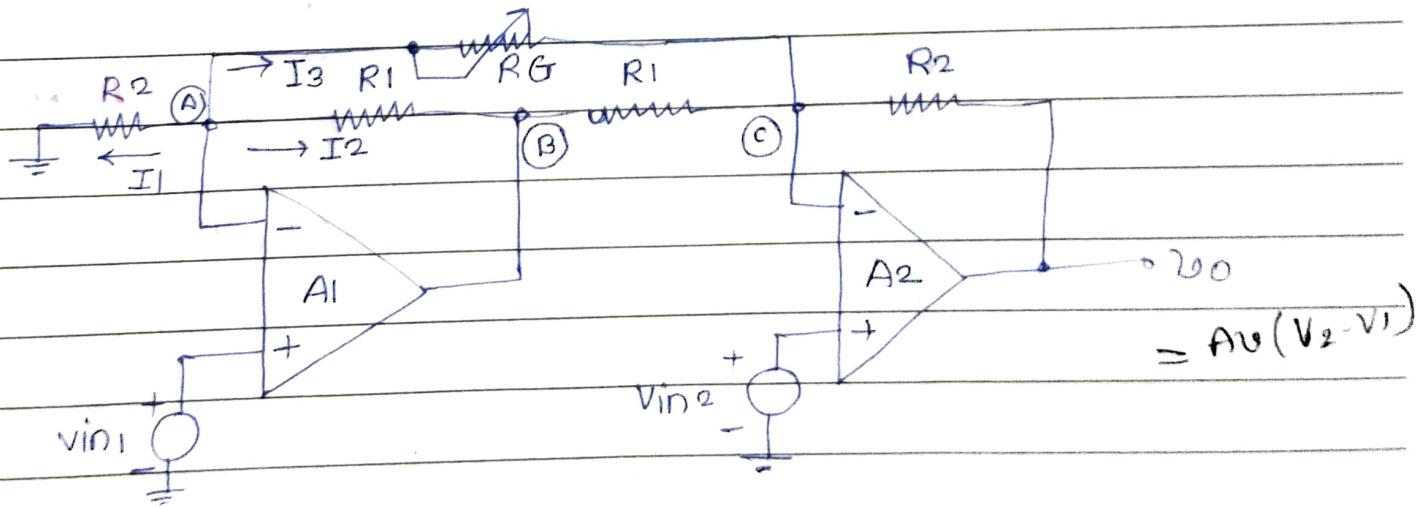

→ Variable resistor  $R_G$  is connected in bet<sup>n</sup> inverting terminals at A1 & A2.

gain is given by,

$$\text{gain} = A_v = 1 + \frac{R_2}{R_1} + \frac{2R_2}{R_G}$$

- By varying  $R_G$  we can vary the gain.

⇒ Advantages:

- Easy to vary the gain.


- Variation in gain does not affect the performance of the amp. as CMRR does not change with change in gain.

⇒ Disadvantages:

- CMRR ↓ with ↑ freq.

-  $R_1$  &  $R_2$  should match exactly.

⇒ IA using 3-OP-amps:

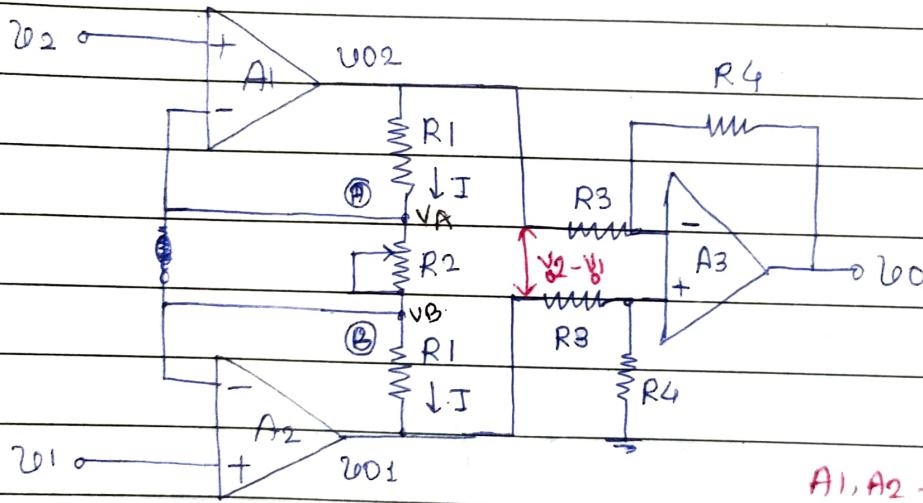

A1, A2 - Vtg. follower.

→ Voltage is given as,

Use virtual ground concept short concept.

$$\text{i.e } v_0 = \text{AF} \cdot v_{\text{in}}$$

$$v_0 = A \cdot v_{\text{id}}$$

$$v_{\text{id}} = v_0/A$$

$$\therefore A \text{ is } \gg, v_{\text{id}} = 0$$

$$\text{i.e } v_1 - v_2 = 0 \quad \therefore v_1 = v_2$$

means  $v_1$  &  $v_2$  are at same potential.

i.e when we short two terminals, they will be at equipotential.

similarly here as  $v_1 = v_2$  we can say that

$V_1$  &  $V_2$  are virtually shorted, even though they are not actually shorted, they are at same potential.

- This phenomenon is called as virtual short concept.

Using virtual short concept,


$$V_A = V_2 \quad \& \quad V_B = V_1$$

Hence expression for current  $I$  is,

$$I = \frac{V_A - V_B}{R_2} = \frac{V_2 - V_1}{R_2}$$

O/P utg. of op-amp  $A_1$  is given by,

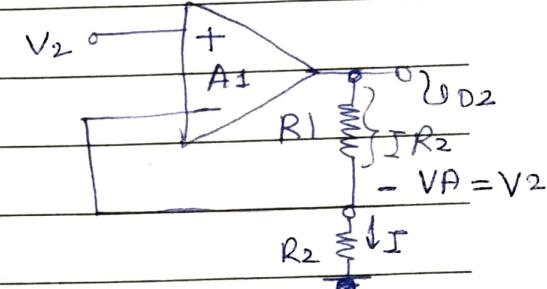
$$\begin{aligned} V_{O2} &= V_A + I R_1 = V_2 + I R_1 \\ &= V_2 + \frac{(V_2 - V_1) \times R_1}{R_2} \end{aligned}$$



$$= \frac{V_2 R_2 + V_2 R_1 - V_1 R_1}{R_2} = \frac{(R_1 + R_2) \cdot V_2 - R_1 V_1}{R_2}$$

O/P of O/P amp  $A_2$  is given as,
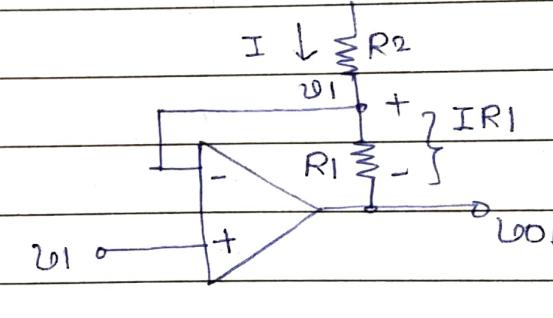
$$\begin{aligned} V_{O1} &= V_B - I R_1 \\ &= V_1 - I R_1 \\ &= V_1 - \frac{(V_2 - V_1) \times R_1}{R_2} \end{aligned}$$



$$= \frac{V_1 R_2 - V_2 R_1 + V_1 R_1}{R_2} = \frac{(R_1 + R_2) \cdot V_1 - R_1 V_2}{R_2}$$

Hence the OIP of the first stage is given by,

$$\begin{aligned} V_{O2} - V_{O1} &= \frac{(R_1 + R_2) \cdot V_2 - R_1 V_1}{R_2} - \frac{(R_1 + R_2) \cdot V_1 - R_1 V_2}{R_2} \\ &= \frac{(R_1 + R_2) \cdot (V_2 - V_1) + R_1 (V_2 - V_1)}{R_2} = \frac{2(R_1 + R_2) \cdot (V_2 - V_1)}{R_2} \end{aligned}$$

$$\therefore V_{O2} - V_{O1} = \left[ 1 + \frac{2R_1}{R_2} \right] \cdot (V_2 - V_1)$$

Hence the gain of the 1st stage is given by,

$$AV_1 = \frac{V_{O2} - V_{O1}}{V_2 - V_1} = 1 + \frac{2R_1}{R_2}$$

- The 2nd stage is a difference amp<sup>r</sup> with a gain of,

$$AV_2 = \frac{R_4}{R_3} \quad V_O = -\frac{R_4}{R_3} (V_1 - V_2) = \frac{R_4}{R_3} (V_2 - V_1)$$

- Hence the overall gain  $A_U$  of the 3 op-amp IA is given by,

$$A_U = A_{U1} \times A_{U2}.$$

$$\therefore A_U = \left[ 1 + \frac{2R_1}{R_2} \right] \times \frac{R_4}{R_3}.$$

- Hence by using a variable resistor  $R_2$  the overall gain can be easily & linearly varied.

- The OIP utg is then given by,

$$V_O = A_U \times (V_1 - V_2)$$

- These IA using 3 op-amps are available in IC form. e.g. IC AD 522 or INA 101

- Disadvantages of IA using 3 op-amps.

- gain changes due to ageing of components & due to change in temperature.

- gain depends upon so many resistances.

#### $\Rightarrow$ Advantages of IA $\Rightarrow$

- Using a single variable resistor we can adjust the gain of the IA.
- IP impedance is very high.
- OIP impedance is very low
- good capacity to reject common mode signals such as noise.



## Applications :

- Temperature indicator
- Temp. controller
- Pressure monitoring & control
- Electronic weighing scale.
- Light intensity meter.