

## - Comparator characteristic:-

### 1. Speed of operation:

- OIP of comparator must switch rapidly bet<sup>n</sup> saturation levels & also respond instantly to any change of conditions at its ZIP.
- i.e BW should be high . ∴ BW ↑, speed ↑.
- By using positive feedback we can ↑ speed of operation.

### 2. Accuracy:-

- Depends upon v<sub>tg</sub> gain, CMRR, IIP offsets & thermal drift.
- when v<sub>tg</sub> gain is high, less IIP is also cause the change in OIP saturation levels.
- CMRR ↑, noise at ZIPS ↓. Hence false triggering is avoided.
- To minimize offset problems, I<sub>i0</sub> & V<sub>i0</sub> must be negligible. also changes in these offsets due to temp. variations should be very slight.
- comparator is one form of ADC.


### 3. Compatibility of OIP:

#### \* Limitations of op-amp as comparator:-

- As we have designed op-amps for amplification purpose, these are having high gain. Hence OIP is very high. & hence not compatible with a particular logic family such as TTL, which requires OIP v<sub>gs</sub> at +SV or OV. ∴ to keep OIP v<sub>gs</sub> swing within specified limits, we have to use extra

⇒ BASIC COMPARATOR :-

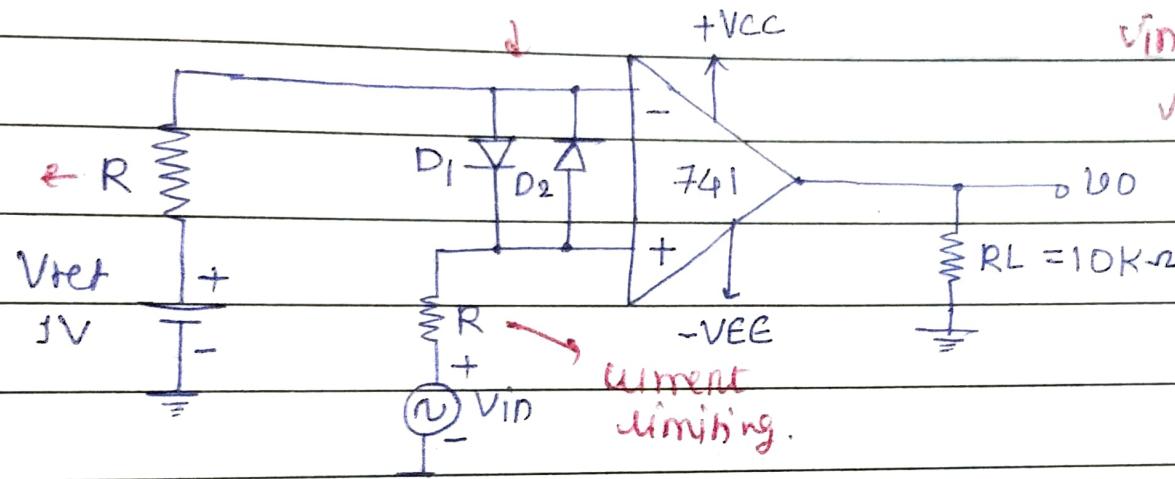protection diodes from excess IIP Vtg ( $V_{ID} \rightarrow 0.7V$ ) <sup>clamped</sup>  $\rightarrow$  clamping diodes



$$V_{in} < V_{ref}, V_o = +V_{sat}$$


$$V_{in} > V_{ref}, V_o = -V_{sat}$$

- OP-amp is used as a comparator.

- A fixed ref. vtg.  $V_{ref}$  of 1V is applied to the (-) IIP & AC IIP is applied at (+) IIP.

- Hence ckt. is called as non-inv. comp<sup>T</sup>. comparator.

- when  $V_{in}$  is less than  $V_{ref}$ , the o/p  $V_o$  is at  $-V_{sat}$  ( $\approx -V_{dd}$ ) because the vrg. at the (-) input is higher than that at the (+) input.
- when  $V_{in}$  is greater than  $V_{ref}$ , the (+) input becomes +ve w.r.t the (-) input, the  $V_o$  goes to  $+V_{sat}$  ( $\approx +V_{dd}$ ).
- Thus  $V_o$  changes from one saturation level to another whenever  $V_{in} \approx V_{ref}$ .
- In short, Comparator is a type of ADC.
- Comparator sometimes called as a voltage-level detector because, for a desired value of  $V_{ref}$ , the vrg. level of the IIP  $V_{in}$  can be detected.


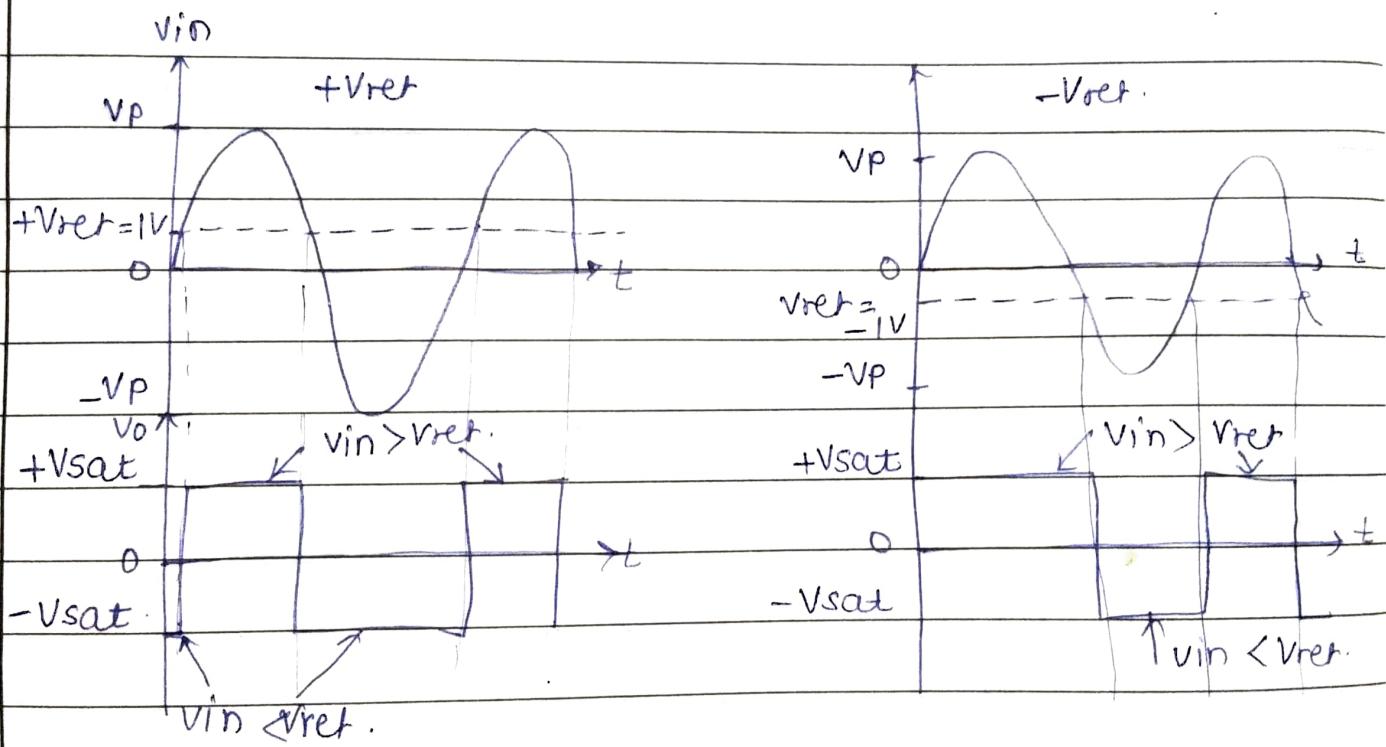


- Diodes D<sub>1</sub> & D<sub>2</sub> protect the op-amp from damage due to excessive IIP vrg.  $V_{in}$ . Because of these diodes, the difference IIP vrg. v<sub>id</sub> of the op-amp is clamped to either 0.7V or -0.7V. Hence diodes are called as clamping diodes.
- R in series with  $V_{in}$  is used to limit the current through D<sub>1</sub> & D<sub>2</sub>.

- To reduce offset problems, a resistance  $R_{\text{ref}} \approx R$  is connected bet<sup>n</sup> the (-) input &  $V_{\text{ref}}$ .
- If  $V_{\text{ref}}$  is -ve, o/p is as shown in fig.  
i.e when  $v_{\text{in}} > V_{\text{ref}}$ ,  $v_o$  is at  $+V_{\text{sat}}$  & when  $v_{\text{in}} < V_{\text{ref}}$ ,  $v_o$  is at  $-V_{\text{sat}}$ .
- Hence to take switching action,  $v_{\text{in}}$  must be large enough.

$\Rightarrow$  Inverting comparator  $\rightarrow$



(5)

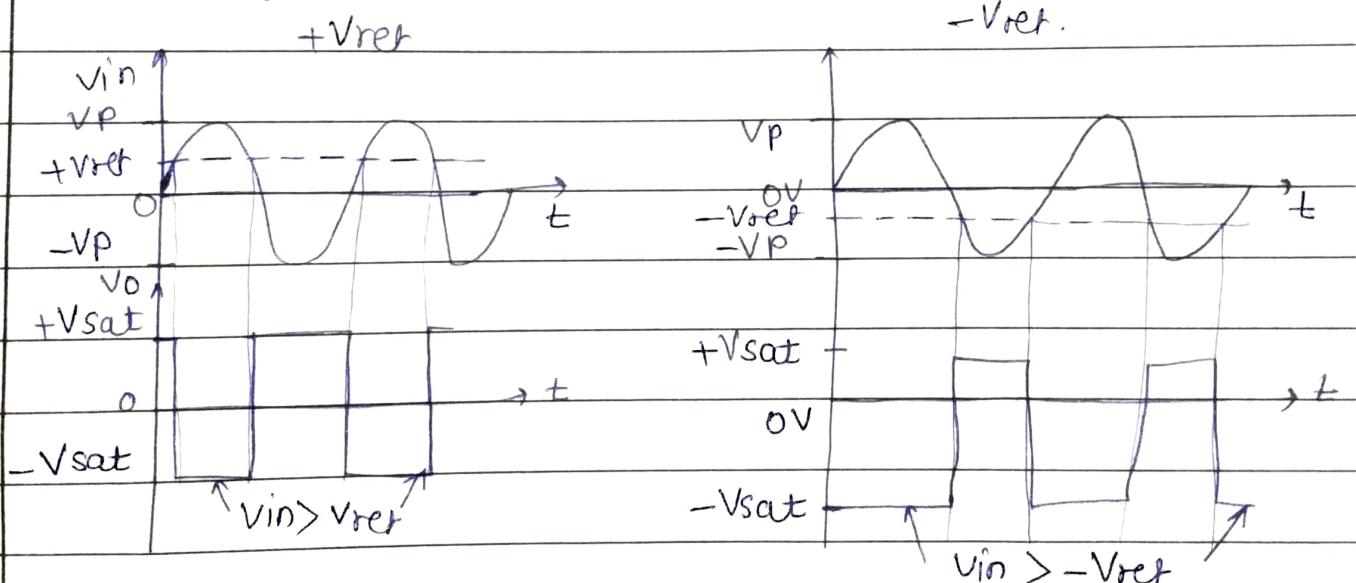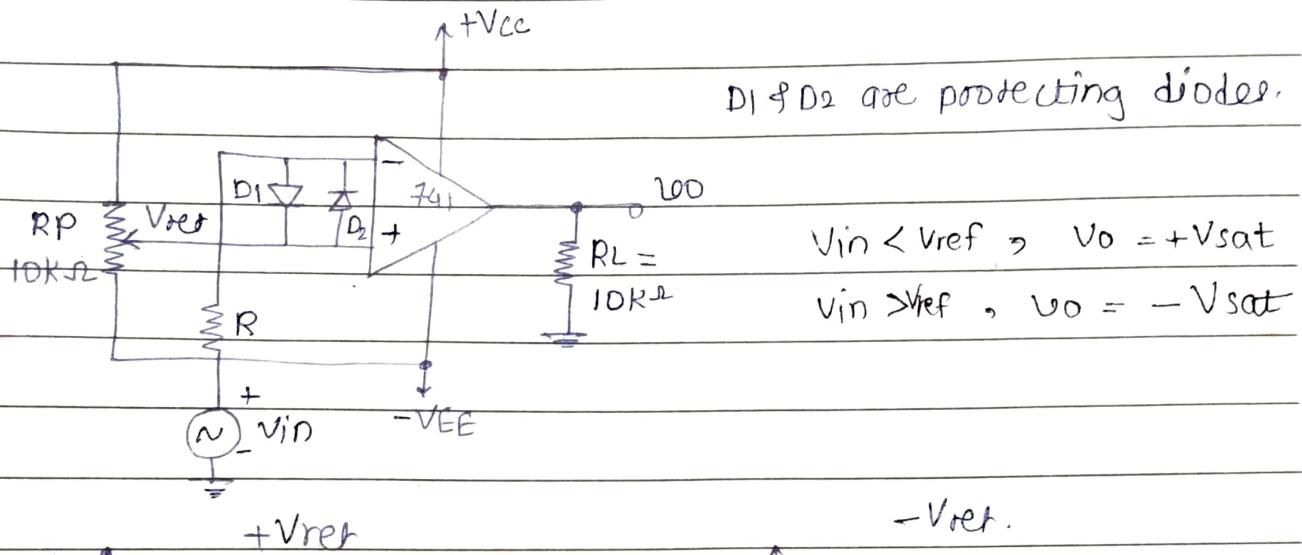

- $V_{\text{ref}}$  is obtained by using a 10kΩ pot that forms a divider with the dc supply vtgs  $+V_{\text{cc}}$  &  $-V_{\text{ee}}$  & the wiper connected to the (+) input.
- As the wiper is moved toward  $-V_{\text{ee}}$ ,  $V_{\text{ref}}$  becomes more -ve, while if it is moved toward  $+V_{\text{cc}}$ ,  $V_{\text{ref}}$  becomes

No.  
more -ve, while if it is moved toward  $+V_{CC}$ ,  $V_{ref}$  becomes more +ve. Thus a  $V_{ref}$  of a desired amplitude & polarity can be obtained by simply adjusting the  $10k\Omega$  pot.



## ZERO-CROSSING DETECTOR

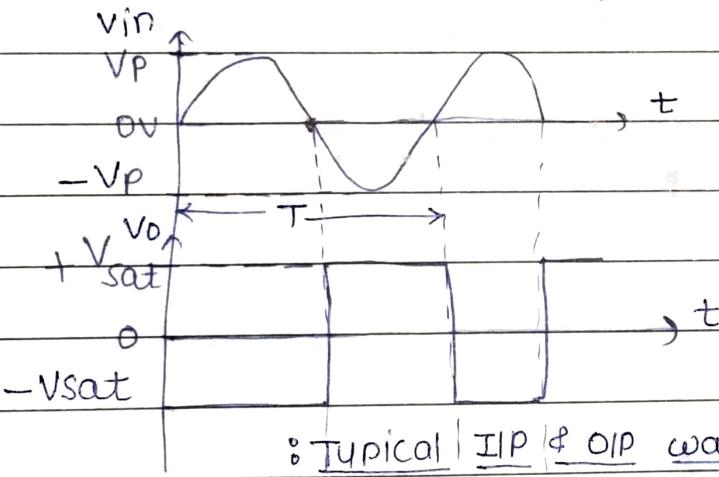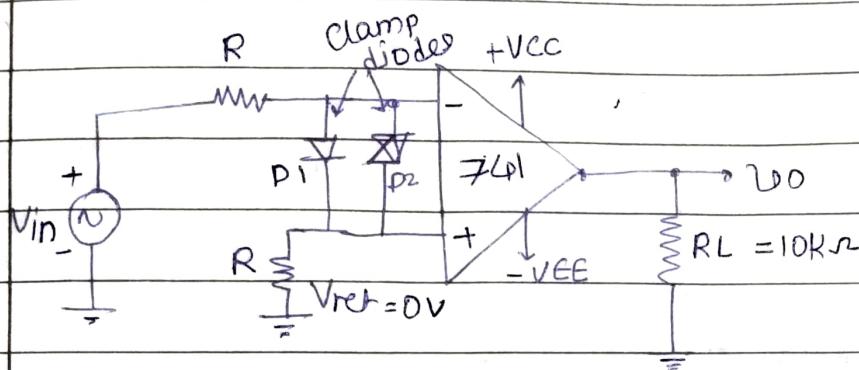

: Typical IIP & OIP waveforms :

- This is the application of comparator. Also called as sine wave to square wave converter.
- For this  $V_{ref} = 0$ .
- $V_O$  is driven into -ve saturation when  $V_{in}$  passes through zero in the positive direction.
- When  $V_{in}$  passes thr' zero in the -ve direction, the OIP  $V_O$  switches & saturates +vely.
- Regenerative or tee fil :-
- Used to change faster & eliminate any false output transitions due to noise signals at the input.


## → Non-Inv Comparator

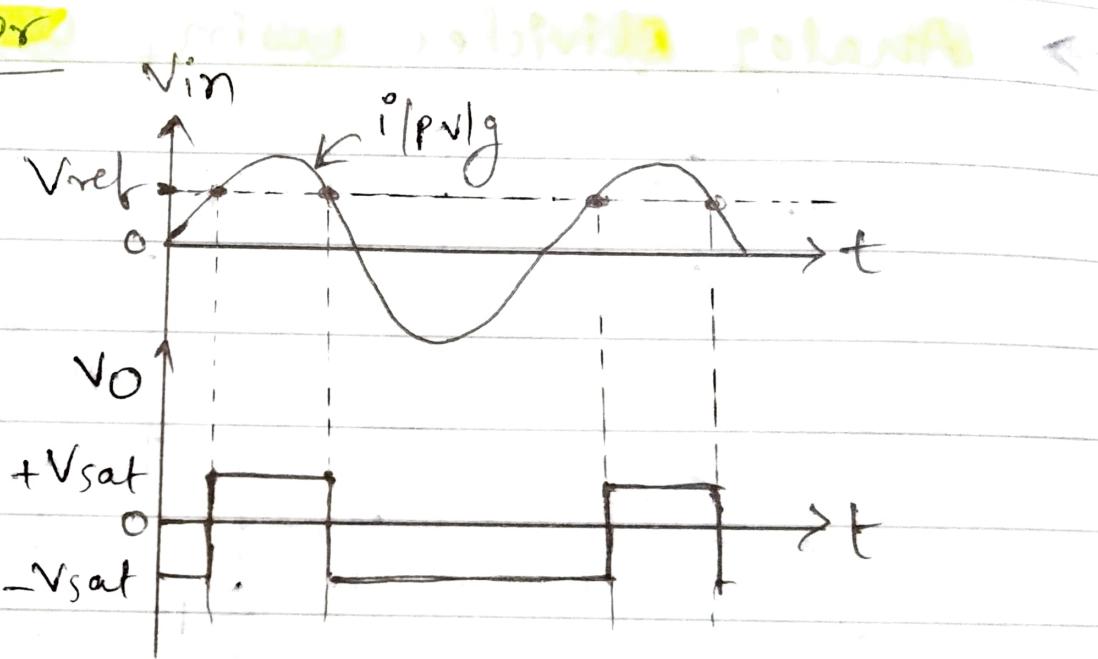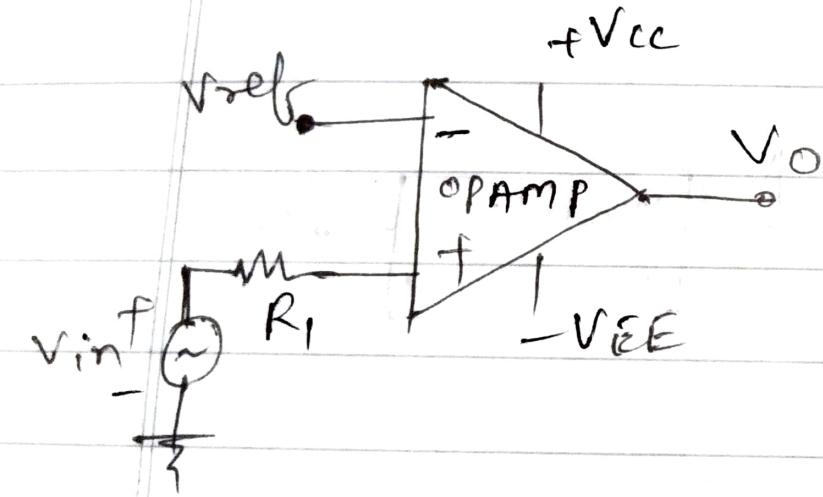


➤ Here positive dc vlg is applied to inv. terminal & ac sig is applied to non-inv. terminal.

$I/p vlg \quad V_d = V_{in} - V_{ref}$ .

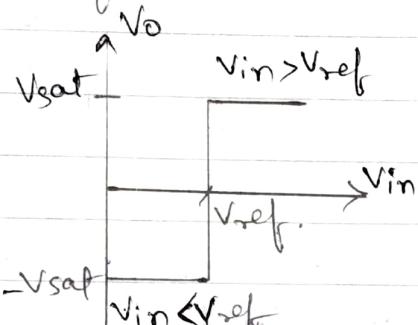
- When  $V_{in}$  is less than  $V_{ref}$ , inv. terminal is at higher potential than non-inv. terminal.  $\therefore V_{d1}$  is -ve & OPAMP o/p will swing to  $-V_{sat}$  volts.
  - When  $V_{in}$  is greater than  $V_{ref}$ , non-inv terminal is at higher potential than inv. terminal.  $\therefore V_{d1}$  is +ve & the OPAMP o/p will swing to  $+V_{sat}$  volts.
- Transfer characteristics



For +ve ref.


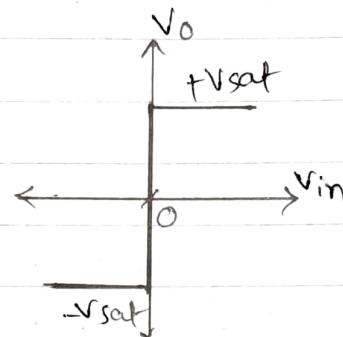


$V_{ref} = 0$

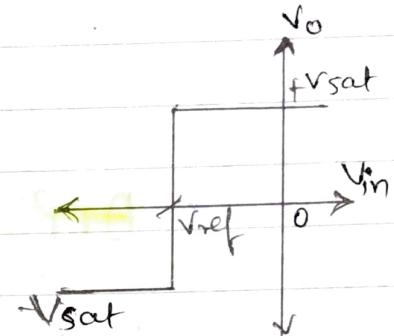

$V_{ref} = -Ve$




### → Inverting Comparator

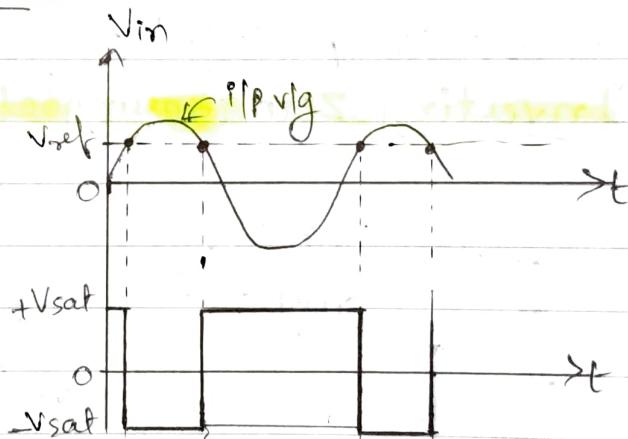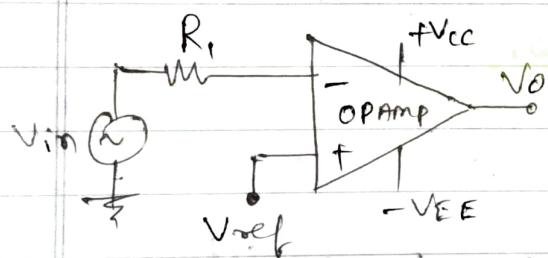

- Here differential i/p vlg  $V_d = \text{sgn}(V_{ref} - V_{in})$ .
- Also here i/p is applied to inv. terminal & reference vlg is applied to non-inv. terminal.
- When  $V_{in}$  is less than  $V_{ref}$ , vlg at non-inv. terminal is higher than vlg at inv. terminal. This makes ' $V_d$ ' +ve & OPAMP o/p will swing to  $+V_{sat}$ .
- When  $V_{in}$  is greater than  $V_{ref}$ , vlg at non-inv terminal is less than vlg at inv. terminal. This makes ' $V_d$ '

-ve & opamp o/p will be -Vsat.

### Transfer characteristics

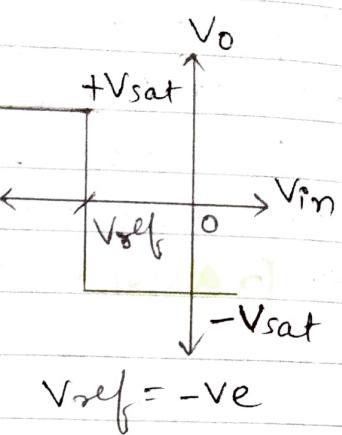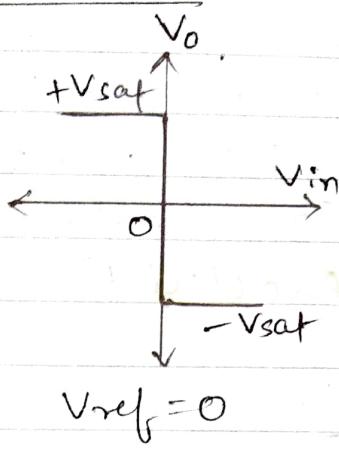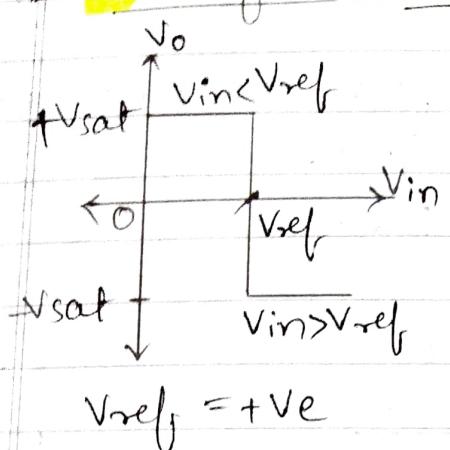


### App^n

Zero crossing detector, window comparator, Level detector, phase detector, schmitt trigger, peak detector.

### Zero Crossing Detector


This is nothing but the comparator in which we are comparing i/p vlg with  $V_{ref} = 0V$ .

### Inverting zero crossing detector

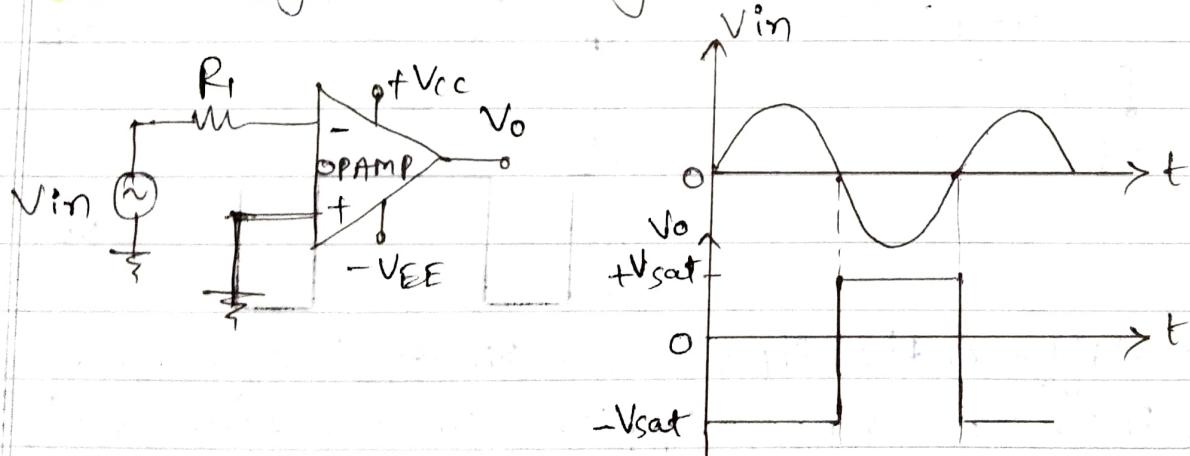



- Here i/p vlg is applied to inv. terminal & non-inv. terminal is connected to ground.
- When  $V_{in} > 0$  then vlg at inv. terminal is more than non-inv. & o/p is swings  $-V_{sat}$ .
- When  $V_{in} < 0$  ie crosses zero then vlg at inv. terminal becomes less than non-inv. & o/p swing to  $+V_{sat}$ .

→ Non-Inv. Zero Crossing detector.

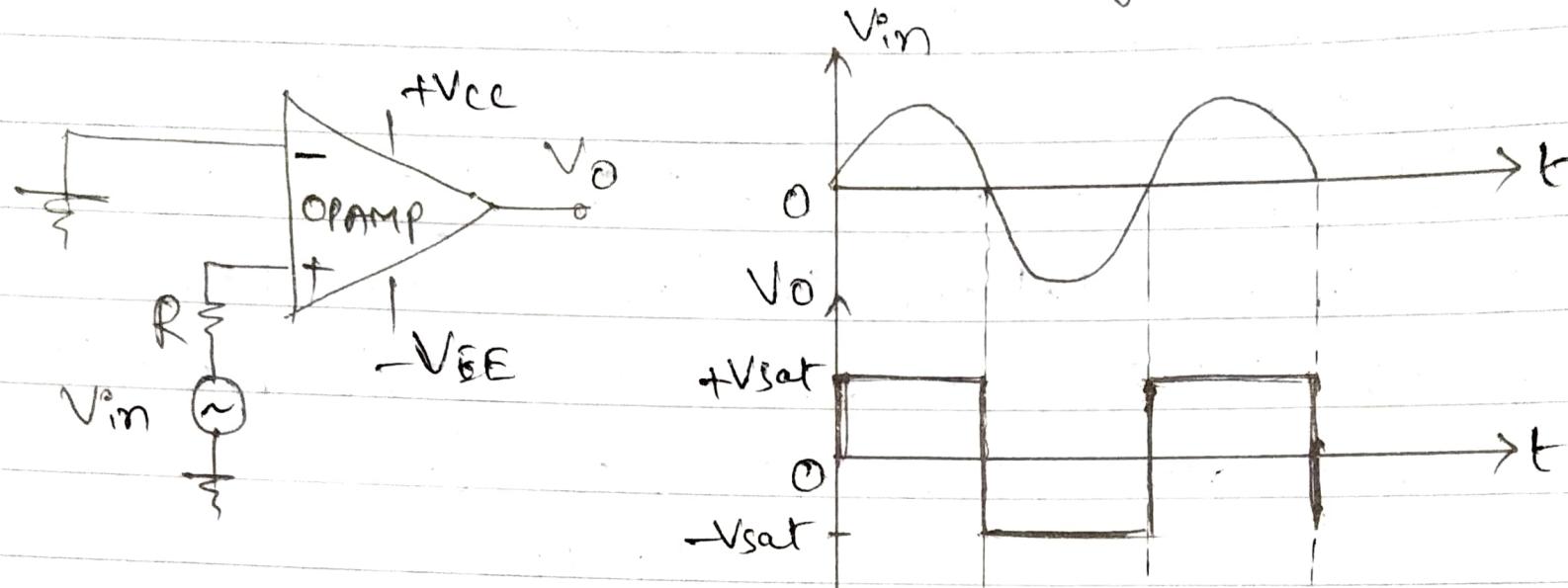

- In this if  $V_{in}$  is applied to non-inv. terminal & inv. terminal is connected to ground.
  - When  $V_{in} > 0$  then  $V_{lg}$  at non-inv. terminal is more than inv. terminal & opamp swings to  $+V_{sat}$ .
  - When  $V_{in} < 0$  i.e. when it crosses zero then  $V_{lg}$  at non-inv. terminal becomes less than inv. & opamp swings to  $-V_{sat}$ .
- Applications
- Synchronizing circuit, Square wave generator.

## Window Detector

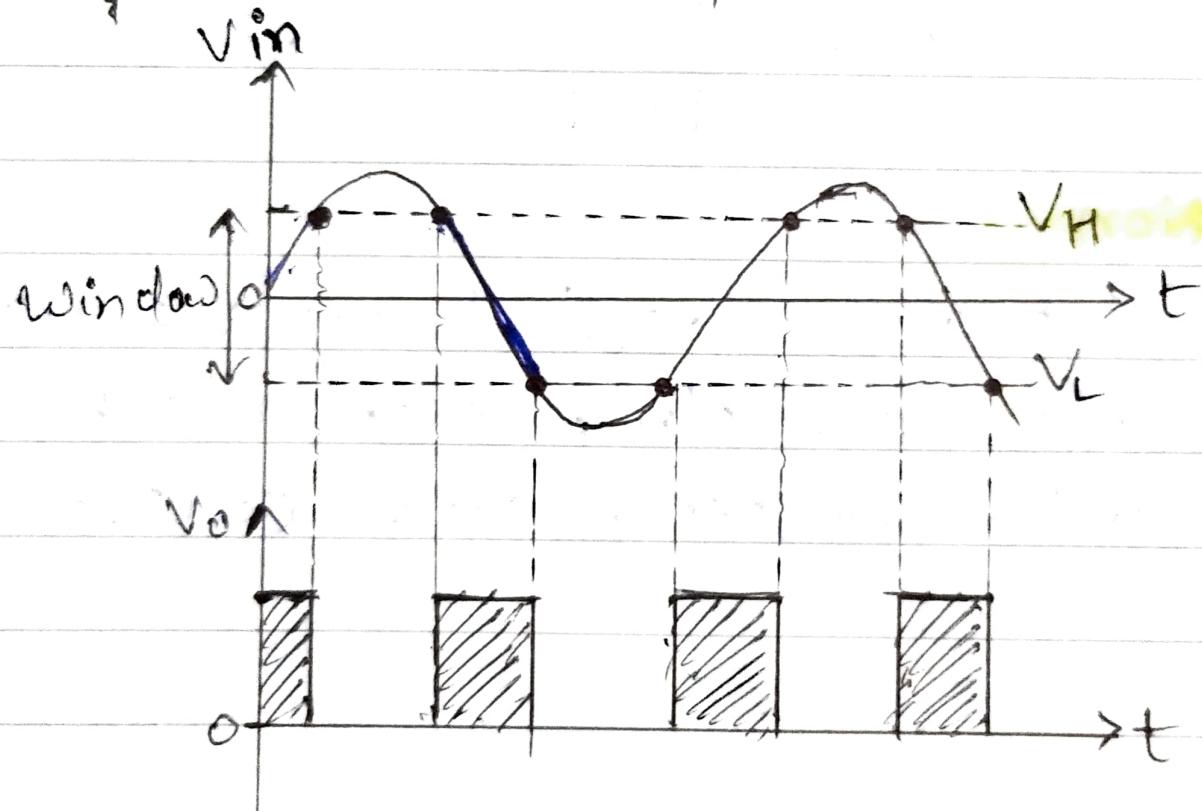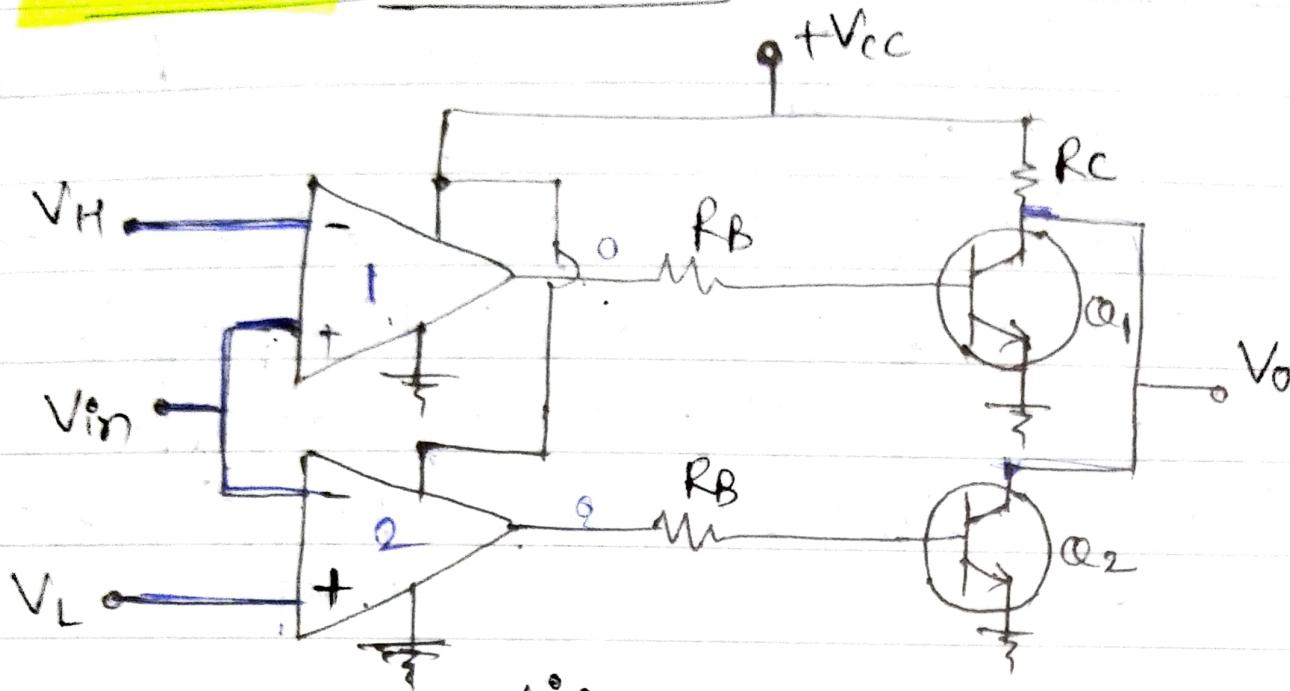

- $V_H$  &  $V_L$  are two reference vgs with  $V_H > V_L$  &  $V_{in}$  as input vlg. The o/p of two comparators are applied to two transistors which operate as a switches. The o/p vlg is obtained at common collector terminal of two Transistor.
- If  $V_{in}$  is between two ref. vlg ie.  $V_L < V_{in} < V_H$  then o/p of both comparators will be low. So both the transistor will remain in off state. So the collector vlg ie. o/p vlg will be equal to +Vcc.  
 $\therefore V_o = +Vcc \text{ for } V_L < V_{in} < V_H.$
- If  $V_{in}$  is less than  $V_L$ , the o/p of comparator 1 will be low & comparator 2 will be high. This will turn off  $\text{Q}_1$  but saturate  $\text{Q}_2$  & o/p vlg will be  $V_{CE(sat)}$  ie. low.  
 $\therefore V_o = V_{CE(sat)} = \text{low for } V_{in} < V_L.$
- If  $V_{in}$  is greater than  $V_H$ , then o/p of comparator 1 will be high & comparator 2 will be low. Thus  $\text{Q}_1$  will saturate &  $\text{Q}_2$  will remain off. The o/p vlg will be  $V_{CE(sat)}$  ie. low.  
 $\therefore V_o = V_{CE(sat)} = \text{low for } V_{in} > V_H.$

From these cases we can say that we will get high vlg when i/p vlg is within window, whereas low o/p vlg indicates that i/p vlg is out of window.

### Application

- Level detector.
- Industrial alarm.
- Digital Computer.
- Barograph indicators.
- Speed indicators.