

Contents

Preface

xi

Roadmap to the Syllabus

xiii

1. BASIC CIRCUIT CONCEPTS

1.1

- 1.1 Introduction 1.1
- 1.2 Resistance 1.1
- 1.3 Inductance 1.2
- 1.4 Capacitance 1.3
- 1.5 Sources 1.4
- 1.6 Some Definitions 1.6
- 1.7 Series and Parallel Combination of Resistors 1.7
- 1.8 Series and Parallel Combination of Inductors 1.9
- 1.9 Series and Parallel Combination of Capacitors 1.10
- 1.10 Star-Delta Transformation 1.10
- 1.11 Source Transformation 1.13
- 1.12 Source Shifting 1.19
 - Exercises* 1.21
 - Objective-Type Questions* 1.22
 - Answers to Objective-Type Questions* 1.23

2. ANALYSIS OF DC CIRCUITS

2.1

- 2.1 Introduction 2.1
- 2.2 Kirchhoff's Laws 2.1
- 2.3 Mesh Analysis 2.2
- 2.4 Supermesh Analysis 2.15
- 2.5 Node Analysis 2.23
- 2.6 Supernode Analysis 2.36
- 2.7 Superposition Theorem 2.42
- 2.8 Thevenin's Theorem 2.62
- 2.9 Norton's Theorem 2.82
- 2.10 Maximum Power Transfer Theorem 2.106
- 2.11 Reciprocity Theorem 2.118
- 2.12 Millman's Theorem 2.122
 - Exercises* 2.127
 - Objective-Type Questions* 2.130
 - Answers to Objective-Type Questions* 2.132

3. ANALYSIS OF AC CIRCUITS

3.1

- 3.1 Introduction 3.1
- 3.2 Mesh analysis 3.1

- 3.3 Node Analysis 3.9
- 3.4 Superposition Theorem 3.14
- 3.5 Thevenin's Theorem 3.27
- 3.6 Norton's Theorem 3.41
- 3.7 Maximum Power Transfer Theorem 3.51
- 3.8 Reciprocity Theorem 3.64
- 3.9 Millman's Theorem 3.68
- Exercises 3.72
- Objective-Type Questions 3.74
- Answers to Objective-Type Questions 3.75

4. MAGNETIC CIRCUITS

4.1

- 4.1 Introduction 4.1
- 4.2 Self-Inductance 4.1
- 4.3 Mutual Inductance 4.2
- 4.4 Coefficient of Coupling (k) 4.2
- 4.5 Inductances in Series 4.3
- 4.6 Inductances in Parallel 4.4
- 4.7 Dot Convention 4.9
- 4.8 Coupled Circuits 4.15
- 4.9 Conductively Coupled Equivalent Circuits 4.37
- Exercises 4.41
- Objective-Type Questions 4.43
- Answers to Objective-Type Questions 4.44

5. GRAPH THEORY

5.1

- 5.1 Introduction 5.1
- 5.2 Graph of a Network 5.1
- 5.3 Graph Terminologies 5.2
- 5.4 Incidence Matrix 5.6
- 5.5 Loop Matrix or Circuit Matrix 5.8
- 5.6 Cutset Matrix 5.10
- 5.7 Relationship Among Submatrices of A, B and Q 5.12
- 5.8 Kirchhoff's Voltage Law 5.24
- 5.9 Kirchhoff's Current Law 5.24
- 5.10 Relation Between Branch Voltage Matrix V_b , Twig Voltage Matrix V_t and Node Voltage Matrix V_n 5.25
- 5.11 Relation Between Branch Current Matrix I_b and Loop Current Matrix I_l 5.26
- 5.12 Network Equilibrium Equation 5.26
- Exercises 5.53
- Objective-Type Questions 5.54
- Answers to Objective-Type Questions 5.55

6. TIME DOMAIN ANALYSIS OF RLC CIRCUITS**6.1**

- 6.1 Introduction 6.1
- 6.2 Initial Conditions 6.1
- 6.3 Resistor–Inductor Circuit 6.27
- 6.4 Resistor–Capacitor Circuit 6.49
- 6.5 Resistor–Inductor–Capacitor Circuit 6.66
- Exercises* 6.79
- Objective-Type Questions* 6.82
- Answers to Objective-Type Questions* 6.85

7. FREQUENCY DOMAIN ANALYSIS OF RLC CIRCUITS**7.1**

- 7.1 Introduction 7.1
- 7.2 Laplace Transformation 7.1
- 7.3 Laplace Transforms of Some Important Functions 7.2
- 7.4 Properties of Laplace Transform 7.4
- 7.5 Inverse Laplace Transform 7.7
- 7.6 Frequency Domain Representaion of RLC Circuits 7.12
- 7.7 Resistor–Inductor Circuit 7.13
- 7.8 Resistor–Capacitor Circuit 7.19
- 7.9 Resistor–Inductor–Capacitor Circuit 7.25
- 7.10 Response of *RL* Circuit to Various Functions 7.31
- 7.11 Response of *RC* Circuit to Various Functions 7.39
- Exercises* 7.49
- Objective-Type Questions* 7.52
- Answers to Objective-Type Questions* 7.53

8. NETWORK FUNCTIONS**8.1**

- 8.1 Introduction 8.1
- 8.2 Driving-Point Functions 8.1
- 8.3 Transfer Functions 8.2
- 8.4 Analysis of Ladder Networks 8.5
- 8.5 Analysis of Non-Ladder Networks 8.15
- 8.6 Poles and Zeros of Network Functions 8.20
- 8.7 Restrictions on Pole and Zero Locations for Driving-Point Functions [Common Factors in $N(s)$ and $D(s)$ Cancelled] 8.21
- 8.8 Restrictions on Pole and Zero Locations for Transfer Functions [Common Factors in $N(s)$ and $D(s)$ Cancelled] 8.21
- 8.9 Time-Domain Behaviour from the Pole-Zero Plot 8.39
- 8.10 Graphical Method for Determination of Residue 8.42
- Exercises* 8.50
- Objective-Type Questions* 8.53
- Answers to Objective-Type Questions* 8.55

9. TWO-PORT NETWORKS

9.1

- 9.1 Introduction 9.1
- 9.2 Open-Circuit Impedance Parameters (Z Parameters) 9.2
- 9.3 Short-Circuit Admittance Parameters (Y Parameters) 9.8
- 9.4 Transmission Parameters (ABCD Parameters) 9.18
- 9.5 Hybrid Parameters (h Parameters) 9.24
- 9.6 Inter-relationships between the Parameters 9.29
- 9.7 Interconnection of Two-Port Networks 9.47
- 9.8 T-Network 9.61
- 9.9 Pi (π)-Network 9.61
- 9.10 Lattice Networks 9.66
- 9.11 Terminated Two-Port Networks 9.69
- Exercises* 9.79
- Objective-Type Questions* 9.82
- Answers to Objective-Type Questions* 9.85

10. SYNTHESIS OF RLC CIRCUITS

10.1

- 10.1 Introduction 10.1
- 10.2 Hurwitz Polynomials 10.1
- 10.3 Positive Real Functions 10.16
- 10.4 Elementary Synthesis Concepts 10.24
- 10.5 Realisation of LC Functions 10.30
- 10.6 Realisation of RC Functions 10.47
- 10.7 Realisation of RL Functions 10.63
- Exercises* 10.72
- Objective-Type Questions* 10.74
- Answers to Objective-Type Questions* 10.76

11. FILTERS

11.1

- 11.1 Introduction 11.1
- 11.2 Classification of Filters 11.1
- 11.3 T-Network 11.1
- 11.4 π -Network 11.4
- 11.5 Characteristic of Filters 11.6
- 11.6 Constant- k Low Pass Filter 11.7
- 11.7 Constant- k High-pass Filter 11.14
- 11.8 Band-pass Filter 11.18
- 11.9 Band-stop Filter 11.22
- 11.10 Terminating Half Sections 11.25
- Exercises* 11.27
- Objective-Type Questions* 11.27
- Answers to Objective-Type Questions* 11.28