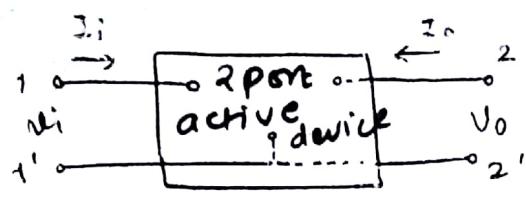


The Hybrid Equivalent Model



two port system

$$v_i = h_{11} I_i + h_{12} v_o$$

$$I_o = h_{21} I_i + h_{22} v_o$$

h -parameter \rightarrow hybrid \rightarrow
(mixture of V & I)

- ① If we set $v_o = 0$ (short ckt o/p terminals)

$$h_{11} = \left. \frac{v_i}{I_i} \right|_{v_o=0} \Omega$$

$$h_{21} = \left. \frac{I_o}{I_i} \right|_{v_o=0} \text{ units:}$$

h_{11} - short ckt i/p impedance parameter

h_{21} - short ckt forward transfer current ratio
parameter.


- ② If we set $I_i = 0$ (open the i/p terminals.)

$$h_{12} = \left. \frac{v_i}{v_o} \right|_{I_i=0} \text{ unitless}$$


$$h_{22} = \left. \frac{I_o}{v_o} \right|_{I_i=0} \text{ siemens}$$

h_{12} = open ckt reverse transfer voltage ratio
parameter

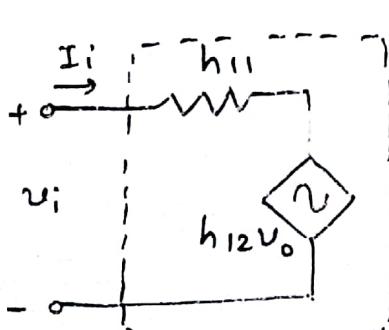h_{22} = open circuit output admittance parameter.



hybrid i/p equivalent

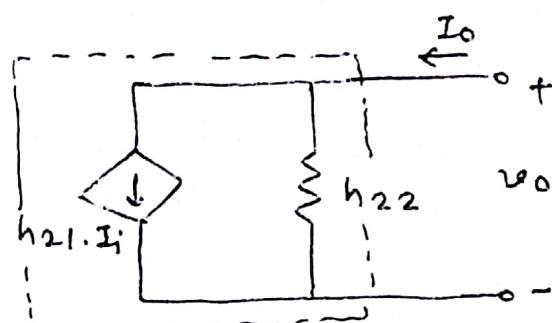


Hybrid o/p equivalent

$h_{11} \rightarrow$ i/p resistance $\rightarrow h_i$


$h_{12} \rightarrow$ reverse transfer vtg ratio $\rightarrow h_r$

$h_{21} \rightarrow$ forward transfer current ratio $\rightarrow h_f$

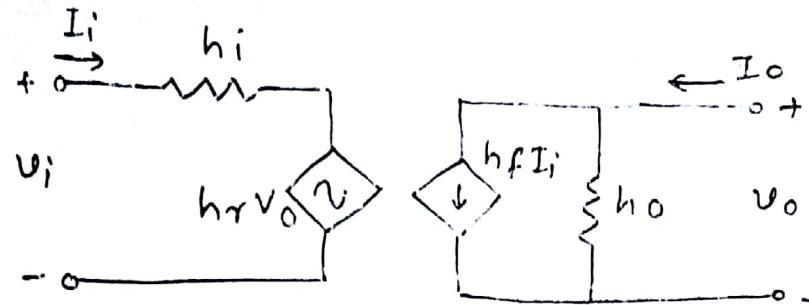
$h_{22} \rightarrow$ o/p conductance $\rightarrow h_o$




complete hybrid equivalent model

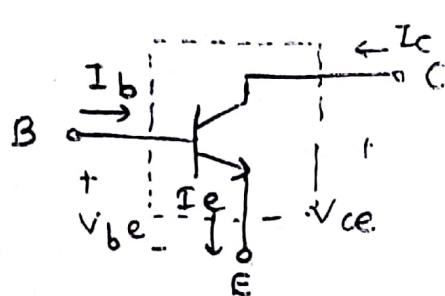


a) Graphical symbol

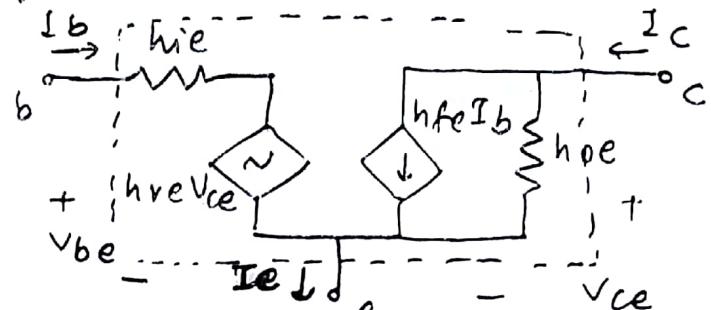

Hybrid Equivalent Model


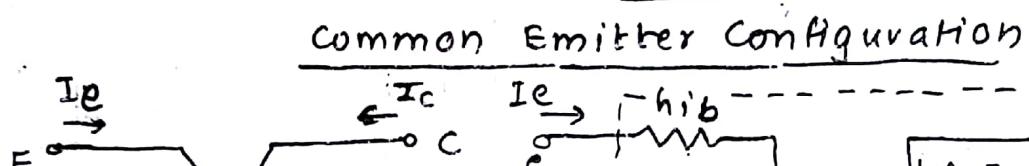


a) graphical symbol


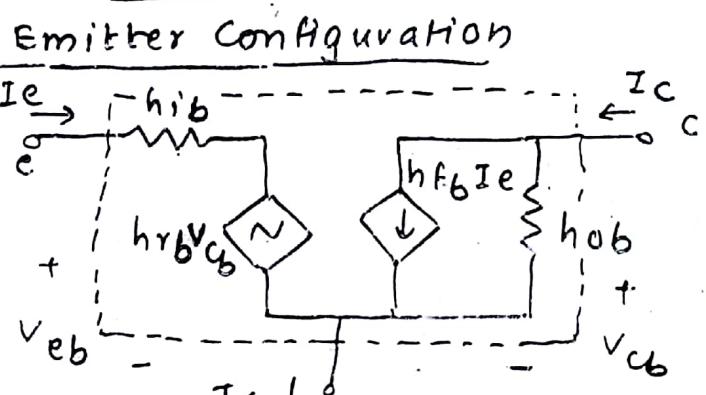


Hybrid Equivalent Model

Common Base Configuration

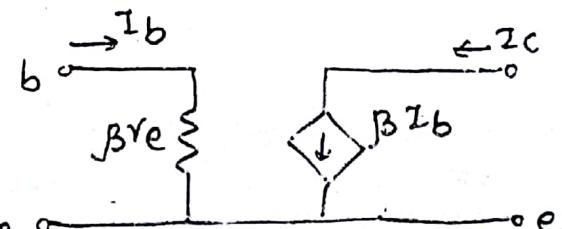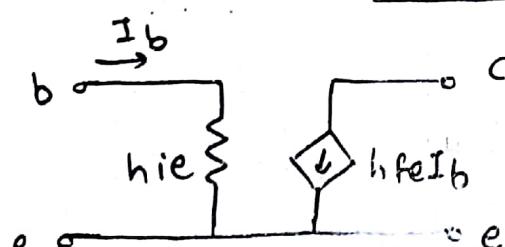

common Emitter Configuration

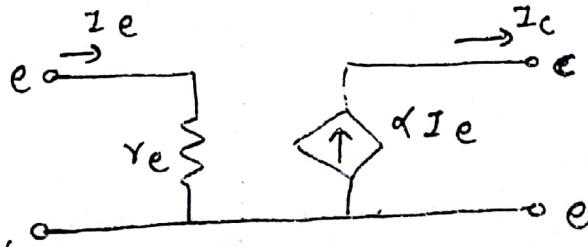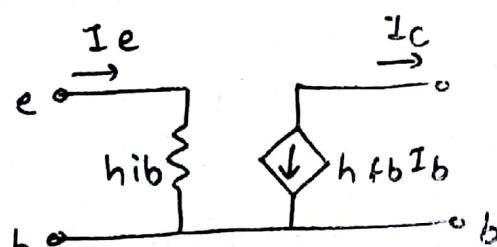

common base configuration



$$\begin{aligned} h_{ie} &= \beta r_e \\ h_{fe} &= \beta \alpha c \end{aligned}$$

$$\begin{aligned} h_{ib} &= r_e \\ h_{fb} &= -\alpha \approx -1 \end{aligned}$$

'Hybrid' vs 'r_e' Model



Graphical Determination of h-parameter

(5)

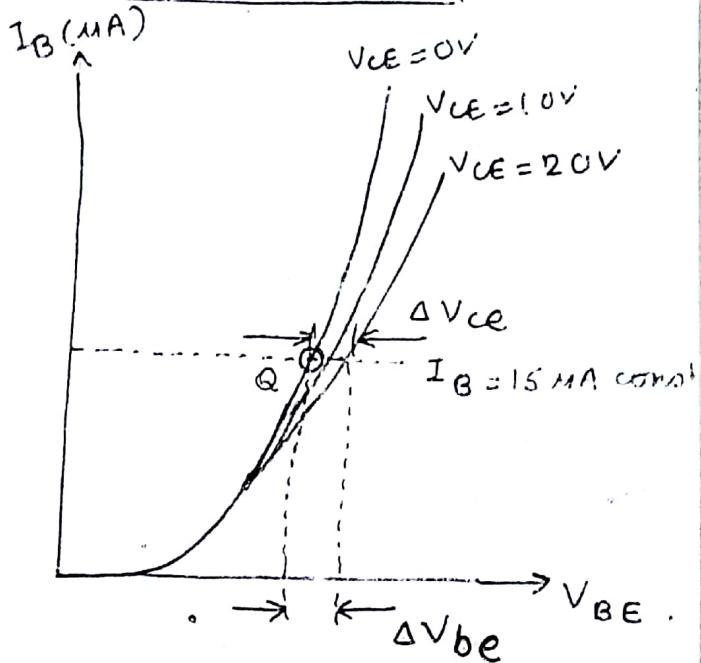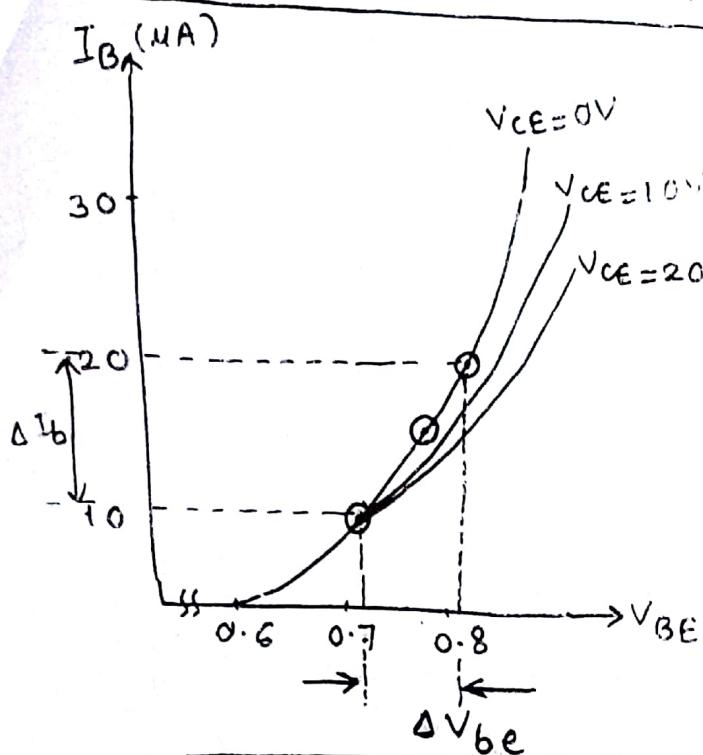

$$|h_{ie}| = \left| \frac{\Delta V_{BE}}{\Delta I_B} \right| \quad |V_{CE} = \text{constant}|$$

$$|h_{re}| = \left| \frac{\Delta V_{BE}}{\Delta V_{CE}} \right| \quad |I_B = \text{constant}|$$

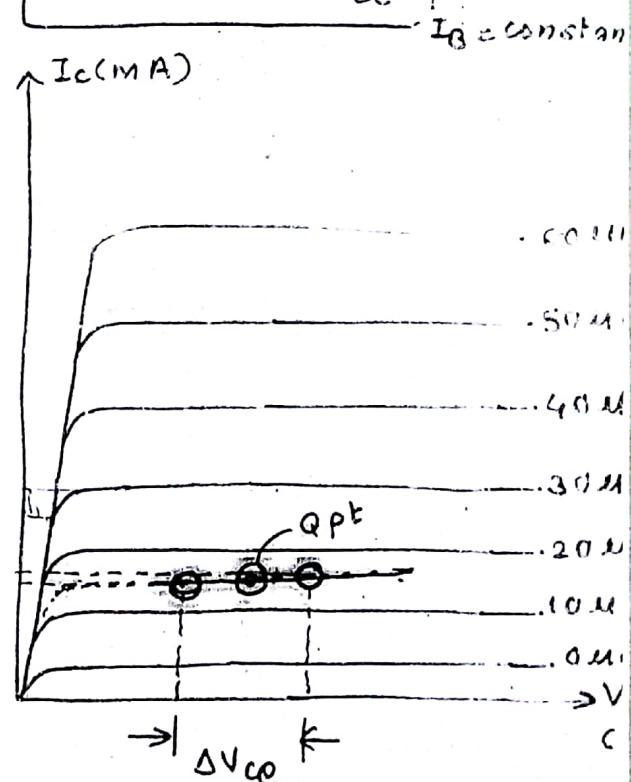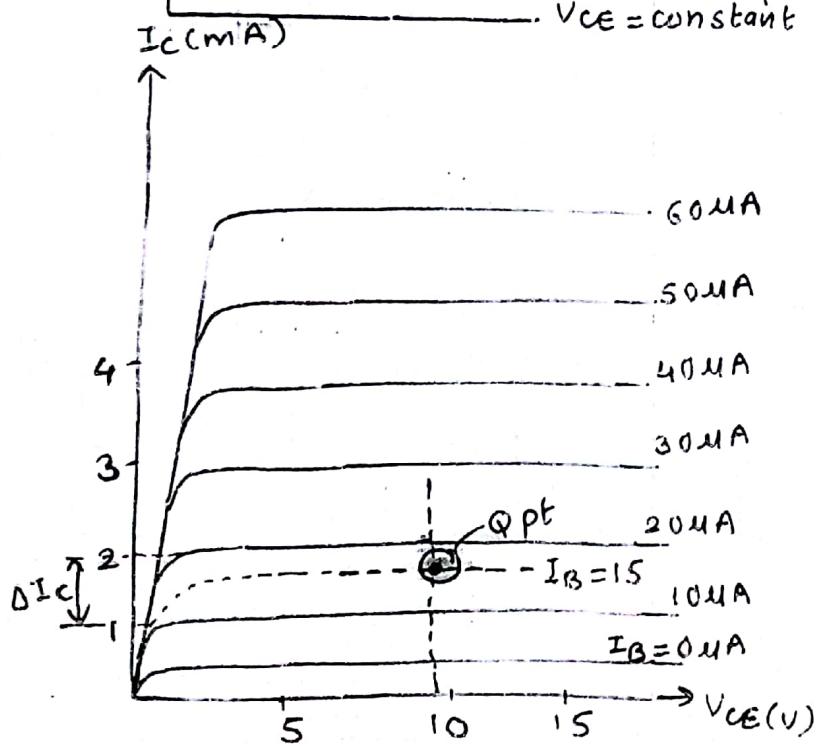

$$|h_{fe}| = \left| \frac{\Delta I_C}{\Delta I_B} \right| \quad |V_{CE} = \text{constant}|$$

$$|h_{oe}| = \left| \frac{\Delta I_C}{\Delta V_{CE}} \right| \quad |I_B = \text{constant}|$$

Parameter	C_E	C_C	C_B
h_i	$1K\Omega$	$1K\Omega$	20Ω
h_{re}	2.5×10^{-4}	≈ 1	3×10^{-4}
h_{fe}	50	50	-0.98
h_o	$25mA/V$	$25mA/V$	$0.5mA/V$
$1/h_o$	$40K\Omega$	$40K\Omega$	$2M\Omega$

Parameter Relationship :-

C_E to C_C	C_E to C_B
$h_{ie} = h_{ie}$	$h_{ib} \approx h_{ie}/(1+h_{fe})$
$h_{rc} = 1 + h_{re}$	$h_{rb} = \frac{h_{ie}h_{oe}}{1+h_{fe}} - h_{re}$
$h_{fc} = -(1+h_{fe})$	$h_{fb} = \frac{-h_{fe}}{1+h_{fe}}$
$h_{oc} = h_{oe}$	$h_{ob} = \frac{h_{oe}}{1+h_{fe}}$

C_E configuration	C_B configuration
$h_{ie} = \beta \gamma_e$	$h_{ib} = \gamma_e$
$h_{fe} = \beta \alpha_c$	$h_{fb} = -\alpha \approx -1$

Graphical determination of h-parameters -

$h_{ie} \approx \frac{\Delta V_{be}}{\Delta I_b}$ (ohms) $V_{ce} = \text{const}$	$h_{fe} \approx \frac{\Delta I_c}{\Delta I_b}$ (unitless) $V_{ce} = \text{constant}$
$h_{re} \approx \frac{\Delta V_{be}}{\Delta V_{ce}}$ (unitless) $I_B = \text{constant}$	$h_{oe} \approx \frac{\Delta I_c}{\Delta V_{ce}}$ (siemens), $I_B = \text{constant}$

* Small signal Amplifier Analysis using Hybrid- π Model-


① CE Amplifier with Bypassed R_E -

(May 11, Dec 14)

* Type of Questions

- ① For a CE amplifier derive the expressions for A_V , A_I , Z_i & Z_o (May 11, 10)
- ② Draw circuit diagram of CE amplifier with voltage divider bias with bypassed R_E & derive expression for voltage gain, current gain, input resistance, output resistance using hybrid π Model which includes early effect. (Dec 14, 10)


Step ① Draw the ac equivalent circuit -

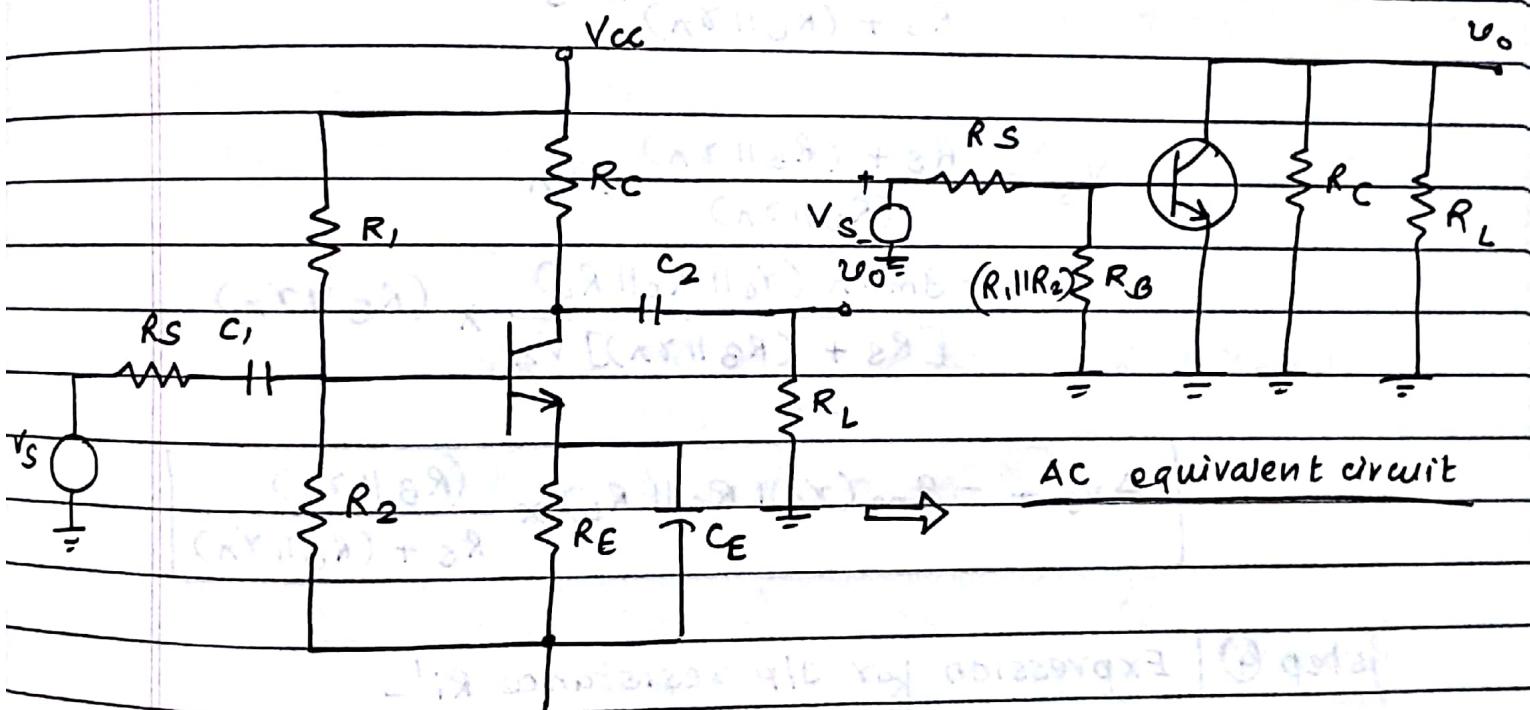

CE Amplifier with bypassed R_E

Step ② Draw hybrid π equivalent ckt -

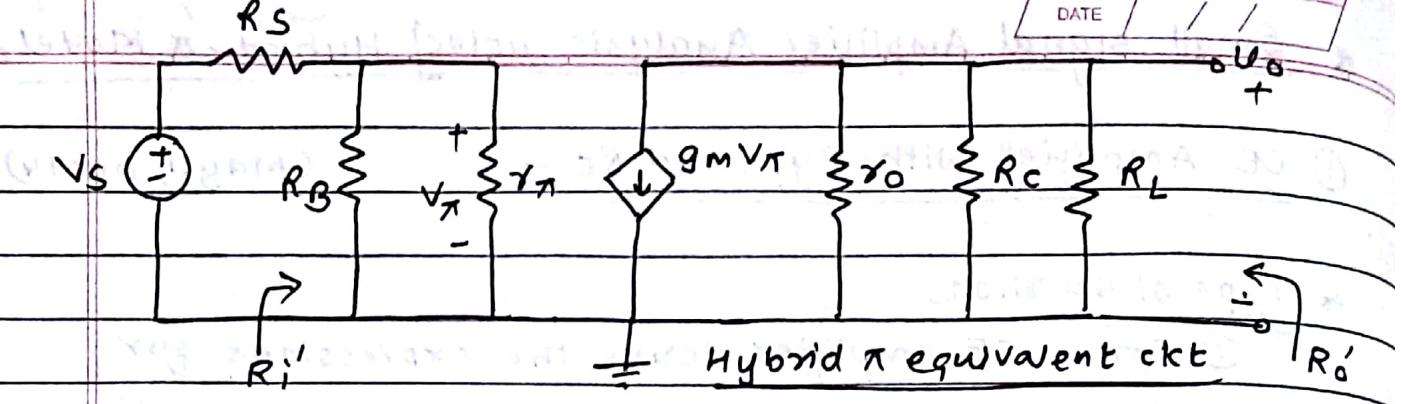Replace the transistor in ac equivalent ckt by the hybrid π equivalent ckt.



Step ③ - Expression for voltage gain (Avs) -

$$Av_s = \frac{V_o}{V_s}$$

$$V_o = -g_m V_\pi (\gamma_0 \parallel R_c \parallel R_L)$$

$$V_\pi = \frac{(R_B \parallel \gamma_\pi)}{R_s + (R_B \parallel \gamma_\pi)} \times V_s \quad (R_B = R_1 \parallel R_2)$$

$$V_s = \frac{R_s + (R_B \parallel \gamma_\pi)}{(R_B \parallel \gamma_\pi)} \times V_\pi$$

$$= \frac{-g_m V_\pi (\gamma_0 \parallel R_c \parallel R_L)}{[R_s + (R_B \parallel \gamma_\pi)]} \times (R_B \parallel \gamma_\pi)$$

$$Av_s = \frac{-g_m (\gamma_0 \parallel R_c \parallel R_L) \times (R_B \parallel \gamma_\pi)}{R_s + (R_B \parallel \gamma_\pi)}$$


Step ④ Expression for input resistance R_i' -

$$R_i' = (R_B \parallel \gamma_\pi) = (R_1 \parallel R_2 \parallel r_m)$$

$$\text{also } R_i = \gamma_\pi$$

Step ⑤ Expression for output Resistance R_o' -

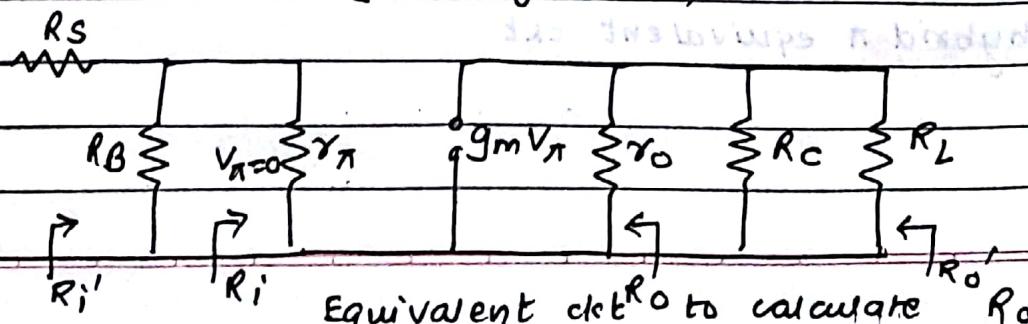R_o' is obtained by setting V_s = 0. As V_s = 0, V_\pi = 0, g_m V_\pi = 0.




Equivalent ckt to calculate R_o'

o/p Resistance back into o/p terminal,

$$R_o' = (\gamma_{o\parallel} R_c \parallel R_L) \text{ also } R_o = \gamma_o$$

step ⑥ Expression for current gain (A_{IS}) -

$$A_{IS} = \frac{I_o}{I_i}$$

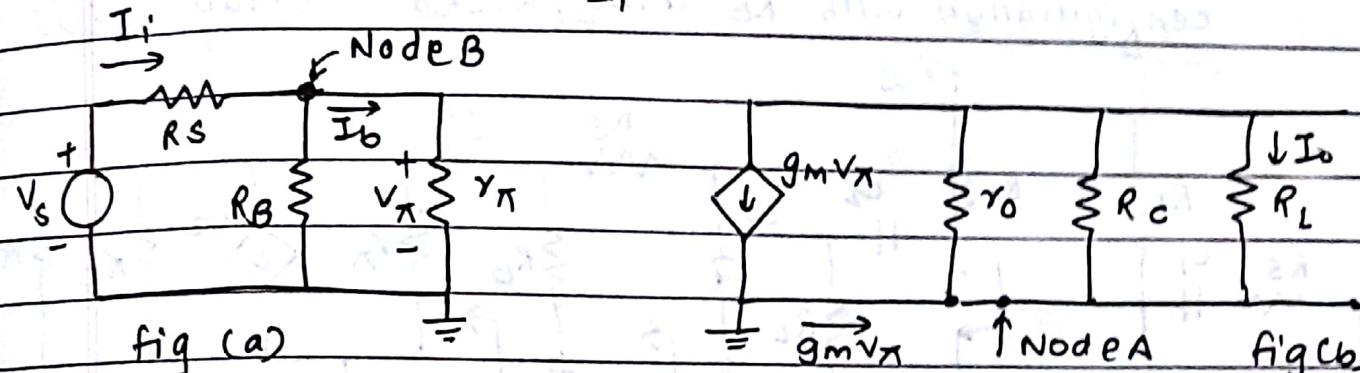

$$\text{using current division Rule, } I_o = \frac{-g_m V_\pi (\gamma_{o\parallel} R_c)}{(\gamma_{o\parallel} R_c) + R_L} \quad (1)$$

$$\text{from fig (a)} \quad V_\pi = I_b \gamma_\pi \quad (2)$$

$$\text{using current division Rule, } I_b = \frac{R_B}{R_B + \gamma_\pi} \times I_i \quad \text{Put in (2)}$$

$$\therefore V_\pi = \frac{R_B \gamma_\pi}{(R_B + \gamma_\pi)} \times I_i = (R_B \parallel \gamma_\pi) I_i$$

Put value of V_π in eqⁿ (1)

$$I_o = \frac{-g_m (\gamma_{o\parallel} R_c)}{R_L + (\gamma_{o\parallel} R_c)} \times (R_B \parallel \gamma_\pi) I_i$$

current gain

$$A_{IS} = \frac{I_o}{I_i} = \frac{-g_m (\gamma_{o\parallel} R_c) (R_B \parallel \gamma_\pi)}{R_L + (\gamma_{o\parallel} R_c)}$$

Advantage - provides high voltage gain (due to low R_i)

Disadvantage - low i/p Resistance


$$R_i = \gamma_\pi \quad \& \quad R_i' = R_1 \parallel R_2 \parallel \gamma_\pi$$

* CE Amplifier with unbypassed RE

DATE / /

Type of Questions -

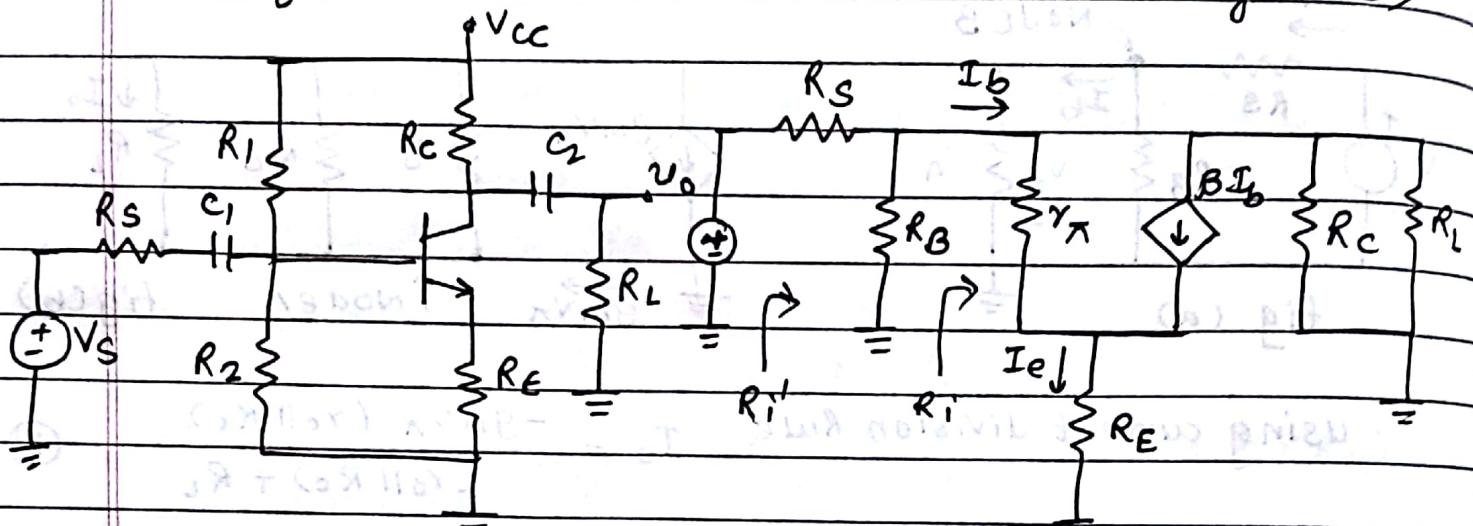- Derive the equations for A_v , A_i , R_i & R_o for NPN transistor in CE mode voltage divider bias configuration with R_E unbypassed. (May 15, 10)



CE amplifier with unbypassed R_E Hybrid π equivalent ckt

Step ① obtain expression for R_i & R'_i

$$R_i = \frac{V_b}{I_b} \quad (1)$$

$$\text{But } V_b = I_b r_\pi + I_e R_E$$

$$= I_b r_\pi + (1+\beta) I_b R_E$$

$$V_b = I_b [r_\pi + (1+\beta) R_E] \text{ Put in eqn(1)}$$


$$R_i = \frac{I_b [r_\pi + (1+\beta) R_E]}{I_b}$$

$$R_i = r_\pi + (1+\beta) R_E$$

$$R'_i = R_B \parallel R_i = (R_1 \parallel R_2) \parallel [r_\pi + (1+\beta) R_E]$$

Step ② obtain expression of voltage gain A_{Vs} -

$$A_{Vs} = \frac{V_o}{V_s}$$

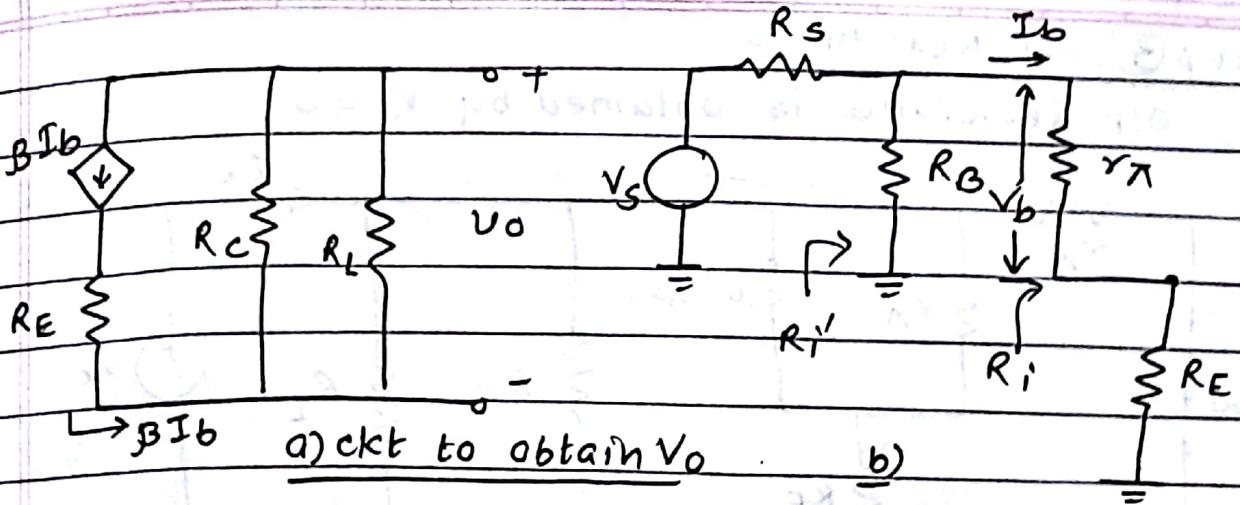

$$V_o = -\beta I_b (R_C \parallel R_L)$$

from fig b), $V_b = I_b R_i$ or $I_b = V_b / R_i$

$$V_o = -\frac{\beta V_b (R_C \parallel R_L)}{R_i} \quad \text{but } V_b = \frac{R_i'}{R_i' + R_S} \times V_s$$

$$V_o = \frac{-\beta R_i' V_s}{(R_i' + R_S)} \times \frac{(R_C \parallel R_L)}{R_i}$$

$$\frac{V_o}{V_s} = \frac{A_{VS}}{1} = \frac{-\beta R_i'}{(R_i' + R_S)} \times \frac{(R_C \parallel R_L)}{R_i}$$

$$\text{But } R_i = r_\pi + (1+\beta) R_E$$

$A_{VS} = \frac{-\beta (R_C \parallel R_L)}{r_\pi + (1+\beta) R_E} \times \frac{R_i'}{(R_i' + R_S)}$	Exact expression
--	------------------

But if $R_i' \gg R_S$ & $(1+\beta) \gg r_\pi$ then


$$A_{VS} \approx \frac{-\beta (R_C \parallel R_L)}{(1+\beta) R_E} \quad \text{if } \beta = (1+\beta)$$

$A_{VS} = \frac{-(R_C \parallel R_L)}{R_E}$

Approximate voltage gain

Step ③ O/P Resistance

O/P Resistance is obtained by $V_S = 0$

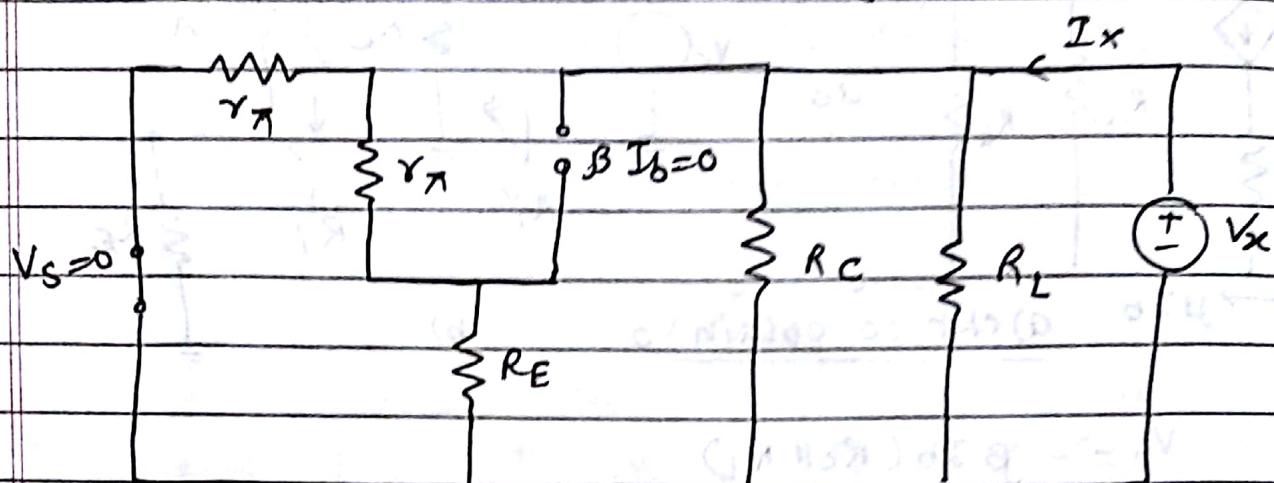

Circuit to obtain output Resistance

As $V_S = 0$, $I_B = 0 \therefore \beta I_B = 0$

$$R_o' = \frac{V_x}{I_x} = R_C \parallel R_L$$

Advantages -

- it increases O/P Impedance (R_o')
- stability of A_v increases w.r.t β

Disadvantage -


Reduction in voltage gain (A_v)

* Common Collector (Emitter Follower) Amplifier -

Type of Questions -


1. Write short note on small signal equivalent of CC ampl.
- circuit
- (May 15, 5)
2. Draw emitter follower circuit & derive an expression for voltage gain A_v . (Dec 15, 10)
 3. Draw a neat circuit diagram of emitter follower configuration & its hybrid- π Model. (Dec 16, 04)

Step ① Redraw the hybrid π circuit

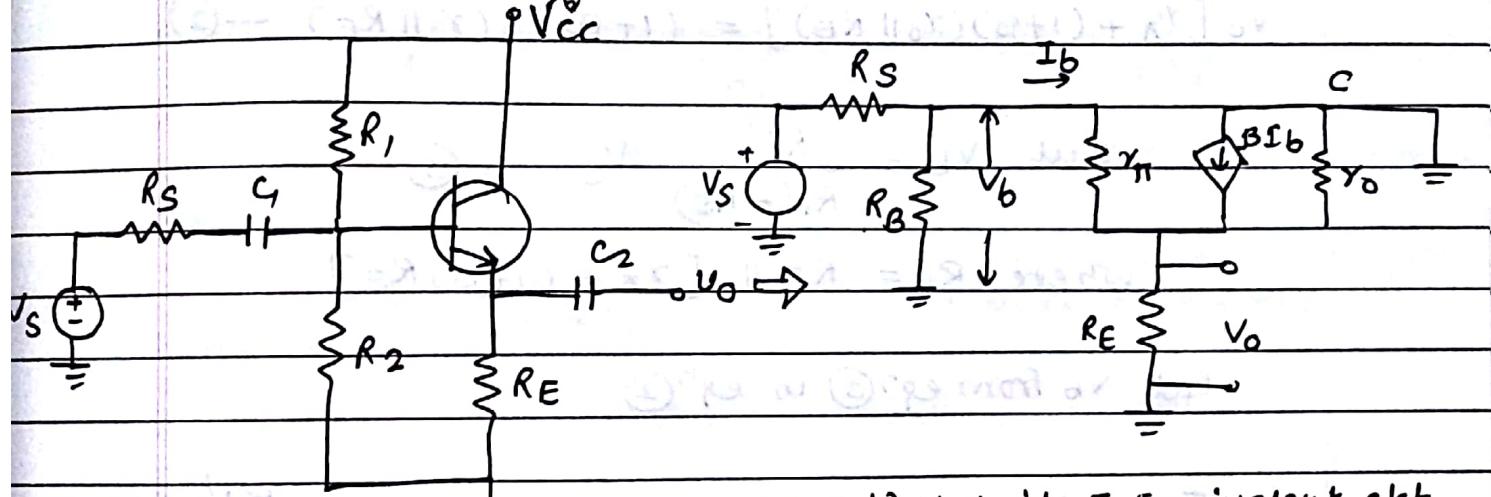

b) Hybrid- π Equivalent ckt

a) Emitter follower amplifier

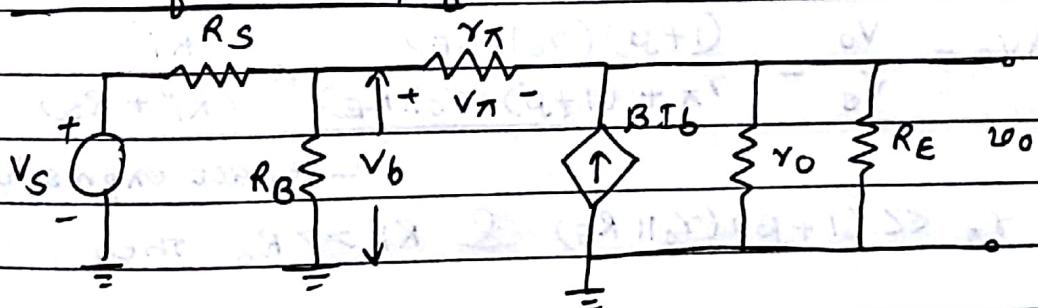

c) simplified hybrid- π Equivalent ckt

Step ② Expression for A_{vS} -

$$V_o = I_b (\gamma_0 \parallel R_E) + \beta I_b (\gamma_0 \parallel R_E)$$

\therefore (current through $(\gamma_0 \parallel R_E)$ is $I_b + \beta I_b$)

$$V_o = (1 + \beta) I_b (\gamma_0 \parallel R_E) \quad \text{--- (1)}$$

$$\text{from fig c)} \quad I_b = \frac{V_\pi}{r_\pi} = \frac{V_b - V_o}{r_\pi} \quad \text{but } V_o = V_0$$

$$\therefore I_b = \frac{V_b - V_0}{r_\pi} \quad \text{Put in eqn ①}$$

$$V_0 = (1+\beta) \left[\frac{V_b - V_0}{r_\pi} \right] (r_0 \parallel R_E)$$

$$= \frac{(1+\beta) V_b}{r_\pi} (r_0 \parallel R_E) - \frac{(1+\beta) V_0}{r_\pi} (r_0 \parallel R_E)$$

$$V_0 \left[1 + \frac{(1+\beta) (r_0 \parallel R_E)}{r_\pi} \right] = \frac{(1+\beta) V_b (r_0 \parallel R_E)}{r_\pi}$$

$$V_0 [r_\pi + (1+\beta)(r_0 \parallel R_E)] = (1+\beta) V_b (r_0 \parallel R_E) \quad \text{--- ②}$$

$$\text{But } V_b = \frac{R_i'}{(R_i' + R_S)} V_s \quad \text{--- ③}$$

$$\text{where } R_i' = R_B \parallel [r_\pi + (1+\beta) R_E]$$

Put V_b from eqn ③ in eqn ②

$$V_0 [r_\pi + (1+\beta)(r_0 \parallel R_E)] = (1+\beta)(r_0 \parallel R_E) \frac{R_i'}{(R_i' + R_S)} \times V_s$$

$$A_v s = \frac{V_0}{V_s} = \frac{(1+\beta)(r_0 \parallel R_E)}{r_\pi + (1+\beta)(r_0 \parallel R_E)} \times \frac{R_i'}{(R_i' + R_S)}$$

exact expression.


If $r_\pi \ll (1+\beta)(r_0 \parallel R_E)$ & $R_i' \gg R_S$ then,

$$A_v s = \frac{(1+\beta)(r_0 \parallel R_E)}{(1+\beta)(r_0 \parallel R_E)} \approx 1 \quad \text{--- Approximate expression}$$


step ③ Input Resistance

Apply KVL to input loop,
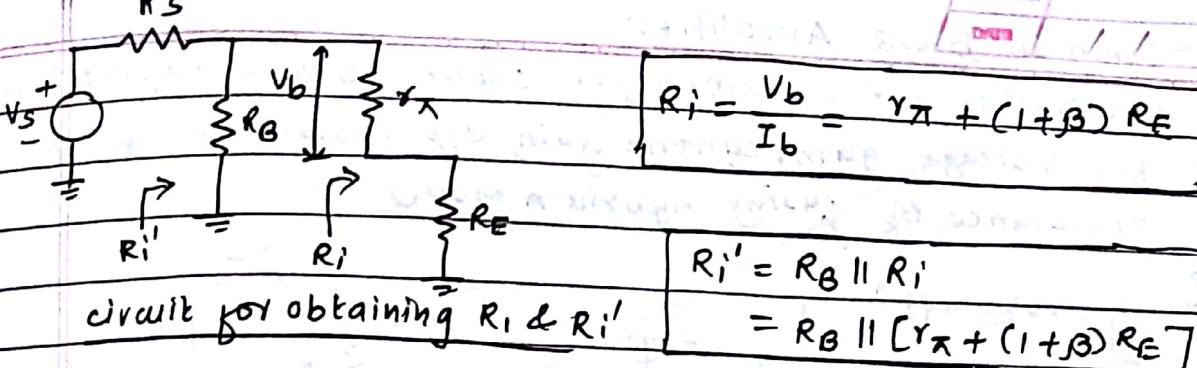
$$\begin{aligned} V_b &= I_b r_\pi + I_e R_E \quad \text{But } I_e = (1+\beta) I_b \\ &= I_b r_\pi + (1+\beta) I_b R_E \\ &= I_b [r_\pi + (1+\beta) R_E] \end{aligned}$$



Step ④ output Resistance -

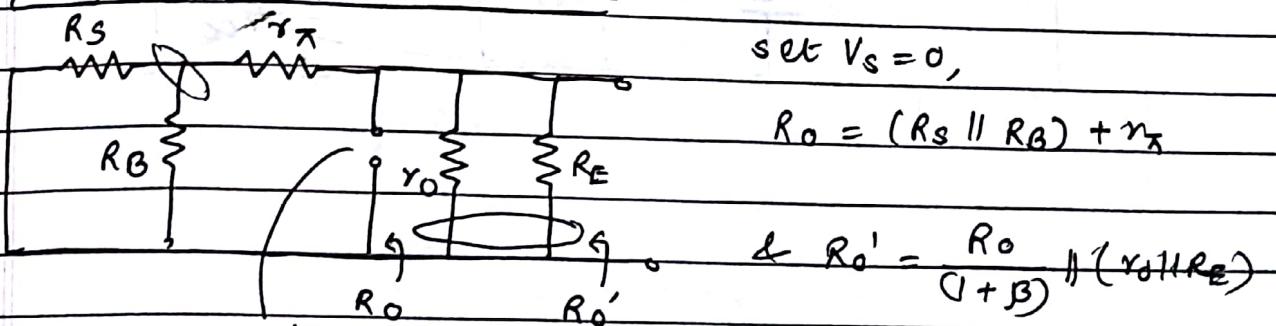


Equivalent circuit to calculate R_o & R'_o where R_o represents reflected resistance from base to emitter.

$$R'_o = \frac{(R_s \parallel R_B) + r_\pi}{(1+\beta)} \parallel (r_o \parallel R_E)$$

Step ⑤ small signal current gain
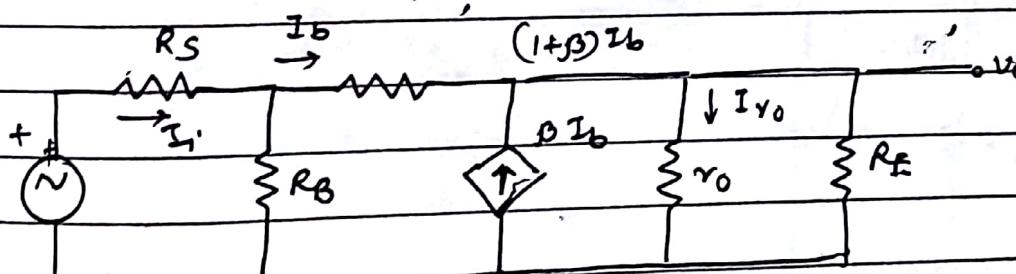
$$A_I = \frac{I_e}{I_i} \quad \text{where } I_e = \text{op current}$$



Equivalent ckt for obtaining A_I

$$I_e = (1+\beta) I_B \quad I_B = \frac{R_B}{(R_B + r_\pi)} I_i$$

$$I'_i = (1+\beta) \frac{R_B}{(R_B + R_i)} \times I_i$$


$$A_I = \frac{I'_e}{I'_i} = \frac{(1+\beta) R_B}{R_B + R_i} \quad \text{if } R_i \gg R_B$$

$$A_I \approx (1+\beta)$$


Common Base Amplifier -

Question - For the common Base amplifier shown, derive expression for voltage gain, current gain, input resistance & output resistance using hybrid π model.


(May 14 12)

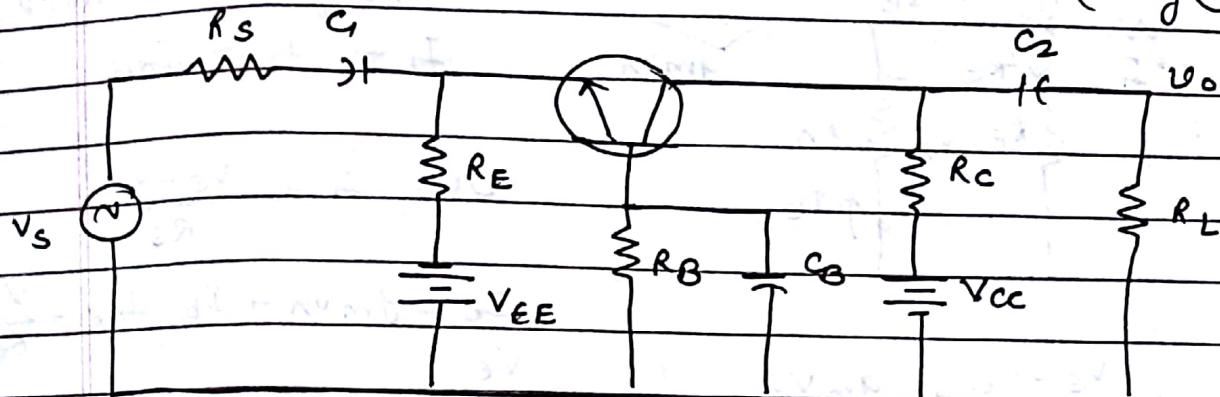

Step ① Draw AC equivalent circuit

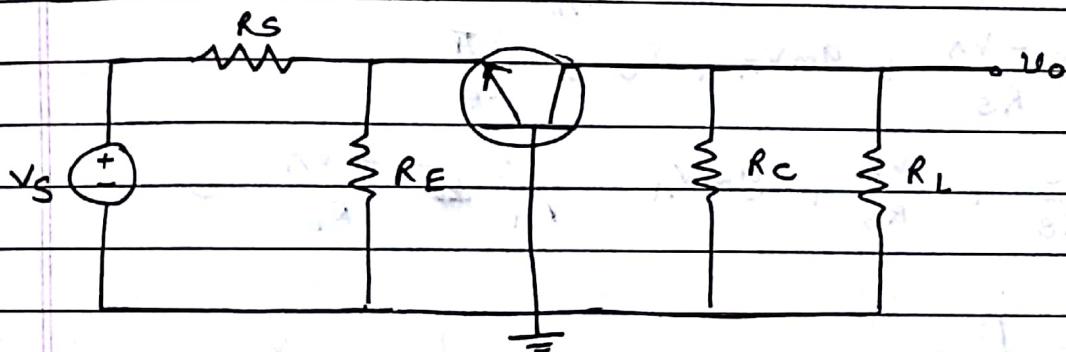

Step ② draw the hybrid π equivalent ckt

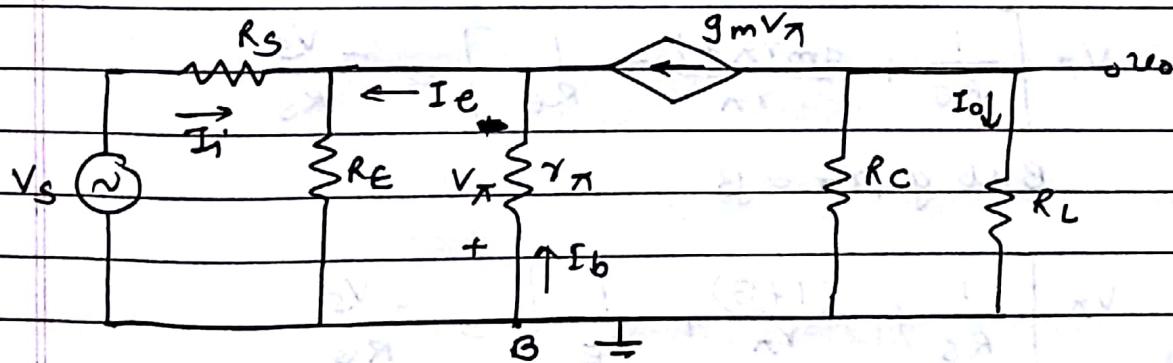

small signal equivalent ckt for CB configuration

Step ③ Expression for small signal voltage gain -


$$V_o = I_o R_L$$

$$\text{but } I_o = \frac{-R_C}{R_C + R_L} \times g_m V_A$$

$$\therefore V_o = \frac{-R_C R_L}{(R_C + R_L)} g_m V_A$$

$$\text{But } \frac{R_C R_L}{R_C + R_L} = (R_C \parallel R_L)$$

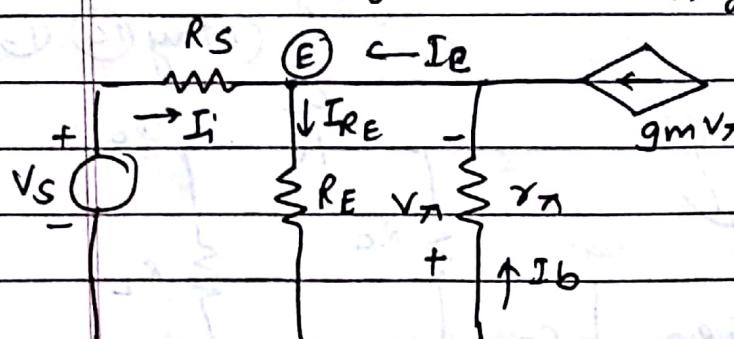$\therefore V_o = -(R_C \parallel R_L) g_m v_{\pi}$ —①



Apply KCL at node E

$$I_i + I_e = I_{RE}$$

$$\text{But } I_i = \frac{V_s - V_e}{R_S}$$

$$I_e = g_m v_{\pi} + I_b, I_{RE} = \frac{V_e}{R_E}$$

$$\therefore \frac{V_s - V_e}{R_S} + g_m v_{\pi} + I_b = \frac{V_e}{R_E}$$

$$\text{But } V_e = -V_{\pi} \& I_b = \frac{V_{\pi}}{R_{\pi}}$$

$$\frac{V_s + V_{\pi}}{R_S} + g_m v_{\pi} + I_b = \frac{-V_{\pi}}{R_E}$$

$$\frac{V_s}{R_S} + \frac{V_{\pi}}{R_S} + g_m v_{\pi} + \frac{V_{\pi}}{R_{\pi}} + \frac{V_{\pi}}{R_E} = 0$$

$$V_{\pi} \left[\frac{1}{R_S} + g_m + \frac{1}{r_{\pi}} + \frac{1}{R_E} \right] = -\frac{V_s}{R_S}$$

$$V_{\pi} \left[\frac{1}{R_S} + \frac{g_m r_{\pi} + 1}{r_{\pi}} + \frac{1}{R_E} \right] = -\frac{V_s}{R_S}$$

$$\text{But } g_m r_{\pi} = \beta$$

$$V_{\pi} \left[\frac{1}{R_S} + \frac{(1+\beta)}{r_{\pi}} + \frac{1}{R_E} \right] = -\frac{V_s}{R_S}$$

$$\therefore V_{\pi} = \frac{-V_s}{R_S \left[\frac{1}{R_S} + \frac{(1+\beta)}{r_{\pi}} + \frac{1}{R_E} \right]}$$

$$R_S \left[\frac{1}{R_S} + \frac{(1+\beta)}{r_{\pi}} + \frac{1}{R_E} \right]$$

$$\text{Let } \frac{1}{R} = \frac{1}{R_S} + \frac{(1+\beta)}{r_{\pi}} + \frac{1}{R_E} \quad \text{Hence } R = R_S \parallel \left(\frac{1+\beta}{r_{\pi}} \parallel R_E \right)$$

$$\therefore V_T = -\frac{V_S}{R_S} \times R = -\frac{V_S}{R_S} \left[R_S \parallel \frac{(1+\beta)}{r_\pi} \parallel R_E \right] \quad (2)$$

Put in eqn ①

$$V_o = -(R_C \parallel R_L) g_m x - \frac{V_S}{R_S} \left[R_S \parallel \frac{(1+\beta)}{r_\pi} \parallel R_E \right]$$

$$\frac{V_o}{V_S} = A_{VS} = g_m \frac{(R_C \parallel R_L)}{R_S} \left[R_S \parallel \frac{(1+\beta)}{r_\pi} \parallel R_E \right]$$

Exact Expression

If we assume $R_S = 0$, parallel combination of R_S , $(1+\beta)/r_\pi$ & R_E approaches to R_S .


$$\therefore R_S \parallel \frac{(1+\beta)}{r_\pi} \parallel R_E = R_S$$

$$\therefore A_{VS} = \frac{g_m (R_C \parallel R_L)}{R_S} \times R_S$$

$$A_{VS} = g_m (R_C \parallel R_L) \quad \text{— Approximate expression}$$

Step ④ Expression for small signal current gain

$$A_{IS} = \frac{I_O}{I_i}$$

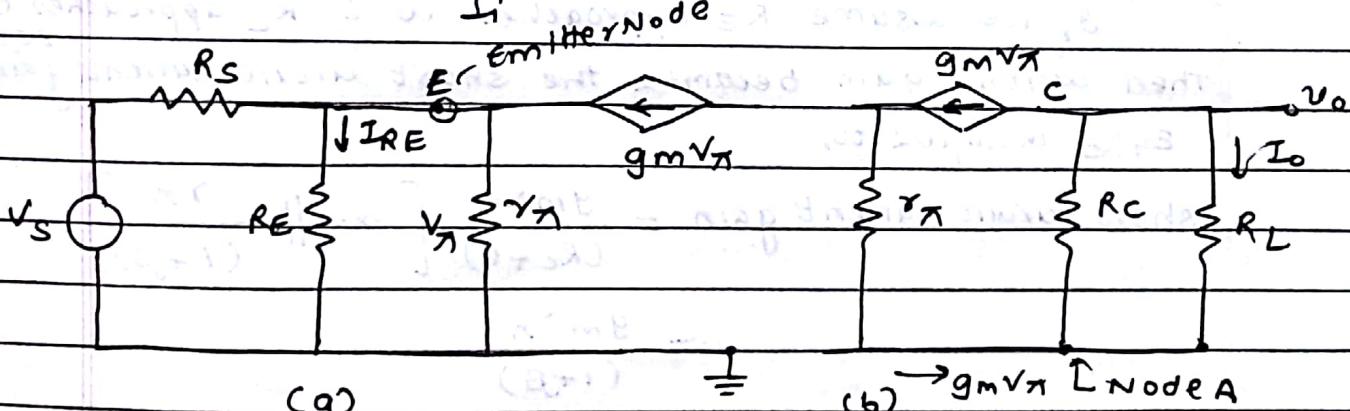

Apply KVL to emitter node.

$$I_i + I_b + g_m V_\pi - I_{RE} = 0$$

$$\therefore I_i + \frac{V_\pi}{r_\pi} + g_m V_\pi + \frac{V_\pi}{R_E} = 0$$

$$V_\pi \left[\frac{1}{r_\pi} + g_m + \frac{1}{R_E} \right] = -I_i$$

$$V_N = \frac{-I_i}{\left[\frac{1}{r_N} + g_m + \frac{1}{R_E} \right]} = \frac{-I_i}{\left[\frac{(1+g_m r_N)}{r_N} + \frac{1}{R_E} \right]}$$

But $g_m r_N = \beta$

$$V_N = \frac{-I_i}{\left[\frac{(1+\beta)}{r_N} + \frac{1}{R_E} \right]} = -I_i \left[R_E \parallel \frac{r_N}{(1+\beta)} \right] \quad (1)$$

Write the expression for current I_o using the principle of current division, current ($g_m V_N$) get divided between R_C & R_L at node A.

$$I_o = \frac{-R_C}{R_C + R_L} \times g_m V_N \quad \text{Put value of } V_N \text{ from eqn 1}$$

$$I_o = \frac{-g_m R_C}{R_C + R_L} \times -I_i \left[R_E \parallel \frac{r_N}{(1+\beta)} \right]$$

$$A_{IS} = \frac{I_o}{I_i} = \frac{g_m R_C}{(R_C + R_L)} \left[R_E \parallel \frac{r_N}{(1+\beta)} \right] \quad (2) \quad \text{exact expression}$$

Approximate expression for current gain,

If we assume R_E approaches ∞ & R_L approaches zero, then current gain becomes the short circuit current gain.

Eqn 2 modifies to,

$$\begin{aligned} \text{short circuit current gain} &= \frac{g_m R_C}{(R_C + 0)} \left[\infty \parallel \frac{r_N}{(1+\beta)} \right] \\ &= \frac{g_m r_N}{(1+\beta)} \end{aligned}$$


But $g_m r_N = \beta$

$$\therefore A_{IS(S.C)} = \frac{\beta}{(1+\beta)} = \alpha \quad \text{-- Approximate expression}$$

Step ⑤ Expression for IIP Resistance

Let R_i = Resistance seen between emitter & ground &

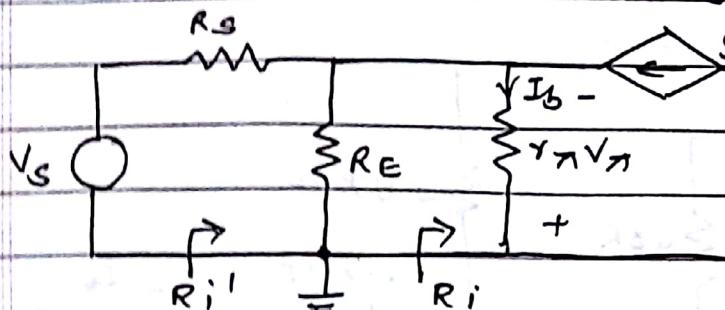$R_i' =$ Resistance seen by the voltage source.



R_i = Resistance between emitter & ground


= γ_π reflected from base side to emitter.

$$R_i = \frac{\gamma_\pi}{(1+\beta)} = \gamma_e \quad \text{as } \gamma_e \text{ is very small as } \beta \text{ is in denominator.}$$

$$R_i' = R_E \parallel R_i = R_E \parallel \frac{\gamma_\pi}{(1+\beta)}$$

Step ⑥ Expression for Output Resistance -

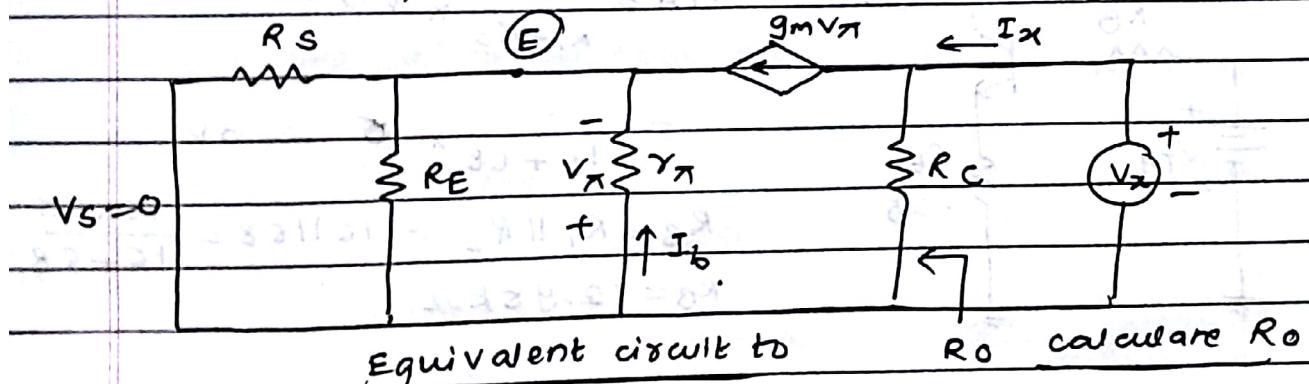Set $V_s = 0$ & assume that a source V_x is connected between o/p terminals as shown in next fig.



Equivalent circuit to calculate R_o

As $V_s = 0, V_\pi = 0 \therefore g_m V_\pi = 0$ so,

$$R_o = R_C \quad R_o' = R_o \parallel R_L = R_C \parallel R_L$$

* Numericals on Hybrid π Model (CE, CB, CC)


~~CE amp!~~

Ex 1) For the given circuit find,

① Determine Z_i , Z_o & A_v no load

② A_v with load

③ A_i

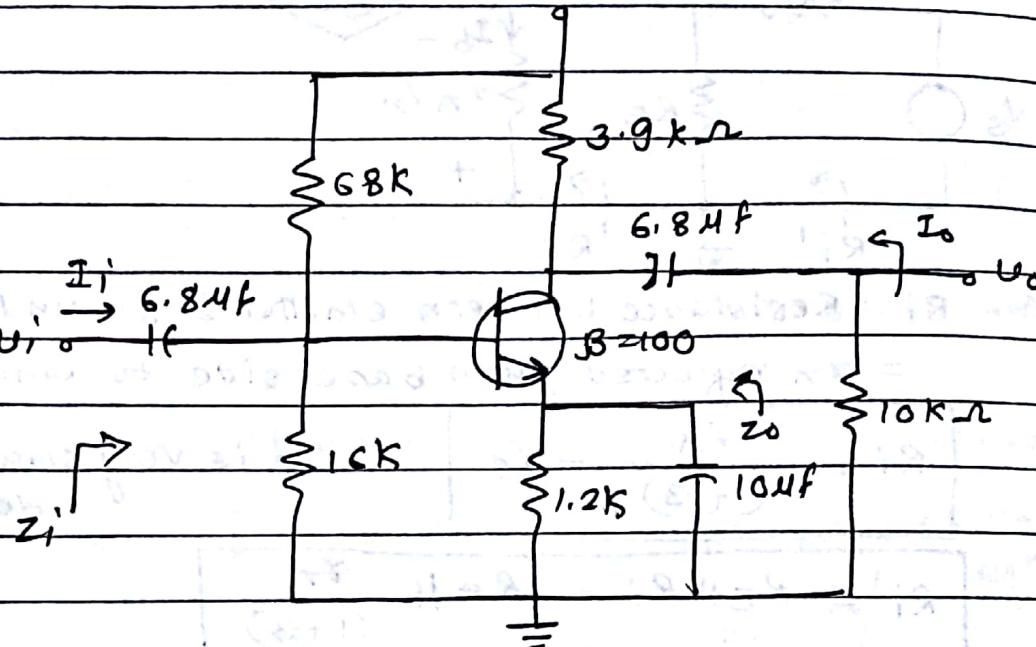

Soln - ckt - CE amplifier with bypassed R_E

Step ① DC analysis

Thevenin's DC equivalent

$$V_{TH} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{16}{16 + 68} \times 16 = 3V$$

$$R_B = R_1 \parallel R_2 = 16 \parallel 68 = \frac{16 \times 68}{16 + 68} = 12.95k\Omega$$

$$R_E = 1.2k\Omega$$


$$I_B = \frac{V_{TH} - V_{BE}}{R_B + (1 + \beta) R_E} = \frac{3 - 0.7}{12.95k\Omega + (101 \times 1.2k\Omega)} = 17.15mA$$

$$I_{CQ} = \beta I_B = 100 \times 17.15mA = 1.715mA$$

$$\text{Let } V_T = 26mV \quad r_\pi = \frac{V_T \beta}{I_{CQ}} = \frac{26 \times 100}{1.715} = 1.516k\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.715}{26 \times 10^{-3}} = 65.96mA/V, \quad r_o = \frac{V_A}{I_{CQ}} = \infty$$

Step ② Small Signal Analysis -

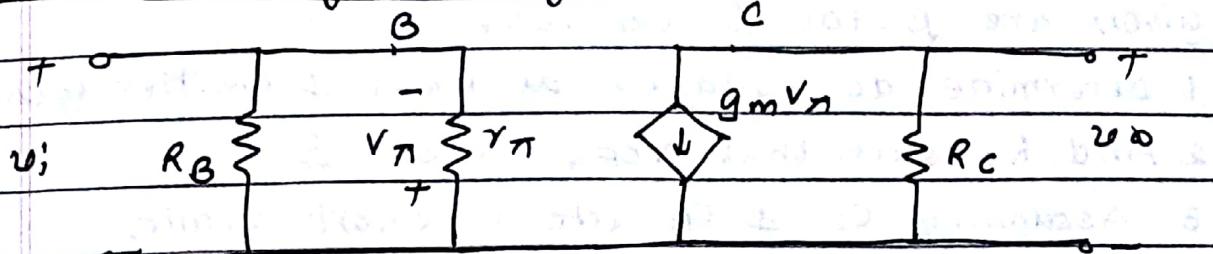

Small Signal Equivalent Model (Without Load)

$$R_i = r_\pi = 1.516 \text{ k}\Omega$$


$$R_i' = R_B \parallel R_i = 1.516 \text{ k} \parallel 12.95 \text{ k} = 1.357 \text{ k}\Omega$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_m V_\pi R_c}{r_\pi} = \frac{-g_m R_c}{V_\pi} = -65.96 \times 3.9 = -257.244$$

$$R_o = \infty$$

$$R_o' = R_c = 3.9 \text{ k}\Omega$$
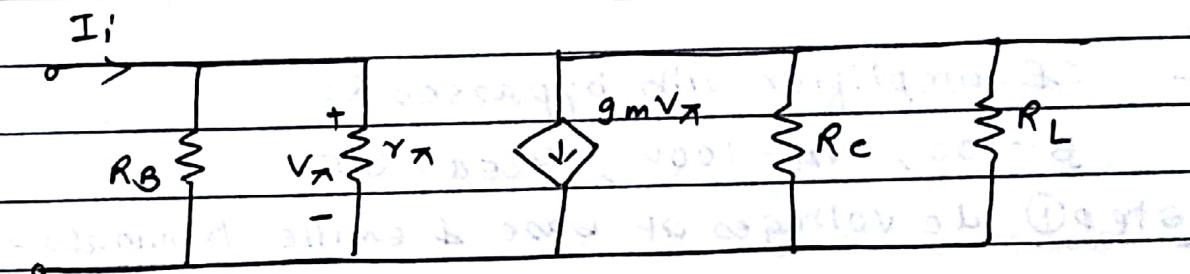
$$A_v = -g_m (R_c \parallel R_L) = -65.96 (3.9 \parallel 10) = -65.96 \times 2.805 = -185$$



$$A_i = \frac{I_o}{I_b} = \frac{I_o}{I_c} \times \frac{I_c}{I_b} \quad \text{But } I_o = -\frac{R_c}{R_c + R_L} \times I_c$$

$$\frac{I_o}{I_c} = -\frac{R_c}{R_c + R_L}, \quad \frac{I_c}{I_b} = \frac{g_m V_\pi}{V_\pi / r_\pi} = g_m r_\pi$$

$$A_i = -\frac{R_c}{R_c + R_L} \times g_m r_\pi$$


$$A_i = (-65.96 \times 1.516) \times \frac{3.9}{3.9 + 10} = -28.05$$

Ex(2) The parameters of the 'transistor' in the circuit given are $\beta = 100$ & $V_A = 100V$

1. Determine dc voltages at base & emitter terminals.
2. Find R_C such that $V_{CEQ} = 3.5V$ &
3. Assuming C_C & C_E acts as short circuit, determine small signal voltage gain $A_V = \frac{V_O}{V_S}$

Determine small signal voltage gain $A_V = \frac{V_O}{V_S}$


(May 14, 10 marks)

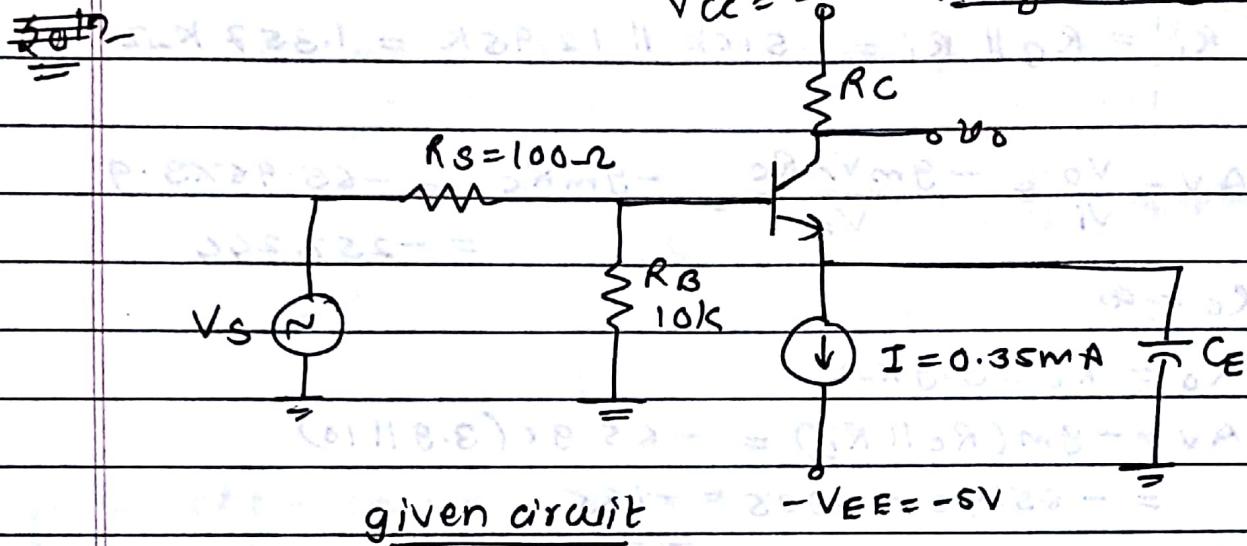

Soln - CE amplifier with bypassed R_E

$$\beta = 100, V_A = 100V, V_{CEQ} = 3.5V$$

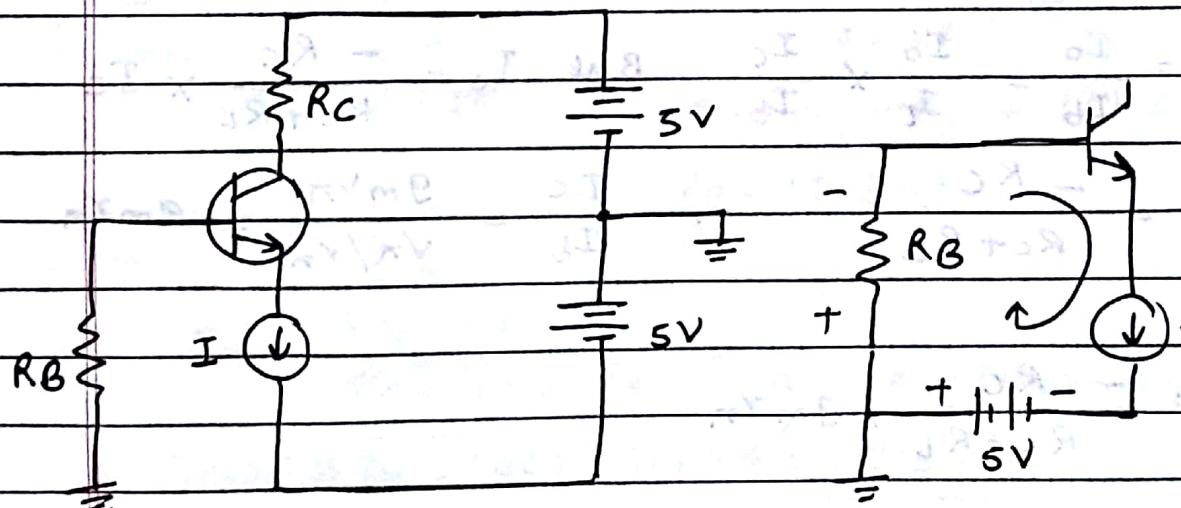step ① dc voltages at base & emitter terminals -




$$I_B = \frac{I_E}{1+\beta} = \frac{I}{1+\beta} = \frac{0.35 \times 10^{-3}}{101} = 3.47 \mu A$$

$$V_B = -I_B R_B = -3.47 \times 10^{-6} \times 10 \times 10^3 = -0.0347V$$

$$V_E = V_B - 0.7 = -0.0347 - 0.7 = -0.7347V$$

Step ② find R_C

$$V_{CEQ} = 3.5V$$

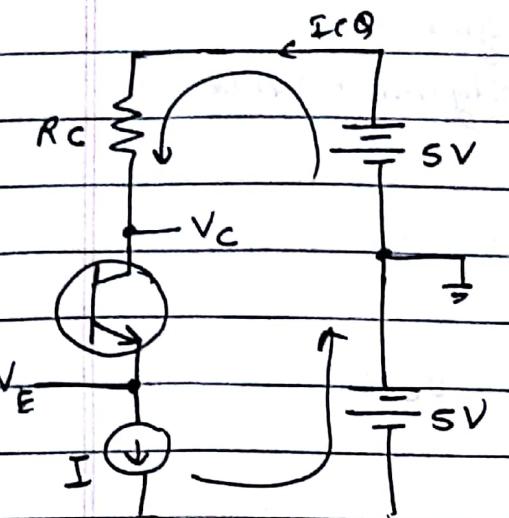

$$V_{CEQ} = V_C - V_E$$

$$3.5V = V_C - (-0.7347)$$

$$V_C = 2.77V$$

$$R_C = \frac{5V - V_C}{I_{CQ}}$$

$$\text{assuming } I_{CQ} = I = 0.35mA$$

$$R_C = \frac{5 - 2.77}{0.35 \times 10^{-3}} = 6.37k\Omega$$

Step ③


$$\gamma_\pi = \frac{V_T \cdot \beta}{V_{CQ}}$$

assume $V_T = 26mV$

$$\gamma_\pi = \frac{26 \times 10^{-3} \times 100}{0.35 \times 10^{-3}} = 743k\Omega$$

$$\gamma_0 = \frac{V_A}{I_{CQ}} = \frac{100}{0.35 \times 10^{-3}} = 285.7k\Omega$$
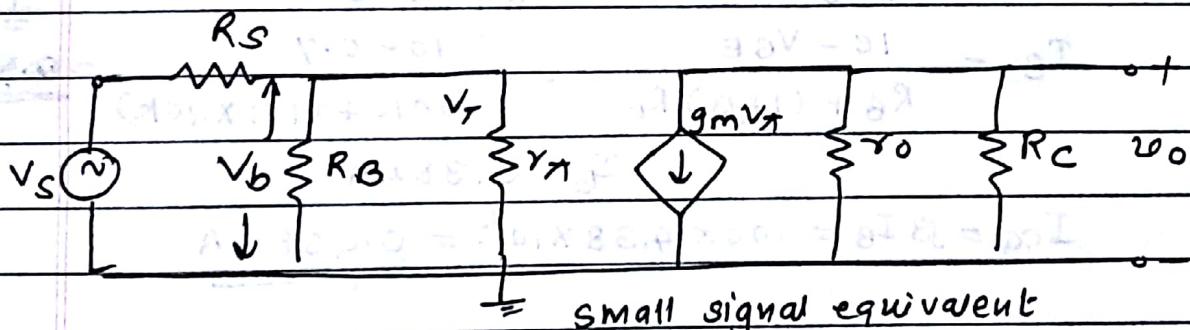
$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.35mA}{26 \times 10^{-3}V} = 13.46mA/V$$



$$\text{Voltage gain } A_V = \frac{V_o}{V_b} = -g_m V_\pi (\gamma_0 || R_C) \quad \text{But } V_b = V_\pi$$

$$\therefore A_V = -g_m (\gamma_0 || R_C) = -13.46 [285.7k \parallel 6.37k] = -83.87$$


$$A_{VS} = \frac{V_o}{V_S} = \frac{R_i}{R_i + R_S} \cdot A_V \quad \text{where } R_i = R_B \parallel \gamma_\pi$$

$$= 10k \parallel 7.43k$$

$$= 4.26k\Omega$$

$$A_{VS} = \frac{V_o}{U_i} = \frac{4.26}{4.26 + 0.1} \times -83.87 = \underline{\underline{-81.94}}$$

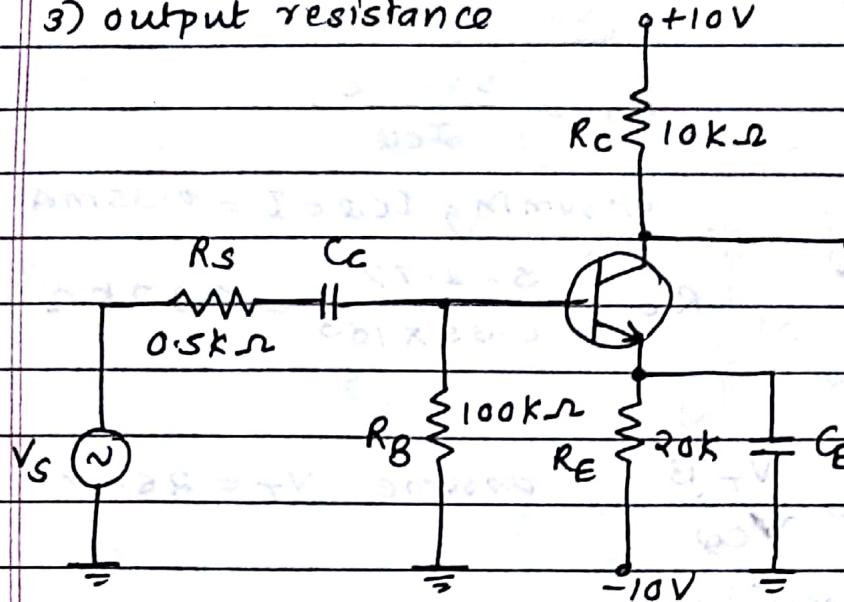- Ex(3) For the circuit shown in fig. let $\beta = 100$, $V_A = 100V$, $V_{BE(on)} = 0.7V$
 determine
 1) small signal voltage gain
 2) input resistance seen by the signal source
 3) output resistance



Soln:- given $\beta = 100$, $V_A = 100V$, $V_{BE(on)} = 0.7V$

DC Analysis -

① find I_{CQ} -

Apply KVL to Base loop,

$$10V = I_B R_B + V_{BE} + (1+\beta) I_B R_E$$

$$I_B = \frac{10 - V_{BE}}{R_B + (1+\beta) R_E} = \frac{10 - 0.7}{100k + (101 \times 20k)} = 4.38 \mu A$$

$$I_{CQ} = \beta I_B = 100 \times 4.38 \times 10^{-6} = 0.438 mA$$

step ② calculate g_m , r_π & r_o -


$$r_\pi = \frac{V_T \beta}{I_{CQ}} = \frac{26 \times 100}{0.438} = 5.94 k\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.438}{26 \times 10^{-3}} = 16.85 mA/V$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{100}{0.438 \times 10^{-3}} = 228.3 k\Omega$$

AC Analysis -

Step ③ Draw hybrid π equivalent ckt

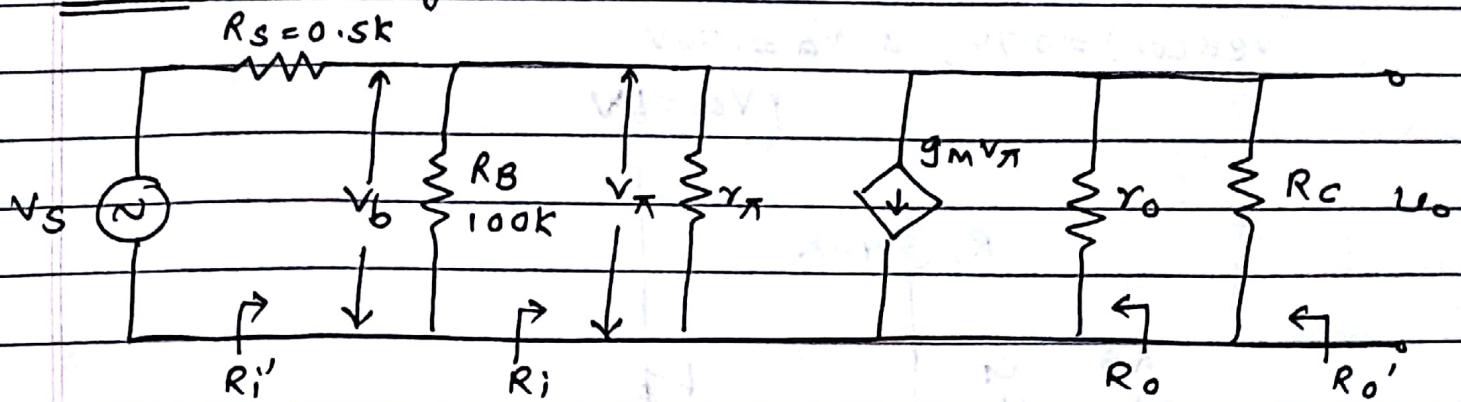

g_{lp} resistance - $R_i = r_\pi = 5.94k\Omega$

$$R_i' = R_i \parallel R_B = 5.94k \parallel 100k = 5.6k\Omega$$

Step ④ Voltage gain (A_{V_s}) -

$$A_{V_s} = \frac{V_o}{V_s} = \frac{V_o}{V_\pi} \times \frac{V_\pi}{V_s}$$

$$V_o = -g_m V_\pi (r_o \parallel R_C)$$

$$\frac{V_o}{V_\pi} = -g_m (r_o \parallel R_C)$$

$$V_\pi = \frac{R_i'}{R_s + R_i'} \cdot V_s$$

$$\frac{V_\pi}{V_s} = \frac{R_i'}{R_s + R_i'}$$

$$A_{V_s} = -g_m (r_o \parallel R_C) \times \frac{R_i'}{R_i' + R_s}$$

$$= -16.85(228.3k \parallel 10k) \frac{5.6}{(5.6 + 0.5)}$$

$$A_{V_s} = -148.2$$

Step ⑤ Output Resistance -

$$R_o = r_o = 228.3k\Omega$$

$$R_o' = r_o \parallel R_C = 228.3k \parallel 10k$$


$$R_o' = 9.58k\Omega$$

CC AMP


PAGE No.	/ /
DATE	/ /

Ex(4) calculate the small signal voltage gain for the emitter follower circuit shown in fig. Assume that $\beta = 100$, $V_{BE(on)} = 0.7V$, & $V_A = 100V$

$$V_{cc} = 6V$$

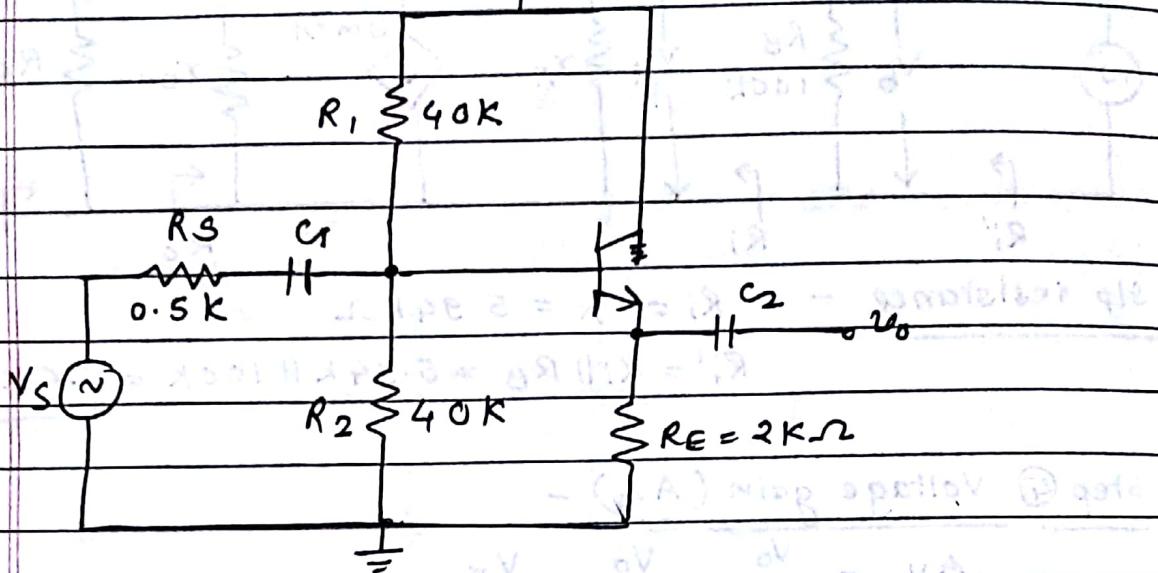Soln DC analysis
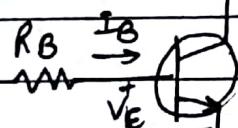
$$R_B = R_1 \parallel R_2 = 40k \parallel 40k = 20k$$



$$V_{TH} = \frac{R_2}{R_1 + R_2} \times V_{cc}$$

$$= \frac{40k}{40k + 40k} \times 6V$$

$$V_{TH} = 3V$$

Thevenin's equivalent circuit

$$I_B = \frac{V_{TH} - V_{BE}}{R_B + (1+\beta)R_E} = \frac{3 - 0.7}{20k + (100 \times 2k)} = 10.36mA$$


$$\& I_{CQ} = \beta I_B = 100 \times 10.36 \times 10^{-6} = 1.036mA$$

AC Analysis


$$\text{calculate } r_\pi \& r_o, \quad r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{100 \times 26mV}{1.036mA} = 2.509k\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{100}{1.036 \times 10^{-3}} = 96.525 \times 10^3 k\Omega$$

DRAW AC equivalent ckt

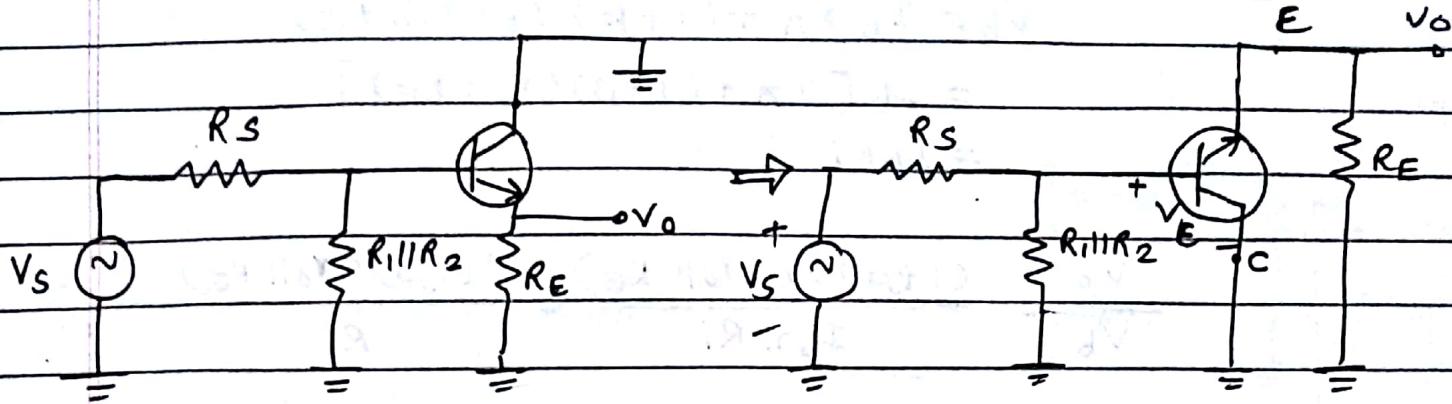

DRAW the hybrid π equivalent ckt-

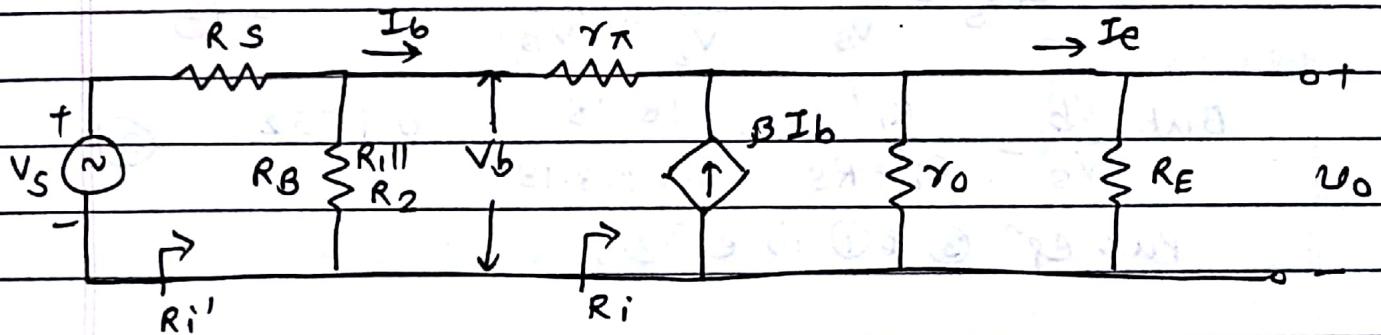

calculate R_i & R_i' -

$$R_i = \frac{V_o}{I_b} \quad \text{Apply KVL to o/p loop,}$$

$$\begin{aligned} V_b &= I_b r_\pi + (1+\beta) I_b (r_o \parallel R_E) \\ &= I_b [r_\pi + (1+\beta) (r_o \parallel R_E)] \end{aligned}$$

$$\begin{aligned} R_i &= \frac{I_b [r_\pi + (1+\beta) (r_o \parallel R_E)]}{I_b} = r_\pi + (1+\beta) (r_o \parallel R_E) \\ &= 2.509k + 101(96.525k \parallel 2k) \end{aligned}$$

$$R_i = 200.408k\Omega$$

$$R_i' = (R_1 \parallel R_2) \parallel R_i = 20k \parallel 200.408k = 18.18k\Omega$$

calculate o/p voltage -

$$\begin{aligned} V_o &= (\beta I_b + I_b) \times (r_o \parallel R_E) \\ &= (1+\beta) I_b (r_o \parallel R_E) \end{aligned}$$

calculate V_b - Apply KVL to outer loop

$$V_b = I_b r_\pi + (1+\beta) I_b (r_{\text{oll}} || R_E)$$

$$= I_b [r_\pi + (1+\beta)(r_{\text{oll}} || R_E)]$$

$$= I_b R_i$$

$$\frac{V_o}{V_b} = \frac{(1+\beta) I_b (r_{\text{oll}} || R_E)}{I_b R_i} = \frac{(1+\beta)(r_{\text{oll}} || R_E)}{R_i}$$

calculate voltage gain

$$A V_S = \frac{V_o}{V_S} = \frac{V_o}{V_b} \times \frac{V_b}{V_S}$$

$$\text{But } \frac{V_b}{V_S} = \frac{R_i'}{R_i' + R_S} = \frac{18 \cdot 18}{0.5 + 18 \cdot 18} = 0.9732$$

Put eqn ③ & ① in eqn ②,


$$A V_S = \frac{(1+\beta)(r_{\text{oll}} || R_E)}{R_i'} \times 0.9732$$

$$= 101 \times (98.525 \text{ k} \parallel 2 \text{ k}) \times 0.9732$$

$$AV_S = 0.961$$

O/P Resistance -

Put $V_S = 0$

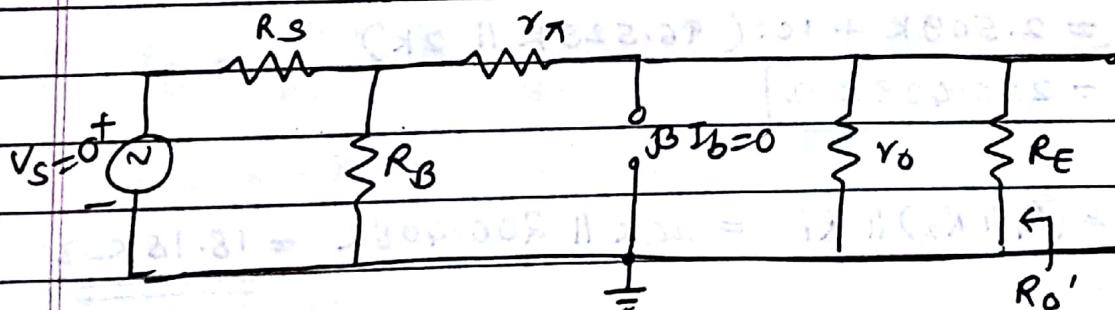


$$R_o' = \frac{[(R_S + R_B) + r_\pi]}{(1+\beta)} \parallel (r_{\text{oll}} || R_E)$$

$$= \frac{[0.5 \parallel 20] + 2.509}{101} \parallel (98.525 \parallel 2) = 29.22 \Omega$$


$$R_o' = 29.22 \Omega$$

CB Amplifier (Ex 1) Determine R_i , R_o , A_v & g_m for amplifier shown in given figure.

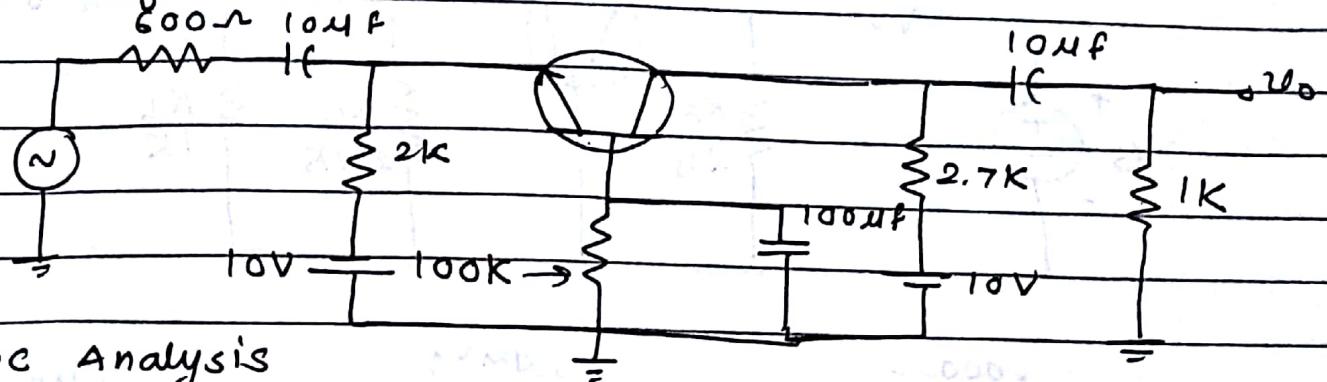

Sol 1) DC Analysis

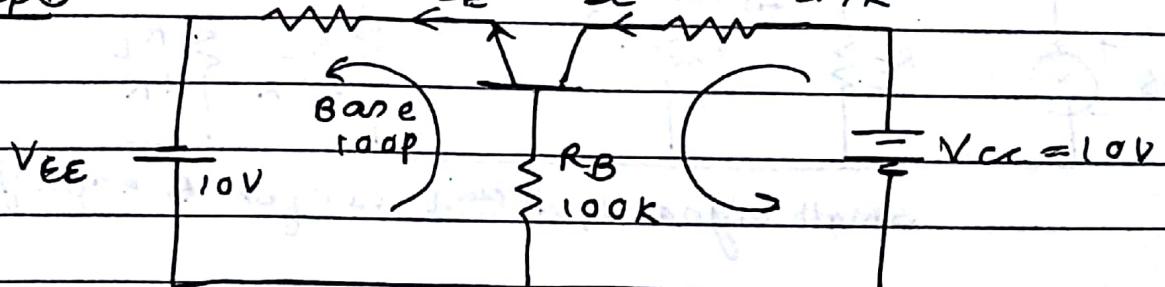Step ① $R_E = 2k \quad I_E \quad R_C = 2.7k$



Apply KVL to base loop,

$$V_{BE} + I_E R_E - 10 + I_B R_B = 0$$

$$V_{BE} + (1 + \beta) I_B R_E + I_B R_B = 10$$

$$I_B = \frac{10 - V_{BE}}{[(1 + \beta) R_E + R_B]} = \frac{10 - 0.7}{(101 \times 2000) + 10000} = 30.79 \text{ mA}$$

$$I_{CQ} = \beta I_B = 100 \times (30.79 \text{ mA}) = 3.079 \text{ mA}$$

Step ② calculate γ_π , γ_o & g_m



$$\gamma_\pi = \frac{V_T \beta}{I_{CQ}} = \frac{26 \times 10^{-3} \times 100}{3.079 \times 10^{-3}} = 844.43 \Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{3.079 \text{ mA}}{26 \times 10^{-3}} = 118.42 \text{ mA/V}$$

$$\gamma_o = \frac{V_A}{I_{CQ}} = \infty \quad (\because V_A = \infty)$$

AC Analysis

Step ③ Draw AC equivalent circuit.

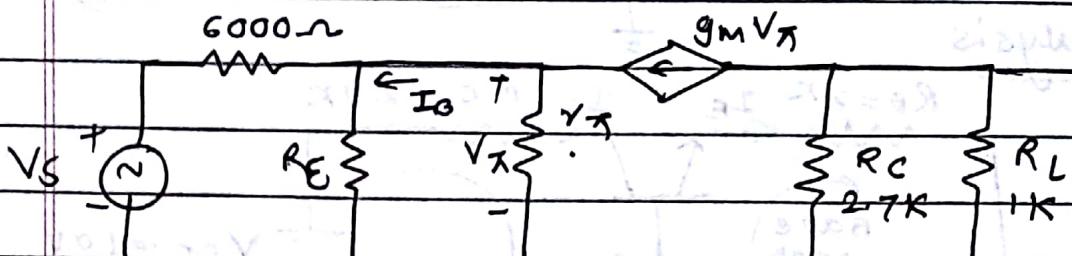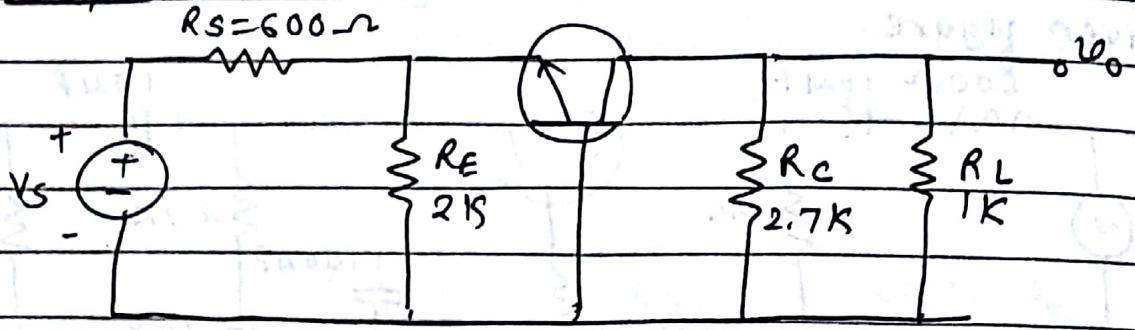

small signal equivalent circuit for common emitter amplifier

Step ④ calculate R_i , R_o , A_V

$$R_i = \frac{r_\pi + R_E}{(1+\beta)} = \frac{84.43}{101} = 836\ \Omega$$

$$R_o = R_C = 2.7\text{k}\Omega$$

$$A_V = g_m (R_C || R_L) = 0.118 (2.7\text{k}\Omega || 1\text{k}\Omega) = 86.108$$

(Ex 2) For the common Base circuit shown, the transistor has parameters $\beta = 120$ & $V_A = \infty$

- ① Determine the quiescent V_{CEQ}
- ② Determine the small signal voltage gain & output resistance

(May 2016, 10')

