


* Class B Amplifiers :-

- amplify half of i/p cycle.
- creates large amount of distortion
- Improved efficiency 78.5% ($\pi/4$)
- Amplifying element is switched off altogether half of the time so can't dissipate power.




* Class B pushpull Amplifiers :-

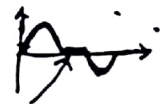- practical ckt using class B is complementary pair or "push-pull" arrangement.
- complementary or Quasi-complementary devices are used to each amplify opposite halves of i/p & then recombined at o/p.
- This provides excellent efficiency.



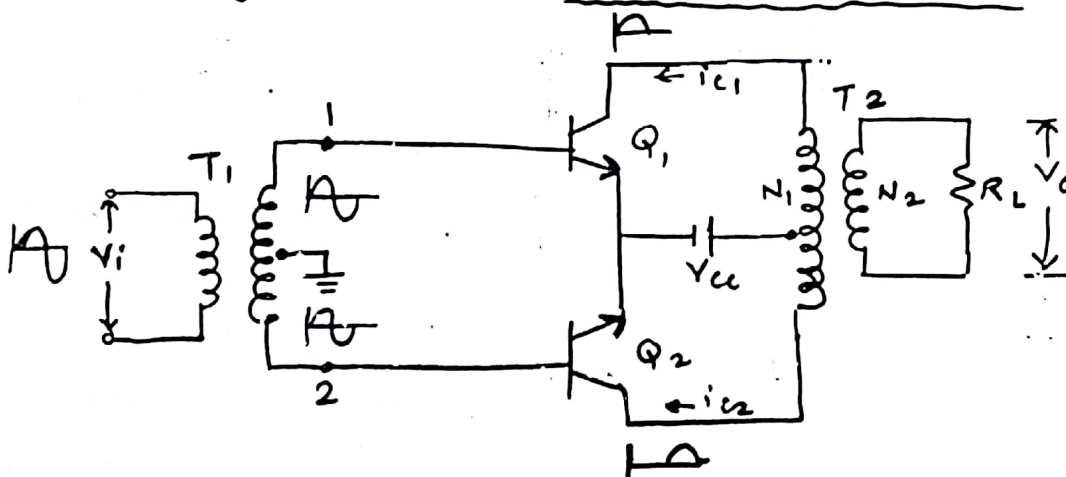But there is a small mismatch at "joins" betⁿ two halves of signal, called crossover distortion.




(1:1:1)
 T_1 : i/p transformer
 T_2 : o/p x'former

- Q_1, Q_2 are biased in cut off (No biasing v/bg at base)


- since Q pt is shifted to cutoff, one transistor will conduct for one half cycle of i/p V_i

- For +ve half cycle, V_i at pt ① = +ve & at pt ② -ve
 Q_1 conducts Q_2 off

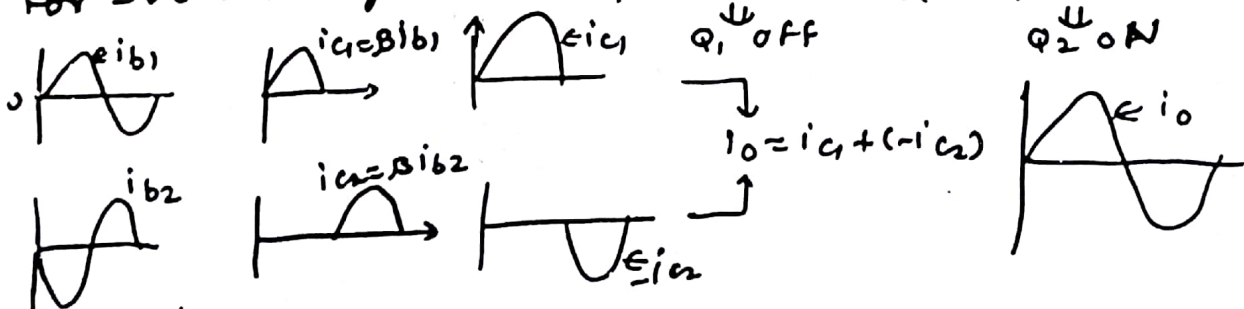- For -ve half cycle V_i at pt ① = -ve & at pt ② +ve
 Q_1 off Q_2 on



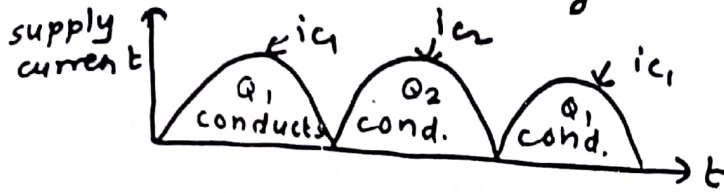
current taken from V_{CC} is in same direction wheather Q_1 or Q_2 is conducting. (16)



① DC Analysis:-

- For both Q_1 & Q_2 , V_{CC} , collector & base currents are same hence both transistors have same ckt.

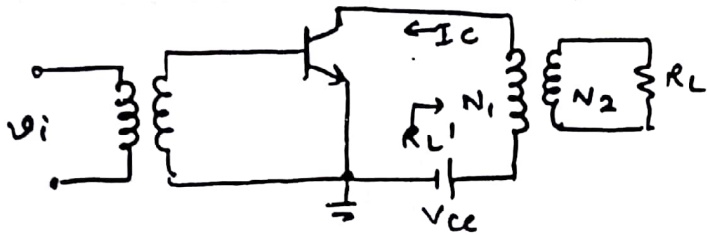\therefore we can do all analysis on only 1 transistor.



\therefore Base biasing is zero,

$$I_{BQ} = 0 \therefore I_{CQ} = \beta I_{BQ} = 0$$

& DC resistance of transformer primary $\cong 0$

$$\therefore V_{CEQ} = V_{CC} \therefore Q \text{ pt } (V_{CC}, 0)$$

Hence DC load line = with slope $-1/R_C = 1/R_P = \infty$

② AC loadline -

- consider R_L' (R_L seen from primary) Apply KVL in collector L

$$V_{CC} - I_C R_L' - V_{CE} = 0$$

$$\therefore I_C = \left(-\frac{1}{R_L'}\right) V_{CE} + \frac{V_{CC}}{R_L'}$$

$$y = mX + c$$

To find 2 pts


$$i) \text{ In Sat, } V_{CE} = 0, \therefore I_C = \frac{V_{CC}}{R_L'}$$

$$ii) \text{ in cutoff, } I_C = 0$$

$$\therefore V_{CE} = V_{CC}$$

\therefore 2 pts for AC load line
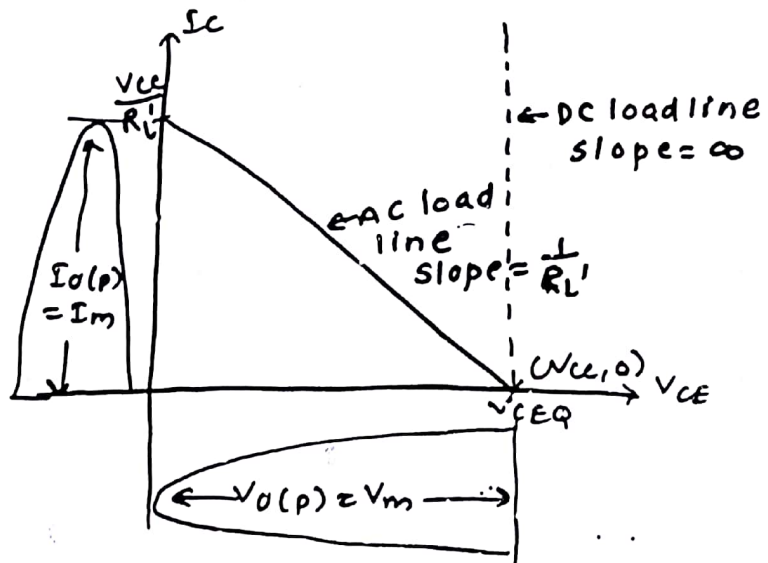
$$\left(0, \frac{V_{CC}}{R_L'}\right) \text{ \& } (V_{CC}, 0)$$



③ P_{ac} given to load -

$$P_{ac} = \frac{V_{rms}^2}{R_L'} = \frac{(V_m/\sqrt{2})^2}{R_L'} = \frac{V_m^2}{2R_L'}$$

$$P_{acmax} = \frac{V_{CC}^2}{2R_L'} \therefore (V_m \text{ is max}) \text{ for max power } V_{CC} = V_m$$

④ DC power i/p to ampl^r (P_{dc})

$$\frac{I_m}{\sqrt{2}} \text{ } \frac{I_m}{\sqrt{2}} \text{ } \frac{I_m}{\sqrt{2}} \therefore I_{av} = \frac{2I_m}{\pi}$$

$$I_m = \frac{V_{CC}}{R_L'} \therefore I_{av} = \frac{2V_{CC}}{\pi R_L'}$$

$$\therefore P_{dmax} = V_{CC} \times I_{av} = V_{CC} \times \frac{2V_{CC}}{\pi R_L'} = \frac{2V_{CC}^2}{\pi R_L'}$$

$$\therefore P_{dmax} = \frac{2V_{CC}^2}{\pi R_L'} = \frac{2V_{CC} \cdot V_m}{\pi R_L'}$$

⑤ Max efficiency :-

$$\% \eta_{\max} = \frac{P_{ac\max}}{P_{dc\max}} \times 100 = \frac{V_{cc}^2}{2R_{L'}} \times \frac{R_{L'} \cdot \pi}{2V_{cc}^2} \times 100 = \frac{\pi}{4} = \underline{\underline{78.5\%}}$$

⑥ Power dissipation in transistor :-

$P_{dc} \Rightarrow$ was for both transistors (\because At a time only one transistor conducts).

$$2P_D = P_{dc} - P_{ac}$$

$$2P_D = \frac{2V_{cc} \cdot V_m}{\pi R_{L'}} - \frac{V_m^2}{2R_{L'}} \quad \therefore \boxed{P_D = \frac{V_{cc} \cdot V_m}{\pi R_{L'}} - \frac{V_m^2}{4R_{L'}}} \quad \text{--- (A)}$$

To find $P_{D\max}$ differentiate P_D wrt V_m & equate to zero

$$\frac{dP_D}{dV_m} = \frac{V_{cc}}{\pi R_{L'}} - \frac{2V_m}{4R_{L'}} = 0$$

$$\therefore \frac{V_{cc}}{\pi R_{L'}} = \frac{2V_m}{4R_{L'}} \quad \therefore \boxed{V_m = \frac{2V_{cc}}{\pi}} \quad \text{put in (A)}$$

$$P_{D\max} = \frac{V_{cc}}{\pi R_{L'}} \cdot \frac{2V_{cc}}{\pi} - \frac{4V_{cc}^2}{\pi^2} \cdot \frac{1}{4R_{L'}} = \frac{2V_{cc}^2}{\pi^2 R_{L'}} - \frac{V_{cc}^2}{\pi^2 R_{L'}}$$

$$\boxed{P_{D\max} = \frac{V_{cc}^2}{\pi^2 R_{L'}}$$

⑦ Figure of Merit (FM)

$$FM = \frac{P_{D\max}}{P_{ac\max}} = \frac{V_{cc}^2}{\pi^2 R_{L'}} \cdot \frac{2R_{L'}}{V_{cc}^2}$$

$$\boxed{FM = 0.2} \quad \therefore P_{D\max} = 0.2 P_{ac\max}$$

Outputs :-

Biassing \rightarrow in cutoff region

No of Transistors \rightarrow 2 one for each half cycle

\rightarrow 78.5% better than class A

η_{\max}

FM

$\rightarrow 0.2$

Disadvantage :-

- High non linear distortion

- cross over distortion


- 2 transistors & 2 transformers are required hence size increases.

* Class B Complementary Symmetry Power Amplifiers:- (18) or Transformerless PA :-


- In single ended or push pull (double ended) amplr, phase shifting x'mers, impedance matching x'mers & bypass capacitors are used. These components makes amplr bulky, costly & not suitable for IC

To overcome this problems complementary symmetry PA are used. →

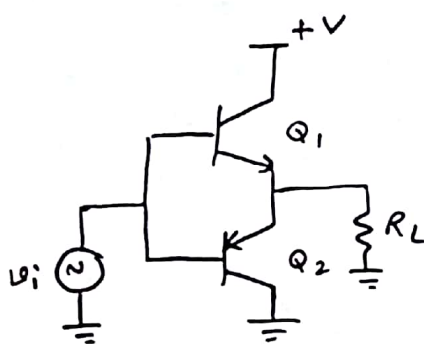
- In this we use nearly matched pair of NPN & PNP transistor instead of phase shifting x'mer
- Operation of transistor is in CC configuratⁿ ∴ gts low o/p impedance nearly matches with that of low i/p impedance of load (speakers).



ckt diagram

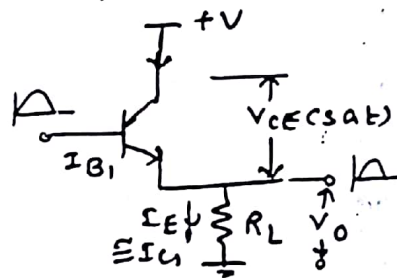

$u_i = +ve$ Half cycle
 Q_1 ON, Q_2 OFF

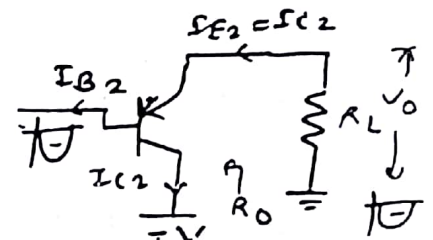


$u_i = -ve$ half
 Q_1 OFF Q_2 ON

For +ve Half cycle :-

- Q_1 is ON, Q_2 OFF
- ckt works as CC amplr with v_o in phase with u_i with high current gain (No vtg gain)
- gives Higher Power η
- ∴ R_o is small $\approx R_L$ (coil resist of speaker) so max power transfered
- Higher η is achieved.

current drawn:-

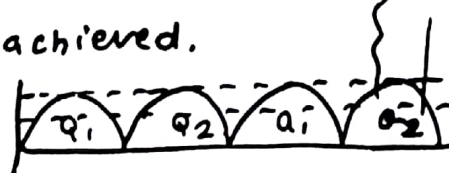

For -ve Half cycle :-

- Q_1 is OFF, Q_2 ON
- works as CC amplr
- o/p is -ve half cycle with high current gain & impedance matching is obtained for max power transfer.

$$I_{DC} = I_{av} = \frac{2I_m}{\pi} = \frac{2}{\pi} \cdot \frac{V_m}{R_L}$$

DC load line :-


∴ DC & AC load lines are same with slope $(-1/R_L)$

$$V_{CC} - I_C R_L - V_{CE} = 0$$

$$I_C = \left(-\frac{1}{R_L}\right) V_{CE} + \frac{V_{CC}}{R_L}$$

$$Y = mx + c$$

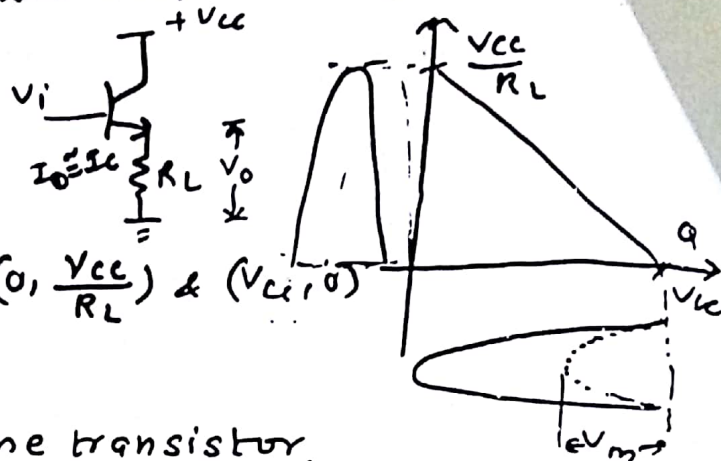∴ Points for load line will be $(0, \frac{V_{CC}}{R_L})$ & $(V_{CC}, 0)$



Power calculations :-

- Assuming operation of only one transistor,

$$V_{CE(sat)} = 0 \quad I_{Cmin} = 0$$

$$a) P_{DC} = V_{CC} \cdot I_{DC} = \frac{V_{CC} \cdot 2 I_m}{\pi R_L} \quad \boxed{P_{DCmax} = \frac{2 V_{CC}^2}{\pi R_L}}$$

$$b) P_{AC} = \frac{(V_m/\sqrt{2})^2}{R_L} = \frac{V_m^2}{2 R_L} \quad \boxed{P_{ACmax} = \frac{V_{CC}^2}{2 R_L}}$$

$$c) \% \eta_{max} = \frac{P_{ACmax}}{P_{DCmax}} \times 100 = \frac{V_{CC}^2}{2 R_L} \times \frac{\pi R_L}{V_{CC}^2} \times 100 = \underline{\underline{78.5\%}}$$

$$d) \text{Power dissipated by both transistors} = P_{DC} - P_{AC} \\ = \frac{2 V_m V_{CC}}{\pi R_L} - \frac{V_m^2}{2 R_L} = P_{D'} \\ \therefore P_D / \text{transistor} = \frac{P_{D'}}{2} = \frac{V_m V_{CC}}{\pi R_L} - \frac{V_m^2}{4 R_L}$$

To find P_{Dmax} differentiating P_D wrt V_m & $= 0$

$$\therefore V_m = \frac{2 V_{CC}}{\pi} \therefore P_{Dmax} = \frac{V_{CC}}{\pi R_L} \times \frac{2 V_{CC}}{\pi} - \frac{1}{4 R_L} \times \frac{4 V_{CC}^2}{\pi^2}$$



$$\boxed{P_{Dmax} = \frac{V_{CC}^2}{\pi^2 R_L}}$$

e) Figure of Merit :-

$$FM = \frac{P_{Dmax}}{P_{ACmax}} = \frac{V_{CC}^2}{\pi^2 R_L} \times \frac{2 R_L}{V_{CC}^2} = 0.2$$

$$\therefore \boxed{P_{Dmax} = 0.2 P_{ACmax}}$$

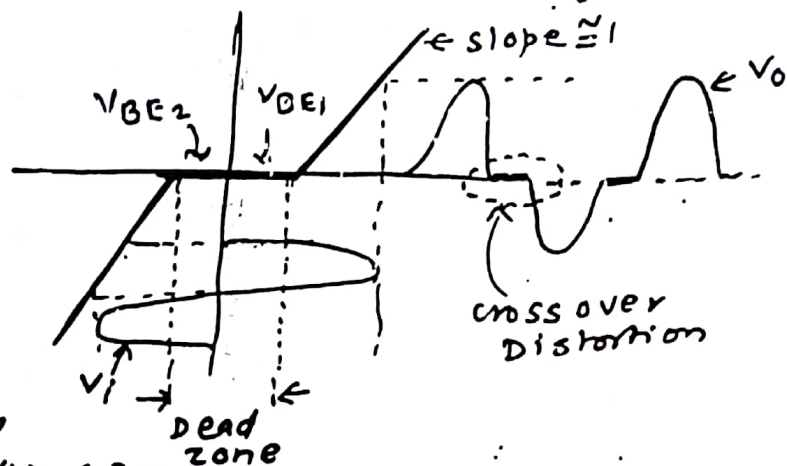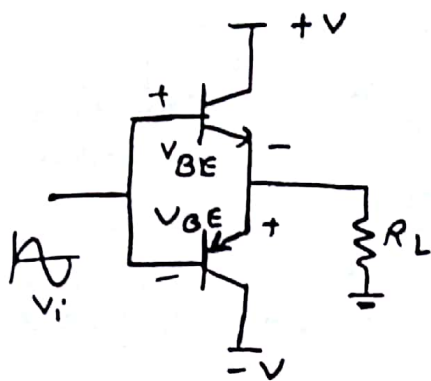* Cross over Distortion in complementary Symmetry PA :- (2.0)



- Assuming $V_{BE1} = V_{BE2} = V_{BE}$

- $V_o = V_i - V_{BE}$ for $-0.7V \gg V_i \gg 0.7V$

- But for interval $-0.7V \gg V_i \gg 0.7V$, both Q_1 & Q_2 are in cutoff & $V_o = 0$

This causes Deadzone & cross over Distortion.


Methods to overcome :-

① Make $V_{BE} = \frac{V_{BB}}{2}$

- When Q_1 is conducting

$$V_o = V_i + \frac{V_{BB}}{2} - V_{BE}$$

$$V_o = V_i$$

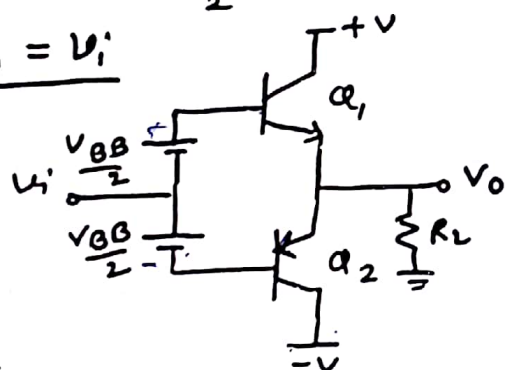


But as temp ↑, $V_{BE} \downarrow$,

$I_B \uparrow$, $I_C \uparrow$, P_D (heat) ↑↑

$I_C \uparrow$, → device may get damaged.

(Because of thermal runaway)

② Diode Biasing

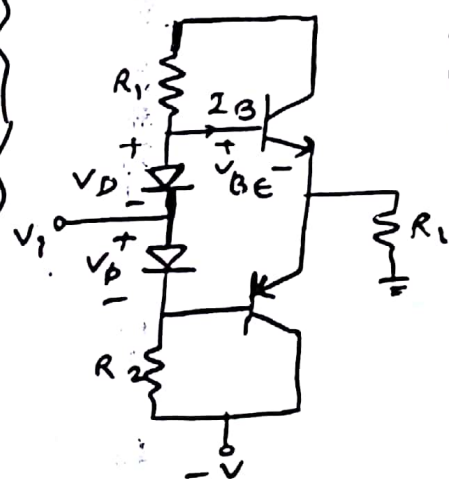




diodes are having same temp coeff for V_D as that of V_{BE}

as temp ↑, $V_{BE} \downarrow$ I_B tries to increase but sometime



V_D also ↓ by same amount ∴ $I_D \uparrow$ keeping I_B constant & avoids thermal runaway.

* Class C Amplifier :-

- Q pt is located below cutoff & o/p current flows for less than half of the i/p cycle.
- current flow in the form of pulses.
- Efficiency is very high
- Angle of conduction of transistor $< 180^\circ$
- \therefore o/p is in the form of pulses it will contain lot of harmonics if resistive load is used. Hence tuned Resonant ckt (Tank) is used as load.
- Tank ckt is tuned to fundamental freq of o/p current pulses.

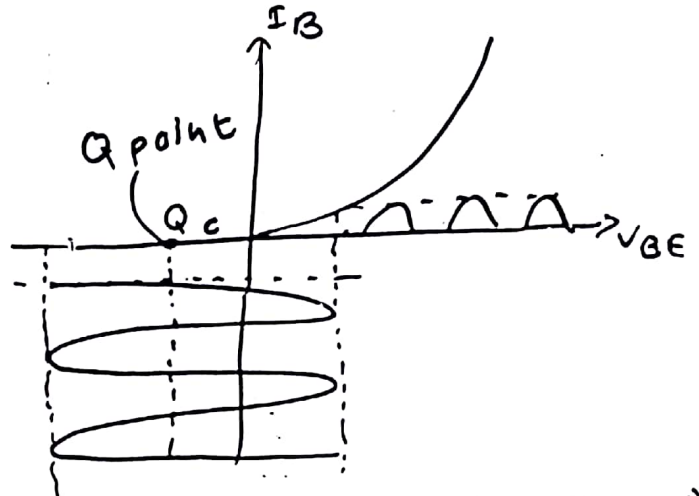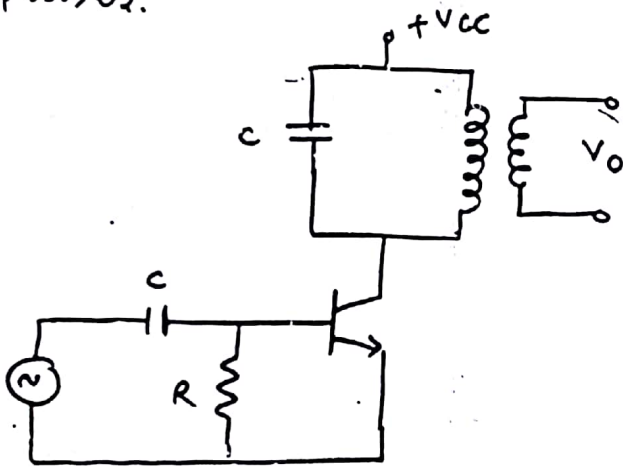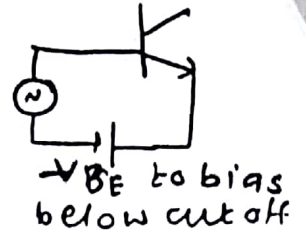

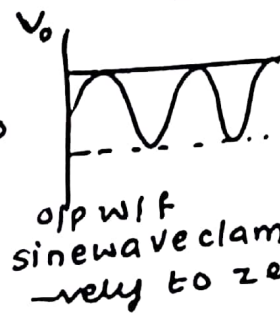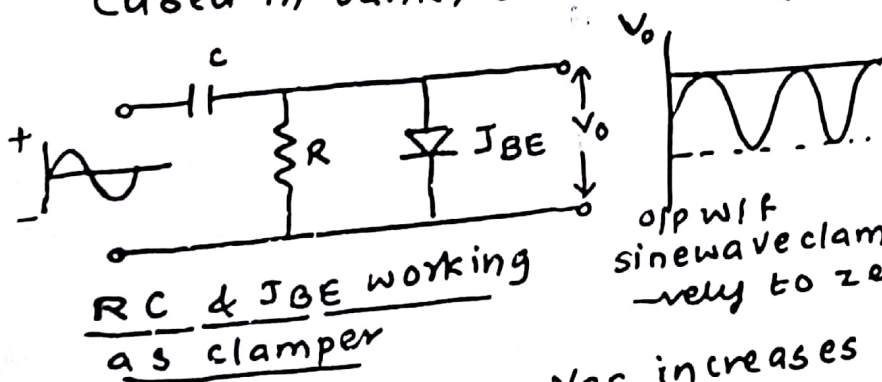- A tuned class c amplifier works as narrow band ampli & can amplify only a small band of freq around resonant freq of tuned ckt.
- It can be used only at RF. Because at AF, size of L & C (used in tank) becomes very large.



- Here RC & JBE works as clammer, & clamps i/p w/f -vely w.r.t OV.

- During each cycle V_{BE} increases beyond zero to make JBE FB during each +ve peak of i/p signal.
- Whenever JBE becomes FB, the operating pt moves from cutoff towards sat \therefore we get narrow collector current pulses.



- The amplitude of these pulses depends upon amplitude of i/p signal.
- The smaller angle of conduct, the less will be average power dissipation $< 180^\circ$ in transistor.
- These pulses when given to tank ckt, we get sine wave across than the freq of which is same as that of i/p signal & amplitude of which depend upon amplitude of pulses.



Applications:-


- ① used in frequency multiplier
 - In this application tank ckt is tuned to 2nd & 3rd harmonic of o/p current pulses.
- ② If f/b is used to strengthen the i/p signal (+ve f/b) then we can get class C oscillator.

* Class AB Pushpull Amplifier:-

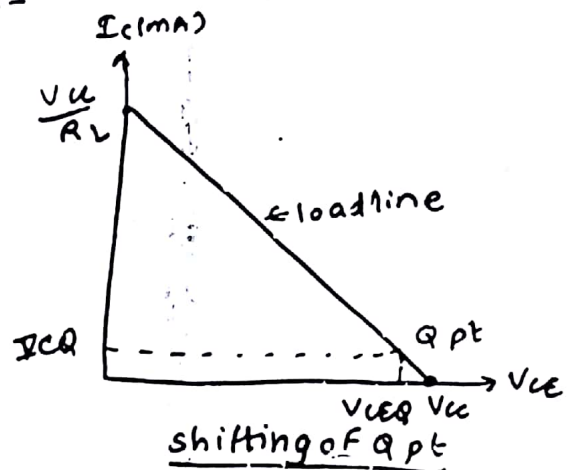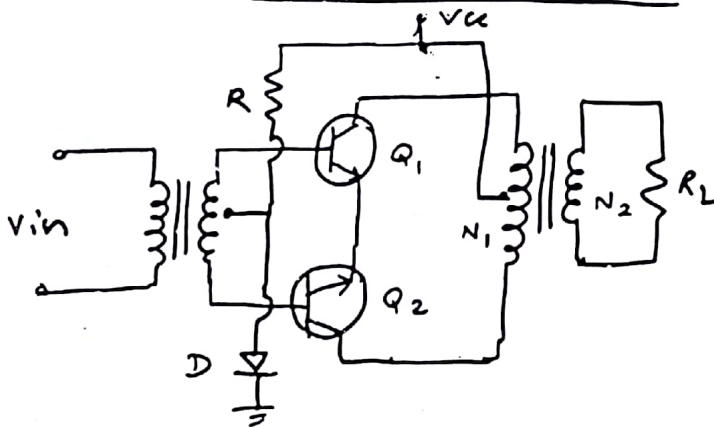

- class B pushpull ampl^r is converted into class AB push pull ampl^r by connecting Resistor R & diode D in the ckt.
- dc v_{tg} across diode is connected to base of both transistors through secondary winding of i/p x'mer.
- This v_{tg} acts as dc bias for transistors because it is equal to cut in v_{tg} & they will conduct for complete half cycle of i/p to eliminate cross over distortion.
- Due to this kind of biasing, Q pt is shifted slightly above x-axis. operation same as class B.

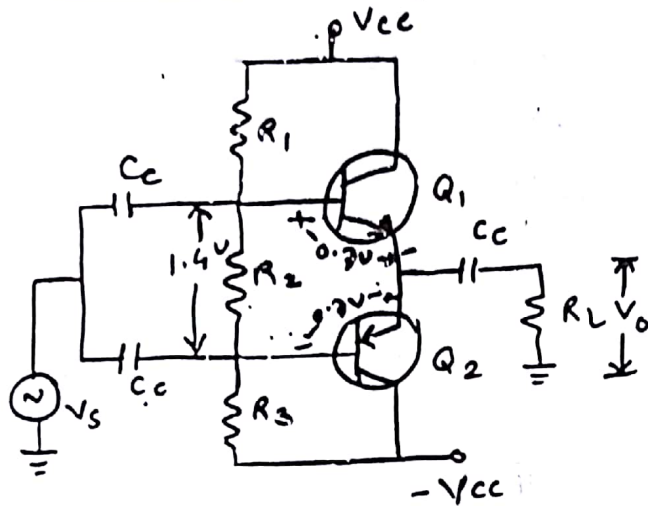* complementary symmetry class AB amplifier:-




→ Here v_{tg} drop across one diode (like push pull) is not sufficient to F.B. the BE junction of both the transistors.

→ 1.4V must appear betⁿ their bases to ensure both BE junctions are F.Bed.

- R_1, R_2 & R_3 are adjusted to give 1.4V const v_{tg} across R_2 .

Drawback:- A fixed bias of 1.4V is applied betⁿ bases of two transistors. But the junction cut in v_{tg} of transistors will change with temp. Thus there is a still possibility of cross over distortion, taking place.

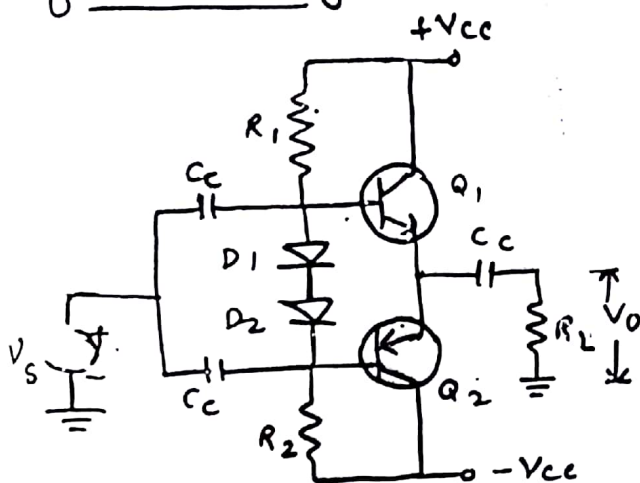* Complementary symmetry class AB Amplifier using Diodes for Biasing:-



- replace R_2 by two series connected diodes to overcome drawback of complementary symmetry class AB

- v_{tg} drop across these diodes will forward bias the BE junction of two transistors.

Advantage:-

diode characteristics are closely matched with char. of BE junction. \therefore changes in temp causes change in v_{tg} drop across diode in same way change in v_{tg} across BE junction. This will eliminate possibility of cross over distortion.

class A

- Q point is selected at the center of active region
- o/p current flows for full cycle of i/p signal
- conduction angle = 360°



- Maximum efficiency

$$\% \eta_{\max} = \frac{P_{ac\max}}{P_{dc}} \times 100 = 50\%$$

- Power dissipatⁿ under no signal condⁿ is max. (disadv)
- Min. one transistor is required
- No crossover distortion
- $P_{D\max} = 2P_{ac\max}$

class B

- Q pt at cutoff
- o/p current only for half cycle
- one transistor conducts for half cycle so 2 transistors are required to obtain class B operation
- $\% \eta_{\max} = 78.54\%$
- Distortion is less, used as linear ampl^r.
- problem of crossover distortion



class B

(24)

- Q pt is set at cutoff region
- o/p current flows for half cycle of i/p signal
- conduction angle = 180°



- Maximum efficiency

$$\% \eta_{\max} = 78.54\%$$

- Power dissipatⁿ under no load condⁿ is zero. Hence it is used as o/p stage of Radio and TV receivers
- Two transistors are required
- crossover distortion
- $P_{D\max} = 0.2 P_{ac\max}$


class C

- Q pt below cutoff
- o/p current for slightly less than half cycle
- one transistor is required.
- $\% \eta_{\max} = 85 \text{ to } 90\%$
- Distortion is more, used as Nonlinear ampl^r, oscillat^r
- No crossover distortion
- only nonlinear distortⁿ.



ex 1) calculate the ilp power, o/p power & efficiency of the amplifier ckt for an ilp v_{ib} that results in a base current of 10mA peak.

Soln:-

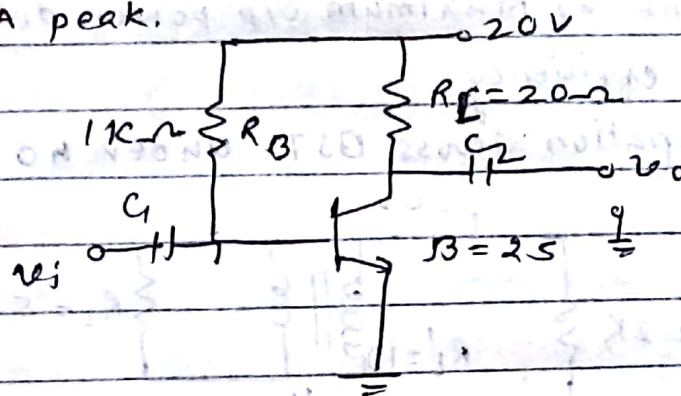

① DC Analysis :-

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{20 - 0.7}{1k\Omega} = 19.3 \mu A$$

$$I_{CQ} = \beta I_B = 25 \times 19.3 \mu A = 482.5 \mu A$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_C = 10.4 V$$

$$P_i(dc) = V_{CC} \times I_{CQ} = 20 \times 482.5 \mu A$$

$$P_i(dc) = 9.65 W$$

② a/p ac Power $P_o(ac)$

$$I_b = 10 \text{ mA (peak)} \text{ --- given}$$

$$I_c = \beta I_b = 25 \times 10 \text{ mA} = 250 \text{ mA}$$

$$P_o(ac) = \frac{I_o^2(p)}{2} \times R_L \quad \text{where } I_o = I_c$$

$$= \frac{(250)^2 \text{ mA}}{2} \times 20 \quad \text{or} \quad \frac{I_c^2(p)}{2} \times R_C$$


$$P_o(ac) = 0.625 W$$

$$\% \eta = \frac{P_o(ac)}{P_i(dc)} \times 100$$

$$= \frac{0.625}{9.65} \times 100$$

$$\% \eta = 6.48\% \approx 6.5\%$$

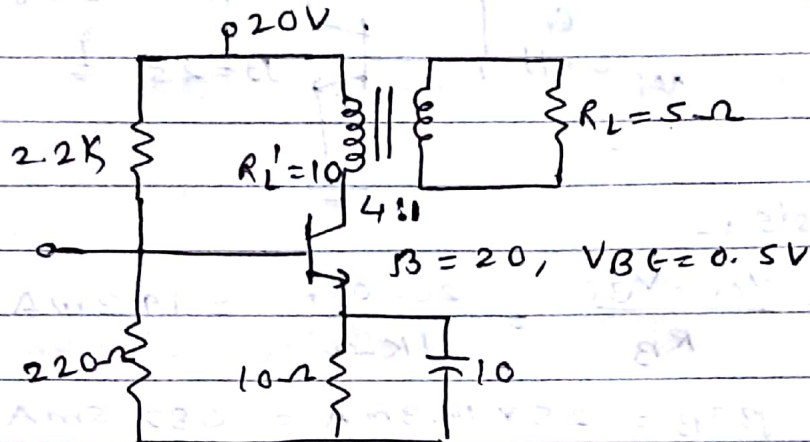- Ex 2) For class A transformer coupled PA, transformer efficiency is 90%. primary winding dc resistance is 10Ω . Determine a) Maximum o/p power delivered to load
b) ckt efficiency
c) Dissipation across BJT under no i/p signal condⁿ.



Solⁿ: - ① DC Analysis

$$I_B = \frac{V_B - V_{BE}}{R_B + (1 + \beta)R_E} \quad \text{--- (1)}$$

$$V_B = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{220}{2.2K + 220} \times 20 =$$

$$\underline{V_B = 1.82 \text{ V}}$$

$$R_B = R_1 \parallel R_2 = 2.2K \parallel 220\Omega$$

$$\underline{R_B = 0.182K \Omega} \quad \text{put in (1)}$$

$$I_B = \frac{1.82 - 0.5}{0.182 + [(1 + 20)10]} = 3.367 \text{ mA}$$

$$I_{CQ} = \beta I_B = 20 \times 3.367 = \underline{67.35 \text{ mA}}$$

$$P_{i(dc)} = V_{CC} \times I_{CQ} = 20V \times$$

$$\boxed{P_{i(dc)} = 1.28 \text{ W}}$$

$$R_L' = n^2 R_L$$

$$= (4)^2 \times 5$$

$$\underline{R_L' = 80 \Omega}$$

primary side.

$$P_o(\text{primary}) = \frac{I_o(p)^2}{2} \times R_L'$$

$$= \frac{I_{CQ}^2}{2} \times R_L'$$

$$P_o'(ac) = \frac{(V_{CEQ})^2}{2 R_L'} = \frac{(18.72)^2}{2 \times 80 \Omega} = \frac{(67.35 \times 10^{-3})^2}{2} \times 80$$

$$\underline{\underline{0.1814 \text{ W}}}$$

$$\boxed{P_o'(ac) = 0.1814 \text{ W}}$$

$$\eta_{(xmer)} = \frac{P_o(\text{sec})}{P_o(\text{prim})} = \frac{P_o'(ac)}{P_o(ac)} = \frac{0.163}{0.1814} = 0.9$$

$$\downarrow$$

$$90$$

$$\underline{P_o(ac) = 0.1814 \text{ W}}$$

$$90 = \frac{P_o(\text{sec})}{0.1814 \text{ W}} \times 100 \therefore P_o(\text{sec}) = 0.163 \text{ W}$$

$$\underline{P_o(\text{sec}) = 0.163 \text{ W}}$$

② ckt efficiency $\eta_o \eta = \frac{P_o(ac)}{P_i(dc)} \times 100$

$$= \frac{0.163}{1.28} \times 100$$

$$\boxed{\eta_o \eta = 12.73\%}$$

③ dissipation across BJT under no i/p signal cond?

$$P_d = P_i(dc) - P_o(ac)$$

$$\boxed{P_d = 1.28 \text{ W} - 0.163 \text{ W} = 1.117 \text{ W}}$$