

9/11/23

Module 1

Basics of Operational Amp



IC741 = opamp

Page No.

Date

Parametric Characteristics
(Opamp and ICs)

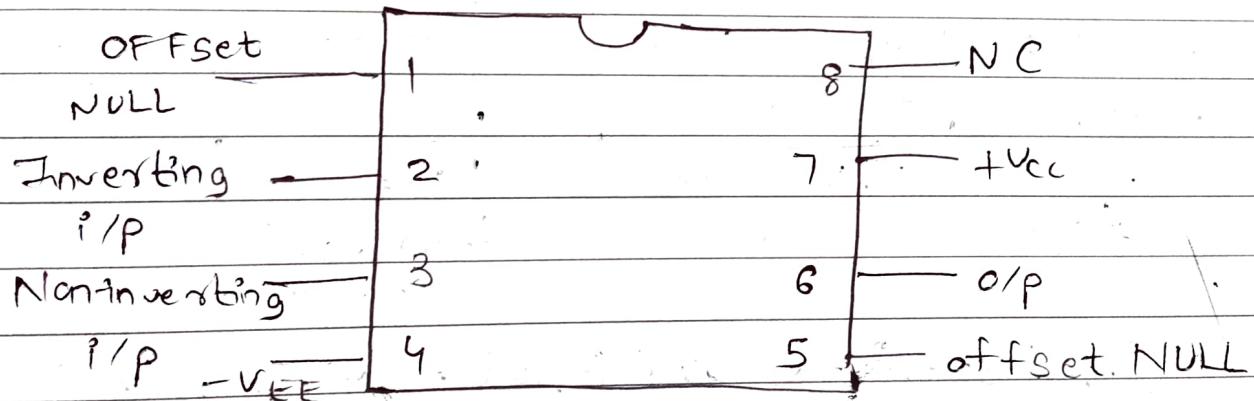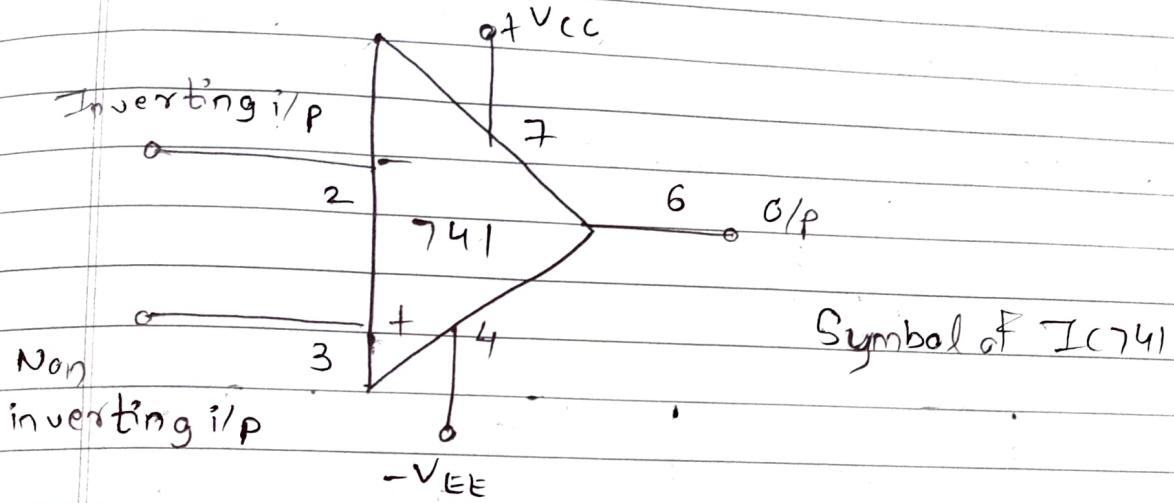opamp = operational amplifier (performs mathematical operations).



Pin diagram of IC741.


- OpAmp is Direct Coupled High Gain Amplifier
consist of one or more differential Amplifier
followed by level translator and output stage
- ② Output stage is generally push-pull, complementary
symmetry pair

① Why opAmp is known as operational Amplifier?

→ With the help of opAmp we can perform mathematical functions like addition, subtraction, multiplication, logarithmic, integration, differentiation etc.

→ It can amplify both DC and AC signal.

* Block Diagram of opAmp:

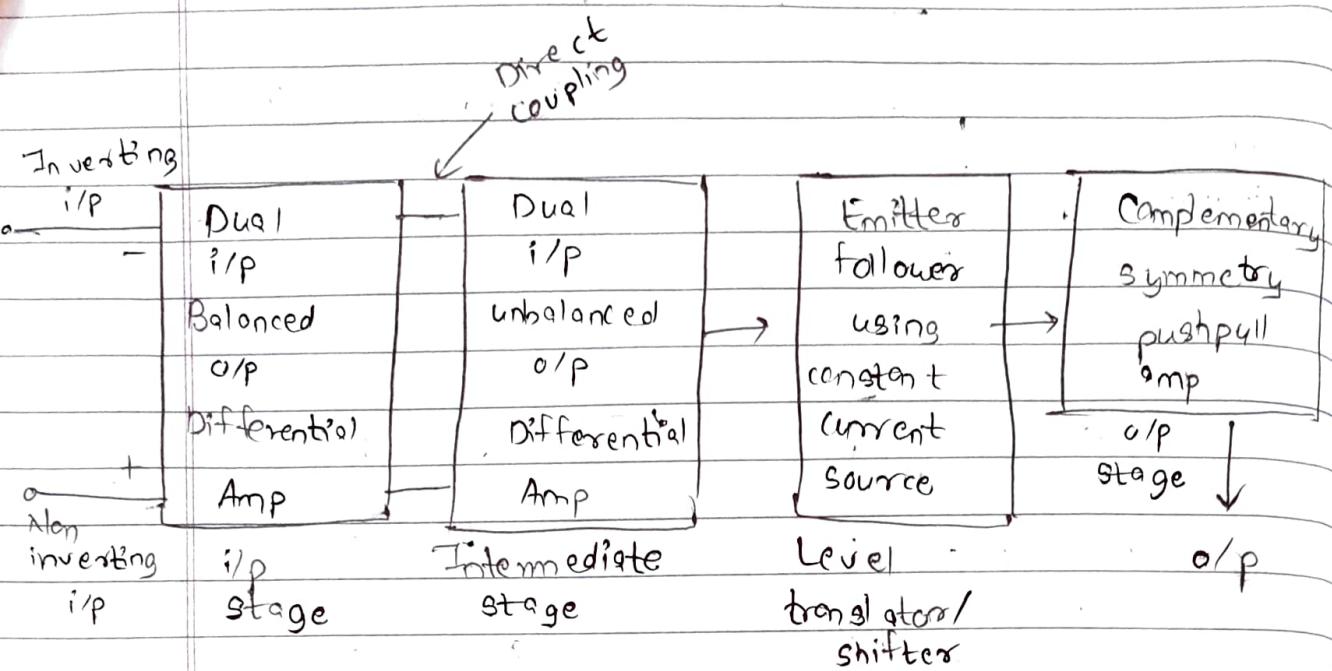


→ Input stage has dual input balanced output differential amplifier and it should have high input impedance.

→ Input stage is directly coupled with dual input unbalanced output diffif amplifier which forms intermediate stage.

→ Third stage consists of level shifter. (generally emitter follower circuit) which shifts the o/p level to ground.

→ A complementary symmetry push-pull amp forms the output stage which should have low output impedance giving high voltage gain.

* Equivalent circuit diagram of op-amp:-

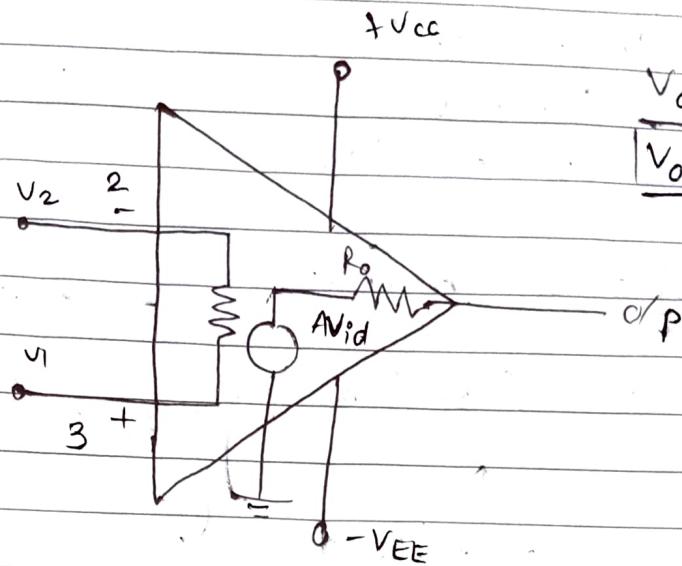

$$V_o = A v_{id}$$


$$\boxed{V_o = A(v_1 - v_2)}$$

* Features of IC 741:-

- (1) No external frequency compensation required.
- (2) Short circuit protection.
- (3) Offset null capability.
- (4) Large common mode and differential voltage ranges.
- (5) Low power consumption.
- (6) No Latch-up problems.

* Different parameters of op-amp-

1) Input offset voltage-

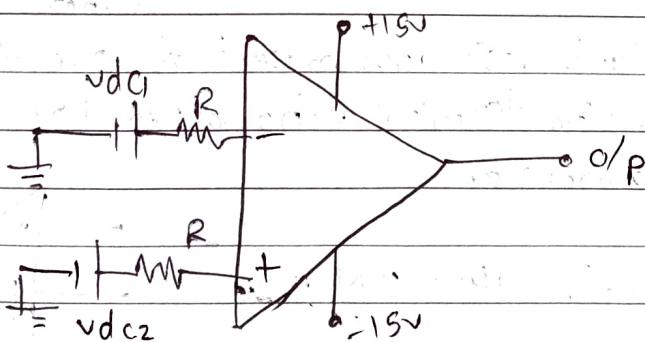

741 C

commercial temperature range
(0 to 70°C)

Page No.

Date

Input offset voltage is voltage that must be applied between two input terminals of op-amp to null the output.

$$V_{IO} = V_{DQ1} - V_{DQ2}$$

For 741C max value of V_{IO} is 6 mV


Precision 741C $\rightarrow 150 \mu\text{V}$

2) Input offset current-

$$I_{IO} = |I_{B1} - I_{B2}|$$

741C $\rightarrow I_{IO(\text{max})} = 200 \text{nA}$

Precision 741C $\rightarrow 6 \text{nA}$

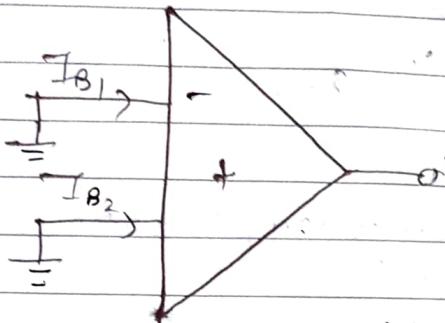

3) Input bias current-

$$I_B = \frac{I_{B1} + I_{B2}}{2}$$


$I_B = 500 \text{nA} \approx 741 \text{C}$

$I_B = \pm 7 \text{nA} = \text{precision}$
741C

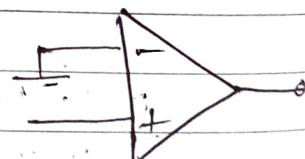4) Input Resistance (R_i) -

It's equivalent resistance present at inverting terminal or non-inverting terminal when other terminal is connected to ground.

$$R_i(\text{max}) = I_C(741) = 2 \text{ M}\Omega$$



5) Input Capacitance:-

It's equivalent capacitance measured at either non-inverting terminal or inverting terminal with other terminal connected to ground.

$$I_{C741C} = 1.4 \text{ pF} \leftarrow \text{Should be as low as possible}$$

6) Input voltage Range:-


When we apply same input signal at both terminals then it is known as common mode signal and input voltage range is defined under this condition.

Max value for $I_{C741} = \pm 13 \text{ V}$.

7) Offset Voltage Adjustment Range :-

This capability to null offset voltage. For this potentiometer of $10 \text{ k}\Omega$ is connected to offset null pins 1 and 5 and variable terminal is connected to $-V_{EE}$. By weaving a potentiometer, we can reduce offset voltage range.

Max value = $\pm 15 \text{ mV}$

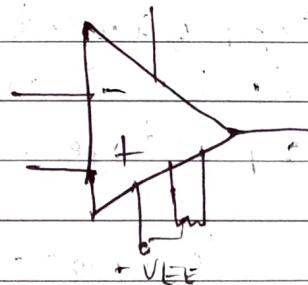

8) Common Mode Rejection Ratio (CMRR)

→

$$\text{CMRR} = \frac{A_d}{A_c} = \frac{\text{differential mode gain}}{\text{common mode gain}}$$

Ideal

op-amp =
 $\text{CMRR} = \infty$

- It indicates ability to reject common mode signal
- It should be high as possible.

Max. value 90 dB

9) Supply Voltage Rejection Ratio (SVRR)

It is ratio of change

$$\text{SVRR} = \frac{\Delta V_{io}}{\Delta V} = \mu\text{V/V}$$

in input offset voltage
with variation in supply voltage

10) Large signal voltage gain:

$$A_d = \frac{V_o}{V_d}$$

Max. value = 2×10^5

11) Supply voltage:- Maximum range = $\pm 15\text{V}$

12) Supply current:- 2 to 3 mA

13) Output resistance: 75 Ω

14) O/p voltage swing:

$$V_{sat} = 0.9 V_{cc}$$

$$V_o(\text{max}) = \pm V_{sat}$$

If supply voltage is $\pm 15\text{V}$, $V_{sat} = \pm 9\text{V}$

15) Slow Rate

$$SR = \frac{dV_o}{dt} \text{ volts/usec} \Big| = 0.5 \text{ v/usec}$$

It's defined as maximum rate of change of output voltage with respect to time. It decides capability of op amp to change its output rapidly.

16) Bandwidth: It is the frequency range of an amplifier over which the signal frequencies are amplified equally.

Bandwidth of 741C = 1 MHz.

17) Gain bandwidth product:- Bandwidth of op amp when gain of amplifier is 1.

18) Output short circuit current:- Max value; 25 mA

Ideal op-amp

Practical
value

R_i	∞	$2 M\Omega$
R_o	0	75Ω
A_v	∞	2×10^5
B.W	∞	1 MHz
CMRR	∞	90 dB
Slew rate	∞	$0.5 V/\mu s_{dc}$
I/p offset voltage	0	6 mV
SVRR	0	$150 \mu V/V$
I/p bias current	0	500 nA
i/p offset current	0	200 nA

Op-amp configuration

Open loop :

- Inverting
- Non inverting
- Differential

Closed loop


- Inverting
- Non-inverting
- Differential

$$V_o = A(V_1 - V_2)$$


$$= -AV_2$$

① Open loop


Inverting

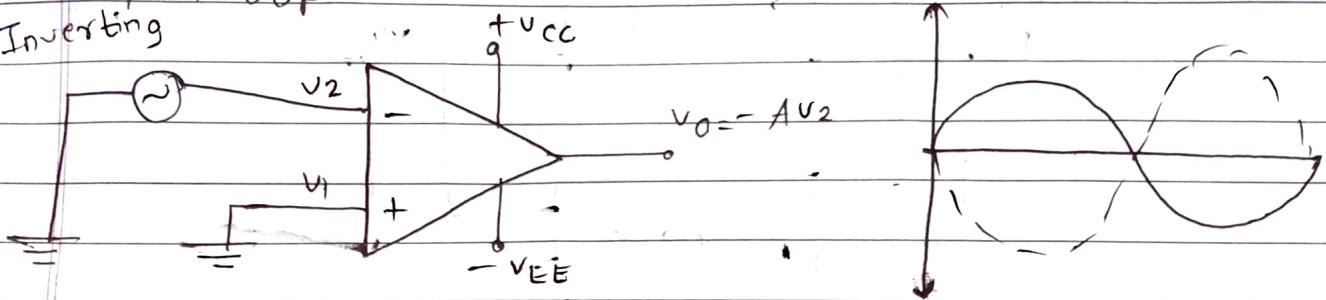


Non-inverting

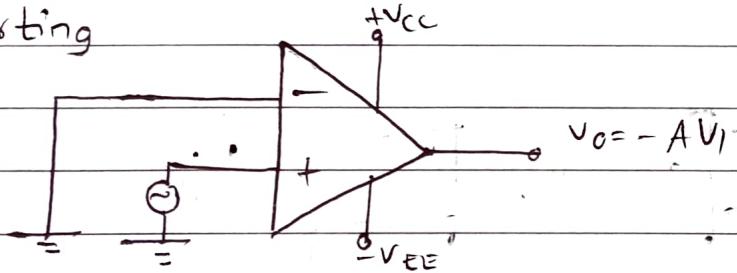


Differential

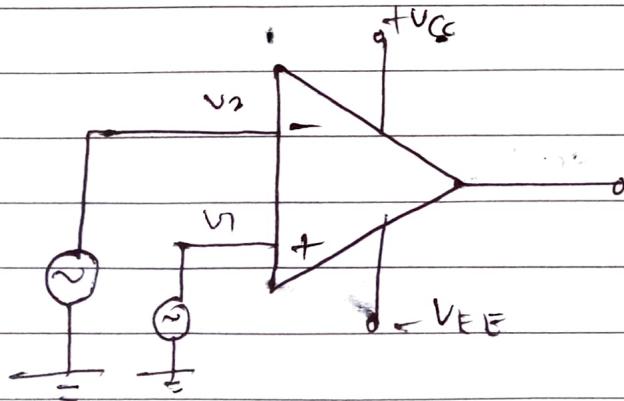


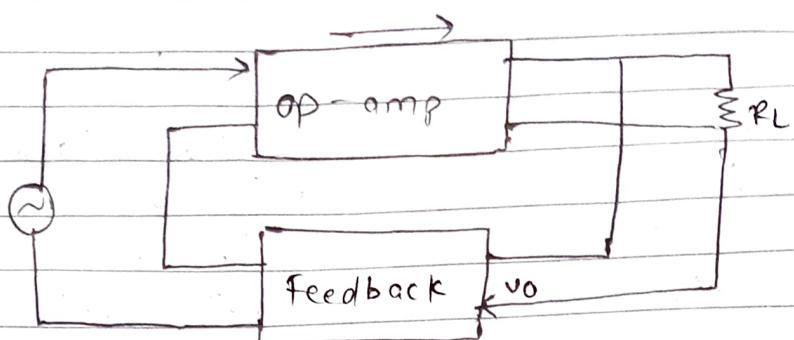


voltage series feedback

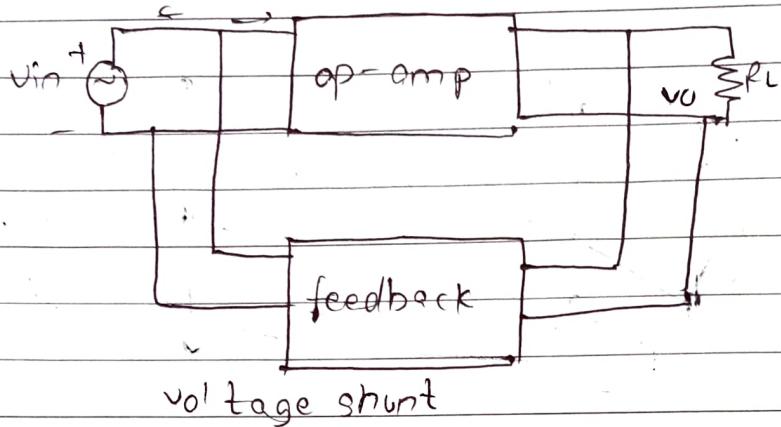

voltage shunt

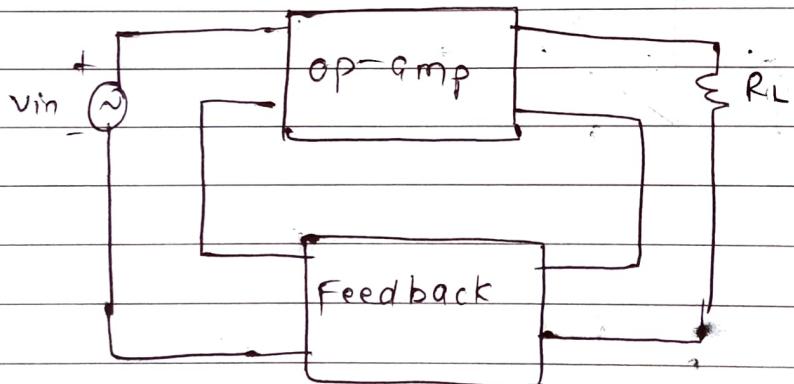


current series

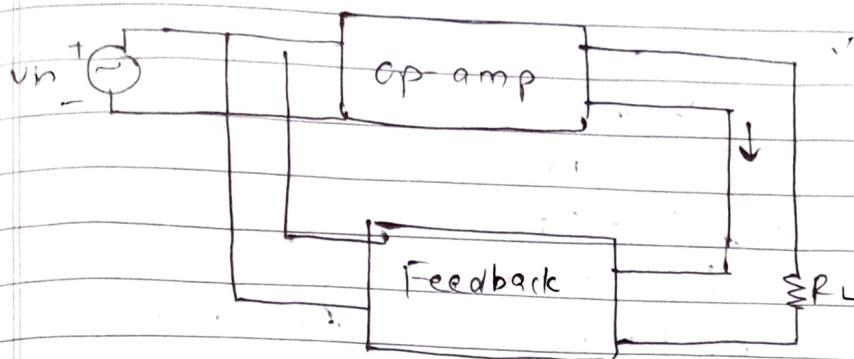

Current shunt

* Voltage series

(Non inverting amp with Feedback)

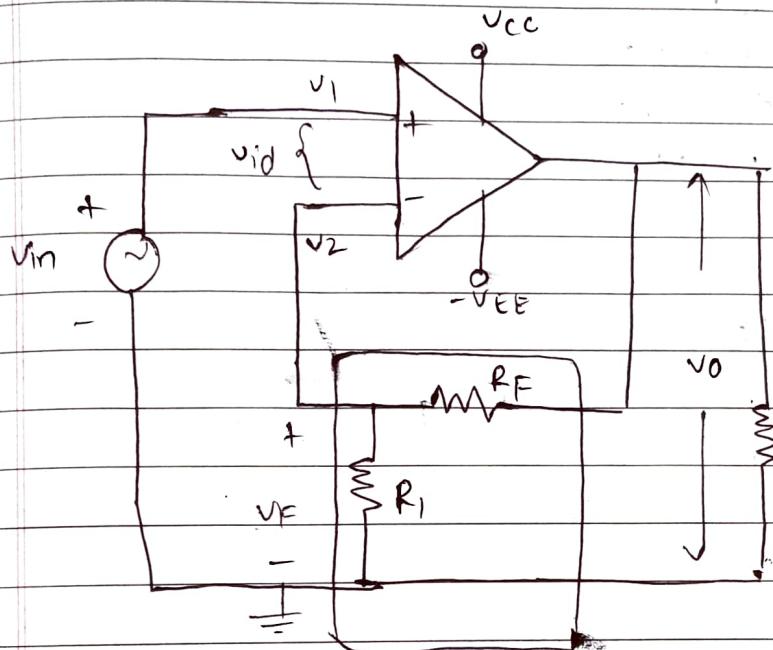

$$V_o = A(v_1 - v_2)$$

$$v_1 = V_{in}$$

$$v_2 = v_f = \frac{R_f}{R_i + R_f} V_o$$

$$V_o = A \left(V_{in} - \frac{R_f}{R_i + R_f} V_o \right)$$

$$V_{cc} \left(1 + A \frac{R_f}{R_i + R_f} \right) = A V_{in}$$

$$\frac{V_o}{V_{in}} = \frac{A}{(1 + A R_i)}$$

$$= A (R_i + R_F)$$

$$= A (R_i + R_F + A R_i)$$

$$= A (R_i + R_F)$$

$$[A R_i > R_i + R_F]$$

$$A_f = \left| \frac{V_o}{V_{in}} = 1 + \frac{R_F}{R_i} \right|$$

$$A_f = A (R_i + R_F)$$

$$R_i + R_F$$

$$R_i + R_F + A R_i$$

$$R_i + R_F$$

$$= A$$


$$1 + A R_i$$

$$R_i + R_F$$

$$A_f = \boxed{\frac{A}{1 + A \beta}}$$

$$\boxed{B = \frac{V_F}{V_o}}$$

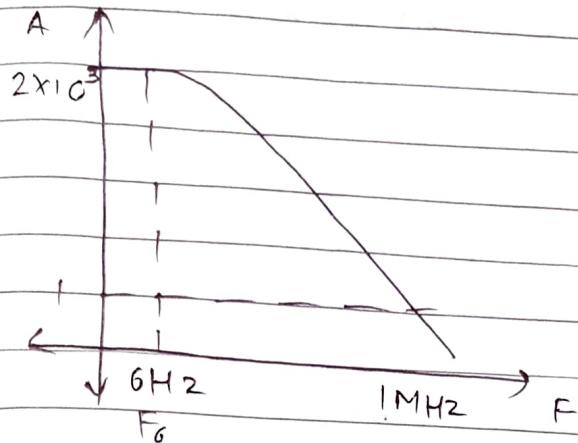* Voltage series feedback amplifier; (Non inverting amp)



$$U_{GB} = A_v F_0$$

$$U_{GB} = A_F F_F$$

$$A_v F_0 = A_F \cdot F_F$$

$$F_F = A_v F_0$$

A_F

$$F_F = \frac{A_F}{A / (1 + A\beta)} = F_0 (1 + A\beta)$$

$$A_v = 1 + \frac{R_F}{R_I}$$

$$A_F = \frac{A}{1 + A\beta}$$

$$R_{if} = R_i (1 + A\beta)$$

$$R_{of} = \frac{R_o}{1 + A\beta}$$

* Break frequency: Frequency at which gain is 3 dB down from its value is known as break frequency (F_0).

→ Unity Gain Bandwidth: The frequency at which frequency gain = 1 is known as unity gain bandwidth.

$$F_f = F_0 (1 + A\beta)$$


$$V_{o0T} = \pm \frac{V_{sat}}{1 + A\beta}$$

- Advantages of negative feedback:

- 1) Input impedance will increase
- 2) Output impedance will reduce
- 3) Bandwidth will increase
- 4) Effect of noise will be minimum
- 5) Output offset voltage will reduce
- 6) Temperature variation effects will be minimum.

* Applications of Non-inverting amp



→ Voltage Follower:

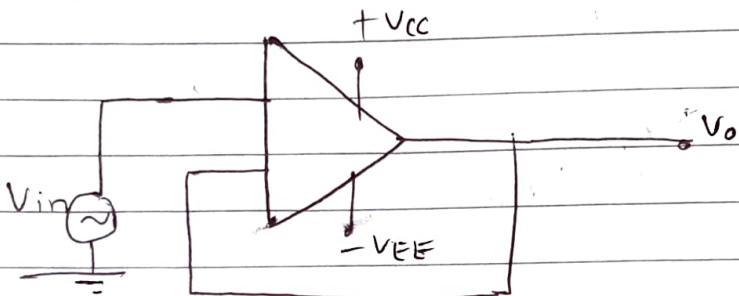

$$A_v = 1 + \frac{R_F}{R_I} \quad \therefore R_F = 0 \quad \therefore A_v = 1$$

$$\beta = \frac{R_I}{R_I + R_F}$$

$$\beta = 1 \quad (\because R_F = 0)$$

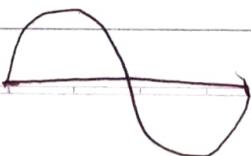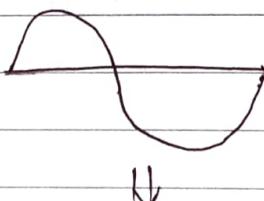

Voltage Follower acts as a buffer.

$$R_{if} = A R_i$$

$$R_{of} = \frac{R_o}{A}$$

$$F_F = A F_o$$

$$V_{out} = \pm V_{sat}$$

- Q. 741C op-Amp having following parameters $R_F = 10k\Omega$
 and $R_i = 1k\Omega$, supply voltage $\pm 15V$. Compute $A_f(A)$,
 R_{if} , R_{of} , F_F , Total output offset voltage with
 feedback.

$$\rightarrow A_f = 1 + \frac{R_F}{R_p} = 1 + \frac{10}{1} = 11$$

$$\begin{aligned} R_{if} &= R_i(1 + A\beta) = 2 \left(1 + 2 \times 10^5 \right) \left(\frac{1}{11} \right) \\ &= 2 \left(1 + \frac{2 \times 10^5}{11} \right) \\ &= 3307.78 \end{aligned}$$

$$\begin{aligned} R_{of} &= \frac{R_o}{1 + A\beta} = \frac{R_o}{1 + 2 \times 10^5 / 11} = \frac{R_o}{18182.82} \\ &= \frac{75}{18182.82} \\ &= 4.12 \times 10^{-3} \\ &= 4.12 m\Omega \end{aligned}$$


$$\begin{aligned}
 F_F &= f_0(1 + A\beta) \\
 &= f_0 \left(1 + 2 \times 10^9 \right) \\
 &= f_0 \left(1 + 2 \times 10^5 \right)
 \end{aligned}$$

$$F_F = 5 \left(1 + 2 \times 10^5 \right) = 90 \text{ MHz}$$

$$V_{o,OT} = \frac{V_{sat}}{1 + A\beta}$$

* Voltage shunt amp: (Inverting amplifier)

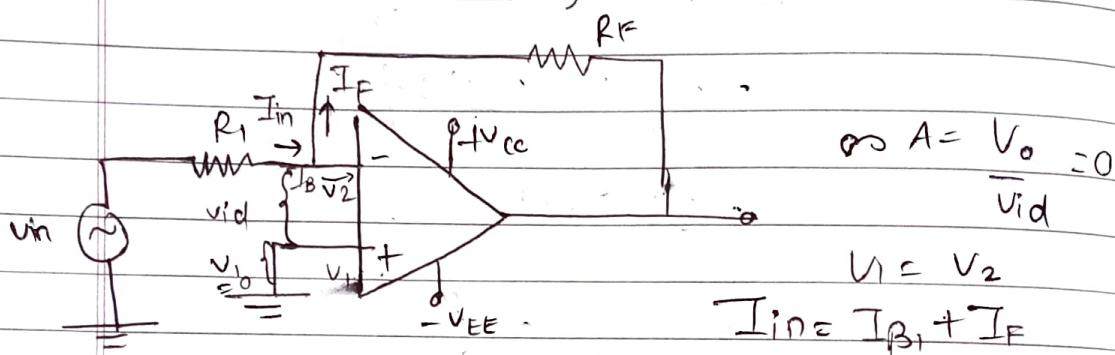Virtual ground: Ideally difference between two input voltage should be zero means voltage at inverting terminal should be equal to voltage at non-inverting terminal. If one terminal is connected to ground, we can say that the other terminal is connected to virtual ground.



$$\frac{V_{in} - V_2}{R_1} = \frac{V_2 - V_o}{R_F}$$

$$\frac{V_{in}}{R_1} = -\frac{V_o}{R_F}$$

$$\boxed{\frac{V_o}{V_{in}} = -\frac{R_F}{R_1}}$$

$$V_{in} - V_2 = V_2 - V_o$$

$$\frac{R_1}{R_1 + R_F}$$

$$V_1 - V_2 = \frac{V_o}{A}$$

$$V_2 = -\frac{V_o}{A}$$

$$\frac{V_{in} + V_o/A}{R_1} = -\frac{V_o/A - V_o}{R_F}$$

$$\left| \frac{V_o}{V_{in}} = -\frac{A R_F}{R_1 + R_F + A R_1} \right|$$

$$A R_1 \gg R_1 + R_F$$

~~* Divide Numerator and Denominator with $R_1 + R_F$.~~

$$\frac{V_o}{V_{in}} = -\frac{A R_F}{R_1 + R_F} \cdot \frac{1 + A R_1}{1 + A R_1}$$

$$\left| A_f = -\frac{A k}{1 + A B} \right|$$

B = Feedback gain

k = Multiplying factor

* ① $B = \frac{R_1}{R_1 + R_F}$

② $R_{iF} = R_1 + \left(\frac{R_F || R_1}{1 + A} \right)$

③ $R_{oF} = \frac{R_o}{1 + A B}$

④ $F_f = F_o (1 + A B)$

⑤ $V_{oOT} = \pm \frac{V_{sat}}{1 + A B}$

* Applications of Inverting Amplifier-

① Current to Voltage Converter

$$\Rightarrow \frac{V_o}{V_{in}} = -\frac{R_F}{R_1}$$


$$V_o = -\frac{R_F}{R_1} V_{in}$$

$$\boxed{V_o = -R_F I_{in.}}$$

② Inverter
C (Choose R_F and
 R_1 same).
(For Designing
inverter)

* Summing, Scaling and Averaging amp:

① Inverting configuration-

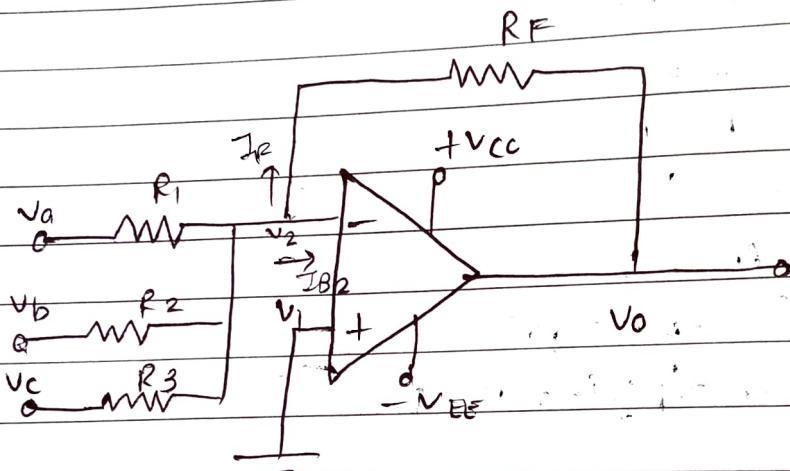

$$I_{at} + I_b + I_c = I_{B2} + I_F$$

$$\therefore I_{at} + I_b + I_c = I_F$$

$$\frac{V_a - V_2}{R_1} + \frac{V_b - V_2}{R_2} + \frac{V_c - V_2}{R_3} = \frac{V_2 - V_o}{R_F}$$

$$\frac{V_a}{R_1} + \frac{V_b}{R_2} + \frac{V_c}{R_3} = -\frac{V_o}{R_F}$$

$$V_o = -R_F \left(\frac{V_a + V_b + V_c}{R_1 + R_2 + R_3} \right)$$

$$\begin{aligned} R_1 &= R_2 = R_3 = R_F = R \\ V_o &= -(V_a + V_b + V_c) \end{aligned}$$

(2) Averaging amp

$$R_F = R$$


$$R_1 = R_2 = R_3 = 3R$$

(3) Scaling amp

$$R_F = R$$

$$R_1 = R_2 = R_3 = \frac{R}{2}$$

* Applications of Non-inverting amp:-

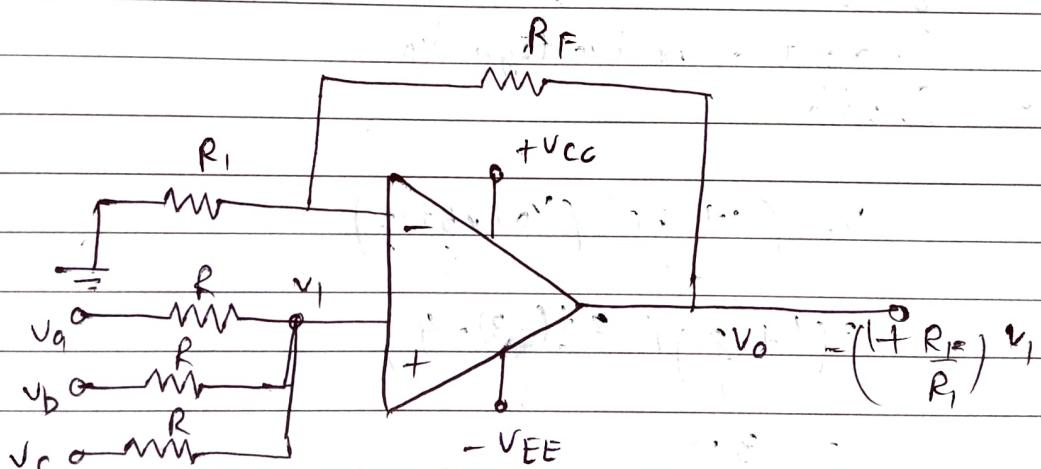

$$V_1 = \left(\frac{R_1/2}{R_1/2 + R} \right) V_a + \left(\frac{R_1/2}{R + R_1/2} \right) V_b + \left(\frac{R_1/2}{R + R_1/2} \right) V_c$$

$$V_o = \left(1 + \frac{R_F}{R_1}\right) \left[\frac{R_1}{R_1 + R_2} \right] (V_a + V_b + V_c)$$

$$= \left(1 + \frac{R_F}{R_1}\right) \left[\frac{R_1}{1.5R_1} \right] (V_a + V_b + V_c)$$

$$V_o = \left(1 + \frac{R_F}{R_1}\right) \left(\frac{V_a + V_b + V_c}{3} \right)$$

To work this circuit as summing amplifier,
 R_F should be twice of R_1 , so that gain of
circuit would become 3 and it will provide a/p
as addition of i/p signals.

* Averaging amplifier: Gain of $\frac{R_F}{R_1}$ value should be

set to 1 so that output will be average of all
3 input signals.

e.g.: For a given circuit supply voltage $\pm 15V$, $V_a = \pm 2V$,
 $V_b = -3V$, $V_c = +4V$, $R_1 = 1k\Omega$, $R_F = 2k\Omega$, $R = 1k\Omega$
Find out output voltage V_o .

\Rightarrow Solution,


$$V_o = \left(1 + \frac{R_F}{R_1}\right) \left(\frac{V_a + V_b + V_c}{3} \right)$$

$$= \left(1 + \frac{2}{1}\right) \left(\frac{2 + (-3) + 4}{3} \right)$$

$$= 3 \times 1$$

$$V_o = 3V$$

Differential amplifier with one op-amp:

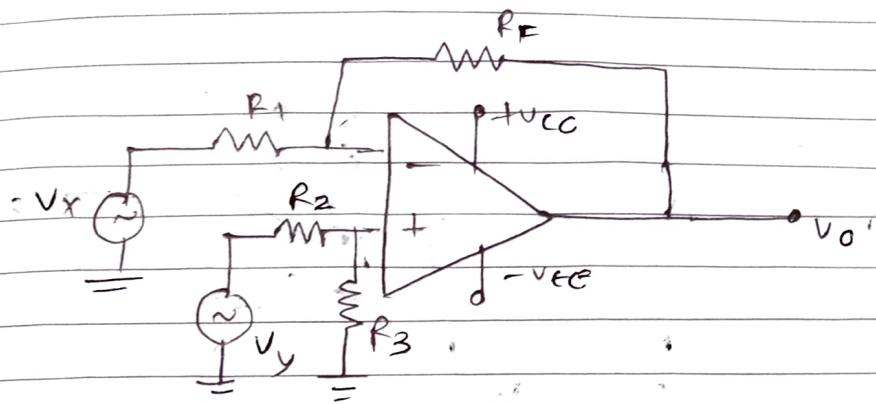

$$V_o = V_{ox} + V_{oy}$$

$$V_{ox} = -\frac{R_F}{R_1} (V_x)$$

$$V_{oy} = \left(1 + \frac{R_F}{R_1}\right) V_y$$

$$= \left(1 + \frac{R_F}{R_1}\right) \left(\frac{R_3}{R_2 + R_3}\right) V_y$$


$$= -\frac{R_F}{R_1} V_x + \left(1 + \frac{R_F}{R_1}\right) \left(\frac{R_3}{R_2 + R_3}\right) V_y$$

$$R_1 = R_2, R_F = R_3$$

$$V_{oy} = -\frac{R_F}{R_1} (V_x - V_y)$$

$$\therefore \boxed{V_o = -\frac{R_F}{R_1} (V_x - V_y)}$$

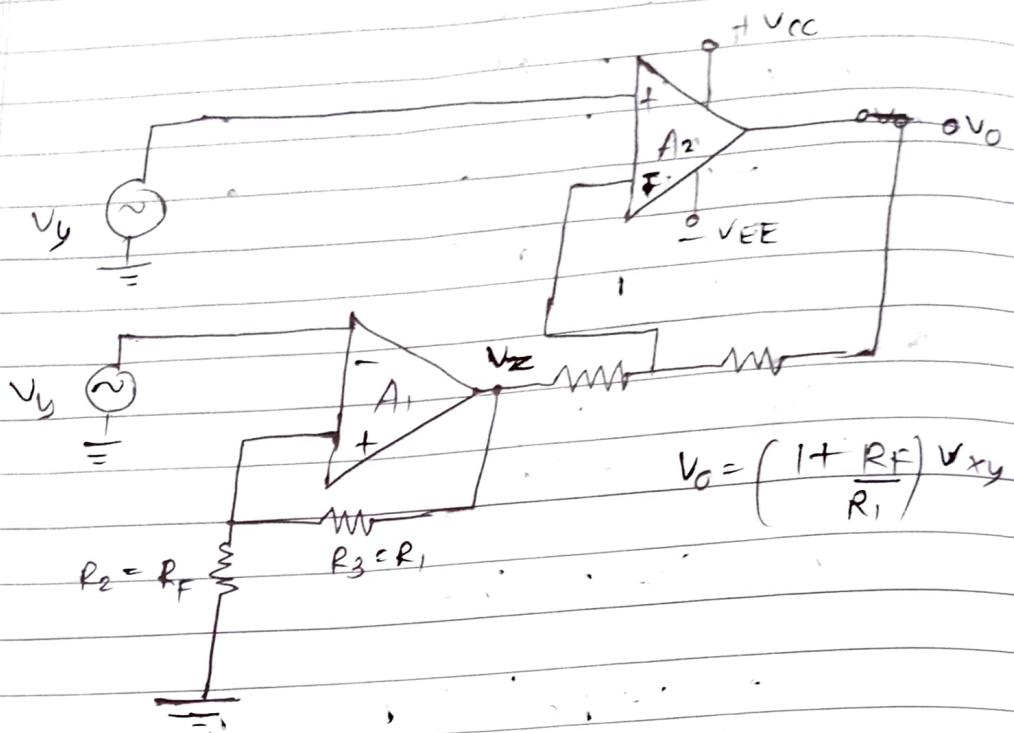* Differential amplifier using two op-amps:



$\Rightarrow A_1$ will work as a non-inverting amp

$$V_z = \left(1 + \frac{R_3}{R_2}\right) V_x$$

$$V_{ox} = V_{ox1} + V_{ox2}$$

$$V_{ox1} = \left(1 + \frac{R_f}{R_1}\right) V_x$$

$$V_{ox2} = -\frac{R_f}{R_1} V_z$$

$$R_1$$

$$V_z = \left(1 + \frac{R_3}{R_2}\right) V_y$$

$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_x + -\frac{R_f}{R_1} \left(1 + \frac{R_3}{R_2}\right) V_y$$

$$R_3 = R_1, R_2 = R_F$$


$$= \left(1 + \frac{R_F}{R_1} \right) V_n + \left(-\frac{R_F}{R_1} \right) \left(1 + \frac{R_1}{R_F} \right) V_y$$

$$= \left(\frac{R_1 + R_F}{R_1} \right) V_n - \frac{R_F}{R_1} \left(\frac{R_F + R_1}{R_F} \right) V_y$$

$$= \left(\frac{R_1 + R_F}{R_1} \right) V_n - V_y$$

$$= \left(1 + \frac{R_F}{R_1} \right) V_x - V_y$$

* Differential amp or Subtractor:-

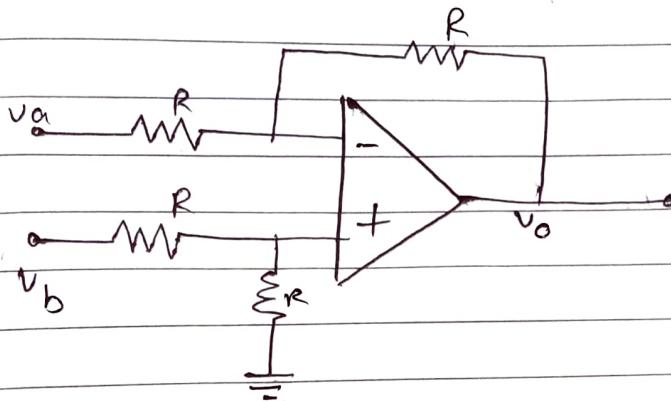


$$V_o = -\frac{R_F}{R_1} (V_a - V_b)$$

$$= -(V_a - V_b)$$

$$\boxed{V_o = V_b - V_a}$$

Ex For given circuit. Define o/p voltage if
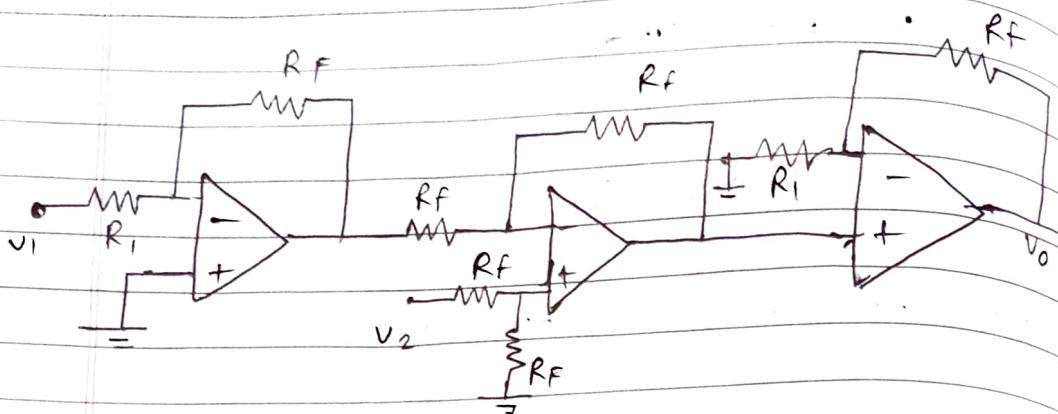
$$R_F = 10 \text{ k}\Omega, R_1 = 1 \text{ k}\Omega$$



$$\underline{V_{O_1} = -R_F}$$

$$\underline{V_1 \quad R_1}$$

$$\underline{V_{O_1} = -R_F \times V_1}$$

$$V_{O_2} = V_2 - V_{O_1}$$

$$= V_2 + \underline{R_F \times V_1} = V_2 + 10V_1$$


$$V_{O_3} = \left(1 + \frac{R_F}{R_1}\right) V_{O_2}$$

$$= \left(1 + \frac{R_F}{R_1}\right) \left(V_2 + \underline{\frac{R_F}{R_1} \times V_1}\right)$$


$$= \left(1 + \frac{10}{1}\right) (V_2 + 10V_1)$$

$$\boxed{V_{O_3} = 11(V_2 + 10V_1)}$$

Instrumentation amplifier :- (IA)

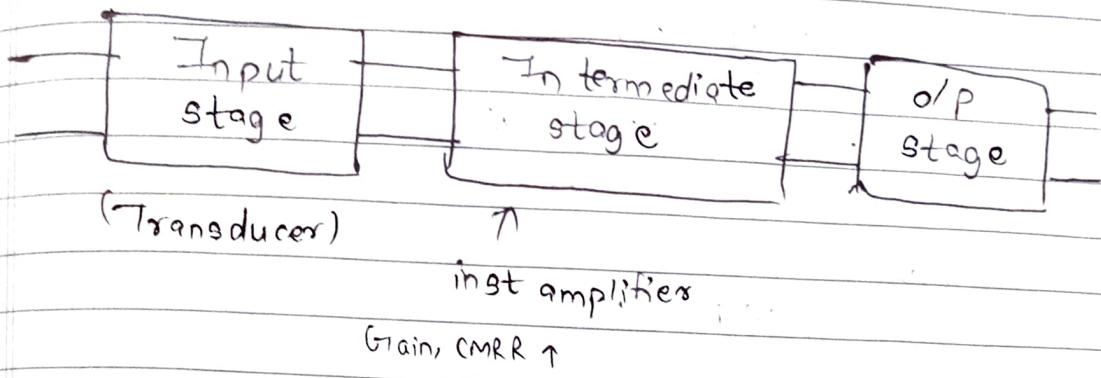


* IA using one op-amp :

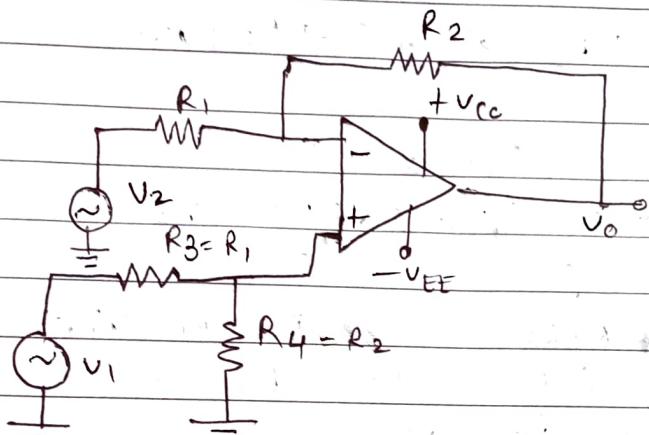

$$V_0 = V_1 - V_2$$

* IA Using 2 op-amp :

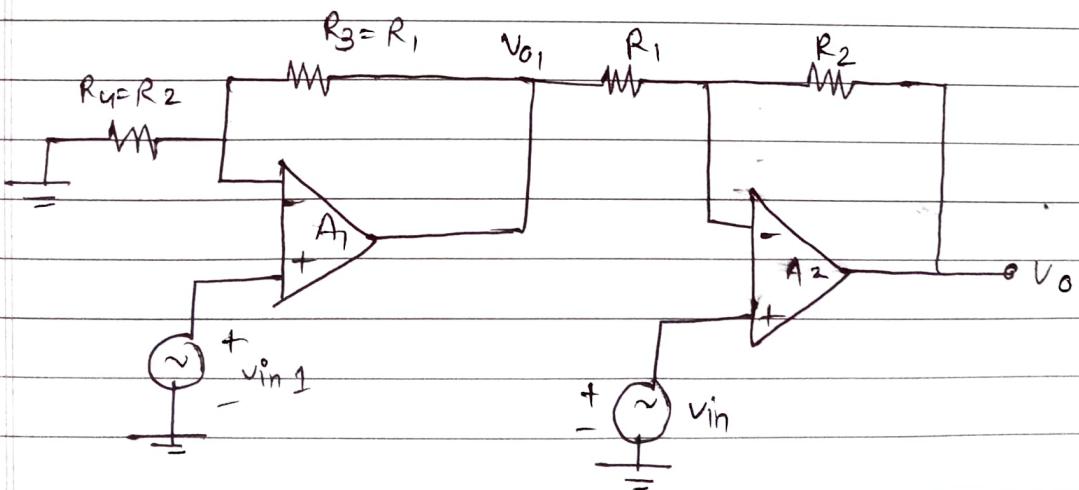

$$V_o = \left(1 + \frac{R_3}{R_4} \right) V_{in1}$$

Due to V_{in1} ,

$$V_o' = - \frac{R_2}{R_1} \times V_{in1}$$

$$= - \frac{R_2}{R_1} \times \left(1 + \frac{R_3}{R_4} \right) V_{in1}$$

Due to V_{in2} ,

$$V_o'' = \left(1 + \frac{R_2}{R_1} \right) V_{in2}$$

$$V_o = V_o' + V_o''$$

$$= - \frac{R_2}{R_1} \left(1 + \frac{R_3}{R_4} \right) V_{in1} + \left(1 + \frac{R_2}{R_1} \right) V_{in2}$$

Replace $R_3 = R_1$, $R_4 = R_2$,

$$= - \frac{R_2}{R_1} \left(1 + \frac{R_1}{R_2} \right) V_{in1} + \left(1 + \frac{R_2}{R_1} \right) V_{in2}$$


$$= - \frac{R_2}{R_1} \cancel{\frac{R_1 R_2}{R_1 R_2}} - \frac{R_2}{R_1} \left(\frac{R_2 + R_1}{R_2} \right) V_{in1} + \left(\frac{R_1 + R_2}{R_1} \right) V_{in2}$$

$$= \left(\frac{R_1 + R_2}{R_1} \right) [V_{in2} - V_{in1}]$$

* Advantages of dual Instrumentation op amp

1. High Input Resistance
2. Low Output Resistance
3. CMRR can be maximized by a variable resistor

* IA using 3A op-amp-

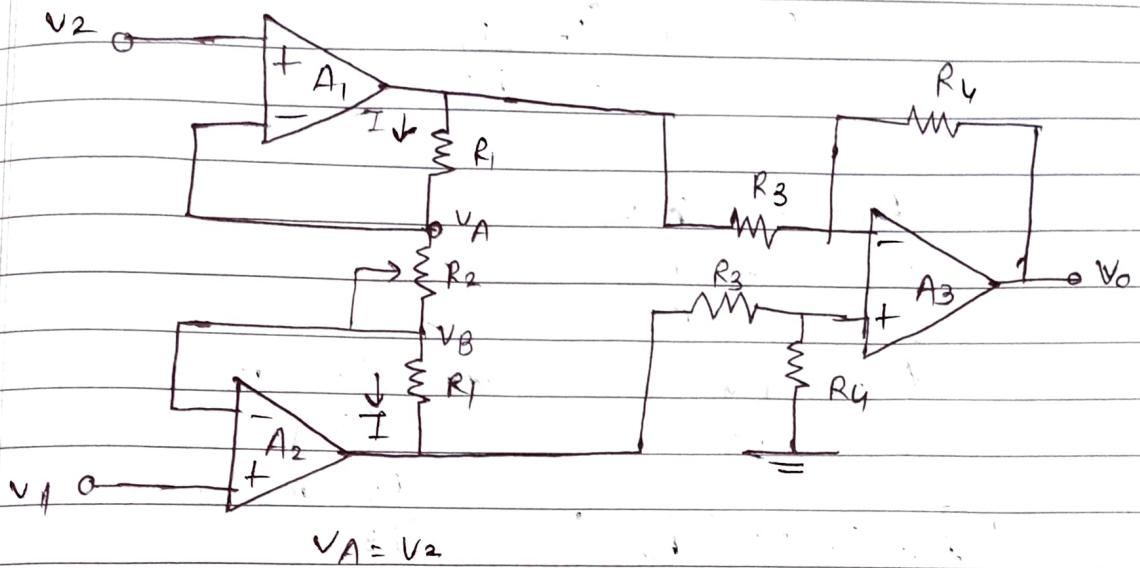

$$I = \frac{V_A - V_B}{R_2}$$

$$V_{O_1} = V_A + I R_1$$

$$V_{O_2} = V_B - I R_1$$

$$\begin{aligned} V_{O_1} &= V_A + I R_1 \\ &= V_2 + \left(\frac{V_2 - V_1}{R_2} \right) R_1 \end{aligned}$$

$$V_{O_1} = \frac{(R_1 + R_2)V_2 - R_1 V_1}{R_2}$$

$$V_{O_2} = \frac{(R_1 + R_2)V_1 - R_1 V_2}{R_2}$$

$$V_o = V_{O_2} - V_{O_1}$$

$$\begin{aligned}
 & \frac{R_1(R_1 + R_2)V_1 - R_1V_2 - [(R_1 + R_2)V_2 + R_1V_1]}{R_2} \\
 & = \frac{R_1V_1 + R_2V_1 - R_1V_2 - R_1V_2 - R_2V_2 + R_1V_1}{R_2} \\
 & = \frac{R_2V_1 - 2R_1V_1 - 2R_1V_2 + R_2V_1 - R_2V_2}{R_2} \\
 & = 2R_1(V_1 - V_2) + R_2(V_1 - V_2) \\
 & = (V_1 - V_2) \left(1 + \frac{2R_1}{R_2} \right).
 \end{aligned}$$

$$Av = A_{V_1} \times A_{V_2}$$

$$A_{V_1} = 1 + \frac{2R_1}{R_2}$$

$$A_{V_2} = \frac{R_2}{R_3} \quad V_0 = -\frac{R_2}{R_3} (V_{O_1} - V_{O_2})$$

$$Av = \left(1 + \frac{2R_1}{R_2} \right) \frac{R_2}{R_3} \quad = \frac{R_2}{R_3} (V_{O_2} - V_{O_1})$$

* Applications of JA:

- eg 1) Temperature indicators
- 2) Pressure monitoring and control
- 3) Temperature controller
- 4) Light Intensity Meter
- 5) Electronic weighing scale.