

# 2

# Analysis of DC Circuits

## 2.1 INTRODUCTION

In Chapter 1, we have studied basic circuit concepts. In network analysis, we have to find currents and voltages in various parts of networks. In this chapter, we will study elementary network theorems like Kirchhoff's laws, mesh analysis and node analysis. These methods are applicable to all types of networks. The first step in analyzing networks is to apply Ohm's law and Kirchhoff's laws. The second step is the solving of these equations by mathematical tools. There are some other methods also to analyse circuits. We will also study superposition theorem, Thevenin's theorem, Norton's theorem, maximum power transfer theorem, Reciprocity theorem and Millman's theorem. We can find currents and voltages in various parts of the circuits with these methods.

## 2.2 KIRCHHOFF'S LAWS

The entire study of electric network analysis is based mainly on Kirchhoff's laws. But before discussing this, it is essential to familiarise ourselves with the following terms:


- Node* A node is a junction where two or more network elements are connected together.
- Branch* An element or number of elements connected between two nodes constitute a branch.
- Loop* A loop is any closed part of the circuit.
- Mesh* A mesh is the most elementary form of a loop and cannot be further divided into other loops. All meshes are loops but all loops are not meshes.

**1. Kirchhoff's Current Law (KCL)** The algebraic sum of currents meeting at a junction or node in an electric circuit is zero.

Consider five conductors, carrying currents  $I_1, I_2, I_3, I_4$  and  $I_5$  meeting at a point  $O$  as shown in Fig. 2.1. Assuming the incoming currents to be positive and outgoing currents negative, we have

$$\begin{aligned} I_1 + (-I_2) + I_3 + (-I_4) + I_5 &= 0 \\ I_1 - I_2 + I_3 - I_4 + I_5 &= 0 \\ I_1 + I_3 + I_5 &= I_2 + I_4 \end{aligned}$$

Thus, the above law can also be stated as the sum of currents flowing towards any junction in an electric circuit is equal to the sum of the currents flowing away from that junction.

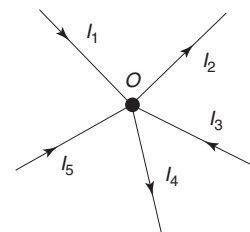


**Fig. 2.1** Kirchhoff's current law

**2. Kirchhoff's Voltage Law (KVL)** The algebraic sum of all the voltages in any closed circuit or mesh or loop is zero.

If we start from any point in a closed circuit and go back to that point, after going round the circuit, there is no increase or decrease in potential at that point. This means that the sum of emfs and the sum of voltage drops or rises meeting on the way is zero.


**3. Determination of Sign** A rise in potential can be assumed to be positive while a fall in potential can be considered negative. The reverse is also possible and both conventions will give the same result.

- (i) If we go from the positive terminal of the battery or source to the negative terminal, there is a fall in potential and so the emf should be assigned a negative sign (Fig. 2.2a). If we go from the negative terminal of the battery or source to the positive terminal, there is a rise in potential and so the emf should be given a positive sign (Fig. 2.2b).

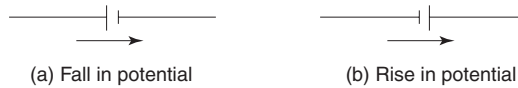

**Fig. 2.2** Sign convention

- (ii) When current flows through a resistor, there is a voltage drop across it. If we go through the resistor in the same direction as the current, there is a fall in the potential and so the sign of this voltage drop is negative (Fig. 2.3a). If we go opposite to the direction of the current flow, there is a rise in potential and hence, this voltage drop should be given a positive sign (Fig. 2.3b).

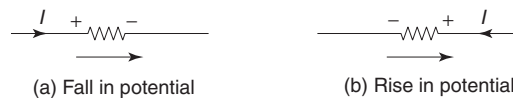

**Fig. 2.3** Sign convention


## 2.3 MESH ANALYSIS

A mesh is defined as a loop which does not contain any other loops within it. Mesh analysis is applicable only for planar networks. A network is said to be planar if it can be drawn on a plane surface without crossovers. In this method, the currents in different meshes are assigned continuous paths so that they do not split at a junction into branch currents. If a network has a large number of voltage sources, it is useful to use mesh analysis. Basically, this analysis consists of writing mesh equations by Kirchhoff's voltage law in terms of unknown mesh currents.

### Steps to be Followed in Mesh Analysis

1. Identify the mesh, assign a direction to it and assign an unknown current in each mesh.
2. Assign the polarities for voltage across the branches.
3. Apply KVL around the mesh and use Ohm's law to express the branch voltages in terms of unknown mesh currents and the resistance.
4. Solve the simultaneous equations for unknown mesh currents.

Consider the network shown in Fig. 2.4 which has three meshes. Let the mesh currents for the three meshes be  $I_1$ ,  $I_2$ , and  $I_3$  and all the three mesh currents may be assumed to flow in the clockwise direction. The choice of direction for any mesh current is arbitrary.

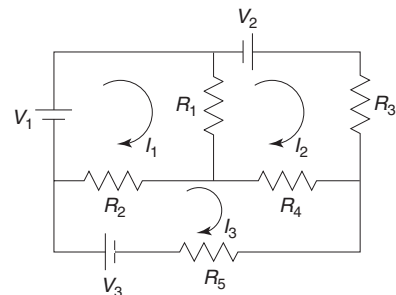

**Fig. 2.4** Circuit for mesh analysis

Applying KVL to Mesh 1,

$$\begin{aligned} V_1 - R_1(I_1 - I_2) - R_2(I_1 - I_3) &= 0 \\ (R_1 + R_2)I_1 - R_1 I_2 - R_2 I_3 &= V_1 \end{aligned} \quad \dots(2.1)$$

Applying KVL to Mesh 2,

$$\begin{aligned} V_2 - R_3 I_2 - R_4(I_2 - I_3) - R_1(I_2 - I_1) &= 0 \\ -R_1 I_1 + (R_1 + R_3 + R_4) I_2 - R_4 I_3 &= V_2 \end{aligned} \quad \dots(2.2)$$

Applying KVL to Mesh 3,

$$\begin{aligned} -R_2(I_3 - I_1) - R_4(I_3 - I_2) - R_5 I_3 + V_3 &= 0 \\ -R_2 I_1 - R_4 I_2 + (R_2 + R_4 + R_5) I_3 &= V_3 \end{aligned} \quad \dots(2.3)$$

Writing Eqs (2.1), (2.2), and (2.3) in matrix form,

$$\begin{bmatrix} R_1 + R_2 & -R_1 & -R_2 \\ -R_1 & R_1 + R_3 + R_4 & -R_4 \\ -R_2 & -R_4 & R_2 + R_4 + R_5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

In general,

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

where,  $R_{11}$  = Self-resistance or sum of all the resistance of mesh 1

$R_{12} = R_{21}$  = Mutual resistance or sum of all the resistances common to meshes 1 and 2

$R_{13} = R_{31}$  = Mutual resistance or sum of all the resistances common to meshes 1 and 3

$R_{22}$  = Self-resistance or sum of all the resistance of mesh 2

$R_{23} = R_{32}$  = Mutual resistance or sum of all the resistances common to meshes 2 and 3

$R_{33}$  = Self-resistance or sum of all the resistance of mesh 3

If the directions of the currents passing through the common resistance are the same, the mutual resistance will have a positive sign, and if the direction of the currents passing through common resistance are opposite then the mutual resistance will have a negative sign. If each mesh current is assumed to flow in the clockwise direction then all self-resistances will always be positive and all mutual resistances will always be negative.

The voltages  $V_1$ ,  $V_2$  and  $V_3$  represent the algebraic sum of all the voltages in meshes 1, 2 and 3 respectively. While going along the current, if we go from negative terminal of the battery to the positive terminal then its emf is taken as positive. Otherwise, it is taken as negative.

### Example 2.1

Find the current through the  $5\ \Omega$  resistor is shown in Fig. 2.5.

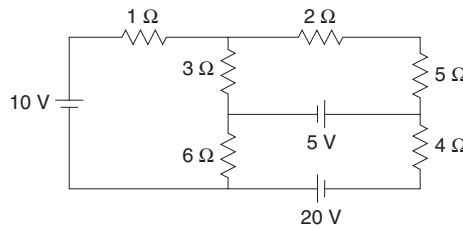


Fig. 2.5

## 2.4 Circuit Theory and Networks—Analysis and Synthesis

**Solution** Assign clockwise currents in three meshes as shown in Fig. 2.6.

Applying KVL to Mesh 1,

$$\begin{aligned} 10 - I_1 - 3(I_1 - I_2) - 6(I_1 - I_3) &= 0 \\ 10I_1 - 3I_2 - 6I_3 &= 10 \end{aligned} \quad \dots(i)$$

Applying KVL to Mesh 2,

$$\begin{aligned} -3(I_2 - I_1) - 2I_2 - 5I_2 - 5 &= 0 \\ -3I_1 + 10I_2 &= -5 \end{aligned} \quad \dots(ii)$$

Applying KVL to Mesh 3,

$$\begin{aligned} -6(I_3 - I_1) + 5 - 4I_3 + 20 &= 0 \\ -6I_1 + 10I_3 &= 25 \end{aligned} \quad \dots(iii)$$

Writing Eqs (i), (ii) and (iii) in matrix form,

$$\begin{bmatrix} 10 & -3 & -6 \\ -3 & 10 & 0 \\ -6 & 0 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ -5 \\ 25 \end{bmatrix}$$

We can write matrix equation directly from Fig. 2.6,

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

where

$R_{11}$  = Self-resistance of Mesh 1 =  $1 + 3 + 6 = 10 \Omega$

$R_{12}$  = Mutual resistance common to meshes 1 and 2 =  $-3 \Omega$

Here, negative sign indicates that the current through common resistance are in opposite direction.

$R_{13}$  = Mutual resistance common to meshes 1 and 3 =  $-6 \Omega$

Similarly,

$$R_{21} = -3 \Omega$$

$$R_{22} = 3 + 2 + 5 = 10 \Omega$$

$$R_{23} = 0$$

$$R_{31} = -6 \Omega$$

$$R_{32} = 0$$

$$R_{33} = 6 + 4 = 10 \Omega$$

For voltage matrix,

$$V_1 = 10 \text{ V}$$

$$V_2 = -5 \text{ V}$$

$$V_3 = \text{algebraic sum of all the voltages in mesh 3} = 5 + 20 = 25 \text{ V}$$


Solving Eqs (i), (ii) and (iii),

$$I_1 = 4.27 \text{ A}$$

$$I_2 = 0.78 \text{ A}$$

$$I_3 = 5.06 \text{ A}$$


$$I_{5\Omega} = I_2 = 0.78 \text{ A}$$

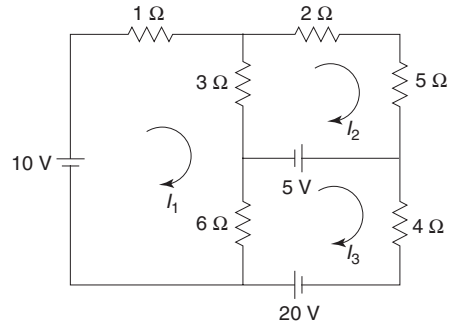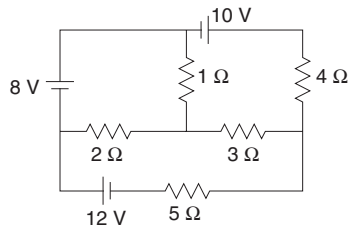

**Fig. 2.6**

**Example 2.2**

Determine the current through the  $5\ \Omega$  resistor of the network shown in Fig. 2.7.

**Fig. 2.7**

**Solution** Assign clockwise currents in three meshes as shown in Fig. 2.8.

Applying KVL to Mesh 1,

$$\begin{aligned} 8 - 1(I_1 - I_2) - 2(I_1 - I_3) &= 0 \\ 3I_1 - I_2 - 2I_3 &= 8 \end{aligned}$$

Applying KVL to Mesh 2,


$$\begin{aligned} 10 - 4I_2 - 3(I_2 - I_3) - 1(I_2 - I_1) &= 0 \\ -I_1 + 8I_2 - 3I_3 &= 10 \end{aligned}$$

Applying KVL to Mesh 3,


$$\begin{aligned} -2(I_3 - I_1) - 3(I_3 - I_2) - 5I_3 + 12 &= 0 \\ -2I_1 - 3I_2 + 10I_3 &= 12 \end{aligned} \quad \dots(\text{iii})$$

Solving Eqs (i), (ii), and (iii),

$$\begin{aligned} I_1 &= 6.01\text{ A} \\ I_2 &= 3.27\text{ A} \\ I_3 &= 3.38\text{ A} \\ I_{5\Omega} &= I_3 = 3.38\text{ A} \end{aligned}$$

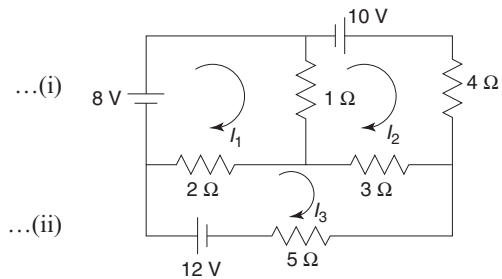**Fig. 2.8****Example 2.3**

Find the current through the  $2\ \Omega$  resistor in the network of Fig. 2.9.

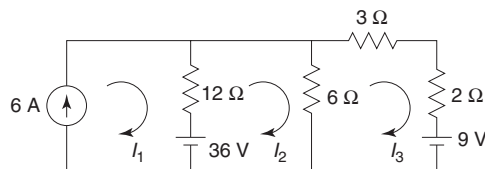**Fig. 2.9**

**Solution** Mesh 1 contains a current source of 6 A. Hence, we can write current equation for Mesh 1. Since direction of current source and mesh current  $I_1$  are same,

$$I_1 = 6 \quad \dots(\text{i})$$

## 2.6 Circuit Theory and Networks—Analysis and Synthesis

Applying KVL to Mesh 2,

$$36 - 12(I_2 - I_1) - 6(I_2 - I_3) = 0$$

$$36 - 12(I_2 - 6) - 6I_2 + 6I_3 = 0$$

$$18I_2 - 6I_3 = 108 \quad \dots(\text{ii})$$

Applying KVL to Mesh 3,

$$-6(I_3 - I_2) - 3I_3 - 2I_3 - 9 = 0$$


$$6I_2 - 11I_3 = 9 \quad \dots(\text{iii})$$

Solving Eqs (ii) and (iii),

$$I_3 = 3 \text{ A}$$

$$I_{2\Omega} = I_3 = 3 \text{ A}$$

**Example 2.4** Find the current through the  $5\ \Omega$  resistor in the network of Fig. 2.10.

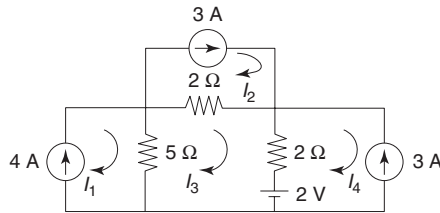

**Fig. 2.10**

**Solution** Writing current equations for Meshes 1, 2 and 4,

$$I_1 = 4 \quad \dots(\text{i})$$

$$I_2 = 3 \quad \dots(\text{ii})$$

$$I_4 = -3 \quad \dots(\text{iii})$$

Applying KVL to Mesh 3,

$$-5(I_3 - I_1) - 2(I_3 - I_2) - 2(I_3 - I_4) - 2 = 0 \quad \dots(\text{iv})$$

Substituting Eqs (i), (ii) and (iii) in Eq. (iv),

$$-5(I_3 - 4) - 2(I_3 - 3) - 2(I_3 + 3) - 2 = 0$$

$$I_3 = 2 \text{ A}$$

$$I_{5\Omega} = I_1 - I_3 = 4 - 2 = 2 \text{ A}$$

## EXAMPLES WITH DEPENDENT SOURCES

**Example 2.5** Obtain the branch currents in the network shown in Fig. 2.11.

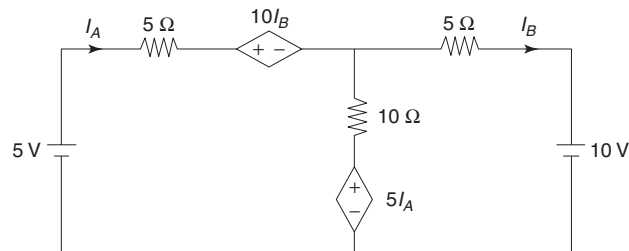


Fig. 2.11

**Solution** Assign clockwise currents in two meshes as shown in Fig. 2.12.

From Fig. 2.12,

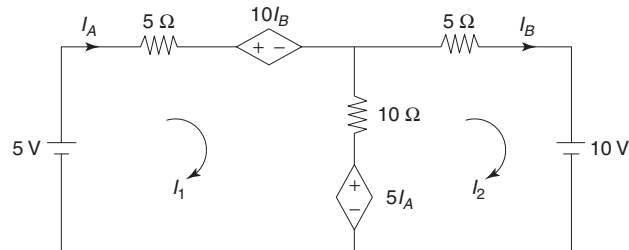


Fig. 2.12

$$I_A = I_1 \quad \dots(i)$$

$$I_B = I_2 \quad \dots(ii)$$

Applying KVL to Mesh 1,

$$5 - 5I_1 - 10I_B - 10(I_1 - I_2) - 5I_A = 0$$

$$5 - 5I_1 - 10I_2 - 10I_1 + 10I_2 - 5I_1 = 0$$

$$-20I_1 = -5$$

$$I_1 = \frac{1}{4} = 0.25 \text{ A} \quad \dots(iii)$$

Applying KVL to Mesh 2,

$$5I_A - 10(I_2 - I_1) - 5I_2 - 10 = 0$$

$$5I_1 - 10I_2 + 10I_1 - 5I_2 = 10$$

$$15I_1 - 15I_2 = 10$$

...(iv)

Putting  $I_1 = 0.25 \text{ A}$  in Eq. (iv),

$$15(0.25) - 15I_2 = 10$$

$$I_2 = -0.416 \text{ A}$$

## 2.8 Circuit Theory and Networks—Analysis and Synthesis

**Example 2.6** Find the mesh currents in the network shown in Fig. 2.13.

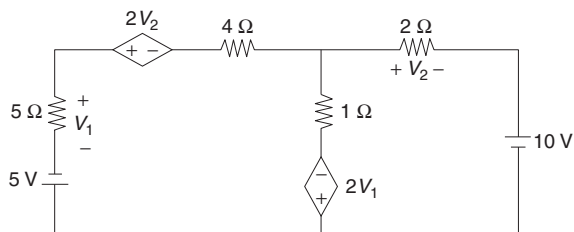


Fig. 2.13

**Solution** Assign clockwise currents in the two meshes as shown in Fig. 2.14.

From Fig. 2.14,

$$V_1 = -5I_1 \quad \dots(i)$$

$$V_2 = 2I_2 \quad \dots(ii)$$

Applying KVL to Mesh 1,

$$-5 - 5I_1 - 2V_2 - 4I_1 - 1(I_1 - I_2) + 2V_1 = 0$$

$$-5 - 5I_1 - 2(2I_2) - 4I_1 - I_1 + I_2 + 2(-5I_1) = 0$$

$$20I_1 + 3I_2 = -5$$

...(iii)

Applying KVL to Mesh 2,

$$-2V_1 - 1(I_2 - I_1) - 2I_2 - 10 = 0$$

$$-2(-5I_1) - I_2 + I_1 - 2I_2 = 10$$

$$11I_1 - 3I_2 = 10$$

...(iv)

Solving Eqs (iii) and (iv),

$$I_1 = 0.161 \text{ A}$$

$$I_2 = -2.742 \text{ A}$$

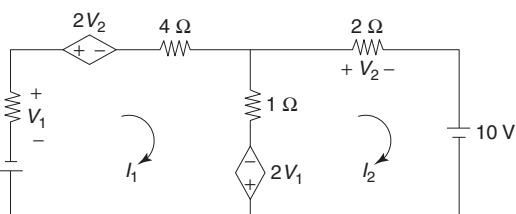


Fig. 2.14

**Example 2.7** Find currents  $I_x$  and  $I_y$  of the network shown in Fig. 2.15.

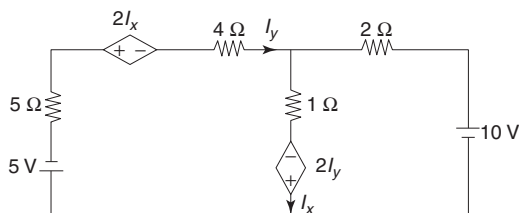


Fig. 2.15



**Solution** Assign clockwise currents in the two meshes as shown in Fig. 2.16.

From Fig. 2.16,

$$I_y = I_1 \quad \dots(i)$$

$$I_x = I_1 - I_2 \quad \dots(ii)$$

Applying KVL to Mesh 1,

$$-5 - 5I_1 - 2I_x - 4I_1 - 1(I_1 - I_2) + 2I_y = 0$$

$$-5 - 5I_1 - 2(I_1 - I_2) - 4I_1 - I_1 + I_2 + 2I_1 = 0$$

$$-5 - 5I_1 - 2I_1 + 2I_2 - 4I_1 - I_1 + I_2 + 2I_1 = 0$$

$$-10I_1 + 3I_2 = 5 \quad \dots(iii)$$

Applying KVL to Mesh 2,

$$-2I_y - 1(I_2 - I_1) - 2I_2 - 10 = 0$$

$$-2I_1 - I_2 + I_1 - 2I_2 = 10$$

$$-I_1 - 3I_2 = 10 \quad \dots(iv)$$


Solving Eqs (iii) and (iv),

$$I_1 = -\frac{15}{11} = -1.364 \text{ A}$$

$$I_2 = -2.878 \text{ A}$$


$$I_y = -1.364 \text{ A}$$

$$I_x = I_1 - I_2 = -1.364 + 2.878 = 1.514 \text{ A}$$

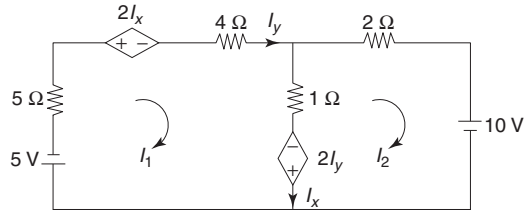


**Fig. 2.16**

**Example 2.8** Find the currents in the three meshes of the network shown in Fig. 2.17.

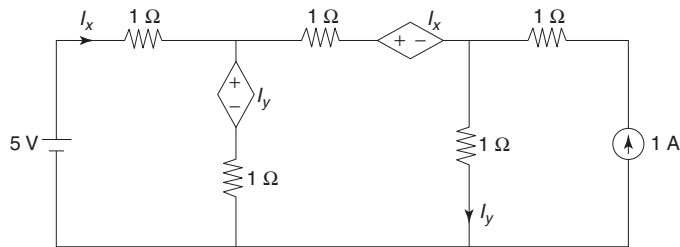

**Fig. 2.17**

**Solution** Assign clockwise currents in the three meshes as shown in Fig. 2.18.

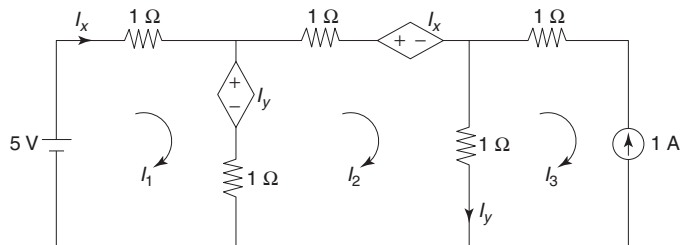

**Fig. 2.18**

## 2.10 Circuit Theory and Networks—Analysis and Synthesis

From Fig. 2.18,

$$I_x = I_1 \quad \dots(i)$$

$$I_x = I_1$$

$$I_y = I_2 - I_3 \quad \dots(ii)$$

Applying KVL to Mesh 1,

$$5 - 1I_1 - I_y - 1(I_1 - I_2) = 0$$

$$5 - I_1 - (I_2 - I_3) - (I_1 - I_2) = 0$$

$$-2I_1 + I_3 = -5 \quad \dots(iii)$$

Applying KVL to Mesh 2,

$$-1(I_2 - I_1) + I_y - 1I_2 - I_x - 1(I_2 - I_3) = 0$$

$$-(I_2 - I_1) + (I_2 - I_3) - I_2 - I_1 - (I_2 - I_3) = 0$$

$$-2I_2 = 0 \quad \dots(iv)$$

For Mesh 3,

$$I_3 = -1 \quad \dots(v)$$

Solving Eqs (iii), (iv) and (v),

$$I_1 = 2 \text{ A}$$

$$I_2 = 0$$

$$I_3 = -1 \text{ A}$$

### Example 2.9

For the network shown in Fig. 2.19, find the power supplied by the dependent voltage source.

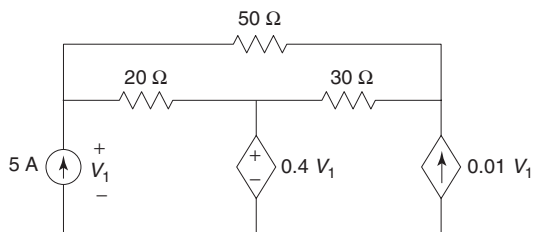


Fig. 2.19

**Solution** Assign clockwise currents in three meshes as shown in Fig. 2.20.

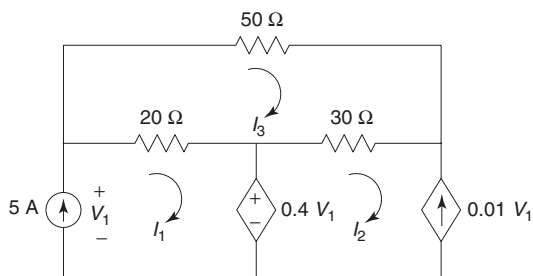


Fig. 2.20

From Fig. 2.20,

$$\begin{aligned} V_1 - 20(I_1 - I_3) - 0.4 V_1 &= 0 \\ 0.6 V_1 &= 20 I_1 - 20 I_3 \\ V_1 &= 33.33 I_1 - 33.33 I_3 \end{aligned} \quad \dots(i)$$

For Mesh 1,

$$I_1 = 5 \quad \dots(ii)$$

For Mesh 2,

$$\begin{aligned} I_2 &= -0.01 V_1 = -0.01(33.33 I_1 - 33.33 I_3) \\ 0.33 I_1 + I_2 - 0.33 I_3 &= 0 \end{aligned} \quad \dots(iii)$$

Applying KVL to Mesh 3,

$$\begin{aligned} -50 I_3 - 30(I_3 - I_2) - 20(I_3 - I_1) &= 0 \\ -20 I_1 - 30 I_2 + 100 I_3 &= 0 \end{aligned} \quad \dots(iv)$$

Solving Eqs (ii), (iii) and (iv),

$$\begin{aligned} I_1 &= 5 \text{ A} \\ I_2 &= -1.47 \text{ A} \\ I_3 &= 0.56 \text{ A} \end{aligned}$$

$$V_1 = 33.33 I_1 - 33.33 I_3 = 33.33(5) - 33.33(0.56) = 148 \text{ V}$$

$$\text{Power supplied by the dependent voltage source} = 0.4 V_1(I_1 - I_2) = 0.4(148)(5 + 1.47) = 383.02 \text{ W}$$

**Example 2.10** Find the voltage  $V_x$  in the network shown in Fig. 2.21.

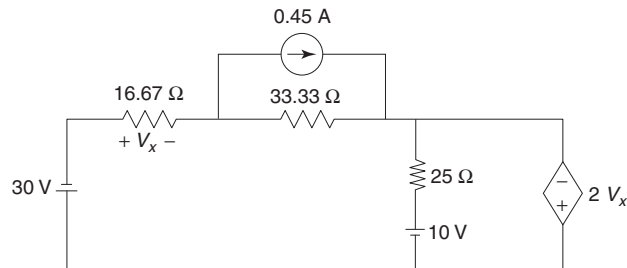


Fig. 2.21

**Solution** Assign clockwise currents in the three meshes as shown in Fig. 2.22.

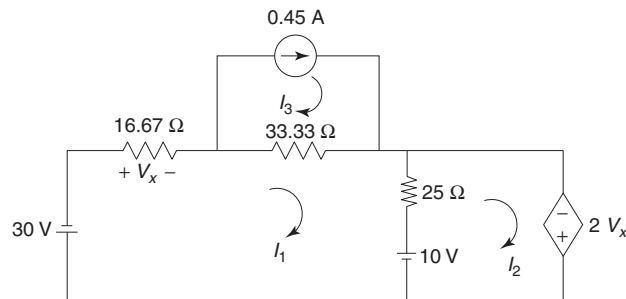


Fig. 2.22

## 2.12 Circuit Theory and Networks—Analysis and Synthesis

From Fig. 2.22,

$$V_x = 16.67 I_1 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$\begin{aligned} -30 - 16.67 I_1 - 33.33(I_1 - I_3) - 25(I_1 - I_2) - 10 &= 0 \\ -30 - 16.67 I_1 - 33.33 I_1 + 33.33 I_3 - 25 I_1 + 25 I_2 - 10 &= 0 \\ -75 I_1 + 25 I_2 + 33.33 I_3 &= 40 \end{aligned} \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$\begin{aligned} 10 - 25(I_2 - I_1) + 2 V_x &= 0 \\ 10 - 25(I_2 - I_1) + 2(16.67 I_1) &= 0 \\ 10 - 25 I_2 + 25 I_1 + 33.34 I_1 &= 0 \\ 58.34 I_1 - 25 I_2 &= -10 \end{aligned} \quad \dots(iii)$$


For Mesh 3,

$$I_3 = 0.45 \quad \dots(iv)$$

Solving Eqs (ii), (iii) and (iv),

$$\begin{aligned} I_1 &= -0.9 \text{ A} \\ I_2 &= -1.7 \text{ A} \\ I_3 &= 0.45 \text{ A} \\ V_x &= 16.67 I_1 = 16.67 (-0.9) = -15 \text{ V} \end{aligned} \quad \dots(v)$$

**Example 2.11** For the network shown in Fig. 2.23, find the mesh currents  $I_1$ ,  $I_2$  and  $I_3$ .

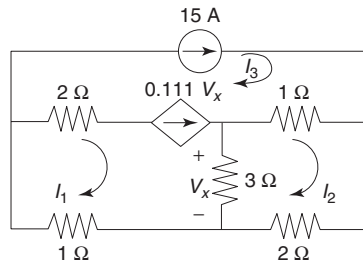

**Fig. 2.23**

**Solution** From Fig. 2.23,

$$V_x = 3(I_1 - I_2) \quad \dots(i)$$

Writing current equation for the two current sources,

$$I_3 = 15 \quad \dots(ii)$$

and

$$\begin{aligned} 0.111 V_x &= I_1 - I_3 \\ 0.111 [3(I_1 - I_2)] &= I_1 - I_3 \end{aligned}$$

$$0.333 I_1 - 0.333 I_2 - I_1 + I_3 = 0$$

$$-0.667 I_1 - 0.333 I_2 + I_3 = 0 \quad \dots(\text{iii})$$

Applying KVL to Mesh 2,

$$-3(I_2 - I_1) - 1(I_2 - I_3) - 2 I_2 = 0$$

$$-3 I_1 + 6 I_2 - I_3 = 0 \quad \dots(\text{iv})$$

Solving Eqs (ii), (iii) and (iv),

$$I_1 = 17 \text{ A}$$

$$I_2 = 11 \text{ A}$$

$$I_3 = 15 \text{ A}$$

**Example 2.12** For the network shown in Fig. 2.24, find the magnitude of  $V_0$  and the current supplied by it, given that power loss in  $R_L = 2 \Omega$  resistor is  $18 \text{ W}$ .

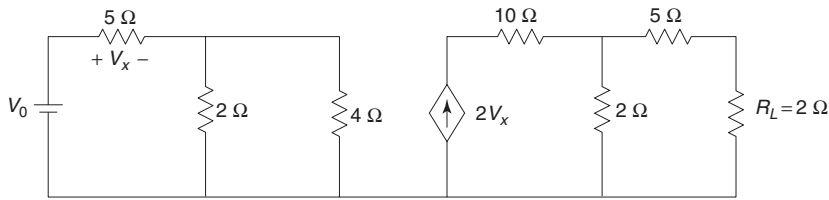


Fig. 2.24

**Solution** Assign clockwise currents in meshes as shown in Fig. 2.25.

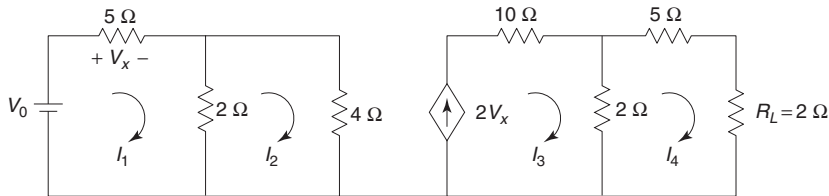


Fig. 2.25

From Fig. 2.25,

$$V_x = 5 I_1 \quad \dots(\text{i})$$

Also,

$$I_4^2 R_L = 18$$

$$I_4^2 (2) = 18$$

$$I_4 = 3 \text{ A} \quad \dots(\text{ii})$$

Applying KVL to Mesh 1,

$$V_0 - 5 I_1 - 2(I_1 - I_2) = 0$$

$$7 I_1 - 2 I_2 = V_0 \quad \dots(\text{iii})$$

## 2.14 Circuit Theory and Networks—Analysis and Synthesis

Applying KVL to Mesh 2,

$$\begin{aligned} -2(I_2 - I_1) - 4I_2 &= 0 \\ -2I_1 + 6I_2 &= 0 \end{aligned} \quad \dots(\text{iv})$$

For Mesh 3,

$$\begin{aligned} I_3 &= 2V_x = 2(5I_1) = 10I_1 \\ 10I_1 - I_3 &= 0 \end{aligned} \quad \dots(\text{v})$$

Applying KVL to Mesh 4,

$$\begin{aligned} -2(I_4 - I_3) - 5I_4 - 2I_4 &= 0 \\ -2I_3 + 9I_4 &= 0 \\ -2I_3 + 9(3) &= 0 \\ I_3 &= 13.5 \text{ A} \end{aligned}$$

From Eq. (v),

$$I_1 = \frac{I_3}{10} = \frac{13.5}{10} = 1.35 \text{ A}$$

From Eq. (iv),

$$\begin{aligned} -2(1.35) + 6I_2 &= 0 \\ I_2 &= 0.45 \text{ A} \end{aligned}$$

From Eq. (iii),

$$\begin{aligned} 7(1.35) - 2(0.45) &= V_0 \\ V_0 &= 8.55 \text{ V} \end{aligned}$$

Current supplied by voltage source  $V_0 = I_1 = 1.35 \text{ A}$

**Example 2.13** In the network shown in Fig. 2.26, find voltage  $V_2$  such that  $V_x = 0$ .

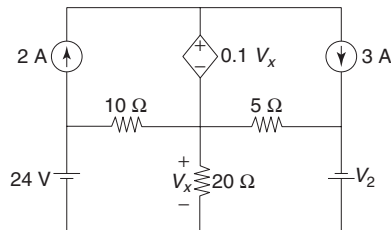


Fig. 2.26

**Solution** Assign clockwise currents in four meshes as shown in Fig. 2.27.

From Fig. 2.27,

$$V_x = 20(I_3 - I_4) \quad \dots(\text{i})$$

Writing current equations for Meshes 1 and 2,

$$I_1 = 2 \quad \dots(\text{ii})$$

$$I_2 = 3 \quad \dots(\text{iii})$$

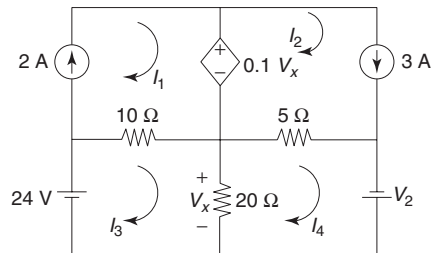


Fig. 2.27

Applying KVL to Mesh 3,

$$24 - 10(I_3 - I_1) - 20(I_3 - I_4) = 0$$

$$24 - 10(I_3 - 2) - 20(I_3 - I_4) = 0$$

$$-30I_3 + 20I_4 = -44 \quad \dots(\text{iv})$$

Applying KVL to Mesh 4,

$$-20(I_4 - I_3) - 5(I_4 - I_2) + V_2 = 0$$

$$-20(I_4 - I_3) - 5(I_4 - 3) + V_2 = 0$$

$$20I_3 - 25I_4 = -V_2 - 15 \quad \dots(\text{v})$$

But

$$V_x = 0$$

$$20(I_3 - I_4) = 0$$

$$I_3 = I_4$$

From Eq. (iv),

$$-30I_3 + 20I_3 = -44$$

$$I_3 = 4.4 \text{ A}$$

$$I_4 = 4.4 \text{ A}$$

From Eq. (v),

$$20(4.4) - 25(4.4) = -V_2 - 15$$

$$V_2 = 7 \text{ V}$$

## 2.4 || SUPERMESH ANALYSIS

Meshes that share a current source with other meshes, none of which contains a current source in the outer loop, form a supermesh. A path around a supermesh doesn't pass through a current source. A path around each mesh contained within a supermesh passes through a current source. The total number of equations required for a supermesh is equal to the number of meshes contained in the supermesh. A supermesh requires one mesh current equation, that is, a KVL equation. The remaining mesh current equations are KCL equations.

**Example 2.14** Find the current in the  $3 \Omega$  resistor of the network shown in Fig. 2.28.

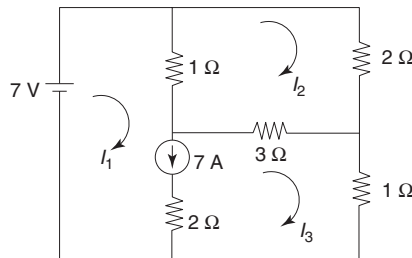


Fig. 2.28

**Solution** Meshes 1 and 3 will form a supermesh.

Writing current equation for the supermesh,

$$I_1 - I_3 = 7 \quad \dots(\text{i})$$

## 2.16 Circuit Theory and Networks—Analysis and Synthesis

Applying KVL to the outer path of the supermesh,

$$\begin{aligned}7 - 1(I_1 - I_2) - 3(I_3 - I_2) - 1I_3 &= 0 \\ -I_1 + 4I_2 - 4I_3 &= -7\end{aligned}\quad \dots(\text{ii})$$

Applying KVL to Mesh 2,

$$\begin{aligned}-1(I_2 - I_1) - 2I_2 - 3(I_2 - I_3) &= 0 \\ I_1 - 6I_2 + 3I_3 &= 0\end{aligned}\quad \dots(\text{iii})$$

Solving Eqs (i), (ii) and (iii),

$$\begin{aligned}I_1 &= 9 \text{ A} \\ I_2 &= 2.5 \text{ A} \\ I_3 &= 2 \text{ A}\end{aligned}$$

Current through the  $3 \Omega$  resistor  $= I_2 - I_3 = 2.5 - 2 = 0.5 \text{ A}$

**Example 2.15** Find the current in the  $5 \Omega$  resistor of the network shown in Fig. 2.29.

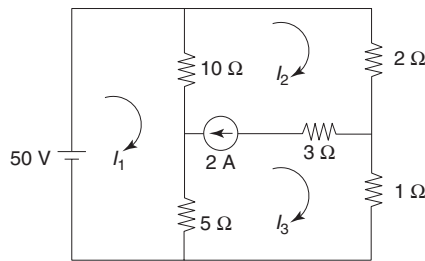


Fig. 2.29

**Solution** Applying KVL to Mesh 1,

$$\begin{aligned}50 - 10(I_1 - I_2) - 5(I_1 - I_3) &= 0 \\ 15I_1 - 10I_2 - 5I_3 &= 50\end{aligned}\quad \dots(\text{i})$$

Mesches 2 and 3 will form a supermesh as these two meshes share a common current source of 2 A.

Writing current equation for the supermesh,

$$I_2 - I_3 = 2 \quad \dots(\text{ii})$$

Applying KVL to the outer path of the supermesh,

$$\begin{aligned}-10(I_2 - I_1) - 2I_2 - 1I_3 - 5(I_3 - I_1) &= 0 \\ -15I_1 + 12I_2 + 6I_3 &= 0\end{aligned}\quad \dots(\text{iii})$$

Solving Eqs (i), (ii) and (iii),

$$\begin{aligned}I_1 &= 20 \text{ A} \\ I_2 &= 17.33 \text{ A} \\ I_3 &= 15.33 \text{ A}\end{aligned}$$



Current through the  $5\ \Omega$  resistor  $= I_1 - I_3 = 20 - 15.33 = 4.67\text{ A}$

**Example 2.16** Determine the power delivered by the voltage source and the current in the  $10\ \Omega$  resistor of the network shown in Fig. 2.30.

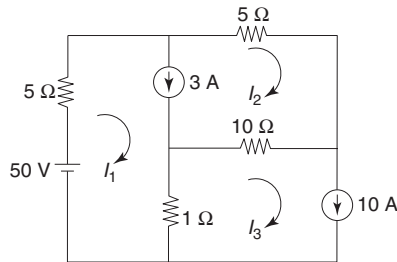


Fig. 2.30

**Solution** Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_1 - I_2 = 3 \quad \dots(i)$$

Applying KVL to the outer path of the supermesh,

$$\begin{aligned} 50 - 5I_1 - 5I_2 - 10(I_2 - I_3) - 1(I_1 - I_3) &= 0 \\ -6I_1 - 15I_2 + 11I_3 &= -50 \end{aligned} \quad \dots(ii)$$

For Mesh 3,

$$I_3 = 10 \quad \dots(iii)$$

Solving Eqs (i), (ii) and (iii),

$$I_1 = 9.76\text{ A}$$

$$I_2 = 6.76\text{ A}$$

$$I_3 = 10\text{ A}$$

Power delivered by the voltage source  $= 50 I_1 = 50 \times 9.76 = 488\text{ W}$

$$I_{10\Omega} = I_3 - I_2 = 10 - 6.76 = 3.24\text{ A}$$

**Example 2.17** For the network shown in Fig. 2.31, find current through the  $8\ \Omega$  resistor.

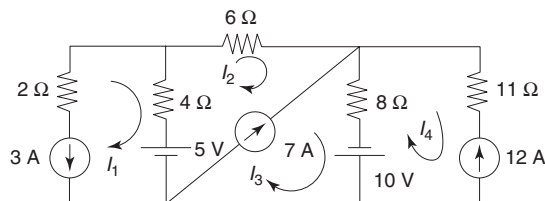


Fig. 2.31

## 2.18 Circuit Theory and Networks—Analysis and Synthesis

Writing current equations for meshes 1 and 4,

$$I_1 = -3 \quad \dots(i)$$

$$I_4 = -12 \quad \dots(ii)$$

Mesches 2 and 3 will form a supermesh.

Writing current equation for the supermesh,

$$I_3 - I_2 = 7 \quad \dots(iii)$$

Applying KVL to the outer path of the supermesh,

$$5 - 4(I_2 - I_1) - 6I_2 - 8(I_3 - I_4) + 10 = 0$$

$$5 - 4(I_2 + 3) - 6I_2 - 8(I_3 + 12) + 10 = 0$$

$$-10I_2 - 8I_3 = 93 \quad \dots(iv)$$

Solving Eqs (iii) and (iv),

$$I_2 = -8.28 \text{ A}$$

$$I_3 = -1.28 \text{ A}$$

$$I_{8\Omega} = I_3 - I_4 = -1.28 + 12 = 10.72 \text{ A}$$

## EXAMPLES WITH DEPENDENT SOURCES

**Example 2.18** In the network of Fig. 2.32, find currents  $I_1$  and  $I_2$ .

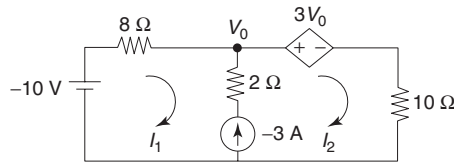


Fig. 2.32

**Solution** From Fig. 2.32,

$$-10 - 8I_1 - V_0 = 0$$

$$V_0 = -10 - 8I_1 \quad \dots(i)$$

Mesches 1 and 2 will form a supermesh.

Writing current equations for the supermesh,

$$I_2 - I_1 = -3 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$-10 - 8I_1 - 3V_0 - 10I_2 = 0$$

$$-10 - 8I_1 - 3(-10 - 8I_1) - 10I_2 = 0$$

$$16I_1 - 10I_2 = -20 \quad \dots(iii)$$


Solving Eqs (ii) and (iii),

$$I_1 = -8.33 \text{ A}$$

$$I_2 = -11.33 \text{ A}$$

**Example 2.19**

In the network of Fig. 2.33, find the current through the  $3\ \Omega$  resistor.

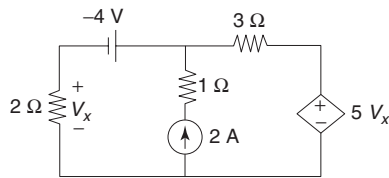**Fig. 2.33**

**Solution** Assign clockwise currents in two meshes as shown in Fig. 2.34.

From Fig. 2.34,

$$V_x = -2 I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh.

Writing current equations for the supermesh,

$$I_2 - I_1 = 2 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$-2 I_1 - 4 - 3 I_2 - 5 V_x = 0$$

$$-2 I_1 - 4 - 3 I_2 - 5(-2 I_1) = 0$$


$$8 I_1 - 3 I_2 = 4 \quad \dots(iii)$$

Solving Eqs (ii) and (iii),


$$I_1 = 2\text{ A}$$

$$I_2 = 4\text{ A}$$

$$I_{3\ \Omega} = I_2 = 4\text{ A}$$

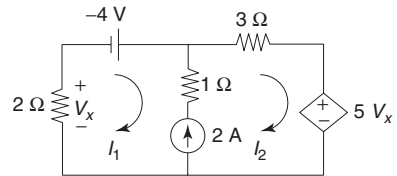**Fig. 2.34****Example 2.20**

Find the currents  $I_1$  and  $I_2$  at the network shown in Fig. 2.35.

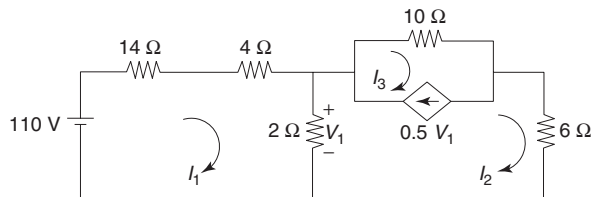**Fig. 2.35**

**Solution** From Fig. 2.35,

$$V_1 = 2(I_1 - I_2)$$

Meshes 2 and 3 will form a supermesh.

Writing current equation for the supermesh,

$$I_3 - I_2 = 0.5 V_1 = 0.5 \times 2(I_1 - I_2) = I_1 - I_2$$

$$I_3 = I_1$$

## 2.20 Circuit Theory and Networks—Analysis and Synthesis

Applying KVL to outer path of the supermesh,

$$\begin{aligned}-2(I_2 - I_1) - 10 I_3 - 6 I_2 &= 0 \\ -2 I_2 + 2 I_1 - 10 I_1 - 6 I_2 &= 0 \\ I_1 &= -I_2\end{aligned}$$

Applying KVL to Mesh 1,

$$\begin{aligned}110 - 14 I_1 - 4 I_1 - 2(I_1 - I_2) &= 0 \\ 110 - 20 I_1 + 2 I_2 &= 0 \\ 110 + 20 I_1 + 2 I_2 &= 0 \\ I_2 &= -5 \text{ A} \\ I_1 &= -I_2 = 5 \text{ A}\end{aligned}$$

**Example 2.21** For the network of Fig. 2.36, find current through the  $8 \Omega$  resistor.

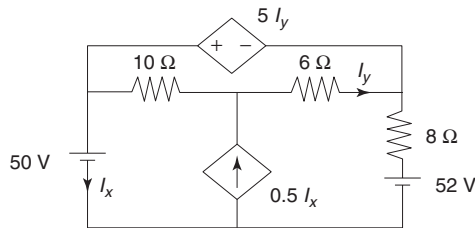


Fig. 2.36

**Solution** Assign clockwise currents to the three meshes as shown in Fig. 2.37.

From Fig. 2.37,

$$I_x = -I_1 \quad \dots(\text{i})$$

$$I_y = I_2 - I_3 \quad \dots(\text{ii})$$

Mesches 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$\begin{aligned}I_2 - I_1 &= 0.5 I_x = 0.5 (-I_1) \\ -0.5 I_1 + I_2 &= 0 \quad \dots(\text{iii})\end{aligned}$$

Applying KVL to the outer path of the supermesh,

$$\begin{aligned}50 - 10(I_1 - I_3) - 6(I_2 - I_3) - 8 I_2 - 52 &= 0 \\ -10 I_1 - 14 I_2 + 16 I_3 &= 2 \quad \dots(\text{iv})\end{aligned}$$

Applying KVL to Mesh 3,

$$\begin{aligned}-5 I_y - 6(I_3 - I_2) - 10(I_3 - I_1) &= 0 \\ -5(I_2 - I_3) - 6(I_3 - I_2) - 10(I_3 - I_1) &= 0 \\ 10 I_1 + I_2 - 11 I_3 &= 0 \quad \dots(\text{v})\end{aligned}$$

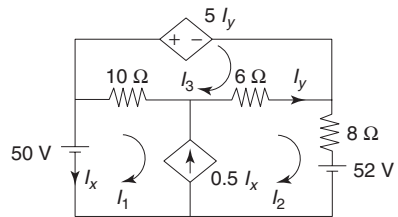


Fig. 2.37

Solving Eqs (iii), (iv) and (v),

$$I_1 = -1.56 \text{ A}$$

$$I_2 = -0.58 \text{ A}$$

$$I_3 = -1.11 \text{ A}$$

$$I_{8\Omega} = I_2 = -0.58 \text{ A}$$

**Example 2.22** For the network shown in Fig. 2.38, find the current through the  $10\ \Omega$  resistor.

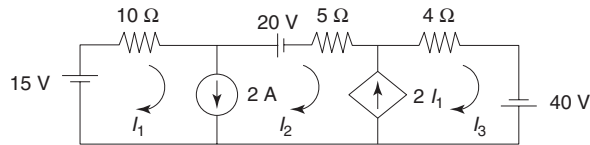


Fig. 2.38

**Solution** Meshes 1, 2 and 3 will form a supermesh.

Writing current equations for the supermesh,

$$I_1 - I_2 = 2 \quad \dots(i)$$

$$I_3 - I_2 = 2 I_1$$

and

$$2 I_1 + I_2 - I_3 = 0 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$15 - 10 I_1 - 20 - 5 I_2 - 4 I_3 + 40 = 0$$

$$10 I_1 + 5 I_2 + 4 I_3 = 35 \quad \dots(iii)$$

Solving Eqs (i), (ii) and (iii),

$$I_1 = 1.96 \text{ A}$$

$$I_2 = -0.04 \text{ A}$$

$$I_3 = 3.89 \text{ A}$$

$$I_{10\Omega} = I_1 = 1.96 \text{ A}$$

**Example 2.23** In the network shown in Fig. 2.39, find the power delivered by the  $4\text{ V}$  source and voltage across the  $2\ \Omega$  resistor.

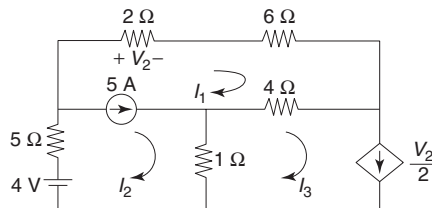


Fig. 2.39

**Solution** From Fig. 2.39,

$$V_2 = 2 I_1 \quad \dots(i)$$

## 2.22 Circuit Theory and Networks—Analysis and Synthesis

Meshe 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1 = 5 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$\begin{aligned} 4 - 5I_2 - 2I_1 - 6I_1 - 4(I_1 - I_3) - 1(I_2 - I_3) &= 0 \\ -12I_1 - 6I_2 + 5I_3 &= -4 \end{aligned} \quad \dots(iii)$$

For Mesh 3,

$$\begin{aligned} I_3 &= \frac{V_2}{2} = \frac{2I_1}{2} = I_1 \\ I_1 - I_3 &= 0 \end{aligned} \quad \dots(iv)$$

Solving Eqs (ii), (iii) and (iv),

$$\begin{aligned} I_1 &= -2 \text{ A} \\ I_2 &= 3 \text{ A} \\ I_3 &= -2 \text{ A} \end{aligned}$$

Power delivered by the 4 V source =  $4I_2 = 4(3) = 12 \text{ W}$

$$V_{2\Omega} = 2I_1 = 2(-2) = -4 \text{ V}$$

**Example 2.24** Find currents  $I_1, I_2, I_3, I_4$  of the network shown in Fig. 2.40.

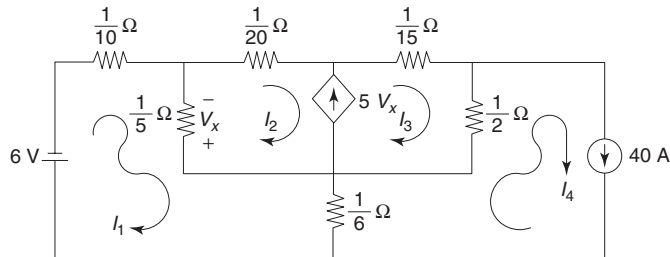


Fig. 2.40

From Fig. 2.40,

$$V_x = \frac{1}{5}(I_2 - I_1) \quad \dots(i)$$

For Mesh 4,

$$I_4 = 40 \quad \dots(ii)$$

Applying KVL to Mesh 1,

$$\begin{aligned} -6 - \frac{1}{10}I_1 - \frac{1}{5}(I_1 - I_2) - \frac{1}{6}(I_1 - I_4) &= 0 \\ -6 - \frac{1}{10}I_1 - \frac{1}{5}I_1 + \frac{1}{5}I_2 - \frac{1}{6}I_1 + \frac{1}{6}(40) &= 0 \\ -\frac{7}{15}I_1 + \frac{1}{5}I_2 &= -\frac{2}{3} \end{aligned} \quad \dots(iii)$$

Mesh 2 and 3 will form a supermesh.

Writing current equation for the supermesh,

$$I_3 - I_2 = 5 V_x = 5 \left[ \frac{1}{5} (I_2 - I_1) \right] = I_2 - I_1$$

$$I_1 - 2I_2 + I_3 = 0 \quad \dots(\text{iv})$$

Applying KVL to the outer path of the supermesh,

$$-\frac{1}{5}(I_2 - I_1) - \frac{1}{20}I_2 - \frac{1}{15}I_3 - \frac{1}{2}(I_3 - I_4) = 0$$

$$-\frac{1}{5}I_2 + \frac{1}{5}I_1 - \frac{1}{20}I_2 - \frac{1}{15}I_3 - \frac{1}{2}I_3 + \frac{1}{2}(40) = 0$$

$$\frac{1}{5}I_1 - \frac{1}{4}I_2 - \frac{17}{30}I_3 = -20 \quad \dots(\text{v})$$

Solving Eqs (iii), (iv) and (v),

$$I_1 = 10 \text{ A}$$

$$I_2 = 20 \text{ A}$$

$$I_3 = 30 \text{ A}$$

$$I_4 = 40 \text{ A}$$

## 2.5 || NODE ANALYSIS

Node analysis is based on Kirchhoff's current law which states that the algebraic sum of currents meeting at a point is zero. Every junction where two or more branches meet is regarded as a node. One of the nodes in the network is taken as *reference node* or *datum node*. If there are  $n$  nodes in any network, the number of simultaneous equations to be solved will be  $(n - 1)$ .

### Steps to be followed in Node Analysis

1. Assuming that a network has  $n$  nodes, assign a reference node and the reference directions, and assign a current and a voltage name for each branch and node respectively.
2. Apply KCL at each node except for the reference node and apply Ohm's law to the branch currents.
3. Solve the simultaneous equations for the unknown node voltages.
4. Using these voltages, find any branch currents required.

### Example 2.25

Determine the current through the  $5 \Omega$  resistor for the network shown in Fig. 2.41.

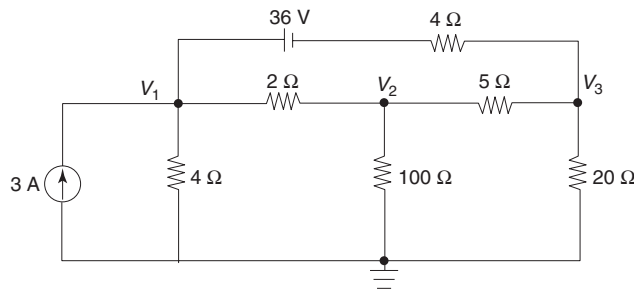


Fig. 2.41

## 2.24 Circuit Theory and Networks—Analysis and Synthesis

**Solution** Assume that the currents are moving away from the nodes.  
Applying KCL at Node 1,

$$\begin{aligned}\frac{V_1}{4} + \frac{V_1 - V_2}{2} + \frac{V_1 - 36 - V_3}{4} &= 3 \\ \left(\frac{1}{4} + \frac{1}{2} + \frac{1}{4}\right)V_1 - \frac{1}{2}V_2 - \frac{1}{4}V_3 &= 3 + \frac{36}{4} \\ V_1 - 0.5V_2 - 0.25V_3 &= 12 \quad \dots(i)\end{aligned}$$

Applying KCL at Node 2,

$$\begin{aligned}\frac{V_2 - V_1}{2} + \frac{V_2}{100} + \frac{V_2 - V_3}{5} &= 0 \\ -\frac{1}{2}V_1 + \left(\frac{1}{2} + \frac{1}{100} + \frac{1}{5}\right)V_2 - \frac{1}{5}V_3 &= 0 \\ -0.5V_1 + 0.71V_2 - 0.2V_3 &= 0 \quad \dots(ii)\end{aligned}$$

Applying KCL at Node 3,

$$\begin{aligned}\frac{V_3 - V_2}{5} + \frac{V_3}{20} + \frac{V_3 - (-36) - V_1}{4} &= 0 \\ -\frac{1}{4}V_1 - \frac{1}{5}V_2 + \left(\frac{1}{5} + \frac{1}{20} + \frac{1}{4}\right)V_3 &= -9 \\ -0.25V_1 - 0.2V_2 + 0.5V_3 &= -9 \quad \dots(iii)\end{aligned}$$

Solving Eqs (i), (ii) and (iii),

$$V_1 = 13.41 \text{ V}$$

$$V_2 = 7.06 \text{ V}$$

$$V_3 = -8.47 \text{ V}$$

$$\text{Current through the } 5 \Omega \text{ resistor} = \frac{V_2 - V_3}{5} = \frac{7.06 - (-8.47)}{5} = 3.11 \text{ A}$$

**Example 2.26** Find the power dissipated in the  $6 \Omega$  resistor for the network shown in Fig. 2.42.

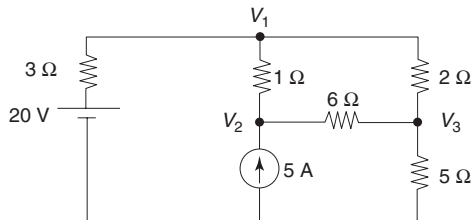


Fig. 2.42



**Solution** Assume that the currents are moving away from the nodes.

Applying KCL at Node 1,

$$\begin{aligned}\frac{V_1 - 20}{3} + \frac{V_1 - V_2}{1} + \frac{V_1 - V_3}{2} &= 0 \\ \left(\frac{1}{3} + 1 + \frac{1}{2}\right)V_1 - V_2 - \frac{1}{2}V_3 &= \frac{20}{3} \\ 1.83V_1 - V_2 - 0.5V_3 &= 6.67\end{aligned}\quad \dots(i)$$

Applying KCL at Node 2,

$$\begin{aligned}\frac{V_2 - V_1}{1} + \frac{V_2 - V_3}{6} &= 5 \\ -V_1 + \left(1 + \frac{1}{6}\right)V_2 - \frac{1}{6}V_3 &= 5 \\ -V_1 + 1.17V_2 - 0.17V_3 &= 5\end{aligned}\quad \dots(ii)$$

Applying KCL at Node 3,

$$\begin{aligned}\frac{V_3 - V_1}{2} + \frac{V_3}{5} + \frac{V_3 - V_2}{6} &= 0 \\ -\frac{1}{2}V_1 - \frac{1}{6}V_2 + \left(\frac{1}{2} + \frac{1}{5} + \frac{1}{6}\right)V_3 &= 0 \\ -0.5V_1 - 0.17V_2 + 0.87V_3 &= 0\end{aligned}\quad \dots(iii)$$

Solving Eqs (i), (ii) and (iii),

$$V_1 = 23.82 \text{ V}$$


$$V_2 = 27.4 \text{ V}$$

$$V_3 = 19.04 \text{ V}$$

$$I_{6\Omega} = \frac{V_2 - V_3}{6} = \frac{27.4 - 19.04}{6} = 1.39 \text{ A}$$

Power dissipated in the  $6\Omega$  resistor  $= (1.39)^2 \times 6 = 11.59 \text{ W}$

**Example 2.27** Find  $V_1$  and  $V_2$  for the network shown in Fig. 2.43.

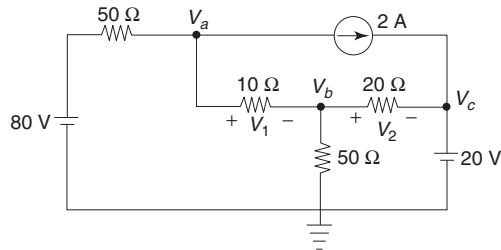

**Fig. 2.43**

## 2.26 Circuit Theory and Networks—Analysis and Synthesis

**Solution** Assume that the currents are moving away from the nodes.

Applying KCL at Node  $a$ ,

$$\begin{aligned}\frac{V_a - 80}{50} + \frac{V_a - V_b}{10} + 2 &= 0 \\ \left(\frac{1}{50} + \frac{1}{10}\right)V_a - \frac{1}{10}V_b &= \frac{80}{50} - 2 \\ 0.12V_a - 0.1V_b &= -0.4\end{aligned}\quad \dots(i)$$

Applying KCL at Node  $b$ ,

$$\begin{aligned}\frac{V_b - V_a}{10} + \frac{V_b}{50} + \frac{V_b - V_c}{20} &= 0 \\ -\frac{1}{10}V_a + \left(\frac{1}{10} + \frac{1}{50} + \frac{1}{20}\right)V_b - \frac{1}{20}V_c &= 0 \\ -0.1V_a + 0.17V_b - 0.05V_c &= 0\end{aligned}\quad \dots(ii)$$

Node  $c$  is directly connected to a voltage source of 20 V. Hence, we can write voltage equation at Node  $c$ .

$$V_c = 20 \quad \dots(iii)$$

Solving Eqs (i), (ii), and (iii),


$$V_a = 3.08 \text{ V}$$

$$V_b = 7.69 \text{ V}$$

$$V_1 = V_a - V_b = 3.08 - 7.69 = -4.61 \text{ V}$$

$$V_2 = V_b - V_c = 7.69 - 20 = -12.31 \text{ V}$$

**Example 2.28** Find the voltage across the  $100 \Omega$  resistor for the network shown in Fig. 2.44.

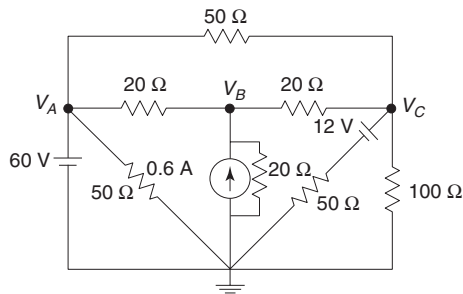

**Fig. 2.44**

**Solution**

Node  $A$  is directly connected to a voltage source of 60 V. Hence, we can write voltage equation at Node  $A$ .

$$V_A = 60 \quad \dots(i)$$

Assume that the currents are moving away from the nodes.

Applying KCL at Node B,

$$\begin{aligned}\frac{V_B - V_A}{20} + \frac{V_B - V_C}{20} + \frac{V_B}{20} &= 0.6 \\ -\frac{1}{20}V_A + \left(\frac{1}{20} + \frac{1}{20} + \frac{1}{20}\right)V_B - \frac{1}{20}V_C &= 0.6 \\ -0.05V_A + 0.15V_B - 0.05V_C &= 0.6\end{aligned}\quad \dots(\text{ii})$$

Applying KCL at Node C,

$$\begin{aligned}\frac{V_C - V_A}{50} + \frac{V_C - V_B}{20} + \frac{V_C - 12}{50} + \frac{V_C}{100} &= 0 \\ -\frac{1}{50}V_A - \frac{1}{20}V_B + \left(\frac{1}{50} + \frac{1}{20} + \frac{1}{50} + \frac{1}{100}\right)V_C &= \frac{12}{50} \\ -0.02V_A - 0.05V_B + 0.1V_C &= 0.24\end{aligned}\quad \dots(\text{iii})$$

Solving Eqs (i), (ii), and (iii),

$$V_C = 31.68 \text{ V}$$

$$\text{Voltage across the } 100 \Omega \text{ resistor} = 31.68 \text{ V}$$

## EXAMPLES WITH DEPENDENT SOURCES

**Example 2.29** Find the voltage across the  $5 \Omega$  resistor in the network shown in Fig. 2.45.

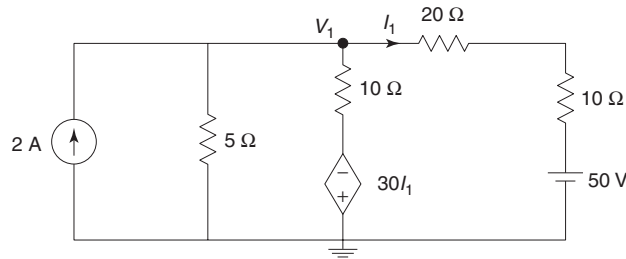


Fig. 2.45

**Solution** From Fig. 2.45,

$$I_1 = \frac{V_1 - 50}{20 + 10} = \frac{V_1 - 50}{30} \quad \dots(\text{i})$$

Assume that the currents are moving away from the node.

## 2.28 Circuit Theory and Networks—Analysis and Synthesis

Applying KCL at Node 1,


$$\begin{aligned}
 2 &= \frac{V_1}{5} + \frac{V_1 + 30}{10} + \frac{V_1 - 50}{30} \\
 2 &= \frac{V_1}{5} + \frac{V_1 + 30 \left( \frac{V_1 - 50}{30} \right)}{10} + \frac{V_1 - 50}{30} \\
 2 &= \frac{V_1}{5} + \frac{2V_1 - 50}{10} + \frac{V_1 - 50}{30} \quad \dots(ii)
 \end{aligned}$$

Solving Eq. (ii),

$$V_1 = 20 \text{ V}$$

Voltage across the  $5 \Omega$  resistor =  $20 \text{ V}$

**Example 2.30** For the network shown in Fig. 2.46, find the voltage  $V_x$ .

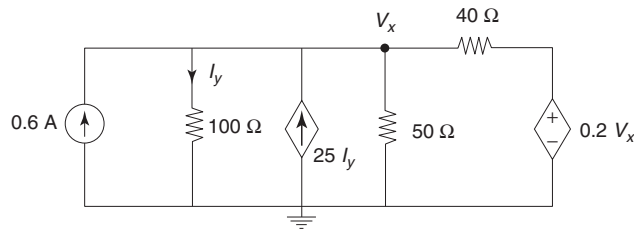

**Fig. 2.46**

**Solution** From Fig. 2.46,


$$I_y = \frac{V_x}{100} \quad \dots(i)$$

Assume that the currents are moving away from the node.

Applying KCL at Node  $x$ ,

$$\begin{aligned}
 25 I_y + 0.6 &= \frac{V_x}{100} + \frac{V_x}{50} + \frac{V_x - 0.2 V_x}{40} \\
 25 \left( \frac{V_x}{100} \right) + 0.6 &= \frac{V_x}{100} + \frac{V_x}{50} + \frac{0.8 V_x}{40} \\
 \left( \frac{1}{4} - \frac{1}{100} - \frac{1}{50} - \frac{0.8}{40} \right) V_x &= -0.6 \\
 0.2 V_x &= -0.6 \\
 V_x &= -3 \text{ V}
 \end{aligned}$$

**Example 2.31** For the network shown in Fig. 2.47, find voltages  $V_1$  and  $V_2$ .

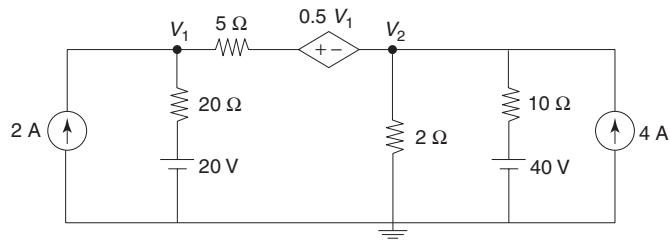

**Fig. 2.47**

**Solution** Assume that the currents are moving away from the nodes.  
Applying KCL at Node 1,

$$\begin{aligned}
 2 &= \frac{V_1 - 20}{20} + \frac{V_1 - 0.5V_1 - V_2}{5} \\
 \left( \frac{1}{20} + \frac{1}{5} - \frac{0.5}{5} \right) V_1 - \frac{1}{5} V_2 &= 3 \\
 0.15V_1 - 0.2V_2 &= 3 \quad \dots(i)
 \end{aligned}$$

Applying KCL at Node 2,


$$\begin{aligned}
 \frac{V_2 + 0.5V_1 - V_1}{5} + \frac{V_2}{2} + \frac{V_2 - 40}{10} &= 4 \\
 \left( \frac{0.5}{5} - \frac{1}{5} \right) V_1 + \left( \frac{1}{5} + \frac{1}{2} + \frac{1}{10} \right) V_2 &= 4 + \frac{40}{10} \\
 -0.1V_1 + 0.8V_2 &= 8 \quad \dots(ii)
 \end{aligned}$$

Solving Eqs (i) and (ii),

$$V_1 = 40 \text{ V}$$

$$V_2 = 15 \text{ V}$$

**Example 2.32** Determine the voltages  $V_1$  and  $V_2$  in the network of Fig. 2.48.

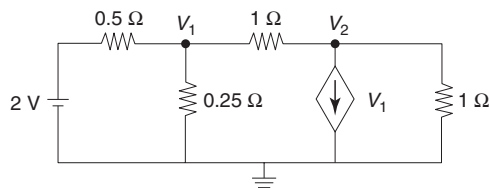

**Fig. 2.48**

### 2.30 Circuit Theory and Networks—Analysis and Synthesis

**Solution** Assume that the currents are moving away from the nodes.

Applying KCL at Node 1,

$$\begin{aligned}\frac{V_1 - 2}{0.5} + \frac{V_1}{0.25} + \frac{V_1 - V_2}{1} &= 0 \\ \left( \frac{1}{0.5} + \frac{1}{0.25} + 1 \right) V_1 - V_2 &= \frac{2}{0.5} \\ 7V_1 - V_2 &= 4\end{aligned}\quad \dots(i)$$


Applying KCL at Node 2,

$$\begin{aligned}\frac{V_2 - V_1}{1} + \frac{V_2}{1} + V_1 &= 0 \\ 2V_2 &= 0 \\ V_2 &= 0\end{aligned}\quad \dots(ii)$$

From Eq. (i),

$$V_1 = \frac{4}{7} \text{ V}$$

**Example 2.33** In the network of Fig. 2.49, find the node voltages  $V_1$ ,  $V_2$  and  $V_3$ .

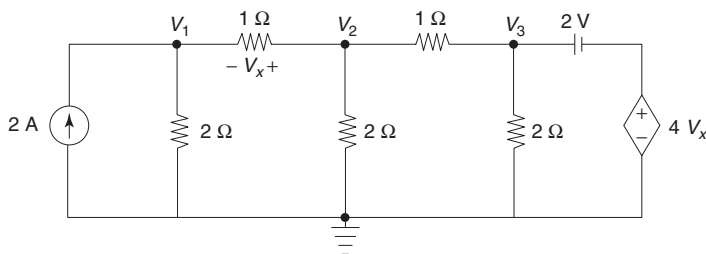

**Fig. 2.49**

**Solution** From Fig. 2.49,

$$V_x = V_2 - V_1 \quad \dots(i)$$

Assume that the currents are moving away from the nodes.

Applying KCL at Node 1,

$$\begin{aligned}2 &= \frac{V_1}{2} + \frac{V_1 - V_2}{1} \\ \left( \frac{1}{2} + 1 \right) V_1 - V_2 &= 2 \\ 1.5V_1 - V_2 &= 2\end{aligned}\quad \dots(ii)$$

Applying KCL at Node 2,

$$\begin{aligned}\frac{V_2 - V_1}{1} + \frac{V_2}{2} + \frac{V_2 - V_3}{1} &= 0 \\ -V_1 + \left(1 + \frac{1}{2} + 1\right)V_2 - V_3 &= 0 \\ -V_1 + 2.5V_2 - V_3 &= 0 \quad \dots(\text{iii})\end{aligned}$$

At Node 3,

$$\begin{aligned}V_3 - 4V_x &= 2 \\ V_3 - 4(V_2 - V_1) &= 2 \\ 4V_1 - 4V_2 + V_3 &= 2 \quad \dots(\text{iv})\end{aligned}$$

Solving Eqs (ii), (iii) and (iv),

$$\begin{aligned}V_1 &= -1.33 \text{ V} \\ V_2 &= -4 \text{ V} \\ V_3 &= -8.67 \text{ V}\end{aligned}$$

### Example 2.34

For the network shown in Fig. 2.50, find the node voltages  $V_1$  and  $V_2$ .

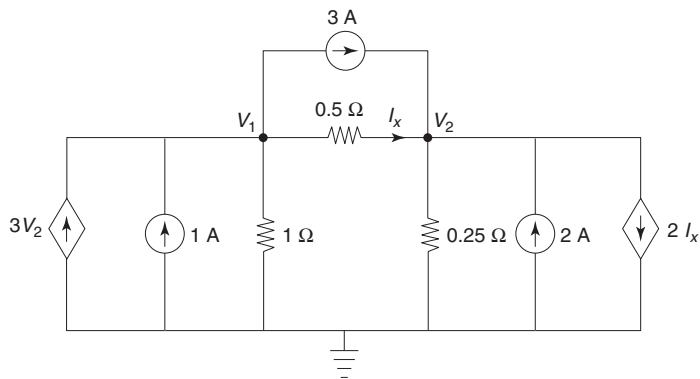


Fig. 2.50

**Solution** From Fig. 2.50,

$$I_x = \frac{V_1 - V_2}{0.5} \quad \dots(\text{i})$$

Assume that the currents are moving away from the nodes.

### 2.32 Circuit Theory and Networks—Analysis and Synthesis

Applying KCL at Node 1,

$$\begin{aligned}
 3V_2 + 1 &= \frac{V_1}{1} + \frac{V_1 - V_2}{0.5} + 3 \\
 \left(1 + \frac{1}{0.5}\right)V_1 - \left(3 + \frac{1}{0.5}\right)V_2 &= -2 \\
 3V_1 - 5V_2 &= -2 \quad \dots(ii)
 \end{aligned}$$

Applying KCL at Node 2,

$$\begin{aligned}
 3 + 2 &= \frac{V_2 - V_1}{0.5} + \frac{V_2}{0.25} + 2I_x \\
 5 &= \frac{V_2 - V_1}{0.5} + \frac{V_2}{0.25} + 2\left(\frac{V_1 - V_2}{0.5}\right) \\
 \left(-\frac{1}{0.5} + \frac{2}{0.5}\right)V_1 + \left(\frac{1}{0.5} + \frac{1}{0.25} - \frac{2}{0.5}\right)V_2 &= 5 \\
 2V_1 + 2V_2 &= 5 \quad \dots(iii)
 \end{aligned}$$

Solving Eqs (ii) and (iii),

$$V_1 = 1.31 \text{ V}$$

$$V_2 = 1.19 \text{ V}$$

**Example 2.35** Find voltages  $V_1$  and  $V_2$  in the network shown in Fig. 2.51.

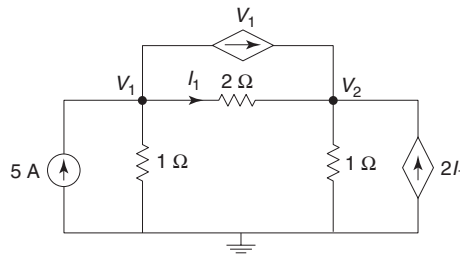


Fig. 2.51

**Solution** From Fig. 2.51,

$$I_1 = \frac{V_1 - V_2}{2} \quad \dots(i)$$

Assume that the currents are moving away from the nodes.

Applying KCL at Node 1,

$$\begin{aligned}
 5 &= \frac{V_1}{1} + \frac{V_1 - V_2}{2} + V_1 \\
 \left(1 + \frac{1}{2} + 1\right)V_1 - \frac{1}{2}V_2 &= 5 \\
 2.5V_1 - 0.5V_2 &= 5 \quad \dots(ii)
 \end{aligned}$$



Applying KCL at Node 2,

$$\frac{V_2 - V_1}{1} + \frac{V_2}{1} = 2I_1 + V_1$$

$$V_2 - V_1 + V_2 = 2\left(\frac{V_1 - V_2}{2}\right) + V_1$$

$$3V_1 = 3V_2$$

$$V_1 = V_2$$

...(iii)

Solving Eqs (ii) and (iii),

$$V_1 = 2.5 \text{ V}$$

$$V_2 = 2.5 \text{ V}$$

### Example 2.36

Find the power supplied by the 10 V source in the network shown in Fig. 2.52.

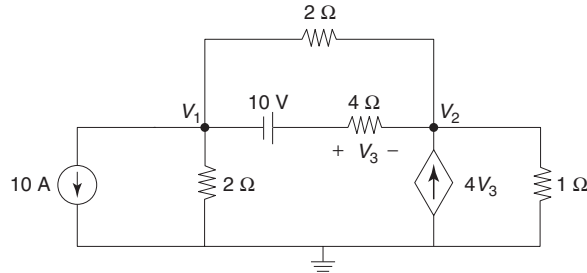


Fig. 2.52

### Solution

From Fig. 2.52,

$$V_3 = V_1 + 10 - V_2$$

...(i)

Assume that the currents are moving away from the nodes.

Applying KCL at Node 1,

$$10 + \frac{V_1}{2} + \frac{V_1 + 10 - V_2}{4} + \frac{V_1 - V_2}{2} = 0$$

$$\left(\frac{1}{2} + \frac{1}{4} + \frac{1}{2}\right)V_1 - \left(\frac{1}{4} + \frac{1}{2}\right)V_2 = -10 - \frac{10}{4}$$

$$1.25V_1 - 0.75V_2 = -12.5$$

...(ii)

Applying KCL at Node 2,

$$\frac{V_2 - 10 - V_1}{4} + \frac{V_2 - V_1}{2} + \frac{V_2}{1} = 4V_3$$

$$\frac{V_2 - 10 - V_1}{4} + \frac{V_2 - V_1}{2} + \frac{V_2}{1} = 4(V_1 + 10 - V_2)$$

### 2.34 Circuit Theory and Networks—Analysis and Synthesis

$$\left(-\frac{1}{4} - \frac{1}{2} - 4\right)V_1 + \left(\frac{1}{4} + \frac{1}{2} + 1 + 4\right)V_2 = \frac{10}{4} + 40$$

$$-4.75V_1 + 5.75V_2 = 42.5 \quad \dots(\text{iii})$$

Solving Eqs (ii) and (iii),

$$V_1 = -11.03 \text{ V}$$

$$V_2 = -1.72 \text{ V}$$

$$I_{10 \text{ V}} = \frac{V_1 + 10 - V_2}{4} = \frac{-11.03 + 10 - (-1.72)}{4} = 0.173 \text{ A}$$

Power supplied by the 10 V source =  $10 \times 0.173 = 1.73 \text{ W}$

**Example 2.37** For the network shown in Fig. 2.53, find voltages  $V_1$  and  $V_2$ .

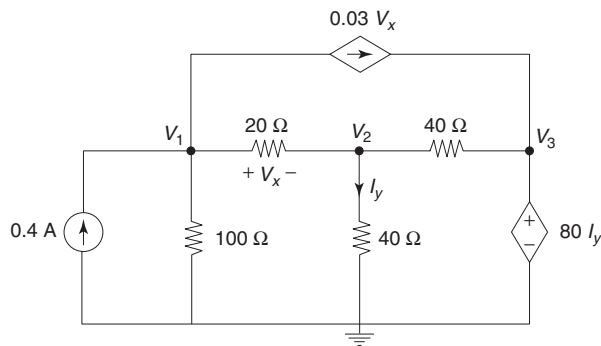


Fig. 2.53

**Solution** From Fig. 2.53,

$$V_x = V_1 - V_2 \quad \dots(\text{i})$$

$$I_y = \frac{V_2}{40} \quad \dots(\text{ii})$$

Assume that the currents are moving away from the nodes.

Applying KCL at Node 1,

$$0.4 = \frac{V_1}{100} + \frac{V_1 - V_2}{20} + 0.03 V_x$$

$$0.4 = \frac{V_1}{100} + \frac{V_1 - V_2}{20} + 0.03(V_1 - V_2)$$

$$\left(\frac{1}{100} + \frac{1}{20} + 0.03\right)V_1 - \left(\frac{1}{20} + 0.03\right)V_2 = 0.4$$

$$0.09V_1 - 0.08V_2 = 0.4 \quad \dots(\text{iii})$$

Applying KCL at Node 2,

$$\begin{aligned}\frac{V_2 - V_1}{20} + \frac{V_2}{40} + \frac{V_2 - V_3}{40} &= 0 \\ -\frac{1}{20} V_1 + \left( \frac{1}{20} + \frac{1}{40} + \frac{1}{40} \right) V_2 - \frac{1}{40} V_3 &= 0 \\ -0.05 V_1 + 0.1 V_2 - 0.025 V_3 &= 0\end{aligned}\quad \dots(\text{iv})$$

For Node 3,

$$\begin{aligned}V_3 &= 80 I_y = 80 \left( \frac{V_2}{40} \right) = 2 V_2 \\ 2 V_2 - V_3 &= 0\end{aligned}\quad \dots(\text{v})$$

Solving Eqs (iii), (iv) and (v),

$$\begin{aligned}V_1 &= 40 \text{ V} \\ V_2 &= 40 \text{ V} \\ V_3 &= 80 \text{ V}\end{aligned}$$

**Example 2.38** Find voltages  $V_a$ ,  $V_b$  and  $V_c$  in the network shown in Fig. 2.54.

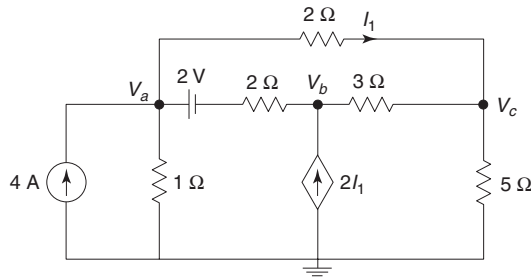


Fig. 2.54

**Solution** From Fig. 2.54,

$$I_1 = \frac{V_a - V_c}{2}$$

Assume that the currents are moving away from the nodes.

Applying KCL at Node  $a$ ,

$$\begin{aligned}4 &= \frac{V_a}{1} + \frac{V_a - V_c}{2} + \frac{V_a - 2 - V_b}{2} \\ \left( 1 + \frac{1}{2} + \frac{1}{2} \right) V_a - \frac{1}{2} V_b - \frac{1}{2} V_c &= 5 \\ 2 V_a - 0.5 V_b - 0.5 V_c &= 5\end{aligned}\quad \dots(\text{i})$$

### 2.36 Circuit Theory and Networks—Analysis and Synthesis

Applying KCL at Node  $b$ ,

$$\frac{V_b + 2 - V_a}{2} + \frac{V_b - V_c}{3} = 2I_1$$

$$\frac{V_b + 2 - V_a}{2} + \frac{V_b - V_c}{3} = 2\left(\frac{V_a - V_c}{2}\right)$$

$$\frac{V_b + 2 - V_a}{2} + \frac{V_b - V_c}{3} = V_a - V_c$$

$$\left(-\frac{1}{2} - 1\right)V_a + \left(\frac{1}{2} + \frac{1}{3}\right)V_b + \left(1 - \frac{1}{3}\right)V_c = -1$$

$$-1.5V_a + 0.83V_b + 0.67V_c = -1 \quad \dots(ii)$$

Applying KCL at Node  $c$ ,

$$\frac{V_c - V_b}{3} + \frac{V_c}{5} = I_1$$

$$\frac{V_c - V_b}{3} + \frac{V_c}{5} = \frac{V_a - V_c}{2}$$

$$-\frac{1}{2}V_a - \frac{1}{3}V_b + \left(\frac{1}{3} + \frac{1}{5} + \frac{1}{2}\right)V_c = 0$$

$$-0.5V_a - 0.33V_b + 1.033V_c = 0 \quad \dots(iii)$$

Solving Eqs (i), (ii), and (iii),

$$V_a = 4.303 \text{ V}$$

$$V_b = 3.88 \text{ V}$$

$$V_c = 3.33 \text{ V}$$

## 2.6 || SUPERNODE ANALYSIS

Nodes that are connected to each other by voltage sources, but not to the reference node by a path of voltage sources, form a *supernode*. A supernode requires one node voltage equation, that is, a KCL equation. The remaining node voltage equations are KVL equations.

**Example 2.39** Determine the current in the  $5 \Omega$  resistor for the network shown in Fig. 2.55.

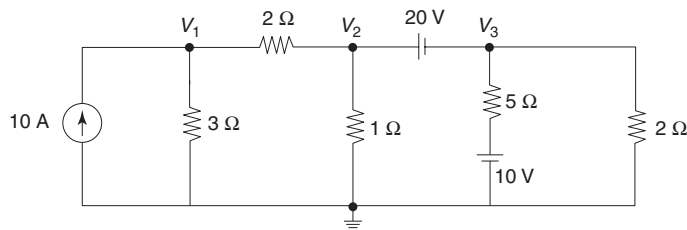


Fig. 2.55

**Solution** Assume that the currents are moving away from the nodes.  
Applying KCL at Node 1,

$$10 = \frac{V_1}{3} + \frac{V_1 - V_2}{2}$$

$$\left(\frac{1}{3} + \frac{1}{2}\right)V_1 - \frac{1}{2}V_2 = 10$$

$$0.83 V_1 - 0.5 V_2 = 10 \quad \dots(i)$$

Nodes 2 and 3 will form a supernode.

Writing voltage equation for the supernode,

$$V_2 - V_3 = 20 \quad \dots(ii)$$

Applying KCL at the supernode,

$$\frac{V_2 - V_1}{2} + \frac{V_2}{1} + \frac{V_3 - 10}{5} + \frac{V_3}{2} = 0$$

$$-\frac{1}{2}V_1 + \left(\frac{1}{2} + 1\right)V_2 + \left(\frac{1}{5} + \frac{1}{2}\right)V_3 = 2$$

$$-0.5 V_1 + 1.5 V_2 + 0.7 V_3 = 2 \quad \dots(iii)$$

Solving Eqs (i), (ii) and (iii),

$$V_1 = 19.04 \text{ V}$$

$$V_2 = 11.6 \text{ V}$$

$$V_3 = -8.4 \text{ V}$$

$$I_{5\Omega} = \frac{V_3 - 10}{5} = \frac{-8.4 - 10}{5} = -3.68 \text{ A}$$

### Example 2.40

Find the power delivered by the 5 A current source in the network shown in Fig. 2.56.

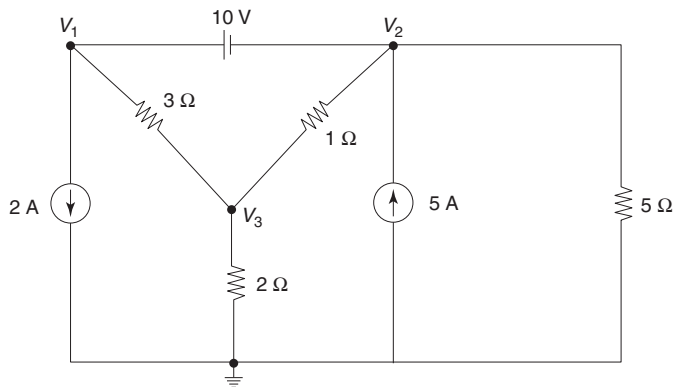


Fig. 2.56

### 2.38 Circuit Theory and Networks—Analysis and Synthesis

**Solution** Assume that the currents are moving away from the nodes.

Nodes 1 and 2 will form a supernode.

Writing voltage equation for the supernode,

$$V_1 - V_2 = 10 \quad \dots(i)$$

Applying KCL at the supernode,

$$\begin{aligned} 2 + \frac{V_1 - V_3}{3} + \frac{V_2}{5} + \frac{V_2 - V_3}{1} &= 5 \\ \frac{1}{3} V_1 + \left(\frac{1}{5} + 1\right) V_2 - \left(\frac{1}{3} + 1\right) V_3 &= 3 \\ 0.33 V_1 + 1.2 V_2 - 1.33 V_3 &= 3 \quad \dots(ii) \end{aligned}$$

Applying KCL at Node 3,

$$\begin{aligned} \frac{V_3 - V_1}{3} + \frac{V_3 - V_2}{1} + \frac{V_3}{2} &= 0 \\ -\frac{1}{3} V_1 - V_2 + \left(\frac{1}{3} + 1 + \frac{1}{2}\right) V_3 &= 0 \\ -0.33 V_1 - V_2 + 1.83 V_3 &= 0 \quad \dots(iii) \end{aligned}$$

Solving Eqs (i), (ii) and (iii),


$$V_1 = 13.72 \text{ V}$$

$$V_2 = 3.72 \text{ V}$$

$$V_3 = 4.51 \text{ V}$$

Power delivered by the 5 A source =  $5 V_2 = 5 \times 3.72 = 18.6 \text{ W}$

**Example 2.41** In the network of Fig. 2.57, find the node voltages  $V_1$ ,  $V_2$  and  $V_3$ .

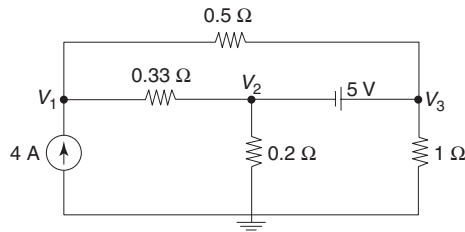

**Fig. 2.57**

**Solution** Assume that the currents are moving away from the nodes.

Applying KCL at Node 1,

$$\begin{aligned} 4 &= \frac{V_1 - V_2}{0.33} + \frac{V_1 - V_3}{0.5} \\ \left(\frac{1}{0.33} + \frac{1}{0.5}\right) V_1 - \frac{1}{0.33} V_2 - \frac{1}{0.5} V_3 &= 4 \\ 5.03 V_1 - 3.03 V_2 - 2 V_3 &= 4 \quad \dots(i) \end{aligned}$$

Nodes 2 and 3 will form a supernode.

Writing voltage equation for the supernode,

$$V_3 - V_2 = 5 \quad \dots(ii)$$

Applying KCL at the supernode,

$$\begin{aligned} \frac{V_2 - V_1}{0.33} + \frac{V_2}{0.2} + \frac{V_3}{1} + \frac{V_3 - V_1}{0.5} &= 0 \\ \left(-\frac{1}{0.33} - \frac{1}{0.5}\right)V_1 + \left(\frac{1}{0.33} + \frac{1}{0.2}\right)V_2 + \left(1 + \frac{1}{0.5}\right)V_3 &= 0 \\ -5.03V_1 + 8.03V_2 + 3V_3 &= 0 \quad \dots(iii) \end{aligned}$$

Solving Eqs (i), (ii) and (iii),

$$\begin{aligned} V_1 &= 2.62 \text{ V} \\ V_2 &= -0.17 \text{ V} \\ V_3 &= 4.83 \text{ V} \end{aligned}$$

## EXAMPLES WITH DEPENDENT SOURCES

**Example 2.42** For the network shown in Fig. 2.58, determine the voltage  $V_x$ .

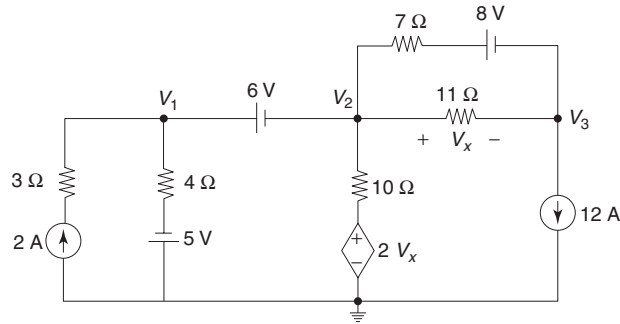


Fig. 2.58

**Solution** From Fig. 2.58,

$$V_x = V_2 - V_3$$

Assume that the currents are moving away from the nodes.

Node 1 and 2 will form a supernode.

Writing voltage equations for the supernode,

$$V_1 - V_2 = 6 \quad \dots(i)$$

Applying KCL at the supernode,

$$\begin{aligned} 2 &= \frac{V_1 + 5}{4} + \frac{V_2 - 2V_x}{10} + \frac{V_2 - 8 - V_3}{7} + \frac{V_2 - V_3}{11} \\ 2 &= \frac{V_1 + 5}{4} + \frac{V_2 - 2(V_2 - V_3)}{10} + \frac{V_2 - 8 - V_3}{7} + \frac{V_2 - V_3}{11} \end{aligned}$$

## 2.40 Circuit Theory and Networks—Analysis and Synthesis

$$\frac{1}{4} V_1 + \left( \frac{1}{10} - \frac{1}{5} + \frac{1}{7} + \frac{1}{11} \right) V_2 + \left( \frac{1}{5} - \frac{1}{7} - \frac{1}{11} \right) V_3 = 2 - \frac{5}{4} + \frac{8}{7}$$

$$0.25 V_1 + 0.133 V_2 - 0.033 V_3 = 1.89 \quad \dots(\text{ii})$$

Applying KCL at Node 3,

$$\frac{V_3 - V_2}{11} + \frac{V_3 + 8 - V_2}{7} + 12 = 0$$

$$\left( -\frac{1}{11} - \frac{1}{7} \right) V_2 + \left( \frac{1}{11} + \frac{1}{7} \right) V_3 = -12 - \frac{8}{7}$$

$$-0.233 V_2 + 0.233 V_3 = -13.14 \quad \dots(\text{iii})$$

Solving Eqs (i), (ii) and (iii),

$$V_1 = 1.8 \text{ V}$$

$$V_2 = -4.2 \text{ V}$$

$$V_3 = -60.6 \text{ V}$$

### Example 2.43

Find the node voltages in the network shown in Fig. 2.59.

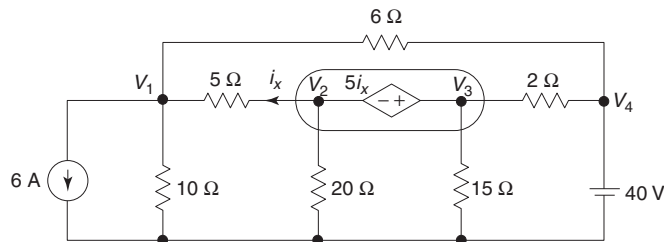


Fig. 2.59

**Solution** From Fig. 2.59,

$$I_x = \frac{V_2 - V_1}{5} \quad \dots(\text{i})$$

For Node 4,

$$V_4 = 40 \quad \dots(\text{ii})$$

Applying KCL at Node 1,

$$6 + \frac{V_1}{10} + \frac{V_1 - V_2}{5} + \frac{V_1 - V_4}{6} = 0$$

$$6 + \frac{V_1}{10} + \frac{V_1 - V_2}{5} + \frac{V_1 - 40}{6} = 0$$

$$\left( \frac{1}{10} + \frac{1}{5} + \frac{1}{6} \right) V_1 - \frac{1}{5} V_2 = \frac{40}{6} - 6$$

$$\frac{7}{15} V_1 - \frac{1}{5} V_2 = \frac{2}{3} \quad \dots(\text{iii})$$



Nodes 2 and 3 will form a supernode,  
Writing voltage equation for the supernode,

$$V_3 - V_2 = 5 I_x = 5 \left( \frac{V_2 - V_1}{5} \right) = V_2 - V_1$$

$$V_1 - 2V_2 + V_3 = 0 \quad \dots(\text{iv})$$

Applying KCL to the supernode,

$$\frac{V_2 - V_1}{5} + \frac{V_2}{20} + \frac{V_3}{15} + \frac{V_3 - V_4}{2} = 0$$

$$\frac{V_2 - V_1}{5} + \frac{V_2}{20} + \frac{V_3}{15} + \frac{V_3 - 40}{2} = 0$$

$$-\frac{1}{5} V_1 + \left( \frac{1}{5} + \frac{1}{20} \right) V_2 + \left( \frac{1}{15} + \frac{1}{2} \right) V_3 = 20$$

$$-\frac{1}{5} V_1 + \frac{1}{4} V_2 + \frac{17}{30} V_3 = 20 \quad \dots(\text{v})$$

Solving Eqs (iii), (iv) and (v),


$$V_1 = 10 \text{ V}$$

$$V_2 = 20 \text{ V}$$

$$V_3 = 30 \text{ V}$$

$$V_4 = 40 \text{ V}$$

**Example 2.44** Find the node voltages in the network shown in Fig. 2.60.

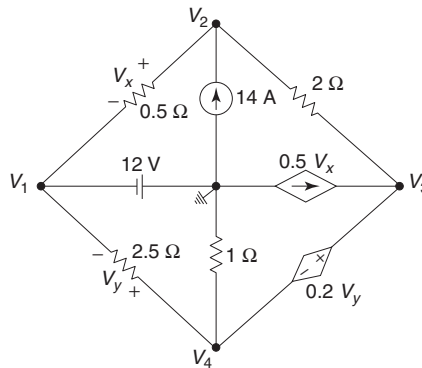

**Fig. 2.60**

**Solution** Selecting the central node as reference node,

$$V_1 = -12 \text{ V} \quad \dots(\text{i})$$

### 2.42 Circuit Theory and Networks—Analysis and Synthesis

Applying KCL at Node 2,

$$\begin{aligned}\frac{V_2 - V_1}{0.5} + \frac{V_2 - V_3}{2} &= 14 \\ -\frac{1}{0.5} V_1 + \left(\frac{1}{0.5} + \frac{1}{2}\right) V_2 - \frac{1}{2} V_3 &= 14 \\ -2 V_1 + 2.5 V_2 - 0.5 V_3 &= 14\end{aligned}\quad \dots(\text{ii})$$

Nodes 3 and 4 will form a supernode,

Writing voltage equation for the supernode,

$$\begin{aligned}V_3 - V_4 &= 0.2 V_y = 0.2 (V_4 - V_1) \\ 0.2 V_1 + V_3 - 1.2 V_4 &= 0\end{aligned}\quad \dots(\text{iii})$$

Applying KCL to the supernode,

$$\begin{aligned}\frac{V_3 - V_2}{2} - 0.5 V_x + \frac{V_4}{1} + \frac{V_4 - V_1}{2.5} &= 0 \\ \frac{V_3 - V_2}{2} - 0.5 (V_2 - V_1) + V_4 + \frac{V_4 - V_1}{2.5} &= 0 \\ \left(0.5 - \frac{1}{2.5}\right) V_1 - \left(\frac{1}{2} + 0.5\right) V_2 + \frac{1}{2} V_3 + \left(1 + \frac{1}{2.5}\right) V_4 &= 0 \\ 0.1 V_1 - V_2 + 0.5 V_3 + 1.4 V_4 &= 0\end{aligned}\quad \dots(\text{iv})$$

Solving Eqs (i), (ii), (iii) and (iv),

$$\begin{aligned}V_1 &= -12 \text{ V} \\ V_2 &= -4 \text{ V} \\ V_3 &= 0 \\ V_4 &= -2 \text{ V}\end{aligned}$$

## 2.7 || SUPERPOSITION THEOREM


It states that ‘in a linear network containing more than one independent source and dependent source, the resultant current in any element is the algebraic sum of the currents that would be produced by each independent source acting alone, all the other independent sources being represented meanwhile by their respective internal resistances.’

The independent voltage sources are represented by their internal resistances if given or simply with zero resistances, i.e., short circuits if internal resistances are not mentioned. The independent current sources are represented by infinite resistances, i.e., open circuits.

The dependent sources are not sources but dissipative components—hence they are active at all times. A dependent source has zero value only when its control voltage or current is zero.

A linear network is one whose parameters are constant, i.e., they do not change with voltage and current.


**Explanation** Consider the network shown in Fig. 2.61. Suppose we have to find current  $I_4$  through resistor  $R_4$ .

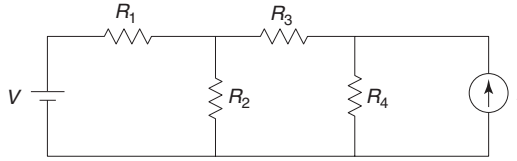


**Fig. 2.61** Network to illustrate superposition theorem

The current flowing through resistor  $R_4$  due to constant voltage source  $V$  is found to be say  $I'_4$  (with proper direction), representing constant current source with infinite resistance, i.e., open circuit.

The current flowing through resistor  $R_4$  due to constant current source  $I$  is found to be say  $I''_4$  (with proper direction), representing the constant voltage source with zero resistance or short circuit.

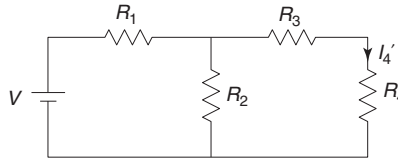

**Fig. 2.62** When voltage source  $V$  is acting alone

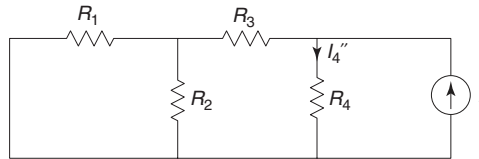

**Fig. 2.63** When current source  $I$  is acting alone

The resultant current  $I_4$  through resistor  $R_4$  is found by superposition theorem.

$$I_4 = I'_4 + I''_4$$

### Steps to be followed in Superposition Theorem

1. Find the current through the resistance when only one independent source is acting, replacing all other independent sources by respective internal resistances.
2. Find the current through the resistance for each of the independent sources.
3. Find the resultant current through the resistance by the superposition theorem considering magnitude and direction of each current.

## 2.44 Circuit Theory and Networks—Analysis and Synthesis

### Example 2.45

Find the current through the  $4\ \Omega$  resistor in Fig. 2.64.

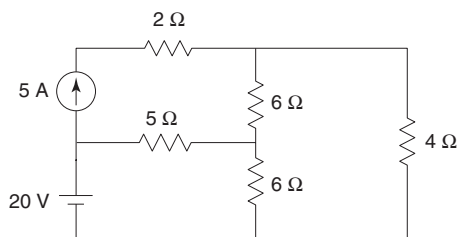


Fig. 2.64

### Solution

**Step I** When the 5 A source is acting alone (Fig. 2.65)

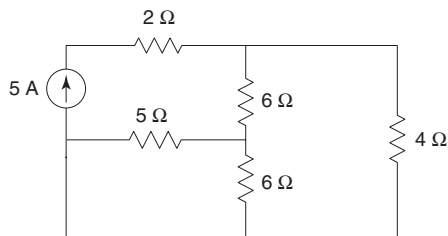


Fig. 2.65

By series-parallel reduction technique (Fig. 2.66),


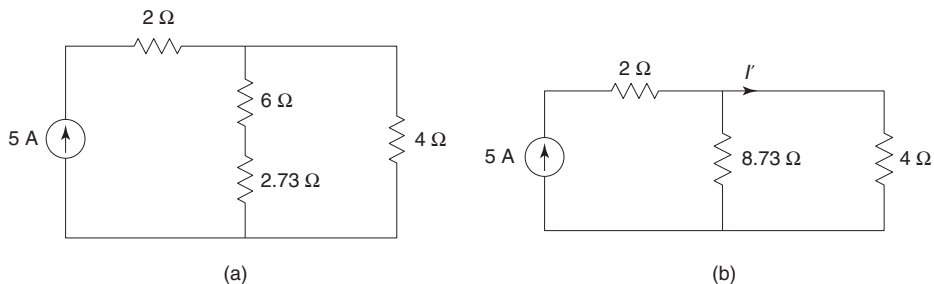


Fig. 2.66


$$I' = 5 \times \frac{8.73}{8.73 + 4} = 3.43\text{ A}(\downarrow)$$

**Step II** When the 20 V source is acting alone (Fig. 2.67)

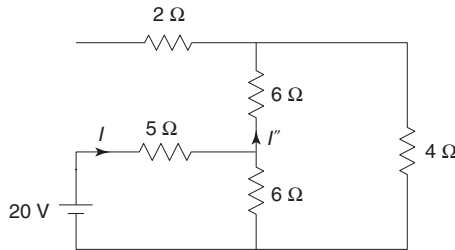

**Fig. 2.67**

By series-parallel reduction technique (Fig. 2.68),

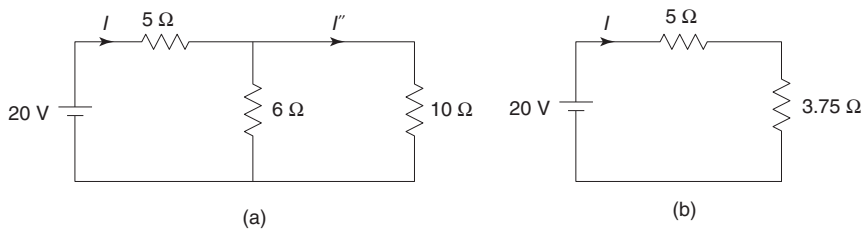

**Fig. 2.68**

$$I = \frac{20}{5 + 3.75} = 2.29 \text{ A}$$


From Fig. 2.68(a), by current-division rule,

$$I'' = 2.29 \times \frac{6}{6 + 10} = 0.86 \text{ A} (\downarrow)$$

**Step III** By superposition theorem,

$$I = I' + I'' = 3.43 + 0.86 = 4.29 \text{ A} (\downarrow)$$

**Example 2.46** Find the current through the 3 Ω resistor in Fig. 2.69.

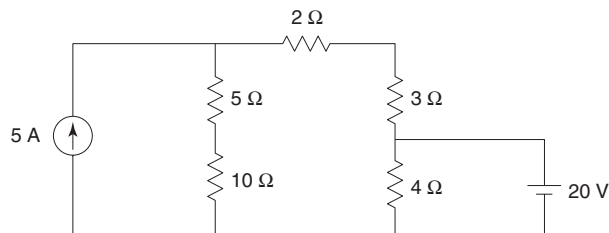


**Fig. 2.69**

## 2.46 Circuit Theory and Networks—Analysis and Synthesis

### Solution


**Step I** When the 5 A source is acting alone (Fig. 2.70)

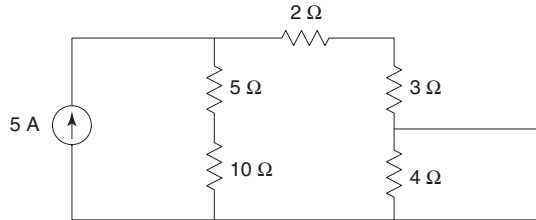

**Fig. 2.70**


By series-parallel reduction technique (Fig. 2.71),

$$I' = 5 \times \frac{15}{15 + 2 + 3} = 3.75 \text{ A} (\downarrow)$$

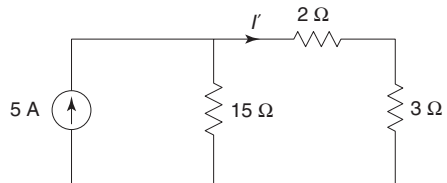


**Fig. 2.71**

**Step II** When the 20 V source is acting alone (Fig. 2.72)

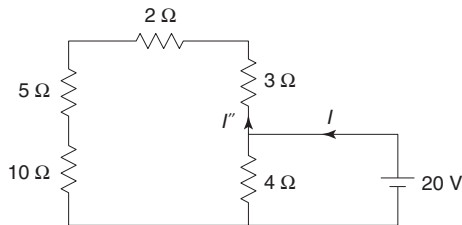

**Fig. 2.72**

By series-parallel reduction technique (Fig. 2.73),

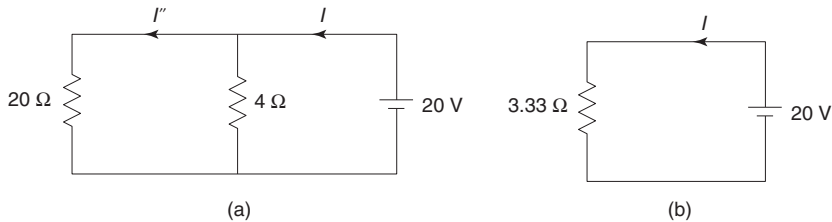

**Fig. 2.73**


$$I = \frac{20}{3.33} = 6 \text{ A}$$

From Fig. 2.73(a), by current-division rule,


$$I'' = 6 \times \frac{4}{20 + 4} = 1 \text{ A} (\uparrow) = -1 \text{ A} (\downarrow)$$

**Step III** By superposition theorem,

$$I = I' + I'' = 3.75 - 1 = 2.75 \text{ A} (\downarrow)$$


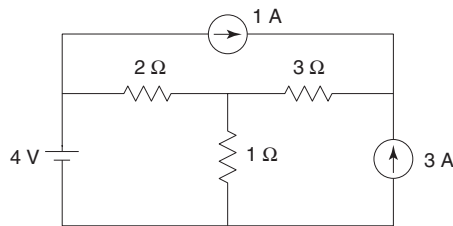
**Example 2.47**Find the current in the  $1\ \Omega$  resistors in Fig. 2.74.**Fig. 2.74****Solution****Step I** When the 4 V source is acting alone (Fig. 2.75)

$$I' = \frac{4}{2+1} = 1.33\text{ A (}\downarrow\text{)}$$

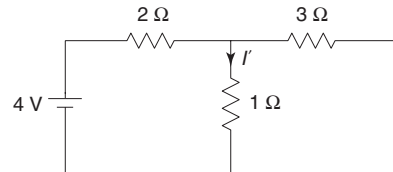**Fig. 2.75****Step II** When the 3 A source is acting alone (Fig. 2.76)

By current-division rule,


$$I'' = 3 \times \frac{2}{1+2} = 2\text{ A (}\downarrow\text{)}$$

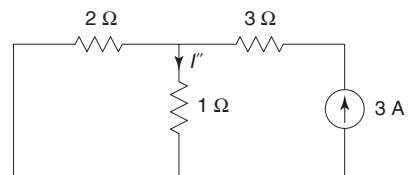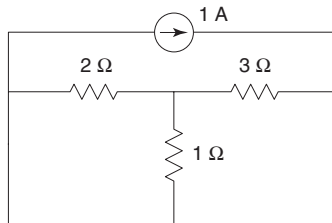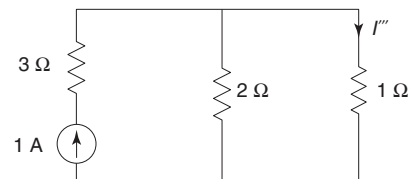**Fig. 2.76****Step III** When the 1 A source is acting alone (Fig. 2.77)**Fig. 2.77**

Redrawing the network (Fig. 2.78),

By current-division rule,

$$I''' = 1 \times \frac{2}{2+1} = 0.66\text{ A (}\downarrow\text{)}$$

**Fig. 2.78****Step IV** By superposition theorem,

$$I = I' + I'' + I''' = 1.33 + 2 + 0.66 = 4\text{ A (}\downarrow\text{)}$$

## 2.48 Circuit Theory and Networks—Analysis and Synthesis

**Example 2.48** Find the voltage  $V_{AB}$  in Fig. 2.79.

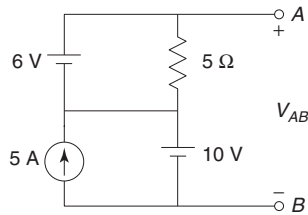


Fig. 2.79

### Solution

**Step I** When the 6 V source is acting alone (Fig. 2.80)

$$V'_{AB} = 6 \text{ V}$$

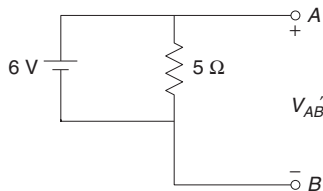


Fig. 2.80

**Step II** When the 10 V source is acting alone (Fig. 2.81)  
Since the resistor of  $5 \Omega$  is shorted, the voltage across it is zero.

$$V''_{AB} = 10 \text{ V}$$

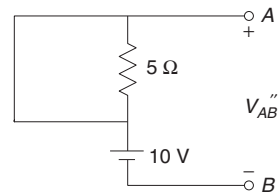


Fig. 2.81

**Step III** When the 5 A source is acting alone (Fig. 2.82)  
Due to short circuit in both the parts,

$$V'''_{AB} = 0$$

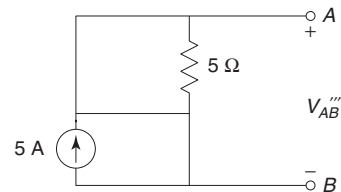


Fig. 2.82

**Step IV** By superposition theorem,

$$V_{AB} = V'_{AB} + V''_{AB} + V'''_{AB} = 6 + 10 + 0 = 16 \text{ V}$$

## EXAMPLES WITH DEPENDENT SOURCES

**Example 2.49** Find the current through the  $6 \Omega$  resistor in Fig. 2.83.

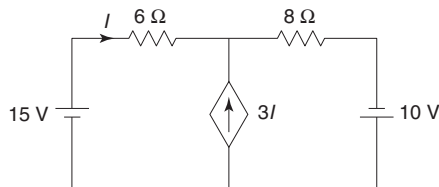


Fig. 2.83



**Solution**

**Step I** When the 15 V source is acting alone (Fig. 2.84)  
From Fig. 2.84,

$$I' = I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1 = 3I' = 3I_1$$

$$4I_1 - I_2 = 0 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$15 - 6I_1 - 8I_2 = 0$$

$$6I_1 + 8I_2 = 15$$

... (iii)

Solving Eqs (ii) and (iii),

$$I_1 = 0.39 \text{ A}$$

$$I_2 = 1.57 \text{ A}$$

$$I' = I_1 = 0.39 \text{ A } (\rightarrow)$$

**Step II** When the 10 V source is acting alone (Fig. 2.85)

From Fig. 2.85,

$$I'' = I_1$$

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1 = 3I'' = 3I_1$$

$$4I_1 - I_2 = 0$$

Applying KVL to the outer path of the supermesh,

$$-6I_1 - 8I_2 + 10 = 0$$

$$6I_1 + 8I_2 = 10$$

..... (iii)

Solving Eqs (ii) and (iii),


$$I_1 = 0.26 \text{ A}$$

$$I_2 = 1.05 \text{ A}$$


$$I'' = I_1 = 0.26 \text{ A } (\rightarrow)$$

**Step III** By superposition theorem,

$$I = I' + I'' = 0.39 + 0.26 = 0.65 \text{ A } (\rightarrow)$$

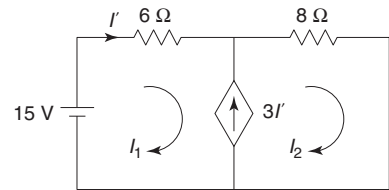


**Fig. 2.84**

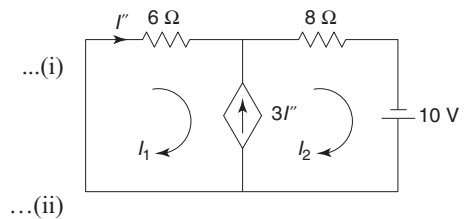

**Fig. 2.85**

**Example 2.50** Find the current  $I_x$  in Fig. 2.86.

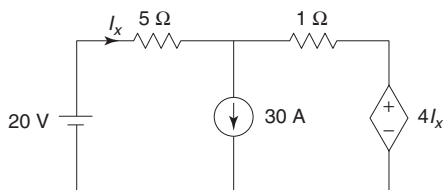

**Fig. 2.86**

## 2.50 Circuit Theory and Networks—Analysis and Synthesis

### Solution

**Step I** When the 30 A source is acting alone (Fig. 2.87)

From Fig. 2.87,

$$I'_x = I_1$$

Meshe 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_1 - I_2 = 30$$

Applying KVL to the outer path of the supermesh,

$$-5I_1 - 1I_2 - 4I'_x = 0$$

$$-5I_1 - I_2 - 4I_1 = 0$$

$$9I_1 + I_2 = 0$$

...(iii)

Solving Eqs (ii) and (iii),

$$I_1 = 3 \text{ A}$$

$$I_2 = -27 \text{ A}$$

$$I'_x = I_1 = 3 \text{ A} (\rightarrow)$$

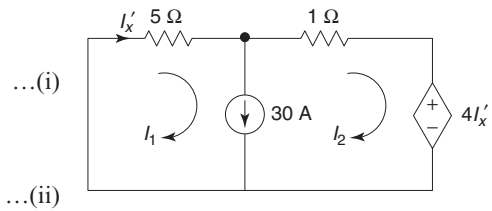


Fig. 2.87

**Step II** When the 20 V source is acting alone (Fig. 2.88)

Applying KVL to the mesh,

$$20 - 5I''_x - 1I''_x - 4I''_x = 0$$

$$I''_x = 2 \text{ A} (\rightarrow)$$

**Step III** By superposition theorem,

$$I_x = I'_x + I''_x = 3 + 2 = 5 \text{ A} (\rightarrow)$$

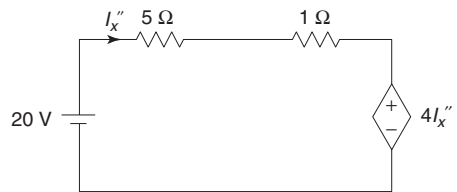


Fig. 2.88

**Example 2.51** Find the current  $I_p$  in Fig. 2.89.

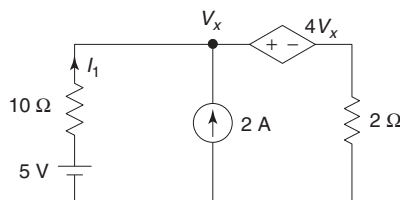


Fig. 2.89

### Solution

**Step I** When the 5 V source is acting alone (Fig. 2.90)

From Fig. 2.90,

$$V_x = 5 - 10I'_1$$

Applying KVL to the mesh,

$$5 - 10I'_1 - 4V_x - 2I'_1 = 0$$

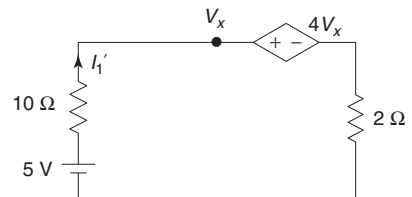


Fig. 2.90

$$\begin{aligned}
 5 - 10I_1' - 4(5 - 10I_1') - 2I_1' &= 0 \\
 5 - 10I_1' - 20 + 40I_1' - 2I_1' &= 0 \\
 I_1' &= \frac{15}{28} = 0.54 \text{ A} (\uparrow)
 \end{aligned}$$

**Step II** When the 2 A source is acting alone (Fig. 2.91)

From Fig. 2.91,

$$V_x = -10I_1' \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1' = 2 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,


$$\begin{aligned}
 -10I_1' - 4V_x - 2I_2 &= 0 \\
 -10I_1' - 4(-10I_1') - 2I_2 &= 0 \\
 30I_1' - 2I_2 &= 0 \quad \dots(iii)
 \end{aligned}$$

Solving Eqs (ii) and (iii),

$$\begin{aligned}
 I_1 &= 0.14 \text{ A} (\uparrow) \\
 I_2 &= 2.14 \text{ A}
 \end{aligned}$$

**Step III** By superposition theorem,


$$I_1 = I_1' + I_1'' = 0.54 + 0.14 = 0.68 \text{ A} (\uparrow)$$

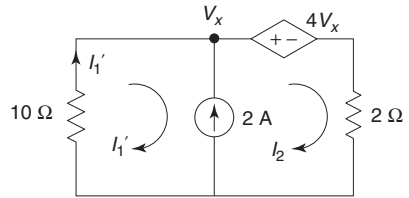

**Fig. 2.91**

### Example 2.52

Determine the current through the  $10 \Omega$  resistor in Fig. 2.92.

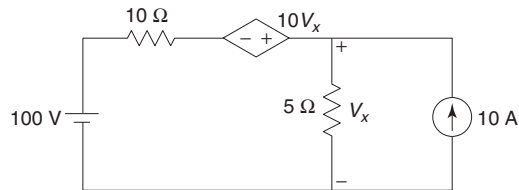

**Fig. 2.92**

### Solution


**Step I** When the 100 V source is acting alone (Fig. 2.93)

From Fig. 2.93,

$$V_x = 5I'$$

Applying KVL to the mesh,

$$\begin{aligned}
 100 - 10I' + 10V_x - 5I' &= 0 \\
 100 - 10I' + 10(5I') - 5I' &= 0
 \end{aligned}$$

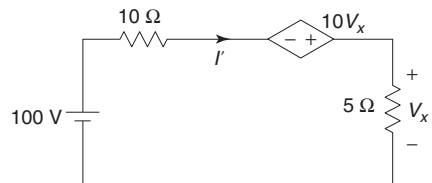

**Fig. 2.93**

## 2.52 Circuit Theory and Networks—Analysis and Synthesis

$$I' = -2.86 \text{ A } (\rightarrow)$$

**Step II** When the 10 A source is acting alone (Fig. 2.94)

From Fig. 2.94,

$$V_x = 5(I_1 - I_2) \quad \dots(i)$$

Applying KVL to Mesh 1,

$$\begin{aligned} -10I_1 + 10V_x - 5(I_1 - I_2) &= 0 \\ -10I_1 + 10\{5(I_1 - I_2)\} - 5(I_1 - I_2) &= 0 \\ 35I_1 - 45I_2 &= 0 \quad \dots(ii) \end{aligned}$$

For Mesh 2,

$$I_2 = -10 \quad \dots(iii)$$

Solving Eqs (ii) and (iii),

$$I_1 = -12.86 \text{ A}$$

$$I_2 = -10 \text{ A}$$

$$I'' = I_1 = -12.86 \text{ A } (\rightarrow)$$

**Step III** By superposition theorem,

$$I = I' + I'' = -2.86 - 12.86 = -15.72 \text{ A } (\rightarrow)$$

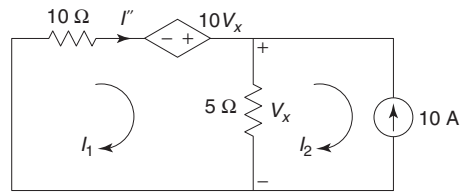


Fig. 2.94

**Example 2.53** Find the current  $I$  in the network of Fig. 2.95.

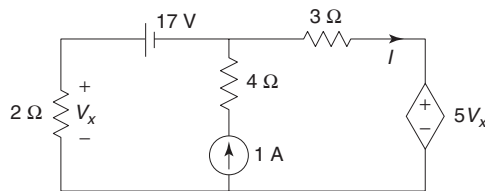


Fig. 2.95

**Solution**

**Step I** When the 17 V source is acting alone (Fig. 2.96)

From Fig. 2.96,

$$V_x = -2I'$$

Applying KVL to the mesh,

$$\begin{aligned} -2I' - 17 - 3I' - 5V_x &= 0 \\ -2I' - 17 - 3I' - 5(-2I') &= 0 \\ I' &= 3.4 \text{ A } (\rightarrow) \end{aligned}$$

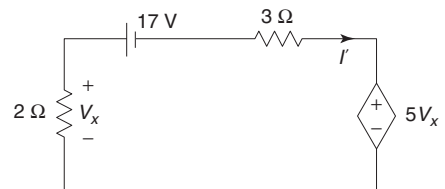


Fig. 2.96

**Step II** When the 1 A source is acting alone (Fig. 2.97)

From Fig. 2.97,

$$V_x = -2I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1 = 1 \quad \dots(ii)$$

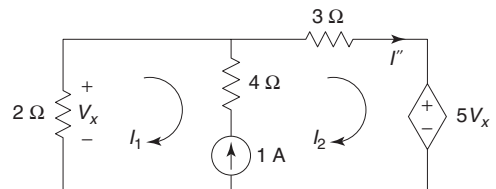


Fig. 2.97

Applying KVL to the outer path of the supermesh,

$$\begin{aligned} -2I_1 - 3I_2 - 5V_x &= 0 \\ -2I_1 - 3I_2 - 5(-2I_1) &= 0 \\ 8I_1 - 3I_2 &= 0 \end{aligned} \quad \dots(\text{iii})$$

Solving Eqs (ii) and (iii),

$$\begin{aligned} I_1 &= 0.6 \text{ A} \\ I_2 &= 1.6 \text{ A} \\ I'' = I_2 &= 1.6 \text{ A} (\rightarrow) \end{aligned}$$

**Step III** By superposition theorem,

$$I = I' + I'' = 3.4 + 1.6 = 5 \text{ A} (\rightarrow)$$

### Example 2.54

Find the voltage  $V_1$  in Fig. 2.98.

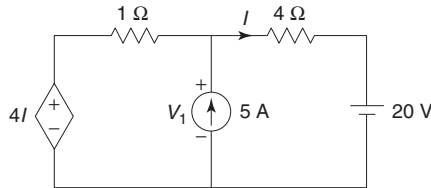


Fig. 2.98

### Solution

**Step I** When the 5 A source is acting alone (Fig. 2.99)

From Fig. 2.99,

$$I = \frac{V_1'}{4}$$

Applying KCL at Node 1,

$$\frac{V_1' - 4I}{1} + \frac{V_1'}{4} = 5$$

$$V_1' - 4\left(\frac{V_1'}{4}\right) + \frac{V_1'}{4} = 5$$

$$V_1' = 20 \text{ V}$$

**Step II** When the 20 V source is acting alone (Fig. 2.100)

Applying KVL to the mesh,

$$4I - I - 4I - 20 = 0$$

$$I = -20 \text{ A}$$

$$V_1'' = 4I - 1(I) = 3I = 3(-20) = -60 \text{ V}$$

**Step III** By superposition theorem,

$$V_1 = V_1' + V_1'' = 20 - 60 = -40 \text{ V}$$

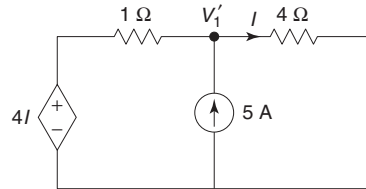


Fig. 2.99

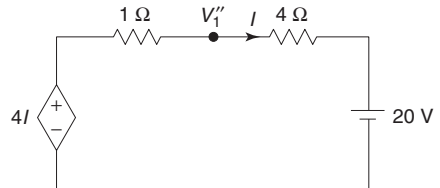


Fig. 2.100

**Example 2.55** Find the current in the  $6\ \Omega$  resistor in Fig. 2.101.

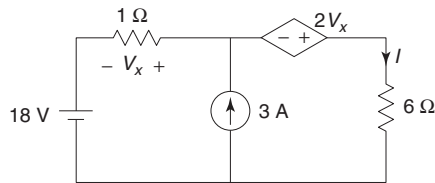


Fig. 2.101

**Solution**

**Step I** When the 18 V source is acting alone (Fig. 2.102)

From Fig. 2.102,

$$V_x = -I'$$

Applying KVL to the mesh,

$$18 - I' + 2V_x - 6I' = 0$$

$$18 - I' - 2I' - 6I' = 0$$

$$I' = 2\text{ A (}\downarrow\text{)}$$

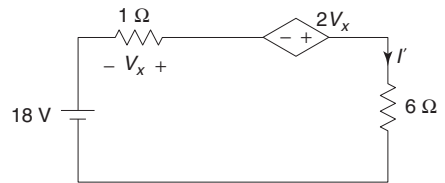


Fig. 2.102

**Step II** When the 3 A source is acting alone (Fig. 2.103)

From Fig. 2.103,

$$V_x = -1 I_1 = -I_1 \quad \dots(\text{i})$$

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1 = 3 \quad \dots(\text{ii})$$

Applying KVL to the outerpath of the supermesh,

$$-1I_1 + 2V_x - 6I_2 = 0$$

$$-I_1 + 2(-I_1) - 6I_2 = 0$$

$$3I_1 + 6I_2 = 0 \quad \dots(\text{iii})$$

Solving Eqs (ii) and (iii),

$$I_1 = -2\text{ A}$$

$$I_2 = 1\text{ A}$$

$$I'' = I_2 = 1\text{ A (}\downarrow\text{)}$$

**Step III** By superposition theorem,

$$I_{6\ \Omega} = I' + I'' = 2 + 1 = 3\text{ A (}\downarrow\text{)}$$

**Example 2.56** Find the current  $I_y$  in Fig. 2.104.

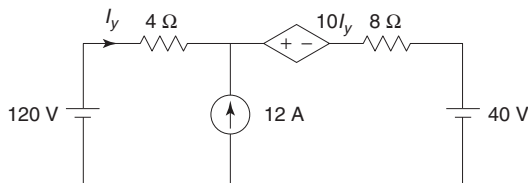


Fig. 2.104

**Solution****Step I** When the 120 V source is acting alone (Fig. 2.105)

Applying KVL to the mesh,

$$120 - 4I_y' - 10I_y' - 8I_y' = 0$$

$$I_y' = 5.45 \text{ A } (\rightarrow)$$

**Step II** When the 12 A source is acting alone (Fig. 2.106)

From Fig. 2.106,

$$I_y'' = I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1 = 12 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$-4I_1 - 10I_y'' - 8I_2 = 0$$

$$-4I_1 - 10I_1 - 8I_2 = 0$$

$$14I_1 + 8I_2 = 0$$

... (iii)

Solving Eqs (ii) and (iii),

$$I_1 = -4.36 \text{ A}$$

$$I_2 = 7.64 \text{ A}$$

$$I_y'' = I_1 = -4.36 \text{ A } (\rightarrow)$$

**Step III** When the 40 V source is acting alone (Fig. 2.107)





Applying KVL to the mesh,

$$-4I_y''' - 10I_y''' - 8I_y''' - 40 = 0$$

$$I_y''' = -\frac{40}{22} = -1.82 \text{ A } (\rightarrow)$$

**Step IV** By superposition theorem,

$$I_y = I_y' + I_y'' + I_y''' = 5.45 \\ -4.36 - 1.82 = -0.73 \text{ A } (\rightarrow)$$

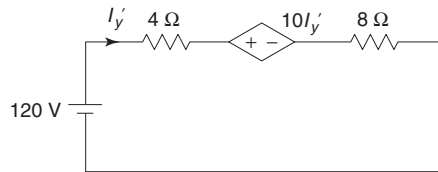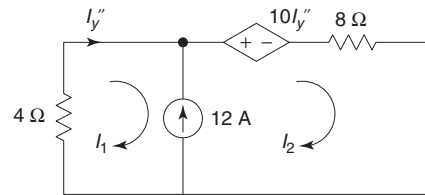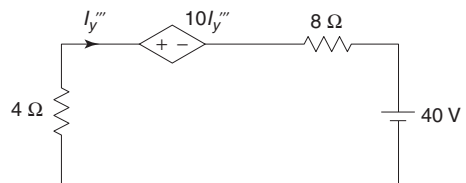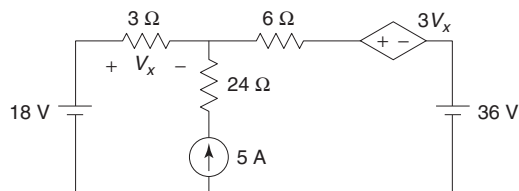**Fig. 2.105****Fig. 2.106****Fig. 2.107****Example 2.57**Find the voltage  $V_x$  in Fig. 2.108.**Fig. 2.108**

## 2.56 Circuit Theory and Networks—Analysis and Synthesis

### Solution

**Step I** When the 18 V source is acting alone (Fig. 2.109)

From Fig. 2.109,

$$V'_x = 3I$$

Applying KVL to the mesh,

$$18 - 3I - 6I - 3V'_x = 0$$

$$18 - 3I - 6I - 3(3I) = 0$$

$$I = 1 \text{ A}$$

$$V'_x = 3 \text{ V}$$

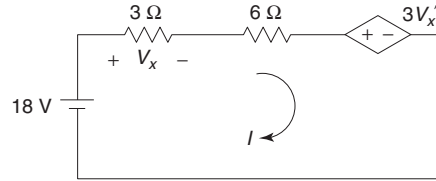


Fig. 2.109

**Step II** When the 5 A source is acting alone (Fig. 2.110)

From Fig. 2.110,

$$V''_x = -3I_1$$

Mesher 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1 = 5$$

Applying KVL to the outer path of the supermesh,

$$-3I_1 - 6I_2 - 3V''_x = 0$$

$$-3I_1 - 6I_2 - 3(3I_1) = 0$$

$$12I_1 + 6I_2 = 0$$

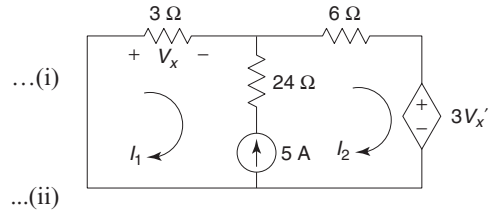


Fig. 2.110

Solving Eqs (ii) and (iii),

$$I_1 = -1.67 \text{ A}$$

$$I_2 = 3.33 \text{ A}$$

$$V''_x = 3I_1 = 3(-1.67) = -5 \text{ V}$$

**Step III** When the 36 V source is acting alone (Fig. 2.111)

From Fig. 2.111,

$$V'''_x = -3I$$

Applying KVL to the mesh,

$$36 + 3V'''_x - 6I - 3I = 0$$

$$36 + 3V'''_x - 6\left(\frac{-V'''_x}{3}\right) - 3\left(\frac{-V'''_x}{3}\right) = 0$$

$$36 + 3V'''_x + 2V'''_x + V'''_x = 0$$

$$V'''_x = -6 \text{ V}$$


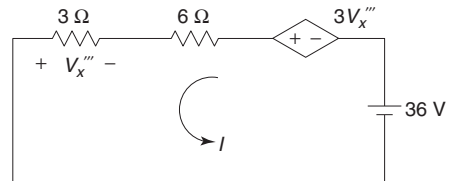


Fig. 2.111

**Step IV** By superposition theorem,

$$V_x = V'_x + V''_x + V'''_x = 3 - 5 - 6 = -8 \text{ V}$$

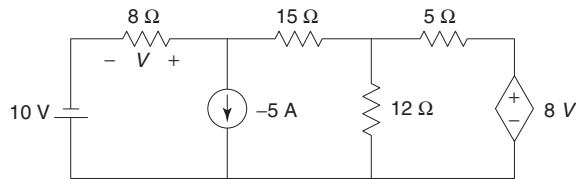

**Example 2.58**Find the voltage  $V$  in the network of Fig. 2.112.**Fig. 2.112****Solution**

**Step I** When the 10 V source is acting alone (Fig. 2.113)

From Fig. 2.113,

$$V' = -8I_1 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$-10 - 8I_1 - 15I_1 - 12(I_1 - I_2) = 0$$

$$35I_1 - 12I_2 = -10 \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$-12(I_2 - I_1) - 5I_2 - 8V' = 0$$

$$-12I_2 + 12I_1 - 5I_2 - 8(-8I_1) = 0$$

$$76I_1 - 17I_2 = 0$$

...(iii)


Solving Eqs (ii) and (iii),

$$I_1 = 0.54 \text{ A}$$

$$I_2 = 2.4 \text{ A}$$

$$V' = -8I_1 = -8(0.54) = -4.32 \text{ V}$$

**Step II** When the  $-5 \text{ A}$  source is acting alone (Fig. 2.114)

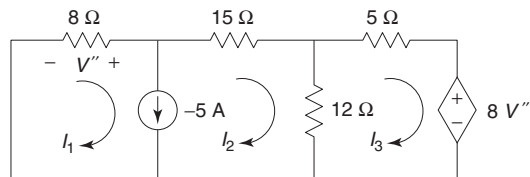**Fig. 2.114**

From Fig. 2.114,

$$V'' = -8I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_1 - I_2 = -5 \quad \dots(ii)$$

## 2.58 Circuit Theory and Networks—Analysis and Synthesis

Applying KVL to the outer path of the supermesh,

$$-8I_1 - 15I_2 - 12(I_2 - I_3) = 0$$

$$-8I_1 - 27I_2 + 12I_3 = 0 \quad \dots(\text{iii})$$

Applying KVL to Mesh 3,

$$-12(I_3 - I_2) - 5I_3 - 8V'' = 0$$

$$-12I_3 + 12I_2 - 5I_3 - 8(-8I_1) = 0$$

$$64I_1 + 12I_2 - 17I_3 = 0 \quad \dots(\text{iv})$$

Solving Eqs (ii), (iii) and (iv),

$$I_1 = 4.97 \text{ A}$$

$$I_2 = 9.97 \text{ A}$$

$$I_3 = 25.74 \text{ A}$$

$$V'' = -8I_1 = -8(-4.97) = -39.76 \text{ V}$$

**Step III** By superposition theorem,

$$V = V' + V'' = -4.32 - 39.76 = -44.08 \text{ V}$$

### Example 2.59

For the network shown in Fig. 2.115, find the voltage  $V_0$ .

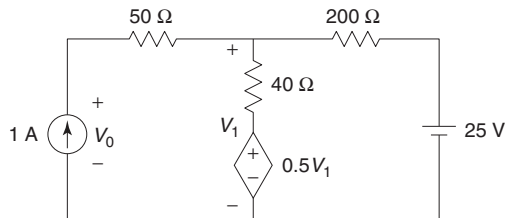


Fig. 2.115

### Solution

**Step I** When the 1 A source is acting alone (Fig. 2.116)

From Fig. 2.116,

$$V_1 = 200 I_2 \quad \dots(\text{i})$$

For Mesh 1,

$$I_1 = 1 \quad \dots(\text{ii})$$

Applying KVL to Mesh 2,

$$0.5V_1 - 40(I_2 - I_1) - 200 I_2 = 0$$

$$0.5(200I_2) - 40I_2 + 40I_1 - 200I_2 = 0$$

$$40I_1 - 140 I_2 = 0 \quad \dots(\text{iii})$$

Solving Eqs (ii) and (iii),

$$I_1 = 1 \text{ A}$$

$$I_2 = 0.29 \text{ A}$$

$$V_0' - 50 I_1 - 200I_2 = 0$$

$$V_0' - 50(1) - 200(0.29) = 0$$

$$V_0' = 108 \text{ V}$$

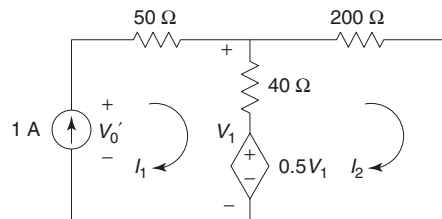


Fig. 2.116

**Step II** When the 25 V source is acting alone (Fig. 2.117)  
From Fig. 2.117,

$$V_1 - 200I - 25 = 0$$

$$V_1 = 200I + 25 \quad \dots(i)$$


Applying KVL to Mesh 1,

$$0.5V_1 - 40I - 200I - 25 = 0$$

$$0.5(200I + 25) - 40I - 200I - 25 = 0$$

$$I = -0.09 \text{ A}$$

$$V_0'' = V_1 = 200I + 25 = 200(-0.09) + 25 = 7 \text{ V}$$

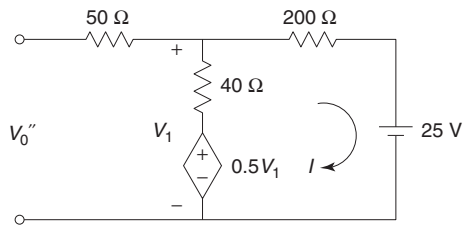


**Fig. 2.117**

**Step III** By superposition theorem,

$$V_0 = V_0' + V_0'' = 108 + 7 = 115 \text{ V}$$

### Example 2.60

For the network shown in Fig. 2.118, find the voltage  $V_x$ .

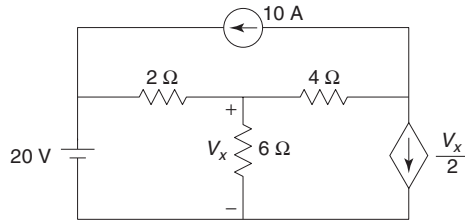

**Fig. 2.118**

### Solution

**Step I** When the 20 V source is acting alone (Fig. 2.119)  
From Fig. 2.119,

$$V'_x = 6(I_1 - I_2) \quad \dots(i)$$

Applying KVL to Mesh 1,

$$20 - 2I_1 - 6(I_1 - I_2) = 0$$

$$8I_1 - 6I_2 = 20 \quad \dots(ii)$$

For Mesh 2,

$$I_2 = \frac{V'_x}{2} = \frac{6(I_1 - I_2)}{2} = 3I_1 - 3I_2$$


$$3I_1 - 4I_2 = 0 \quad \dots(iii)$$

Solving Eqs (ii) and (iii),

$$I_1 = 5.71 \text{ A}$$

$$I_2 = 4.29 \text{ A}$$

$$V'_x = 6(I_1 - I_2) = 6(5.71 - 4.29) = 8.52 \text{ V}$$

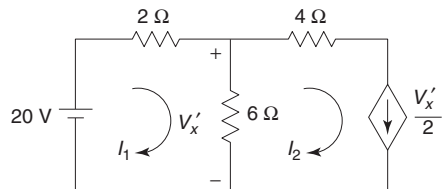

**Fig. 2.119**

## 2.60 Circuit Theory and Networks—Analysis and Synthesis

**Step II** When the 10 A source is acting alone (Fig. 2.120)

From Fig. 2.120,

$$V_x'' = 6(I_1 - I_2) \quad \dots(i)$$

Applying KVL to Mesh 1,

$$\begin{aligned} -2(I_1 - I_3) - 6(I_1 - I_2) &= 0 \\ 8I_1 - 6I_2 - 2I_3 &= 0 \end{aligned} \quad \dots(ii)$$

For Mesh 2,

$$\begin{aligned} I_2 = \frac{V_x''}{2} = \frac{6(I_1 - I_2)}{2} &= 3I_1 - 3I_2 \\ 3I_1 - 4I_2 &= 0 \end{aligned} \quad \dots(iii)$$

For Mesh 3,

$$I_3 = -10 \quad \dots(iv)$$

Solving Eqs (ii), (iii) and (iv),

$$I_1 = -5.71 \text{ A}$$


$$I_2 = -4.29 \text{ A}$$

$$I_3 = -10 \text{ A}$$

$$V_x'' = 6(I_1 - I_2) = 6(-5.71 + 4.29) = -8.52 \text{ V}$$


**Step III** By superposition theorem,

$$V_x = V_x' + V_x'' = 8.52 - 8.52 = 0$$

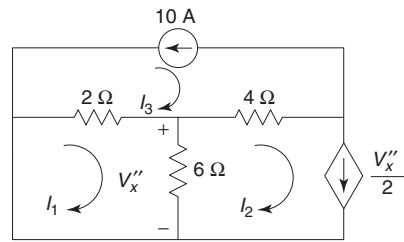

**Fig. 2.120**

**Example 2.61** Calculate the current  $I$  in the network shown in Fig. 2.121.

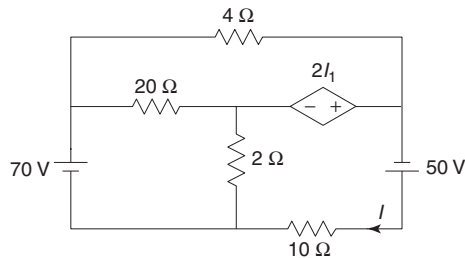

**Fig. 2.121**

**Solution**

**Step I** When the 70 V source is acting alone (Fig. 2.122)

From Fig. 2.122,


$$I' = I_3 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$\begin{aligned} -4I_1 - 2I_1 - 20(I_1 - I_2) &= 0 \\ 26I_1 - 20I_2 &= 0 \end{aligned} \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$\begin{aligned} 70 - 20(I_2 - I_1) - 2(I_2 - I_3) &= 0 \\ -20I_1 + 22I_2 - 2I_3 &= 70 \end{aligned} \quad \dots(iii)$$

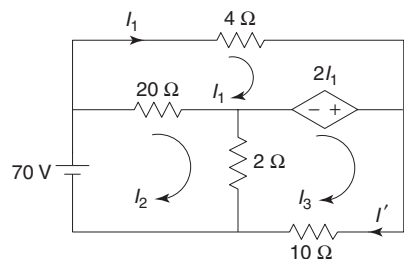

**Fig. 2.122**

Applying KVL to Mesh 3,

$$-2(I_3 - I_2) + 2I_1 - 10I_3 = 0$$

$$2I_1 + 2I_2 - 12I_3 = 0 \quad \dots(\text{iv})$$

Solving Eqs (ii), (iii) and (iv),

$$I_1 = 8.94 \text{ A}$$

$$I_2 = 11.62 \text{ A}$$

$$I_3 = 3.43 \text{ A}$$

$$I' = I_3 = 3.43 \text{ A} (\leftarrow)$$

**Step II** When the 50 V source is acting alone (Fig. 2.123)

From Fig. 2.123,

$$I'' = I_3 \quad \dots(\text{i})$$

Applying KVL to Mesh 1,

$$-4I_1 - 2I_1 - 20(I_1 - I_2) = 0$$

$$26I_1 - 20I_2 = 0 \quad \dots(\text{ii})$$

Applying KVL to Mesh 2,

$$-20(I_2 - I_1) - 2(I_2 - I_3) = 0$$

$$-20I_1 + 22I_2 - 2I_3 = 0 \quad \dots(\text{iii})$$

Applying KVL to Mesh 3,

$$-2(I_3 - I_2) + 2I_1 + 50 - 10I_3 = 0$$

$$2I_1 + 2I_2 - 12I_3 = -50 \quad \dots(\text{iv})$$


Solving Eqs (ii), (iii), and (iv),

$$I_1 = 1.06 \text{ A}$$

$$I_2 = 1.38 \text{ A}$$

$$I_3 = 4.57 \text{ A}$$

$$I'' = I_3 = 4.57 \text{ A} (\leftarrow)$$

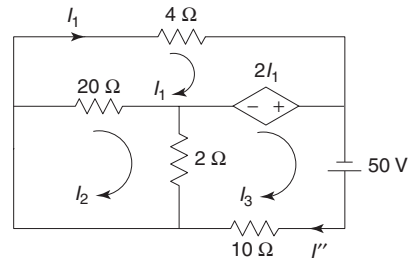


**Fig. 2.123**

**Step III** By superposition theorem,

$$I = I' + I'' = 3.43 + 4.57 = 8 \text{ A} (\leftarrow)$$

**Example 2.62** Find the voltage  $V_0$  in the network of Fig. 2.124.

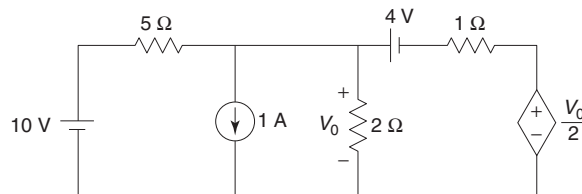

**Fig. 2.124**

## 2.62 Circuit Theory and Networks—Analysis and Synthesis

### Solution

**Step I** When the 10 V source is acting alone (Fig. 2.125)

Applying KCL at the node,

$$\begin{aligned}\frac{V'_0 - 10}{5} + \frac{V'_0}{2} + \frac{V'_0 - \frac{V'_0}{2}}{1} &= 0 \\ \left(\frac{1}{5} + \frac{1}{2} + \frac{1}{2}\right)V'_0 &= 2 \\ V'_0 &= 1.67 \text{ V}\end{aligned}$$

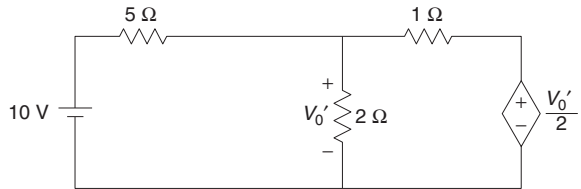


Fig. 2.125

**Step II** When the 1A current source is acting alone (Fig. 2.126)

Applying KCL at the node,

$$\begin{aligned}\frac{V''_0}{5} + 1 + \frac{V''_0}{2} + \frac{V''_0 - \frac{V''_0}{2}}{1} &= 0 \\ \left(\frac{1}{5} + \frac{1}{2} + \frac{1}{2}\right)V''_0 &= -1 \\ V''_0 &= -0.83 \text{ V}\end{aligned}$$

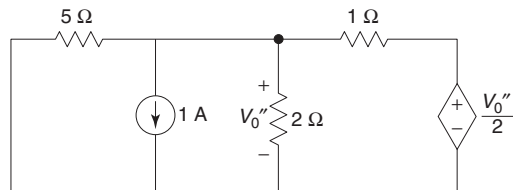


Fig. 2.126

**Step III** When the 4 V source is acting alone (Fig. 2.127)

Applying KCL at the node,

$$\begin{aligned}\frac{V'''_0}{5} + \frac{V'''_0}{2} + \frac{V'''_0 - 4 - \frac{V'''_0}{2}}{1} &= 0 \\ \left(\frac{1}{5} + \frac{1}{2} + \frac{1}{2}\right)V'''_0 &= 4 \\ V'''_0 &= 3.33 \text{ V}\end{aligned}$$

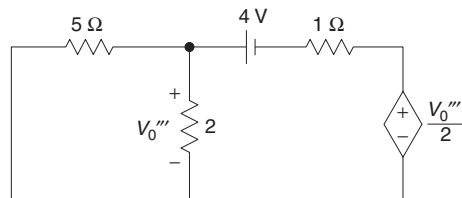



Fig. 2.127

**Step IV** By superposition theorem,


$$V_0 = V'_0 + V''_0 + V'''_0 = 1.67 - 0.83 + 3.33 = 4.17 \text{ V}$$

## 2.8 THEVENIN'S THEOREM

It states that 'any two terminals of a network can be replaced by an equivalent voltage source and an equivalent series resistance. The voltage source is the voltage across the two terminals with load, if any, removed. The series resistance is the resistance of the network measured between two terminals with load removed and constant voltage source being replaced by its internal resistance (or if it is not given with zero resistance, i.e., short circuit) and constant current source replaced by infinite resistance, i.e., open circuit.'

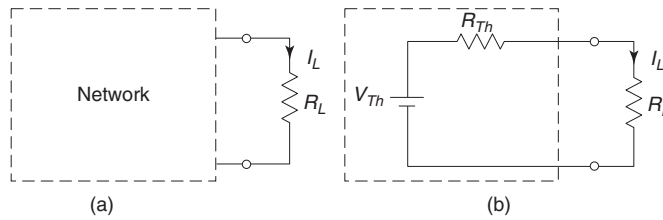**Fig. 2.128** Network illustrating Thevenin's theorem

**Explanation** Consider a simple network as shown in Fig. 2.129.

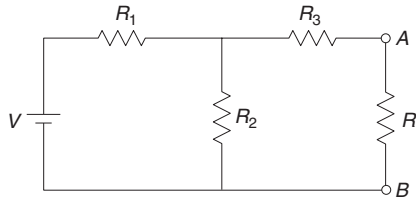**Fig. 2.129** Network

For finding load current through  $R_L$ , first remove the load resistor  $R_L$  from the network and calculate open circuit voltage  $V_{Th}$  across points  $A$  and  $B$  as shown in Fig. 2.130.

$$V_{Th} = \frac{R_2}{R_1 + R_2} V$$

For finding series resistance  $R_{Th}$ , replace the voltage source by a short circuit and calculate resistance between points  $A$  and  $B$  as shown in Fig. 2.131.

$$R_{Th} = R_3 + \frac{R_1 R_2}{R_1 + R_2}$$




Thevenin's equivalent network is shown in Fig. 2.132.

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

If the network contains both independent and dependent sources, Thevenin's resistance  $R_{Th}$  is calculated as,

$$R_{Th} = \frac{V_{Th}}{I_N}$$

where  $I_N$  is the short-circuit current which would flow in a short circuit placed across the terminals  $A$  and  $B$ . Dependent sources are active at all times. They have zero values only when the control voltage or current is zero.  $R_{Th}$  may be negative in some

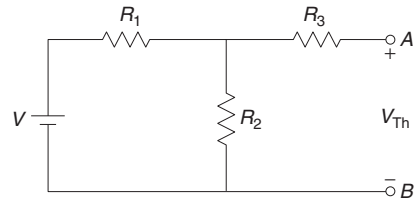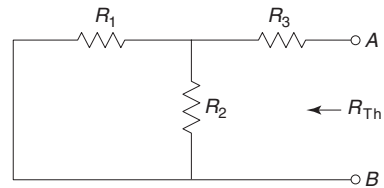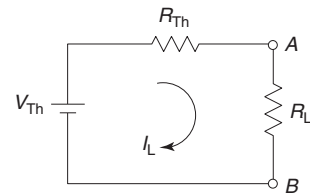**Fig. 2.130** Calculation of  $V_{Th}$ **Fig. 2.131** Calculation of  $R_{Th}$ **Fig. 2.132** Thevenin's equivalent network

## 2.64 Circuit Theory and Networks—Analysis and Synthesis

cases which indicates negative resistance region of the device, i.e., as voltage increases, current decreases in the region and vice-versa.

If the network contains only dependent sources then

$$V_{Th} = 0$$

$$I_N = 0$$

For finding  $R_{Th}$  in such a network, a known voltage  $V$  is applied across the terminals  $A$  and  $B$  and current is calculated through the path  $AB$ .

$$R_{Th} = \frac{V}{I}$$

or a known current source  $I$  is connected across the terminals  $A$  and  $B$  and voltage is calculated across the terminals  $A$  and  $B$ .

$$R_{Th} = \frac{V}{I}$$

Thevenin's equivalent network for such a network is shown in Fig. 2.133.

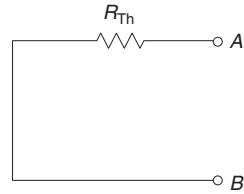


Fig. 2.133 Thevenin's equivalent network

### Steps to be Followed in Thevenin's Theorem

1. Remove the load resistance  $R_L$ .
2. Find the open circuit voltage  $V_{Th}$  across points  $A$  and  $B$ .
3. Find the resistance  $R_{Th}$  as seen from points  $A$  and  $B$ .
4. Replace the network by a voltage source  $V_{Th}$  in series with resistance  $R_{Th}$ .
5. Find the current through  $R_L$  using Ohm's law.

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

### Example 2.63

Determine the current through the  $24\ \Omega$  resistor in Fig. 2.134.

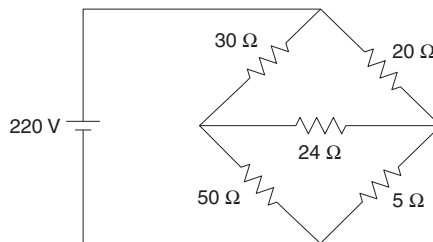


Fig. 2.134

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.135)

$$I_1 = \frac{220}{30 + 50} = 2.75\text{ A}$$

$$I_2 = \frac{220}{20 + 5} = 8.8\text{ A}$$

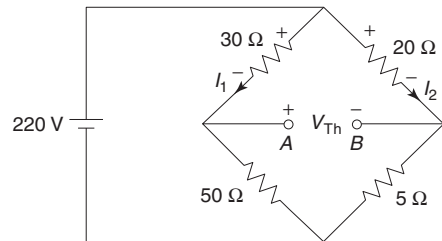


Fig. 2.135




Writing the  $V_{Th}$  equation,

$$V_{Th} + 30I_1 - 20I_2 = 0$$

$$V_{Th} = 20I_2 - 30I_1 = 20(8.8) - 30(2.75) = 93.5 \text{ V}$$


**Step II** Calculation of  $R_{Th}$  (Fig. 2.136)

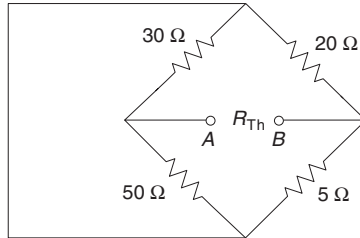

**Fig. 2.136**

Redrawing the circuit (Fig. 2.137),


$$R_{Th} = (30 \parallel 50) + (20 \parallel 5) = 22.75 \Omega$$

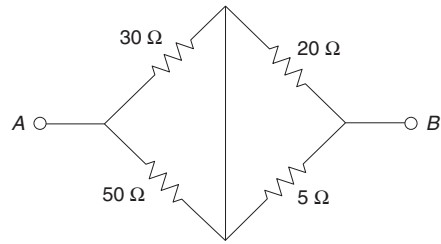

**Fig. 2.137**


**Step III** Calculation of  $I_L$  (Fig. 2.138)

$$I_L = \frac{93.5}{22.75 + 24} = 2 \text{ A}$$

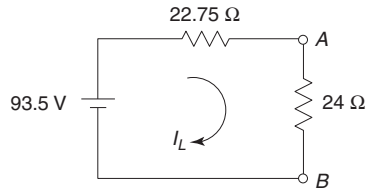

**Fig. 2.138**

**Example 2.64** Find the current through the  $20 \Omega$  resistor in Fig. 2.139.

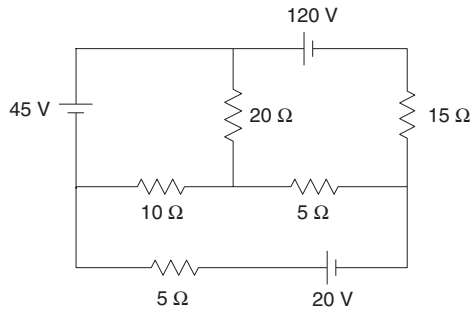

**Fig. 2.139**

## 2.66 Circuit Theory and Networks—Analysis and Synthesis

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.140)

Applying KVL to Mesh 1,

$$\begin{aligned} 45 - 120 - 15I_1 - 5(I_1 - I_2) - 10(I_1 - I_2) &= 0 \\ 30I_1 - 15I_2 &= -75 \quad \dots(i) \end{aligned}$$

Applying KVL to Mesh 2,

$$\begin{aligned} 20 - 5I_2 - 10(I_2 - I_1) - 5(I_2 - I_1) &= 0 \\ -15I_1 + 20I_2 &= 20 \quad \dots(ii) \end{aligned}$$

Solving Eqs (i) and (ii),

$$I_1 = -3.2 \text{ A}$$


$$I_2 = -1.4 \text{ A}$$

Writing the  $V_{Th}$  equation,

$$45 - V_{Th} - 10(I_1 - I_2) = 0$$

$$V_{Th} = 45 - 10(I_1 - I_2) = 45 - 10[-3.2 - (-1.4)] = 63 \text{ V}$$

**Step II** Calculation of  $R_{Th}$  (Fig. 2.141)

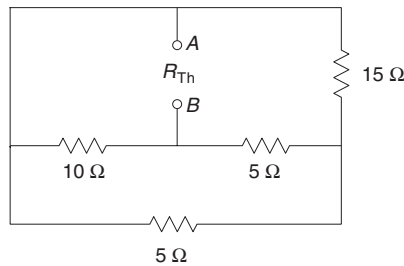

**Fig. 2.141**


Converting the delta formed by resistors of  $10 \Omega$ ,  $5 \Omega$  and  $5 \Omega$  into an equivalent star network (Fig. 2.142),

$$R_1 = \frac{10 \times 5}{20} = 2.5 \Omega$$


$$R_2 = \frac{10 \times 5}{20} = 2.5 \Omega$$

$$R_3 = \frac{5 \times 5}{20} = 1.25 \Omega$$


Simplifying the network (Fig. 2.143 and Fig. 2.144),

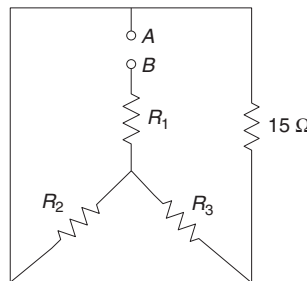

**Fig. 2.142**

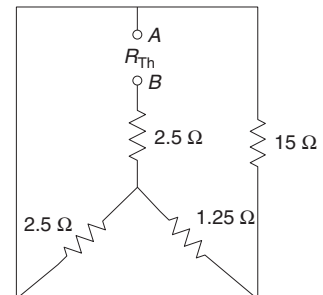

**Fig. 2.143**

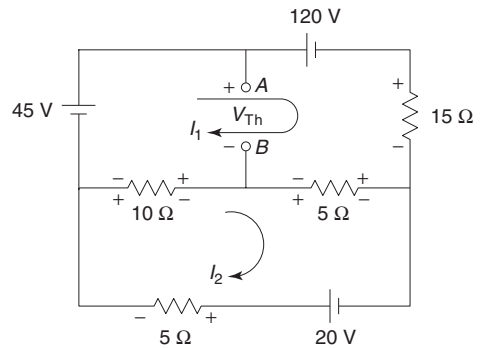

**Fig. 2.140**

$$R_{Th} = (16.25 \parallel 2.5) + 2.5 = 4.67 \, \Omega$$

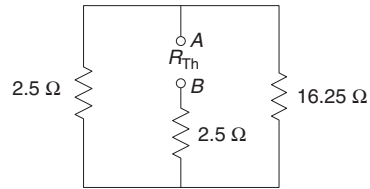


Fig. 2.144

**Step III** Calculation of  $I_L$  (Fig. 2.145)

$$I_L = \frac{63}{4.67 + 20} = 2.55 \text{ A}$$

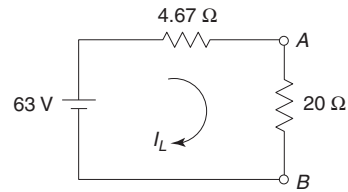


Fig. 2.145

### Example 2.65

Find the current through the  $10 \, \Omega$  resistor in Fig. 2.146.

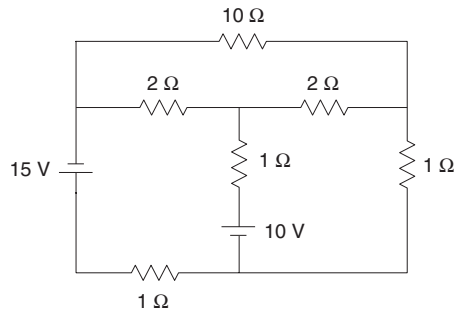


Fig. 2.146

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.147)

Applying KVL to Mesh 1,

$$\begin{aligned} -15 - 2I_1 - 1(I_1 - I_2) - 10 - 1I_1 &= 0 \\ 4I_1 - I_2 &= -25 \end{aligned} \quad \dots(i)$$

Applying KVL to Mesh 2,

$$\begin{aligned} 10 - 1(I_2 - I_1) - 2I_2 - 1I_2 &= 0 \\ -I_1 + 4I_2 &= 10 \end{aligned} \quad \dots(ii)$$

Solving Eqs (i) and (ii),

$$I_1 = -6 \text{ A}$$

$$I_2 = 1 \text{ A}$$

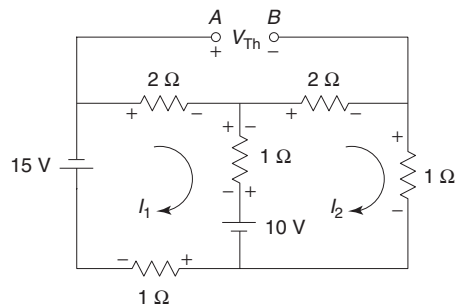


Fig. 2.147

## 2.68 Circuit Theory and Networks—Analysis and Synthesis


Writing the  $V_{Th}$  equation,

$$-V_{Th} + 2I_2 + 2I_1 = 0$$

$$V_{Th} = 2I_1 + 2I_2 = 2(-6) + 2(1) = -10 \text{ V}$$

$$= 10 \text{ V (the terminal } B \text{ is positive w.r.t. } A)$$

**Step II** Calculation of  $R_{Th}$  (Fig. 2.148)

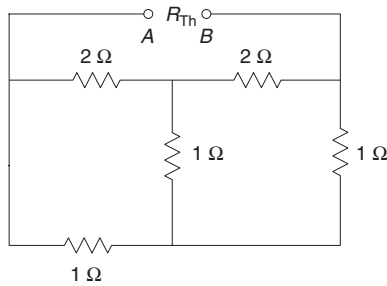


**Fig. 2.148**

Converting the star network formed by resistors of  $2 \Omega$ ,  $2 \Omega$  and  $1 \Omega$  into an equivalent delta network (Fig. 2.149),

$$R_1 = 2 + 2 + \frac{2 \times 2}{1} = 8 \Omega$$


$$R_2 = 2 + 1 + \frac{2 \times 1}{2} = 4 \Omega$$

$$R_3 = 2 + 1 + \frac{2 \times 1}{2} = 4 \Omega$$

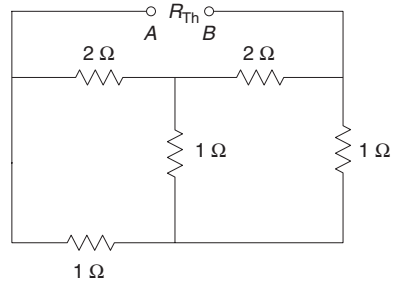

**Fig. 2.149**

Simplifying the network (Fig. 2.150),

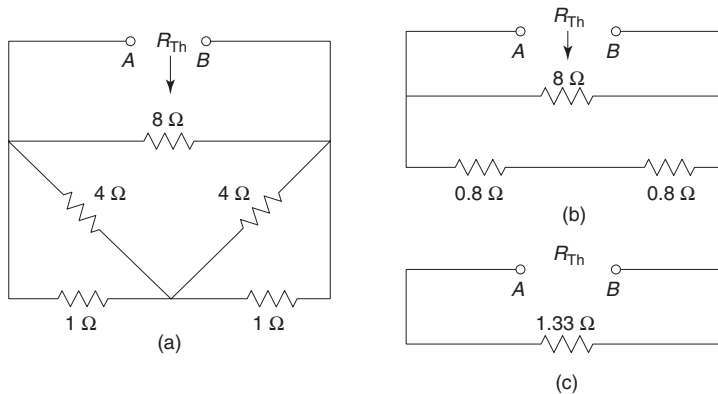


**Fig. 2.150**

$$R_{Th} = 1.33 \, \Omega$$

**Step III** Calculation of  $I_L$  (Fig. 2.151)


$$I_L = \frac{10}{1.33 + 10} = 0.88 \, \text{A} \, (\uparrow)$$

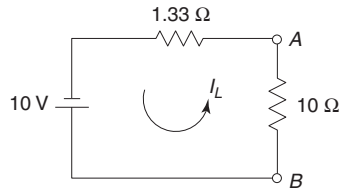

**Fig. 2.151**

### Example 2.66


Find the current through the  $1 \, \Omega$  resistor in Fig. 2.152.

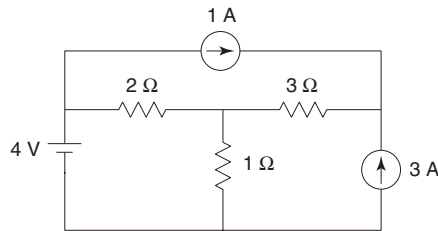

**Fig. 2.152**

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.153)

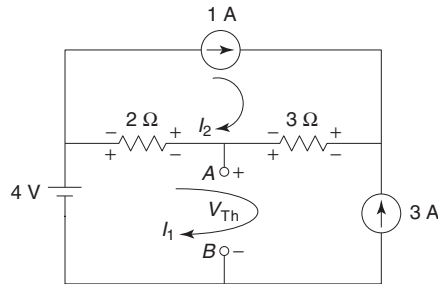

**Fig. 2.153**

Writing the current equations for Meshes 1 and 2,

$$I_1 = -3$$

$$I_2 = 1$$

Writing the  $V_{Th}$  equation,

$$4 - 2(I_1 - I_2) - V_{Th} = 0$$


$$V_{Th} = 4 - 2(I_1 - I_2) = 4 - 2(-4) = 12 \, \text{V}$$

**Step II** Calculation of  $R_{Th}$  (Fig. 2.154)


$$R_{Th} = 2 \, \Omega$$

**Step III** Calculation of  $I_L$  (Fig. 2.155)

$$I_L = \frac{12}{2 + 1} = 4 \, \text{A}$$

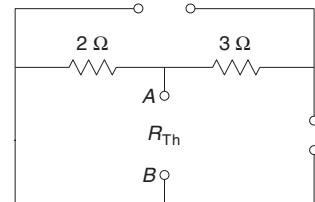

**Fig. 2.154**

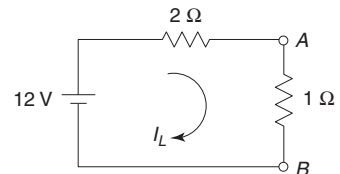

**Fig. 2.155**

## EXAMPLES WITH DEPENDENT SOURCES

**Example 2.67** Obtain the Thevenin equivalent network for the given network of Fig. 2.156 at terminals A and B.

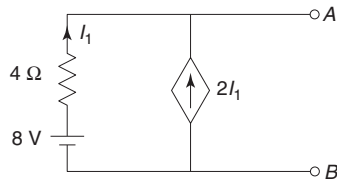


Fig. 2.156

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.157)

From Fig. 2.157,

$$\begin{aligned} I_1 &= -2I_1 \\ 3I_1 &= 0 \\ I_1 &= 0 \end{aligned}$$

Writing the  $V_{Th}$  equation,

$$\begin{aligned} 8 - 0 - V_{Th} &= 0 \\ V_{Th} &= 8 \text{ V} \end{aligned}$$

**Step II** Calculation of  $I_N$  (Fig. 2.158),

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$\begin{aligned} I_2 - I_1 &= 2I_1 \\ 3I_1 - I_2 &= 0 \end{aligned} \quad \dots(i)$$

Applying KVL to the outer path of the supermesh,

$$\begin{aligned} 8 - 4I_1 &= 0 \\ I_1 &= 2 \end{aligned} \quad \dots(ii)$$

Solving Eqs (i) and (ii),

$$\begin{aligned} I_2 &= 6 \text{ A} \\ I_N &= I_2 = 6 \text{ A} \end{aligned}$$

**Step III** Calculation of  $R_{Th}$

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{8}{6} = 1.33 \Omega$$

**Step IV** Thevenin's Equivalent Network (Fig. 2.159)

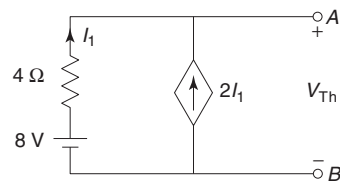


Fig. 2.157

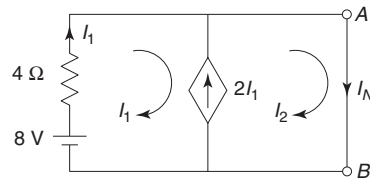


Fig. 2.158

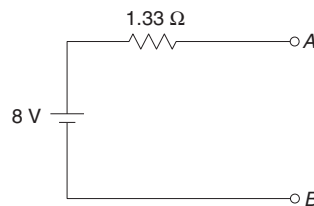
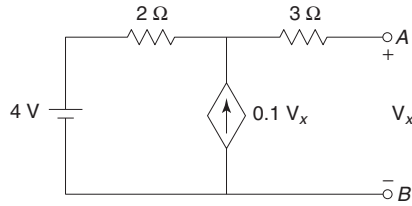


Fig. 2.159

**Example 2.68**

Find Thevenin's equivalent network of Fig. 2.160.

**Fig. 2.160****Solution****Step I** Calculation of  $V_{Th}$  (Fig. 2.161)

$$V_x = V_{Th}$$

$$I_1 = -0.1 V_x$$

Writing the  $V_{Th}$  equation,


$$4 - 2I_1 - V_x = 0$$

$$4 - 2(-0.1V_x) - V_x = 0$$

$$4 - 0.8V_x = 0$$

$$V_x = 5 \text{ V}$$

$$V_x = V_{Th} = 5 \text{ V}$$


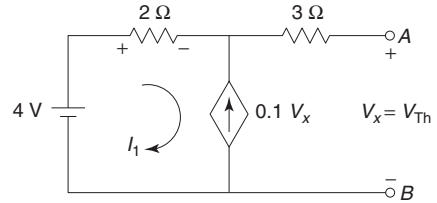
**Fig. 2.161****Step II** Calculation of  $I_N$  (Fig. 2.162)

From Fig. 2.162,


$$V_x = 0$$

The dependent source  $0.1 V_x$  depends on the controlling variable  $V_x$ . When  $V_x = 0$ , the dependent source vanishes, i.e.,  $0.1 V_x = 0$  as shown in Fig. 2.163.

$$I_N = \frac{4}{2+3} = 0.8 \text{ A}$$

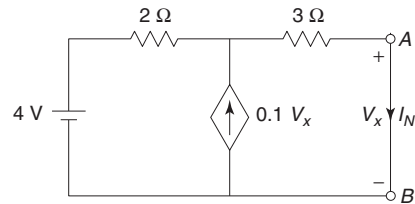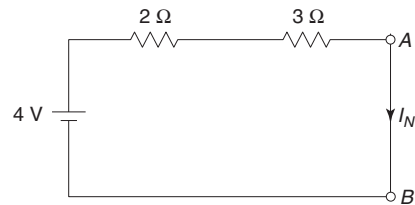**Fig. 2.162****Fig. 2.163****Step III** Calculation of  $R_{Th}$ 

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{5}{0.8} = 6.25 \Omega$$

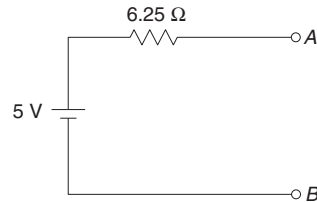**Step IV** Thevenin's Equivalent Network (Fig. 2.164)**Fig. 2.164**

**Example 2.69** Obtain the Thevenin equivalent network of Fig. 2.165 for the terminals A and B.

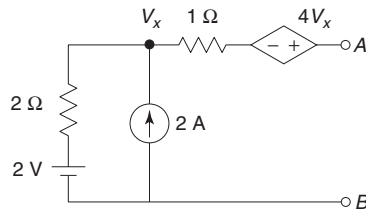


Fig. 2.165

**Solution**

**Step I** Calculation of  $V_{Th}$  (Fig. 2.166)

From Fig. 2.166,

$$2 - 2I_1 - V_x = 0$$

$$V_x = 2 - 2I_1$$

For Mesh 1,

$$I_1 = -2 \text{ A}$$

$$V_x = 2 - 2(-2) = 6 \text{ V}$$

Writing the  $V_{Th}$  equation,

$$2 - 2I_1 - 0 + 4V_x - V_{Th} = 0$$

$$2 - 2(-2) - 0 + 4(6) - V_{Th} = 0$$

$$V_{Th} = 30 \text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.167)

From Fig. 2.167,

$$V_x = 2 - 2I_1$$

Meshes 1 and 2 will form a supermesh,

Writing current equation for the supermesh

$$I_2 - I_1 = 2$$

Applying KVL to the outer path of the supermesh,

$$2 - 2I_1 - 1I_2 + 4V_x = 0$$

$$2 - 2I_1 - I_2 + 4(2 - 2I_1) = 0$$

$$10I_1 + I_2 = 10$$

Solving Eqs (ii) and (iii),

$$I_1 = 0.73 \text{ A}$$

$$I_2 = 2.73 \text{ A}$$

$$I_N = I_2 = 2.73 \text{ A}$$

**Step III** Calculation of  $R_{Th}$

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{30}{2.73} = 10.98 \Omega$$

**Step IV** Thevenin's Equivalent Network (Fig. 2.168)

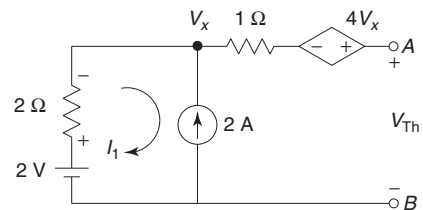


Fig. 2.166

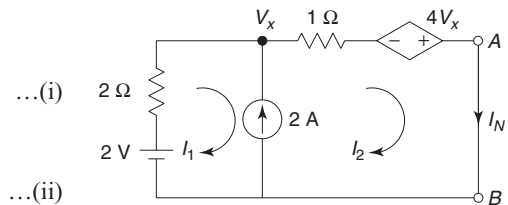


Fig. 2.167


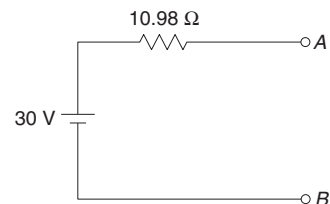


Fig. 2.168

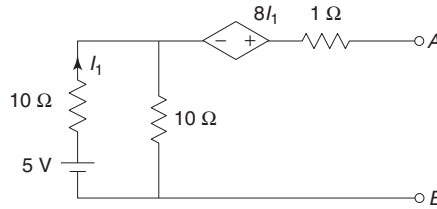

**Example 2.70**

Find the Thevenin equivalent network of Fig. 2.169 for the terminals A and B.

**Fig. 2.169****Solution****Step I** Calculation of  $V_{Th}$  (Fig. 2.170)

Applying KVL to the mesh,

$$5 - 10I_1 - 10I_1 = 0$$

$$I_1 = \frac{5}{20} = 0.25 \text{ A}$$

Writing the  $V_{Th}$  equation,

$$5 - 10I_1 + 8I_1 - 0 - V_{Th} = 0$$

$$V_{Th} = 5 - 2I_1 = 5 - 2(0.25) = 4.5 \text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.171)

Applying KVL to Mesh 1,

$$5 - 10I_1 - 10(I_1 - I_2) = 0$$

$$20I_1 - 10I_2 = 5$$

Applying KVL to Mesh 2,

$$-10(I_2 - I_1) + 8I_1 - 1I_2 = 0$$

$$18I_1 - 11I_2 = 0 \quad \dots(ii)$$

Solving Eqs (i) and (ii),




$$I_1 = 1.375 \text{ A}$$

$$I_2 = 2.25 \text{ A}$$

$$I_N = I_2 = 2.25 \text{ A}$$

**Step III** Calculation of  $R_{Th}$ 

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{4.5}{2.25} = 2 \Omega$$

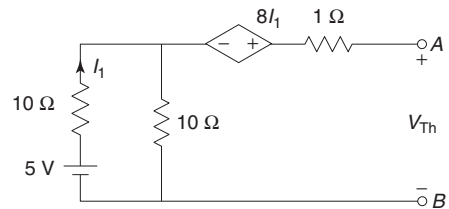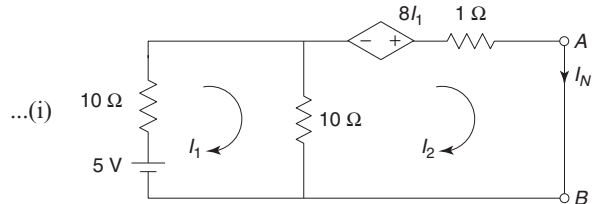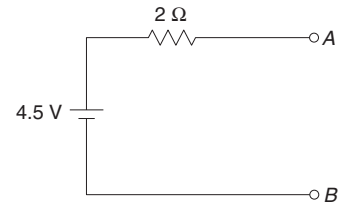**Step IV** Thevenin's Equivalent Network (Fig. 2.172)**Fig. 2.170****Fig. 2.171****Fig. 2.172**

**Example 2.71** Find  $V_{Th}$  and  $R_{Th}$  between terminals A and B of the network shown in Fig. 2.173.

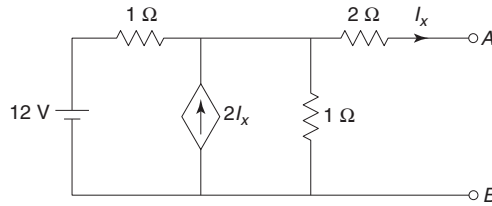


Fig. 2.173

**Solution**

**Step I** Calculation of  $V_{Th}$  (Fig. 2.174)

$$I_x = 0$$

The dependent source  $2I_x$  depends on the controlling variable  $I_x$ . When  $I_x = 0$ , the dependent source vanishes, i.e.,  $2I_x = 0$  as shown in Fig. 2.174.

Writing the  $V_{Th}$  equation,

$$V_{Th} = 12 \times \frac{1}{1+1} = 6 \text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.175)

From Fig. 2.175,

$$I_x = \frac{V_1}{2}$$

Applying KCL at Node 1,

$$\frac{V_1 - 12}{1} + \frac{V_1}{1} + \frac{V_1}{2} = 2I_x$$

$$V_1 + V_1 + \frac{V_1}{2} - 12 = 2 \left( \frac{V_1}{2} \right)$$

$$V_1 = 8 \text{ V}$$

$$I_N = \frac{V_1}{2} = \frac{8}{2} = 4 \text{ A}$$

**Step III** Calculation of  $R_{Th}$

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{6}{4} = 1.5 \Omega$$

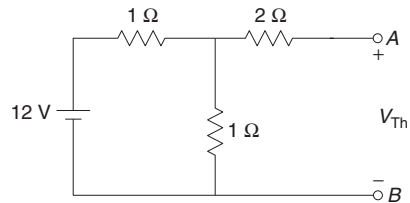


Fig. 2.174

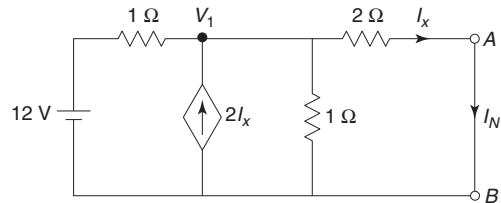


Fig. 2.175

**Example 2.72** Obtain the Thevenin equivalent network of Fig. 2.176 for the given network at terminals a and b.

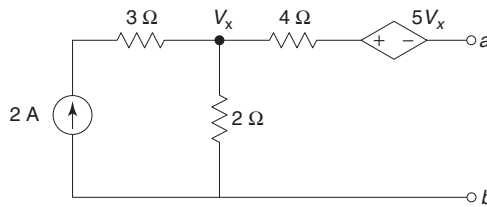


Fig. 2.176

**Solution****Step I** Calculation of  $V_{Th}$  (Fig. 2.177)Applying KCL at Node  $x$ ,

$$2 = \frac{V_x}{2}$$

$$V_x = 4 \text{ V}$$

Writing the  $V_{Th}$  equation,

$$V_{Th} = V_x - 5V_x = -4V_x$$

$$= -16 \text{ V} \quad (\text{the terminal } a \text{ is negative w.r.t. } b)$$

**Step II** Calculation of  $I_N$  (Fig. 2.178)Applying KCL at Node  $x$ ,

$$2 = \frac{V_x}{2} + \frac{V_x - 5V_x}{4}$$

$$2 = \frac{V_x}{2} - V_x = -\frac{V_x}{2}$$

$$V_x = -4 \text{ V}$$

$$I_N = \frac{V_x - 5V_x}{4} = -V_x = 4 \text{ A}$$

**Step III** Calculation of  $R_{Th}$ 

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{-16}{4} = -4 \Omega$$

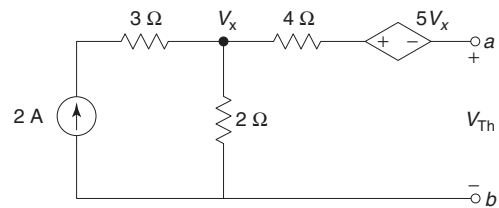
**Step IV** Thevenin's Equivalent Network (Fig. 2.179)

Fig. 2.177

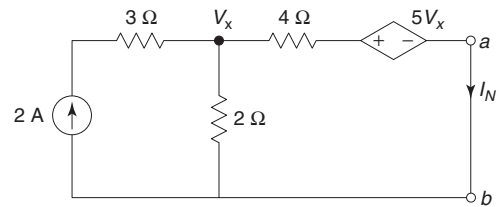


Fig. 2.178

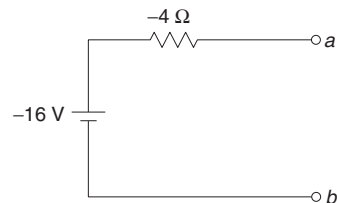


Fig. 2.179

**Example 2.73** Obtain the Thevenin equivalent network of Fig. 2.180 for the given network.

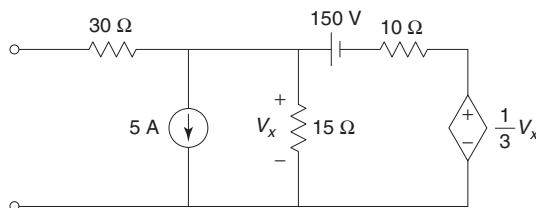


Fig. 2.180

## 2.76 Circuit Theory and Networks—Analysis and Synthesis

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.181)

From Fig. 2.181,

$$V_x = V_{Th}$$

Applying KCL at the node,

$$\frac{V_x - 150 - \frac{1}{3}V_x}{10} + \frac{V_x}{15} + 5 = 0$$

$$V_x = 75 \text{ V}$$

$$V_{Th} = 75 \text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.182)

Applying KCL at Node  $x$ ,

$$\frac{V_x}{30} + 5 + \frac{V_x}{15} + \frac{V_x - 150 - \frac{1}{3}V_x}{10} = 0$$

$$\frac{V_x}{30} + \frac{V_x}{15} + \frac{V_x}{10} - \frac{V_x}{30} = 15 - 5$$

$$V_x = 60 \text{ V}$$

$$I_N = \frac{V_x}{30} = \frac{60}{30} = 2 \text{ A}$$

**Step III** Calculation of  $R_{Th}$

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{75}{2} = 37.5 \Omega$$

**Step IV** Thevenin's Equivalent Network (Fig. 2.183)

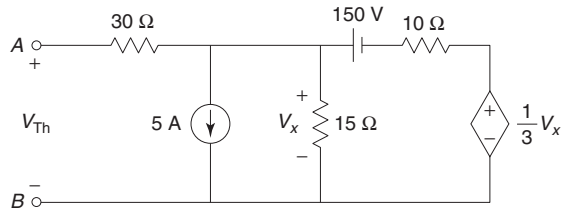


Fig. 2.181

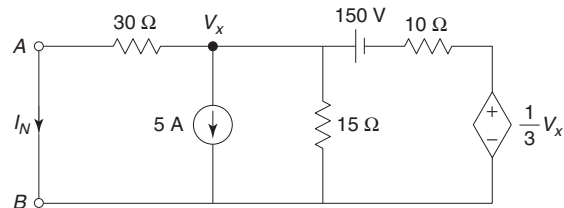


Fig. 2.182

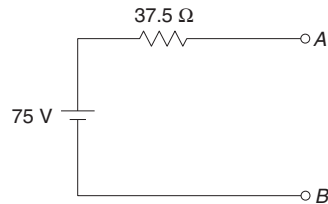


Fig. 2.183

### Example 2.74

Find the Thevenin's equivalent network of the network to the left of A-B in the Fig. 2.184.

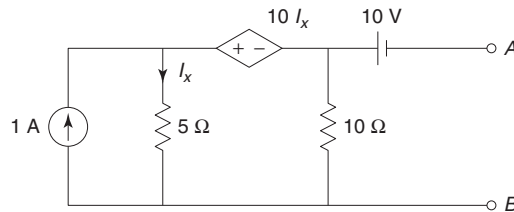


Fig. 2.184

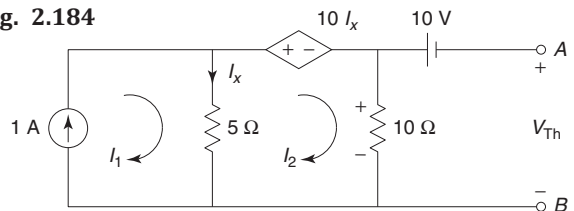


Fig. 2.185

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.185)

From Fig. 2.185,

$$I_x = I_1 - I_2 \quad \dots(i)$$

For Mesh 1,

$$I_1 = 1 \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$-5(I_2 - I_1) - 10I_x - 10I_2 = 0$$

$$-5(I_2 - I_1) - 10(I_1 - I_2) - 10I_2 = 0$$

$$5I_1 + 5I_2 = 0 \quad \dots(iii)$$

Solving Eqs (ii) and (iii),

$$I_1 = 1 \text{ A}$$

$$I_2 = -1 \text{ A}$$

$$I_x = I_1 - I_2 = 1 - (-1) = 2 \text{ A}$$

Writing the  $V_{Th}$  equation,

$$10I_2 - 10 - V_{Th} = 0$$

$$10(-1) - 10 - V_{Th} = 0$$

$$V_{Th} = -20 \text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.186)

From Fig. 2.186,

$$I_x = I_1 - I_2 \quad \dots(i)$$

For Mesh 1,

$$I_1 = 1 \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$-5(I_2 - I_1) - 10I_x - 10(I_2 - I_3) = 0$$

$$-5(I_2 - I_1) - 10(I_1 - I_2) - 10(I_2 - I_3) = 0$$

$$-5I_1 - 5I_2 + 10I_3 = 0 \quad \dots(iii)$$

Applying KVL to Mesh 3,

$$-10(I_3 - I_2) - 10 = 0$$

$$10I_2 - 10I_3 = 10 \quad \dots(iv)$$

Solving Eqs (ii), (iii) and (iv),

$$I_1 = 1 \text{ A}$$

$$I_2 = 3 \text{ A}$$

$$I_3 = 2 \text{ A}$$

$$I_N = I_3 = 2 \text{ A}$$

**Step III** Calculation of  $R_{Th}$

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{-20}{2} = -10 \Omega$$

**Step IV** Thevenin's Equivalent Network (Fig. 2.187)

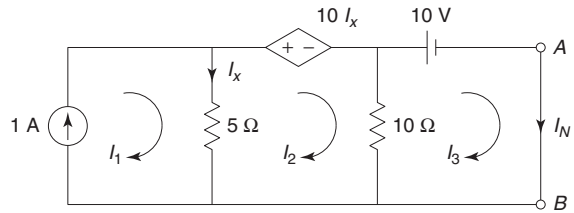


Fig. 2.186

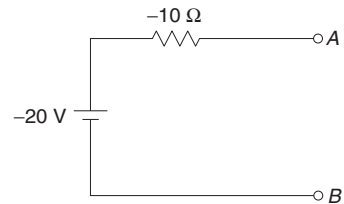


Fig. 2.187

**Example 2.75** Find Thevenin's equivalent network at terminals A and B in the network of Fig. 2.188.

## 2.78 Circuit Theory and Networks—Analysis and Synthesis

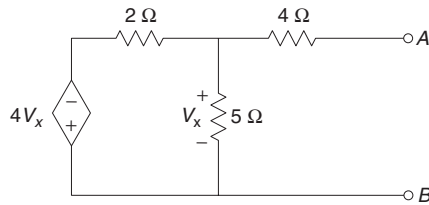


Fig. 2.188

### Solution

Since the network does not contain any independent source,

$$V_{Th} = 0$$

$$I_N = 0$$

But the  $R_{Th}$  can be calculated by applying a known voltage source of 1 V at the terminals  $A$  and  $B$  as shown in Fig. 2.189.

$$R_{Th} = \frac{V}{I} = \frac{1}{I}$$

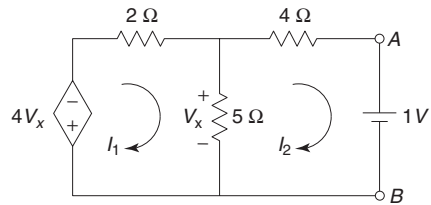


Fig. 2.189

From Fig. 2.189,

$$V_x = 5(I_1 - I_2) \quad \dots(i)$$

Applying KVL to Mesh 1,

$$-4V_x - 2I_1 - 5(I_1 - I_2) = 0$$

$$-4[5(I_1 - I_2)] - 2I_1 - 5I_1 + 5I_2 = 0$$

$$-27I_1 + 25I_2 = 0 \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$-5(I_2 - I_1) - 4I_2 - 1 = 0$$

$$5I_1 - 9I_2 = 1 \quad \dots(iii)$$

Solving Eqs (ii) and (iii),

$$I_1 = -0.21 \text{ A}$$

$$I_2 = -0.23 \text{ A}$$

Hence, current supplied by voltage source of 1 V is 0.23 A.

$$R_{Th} = \frac{1}{0.23} = 4.35 \Omega$$

Hence, Thevenin's equivalent network is shown in Fig. 2.190.

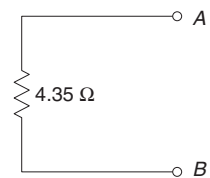


Fig. 2.190

**Example 2.76** Find the current in the  $9 \Omega$  resistor in Fig. 2.191.

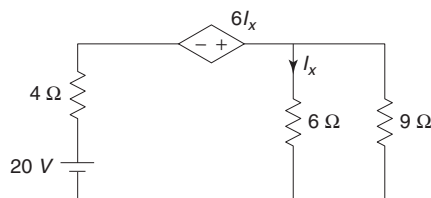


Fig. 2.191

**Solution****Step I** Calculation of  $V_{Th}$  (Fig. 2.192)

Applying KVL to the mesh,

$$20 - 4I_x + 6I_x - 6I_x = 0$$

$$I_x = 5 \text{ A}$$

Writing the  $V_{Th}$  equation,

$$6I_x - V_{Th} = 0$$

$$6(5) - V_{Th} = 0$$

$$V_{Th} = 30 \text{ V}$$


**Step II** Calculation of  $I_N$  (Fig. 2.193).

From Fig. 2.193,

$$I_x = 0$$

The dependent source  $6I_x$  depends on the controlling variable  $I_x$ . When  $I_x = 0$ , the dependent source vanishes, i.e.,  $6I_x = 0$  as shown in Fig. 2.194.



$$I_N = \frac{20}{4} = 5 \text{ A}$$

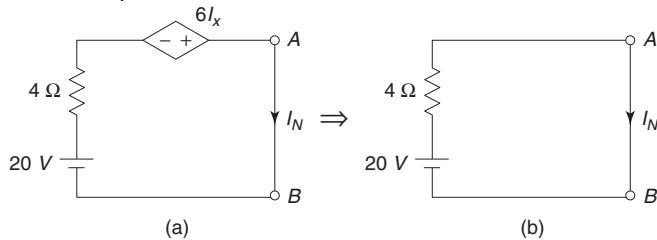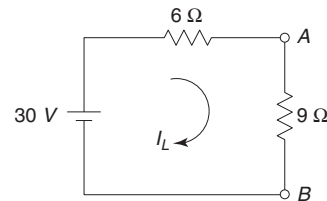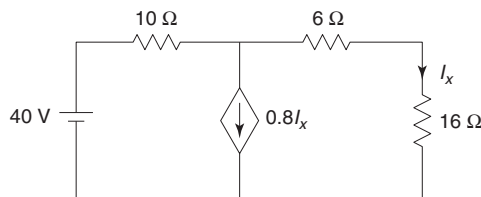**Fig. 2.194****Step III** Calculation of  $R_{Th}$ 

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{30}{5} = 6 \Omega$$

**Step IV** Calculation of  $I_L$  (Fig. 2.195)

$$I_L = \frac{30}{6+9} = 2 \text{ A}$$

**Fig. 2.195****Example 2.77**Determine the current in the  $16 \Omega$  resistor in Fig. 2.196.**Fig. 2.196**

## 2.80 Circuit Theory and Networks—Analysis and Synthesis

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.197)

From Fig. 2.197,

$$I_x = 0$$

The dependent source  $0.8I_x$  depends on the controlling variable  $I_x$ . When  $I_x = 0$ , the dependent source vanishes, as shown in Fig. 2.198.

i.e.,

$$0.8I_x = 0$$

$$V_{Th} = 40 \text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.199)

From Fig. 2.199,

$$I_x = I_2$$

...(i)

Meshes 1 and 2 will form a supermesh,

Writing current equation for the supermesh,

$$I_1 - I_2 = 0.8 I_x = 0.8 I_2$$

...(ii)

$$I_1 - 1.8 I_2 = 0$$

Applying KVL to the outer path of the supermesh,

$$40 - 10 I_1 - 6 I_2 = 0$$

$$10 I_1 + 6 I_2 = 40$$

...(iii)

Solving Eqs (ii) and (iii),

$$I_1 = 3 \text{ A}$$

$$I_2 = \frac{5}{3} \text{ A}$$

$$I_N = I_2 = \frac{5}{3} \text{ A}$$

**Step III** Calculation of  $R_{Th}$

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{40}{\frac{5}{3}} = 24 \Omega$$

**Step IV** Calculation of  $I_L$  (Fig. 2.200)

$$I_L = \frac{40}{24 + 16} = 1 \text{ A}$$

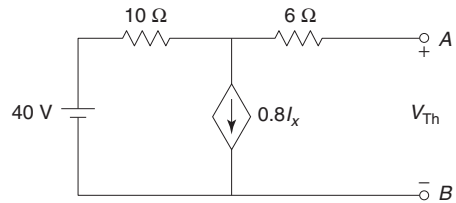


Fig. 2.197

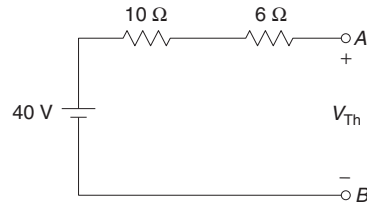


Fig. 2.198

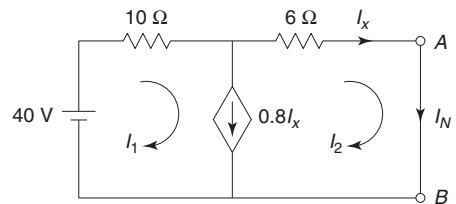


Fig. 2.199

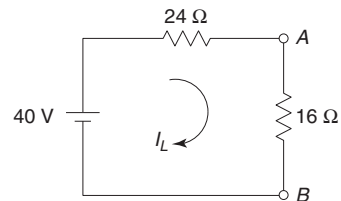


Fig. 2.200

### Example 2.78

Find the current in the  $6 \Omega$  resistor in Fig. 2.201.

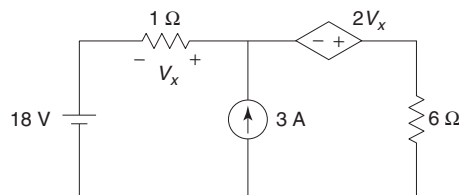


Fig. 2.201



**Solution****Step I** Calculation of  $V_{Th}$  (Fig. 2.202)

From Fig. 2.202,

$$V_x = -1I_1 = -I_1 \quad \dots(i)$$

For Mesh 1,

$$I_1 = -3 \text{ A} \quad \dots(ii)$$

$$V_x = 3 \text{ V}$$

Writing the  $V_{Th}$  equation,

$$18 - 1I_1 + 2V_x - V_{Th} = 0$$

$$18 + 3 + 2(3) - V_{Th} = 0$$

$$V_{Th} = 27 \text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.203)

From Fig. 2.203,

$$V_x = -I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh,  
Writing current equation for supermesh,

$$I_2 - I_1 = 3 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$18 - 1I_1 + 2V_x = 0$$

$$18 - I_1 + 2(-I_1) = 0 \quad \dots(iii)$$

$$I_1 = 6 \text{ A}$$

Solving Eqs (ii) and (iii),

$$I_2 = 9 \text{ A}$$





$$I_N = I_2 = 9 \text{ A}$$

**Step III** Calculation of  $R_{Th}$ 

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{27}{9} = 3 \Omega$$

**Step IV** Calculation of  $I_L$  (Fig. 2.204)

$$I_L = \frac{27}{3+6} = 3 \text{ A}$$

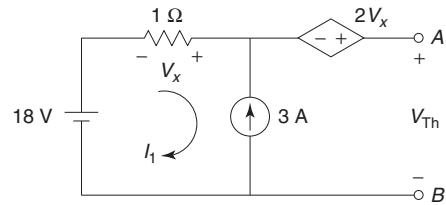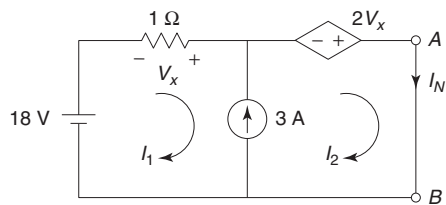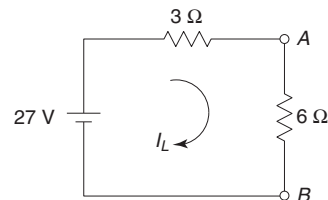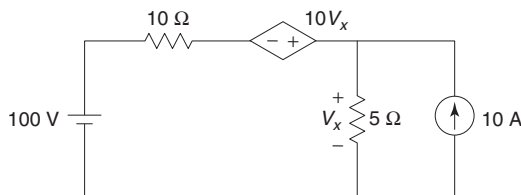**Fig. 2.202****Fig. 2.203****Fig. 2.204****Example 2.79**Find the current in the  $10 \Omega$  resistor.**Fig. 2.205**

## 2.82 Circuit Theory and Networks—Analysis and Synthesis

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.206)

From Fig. 2.206,

$$V_x = 10 \times 5 = 50 \text{ V}$$

Writing the  $V_{Th}$  equation,

$$100 - V_{Th} + 10V_x - V_x = 0$$

$$100 - V_{Th} + 9V_x = 0$$

$$100 - V_{Th} + 9(50) = 0$$

$$V_{Th} = 550 \text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.207)

From Fig. 2.207,

$$V_x = 5(I_N + 10)$$

Applying KVL to Mesh 1,

$$100 + 10V_x - V_x = 0$$

$$V_x = -\frac{100}{9}$$

$$-\frac{100}{9} = 5I_N + 50$$

$$I_N = -\frac{550}{45} \text{ A}$$

**Step III** Calculation of  $R_{Th}$

$$R_{Th} = \frac{550}{-\frac{550}{45}} = -45 \Omega$$

**Step IV** Calculation of  $I_L$  (Fig. 2.208)

$$I_L = \frac{550}{-45 + 10} = -\frac{110}{7} \text{ A}$$

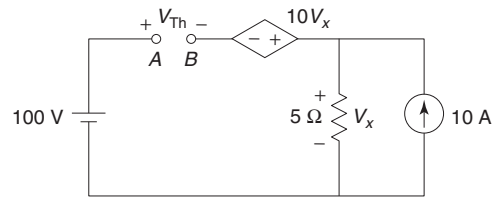


Fig. 2.206

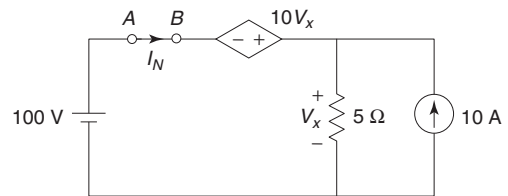


Fig. 2.207

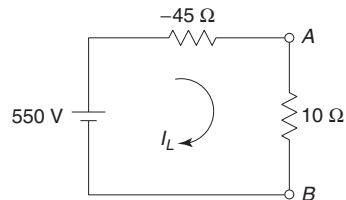


Fig. 2.208

## 2.9 NORTON'S THEOREM

It states that 'any two terminals of a network can be replaced by an equivalent current source and an equivalent parallel resistance.' The constant current is equal to the current which would flow in a short circuit placed across the terminals. The parallel resistance is the resistance of the network when viewed from these open-circuited terminals after all voltage and current sources have been removed and replaced by internal resistances.


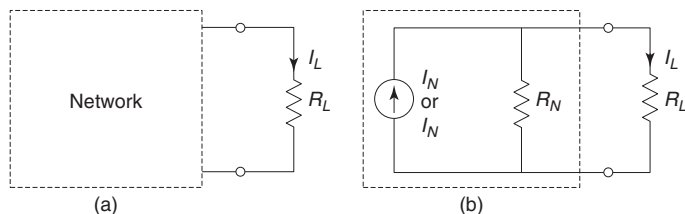


Fig. 2.209 Network illustrating Norton's theorem

**Explanation** Consider a simple network as shown in Fig. 2.210.

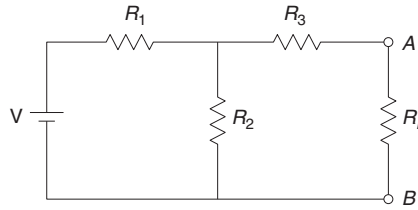

**Fig. 2.210** Network

For finding load current through  $R_L$ , first remove the load resistor  $R_L$  from the network and calculate short circuit current  $I_{SC}$  or  $I_N$  which would flow in a short circuit placed across terminals  $A$  and  $B$  as shown in Fig. 2.211.

For finding parallel resistance  $R_N$ , replace the voltage source by a short circuit and calculate resistance between points  $A$  and  $B$  as shown in Fig. 2.212.

$$R_N = R_3 + \frac{R_1 R_2}{R_1 + R_2}$$

Norton's equivalent network is shown in Fig. 2.213.

$$I_L = I_N \frac{R_N}{R_N + R_L}$$

If the network contains both independent and dependent sources, Norton's resistance  $R_N$  is calculated as

$$R_N = \frac{V_{Th}}{I_N}$$

where  $V_{Th}$  is the open-circuit voltage across terminals  $A$  and  $B$ . If the network contains only dependent sources, then


$$V_{Th} = 0$$

$$I_N = 0$$


To find  $R_{Th}$  in such network, a known voltage  $V$  or current  $I$  is applied across the terminals  $A$  and  $B$ , and the current  $I$  or the voltage  $V$  is calculated respectively.

$$R_N = \frac{V}{I}$$


Norton's equivalent network for such a network is shown in Fig. 2.214.

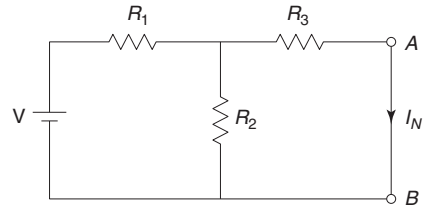


**Fig. 2.211** Calculation of  $I_N$

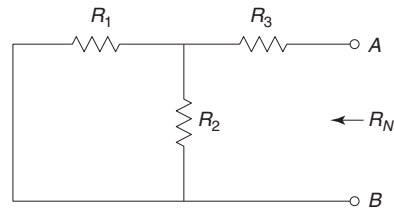

**Fig. 2.212** Calculation of  $R_N$

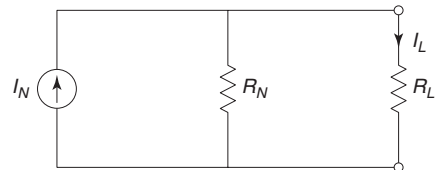

**Fig. 2.213** Norton's equivalent network

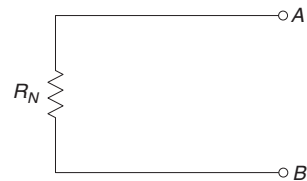

**Fig. 2.214** Norton's equivalent network

## 2.84 Circuit Theory and Networks—Analysis and Synthesis

### Steps to be followed in Norton's Theorem

1. Remove the load resistance  $R_L$  and put a short circuit across the terminals.
2. Find the short-circuit current  $I_{SC}$  or  $I_N$ .
3. Find the resistance  $R_N$  as seen from points  $A$  and  $B$ .
4. Replace the network by a current source  $I_N$  in parallel with resistance  $R_N$ .
5. Find current through  $R_L$  by current-division rule.

$$I_L = \frac{I_N R_N}{R_N + R_L}$$

### Example 2.80

Find the current through the  $10\ \Omega$  resistor in Fig. 2.215.

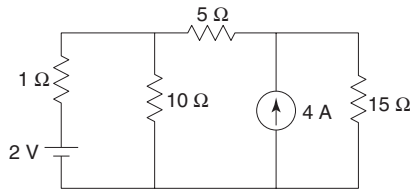


Fig. 2.215

### Solution

**Step I** Calculation of  $I_N$  (Fig. 2.216)

Applying KVL to Mesh 1,

$$2 - 1I_1 = 0$$

$$I_1 = 2$$

...(i)

Mesher 2 and 3 will form a supermesh.

Writing the current equation for the supermesh,

$$I_3 - I_2 = 4$$

...(ii)

Applying KVL to the supermesh,

$$-5I_2 - 15I_3 = 0$$

...(iii)

Solving Eqs (i), (ii) and (iii),

$$I_1 = 2\text{ A}$$

$$I_2 = -3\text{ A}$$

$$I_3 = 1\text{ A}$$

$$I_N = I_1 - I_2 = 2 - (-3) = 5\text{ A}$$

**Step II** Calculation of  $R_N$  (Fig. 2.217)

$$R_N = 1 \parallel (5 + 15) = 0.95\ \Omega$$

**Step III** Calculation of  $I_L$  (Fig. 2.218)

$$I_L = 5 \times \frac{0.95}{0.95 + 10} = 0.43\text{ A}$$

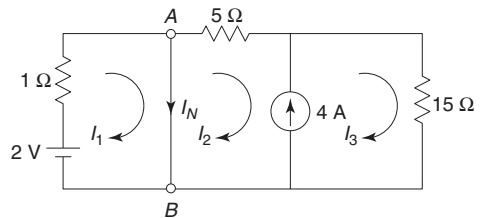


Fig. 2.216

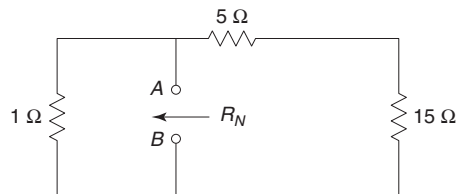


Fig. 2.217

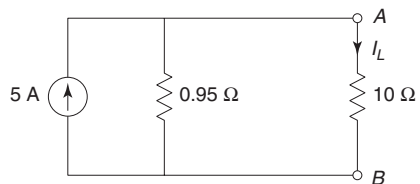
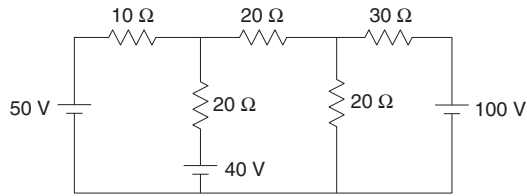


Fig. 2.218

**Example 2.81**Find the current through the  $10\ \Omega$  resistor in Fig. 2.219.**Fig. 2.219****Solution****Step I** Calculation of  $I_N$  (Fig. 2.220)

Applying KVL to Mesh 1,

$$\begin{aligned} 50 - 20(I_1 - I_2) - 40 &= 0 \\ 20I_1 - 20I_2 &= 10 \end{aligned} \quad \dots(i)$$

Applying KVL to Mesh 2,

$$\begin{aligned} 40 - 20(I_2 - I_1) - 20I_2 - 20(I_2 - I_3) &= 0 \\ -20I_1 + 60I_2 - 20I_3 &= 40 \quad \dots(ii) \end{aligned}$$

Applying KVL to Mesh 3,

$$\begin{aligned} -20(I_3 - I_2) - 30I_3 - 100 &= 0 \\ -20I_2 + 50I_3 &= -100 \quad \dots(iii) \end{aligned}$$


Solving Eqs (i), (ii) and (iii),

$$I_1 = 0.81\text{ A}$$


$$I_N = I_1 = 0.81\text{ A}$$

**Step II** Calculation of  $R_N$  (Fig. 2.221)

$$R_N = [(20 \parallel 30) + 20] \parallel 20 = 12.3\ \Omega$$

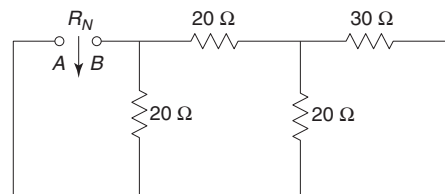**Fig. 2.221****Step III** Calculation of  $I_L$  (Fig. 2.222)

$$I_L = 0.81 \times \frac{12.3}{12.3 + 10} = 0.45\text{ A}$$

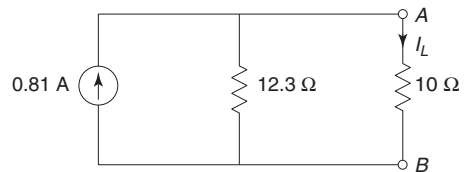**Fig. 2.222**

**Example 2.82** Find the current through the  $8\ \Omega$  resistor in Fig. 2.223.

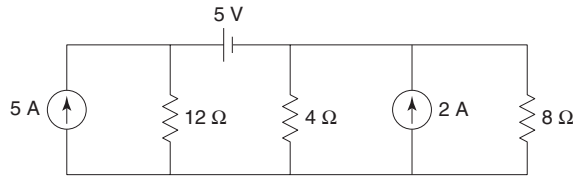


Fig. 2.223

**Solution**

**Step I** Calculation of  $I_N$  (Fig. 2.224)

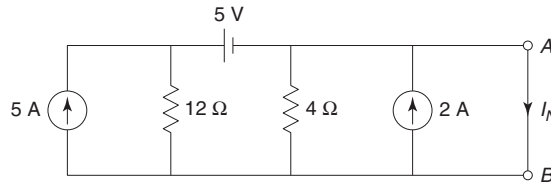


Fig. 2.224

The resistor of the  $4\ \Omega$  gets shorted as it is in parallel with the short circuit. Simplifying the network by source transformation (Fig. 2.225),

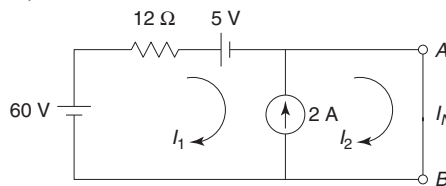


Fig. 2.225

Meshes 1 and 2 will form a supermesh.

Writing the current equation for the supermesh,

$$I_2 - I_1 = 2$$

Applying KVL to the supermesh,

$$60 - 12I_1 - 5 = 0$$

$$12I_1 = 55$$

Solving Eqs (i) and (ii),

$$I_1 = 4.58\text{ A}$$

$$I_2 = 6.58\text{ A}$$

$$I_N = I_2 = 6.58\text{ A}$$

**Step II** Calculation of  $R_N$  (Fig. 2.226)

$$R_N = 12 \parallel 4 = 3\ \Omega$$

**Step III** Calculation of  $I_L$  (Fig. 2.227)

$$I_L = 6.58 \times \frac{3}{3+8} = 1.79\text{ A}$$

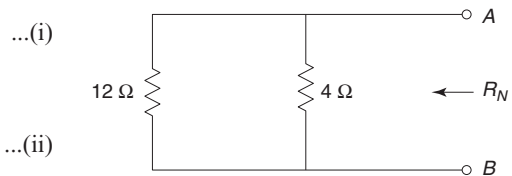


Fig. 2.226

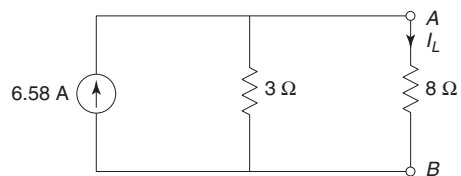
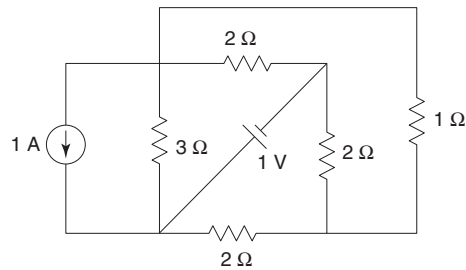
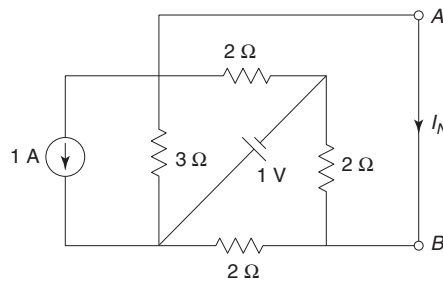
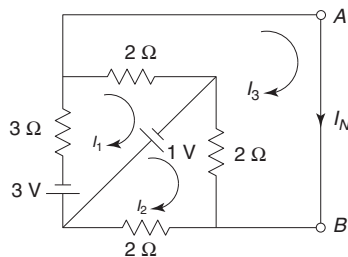


Fig. 2.227

**Example 2.83**Find the current through the  $1\ \Omega$  resistor in Fig. 2.228.**Fig. 2.228****Solution****Step I** Calculation of  $I_N$  (Fig. 2.229)**Fig. 2.229**

By source transformation (Fig. 2.230),

**Fig. 2.230**

Applying KVL to Mesh 1,

$$-3 - 3I_1 - 2(I_1 - I_3) + 1 = 0$$

$$5I_1 - 2I_3 = -2$$

...(i)

## 2.88 Circuit Theory and Networks—Analysis and Synthesis

Applying KVL to Mesh 2,

$$\begin{aligned} -1 - 2(I_2 - I_3) - 2I_2 &= 0 \\ 4I_2 - 2I_3 &= -1 \end{aligned} \quad \dots(\text{ii})$$

Applying KVL to Mesh 3,

$$\begin{aligned} -2(I_3 - I_1) - 2(I_3 - I_2) &= 0 \\ -2I_1 - 2I_2 + 4I_3 &= 0 \end{aligned} \quad \dots(\text{iii})$$

Solving Eqs (i), (ii) and (iii),


$$\begin{aligned} I_1 &= -0.64 \text{ A} \\ I_2 &= -0.55 \text{ A} \\ I_3 &= -0.59 \text{ A} \\ I_N = I_3 &= -0.59 \text{ A} \end{aligned}$$

**Step II** Calculation of  $R_N$  (Fig. 2.231)


$$R_N = 2.2 \Omega$$

**Step III** Calculation of  $I_L$  (Fig. 2.232)

$$I_L = 0.59 \times \frac{2.2}{2.2 + 1} = 0.41 \text{ A}$$

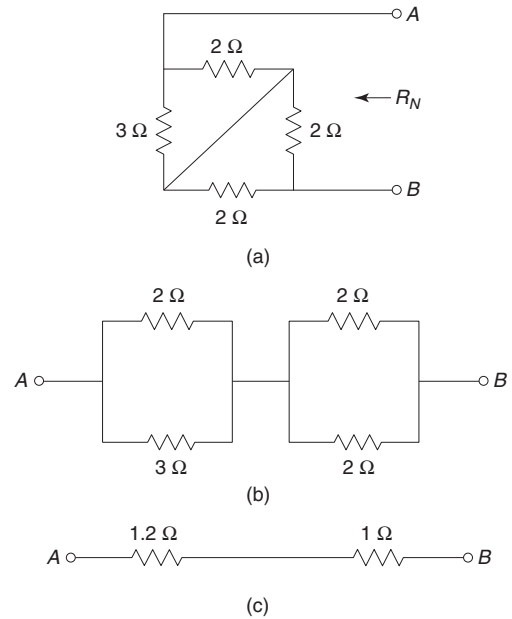


**Fig. 2.231**

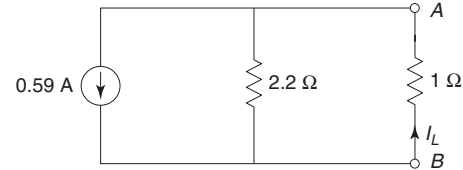

**Fig. 2.232**

## EXAMPLES WITH DEPENDENT SOURCES

**Example 2.84** Find Norton's equivalent network across terminals A and B of Fig. 2.233.

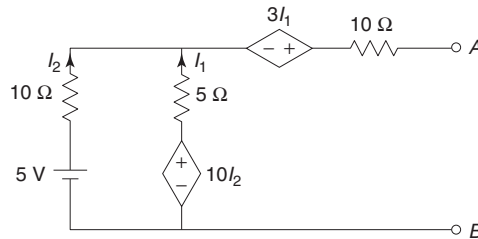

**Fig. 2.233**



**Solution****Step I** Calculation of  $V_{Th}$  (Fig. 2.234)

From Fig. 2.234,

$$I_2 = I_x$$

$$I_1 = -I_x$$

Applying KVL to the mesh,

$$5 - 10I_x - 5I_x - 10I_2 = 0$$

$$5 - 10I_x - 5I_x - 10I_x = 0$$

$$I_x = 0.2 \text{ A}$$

$$I_1 = -0.2 \text{ A}$$

Writing the  $V_{Th}$  equation,

$$5 - 10I_x + 3I_1 - V_{Th} = 0$$

$$5 - 10(0.2) + 3(-0.2) - V_{Th} = 0$$

$$V_{Th} = 2.4 \text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.235)

From Fig. 2.235,

$$I_2 = I_x \quad \dots(i)$$

$$I_1 = I_y - I_x \quad \dots(ii)$$

Applying KVL to Mesh 1,

$$5 - 10I_x - 5(I_x - I_y) - 10I_2 = 0$$

$$5 - 10I_x - 5I_x + 5I_y - 10I_x = 0$$

$$25I_x - 5I_y = 5 \quad \dots(iii)$$

Applying KVL to Mesh 2,

$$10I_2 - 5(I_y - I_x) + 3I_1 - 10I_y = 0$$

$$10I_x - 5I_y + 5I_x + 3(I_y - I_x) - 10I_y = 0$$

$$12I_x - 12I_y = 0 \quad \dots(iv)$$

Solving Eqs (iii) and (iv),




$$I_x = 0.25 \text{ A}$$

$$I_y = 0.25 \text{ A}$$

$$I_N = I_y = 0.25 \text{ A}$$

**Step III** Calculation of  $R_N$ 

$$R_N = \frac{V_{Th}}{I_N} = \frac{2.4}{0.25} = 9.6 \Omega$$

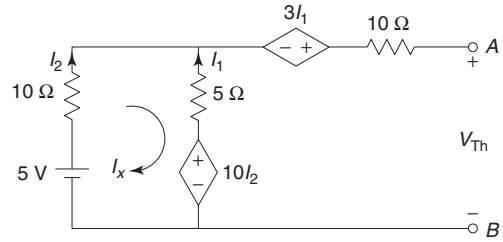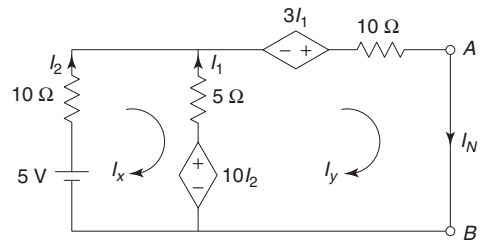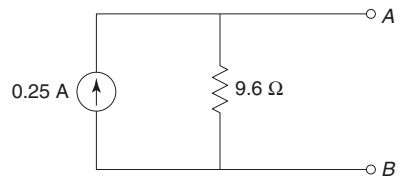**Step IV** Norton's Equivalent Network (Fig. 2.236)**Fig. 2.234****Fig. 2.235****Fig. 2.236**

**Example 2.85**

For the network shown in Fig. 2.237, find Norton's equivalent network.

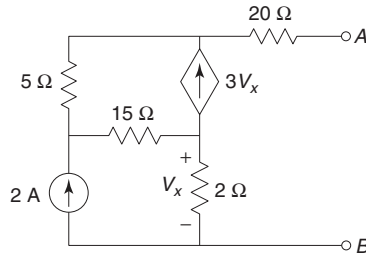


Fig. 2.237

**Solution**

**Step I** Calculation of  $V_{Th}$  (Fig. 2.238)

From Fig. 2.238,

$$V_x = 2I_2 \quad \dots(i)$$

For Mesh 1,

$$I_1 = -3V_x = -3(2I_2) = -6I_2 \quad \dots(ii)$$

For Mesh 2,

$$I_2 = 2 \quad \dots(iii)$$

$$I_1 = -6I_2 = -6(2) = -12 \text{ A}$$

Writing the  $V_{Th}$  equation,

$$V_{Th} - 0 + 5I_1 + 15(I_1 - I_2) - 2I_2 = 0$$

$$V_{Th} + 5(-12) + 15(-12 - 2) - 2(2) = 0$$

$$V_{Th} = 274 \text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.239)

From Fig. 2.239,

$$V_x = 2(I_2 - I_3) \quad \dots(i)$$

For Mesh 2,

$$I_2 = 2 \quad \dots(ii)$$

Mesches 1 and 3 will form a supermesh.

Writing the current equation for the supermesh,

$$I_3 - I_1 = 3V_x = 3[2(I_2 - I_3)] = 6I_2 - 6I_3$$

$$I_1 + 6I_2 - 7I_3 = 0 \quad \dots(iii)$$

Applying KVL to the outer path of the supermesh,

$$-5I_1 - 20I_3 - 2(I_3 - I_2) - 15(I_1 - I_2) = 0$$

$$-20I_1 + 17I_2 - 22I_3 = 0 \quad \dots(iv)$$

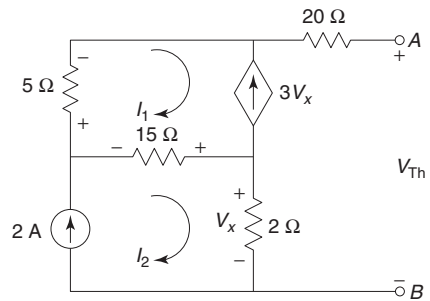


Fig. 2.238

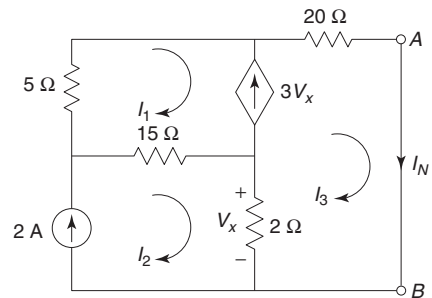


Fig. 2.239

Solving Eqs (ii), (iii) and (iv),

$$I_1 = -0.16 \text{ A}$$

$$I_2 = 2 \text{ A}$$


$$I_3 = 1.69 \text{ A}$$

$$I_N = I_3 = 1.69 \text{ A}$$

**Step III** Calculation of  $R_N$


$$R_N = \frac{V_{Th}}{I_N} = \frac{274}{1.69} = 162.13 \Omega$$

**Step IV** Norton's Equivalent Network (Fig. 2.240)

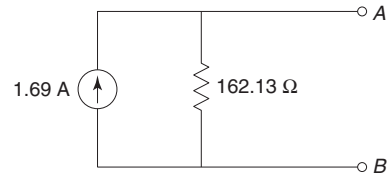

**Fig. 2.240**


**Example 2.86** Obtain Norton's equivalent network across A-B in the network of Fig. 2.241.

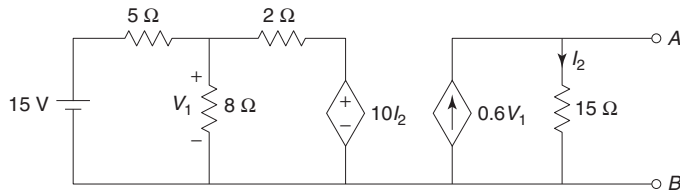

**Fig. 2.241**

**Solution**

**Step I** Calculation of  $V_{Th}$  (Fig. 2.242)

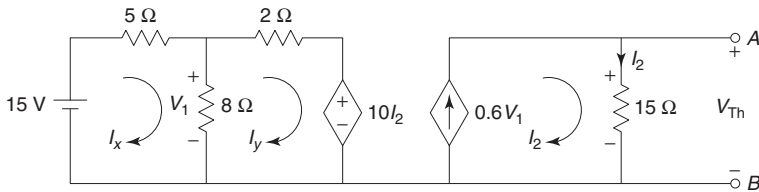

**Fig. 2.242**

From Fig. 2.242,

$$V_1 = 8(I_x - I_y) \quad \dots(i)$$

Applying KVL to Mesh 1,

$$15 - 5I_x - 8(I_x - I_y) = 0$$

$$13I_x - 8I_y = 15 \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$-8(I_y - I_x) - 2I_y - 10I_2 = 0$$

$$8I_x - 10I_y - 10I_2 = 0 \quad \dots(iii)$$

## 2.92 Circuit Theory and Networks—Analysis and Synthesis

For Mesh 3,

$$I_2 = 0.6V_1 = 0.6[8(I_x - I_y)]$$

$$4.8I_x - 4.8I_y - I_2 = 0 \quad \dots(\text{iv})$$

Solving Eqs (ii), (iii) and (iv),

$$I_x = 3.28 \text{ A}$$

$$I_y = 3.45 \text{ A}$$

$$I_2 = -0.83 \text{ A}$$

Writing the  $V_{\text{Th}}$  equation,

$$15I_2 - V_{\text{Th}} = 0$$

$$15(-0.83) - V_{\text{Th}} = 0$$

$$V_{\text{Th}} = -12.45 \text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.243)

From Fig. 2.243,

$$I_2 = 0$$

The dependent source of  $10I_2$  depends on the controlling variable  $I_2$ . When  $I_2 = 0$ , the dependent source vanishes, i.e.  $10I_2 = 0$  as shown in Fig. 2.244.

From Fig. 2.244,

$$V_1 = 8(I_x - I_y) \quad \dots(\text{i})$$

Applying KVL to Mesh 1,

$$15 - 5I_x - 8(I_x - I_y) = 0$$

$$13I_x - 8I_y = 15 \quad \dots(\text{ii})$$

Applying KVL to Mesh 2,

$$-8(I_y - I_x) - 2I_y = 0$$

$$-8I_x + 10I_y = 0 \quad \dots(\text{iii})$$

Solving Eqs (ii) and (iii),

$$I_x = 2.27 \text{ A}$$

$$I_y = 1.82 \text{ A}$$

$$V_1 = 8(I_x - I_y) = 8(2.27 - 1.82) = 3.6 \text{ V}$$

For Mesh 3,

$$I_N = 0.6V_1 = 0.6(3.6) = 2.16 \text{ A}$$

**Step III** Calculation of  $R_N$

$$R_N = \frac{V_{\text{Th}}}{I_N} = \frac{-12.45}{2.16} = -5.76 \Omega$$

**Step IV** Norton's Equivalent Network (Fig. 2.245)

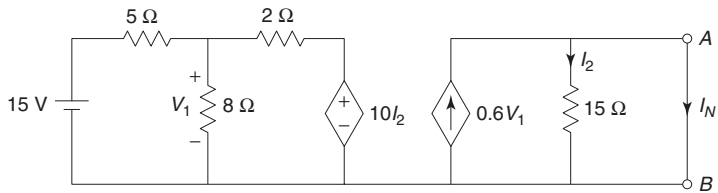


Fig. 2.243

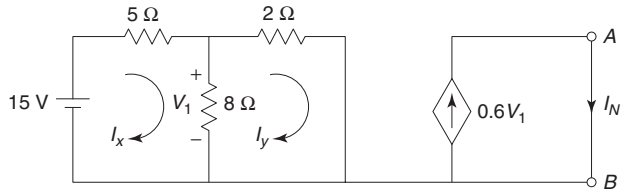


Fig. 2.244

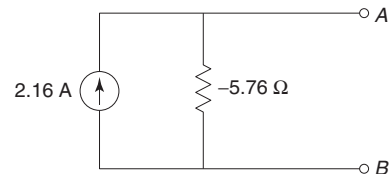
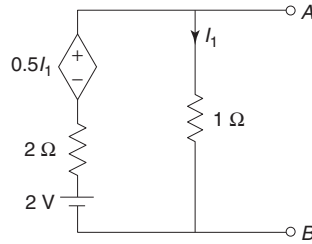


Fig. 2.245

**Example 2.87**

Find Norton's equivalent network of Fig. 2.246.

**Fig. 2.246****Solution****Step I** Calculation of  $V_{Th}$  (Fig. 2.247)

Applying KVL to the mesh,

$$2 - 2I_1 + 0.5I_1 - 1I_1 = 0$$

$$2 - 2.5I_1 = 0$$

$$I_1 = 0.8 \text{ A}$$

Writing the  $V_{Th}$  equation,

$$1I_1 - V_{Th} = 0$$

$$1(0.8) - V_{Th} = 0$$

$$V_{Th} = 0.8 \text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.248)When a short circuit is placed across the  $1 \Omega$  resistor, it gets shorted.





$$I_1 = 0$$

The dependent source of  $0.5I_1$  depends on the controlling variable  $I_1$ . When  $I_1 = 0$ , the dependent source vanishes, i.e.  $0.5I_1 = 0$  as shown in Fig. 2.249.

$$I_N = \frac{2}{2} = 1 \text{ A}$$


**Step III** Calculation of  $R_N$ 

$$R_N = \frac{V_{Th}}{I_N} = \frac{0.8}{1} = 0.8 \Omega$$

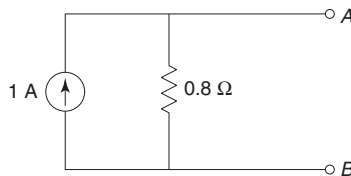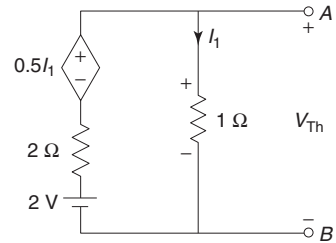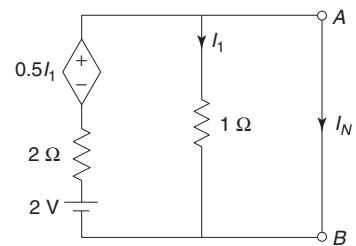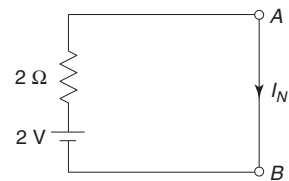**Step IV** Norton's Equivalent Network (Fig. 2.250)**Fig. 2.250****Fig. 2.247****Fig. 2.248****Fig. 2.249**

**Example 2.88**

Find Norton's equivalent network at the terminals A and B of Fig. 2.251.

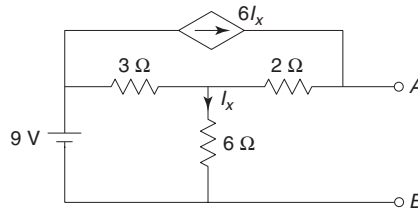**Fig. 2.251****Solution****Step I** Calculation of  $V_{Th}$  (Fig. 2.252)

From Fig. 2.252,

$$I_x = I_1 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$9 - 3(I_1 - I_2) - 6I_1 = 0$$

$$9I_1 - 3I_2 = 9 \quad \dots(ii)$$

For Mesh 2,

$$I_2 = 6I_x = 6I_1$$

$$6I_1 - I_2 = 0 \quad \dots(iii)$$

Solving Eqs (ii) and (iii),

$$I_1 = -1 \text{ A}$$

$$I_2 = -6 \text{ A}$$

Writing the  $V_{Th}$  equation,

$$9 - 3(I_1 - I_2) + 2I_2 - V_{Th} = 0$$

$$9 - 3(-1 + 6) + 2(-6) - V_{Th} = 0$$

$$V_{Th} = -18 \text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.253)

From Fig. 2.253,

$$I_x = I_1 - I_3 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$9 - 3(I_1 - I_2) - 6(I_1 - I_3) = 0$$

$$9I_1 - 3I_2 - 6I_3 = 9 \quad \dots(ii)$$

For Mesh 2,



$$I_2 = 6I_x = 6(I_1 - I_3)$$

$$6I_1 - I_2 - 6I_3 = 0 \quad \dots(iii)$$

Applying KVL to Mesh 3,

$$-6(I_3 - I_1) - 2(I_3 - I_2) = 0$$

$$-6I_1 - 2I_2 + 8I_3 = 0 \quad \dots(iv)$$

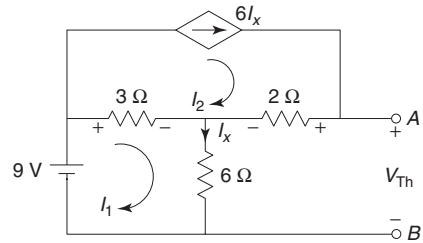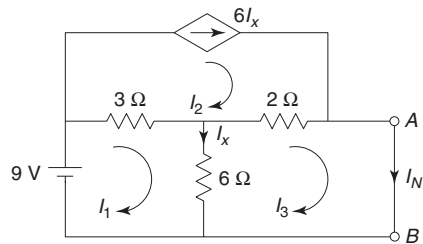**Fig. 2.252****Fig. 2.253**

Solving Eqs (ii), (iii) and (iv),

$$I_1 = 5 \text{ A}$$

$$I_2 = 3 \text{ A}$$

$$I_3 = 4.5 \text{ A}$$

$$I_N = I_3 = 4.5 \text{ A}$$

**Step III** Calculation of  $R_N$

$$R_N = \frac{V_{Th}}{I_N} = \frac{-18}{4.5} = -4 \Omega$$

**Step IV** Norton's Equivalent Network (Fig. 2.254)

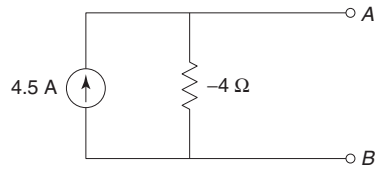


Fig. 2.254

**Example 2.89** Find Norton's equivalent network to the left of terminal A-B in Fig. 2.255.

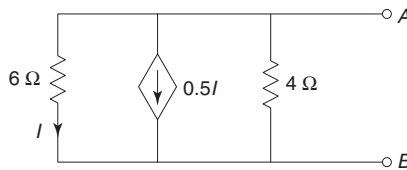


Fig. 2.255

**Solution** Since the network does not contain any independent source,

$$V_{Th} = 0$$

$$I_N = 0$$

But  $R_N$  can be calculated by applying a known current source of 1 A at the terminals A and B as shown in Fig. 2.256.

From Fig. 2.256,

$$I = \frac{V}{6}$$

Applying KCL at the node,

$$\frac{V}{6} + 0.5I + \frac{V}{4} = 1$$

$$\frac{V}{6} + 0.5\left(\frac{V}{6}\right) + \frac{V}{4} = 1$$

$$\left(\frac{1}{6} + \frac{0.5}{6} + \frac{1}{4}\right)V = 1$$

$$V = 2$$

$$R_N = \frac{V}{1} = \frac{2}{1} = 2 \Omega$$

Hence, Norton's equivalent network is shown in Fig. 2.257.

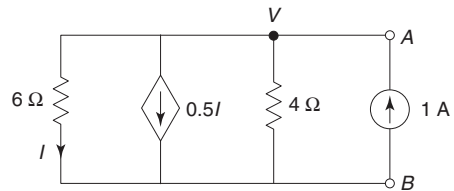


Fig. 2.256

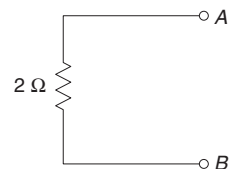


Fig. 2.257

**Example 2.90**

Find the current through the  $2\ \Omega$  resistor in the network shown in Fig. 2.258.

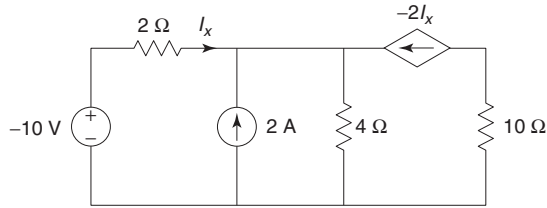


Fig. 2.258

**Solution**

**Step I** Calculation of  $V_{Th}$  (Fig. 2.259)

From Fig. 2.259,

$$I_x = 0$$

The dependent source of  $-2I_x$  depends on the controlling variable  $I_x$ . When  $I_x = 0$ , the dependent source vanishes, i.e.  $-2I_x = 0$  as shown in Fig. 2.260.

$$I_1 = 2$$

Writing the  $V_{Th}$  equation,

$$-10 - V_{Th} - 4I_1 = 0$$

$$-10 - V_{Th} - 4(2) = 0$$

$$V_{Th} = -18\text{ V}$$

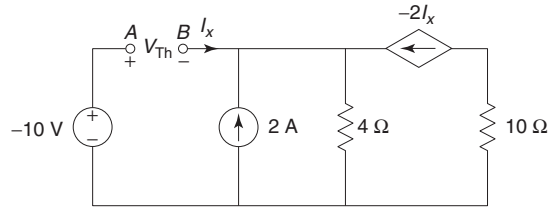


Fig. 2.259

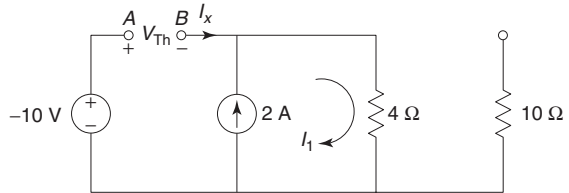


Fig. 2.260

**Step II** Calculation of  $I_N$  (Fig. 2.261)

From Fig. 2.261,

$$I_x = I_1 \quad \dots(i)$$

Mesh 1 and 2 will form a supermesh.

Writing the current equation for the supermesh,

$$I_2 - I_1 = 2 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$-10 - 4(I_2 - I_3) = 0$$

$$-4I_2 + 4I_3 = 10 \quad \dots(iii)$$

For Mesh 3,

$$I_3 = -(-2I_x) = 2I_x = 2I_1$$

$$2I_1 - I_3 = 0 \quad \dots(iv)$$

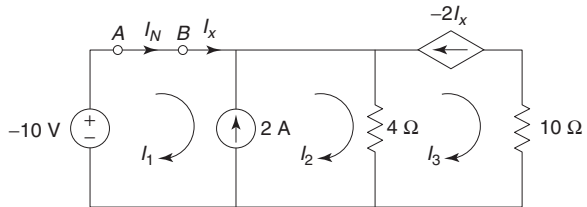


Fig. 2.261



Solving Eqs (ii), (iii) and (iv),

$$I_1 = 4.5 \text{ A}$$

$$I_2 = 6.5 \text{ A}$$

$$I_3 = 9 \text{ A}$$


$$I_N = I_1 = 4.5 \text{ A}$$

**Step III** Calculation of  $R_N$

$$R_N = \frac{V_{Th}}{I_N} = \frac{-18}{4.5} = -4 \Omega$$


**Step IV** Calculation of  $I_L$  (Fig. 2.262)

$$I_L = 4.5 \times \frac{-4}{-4 + 2} = 9 \text{ A}$$

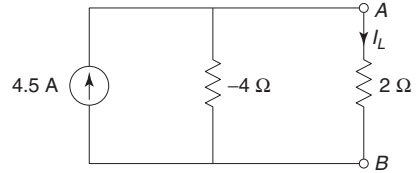

**Fig. 2.262**

**Example 2.91** Find the current through the  $2\Omega$  resistor in the network of Fig. 2.263.

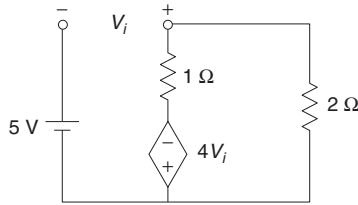

**Fig. 2.263**

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.264)

From Fig. 2.264,


$$5 + V_i + 4V_i = 0$$

$$V_i = -1 \text{ V}$$

Writing the  $V_{Th}$  equation,

$$-4V_i - V_{Th} = 0$$

$$V_{Th} = -4V_i = -4(-1) = 4 \text{ V}$$

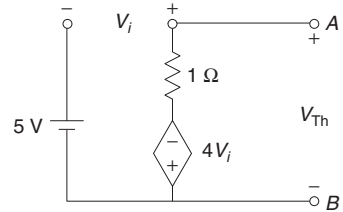

**Fig. 2.264**

**Step II** Calculation of  $I_N$  (Fig. 2.265)

From Fig. 2.265,


$$5 + V_i = 0$$

$$V_i = -5 \text{ V}$$

Applying KVL to the mesh,

$$-4V_i - 1I_N = 0$$

$$I_N = -4V_i = -4(-5) = 20 \text{ A}$$

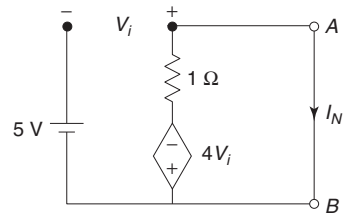

**Fig. 2.265**


## 2.98 Circuit Theory and Networks—Analysis and Synthesis

**Step III** Calculation of  $R_N$

$$R_N = \frac{V_{Th}}{I_N} = \frac{4}{20} = 0.2 \, \Omega$$

**Step IV** Calculation of  $I_L$  (Fig. 2.266)


$$I_L = 20 \times \frac{0.2}{0.2 + 2} = 1.82 \, \text{A}$$

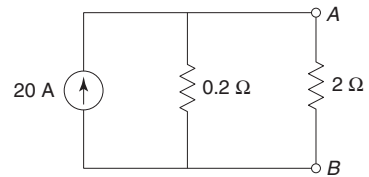

**Fig. 2.266**

### Example 2.92

Find the current in the  $2 \, \Omega$  resistor in the network of Fig. 2.267.

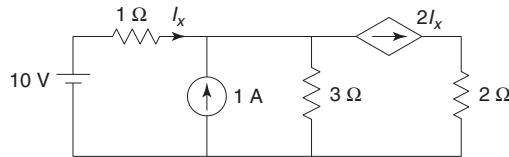

**Fig. 2.267**

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.268)

Mesches 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1 = 1 \quad \dots(i)$$

Applying KVL to the outer path of the supermesh,

$$10 - 1I_1 - 3I_2 = 0$$

$$I_1 + 3I_2 = 10 \quad \dots(ii)$$

Solving Eqs (i) and (ii),

$$I_1 = 1.75 \, \text{A}$$


$$I_2 = 2.75 \, \text{A}$$

Writing the  $V_{Th}$  equation,

$$3I_2 - V_{Th} = 0$$

$$3(2.75) - V_{Th} = 0$$

$$V_{Th} = 8.25 \, \text{V}$$

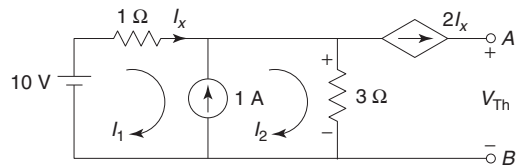

**Fig. 2.268**

**Step II** Calculation of  $I_N$  (Fig. 2.269)

From Fig. 2.269,

$$I_x = I_1 \quad \dots(i)$$


Mesches 1 and 2 will form a supermesh.

Writing the current equation for the supermesh,

$$I_2 - I_1 = 1 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$10 - 1I_1 - 3(I_2 - I_3) = 0$$

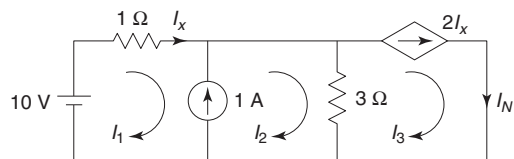

**Fig. 2.269**

$$I_1 + 3I_2 - 3I_3 = 10 \quad \dots(\text{iii})$$

For Mesh 3,

$$\begin{aligned} I_3 &= 2I_x = 2I_1 \\ 2I_1 - I_3 &= 0 \quad \dots(\text{iv}) \end{aligned}$$

Solving Eqs (ii), (iii) and (iv),

$$\begin{aligned} I_1 &= -3.5 \text{ A} \\ I_2 &= -2.5 \text{ A} \\ I_3 &= -7 \text{ A} \\ I_N = I_3 &= -7 \text{ A} \end{aligned}$$

**Step III** Calculation of  $R_N$

$$R_N = \frac{V_{Th}}{I_N} = \frac{8.25}{-7} = -1.18 \, \Omega$$

**Step IV** Calculation of  $I_L$  (Fig. 2.270)

$$I_L = -7 \times \frac{-1.18}{-1.18 + 2} = 10.07 \text{ A}$$

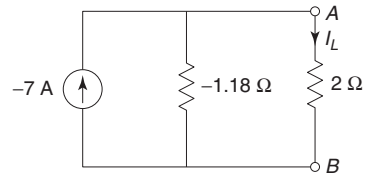


Fig. 2.270

### Example 2.93

Find the current through the  $10 \, \Omega$  resistor for the network of Fig. 2.271.

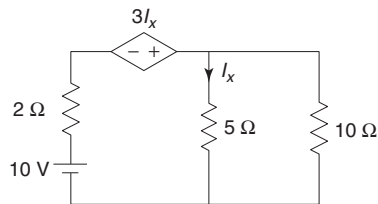


Fig. 2.271

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.272)

Applying KVL to the mesh,

$$\begin{aligned} 10 - 2I_x + 3I_x - 5I_x &= 0 \\ I_x &= 2.5 \text{ A} \end{aligned}$$

Writing the  $V_{Th}$  equation,

$$\begin{aligned} 5I_x - V_{Th} &= 0 \\ 5(2.5) - V_{Th} &= 0 \\ V_{Th} &= 12.5 \text{ V} \end{aligned}$$

**Step II** Calculation of  $I_N$  (Fig. 2.273)

From Fig. 2.273,

$$I_x = 0$$

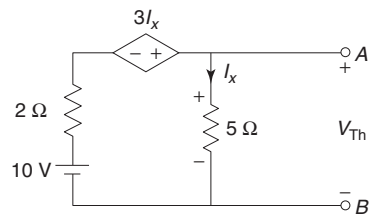


Fig. 2.272

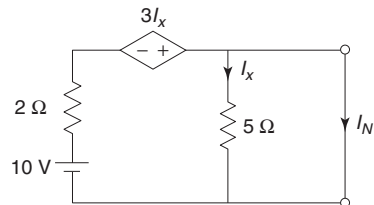


Fig. 2.273

## 2.100 Circuit Theory and Networks—Analysis and Synthesis

The dependent source of  $3 I_x$  depends on the controlling variable  $I_x$ . When  $I_x = 0$ , the dependent source  $3 I_x$  vanishes, i.e.  $3 I_x = 0$  as shown in Fig. 2.274.


$$I_N = \frac{10}{2} = 5 \text{ A}$$

**Step III** Calculation of  $R_N$


$$R_N = \frac{V_{Th}}{I_N} = \frac{12.5}{5} = 2.5 \Omega$$

**Step IV** Calculation of  $I_L$  (Fig. 2.275)

$$I_L = 5 \times \frac{2.5}{2.5 + 10} = 1 \text{ A}$$

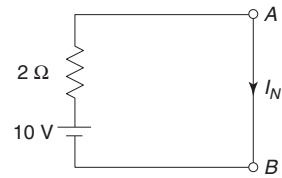


**Fig. 2.274**

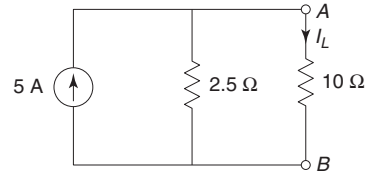

**Fig. 2.275**

### Example 2.94

Find the current through the  $5 \Omega$  resistor in the network of Fig. 2.276.

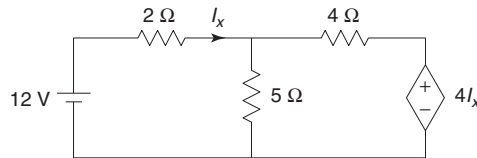

**Fig. 2.276**

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.277)

Applying KVL to the mesh,

$$\begin{aligned} 12 - 2I_x - 4I_x - 4I_x &= 0 \\ 12 - 10I_x &= 0 \\ I_x &= 1.2 \text{ A} \end{aligned}$$

Writing the  $V_{Th}$  equation,

$$\begin{aligned} 12 - 2I_x - V_{Th} &= 0 \\ 12 - 2(1.2) - V_{Th} &= 0 \\ V_{Th} &= 9.6 \text{ V} \end{aligned}$$

**Step II** Calculation of  $I_N$  (Fig. 2.278)

From Fig. 2.278,

$$I_x = I_1 \quad \dots(i)$$

Applying KVL to Mesh 1,


$$\begin{aligned} 12 - 2I_1 &= 0 \\ I_1 &= 6 \text{ A} \quad \dots(ii) \end{aligned}$$

Applying KVL to Mesh 2,


$$\begin{aligned} -4I_2 - 4I_x &= 0 \\ -4I_2 - 4I_1 &= 0 \quad \dots(iii) \end{aligned}$$

Solving Eqs (ii) and (iii),

$$\begin{aligned} I_2 &= -6 \text{ A} \\ I_N = I_1 - I_2 &= 6 - (-6) = 12 \text{ A} \end{aligned}$$

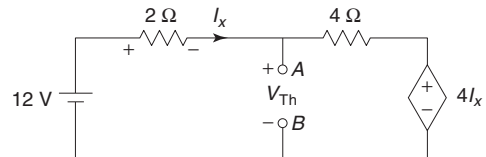

**Fig. 2.277**

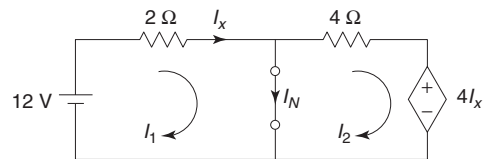

**Fig. 2.278**

**Step III** Calculation of  $R_N$

$$R_N = \frac{V_{Th}}{I_N} = \frac{9.6}{12} = 0.8 \, \Omega$$

**Step IV** Calculation of  $I_L$  (Fig. 2.279)

$$I_L = 12 \times \frac{0.8}{0.8 + 5} = 1.66 \, \text{A}$$

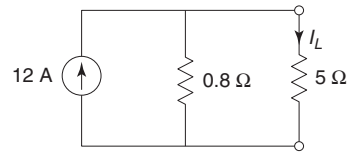


Fig. 2.279

### Example 2.95

Find the current through the  $10 \, \Omega$  resistor for the network of Fig. 2.280.

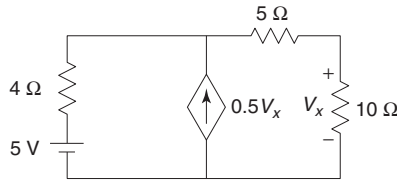


Fig. 2.280

**Solution**

**Step I** Calculation of  $V_{Th}$  (Fig. 2.281)

For the mesh,

$$I = -0.5V_x = -0.5V_{Th}$$

Writing the  $V_{Th}$  equation,

$$5 - 4I - 0 - V_{Th} = 0$$

$$5 - 4(-0.5V_{Th}) - V_{Th} = 0$$

$$V_{Th} = -5 \, \text{V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.282)

From Fig. 2.282,

$$V_x = 0$$

The dependent source of  $0.5 V_x$  depends on the controlling variable  $V_x$ . When  $V_x = 0$ , the dependent source vanishes, i.e.  $0.5 V_x = 0$  as shown in Fig. 2.283.

$$I_N = \frac{5}{4+5} = \frac{5}{9} \, \text{A}$$

**Step III** Calculation of  $R_N$

$$R_N = \frac{V_{Th}}{I_N} = \frac{-5}{\frac{5}{9}} = -9 \, \Omega$$

**Step IV** Calculation of  $I_L$  (Fig. 2.284)

$$I_L = \frac{5}{9} \times \frac{-9}{-9+10} = -5 \, \text{A}$$

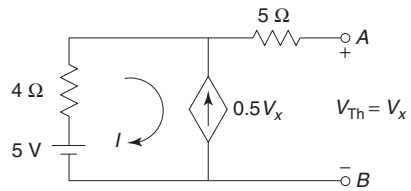


Fig. 2.281

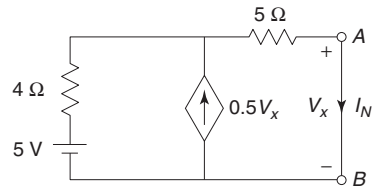


Fig. 2.282

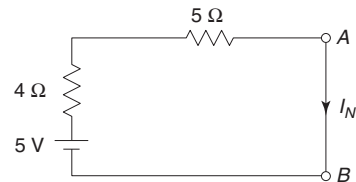


Fig. 2.283

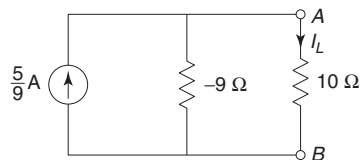


Fig. 2.284

**Example 2.96**

Find the current through the  $10\ \Omega$  resistor in the network shown in Fig. 2.285.

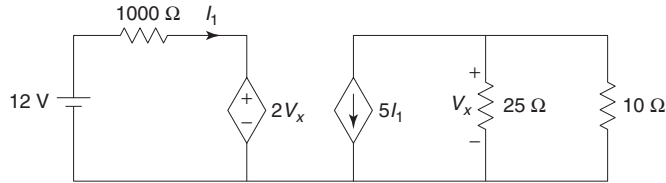


Fig. 2.285

**Solution**

**Step I** Calculation of  $V_{Th}$  (Fig. 2.286)

From Fig. 2.286,

$$V_x = -25(5I_1) = -125I_1 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$12 - 1000I_1 - 2V_x = 0$$

$$12 - 1000I_1 - 2(-125I_1) = 0 \quad \dots(ii)$$

$$I_1 = 0.016\text{ A}$$

$$V_x = -125I_1 = -125(0.016) = -2\text{ V}$$

Writing the  $V_{Th}$  equation,

$$V_{Th} = V_x = -2\text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.287)

From Fig. 2.287,

$$V_x = 0$$

The dependent source of  $2V_x$  depends on the controlling variable  $V_x$ . When  $V_x = 0$ , the dependent source vanishes, i.e.  $2V_x = 0$ , as shown in Fig. 2.288.

$$I_1 = \frac{12}{1000} = 0.012\text{ A}$$

$$I_N = -5I_1 = -5(0.012) = -0.06\text{ A}$$

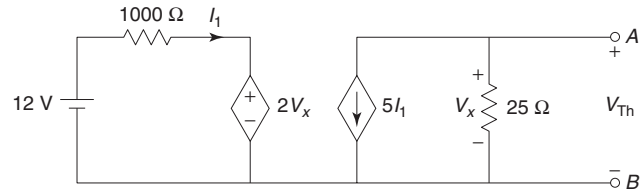


Fig. 2.286

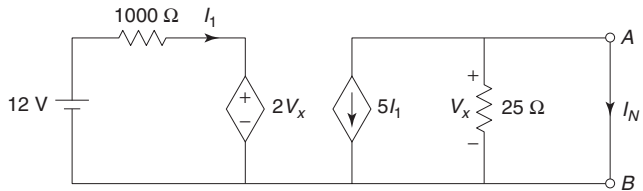


Fig. 2.287

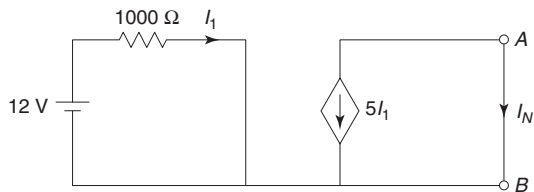


Fig. 2.288

**Step III** Calculation of  $R_N$

$$R_N = \frac{V_{Th}}{I_N} = \frac{-2}{-0.06} = 33.33\ \Omega$$

**Step IV** Calculation of  $I_L$  (Fig. 2.289)

$$I_L = -0.06 \times \frac{33.33}{33.33 + 10} = -0.046\text{ A}$$

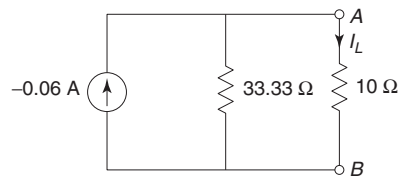
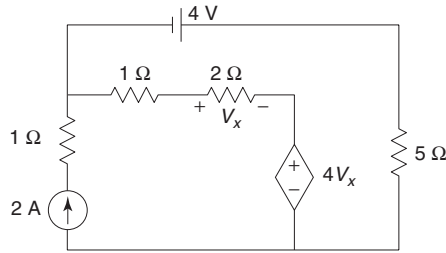


Fig. 2.289

**Example 2.97**Find the current through the  $5\ \Omega$  resistor for the network of Fig. 2.290.**Fig. 2.290****Solution****Step I** Calculation of  $V_{Th}$  (Fig. 2.291)

From Fig. 2.291,

$$V_x = 2I$$

For the mesh,

$$I = 2$$

$$V_x = 2(2) = 4\text{ V}$$

Writing the  $V_{Th}$  equation,

$$4V_x + 2I + 1I + 4 - V_{Th} = 0$$

$$4(4) + 2(2) + 2 + 4 - V_{Th} = 0$$

$$V_{Th} = 26\text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.292)

From Fig. 2.292,

$$V_x = 2(I_1 - I_2)$$

For Mesh 1,

$$I_1 = 2$$

Applying KVL to Mesh 2,

$$4V_x - 2(I_2 - I_1) - 1(I_2 - I_1) + 4 = 0$$

$$4[2(I_1 - I_2)] - 2I_2 + 2I_1 - I_2 + I_1 + 4 = 0$$

$$11I_1 - 11I_2 = -4$$

Solving Eqs (ii) and (iii),

$$I_1 = 2\text{ A}$$

$$I_2 = 2.36\text{ A}$$




$$I_N = I_2 = 2.36\text{ A}$$

**Step III** Calculation of  $R_N$ 

$$R_N = \frac{V_{Th}}{I_N} = \frac{26}{2.36} = 11.02\ \Omega$$

**Step IV** Calculation of  $I_L$  (Fig. 2.293)

$$I_L = 2.36 \times \frac{11.02}{11.02 + 5} = 1.62\text{ A}$$

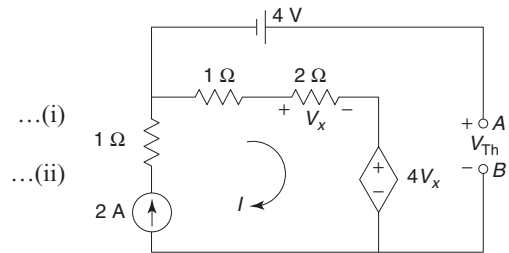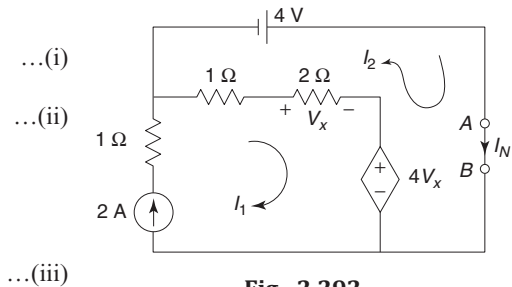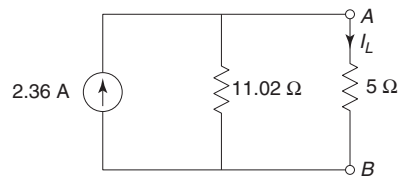**Fig. 2.291****Fig. 2.292****Fig. 2.293**

**Example 2.98**

Find the current through the  $1\ \Omega$  resistor in the network of Fig. 2.294.

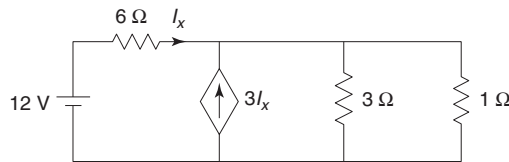


Fig. 2.294

**Solution**

**Step I** Calculation of  $V_{Th}$  (Fig. 2.295)

From Fig. 2.295,

$$I_x = I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh.

Writing the current equation for the supermesh,

$$I_2 - I_1 = 3I_x = 3I_1$$

$$4I_1 - I_2 = 0 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$12 - 6I_1 - 3I_2 = 0$$

$$6I_1 + 3I_2 = 12 \quad \dots(iii)$$

Solving Eqs (ii) and (iii),

$$I_1 = 0.67\text{ A}$$

$$I_2 = 2.67\text{ A}$$

Writing the  $V_{Th}$  equation,

$$3I_2 - V_{Th} = 0$$

$$3(2.67) - V_{Th} = 0$$

$$V_{Th} = 8\text{ V}$$

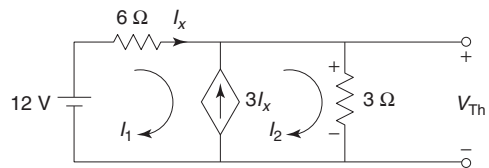


Fig. 2.295

**Step II** Calculation of  $I_N$  (Fig. 2.296)

When a short circuit is placed across a  $3\ \Omega$  resistor, it gets shorted as shown in Fig. 2.297.

From Fig. 2.297,

$$I_x = I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh.

Writing the current equation for the supermesh,

$$I_2 - I_1 = 3I_x = 3I_1$$

$$4I_1 - I_2 = 0 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$12 - 6I_1 = 0$$

$$I_1 = 2 \quad \dots(iii)$$

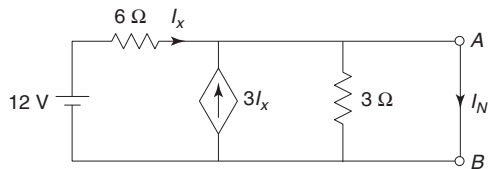


Fig. 2.296

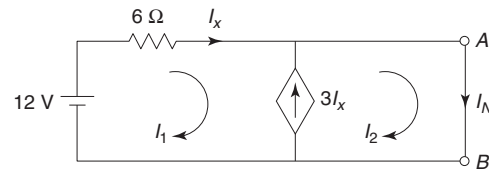


Fig. 2.297



Solving Eqs (ii) and (iii),

$$I_1 = 2 \text{ A}$$

$$I_2 = 8 \text{ A}$$


$$I_N = I_2 = 8 \text{ A}$$

**Step III** Calculation of  $R_N$

$$R_N = \frac{V_{Th}}{I_N} = \frac{8}{8} = 1 \Omega$$

**Step IV** Calculation of  $I_L$  (Fig. 2.298)


$$I_L = 8 \times \frac{1}{1+1} = 4 \text{ A}$$

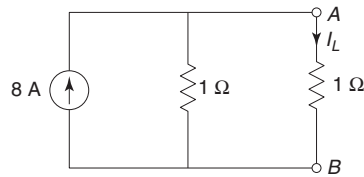

**Fig. 2.298**

### Example 2.99

Find the current through the  $1.6 \Omega$  resistor in the network of Fig. 2.299.

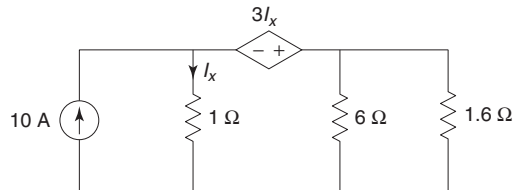

**Fig. 2.299**

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.300)

From Fig. 2.300,

$$I_x = I_1 - I_2 \dots (i)$$

For Mesh 1,

$$I_1 = 10 \dots (ii)$$

Applying KVL to Mesh 2,

$$-1(I_2 - I_1) + 3I_x - 6I_2 = 0$$

$$-I_2 + I_1 + 3(I_1 - I_2) - 6I_2 = 0$$

$$4I_1 - 10I_2 = 0$$

$\dots (iii)$

Solving Eqs (ii) and (iii),

$$I_1 = 10 \text{ A}$$


$$I_2 = 4 \text{ A}$$

Writing the  $V_{Th}$  equation,

$$6I_2 - V_{Th} = 0$$

$$6(4) - V_{Th} = 0$$

$$V_{Th} = 24 \text{ V}$$

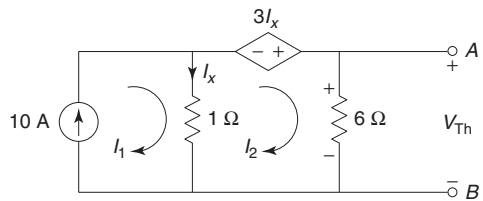

**Fig. 2.300**

## 2.106 Circuit Theory and Networks—Analysis and Synthesis

**Step II** Calculation of  $I_N$  (Fig. 2.301)

When a short circuit is placed across the  $3\ \Omega$  resistor, it gets shorted as shown in Fig. 2.302.

From Fig. 2.302,

$$I_x = I_1 - I_2 \quad \dots(i)$$

For Mesh 1,

$$I_1 = 10 \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$-1(I_2 - I_1) + 3I_x = 0$$

$$-I_2 + I_1 + 3(I_1 - I_2) = 0$$

$$4I_1 - 4I_2 = 0 \quad \dots(iii)$$

Solving Eqs (ii) and (iii),

$$I_1 = 10\text{ A}$$

$$I_2 = 10\text{ A}$$


$$I_N = I_2 = 10\text{ A}$$

**Step III** Calculation of  $R_N$


$$R_N = \frac{V_{Th}}{I_N} = \frac{24}{10} = 2.4\ \Omega$$

**Step IV** Calculation of  $I_L$  (Fig. 2.303)


$$I_L = 10 \times \frac{2.4}{2.4 + 1.6} = 6\text{ A}$$

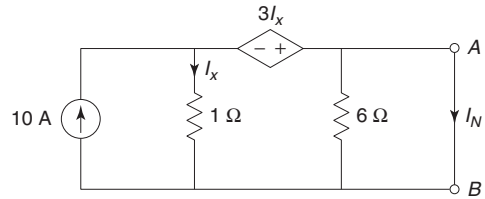

**Fig. 2.301**

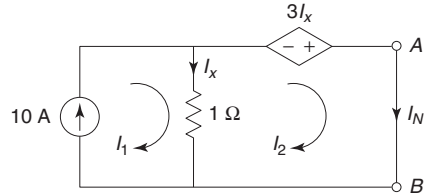

**Fig. 2.302**

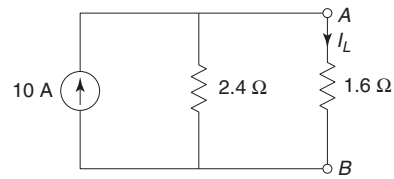

**Fig. 2.303**

## 2.10 || MAXIMUM POWER TRANSFER THEOREM

It states that ‘the maximum power is delivered from a source to a load when the load resistance is equal to the source resistance.’


**Proof** From Fig. 2.304,

$$I = \frac{V}{R_s + R_L}$$

$$\text{Power delivered to the load } R_L = P = I^2 R_L = \frac{V^2 R_L}{(R_s + R_L)^2}$$

To determine the value of  $R_L$  for maximum power to be transferred to the load,

$$\begin{aligned} \frac{dP}{dR_L} &= 0 \\ \frac{dP}{dR_L} &= \frac{d}{dR_L} \frac{V^2 R_L}{(R_s + R_L)^2} R_L \\ &= \frac{V^2 [(R_s + R_L)^2 - (2R_L)(R_s + R_L)]}{(R_s + R_L)^4} \end{aligned}$$

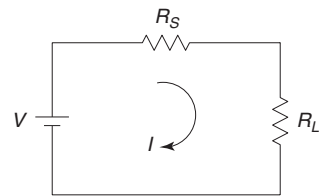

**Fig. 2.304** Network illustrating maximum power transfer theorem

$$(R_s + R_L)^2 - 2 R_L (R_s + R_L) = 0$$


$$R_s^2 + R_L^2 + 2 R_s R_L - 2 R_L R_s - 2 R_L^2 = 0$$

$$R_s = R_L$$

Hence, the maximum power will be transferred to the load when load resistance is equal to the source resistance.

**Steps to be followed in Maximum Power Transfer Theorem**

1. Remove the variable load resistor  $R_L$ .
2. Find the open circuit voltage  $V_{Th}$  across points  $A$  and  $B$ .
3. Find the resistance  $R_{Th}$  as seen from points  $A$  and  $B$ .
4. Find the resistance  $R_L$  for maximum power transfer.

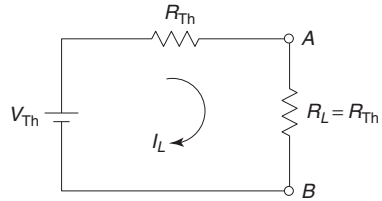

**Fig. 2.305** Thevenin's equivalent network


$$R_L = R_{Th}$$

5. Find the maximum power (Fig. 2.305).

$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{V_{Th}}{2R_{Th}}$$

$$P_{max} = I_L^2 R_L = \frac{V_{Th}^2}{4R_{Th}^2} \times R_{Th} = \frac{V_{Th}^2}{4R_{Th}}$$

**Example 2.100** For the value of resistance  $R_L$  in Fig. 2.306 for maximum power transfer and calculate the maximum power.

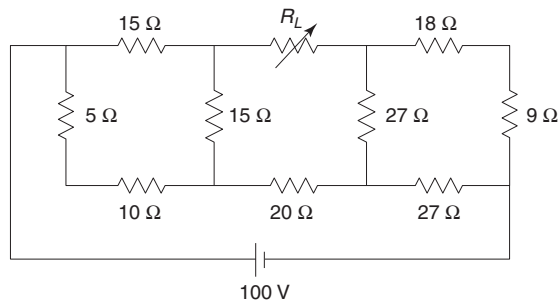

**Fig. 2.306**

## 2.108 Circuit Theory and Networks—Analysis and Synthesis

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.307)

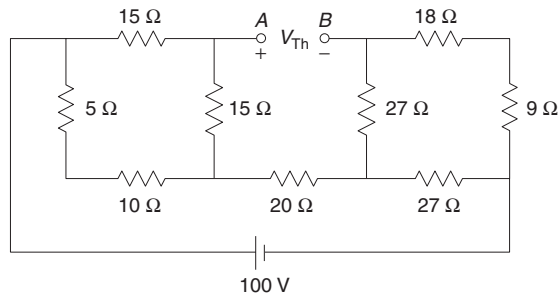


Fig. 2.307

By star-delta transformation (Fig. 2.308),

$$I = \frac{100}{5 + 5 + 20 + 9 + 9} = 2.08 \text{ A}$$

Writing the  $V_{Th}$  equation,

$$\begin{aligned} 100 - 5I - V_{Th} - 9I &= 0 \\ V_{Th} &= 100 - 14I \\ &= 100 - 14(2.08) \\ &= 70.88 \text{ V} \end{aligned}$$



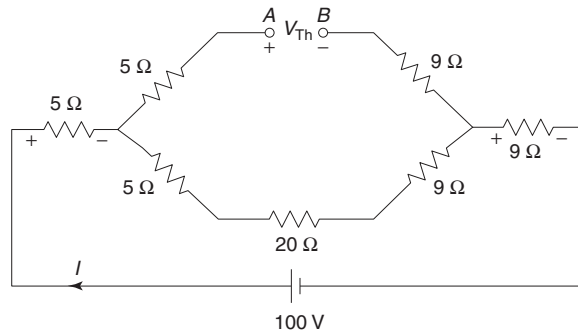


Fig. 2.308

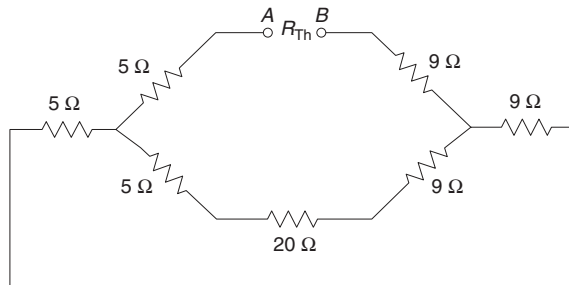
**Step II** Calculation of  $R_{Th}$  (Fig. 2.309)




(a)

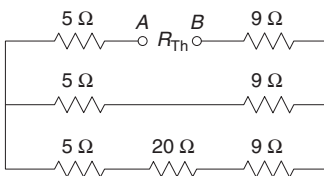

(b)

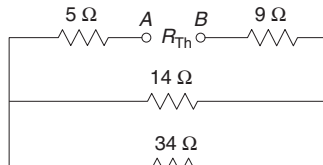

(c)

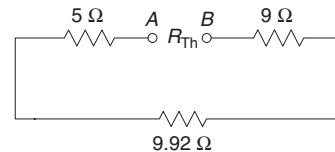

(d)

Fig. 2.309

$$R_{Th} = 23.92 \, \Omega$$

**Step III** Calculation of  $R_L$   
For maximum power transfer,

$$R_L = R_{Th} = 23.92 \, \Omega$$

**Step IV** Calculation of  $P_{max}$  (Fig. 2.310)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(70.88)^2}{4 \times 23.92} = 52.51 \, \text{W}$$

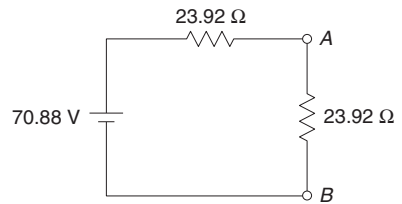


Fig. 2.310

**Example 2.101** For the value of resistance  $R_L$  in Fig. 2.311 for maximum power transfer and calculate the maximum power.

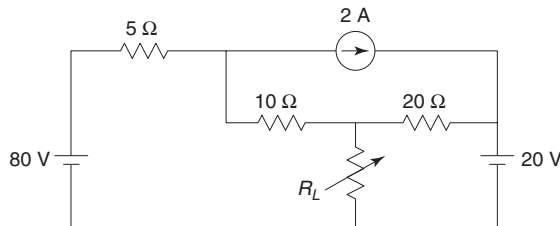


Fig. 2.311

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.312)

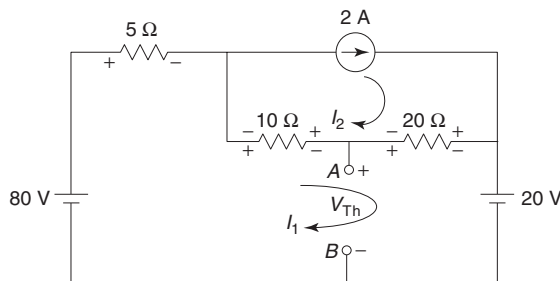


Fig. 2.312

Applying KVL to Mesh 1,

$$\begin{aligned} 80 - 5I_1 - 10(I_1 - I_2) - 20(I_1 - I_2) - 20 &= 0 \\ 35I_1 - 30I_2 &= 60 \end{aligned}$$

...(i)

Writing the current equation for Mesh 2,

$$I_2 = 2$$

...(ii)

### 2.110 Circuit Theory and Networks—Analysis and Synthesis

Solving Eqs (i) and (ii),

$$I_1 = 3.43 \text{ A}$$

Writing the  $V_{Th}$  equation,

$$V_{Th} - 20(I_1 - I_2) - 20 = 0$$

$$V_{Th} = 20(3.43 - 2) + 20 = 48.6 \text{ V}$$

**Step II** Calculation of  $R_{Th}$  (Fig. 2.313)

$$R_{Th} = 15 \parallel 20 = 8.57 \Omega$$

**Step III** Calculation of  $R_L$

For maximum power transfer,

$$R_L = R_{Th} = 8.57 \Omega$$

**Step IV** Calculation of  $P_{max}$  (Fig. 2.314)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(48.6)^2}{4 \times 8.57} = 68.9 \text{ W}$$

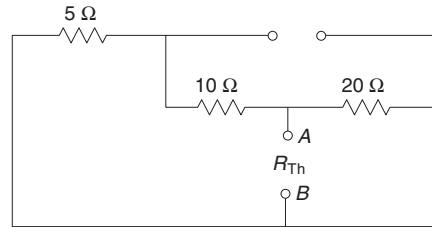


Fig. 2.313

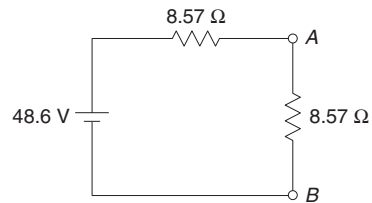


Fig. 2.314

**Example 2.102** For the value of resistance  $R_L$  in Fig. 2.315 for maximum power transfer and calculate the maximum power.

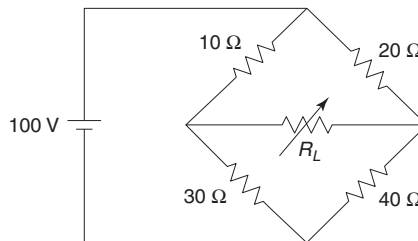


Fig. 2.315

**Solution**

**Step I** Calculation of  $V_{Th}$  (Fig. 2.316)

$$I_1 = \frac{100}{10 + 30} = 2.5 \text{ A}$$

$$I_2 = \frac{100}{20 + 40} = 1.66 \text{ A}$$

Writing the  $V_{Th}$  equation,

$$V_{Th} + 10I_1 - 20I_2 = 0$$

$$V_{Th} = 20I_2 - 10I_1 = 20(1.66) - 10(2.5) = 8.2 \text{ V}$$


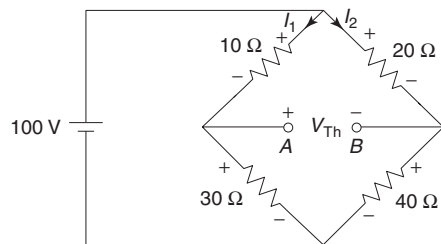


Fig. 2.316


**Step II** Calculation of  $R_{Th}$  (Fig. 2.317)

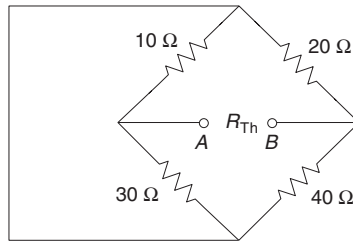

**Fig. 2.317**

Redrawing the network (Fig. 2.318),

$$R_{Th} = (10 \parallel 30) + (20 \parallel 40) = 20.83 \Omega$$

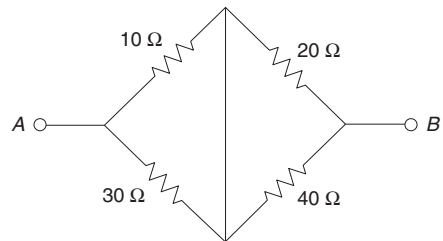

**Fig. 2.318**


**Step III** Value of  $R_L$

For maximum power transfer,

$$R_L = R_{Th} = 20.83 \Omega$$

**Step IV** Calculation of  $P_{max}$  (Fig. 2.319)


$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(8.2)^2}{4 \times 20.83} = 0.81 \text{ W}$$

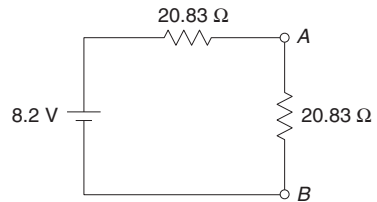

**Fig. 2.319**

### Example 2.103

For the value of resistance  $R_L$  in Fig. 2.320 for maximum power transfer and calculate the maximum power.

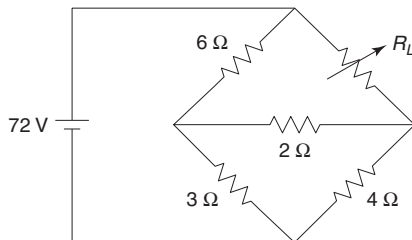

**Fig. 2.320**

## 2.112 Circuit Theory and Networks—Analysis and Synthesis

### Solution

**Step I** Calculation of  $V_{Th}$  (Fig. 2.321)

Applying KVL to Mesh 1,

$$\begin{aligned} 72 - 6I_1 - 3(I_1 - I_2) &= 0 \\ 9I_1 - 3I_2 &= 72 \dots (i) \end{aligned}$$

Applying KVL to Mesh 2,

$$\begin{aligned} -3(I_2 - I_1) - 2I_2 - 4I_2 &= 0 \\ -3I_1 + 9I_2 &= 0 \dots (ii) \end{aligned}$$

Solving Eqs (i) and (ii),

$$I_1 = 9 \text{ A}$$

$$I_2 = 3 \text{ A}$$

Writing the  $V_{Th}$  equation,

$$\begin{aligned} V_{Th} - 6I_1 - 2I_2 &= 0 \\ V_{Th} &= 6I_1 + 2I_2 = 6(9) + 2(3) = 60 \text{ V} \end{aligned}$$

**Step II** Calculation of  $R_{Th}$  (Fig. 2.322)

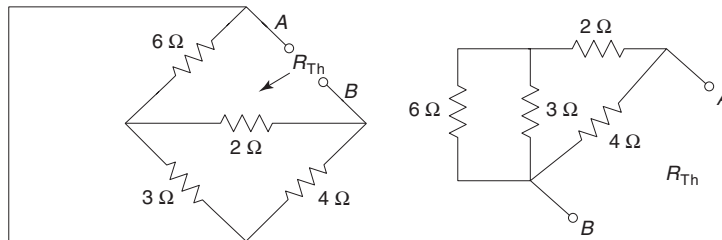


Fig. 2.322

$$R_{Th} = [(6 \parallel 3) + 2] \parallel 4 = 2 \Omega$$

**Step III** Calculation of  $R_L$

For maximum power transfer,

$$R_L = R_{Th} = 2 \Omega$$

**Step IV** Calculation of  $P_{max}$  (Fig. 2.323)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(60)^2}{4 \times 2} = 450 \text{ W}$$

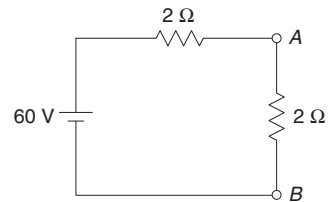


Fig. 2.323

## EXAMPLES WITH DEPENDENT SOURCES

**Example 2.104** For the network shown in Fig. 2.324, find the value of  $R_L$  for maximum power transfer. Also, calculate maximum power.



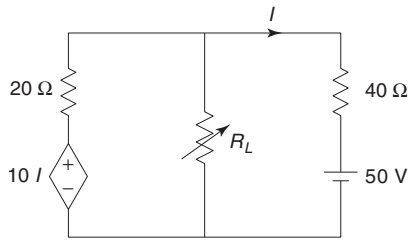


Fig. 2.324

**Solution****Step I** Calculation of  $V_{Th}$  (Fig. 2.325)

Applying KVL to the mesh,

$$10I - 20I - 40I - 50 = 0$$

$$I = -1 \text{ A}$$

Writing the  $V_{Th}$  equation,

$$V_{Th} - 40I - 50 = 0$$

$$V_{Th} - 40(-1) - 50 = 0$$

$$V_{Th} = 10 \text{ V}$$

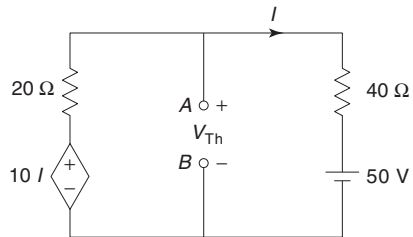


Fig. 2.325

**Step II** Calculation of  $I_N$  (Fig. 2.326)

From Fig. 2.326,

$$I = I_2 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$10I - 20I_1 = 0$$

$$10I_2 - 20I_1 = 0 \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$-40I_2 - 50 = 0$$

$$I_2 = -1.25 \text{ A}$$

$$\dots(iii)$$

Solving Eqs (i), (ii) and (iii),

$$I_1 = -0.625 \text{ A}$$

$$I_N = I_1 - I_2 = -0.625 + 1.25 = 0.625 \text{ A}$$

**Step III** Calculation of  $R_N$ 

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{10}{0.625} = 16 \Omega$$

**Step IV** Calculation of  $R_L$ 

For maximum power transfer,

$$R_L = R_{Th} = 16 \Omega$$

**Step V** Calculation of  $P_{max}$  (Fig. 2.327)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(10)^2}{4 \times 16} = 1.56 \text{ W}$$

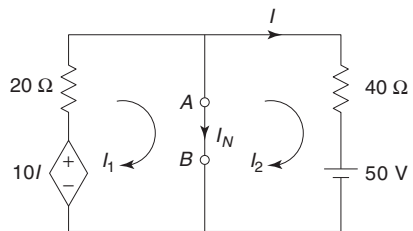


Fig. 2.326

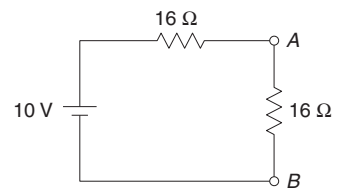


Fig. 2.327

**Example 2.105** For the network shown in Fig. 2.328, calculate the maximum power that may be dissipated in the load resistor  $R_L$ .

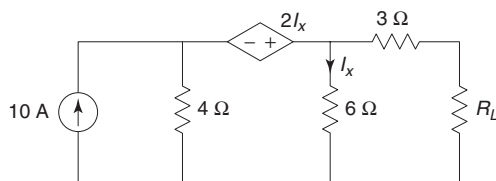


Fig. 2.328

**Solution**

**Step I** Calculation of  $V_{Th}$  (Fig. 2.329)

From Fig. 2.329,

$$I_x = I_2$$

For Mesh 1,

$$I_1 = 10$$

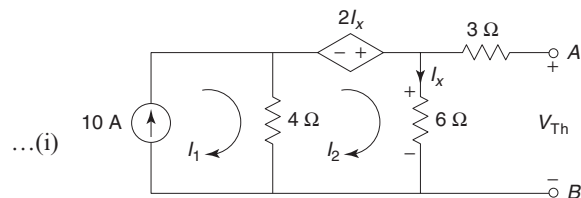


Fig. 2.329

Applying KVL to Mesh 2,

$$-4(I_2 - I_1) + 2I_x - 6I_2 = 0$$

$$-4I_2 + 4I_1 + 2I_2 - 6I_2 = 0$$

$$4I_1 - 8I_2 = 0$$

...(iii)

Solving Eqs (ii) and (iii),

$$I_1 = 10 \text{ A}$$

$$I_2 = 5 \text{ A}$$

Writing the  $V_{Th}$  equation,

$$6I_2 - 0 - V_{Th} = 0$$

$$V_{Th} = 6I_2 = 6(5) = 30 \text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.330)

From Fig. 2.330,

$$I_x = I_2 - I_3$$

For Mesh 1,

$$I_1 = 10$$

Applying KVL to Mesh 2,

$$-4(I_2 - I_1) + 2I_x - 6(I_2 - I_3) = 0$$

$$-4I_2 + 4I_1 + 2(I_2 - I_3) - 6I_2 + 6I_3 = 0$$

$$4I_1 - 8I_2 + 4I_3 = 0$$

...(iii)

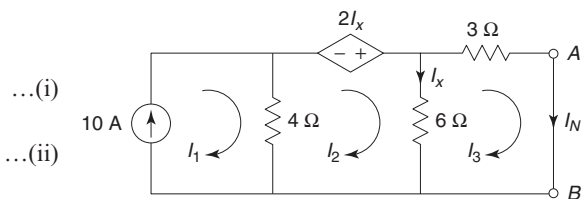


Fig. 2.330

Applying KVL to Mesh 3,

$$-6(I_3 - I_2) - 3I_3 = 0$$

$$6I_2 - 9I_3 = 0$$

...(iv)

Solving Eqs (ii), (iii) and (iv),

$$I_1 = 10 \text{ A}$$

$$I_2 = 7.5 \text{ A}$$

$$I_3 = 5 \text{ A}$$

$$I_N = I_3 = 5 \text{ A}$$

**Step III** Calculation of  $R_{Th}$


$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{30}{5} = 6 \Omega$$

**Step IV** Calculation of  $R_L$   
For maximum power transfer,

$$R_L = R_{Th} = 6 \Omega$$


**Step V** Calculation of  $P_{max}$  (Fig. 2.331)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(30)^2}{4 \times 16} = 37.5 \text{ W}$$

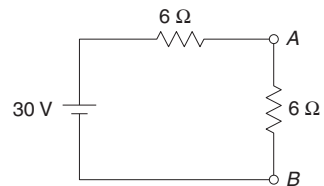

**Fig. 2.331**

**Example 2.106** For the network shown in Fig. 2.332, find the value of  $R_L$  for maximum power transfer. Also, find maximum power.

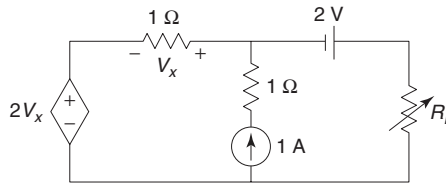

**Fig. 2.332**

**Solution**

**Step I** Calculation of  $V_{Th}$  (Fig. 2.333)


From Fig. 2.333,

$$V_x = -1I = -I \quad \dots(i)$$

For Mesh 1,

$$I = -1 \quad \dots(ii)$$

$$V_x = 1 \text{ V}$$

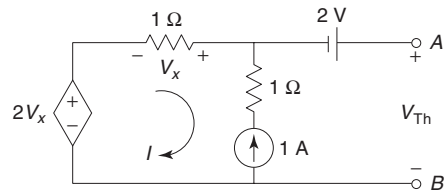

**Fig. 2.333**

## 2.116 Circuit Theory and Networks—Analysis and Synthesis

Writing the  $V_{Th}$  equation,

$$2V_x - 1I + 2 - V_{Th} = 0$$

$$2(1) - (-1) + 2 - V_{Th} = 0$$

$$V_{Th} = 5 \text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.334)

From Fig. 2.334,

$$V_x = -1I_1 = -I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh.

Writing the current equation for the supermesh,

$$I_2 - I_1 = 1 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$2V_x - 1I_1 + 2 = 0$$

$$2(-I_1) - I_1 + 2 = 0$$

$$3I_1 = 0$$

...(iii)

Solving Eqs (ii) and (iii),

$$I_1 = 0.67 \text{ A}$$

$$I_2 = 1.67 \text{ A}$$

$$I_N = I_2 = 1.67 \text{ A}$$

**Step III** Calculation of  $R_{Th}$

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{5}{1.67} = 3 \Omega$$

**Step IV** Calculation of  $R_L$

For maximum power transfer,

$$R_L = R_{Th} = 3 \Omega$$

**Step V** Calculation of  $P_{max}$  (Fig. 2.335)

$$P_{max} = \frac{V_{Th}^2}{4 R_{Th}} = \frac{(5)^2}{4 \times 3} = 2.08 \text{ W}$$

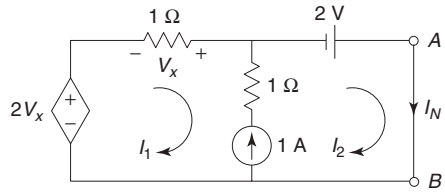


Fig. 2.334

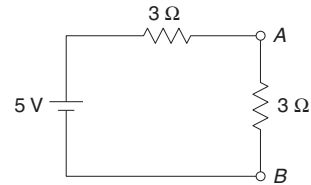


Fig. 2.335

**Example 2.107** What will be the value of  $R_L$  in Fig. 2.336 to get maximum power delivered to it? What is the value of this power?

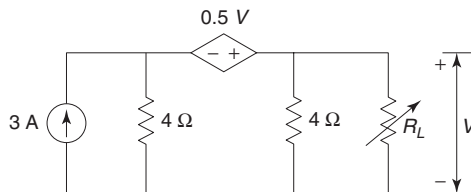


Fig. 2.336

**Solution****Step I** Calculation of  $V_{Th}$  (Fig. 2.337)

By source transformation,

From Fig. 2.337,

$$V_{Th} = 4I$$

Applying KVL to the mesh,

$$12 - 4I + 0.5 V_{Th} - 4I = 0$$

$$12 - V_{Th} + 0.5 V_{Th} - V_{Th} = 0$$





$$V_{Th} = 8 \text{ V}$$

**Step II** Calculation of  $I_N$  (Fig. 2.338)If two terminals  $A$  and  $B$  are shorted, the  $4 \Omega$  resistor gets shorted.

$$V = 0$$

Dependent source  $0.5 V$  depends on the controlling variable  $V$ . When  $V = 0$ , the dependent source vanishes, i.e.  $0.5 V = 0$  as shown in Fig. 2.339 and Fig. 2.340.

$$I_N = \frac{12}{4} = 3 \text{ A}$$

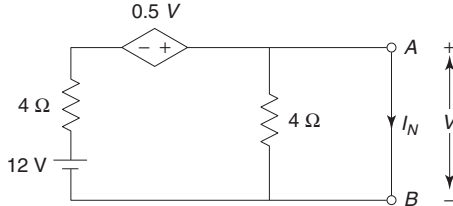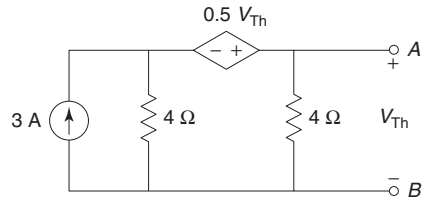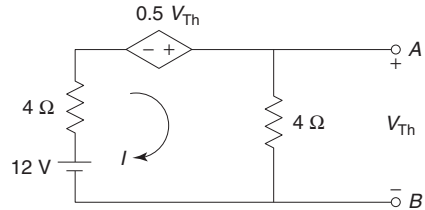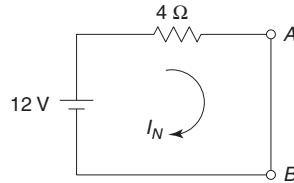**Fig. 2.339****Fig. 2.337****Fig. 2.338****Fig. 2.340****Step III** Calculation of  $R_{Th}$ 

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{8}{3} = 2.67 \Omega$$


**Step IV** Calculation of  $R_L$ 

For maximum power transfer,

$$R_L = R_{Th} = 2.67 \Omega$$

**Step V** Calculation of  $P_{max}$  (Fig. 2.341)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(8)^2}{4 \times 2.67} = 6 \text{ W}$$

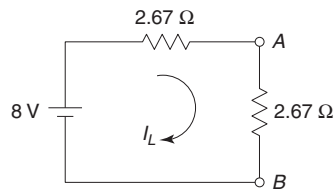**Fig. 2.341**

## 2.11 || RECIPROCITY THEOREM

It states that ‘in a linear, bilateral, active, single source network, the ratio of excitation to response remains same when the positions of excitation and response are interchanged.’

In other words, it may be stated as ‘if a single voltage source  $V_a$  in the branch ‘a’ produces a current  $I_b$  in the branch ‘b’ then if the voltage source  $V_a$  is removed and inserted in the branch ‘b’, it will produce a current  $I_b$  in branch ‘a’.

**Explanation** Consider a network shown in Fig. 2.342.

When the voltage source  $V$  is applied at the port 1, it produces a current  $I$  at the port 2. If the positions of the excitation (source) and response are interchanged, i.e., if the voltage source is applied at the port 2 then it produces a current  $I$  at the port 1 (Fig. 2.343).

The limitation of this theorem is that it is applicable only to a single-source network. This theorem is not applicable in the network which has a dependent source. This is applicable only in linear and bilateral networks. In the reciprocity theorem, position of any passive element (R, L, C) do not change. Only the excitation and response are interchanged.

### Steps to be followed in Reciprocity Theorem

1. Identify the branches between which reciprocity is to be established.
2. Find the current in the branch when excitation and response are not interchanged.
3. Find the current in the branch when excitation and response are interchanged.

### Example 2.108

Calculate current  $I$  and verify the reciprocity theorem for the network shown in Fig. 2.344.

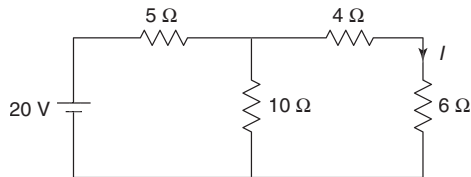


Fig. 2.344

### Solution

**Case I** Calculation of current  $I$  when excitation and response are not interchanged (Fig. 2.345)

Applying KVL to Mesh 1,

$$20 - 5I_1 - 10(I_1 - I_2) = 0$$

$$15I_1 - 10I_2 = 20 \quad \dots(i)$$

Applying KVL to Mesh 2,

$$-10(I_2 - I_1) - 4I_2 - 6I_2 = 0$$

$$-10I_1 + 20I_2 = 0 \quad \dots(ii)$$

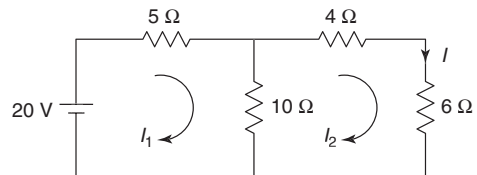


Fig. 2.345

Solving Eqs (i) and (ii),

$$I_1 = 2 \text{ A}$$

$$I_2 = 1 \text{ A}$$

$$I = I_2 = 1 \text{ A}$$

**Case II** Calculation of current  $I$  when excitation and response are interchanged (Fig. 2.346).

Applying KVL to Mesh 1,

$$-5I_1 - 10(I_1 - I_2) = 0$$

$$15I_1 - 10I_2 = 0 \quad \dots(i)$$

Applying KVL to Mesh 2,

$$-10(I_2 - I_1) - 4I_2 - 20 - 6I_2 = 0$$

$$-10I_1 + 20I_2 = -20 \quad \dots(ii)$$


Solving Eqs (i) and (ii),

$$I_1 = -1 \text{ A}$$

$$I_2 = -1.5 \text{ A}$$


$$I = -I_1 = 1 \text{ A}$$

Since the current  $I$  remains the same in both the cases, reciprocity theorem is verified.

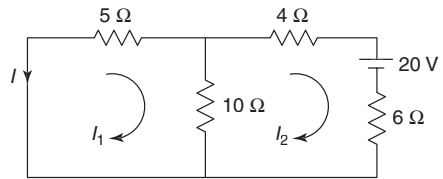

**Fig. 2.346**

**Example 2.109** Find the current  $I$  and verify reciprocity theorem for the network shown in Fig. 2.347.

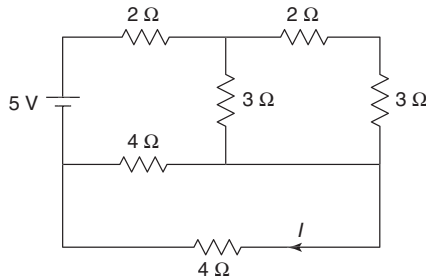

**Fig. 2.347**

### Solution

**Case I** Calculation of the current  $I$  when excitation and response are not interchanged (Fig. 2.348)

Applying KVL to Mesh 1,


$$5 - 2I_1 - 3(I_1 - I_2) - 4(I_1 - I_3) = 0$$

$$9I_1 - 3I_2 - 4I_3 = 5 \quad \dots(i)$$

Applying KVL to Mesh 2,

$$-3(I_2 - I_1) - 2I_2 - 3I_2 = 0$$

$$-3I_1 + 8I_2 = 0 \quad \dots(ii)$$

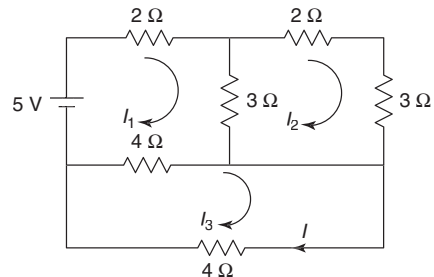

**Fig. 2.348**

**2.120** *Circuit Theory and Networks—Analysis and Synthesis*

Applying KVL to Mesh 3,

$$-4(I_3 - I_1) - 4I_3 = 0$$

$$-4I_1 + 8I_3 = 0$$

...(iii)

Solving Eqs (i), (ii) and (iii),

$$I_1 = 0.85 \text{ A}$$

$$I_2 = 0.32 \text{ A}$$

$$I_3 = 0.43 \text{ A}$$

$$I = I_3 = 0.43 \text{ A}$$

**Case II** Calculation of current  $I$  when excitation and response are interchanged (Fig. 2.349).

Applying KVL to Mesh 1,

$$-2I_1 - 3(I_1 - I_2) - 4(I_1 - I_3) = 0$$

$$9I_1 - 3I_2 - 4I_3 = 0$$

Applying KVL to Mesh 2,

$$-3(I_2 - I_1) - 2I_2 - 3I_2 = 0$$

$$-3I_1 + 8I_2 = 0$$

Applying KVL to Mesh 3,

$$-4(I_3 - I_1) + 5 - 4I_3 = 0$$

$$-4I_1 + 8I_3 = 5$$


Solving Eqs (i), (ii) and (iii),

$$I_1 = 0.43 \text{ A}$$

$$I_2 = 0.16 \text{ A}$$

$$I_3 = 0.84 \text{ A}$$

$$I = I_1 = 0.43 \text{ A}$$

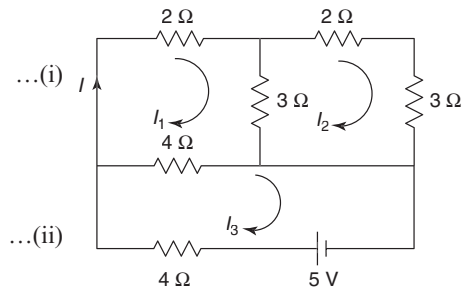


**Fig. 2.349**

...(iii)

Since the current  $I$  remains the same in both the cases, reciprocity theorem is verified.

**Example 2.110** Find the voltage  $V$  and verify reciprocity theorem for the network shown in Fig. 2.350.

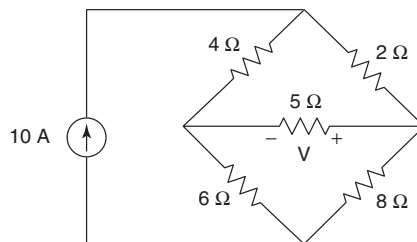

**Fig. 2.350**



**Solution**

**Case I** Calculation of the voltage  $V$  when excitation and response are not interchanged (Fig. 2.351)

For Mesh 1,

$$I_1 = 10 \quad \dots(i)$$

Applying KVL to Mesh 2,

$$-4(I_2 - I_1) - 2I_2 - 5(I_2 - I_3) = 0$$

$$-4I_1 + 11I_2 - 5I_3 = 0 \quad \dots(ii)$$

Applying KVL to Mesh 3,

$$-6(I_3 - I_1) - 5(I_3 - I_2) - 8I_3 = 0$$

$$-6I_1 - 5I_2 + 19I_3 = 0 \quad \dots(iii)$$


Solving Eqs (i), (ii) and (iii),

$$I_1 = 10 \text{ A}$$

$$I_2 = 5.76 \text{ A}$$


$$I_3 = 4.67 \text{ A}$$

$$V = 5(I_2 - I_3) = 5(5.76 - 4.67) = 5.45 \text{ V}$$

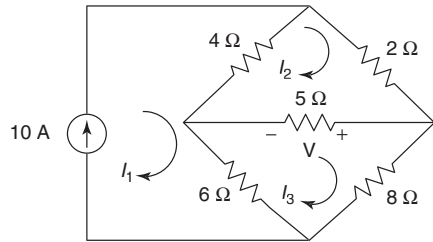

**Fig. 2.351**

**Case II** Calculation of voltage  $V$  when excitation and response are interchanged (Fig. 2.352).

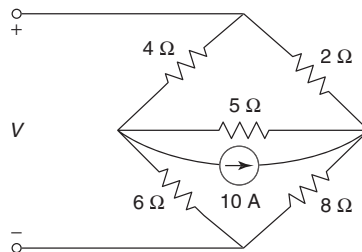

**Fig. 2.352**

By source transformation (Fig. 2.353),

Applying KVL to Mesh 1,

$$-4I_1 - 2I_1 - 50 - 5(I_1 - I_2) = 0$$

$$11I_1 - 5I_2 = -50 \quad \dots(i)$$

Applying KVL to Mesh 2,


$$-6I_2 - 5(I_2 - I_1) + 50 - 8I_2 = 0$$

$$-5I_1 + 19I_2 = 50 \quad \dots(ii)$$

Solving Eqs (i) and (ii),

$$I_1 = -3.8 \text{ A}$$

$$I_2 = 1.63 \text{ A}$$

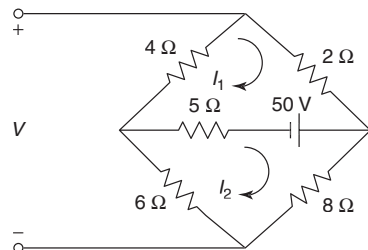

**Fig. 2.353**

## 2.122 Circuit Theory and Networks—Analysis and Synthesis

From Fig. 2.353,

$$V + 4I_1 + 6I_2 = 0$$


$$V + 4(-3.8) + 6(1.63) = 0$$

$$V = 5.42 \text{ V}$$

Since the voltage  $V$  is same in both the cases, the reciprocity theorem is verified.

## 2.12 || MILLMAN'S THEOREM

It states that 'if there are  $n$  voltage sources  $V_1, V_2, \dots, V_n$  with internal resistances  $R_1, R_2, \dots, R_n$  respectively connected in parallel then these voltage sources can be replaced by a single voltage source  $V_m$  and a single series resistance  $R_m$ , '(Fig. 2.354).

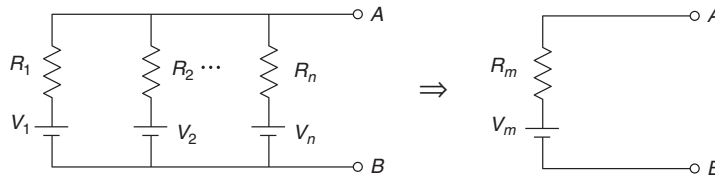

**Fig. 2.354** Millman's network


where

$$V_m = \frac{V_1 G_1 + V_2 G_2 + \dots + V_n G_n}{G_1 + G_2 + \dots + G_n}$$

and

$$R_m = \frac{1}{G_m} = \frac{1}{G_1 + G_2 + \dots + G_n}$$


**Explanation** By source transformation, each voltage source in series with a resistance can be converted to a current source in parallel with a resistance as shown in Fig. 2.355.

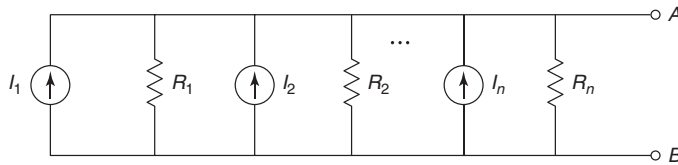

**Fig. 2.355** Equivalent network

Let  $I_m$  be the resultant current of the parallel current sources and  $R_m$  be the equivalent resistance as shown in Fig. 2.356.

$$I_m = I_1 + I_2 + \dots + I_n = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} = V_1 G_1 + V_2 G_2 + \dots + V_n G_n$$

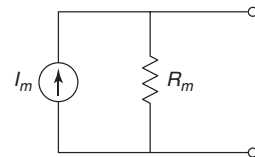


**Fig. 2.356** Equivalent network

$$\frac{1}{R_m} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$G_m = G_1 + G_2 + \dots + G_n$$

By source transformation, the parallel circuit can be converted into a series circuit as shown in Fig. 2.357.


$$V_m = I_m R_m = \frac{I_m}{G_m} = \frac{V_1 G_1 + V_2 G_2 + \dots + V_n G_n}{G_1 + G_2 + \dots + G_n}$$

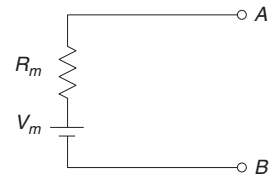

**Fig. 2.357** Millman's equivalent network

### Dual of Millman's Theorem

It states that 'if there are  $n$  current sources  $I_1, I_2, \dots, I_n$  with internal resistances  $R_1, R_2, \dots, R_n$  respectively, connected in series then these current sources can be replaced by a single current source  $I_m$  and a single parallel resistance  $R_m$ ' (Fig. 2.358).

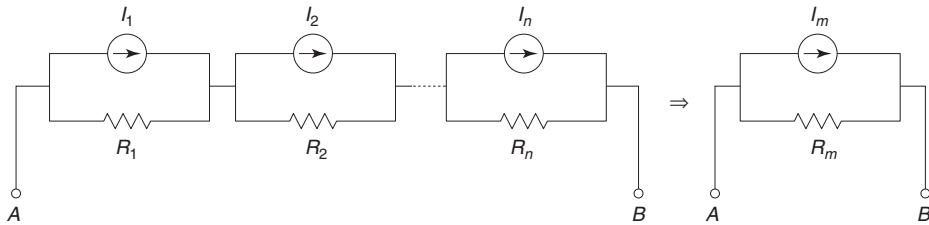

**Fig. 2.358** Millman's network

where

$$I_m = \frac{I_1 R_1 + I_2 R_2 + \dots + I_n R_n}{R_1 + R_2 + \dots + R_n}$$

$$R_m = R_1 + R_2 + \dots + R_n$$

### Steps to be followed in Millman's Theorem

1. Remove the load resistance  $R_L$ .
2. Find Millman's voltage across points  $A$  and  $B$ .

$$V_m = \frac{V_1 G_1 + V_2 G_2 + \dots + V_n G_n}{G_1 + G_2 + \dots + G_n}$$

3. Find the resistance  $R_m$  between points  $A$  and  $B$ .

$$R_m = \frac{1}{G_1 + G_2 + \dots + G_n}$$

4. Replace the network by a voltage source  $V_m$  in series with the resistance  $R_m$ .
5. Find the current through  $R_L$  using ohm's law.

$$I_L = \frac{V_m}{R_m + R_L}$$

**Example 2.111** Find Millman's equivalent for the left of the terminals A-B in Fig. 2.359.

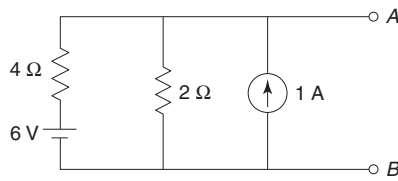


Fig. 2.359

**Solution** By source transformation, the network is redrawn as shown in Fig. 2.360.

**Step I** Calculation of  $V_m$

$$V_m = \frac{V_1 G_1 + V_2 G_2}{G_1 + G_2} = \frac{6\left(\frac{1}{4}\right) + 2\left(\frac{1}{2}\right)}{\frac{1}{4} + \frac{1}{2}} = 3.33 \text{ V}$$

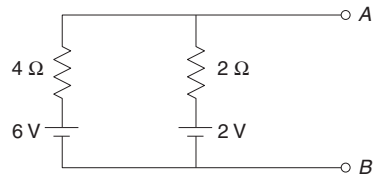


Fig. 2.360

**Step II** Calculation of  $R_m$

$$R_m = \frac{1}{G_m} = \frac{1}{G_1 + G_2} = \frac{1}{\frac{1}{4} + \frac{1}{2}} = 1.33 \text{ } \Omega$$

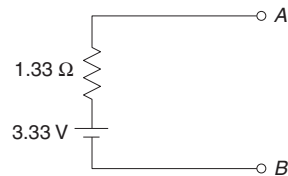


Fig. 2.361

**Step III** Millman's Equivalent Network (Fig. 2.361)

**Example 2.112** Find the current through the 10 Ω resistor in the network of Fig. 2.362.

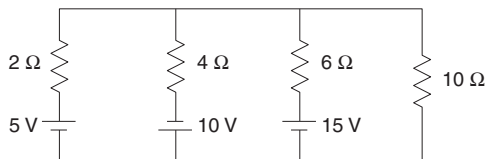


Fig. 2.362

**Solution**

**Step I** Calculation of  $V_m$


$$V_m = \frac{V_1 G_1 + V_2 G_2 + V_3 G_3}{G_1 + G_2 + G_3} = \frac{5\left(\frac{1}{2}\right) - 10\left(\frac{1}{4}\right) + 15\left(\frac{1}{6}\right)}{\frac{1}{2} + \frac{1}{4} + \frac{1}{6}} = 2.73 \text{ V}$$

**Step II** Calculation of  $R_m$

$$R_m = \frac{1}{G_m} = \frac{1}{\frac{1}{2} + \frac{1}{4} + \frac{1}{6}} = 1.09 \, \Omega$$

**Step III** Calculation of  $I_L$  (Fig. 2.363)


$$I_L = \frac{2.73}{1.09 + 10} = 0.25 \, \text{A}$$

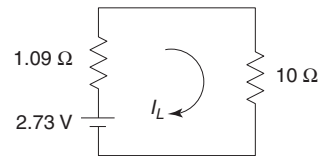

**Fig. 2.363**

### Example 2.113

Find the current through the  $10 \, \Omega$  resistor in the network of Fig. 2.364.

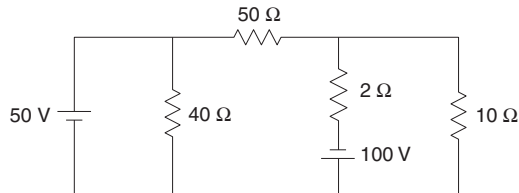


**Fig. 2.364**

### Solution

Since the  $40 \, \Omega$  resistor is connected in parallel with the  $50 \, \text{V}$  source, it becomes redundant. The network can be redrawn as shown in Fig. 2.365.

**Step I** Calculation of  $V_m$

$$V_m = \frac{V_1 G_1 + V_2 G_2}{G_1 + G_2} = \frac{50 \left( \frac{1}{50} \right) - 100 \left( \frac{1}{20} \right)}{\frac{1}{50} + \frac{1}{20}} = -57.15 \, \text{V}$$

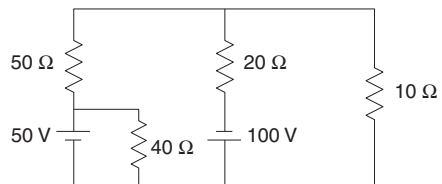


**Fig. 2.365**

**Step II** Calculation of  $R_m$

$$R_m = \frac{1}{G_m} = \frac{1}{G_1 + G_2} = \frac{1}{\frac{1}{50} + \frac{1}{20}} = 14.29 \, \Omega$$

**Step III** Calculation of  $I_L$  (Fig. 2.366)

$$I_L = \frac{57.15}{14.29 + 10} = 2.35 \, \text{A}$$

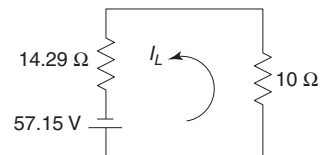


**Fig. 2.366**

### Example 2.114


Draw Millman's equivalent network across terminals  $AB$  in the network of Fig. 2.367.

**2.126** *Circuit Theory and Networks—Analysis and Synthesis*

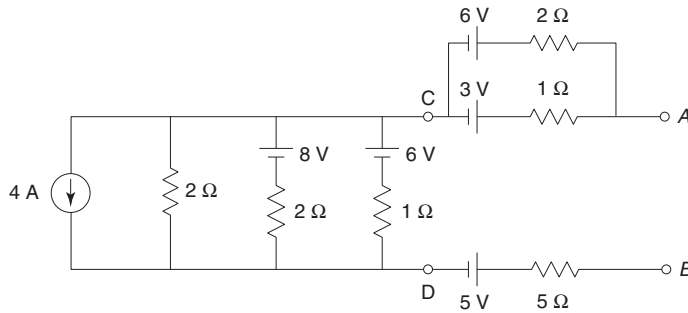

**Fig. 2.367**

**Step I** By source transformation, the network is redrawn as shown in Fig. 2.368.

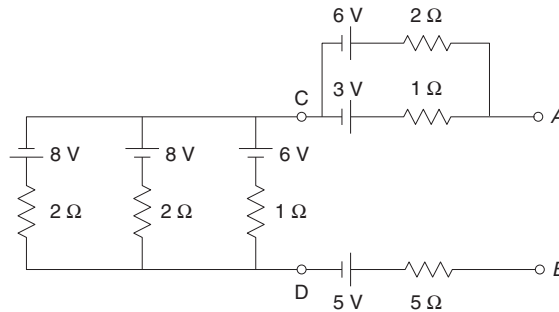

**Fig. 2.368**

**Step II** Applying Millman's theorem at terminals  $CD$ ,

$$V_{m_1} = \frac{V_1 G_1 + V_2 G_2 + V_3 G_3}{G_1 + G_2 + G_3} = \frac{-8\left(\frac{1}{2}\right) + 8\left(\frac{1}{2}\right) + 6(1)}{\frac{1}{2} + \frac{1}{2} + 1} = 3 \text{ V}$$

$$R_{m_1} = \frac{1}{G_{m_1}} = \frac{1}{G_1 + G_2 + G_3} = \frac{1}{\frac{1}{2} + \frac{1}{2} + 1} = 0.5 \text{ } \Omega$$

**Step III** Applying Millman's theorem at terminals  $CA$ ,

$$V_{m_2} = \frac{V_4 G_4 + V_5 G_5}{G_4 + G_5} = \frac{6\left(\frac{1}{2}\right) + 3(1)}{\frac{1}{2} + 1} = 4 \text{ V}$$

$$R_{m_2} = \frac{1}{G_{m_2}} = \frac{1}{G_4 + G_5} = \frac{1}{\frac{1}{2} + 1} = 0.67 \text{ } \Omega$$

**Step IV** Millman's Equivalent Network (Fig. 2.369)

Simplifying Fig. 2.369 further, the Millman's equivalent network is shown in Fig. 2.370.

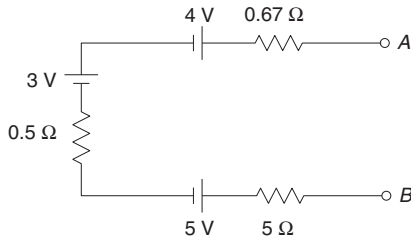


Fig. 2.369

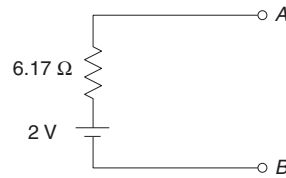


Fig. 2.370

## Exercises

### Mesh Analysis

- 2.1 Find currents  $I_x$  and  $I_y$  in the network shown in Fig. 2.371.

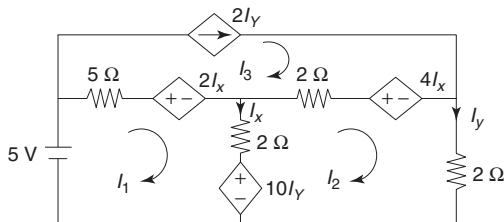


Fig. 2.371

[0.5 A, 0.1 A]

- 2.2 In the network shown in Fig. 2.372, find  $V_3$  if element  $A$  is a

- short circuit
- 5 Ω resistor
- 20 V independent voltage source, positive reference on the right
- dependent voltage source of  $1.5 i_1$ , with positive reference on the right
- dependent current source  $5 i_1$ , arrow directed to the right

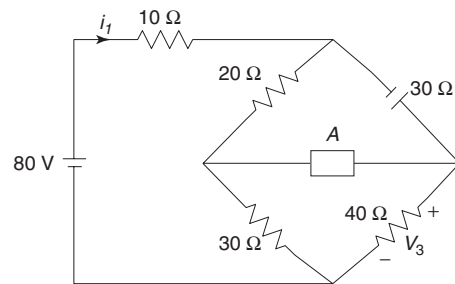


Fig. 2.372

[69.4 V, 72.38 V, 73.68 V, 70.71 V, 97.39 V]

- 2.3 Find currents  $I_1$ ,  $I_2$ , and  $I_3$  in the network shown in Fig. 2.373.


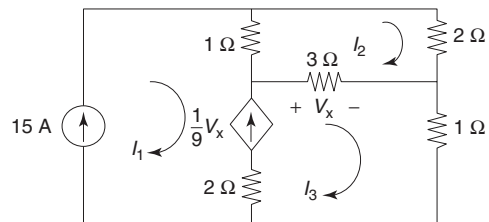


Fig. 2.373

[15 A, 11 A, 17 A]

**2.128** *Circuit Theory and Networks—Analysis and Synthesis*


- 2.4** Find currents  $I_x$  in the network shown in Fig. 2.374.

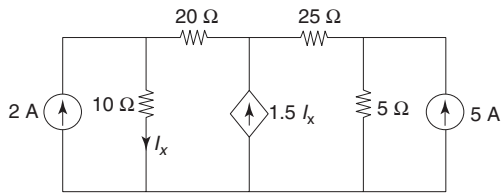

**Fig. 2.374**

[8.33 A]


- 2.5** Find currents  $I_1$  in the network shown in Fig. 2.375.

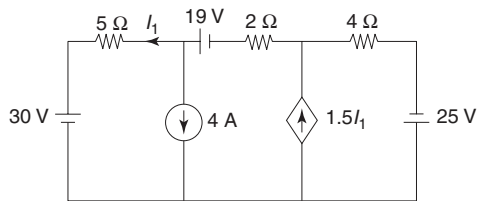

**Fig. 2.375**

[-12 A]


- 2.8** Find the voltage  $V_x$  in the network shown in Fig. 2.378.

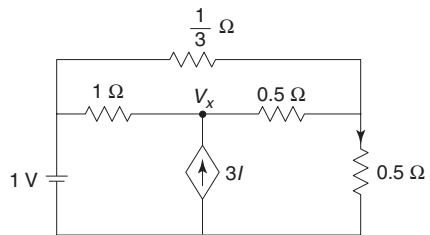

**Fig. 2.378**

[6.2 V]

- 2.9** Determine  $V_1$  in the network shown in Fig. 2.379.

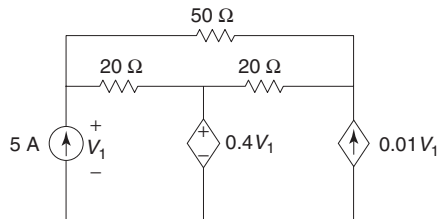


**Fig. 2.379**

[140 V]

**Node Analysis**


- 2.6** Find the voltage  $V_x$  in the network shown in Fig. 2.376.

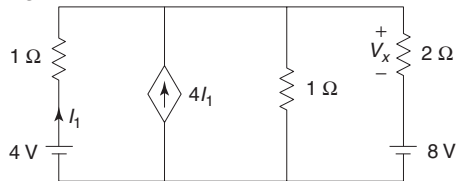

**Fig. 2.376**

[-4.31 V]


- 2.10** Find the voltage  $V_y$  in the network shown in Fig. 2.380.

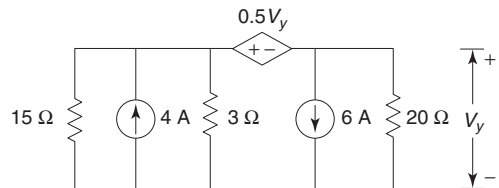

**Fig. 2.380**

[-10 V]


- 2.7** Find the currents  $V_x$  in the network shown in Fig. 2.377.

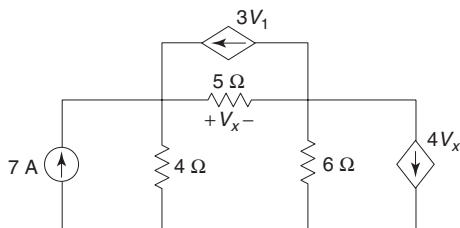

**Fig. 2.377**

[2.09 V]

- 2.11** Find the voltage  $V_2$  in the network shown in Fig. 2.381.

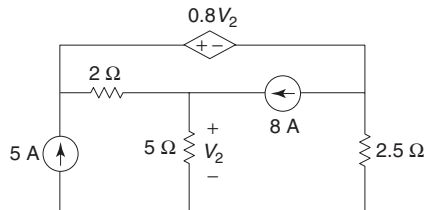


**Fig. 2.381**

[25.9 V]




**Superposition Theorem**

2.12 Find the voltage  $V_x$  in Fig. 2.382.

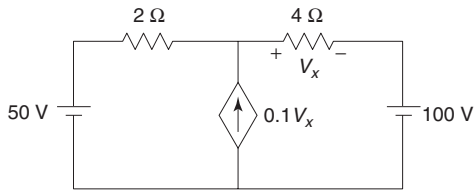**Fig. 2.382**


[−38.5 V]

2.13 Determine the voltages  $V_1$  and  $V_2$  in Fig. 2.383.

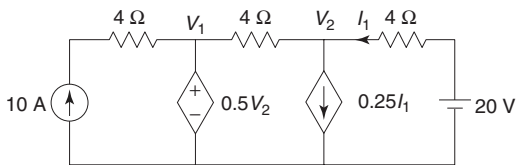**Fig. 2.383**

[6 V, 12 V]

2.14 Find the voltage  $V_x$  in Fig. 2.384.

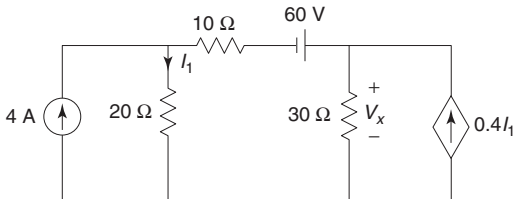
**Fig. 2.384**

[7.5 V]

**Thevenin's Theorem**


2.15 Determine Thevenin's equivalent network for figures 2.385 to 2.388 shown below.

(i)

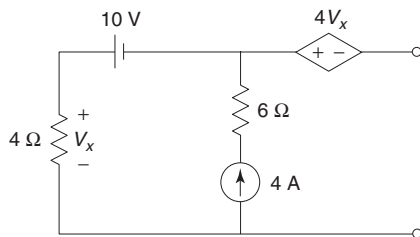**Fig. 2.385**


[−58 V, 12 Ω]

(ii)

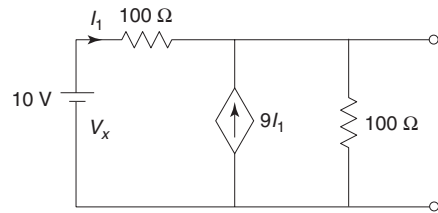**Fig. 2.386**


[9.09 V, 9.09 Ω]

(iii)

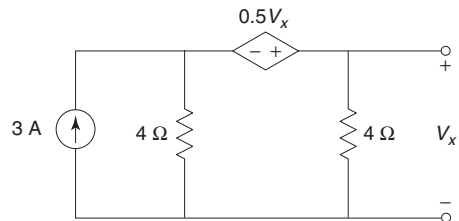**Fig. 2.387**


[8 V, 2.66 Ω]

(iv)

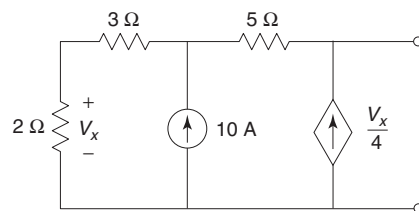**Fig. 2.388**

[150 V, 20 Ω]

2.16 Find the current  $I_x$  in Fig. 2.389.

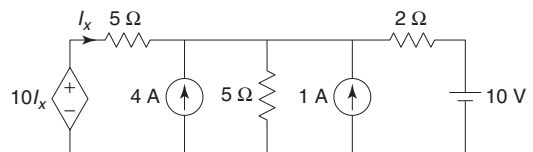**Fig. 2.389**

[4 A]

## 2.130 Circuit Theory and Networks—Analysis and Synthesis

- 2.17 Find the current in the  $24\ \Omega$  resistor in Fig. 3.390.

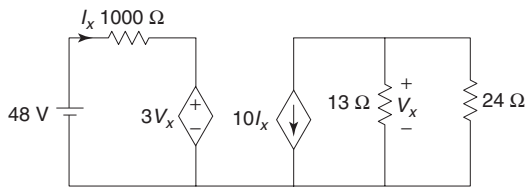


Fig. 3.390

[0.225 A]

### Norton's Theorem

- 2.18 Find Norton's equivalent network and hence find the current in the  $10\ \Omega$  resistor in Fig. 2.391.

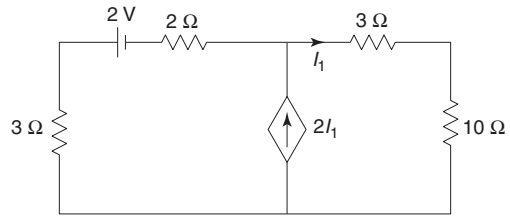


Fig. 2.391

[0.25 A]

- 2.19 Find Norton's equivalent network in Fig. 2.392.

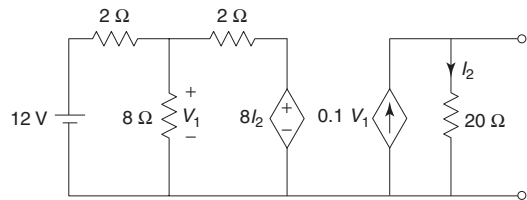


Fig. 2.392

[0.533 A, 31 Ω]

## Objective-Type Questions

- 2.1 Two electrical sub-networks  $N_1$  and  $N_2$  are connected through three resistors as shown in Fig. 2.393. The voltages across the  $5\ \Omega$  resistor and  $1\ \Omega$  resistor are given to be 10 V and 5 V respectively. Then the voltage across the  $15\ \Omega$  resistor is

(a)  $-105\ \text{V}$  (b)  $105\ \text{V}$   
(c)  $-15\ \text{V}$  (d)  $15\ \text{V}$

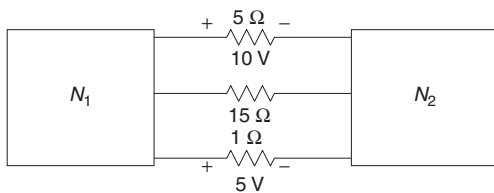


Fig. 2.393

- 2.2 The nodal method of circuit analysis is based on
- (a) KVL and Ohm's law  
(b) KCL and Ohm's law  
(c) KCL and KVL  
(d) KCL, KVL and Ohm's law

- 2.3 The voltage across terminals  $a$  and  $b$  in Fig. 2.394 is

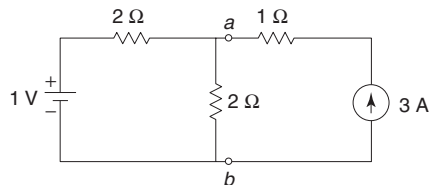


Fig. 2.394

(a)  $0.5\ \text{V}$  (b)  $3\ \text{V}$   
(c)  $3.5\ \text{V}$  (d)  $4\ \text{V}$

- 2.4 The voltage  $V_0$  in Fig. 2.395 is

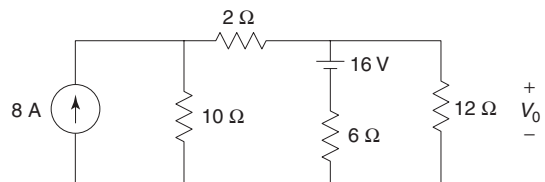


Fig. 2.395

(a)  $48\ \text{V}$  (b)  $24\ \text{V}$   
(c)  $36\ \text{V}$  (d)  $28\ \text{V}$

- 2.5 The dependent current source shown in Fig. 2.396.

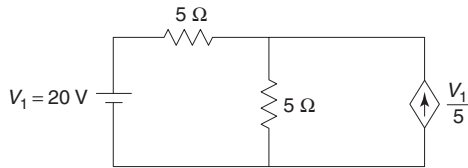


Fig. 2.396

- (a) delivers 80 W (b) absorbs 80 W  
(c) delivers 40 W (d) absorbs 40 W
- 2.6 If  $V = 4$  in Fig. 2.397, the value of  $I_s$  is given by

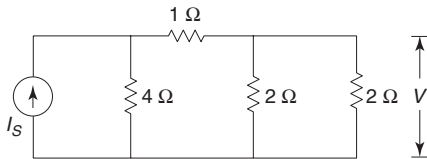


Fig. 2.397

- (a) 6 A (b) 2.5 A  
(c) 12 A (d) none of these
- 2.7 The value of  $V_x$ ,  $V_y$  and  $V_z$  in Fig. 2.398 shown are

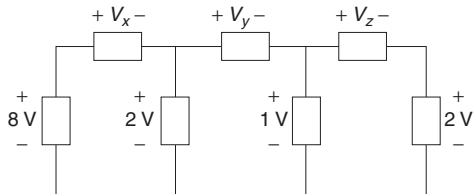


Fig. 2.398

- (a) -6, 3, -3 (b) -6, -3, 1  
(c) 6, 3, 3 (d) 6, 1, 3
- 2.8 The circuit shown in Fig. 2.399 is equivalent to a load of

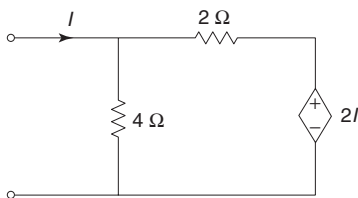


Fig. 2.399

- (a)  $\frac{4}{3} \Omega$  (b)  $\frac{8}{3} \Omega$   
(c)  $4 \Omega$  (d)  $2 \Omega$

- 2.9 In the network shown in Fig. 2.400, the effective resistance faced by the voltage source is

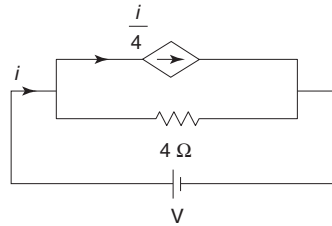


Fig. 2.400

- (a)  $4 \Omega$  (b)  $3 \Omega$   
(c)  $2 \Omega$  (d)  $1 \Omega$
- 2.10 A network contains only an independent current source and resistors. If the values of all resistors are doubled, the value of the node voltages will
- (a) become half  
(b) remain unchanged  
(c) become double  
(d) none of these
- 2.11 The value of the resistance  $R$  connected across the terminals  $A$  and  $B$  in Fig. 2.401, which will absorb the maximum power is

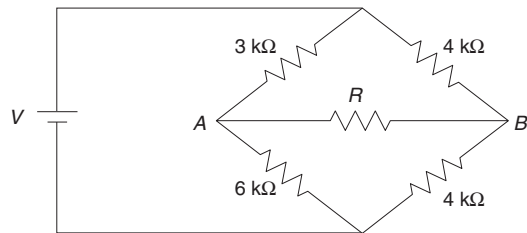



Fig. 2.401

- (a)  $4 \text{ k}\Omega$  (b)  $4.11 \text{ k}\Omega$   
(c)  $8 \text{ k}\Omega$  (d)  $9 \text{ k}\Omega$
- 2.12 Superposition theorem is not applicable to networks containing
- (a) nonlinear elements  
(b) dependent voltage source

**2.132** *Circuit Theory and Networks—Analysis and Synthesis*

- (c) dependent current source  
(d) transformers


**2.13** The value of  $R$  required for maximum power transfer in the network shown in Fig. 2.402 is

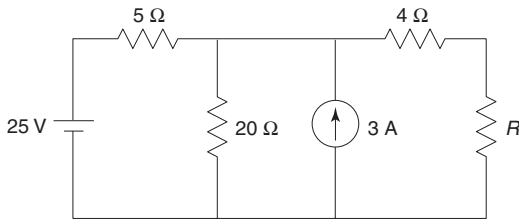

**Fig. 2.402**

- (a)  $2\ \Omega$                       (b)  $4\ \Omega$   
(c)  $8\ \Omega$                       (d)  $16\ \Omega$


**2.14** In the network of Fig. 2.403, the maximum power is delivered to  $R_L$  if its value is

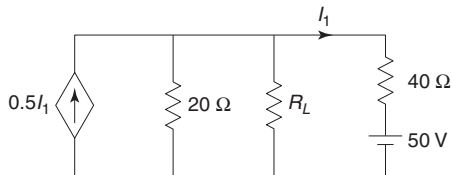

**Fig. 2.403**

- (a)  $16\ \Omega$                       (b)  $\frac{40}{3}\ \Omega$   
(c)  $60\ \Omega$                       (d)  $20\ \Omega$


**2.15** The maximum power that can be transferred to the load  $R_L$  from the voltage source in Fig. 2.404 is

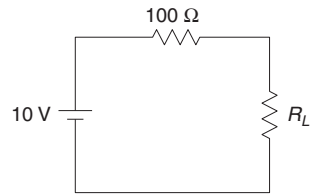

**Fig. 2.404**

- (a)  $1\ \text{W}$                       (b)  $10\ \text{W}$   
(c)  $0.25\ \text{W}$                       (d)  $0.5\ \text{W}$


**2.16** For the circuit shown in Fig. 2.405, Thevenin's voltage and Thevenin's equivalent resistance at terminals  $a$ - $b$  is

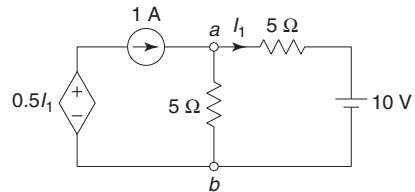

**Fig. 2.405**

- (a)  $5\ \text{V}$  and  $2\ \Omega$                       (b)  $7.5\ \text{V}$  and  $2.5\ \Omega$   
(c)  $4\ \text{V}$  and  $2\ \Omega$                       (d)  $3\ \text{V}$  and  $2.5\ \Omega$

**2.17** The value of  $R_L$  in Fig. 2.406 for maximum power transfer is

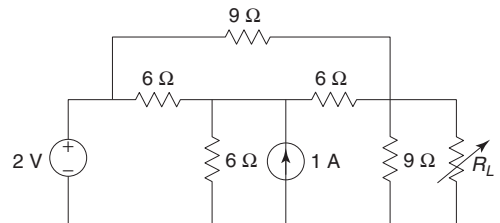

**Fig. 2.406**

- (a)  $3\ \Omega$                       (b)  $1.125\ \Omega$   
(c)  $4.1785\ \Omega$                       (d) none of these

## Answers to Objective-Type Questions

- 2.1. (a)      2.2. (b)      2.3. (c)      2.4. (d)      2.5. (a)      2.6. (d)      2.7. (a)  
2.8. (a)      2.9. (d)      2.10. (b)      2.11. (a)      2.12. (a)      2.13. (c)      2.14. (a)  
2.15. (c)      2.16. (b)      2.17. (a)