

★ Introduction to Timer

An electronic timer is a circuit which drives other systems such as alarm, control system, after a specific time period depending on the values of components used. This time period can be varied. The basic idea behind the time is charging & discharging of an external capacitor through switching circuitry.


⇒ Applications

Oscillator, pulse generator, ramp or square wave generator, Monostable, Astable, bistable multivibrator.


⇒ Features

- Operation on $\pm 5V$ to $\pm 18V$ supply voltage in both astable & monostable modes.
- Timing from microseconds to hours.
- High current output.
- Output can drive TTL family.
- Reliable, easy to use, low cost.

⇒ PIN diagram

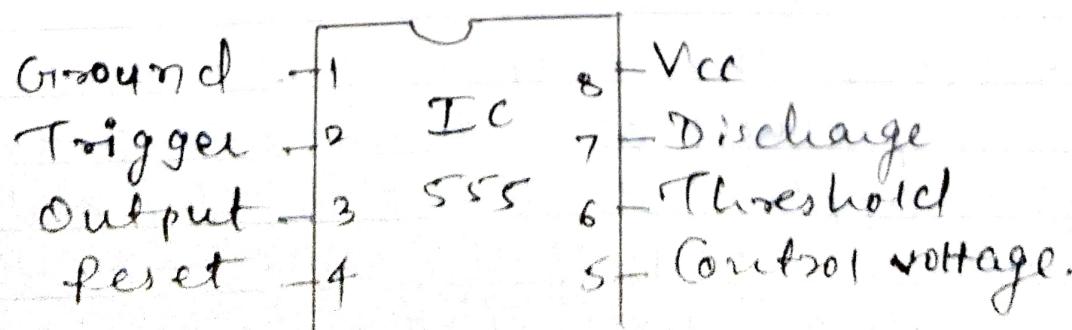

* Block diagram.

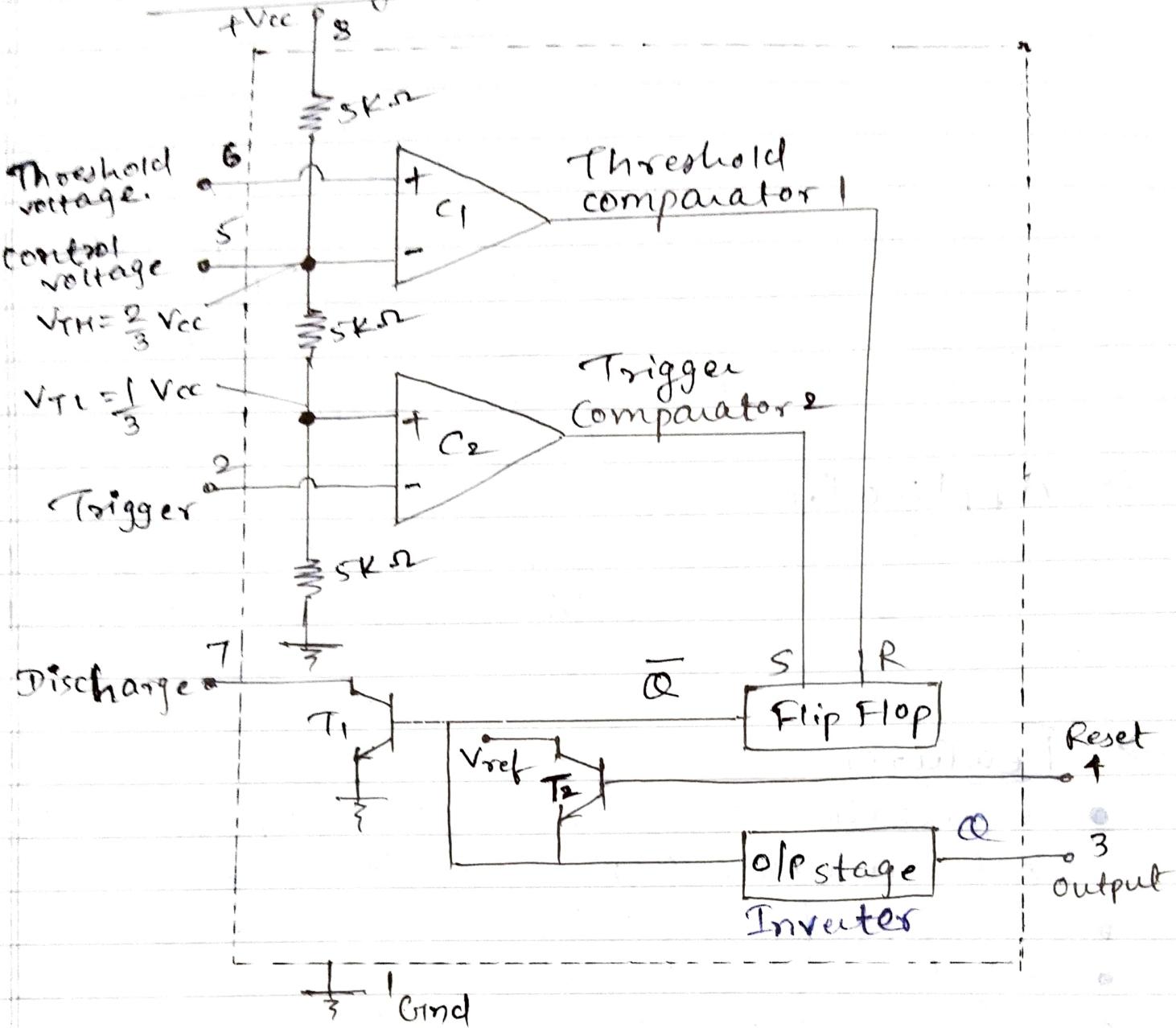

→ PIN FUNCTION

- Ground: All voltages are measured with respect to this terminal.
- Trigger: The output of the timer depends on amplitude of external ~~control~~ trigger pulse applied to this pin. The output of timer is HIGH if the voltage at this pin is less than $\frac{1}{3} V_{cc}$. The output remains high.

as long as the trigger terminal is held at a low voltage.

Output: This is the output of the timer & the load is to be connected to this pin. There are two ways a load can be connected to the op terminal. either pin 3 & ground (pin 1) or between pin 3 & supply voltage Vcc (pin 8).

When the output is low, the load current flows through the load connected between pin 3 & +Vcc into the output terminal & is called the sink current.


When the output is high, the current through the load between pin 3 & +Vcc is zero. This current is called source current.

Reset: The 555 timer can be reset by applying a -ve pulse to this pin. When the reset function is not in use, this terminal should be connected to +Vcc to avoid any possibility of false triggering.


Control voltage: An external voltage applied to this terminal changes the threshold as well as trigger voltage. By imposing a voltage on this pin or by connecting a pot between this pin & ground, the pulse width of output voltage wave form can be varied. When not in use, the control pin should be bypassed to ground with 0.01μF capacitor to prevent any noise prob.

- Threshold: When the voltage at this pin is greater than or equal to $\frac{2}{3} V_{CC}$, the output of comparator 1 goes high, which in turn switches the output of the timer low.
- Discharge: This pin is connected internally to the collector of transistor T_1 , as shown in fig. When output is high, T_1 is off & acts as an open circuit to external capacitor 'C' connected across it. When output is low, T_1 is saturated (ON) & acts as a shorting out the external capacitor C to ground.
- $+V_{CC}$: The supply voltage of $+5V$ to $+18V$ is applied to this pin with respect to ground.

* Astable Multivibrator

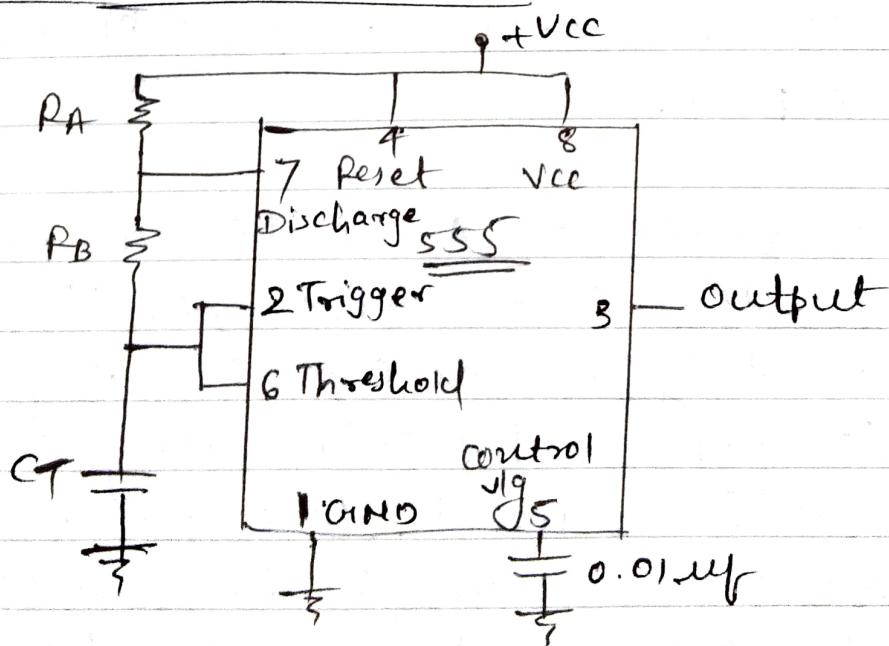

- Astable multivibrator is a circuit which will trigger itself & go from one state to another state after a predetermined interval of time. It has two quasi stable states generating rectangular waveforms.
- Initially capacitor is kept unchanged. When V_{cc} is applied, the internal transistor is held OFF & the output goes high. The external capacitor C_T charges through R_A & R_B with time constant $(R_A + R_B)C_T$.
- When the voltage across capacitor reaches $\frac{2}{3}V_{cc}$ it makes a positive transition near the reference voltage of comparator 'C', ie. $Q_P^{C_1}$ goes high which resets the flip flop. The output of I_C goes low. The internal Transistor T_1 is ON & capacitor discharges through R_B & internal transistor T_1 to ground.
- When capacitor discharges to $\frac{1}{3}V_{cc}$, it makes output of comparator 'C' high, which sets the flip flop. The output goes high. The internal transistor T_1 becomes off & capacitor again starts charging. The discharging timeconstant is $R_B C_T$.
- Subsequently capacitor charges from $\frac{1}{3}V_{cc}$ to $\frac{2}{3}V_{cc}$ & discharges from $\frac{2}{3}V_{cc}$ to $\frac{1}{3}V_{cc}$. The cycle repeats & generates rectangular pulses at the output.

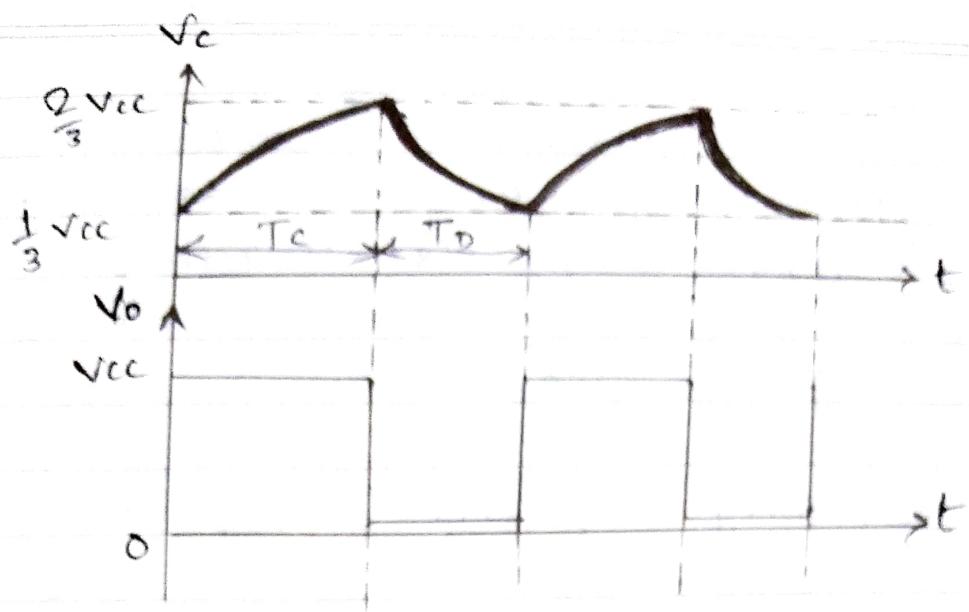

$$T_{ON} \text{ ie. } T_c = (R_A + R_B)C_T \ln\left(\frac{V_{CC} - \frac{1}{3}V_{CC}}{V_{CC} - \frac{2}{3}V_{CC}}\right)$$

$$\therefore T_c = (R_A + R_B)C_T \ln\left(\frac{\frac{2}{3}V_{CC}}{\frac{1}{3}V_{CC}}\right)$$

$$\boxed{T_c = 0.693(R_A + R_B)C_T}$$

$$T_{OFF} \text{ ie. } T_{off} = R_B \cdot C_T \ln\left(\frac{0 - \frac{2}{3}V_{CC}}{0 - \frac{1}{3}V_{CC}}\right) = 0.693 R_B C_T.$$

Total time $T = T_{ON} + T_{OFF}$

$$T = 0.693(R_A + R_B)C_T + 0.693R_B C_T$$

$$\text{Duty cycle} = \frac{T_{ON}}{T}$$

$$= \frac{0.693(R_A + R_B)C_T}{0.693(R_A + R_B)C_T + 0.693R_B C_T}$$

$$= \frac{R_A + R_B}{R_A + 2R_B} \times 100$$

$$\text{Frequency} = \frac{1}{T} = \frac{1}{0.693(R_A + 2R_B)C_T}$$


$$F = \frac{1.45}{(R_A + 2R_B) \cdot C_T} \text{ Hz} //$$

→ Application

- Square Wave Oscillator
- Free running ramp generator
- Voltage control oscillator
- Schmitt trigger.




Monostable Multivibrator

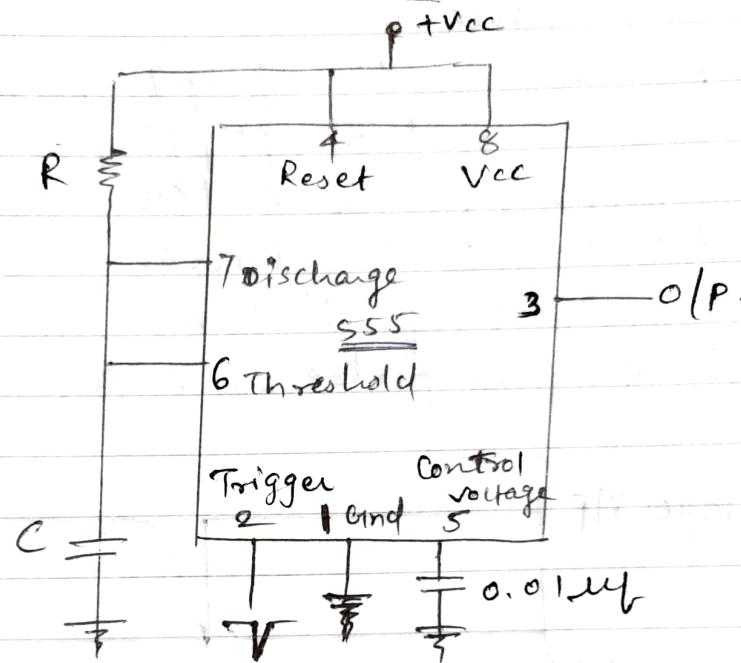

→ Monostable multivibrator is a circuit which is normally in the stable state. On the application of an External Trigger, the output goes to the quasi stable state, remains for predetermined interval of time & comes back to the original stable state.

→ Before the application of trigger pulse, the voltage at trigger input pin 2 is high. The op of comparator C_2 is low, making the flip flop output \bar{Q} to high & V_o is low. The discharge Transistor T_1 is on & hence the external capacitor is in discharge state.

- On the application of $-ve$ going pulse below $\frac{1}{3}V_{cc}$ at pin 2, makes output of comparator K_2 high which in turn sets the flip flop, \bar{Q} is low & Q of timer is high.
- The internal ~~cap~~ transistor T_1 becomes off. The capacitor 'C' charges through R . ~~Take about~~
- When capacitor voltage reaches $\frac{2}{3}V_{cc}$, it crosses the reference voltage of comparator K_1 whose output resets the flip flop. Output is low. Then \bar{Q} output of flip flop is high. The transistor T_1 is ON & external capacitor C instantaneously discharges.
- The output of the monostable remains low until trigger pulse is again applied.

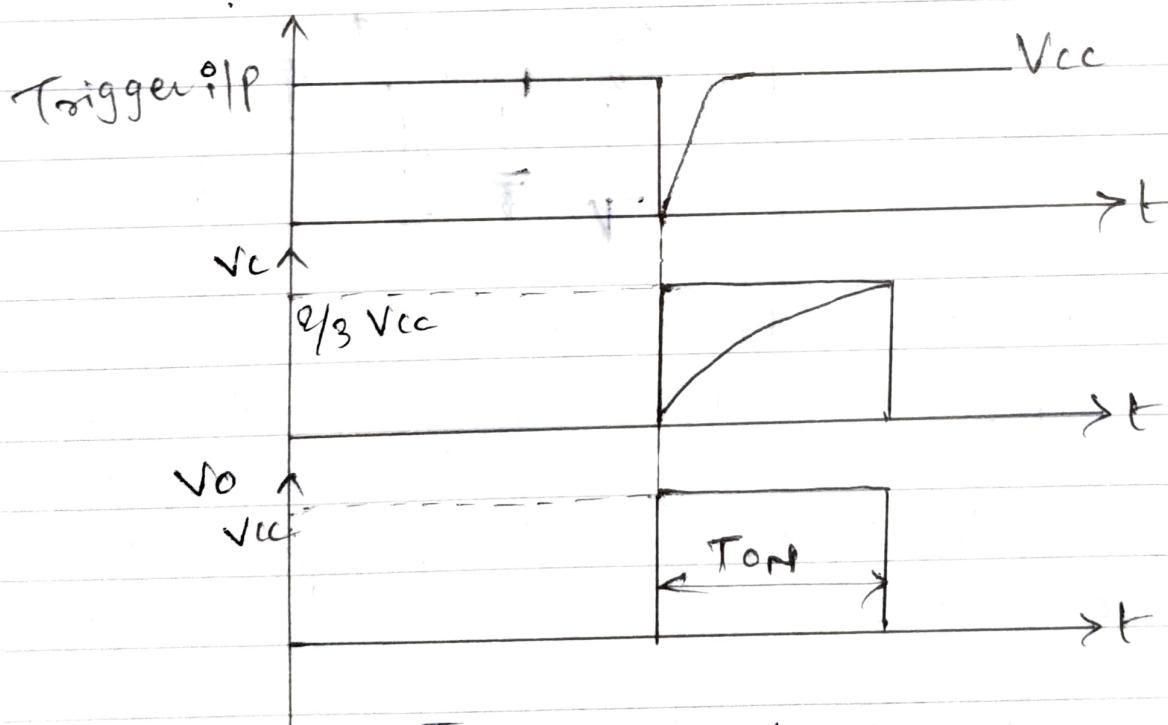

Time duration for which capacitor charges from 0 to $\frac{2}{3}V_{cc}$.

$$\frac{2}{3}V_{cc} = V_{cc} \left[1 - e^{-\frac{T_{on}}{RC}} \right]$$

$$\frac{2}{3} V_{cc} \cdot e^{-\frac{T_{on}}{RC}} = 1 - \frac{2}{3} = \frac{1}{3}$$

Taking log on both sides.

$$-\frac{T_{on}}{RC} = \ln \frac{1}{3}$$

$$T_{on} = RC \ln 3$$

$$T_{on} = 1.1 RC$$

↳ Some applications of monostable multivibrator

→ Application

- Frequency divider
- Missing pulse detector
- Pulse width modulator
- Retriggerable monostable M.V.

① In an Astable multivibrator ckt, $R_A = 27\text{ k}\Omega$, $R_B = 39\text{ k}\Omega$, $C_T = 0.1\text{ \mu F}$. Calculate frequency of oscillations of c/p. Also calculate T_{ON} & T_{OFF} .

$$\rightarrow R_A = 27\text{ k}\Omega, R_B = 39\text{ k}\Omega, C_T = 0.1\text{ \mu F}.$$

$$T_{ON} = 0.693(R_A + R_B)C_T.$$

$$= 0.693(27\text{ k} + 39\text{ k})0.1 \times 10^{-6}$$

$$= 0.693 \times 66 \times 10^3 \times 1 \times 10^{-7} = 4.57\text{ ms}$$

$$T_{OFF} = 0.693 R_B C_T.$$

$$= 0.693 \times 39 \times 10^3 \times 0.1 \times 10^{-6}$$

$$= 2.7027\text{ ms.}$$

$$\text{Total time period } T = T_{ON} + T_{OFF}$$

$$= (4.57 + 2.70) = 7.276\text{ ms}$$

$$\text{Frequency of oscillation } f = \frac{1}{T} = \frac{1}{7.276 \times 10^{-3}}$$

$$\therefore f = \frac{10^3}{7.276} = \frac{1000}{7.2765} = 137.43\text{ Hz}$$

② Design an Astable multivibrator using T_{CS555} with a freq. of 2kHz & duty cycle 80%. Draw the designed ckt.

$$\rightarrow F = 2\text{ kHz}, \text{ Duty cycle} = 80\%.$$

$$\text{Duty cycle} = \frac{T_{ON}}{T} = \frac{R_A + R_B}{R_A + 2R_B} = 80\% = \frac{8}{10}$$

$$\frac{R_A + R_B}{R_A + 2R_B} = \frac{4}{5}$$

$$\therefore 5R_A + 5R_B = 4R_A + 8R_B$$

$$\therefore R_A = 3R_B$$

Frequency of oscillation,

$$f = 1.44$$

$$(R_A + 2R_B)C_T$$

$$\text{Let } C_T = 0.1 \mu\text{F}$$

$$\therefore 2 \times 10^3 = 1.44$$

$$(R_A + 2R_B) \times 0.1 \times 10^{-6}$$

$$R_A + 2R_B = \frac{1.44}{2 \times 10^3 \times 1 \times 10^{-7}}$$

$$= \frac{1.44}{2 \times 10^{-4}} = \frac{1.44 \times 10 \times 10^3}{2}$$


$$= 7.2 \text{ k}\Omega$$

$$\therefore 3R_B + 2R_B = 7.2 \text{ k}\Omega \quad \text{as } R_A = 3R_B.$$

$$\therefore 5R_B = 7.2 \text{ k}\Omega$$

$$\therefore R_B = \frac{7.2}{5} \text{ k}\Omega = 1.44 \text{ k}\Omega$$
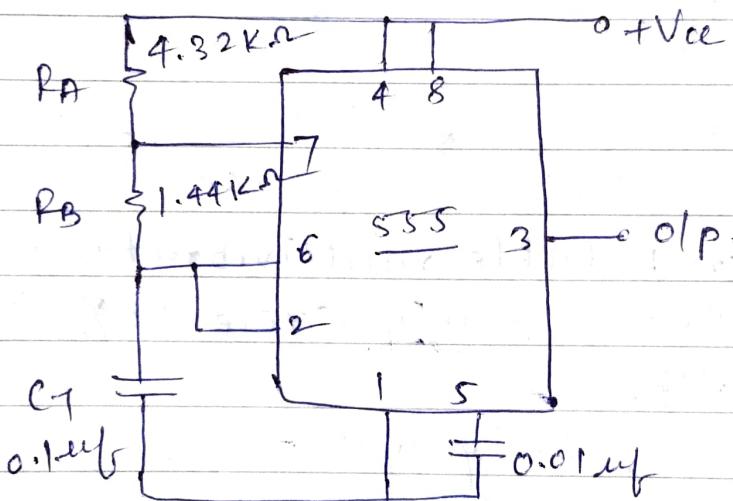
$$\& R_A = 3 \times 1.44 \times 10^3 = 4.32 \text{ k}\Omega$$



③ If $R_3 = 10 \text{ k}\Omega$, $C_7 = 0.05 \mu\text{F}$, calculate time period of monostable multivibrator using 555 & draw the circuit diagram.


$$\rightarrow R = 10 \text{ k}\Omega, C_7 = 0.05 \mu\text{F}$$

$$\text{Time period} = 1.1 \times R \times C_7$$

$$\text{i.e. pulse width} = 1.1 \times 10 \times 10^3 \times 0.05 \times 10^{-6}$$

$$= 5.5 \times 10^{-5} = 5.5 \times 10^{-2} \times 10^{-3} \text{ sec.}$$

$$T = 0.55 \text{ ms.}$$

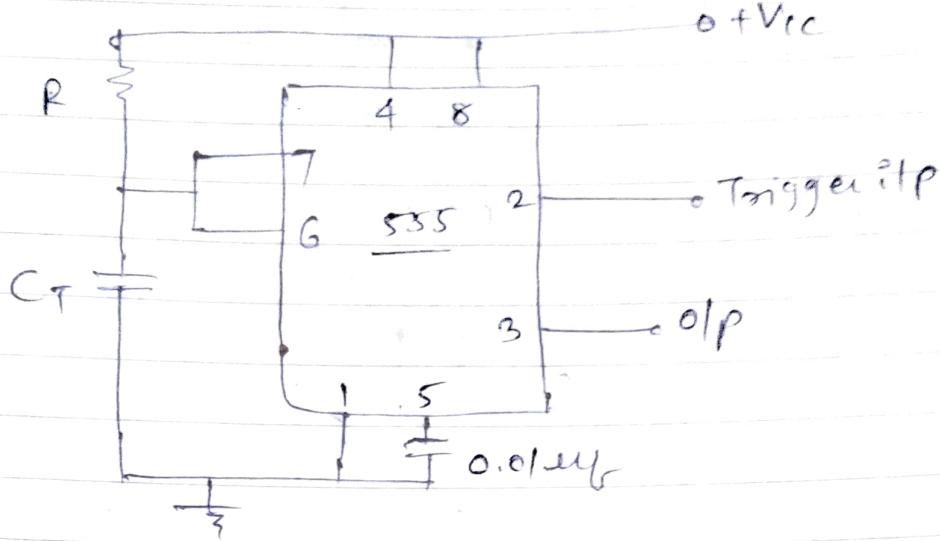

- ④ Draw the circuit diagram of astable multivibrator using IC 555 to obtain 50% duty cycle. Determine values of components used at 1KHz frequency, when $C_T = 1\text{ }\mu\text{F}$. Draw waveform of astable multivibrator.
- Duty cycle = 50%, $f = 1\text{ KHz}$, $C_T = 1\text{ }\mu\text{F}$.

For duty cycle = 50%.

$t_C = t_D$ ie. charging time = Discharging time

$$\therefore T_{ON} = T_{OFF}$$

$$f = 1\text{ KHz}$$

$$T = \frac{1}{f} = \frac{1}{1\text{ KHz}} = \frac{1}{10^3} = 1 \times 10^{-3} \text{ sec.}$$

$$\text{Total time } T = T_{ON} + T_{OFF}$$

$$= 2T_{ON}$$

$$T_{ON} = T_{OFF} = \frac{T}{2} = \frac{1\text{ ms}}{2} = 0.5\text{ msec.}$$

$$T_{OFF} = 0.693 R_B C_T$$

$$0.5\text{ ms} = 0.693 \times R_B \times 1 \times 10^{-6}$$

$$\therefore R_B = \frac{0.5 \times 10^3}{0.693 \times 10^{-6}}$$

$$= 0.5 / 0.693 \times 10^3 = 0.72 \times 1000$$



$$R_B = 721.5 \Omega$$

$$T_{ON} = 0.693 (R_A + R_B) C_T$$

$T_{ON} = 0.693 R_A C_T$... neglecting R_B .

As, $T_{ON} = T_{OFF}$

$$R_A = R_B = 72 \text{ k}\Omega$$

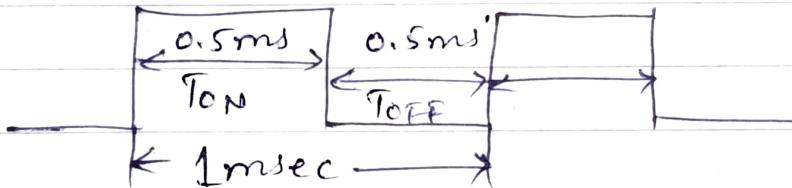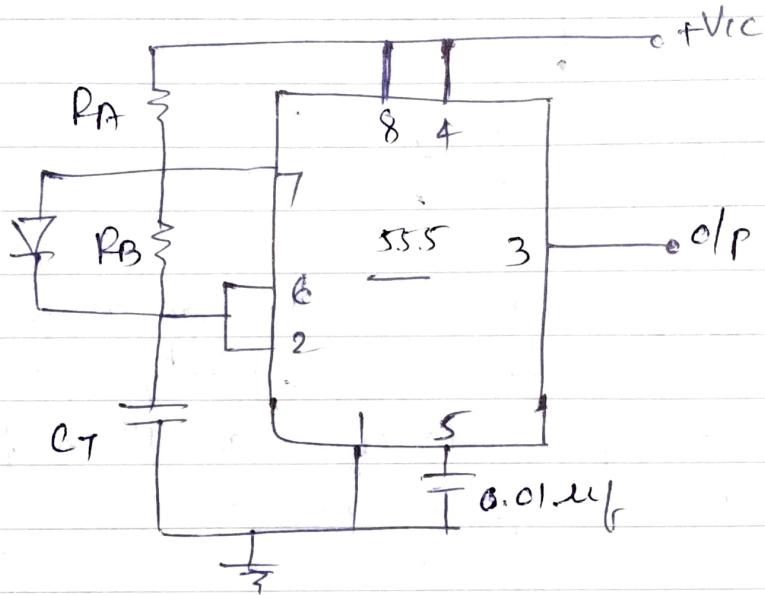

(5) Determine pulselength of monostable multivibrator.

$$\text{if } C = 0.047 \mu\text{F}, R = 56 \text{ k}\Omega$$

$$\rightarrow \text{pulse width } t_p = 1.1 \times R \times C$$

$$= 1.1 \times 56 \times 10^3 \times 0.047 \times 10^{-6}$$

$$t_p = 2.8952 \times 10^{-3}$$

$$t_p = 2.90 \text{ msec.}$$

(6) If $R_A = 2 \text{ k}\Omega$, $R_B = 5 \text{ k}\Omega$, $C_T = 2.5 \mu\text{F}$, calculate T_{ON} , T_{OFF} . IC 555 as astable multivibrator.

Determine duty cycle of ckt using above component.

$$\rightarrow R_A = 2\text{ k}\Omega, R_B = 5\text{ k}\Omega, C_T = 2.5\text{ nF}$$

$$T_{ON} = 0.693 (R_A + R_B) C_T$$

$$= 0.693 (2\text{ k}\Omega + 5\text{ k}\Omega) \times 2.5 \times 10^{-9}$$

$$= 0.693 \times 7 \times 10^3 \times 2.5 \times 10^{-9}$$

$$T_{ON} = 12.1275 \text{ ms.}$$

$$T_{OFF} = 0.693 \times R_B \times C_T$$

$$= 0.693 \times 5 \times 10^3 \times 2.5 \times 10^{-9}$$

$$= 0.693 \times 5 \times 2.5 \times 10^{-9}$$

$$T_{OFF} = 8.66 \text{ msec.}$$

$$\text{Total time, } T = T_{ON} + T_{OFF}$$

$$= 12.12 + 8.66$$

$$T = 20.79 \text{ msec.}$$

$$\% \text{ Duty cycle} = \frac{T_{ON}}{T} \times 100\%$$

$$= \frac{12.1275}{20.79} \times 100\%$$

$$\% \text{ Duty cycle} = 58.33\%$$

7) In monostable multivibrator using IC 555, $R = 15\text{ k}\Omega$, o/p pulse width $t_p = 10\text{ ms}$. Determine value of C . Draw designed ckt.

$$\rightarrow R = 15\text{ k}\Omega, t_p = 10\text{ ms}, C = ?$$


$$t_p = 1.1 \times R \times C$$

$$10\text{ ms} = 1.1 \times 15 \times 10^3 \times C$$

$$\therefore C = \frac{10 \times 10^{-3}}{1.1 \times 15 \times 10^3} = \frac{10}{16.5} \times 10^{-6}$$

$$\therefore C = 0.606 \times 10^{-6} \text{ F}$$

$$\therefore C = 0.6 \mu\text{F}$$

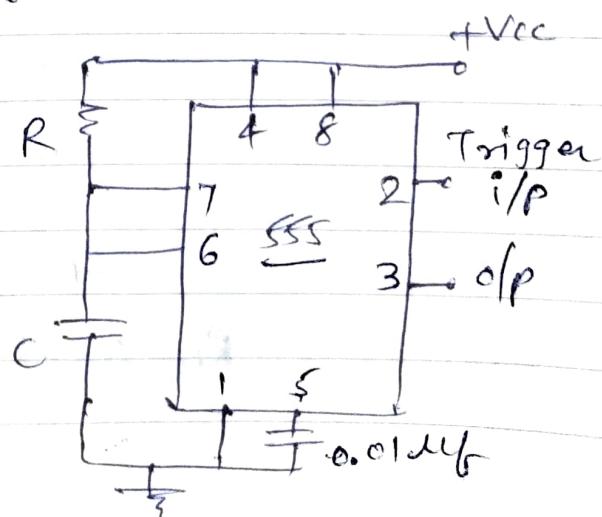

(Q) Design an Astable multivibrator using IC555 with free running freq. of 1KHz & duty cycle 70%, Assume $C_T = 0.1\mu F$. Draw designed ckt & wave form.

$$\rightarrow f = 1\text{KHz}, \text{duty cycle} = 70\%, C_T = 0.1\mu F$$

$$\text{Duty cycle} = \frac{R_A + R_B}{R_A + 2R_B} = 70\% = \frac{70}{100} = \frac{7}{10}$$

$$\therefore \frac{R_A + R_B}{R_A + 2R_B} = \frac{7}{10}$$

$$\therefore 7R_A + 14R_B = 10R_A + 10R_B$$

$$\therefore 4R_B = 3R_A$$

$$\therefore R_B = \frac{3}{4} R_A \quad \rightarrow \textcircled{1}$$

$$\text{Free running freq. } f = \frac{1.44}{(R_A + 2R_B)C_T}$$

$$\therefore R_A + 2R_B = \frac{1.44}{f \times C_T}$$

$$\therefore R_A + 2R_B = \frac{1.44}{1 \times 10^3 \times 0.1 \times 10^{-6}}$$

$$\therefore = 1.44 \times 10^4$$

$$\therefore R_A + 2R_B = 14.4 \text{ k}\Omega$$

but from equation $\textcircled{1}$

$$R_A + 2 \times \frac{3}{4} R_A = 14.4 \text{ k}\Omega$$

$$\frac{5}{2} R_A = 14.4 \text{ k}\Omega$$


$$R_A = \frac{2 \times 14.4 \text{ k}\Omega}{5} = 5.76 \text{ k}\Omega$$

$$R_B = \frac{3}{4} \times 5.76 \text{ k}\Omega = 4.32 \text{ k}\Omega$$


$$\therefore R_A = 5.76 \text{ k}\Omega, R_B = 4.32 \text{ k}\Omega, C_T = 0.1\mu F$$

* Applications of IC 555 :-


1) Pulse width modulation:-

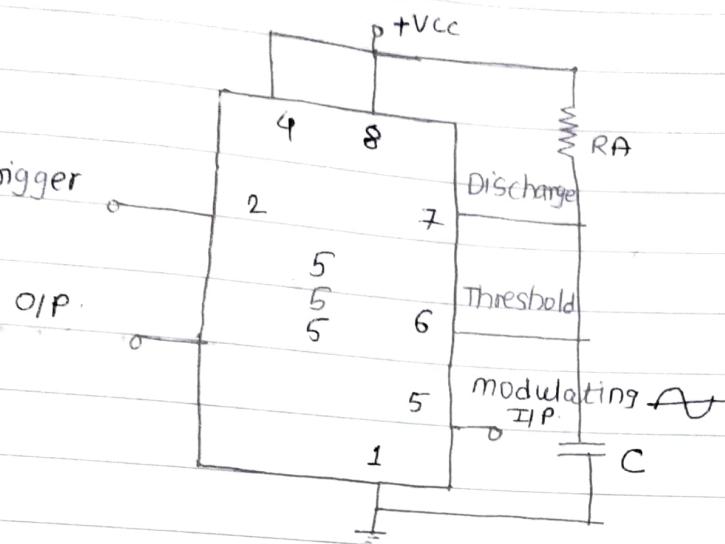

- Basically a mmv with modulating IIP signal applied at pin no 5.
- Continuous trigger is applied at pin no 2. A series of pulses are generated at O/P, the duration of which depends on the modulating input at pin no 5.
- modulating IIP gets superimposed upon the already existing voltage ($2/3$)V_{CC} at inverting IIP terminal of upper comparator.
- This in turn changes the threshold level of V_C & the O/P pulse width modulation takes place.
- O/P freq remains same as that of the applied trigger pulse. only the duty cycle will change.

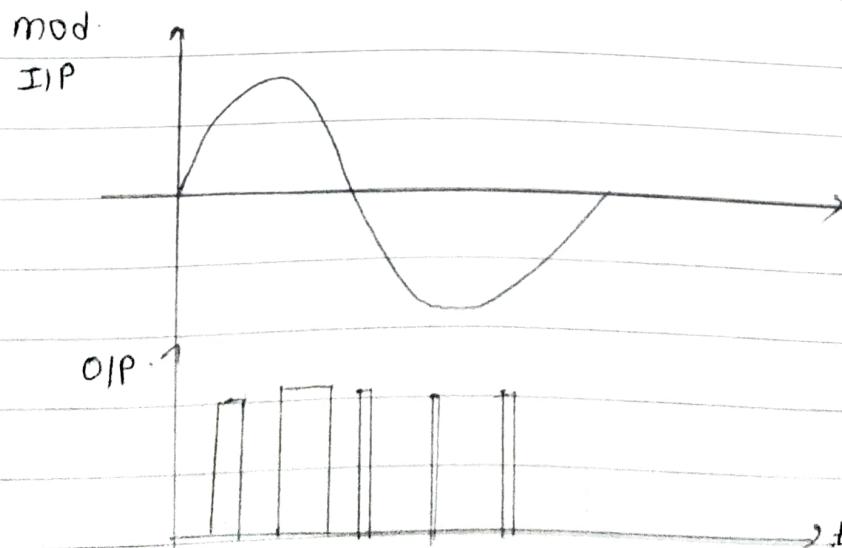

2) Pulse Position modulator:-

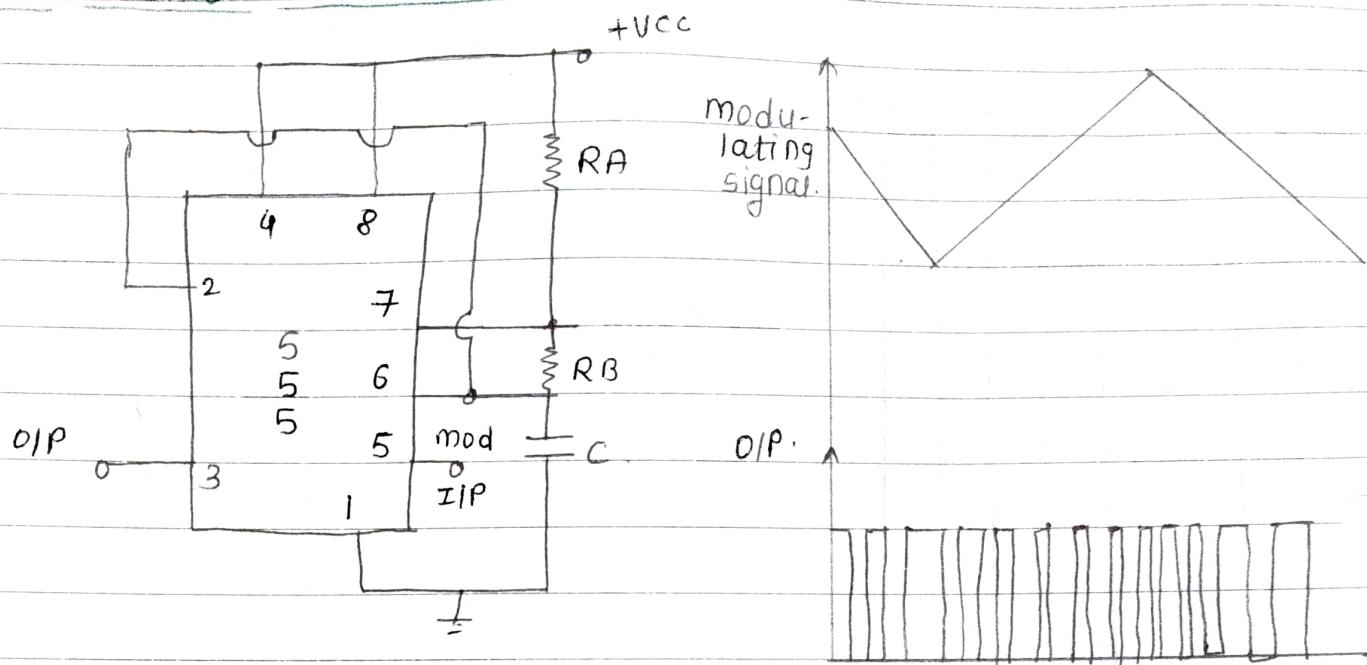

- PPM can be constructed by applying modulating signal to pins 5 of 555 connected for astable operation. The O/P pulse position varies with the modulating signal, since the threshold utg & hence the time delay is varied. Here triangular wave is applied as modulating signal. [$RA = 3.9\text{ k}\Omega$, $RB = 3\text{ k}\Omega$, $C = 0.01\text{ \mu F}$.]

$$V_{CC} = 5\text{ V}$$

3) Schmitt Trigger:-

