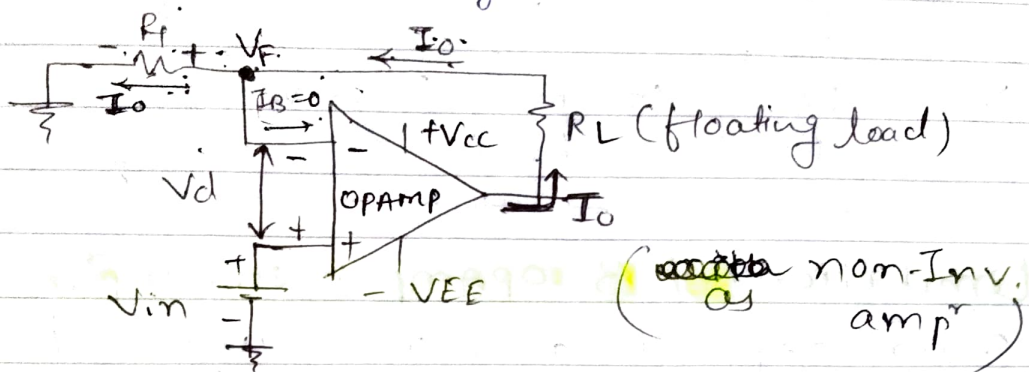


→ Voltage to current (V to I) converter with floating load

- > Here load is called floating load because it is not connected to ground.



- > I/p v/g is applied to non-inv. terminal of OPAMP. R_L is connected in place of f/b resistor R_f .
- > As the f/b v/g across R_f is proportional to the o/p c/n I_o & appears in series with i/p v/g. Therefore it is called as c/n series -ve f/b amp.

- > By apply KVL to i/p loop,

$$V_{in} = V_d + V_f$$

But as the gain of OPAMP is very large we can neglect V_d i.e. $V_d \approx 0$

$$\therefore V_{in} = V_f$$


$$= R_f \times I_o \quad \text{--- becoz } I_B \approx 0 \therefore R_f = \infty \text{ or high}$$

$$\therefore I_o = \frac{V_{in}}{R_f}$$

- > Thus it shows that i/p v/g is converted into proportional o/p c/n $I_o = V_{in}/R_f$, if R_f is a precision resistor then we can adjust o/p c/n.

→ Appⁿ → low v/g dc & ac voltmeter, LED & zener diode Tester.

[f/b → feedback]

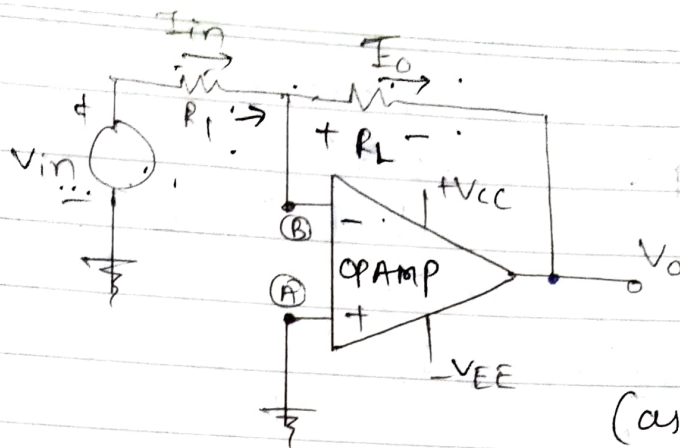

(as Inverting amp)

- > Here we are applying i/p vlg at inv. terminal.
As due to virtual ground concept c/n flowing in to the inverting terminal is zero.


$$\therefore I_{in} = I_o$$

But $I_{in} = V_{in}/R_1$... 'B' is at virtual gnd.

Thus c/n flowing through the load is proportional to i/p vlg V_{in} . $\therefore I_o = V_{in}/R_1$

- **Appⁿ** → As a relay driver, LED driver, DC voltmeter, Zener diode testing.

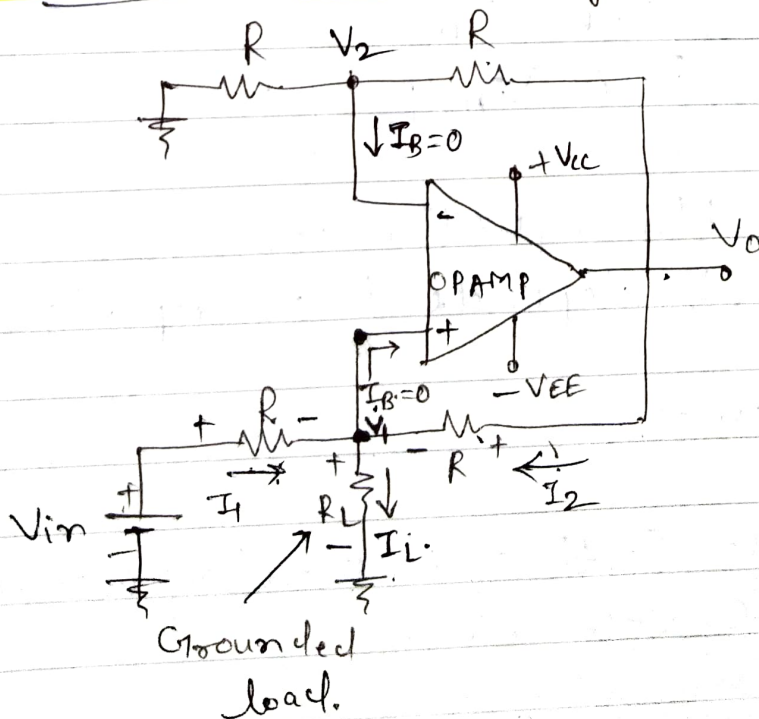→ **V to I Converter with grounded load.**



Applying KCL at node V_1 ,

$$I_B + I_L = I_1 + I_2$$

$$\text{but } I_B = 0$$

$$\therefore I_L = I_1 + I_2 \rightarrow (1)$$

$$\& I_1 = \frac{V_{in} - V_1}{R} \quad \& I_2 = \frac{V_o - V_1}{R}$$

substituting these values in eqⁿ (1).

$$I_L = \frac{V_{in} - V_1}{R} + \frac{V_o - V_1}{R}$$

$$\therefore I_L R = V_{in} + V_o - 2V_1$$

$$\therefore V_1 = \frac{V_{in} + V_o - I_L R}{2} \rightarrow (2)$$

As the OPAMP is in non-Inverting mode,

$$\text{Gain } A_{VF} = 1 + \frac{R}{R} = 2$$

$$\& V_o = A_{VF} \times V_1 = 2V_1$$

Substituting V_1 from eqⁿ (2),

$$V_o = V_{in} + V_o - I_L R$$

$$\therefore I_L R = V_{in}$$


$$\therefore \boxed{I_L = V_{in}/R}$$

Thus from this equation it is clear that load c/n is dependent on i/p v/g & resistor R .

> A_{VF} is same.

Zener diode testing, As a relay driver, LED driver, DC voltmeter.

Current to voltage converter (I to V)

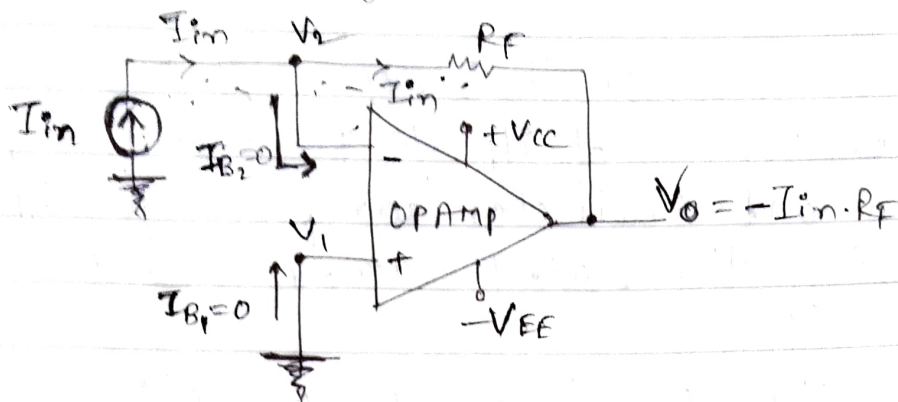

> As per the concept of virtual short.

$$V_1 \approx V_2$$

& as i/p impedance is very high $\therefore I_{B1} = I_{B2} \approx 0$.

Gain of inverting amp,

$$A_{VF} = \frac{-R_F}{R_i} = \frac{V_o}{V_{in}}$$

$$\therefore V_o = -\frac{R_F}{R_i} V_{in} \rightarrow (1)$$

> As $V_1 \approx V_2$ and $V_1 = 0$ as non-Inv. terminal is connected to ground $\therefore V_2 = 0$.

Thus inverting terminal is also at ground potential & entire i/p vlg appears across R_i .

$$\therefore I_{in} \approx V_{in} / R_i$$

$$\therefore V_{in} = I_{in} \cdot R_i$$

put this value in equation (1).

$$\therefore V_o = -\frac{R_F}{R_i} I_{in} \cdot R_i$$

$$\therefore \boxed{V_o = -R_F \cdot I_{in}}$$

which indicates that o/p vlg is proportional to i/p current I_{in} .

> Appⁿ \rightarrow light intensity meter, D/A converter.