

- A fluctuating d.c voltage may result in an erratic operation of electronic devices & circuits.  
e.g. it may cause a frequency shift in an oscillator, change of calibration in instruments, distortion in the o/p of power amplifiers etc.
- In order to avoid fluctuations, a voltage regulator ckt is used.
- A voltage regulator is connected between the filter & the load.
- Its function is to maintain a constant o/p d.c v.tg inspite of a.c i/p v.tg fluctuations or changes in load resistance values.

### \* Voltage Regulation -

An ideal voltage regulator will maintain a constant dc output voltage regardless of changes in either its input voltage or its load current demand.

e.g. consider  $\pm 5\text{Vdc}$  regulator shown in next fig.

- A change in the regulator i/p voltage shown as  $\Delta V_s$  (in fig a) would not appear at the regulator o/p.
- It may be carefully noted that  $\Delta V_s$  could be either a change in steady-state (dc) value of  $V_s$  or could be some ripple voltage.
- In either case, the change in  $V_L$  for the ideal regulator would be 0V.
- We have assumed that the value of i/p v.tg to the v.tg regulator ( $V_s$ ) does not decrease below the value required to maintain the operation of v.tg regulator.

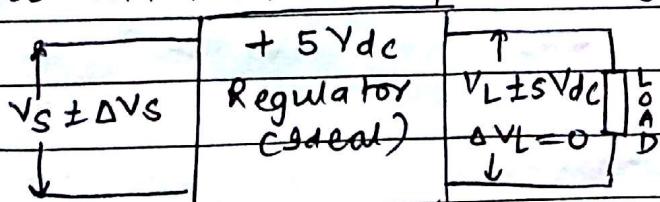


fig a)

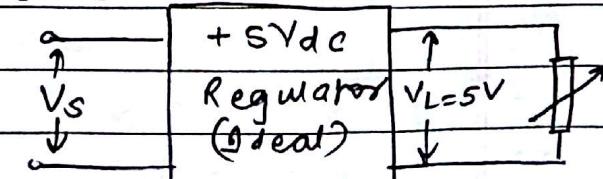


fig b)

- As a thumb rule, a regulator cannot have 5Vdc o/p if the i/p is less than 5Vdc.
- Fig a) & b) shows how an ideal voltage regulator would respond to a change in load current demand.
- The ideal voltage regulator maintains a constant o/p vtq (ie  $\Delta V_L = 0$ ) despite the changes in load current demand.
- Accordingly, we have two ways of specifying the quality of regulation for a voltage regulator.
  - (1) Line Regulation    (2) Load Regulation.

### (1) Line Regulation -

In actual practice, a change in i/p vtq to a voltage regulator will cause a change in its o/p or load voltage.

- The line regulation rating of a voltage regulator indicates the change in o/p vtq that will occur per unit change in the i/p voltage.
- The line regulation of a voltage regulator is given by,

$$\text{Line Regulation} = \frac{\Delta V_L}{\Delta V_S}$$

where  $\Delta V_L$  = the change in o/p vtq usually in mV or

$\Delta V_S$  = the change in i/p vtq in Volts

The line Regulation is expressed as  $(V/V)$  or  $(mV/V)$

## ② Load Regulation -

In practice, the voltage regulator will also experience a slight change in o/p vtg when there is a change in load current demand.

- The load regulation indicates the change in o/p vtg that will occur per unit change in load current.

- Mathematically, the load regulation may be expressed as

$$\text{Load Regulation} = \frac{V_{NL} - V_{FL}}{\Delta I_L}$$

where  $V_{NL}$  = no load o/p vtg

$V_{FL}$  = full load o/p vtg

$\Delta I_L$  = the change in load current demand

- The load regulation of a voltage regulator is expressed in terms of  $\mu\text{V}/\mu\text{A}$

- Line/load regulation values should be lower for the better quality of regulation.


- Voltage Regulation is expressed as the ability of the regulator to maintain a constant o/p vtg inspite of a.c. i/p vtg fluctuations & changes in load resistance.

$$\% \text{ regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100$$

where  $V_{NL}$  = no load vtg

$V_{FL}$  = Full load vtg

## \* Zener Diode shunt Regulator -

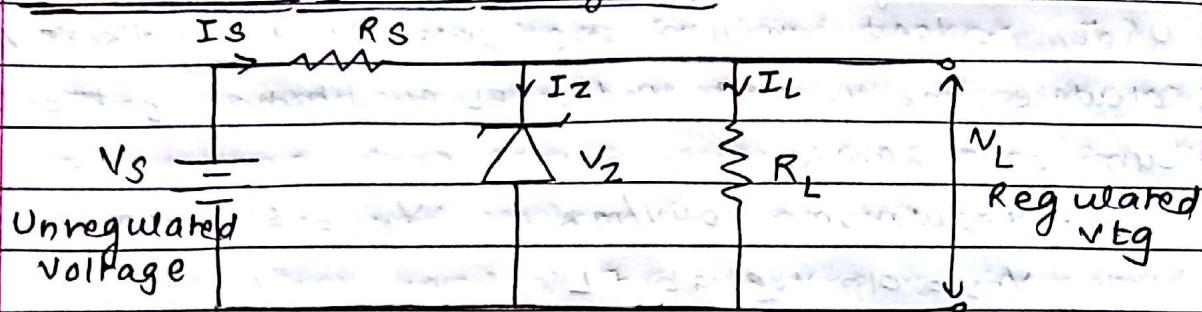

- Above fig shows a circuit of zener diode shunt regulator.

- since the zener is connected in parallel (or shunt) with the load, therefore the circuit is known as shunt Regulator.

- A resistance ( $R_s$ ) is connected in series with zener to limit current in the circuit.

- Therefore the resistance  $R_s$  is also known as series current limiting resistor.

- The o/p vbg ( $V_L$ ) is taken across the load resistance ( $R_L$ ).

- For proper operation, the o/p vbg ( $V_s$ ) must be greater than the zener voltage ( $V_z$ ).

- This ensures that zener operates in the reverse breakdown region.

- The i/p current (i.e current through the limiting resistor) is given by the relation,

$$I_s = \frac{V_s - V_z}{R_s}$$

where  $V_s$  = d.c i/p vbg to the regulator ckt

$V_z$  = zener voltage

- Ideal zener diode acts as a constant voltage source of voltage ( $V_z$ ).

- A practical zener diode has a finite value of resistance called zener resistance ( $r_z$ ).

- Because of the zener resistance, there is a voltage drop across it which is equal to  $I_z \cdot r_z$ .
- Therefore the voltage across the terminals of the zener diode (which is equal to load voltage),  

$$V_L = V_z + I_z \cdot r_z$$
- If zener resistance is negligible, then load voltage  

$$V_L = V_z$$

& the current through the load resistance is given by the relation,

$$I_L = \frac{V_L}{R_L}$$


- Input current is the sum of zener current & load current i.e.  $I_S = I_z + I_L$  or  $I_z = I_S - I_L$

### \* Working of Zener diode shunt Regulator :-

It may be explained under the two levels namely regulation with varying input voltage & regulation with varying load resistance.
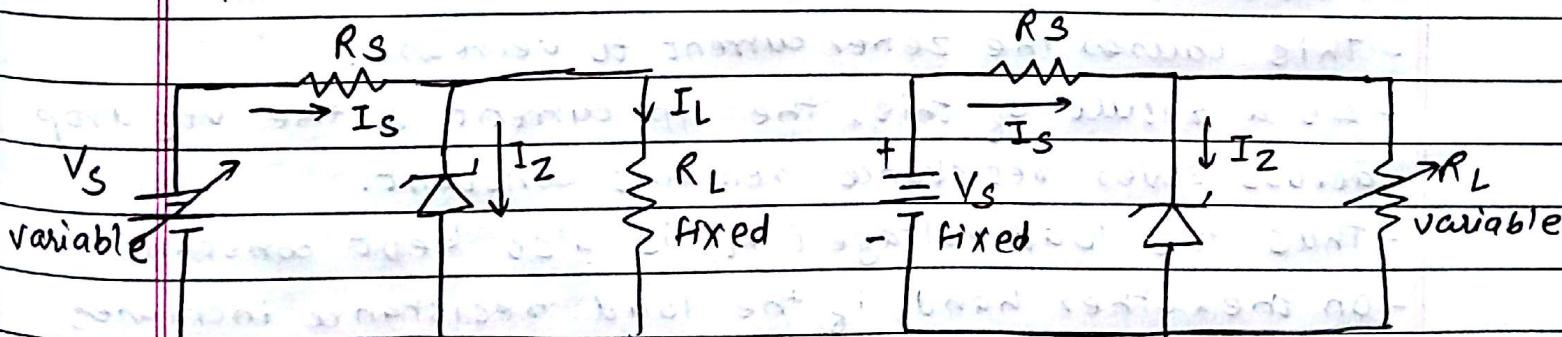
#### ① Regulation with varying input voltage :-

Consider the regulator circuit as shown in fig a). Here the load resistor ( $R_L$ ) is kept fixed & the input voltage ( $V_s$ ) series within the limits.



a) varying input voltage

b) varying load resistance

- As the input voltage increases, the input current ( $I_S$ ) also

increases. This increases the current through zener diode, without affecting the load current ( $I_L$ ).

- The increase in input current will also increase the voltage drop across series resistance ( $R_s$ ), thereby keeping the load voltage ( $V_L$ ) as constant.
- On the other hand, if the i/p vtg is decreased, the i/p current also decreases.
- As a result of this the current through zener will also decrease.
- Consequently, the voltage drop across series resistance will be reduced.
- Thus the load voltage ( $V_L$ ) & load current ( $I_L$ ) remains constant.

## 2. Regulation with varying load Resistance -

- consider the regulator ckt in fig b)
- Here the i/p vtg ( $V_s$ ) is kept fixed & the load resistance ( $R_L$ ) varies.
- The variation of load resistance changes the current ( $I_L$ ) through it, thereby changing voltage ( $V_L$ ) across it.
- When the load resistance decreases, the load current increases.
- This causes the zener current to decrease.
- As a result of this, the i/p current & the vtg drop across series resistance remains constant.
- Thus the load voltage ( $V_L$ ) is also kept constant.
- On the other hand, if the load resistance increases the load current decreases.
- As a result of this, the zener current increases.
- This again keeps the value of i/p current & vtg


drop across series resistance is constant.

- Thus the load voltage remains constant.
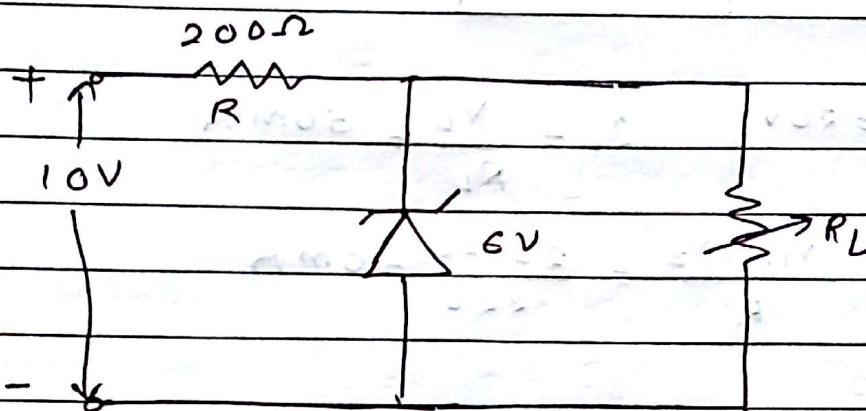
### Numericals

(Ex1)

For the given circuit, find  $I$ ,  $I_Z$ ,  $I_L$  for  $R_L = 300\Omega$  &  $R_L = 100\Omega$



Q1 (a) For  $R_L = 100\Omega$

$$I_L = \frac{V_Z}{R_L} = \frac{6}{100} = 0.06A \text{ or } 60mA$$

$$I = \frac{V_{in} - V_Z}{R} = \frac{10 - 6}{200} = 20mA$$

$$I_Z = I - I_L = 20 - 60mA = -40mA$$


(b) for  $R_L = 300\Omega$

$$I_L = \frac{V_Z}{R_L} = \frac{6}{300} = 20mA$$

$$I = \frac{V_{in} - V_Z}{R} = \frac{10 - 6}{200} = 20mA$$

$$I_Z = I - I_L = 0mA$$

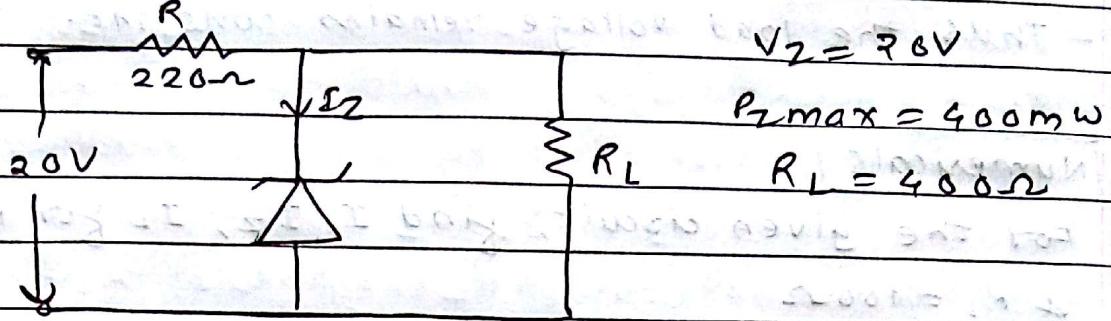Ex 2) Determine  $V_L$ ,  $I_L$ ,  $I_Z$  &  $I_R$  for N/W shown.



Soln

$$V_L = V_z = 20\text{V}, \quad I_L = \frac{V_L}{R_L} = \frac{20}{400} = 50\text{mA}$$

$$I_R = \frac{V_{in} - V_z}{R} = \frac{20 - 20}{220} = 0\text{mA}$$

- If  $R_L \uparrow$  se,  $I_L \downarrow$  se. As a result of this  $I_Z \uparrow$  se. This again keeps the value of i/p v<sub>lg</sub> & v<sub>lg</sub> clomp across series resistance as constant. Thus the load v<sub>lg</sub> 'V<sub>L</sub>' remains constant.

→ Optimum value of cln limiting resistor

- When i/p v<sub>lg</sub> is minimum & load cln is maximum, sufficient cln must be supplied to keep zener diode within its breakdown region.
- When i/p v<sub>lg</sub> is maximum & load cln is minimum the zener cln must not use the maximum rated value.

$$R_s(\text{min}) = \frac{V_s(\text{max}) - V_z}{I_z(\text{max}) + I_L(\text{min})}$$

$$R_s(\text{max}) = \frac{V_s(\text{min}) - V_z}{I_z(\text{min}) + I_L(\text{max})}$$

$R_s$  should be  $R_s(\text{min}) < R_s < R_s(\text{max})$

→ Advantages

- Very simple ckt
- low cost & requires only 2 or 3 components.

→ Disadvantages

- Poor efficiency for heavy load.
- Dc o/p v<sub>lg</sub> slightly changes due to Zener Resistance.
- O/p v<sub>lg</sub> is not adjustable because  $V_o = V_z$ .

→ Application

- Used in emitter follower regulator.
- Used with small load cln range over which the o/p dc v<sub>lg</sub> remains constant.